



MADE EASY
Leading Institute for ESE, GATE & PSUs

Detailed Solutions

**ESE-2026
Mains Test Series**

**Electrical Engineering
Test No : 11**

Section-A

Q.1 (a) Solution:

Given, kVA rating of transformers,

$$S = 10 \text{ kVA}$$

(i)

$$P_{\text{out}} = 10 \times 0.8 = 8 \text{ kW}$$

$$P_{\text{cu, fL}} = 60 \times (2)^2 = 240 \text{ W}$$

$$P_{\text{core}} = 100 \text{ W}$$

$$\% \eta = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{losses}}} \times 100$$

$$\% \eta = \frac{8000}{8000 + 240 + 100} \times 100 = 95.92\%$$

(ii) Per unit rating at which the transformer efficiency is maximum

$$x = \sqrt{\frac{P_{\text{core}}}{P_{\text{cu, fL}}}} = \sqrt{\frac{100}{240}} = 0.6455 \text{ pu}$$

$$\eta_{\text{max}} = \frac{S \times x \times \text{p.f.}}{S \times x \times \text{p.f.} + 2P_{\text{core}}} \times 100$$

$$= \frac{10 \times 10^3 \times 0.6455 \times 0.8}{10 \times 10^3 \times 0.6455 \times 0.8 + 2 \times 100} \times 100 = 96.27\%$$

(iii) Total power output in 24 hrs,

$$E_{\text{out}} = 0 + (10 \times 0.7 \times 0.8 \times 10) + (10 \times 0.9 \times 0.9 \times 8)$$

$$= 120.8 \text{ kWhr}$$

$$E_{\text{core}} = 100 \times 24 = 2.4 \text{ kWhr}$$

$$E_{\text{cu}} = 240 \times (0.7)^2 \times 10 + 240 \times (0.9)^2 \times 8$$

$$= 2.7312 \text{ kWhr}$$

$$\% \eta_{\text{all day}} = \frac{120.8}{120.8 + 2.4 + 2.7312} \times 100 = 95.93\%$$

Q.1 (b) Solution:

Inductance per phase, $L = \frac{X_L}{2\pi f} = \frac{5}{2\pi \times 50} = 0.0159 \text{ H}$

Capacitance per phase, $C = 0.01 \mu\text{F} = 10^{-8} \text{ F}$

(i) Maximum value of recovery voltage (phase to neutral)

$$E_{\text{max}} = \sqrt{2} \times \frac{11}{\sqrt{3}} = 8.98 \text{ kV}$$

$$\therefore \text{Peak re-striking voltage} = 2 E_{\text{max}}$$

$$= 2 \times 8.98$$

$$= 17.96 \text{ kV}$$

(ii) Frequency of oscillations is

$$f_n = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.0159 \times 10^{-6}}}$$

$$= 12,628 \text{ Hz}$$

(iii) Peak re-striking voltage occurs at a time t given by:

$$t = \frac{1}{2f_n} = \pi\sqrt{LC}$$

$$= \pi\sqrt{0.0159 \times 10^{-8}}$$

$$= 39.6 \times 10^{-5} \text{ sec}$$

$$= 39.6 \mu\text{sec}$$

\therefore Average rate of rise of re-striking voltage


$$= \frac{\text{Peak re-striking voltage}}{\text{Time upto first peak}} = \frac{17.96 \text{ kV}}{39.6 \mu\text{sec}}$$

$$= 453 \times 10^3 \text{ kV/sec}$$

Q.1 (c) Solution:

There will be no freewheeling action if $\alpha \leq 30^\circ$.

Source current waveform is shown below:

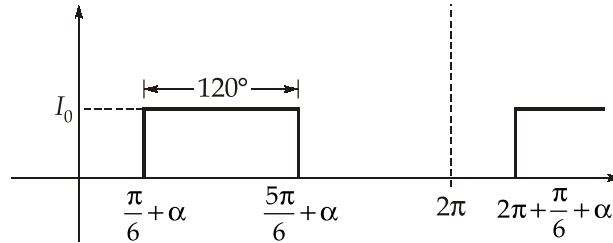

To find displacement factor and distortion factor, we should know Fourier coefficients for $n = 1$.

Fourier series expression is

$$f(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} [a_n \cos(n\alpha x) + b_n \sin(n\alpha x)]$$

Trigonometric expression is $f(t) = \frac{a_0}{2} + \sqrt{a_n^2 + b_n^2} \sum_{n=1}^{\infty} \sin(n\alpha x + \theta)$

Where $\theta = \tan^{-1} \frac{a_n}{b_n}$

If $n = 1$,

$$a_1 = \frac{1}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} I_s \cos \omega t d\alpha x = -\frac{\sqrt{3}}{\pi} I_a \sin \alpha$$

$$a_1 = \frac{1}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} I_s \sin \omega x d\alpha x = -\frac{\sqrt{3}}{\pi} I_a \cos \alpha$$

Displacement angle, $\theta = \tan^{-1} \frac{a_1}{b_1} = -\alpha$

Displacement factor, DPF = $\cos \alpha$

RMS value of fundamental source current,

$$I_{s1} = \frac{\sqrt{a_n^2 + b_n^2}}{\sqrt{2}} = \frac{I_0}{\pi} \sqrt{\frac{3}{2}}$$

From the waveform, RMS value of source current,

$$I_s = \frac{I_s}{\sqrt{3}}$$

Distortion factor,
$$DF = \frac{I_{s1}}{I_s} = \frac{3}{\pi\sqrt{2}}$$

Power factor,
$$DF \times DPF = \frac{3}{\pi\sqrt{2}} \cos \alpha = \frac{3}{\pi\sqrt{2}} \cos 15^\circ = 0.6522$$

Q.1 (d) Solution:

$$\begin{aligned} \text{(i)} \quad \bar{A}\bar{C} + ABC + A\bar{C} &= \bar{C}(\bar{A} + A) + ABC \\ &= ABC + \bar{C} \\ &= (\bar{C} + C)(\bar{C} + AB) \\ &= \bar{C} + AB \end{aligned}$$

$$\begin{aligned} \text{(ii)} \quad (\bar{x}\bar{y} + z) + z + xy + wz &= \bar{x}\bar{y} \cdot \bar{z} + z + xy + wz \\ &= (x + y)\bar{z} + z + xy \\ &= (z + \bar{z})[z + (x + y)] + xy \\ &= x + y + z + xy \\ &= x + y + z \end{aligned}$$

$$\begin{aligned} \text{(iii)} \quad \bar{A}B(\bar{D} + \bar{C}D) + B(A + \bar{A}CD) &= \bar{A}B(\bar{D} + D)(\bar{D} + \bar{C}) + B(A + \bar{A})(A + CD) \\ &= \bar{A}B(\bar{D} + \bar{C}) + B(A + CD) \\ &= B[\bar{A}\bar{D} + \bar{A}\bar{C} + A + CD] \\ &= B[(A + \bar{A})(A + \bar{D}) + \bar{A}\bar{C} + CD] \\ &= B[A + \bar{D} + \bar{A}\bar{C} + CD] \\ &= B[(A + \bar{A})(A + \bar{C}) + (\bar{D} + D)(\bar{D} + C)] \\ &= B[A + \bar{C} + \bar{D} + C] \\ &= B[A + \bar{D} + 1] \\ &= B \end{aligned}$$

$$\begin{aligned} \text{(iv)} \quad (\bar{A} + C)(\bar{A} + \bar{C})(A + B + \bar{C}D) &= (\bar{A} + \bar{A}\bar{C} + \bar{A}C + C\bar{C})(A + B + \bar{C}D) \\ &= (\bar{A} + \bar{A}\bar{C})(A + B + \bar{C}D) \\ &= \bar{A}(A + B + \bar{C}D) \\ &= \bar{A}(B + \bar{C}D) \end{aligned}$$

$$\begin{aligned} \text{(v)} \quad AB\bar{C}D + \bar{A}BD + ABCD &= ABD + \bar{A}BD \\ &= BD \end{aligned}$$

$$\begin{aligned} \text{(vi)} \quad (\bar{a} + \bar{c})(a + \bar{b} + \bar{c}) &= a\bar{a} + \bar{a}(\bar{b} + \bar{c}) + \bar{c}a + \bar{c}(\bar{b} + \bar{c}) \\ &= \bar{a}\bar{b} + \bar{a}\bar{c} + \bar{c}a + \bar{c}\bar{b} + \bar{c} \\ &= \bar{a}\bar{b} + \bar{a}\bar{c} + \bar{c} + \bar{c}\bar{b} \\ &= \bar{a}\bar{b} + \bar{c} + \bar{c}\bar{b} \\ &= \bar{a}\bar{b} + \bar{c} \end{aligned}$$

Q.1 (e) Solution:

The open loop transfer function is,

$$\begin{aligned} G(s) &= \left(K_p + \frac{K_I}{s} \right) \frac{25}{s^2 + 10s + 25} \\ G(s) &= \frac{(K_p s + K_I)25}{s(s^2 + 10s + 25)} \end{aligned}$$

The system is 'type-1' system, so the error constant is velocity error constant.

$$\begin{aligned} \therefore K_V &= \lim_{s \rightarrow 0} s \cdot G(s) \\ 100 &= \lim_{s \rightarrow 0} s \cdot \frac{(K_p s + K_I)25}{s(s^2 + 10s + 25)} \end{aligned}$$

$$\therefore K_I = 100$$

The characteristic equation,

$$\begin{aligned} 1 + G(s)H(s) &= 0 \\ 1 + \left(\frac{K_p s + 100}{s} \right) \left(\frac{25}{s^2 + 10s + 25} \right) &= 0 \end{aligned}$$

$$s^3 + 10s^2 + 25s + 25K_p s + 2500 = 0$$

$$s^3 + 10s^2 + (25K_p + 25)s + 2500 = 0$$

By using Routh-Hurwitz table,

$$\begin{array}{l|ll} s^3 & 1 & (25 + 25K_p) \\ s^2 & 10 & 2500 \\ s^1 & 25 + 25K_p - 250 & \\ s^0 & 2500 & \end{array}$$

Since the system is stable.

So, $25 + 25K_p - 250 \geq 0$

$\therefore K_p \geq \frac{225}{25}$

$\therefore K_p \geq 9$

The critical value of $K_p = 9$, at which the system is marginally stable.

Q.2 (a) (i) Solution:

The expression can be generated using single op-amp with summing integrator circuit. The output of summing integrator with three inputs is given by,

$$V_{out} = -\int_0^t \left(\frac{1}{R_1 C_F} V_{in1} + \frac{1}{R_2 C_F} V_{in2} + \frac{1}{R_3 C_F} V_{in3} \right) dt$$

Comparing this with the given expression we get,

$$\frac{1}{R_1 C_F} = 1$$

$$\frac{1}{R_2 C_F} = 2$$

$$\frac{1}{R_3 C_F} = 5$$


Let us choose C_F as $10 \mu\text{F}$,

Then,

$$R_1 = 100 \text{ k}\Omega,$$

$$R_2 = 50 \text{ k}\Omega,$$

$$R_3 = 20 \text{ k}\Omega$$

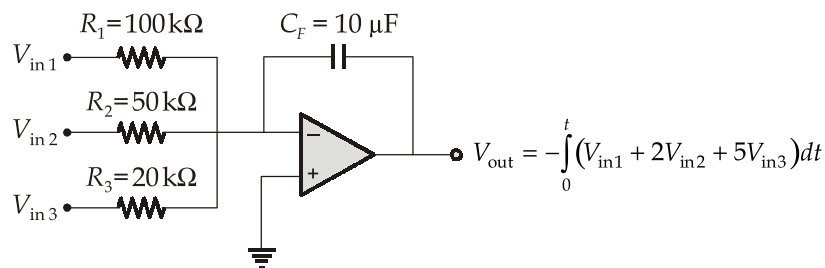

Q.2 (a) (ii) Solution:

The gain of an instrument amplifier is given by,

$$A = \frac{V_{out}}{V_{in2} - V_{in1}} = \left(1 + \frac{2R_F}{R_G} \right) \left(\frac{R_2}{R_1} \right)$$

In the circuit given, we have,

$$R_1 = 200 \Omega,$$

$$R_2 = 100 \Omega,$$

and

$$R_F = 100 \text{ k}\Omega$$

R_G is the series combination of 100Ω and potentiometer of $100 \text{ k}\Omega$.

Let potentiometer resistance is 0Ω at start,

Hence,
$$R_G = 100 + 0 = 100 \Omega$$

Gain,
$$A = \left(1 + \frac{2 \times 100 \times 10^3}{100}\right) \left(\frac{100}{200}\right) = 1000.5$$

When potentiometer resistance is at its maximum value, then

$$R_G = 100 + (100 \times 10^3) = 100.1 \text{ k}\Omega$$

Therefore,
$$\text{Gain, } A = \left(1 + \frac{2 \times 100 \times 10^3}{100.1 \times 10^3}\right) \left(\frac{100}{200}\right) = 1.5$$

\therefore For all practical purpose, the gain can be varied from 1.5 to 1000.5

Q.2 (b) Solution:

(i) Given: Closed loop transfer function,

$$T(s) = \frac{C(s)}{R(s)} = \frac{ks + a}{s^2 + bs + a}$$

We know that,
$$T(s) = \frac{C(s)}{R(s)} = \frac{G(s)}{1 + G(s)}$$

$$[1 + G(s)] T(s) = G(s)$$

$$G(s) = \frac{T(s)}{1 - T(s)}$$

$$\begin{aligned} G(s) &= \frac{(ks + a) / (s^2 + bs + a)}{1 - \frac{(ks + a)}{s^2 + bs + a}} \\ &= \frac{ks + a}{s^2 + bs + a - ks - a} = \frac{ks + a}{s^2 + (b - k)s} = \frac{ks + a}{s(s + b - k)} \end{aligned}$$

\therefore The open loop transfer function,

$$G(s) = \frac{ks + a}{s(s + b - k)}$$

We know that, for ramp input,

$$\text{Steady state error, } e_{ss} = \frac{1}{k_v} \quad (\text{where, } k_v = \text{velocity error coefficient})$$

$$\text{where, } k_v = \lim_{s \rightarrow 0} s \cdot G(s) = \lim_{s \rightarrow 0} s \cdot \frac{ks + a}{s(s + b - k)}$$

$$\therefore k_v = \frac{a}{b - k}$$

$$\text{Steady state error, } e_{ss} = \frac{1}{k_v} = \frac{1}{\frac{a}{b - k}} = \frac{b - k}{a}$$

$$\therefore e_{ss} = \frac{b - k}{a}$$

$$\text{(ii) Given: steady state error, } e_{ss} = 15\% = \frac{15}{100}$$

$$\therefore e_{ss} = \frac{b - k}{a} = \frac{15}{100}$$

$$20(b - k) = 3a$$

$$b - k = \frac{3}{20}a$$

$$\therefore k = b - \frac{3}{20}a$$

Q.2 (c) Solution:

Checking for discontinuity of inductor current, if $L < L_{\min}$ then converter is working in discontinuous mode.

Now, boundary conditions

$$L \frac{\partial I_L}{\partial t} = V_0 \quad (\text{Force charging time i.e. S is OFF})$$

At boundary $L = L_{\min}$

$$L \frac{\Delta I_L}{(1 - D)T_S} = V_0 \quad \dots \text{(i)}$$

Now,

$$I_{\min} = 0 \text{ at boundary}$$

$$0 = \left(I_{L \text{ avg}} \right) - \frac{\Delta I_L}{2} \quad \dots \text{(ii)}$$

$$(I_{L,avg}) = I_0 + I_S = I_0 + \frac{D}{1-D} I_0$$

$$(I_{L,avg}) = \left(\frac{1}{1-D} \right) I_0 \quad \dots \text{(iii)}$$

From equation (ii) and (iii) we get

$$\left(\frac{1}{1-D} \right) I_0 = \frac{\Delta I_L}{2}$$

$$\Delta I_L = \left(\frac{2}{1-D} \right) I_0$$

Again from equation (i)

$$L_{\min} \frac{\Delta I_L}{(1-D)T_S} = I_0 R$$

$$L_{\min} \frac{2I_0}{(1-D)^2 T_S} = I_0 R$$


$$L_{\min} = \frac{(1-D)^2 R}{2f}$$

Now

$$L_{\min} = \frac{(1-0.4)^2 \times 5}{2 \times 100 \times 10^3} = 9 \mu\text{H}$$

Now as $L < L_{\min}$ So converter is in discontinuous mode. Now for discontinuous mode of Buck-Boost converter,
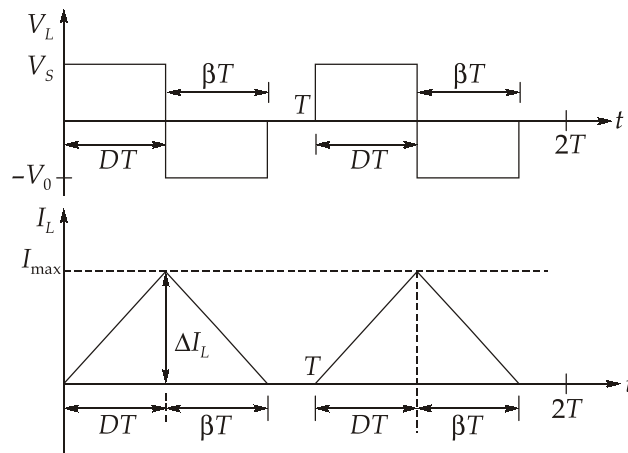
$$V_0 = \frac{D}{\beta} V_S \quad \dots \text{(iv)}$$



For discontinuous mode

$$(I_{L\text{avg}}) = \frac{1}{2} \times \Delta I_L \times (D + \beta) \quad \dots \text{(v)}$$

As average capacitor current is zero,

$$\begin{aligned} (I_{L\text{avg}}) &= I_S + I_0 = \left(\frac{D}{\beta} I_0 + I_0 \right) \\ &= \frac{I_0}{\beta} (D + \beta) \quad \dots \text{(vi)} \end{aligned}$$

From equation (v) and (vi)

$$\frac{1}{2} \times \Delta I_L \times (D + \beta) = \frac{I_0}{\beta} (D + \beta)$$

$$\frac{1}{2} \Delta I_L = \frac{I_0}{\beta}$$

$$\Delta I_L = \frac{2I_0}{\beta}$$

Again,

$$L \frac{di_L}{dt} = V_0$$

$$L \frac{\Delta I_L}{\beta T_S} = I_0 R$$

$$L \frac{2I_0 / \beta}{\beta T_S} = I_0 R$$

$$\frac{2L}{\beta^2 T_S} = R$$

$$\beta^2 = \frac{2Lf_s}{R}$$

$$\beta = \sqrt{\frac{2Lf_s}{R}} = \sqrt{\frac{2 \times 6 \times 10^{-6} \times 100 \times 10^3}{5}} = 0.49$$

Now from equation (iv),

$$V_0 = \frac{D}{\beta} V_S = \frac{0.4}{0.49} \times 24$$

(i) $V_0 = 19.6$ Volts

(ii) $I_0 = \frac{V_0}{R} = \frac{19.6}{5} \text{ V} = 3.91 \text{ Amp}$

(iii) Average inductor current $(I_{L \text{ avg}}) = I_S + I_0 = \frac{I_0(D+\beta)}{\beta}$

$$(I_{L \text{ avg}}) = \frac{3.91(0.4+0.49)}{0.49} = 7.11 \text{ Amp}$$

(iv) Average switch current, $S =$ Average source current

$$I_S = \frac{D}{\beta} I_0 = 3.19 \text{ Amp}$$

Q.3 (a) Solution:

Given that,

Message signal, $m(t) = \cos(2000\pi t) + 2\sin(2000\pi t)$

Carrier signal, $c(t) = 100\cos(2\pi f_c t); f_c = 100 \text{ kHz}$

(i) The standard time domain expression for the LSSB-AM signal can be given as,

$$s(t) = A_c m(t) \cos(2\pi f_c t) + A_c \hat{m}(t) \sin(2\pi f_c t)$$

$\hat{m}(t)$ is the Hilbert transform of the message signal $m(t)$.

$$\hat{m}(t) = \sin(2000\pi t) - 2\cos(2000\pi t)$$

So,

$$\begin{aligned} s(t) &= 100 [\cos(2000\pi t) + 2\sin(2000\pi t)] \cos(2\pi f_c t) \\ &\quad + 100 [\sin(2000\pi t) - 2\cos(2000\pi t)] \sin(2\pi f_c t) \\ &= 100 [\cos(2\pi f_c t) \cos(2000\pi t) + \sin(2\pi f_c t) \sin(2000\pi t)] \\ &\quad + 200 [\cos(2\pi f_c t) \sin(2000\pi t) - \sin(2\pi f_c t) \cos(2000\pi t)] \\ s(t) &= 100\cos[2\pi(f_c - 1000)t] - 200\sin[2\pi(f_c - 1000)t] \end{aligned}$$


(ii) By taking the Fourier transform of the above time domain expression of LSSB-AM signal $s(t)$, we get,

$$\begin{aligned} S(f) &= 50[\delta(f - f_c + 1000) + \delta(f + f_c - 1000)] \\ &\quad + j100[\delta(f - f_c + 1000) - \delta(f + f_c - 1000)] \\ &= (50 + j100) \delta(f - f_c + 1000) + (50 - j100) \delta(f + f_c - 1000) \end{aligned}$$

Hence, the magnitude spectrum of the signal can be given as,

$$\begin{aligned} |S(f)| &= \sqrt{(50)^2 + (100)^2} [\delta(f - f_c + 1000) + \delta(f + f_c - 1000)] \\ &= 50\sqrt{5} [\delta(f - f_c + 1000) + \delta(f + f_c - 1000)] \end{aligned}$$

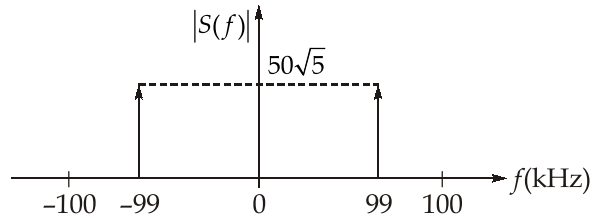The magnitude spectrum can be plotted, by taking $f_c = 100$ kHz, as follows



Q.3 (b) Solution:

Given, impulse response,
$$h[n] = \begin{cases} a^n; & n \geq 0 \\ 0; & n < 0 \end{cases}$$

Also we can write,

$$h[n] = a^n u[n]$$

$$x[n] = \begin{cases} 1; & 0 \leq n \leq N - 1 \\ 0; & \text{otherwise} \end{cases}$$

Also we can write,

$$x[n] = u[n] - u[n - N]$$

by taking z-transform,

$$H(z) = \frac{1}{1 - az^{-1}}; \quad |z| > |a|$$

$$X(z) = \frac{1 - z^{-N}}{1 - z^{-1}}; \quad \text{All } z \text{ (by shifting property)}$$

Therefore,

$$Y(z) = X(z)H(z)$$

$$= \frac{1}{1 - az^{-1}} \cdot \frac{1 - z^{-N}}{1 - z^{-1}} = \frac{1 - z^{-N}}{(1 - z^{-1})(1 - az^{-1})}$$

$$= \frac{1}{(1 - z^{-1})(1 - az^{-1})} - \frac{z^{-N}}{(1 - z^{-1})(1 - az^{-1})}$$

The ROC is $|z| > |a|$. Consider

$$P(z) = \frac{1}{(1 - z^{-1})(1 - az^{-1})} = \frac{A}{1 - z^{-1}} + \frac{B}{1 - az^{-1}}$$

For,

$$A = \frac{1}{1 - az^{-1}} \Big|_{z^{-1}=1} = \frac{1}{1 - a}$$

$$B = \frac{1}{1 - z^{-1}} \Big|_{z^{-1}=\frac{1}{a}} = \frac{1}{1 - a^{-1}}$$

\therefore

$$P(z) = \frac{1}{1 - z^{-1}} + \frac{1}{1 - az^{-1}}$$

Therefore,
$$p(n) = \frac{1}{1-a}u[n] + \frac{1}{1-a^{-1}}a^n u[n]$$

Now, note that,

$$Y(z) = P(z)[1 - z^{-N}]$$

by taking inverse z-transform

$$y[n] = p(n) - p[n - N]$$

$$y[n] = \frac{1}{1-a}\{u[n] - u[n - N]\} + \frac{1}{1-a^{-1}}\{a^n u[n] - a^{n-N} u[n - N]\}$$

This may write as,

$$y[n] = \begin{cases} 0 & ; \quad n < 0 \\ \frac{(a^n - a^{-1})}{(1 - a^{-1})} & ; \quad 0 \leq n \leq N - 1 \\ \frac{a^n(1 - a^{-N})}{(1 - a^{-1})} & ; \quad n > N - 1 \end{cases}$$

Q.3 (c) Solution:

Given : $P(x_1) = 0.4$; $P(x_2) = 0.19$; $P(x_3) = 0.16$;
 $P(x_4) = 0.15$; $P(x_5) = 0.1$

(i) Shannon fano :

Symbol (x_i)	Probabilities $P(x_i)$	Stage-1	Stage-2	Stage-3	Codeword	Length (n_i)
x_1	0.4	0	0		00	2
x_2	0.19	0	1		01	2
x_3	0.16	1	0		10	2
x_4	0.15	1	1	0	110	3
x_5	0.1	1	1	1	111	3

Efficiency,
$$\eta = \frac{H(x)}{\bar{L}}$$

where, $H(x)$ = Entropy of source and

\bar{L} = Average codeword length

$$H(x) = \sum_{i=1}^5 P(x_i) \log_2 \frac{1}{P(x_i)} = - \sum_{i=1}^5 P(x_i) \log_2 P(x_i)$$

$$\begin{aligned} H(x) &= -[0.4 \log_2(0.4) + 0.19 \log_2(0.19) + 0.16 \log_2(0.16) + 0.15 \log_2(0.15) + 0.1 \log_2(0.1)] \\ &= 2.15 \text{ bits/symbol} \end{aligned}$$


$$\bar{L} = \sum_{i=1}^5 n_i P(x_i)$$

$$\bar{L} = 2 \times 0.4 + 2 \times 0.19 + 2 \times 0.16 + 3 \times 0.15 + 3 \times 0.1 = 2.25$$

Efficiency, $\eta = \frac{H(x)}{\bar{L}} = \frac{2.15}{2.25} = 0.95555$

$$\eta = 95.56\% \quad \dots(i)$$

(ii) Huffman code

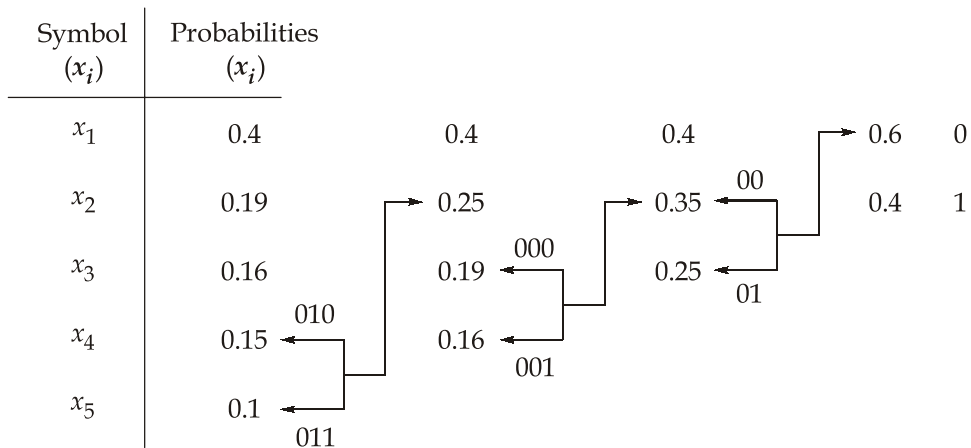

Symbol (x_i)	Probabilities (x_i)	Codeword	Length (n_i)
x_1	0.4	1	1
x_2	0.19	000	3
x_3	0.16	001	3
x_4	0.15	010	3
x_5	0.1	011	3

$$H(x) = 2.15 \text{ bits/symbol}$$

Average codeword length, $\bar{L} = \sum_{i=1}^5 n_i P(x_i)$

$$\bar{L} = 1 \times 0.4 + 3 \times 0.19 + 3 \times 0.16 + 3 \times 0.15 + 3 \times 0.1 = 2.2$$

Efficiency, $\eta = \frac{H(x)}{\bar{L}} = \frac{2.15}{2.2} = 0.9773$

$$\eta = 97.73\% \quad \dots(ii)$$

From equations (i) and (ii), we can say that the efficiency of Huffman coding is more than that of Shannon fano coding.

Q.4 (a) Solution:

Given, Window size, $M = 7$

$$H_d(e^{j\omega}) = \begin{cases} e^{-j3\omega} & , \frac{-3\pi}{4} \leq \omega \leq \frac{3\pi}{4} \\ 0 & , \frac{3\pi}{4} < |\omega| \leq \pi \end{cases}$$

The filter coefficients are given by

$$\begin{aligned} h_d(n) &= \frac{1}{2\pi} \int_{-\pi}^{\pi} H_d(e^{j\omega}) e^{j\omega n} d\omega \\ h_d(n) &= \frac{1}{2\pi} \int_{-3\pi/4}^{3\pi/4} e^{-j3\omega} e^{j\omega n} d\omega \\ &= \frac{1}{2\pi} \int_{-3\pi/4}^{3\pi/4} e^{+j(n-3)\omega} d\omega \\ &= \frac{1}{2\pi} \left[\frac{e^{j(n-3)\omega}}{j(n-3)} \right]_{-3\pi/4}^{3\pi/4} \\ &= \frac{1}{2\pi j(n-3)} \left[e^{j\frac{3\pi}{4}(n-3)} - e^{-j\frac{3\pi}{4}(n-3)} \right] \\ &= \frac{1}{\pi(n-3)} \sin\left(\frac{3\pi(n-3)}{4}\right); n \neq 3 \end{aligned}$$

Using L-Hospital's rule,

$$h_d(3) = \frac{\frac{3\pi}{4} \cos \frac{3\pi}{4}(n-3)}{\pi} = \frac{3}{4} = 0.75$$

The filter coefficients,

$$\begin{aligned} h_d(0) &= \frac{-1}{3\pi} \sin\left(\frac{-9\pi}{4}\right) = 0.075 \\ h_d(1) &= \frac{-1}{2\pi} \sin\left(\frac{-6\pi}{4}\right) = -0.159 \\ h_d(2) &= \frac{-1}{\pi} \sin\left(\frac{-3\pi}{4}\right) = 0.225 \\ h_d(4) &= \frac{1}{\pi} \sin\left(\frac{3\pi}{4}\right) = 0.225 \end{aligned}$$

$$h_d(5) = \frac{1}{2\pi} \sin\left(\frac{6\pi}{4}\right) = -0.159$$

$$h_d(6) = \frac{1}{3\pi} \sin\left(\frac{9\pi}{4}\right) = 0.075$$

The Hamming window function is,

$$W(n) = \begin{cases} 0.54 - 0.46 \cos \frac{2\pi n}{M-1} & ; 0 \leq n \leq M-1 \\ 0 & ; \text{otherwise} \end{cases}$$

For $M = 7$,

$$W(n) = 0.54 - 0.46 \cos\left(\frac{2\pi n}{6}\right); 0 \leq n \leq 6$$

$$W(0) = 0.08, W(1) = 0.31, W(2) = 0.77, W(3) = 1, W(4) = 0.77, W(5) = 0.31, W(6) = 0.08$$

The filter coefficients of the resultant filter,

$$h(n) = h_d(n)W(n); 0 \leq n \leq M-1$$

$$h(0) = h(6) = 0.075 \times 0.08 = 0.006$$

$$h(1) = h(5) = -0.159 \times 0.31 = -0.0493$$

$$h(2) = h(4) = 0.225 \times 0.77 = 0.1733$$

$$h(3) = 0.75 \times 1 = 0.75$$


The frequency response of designed filter,

$$H(e^{j\omega}) = \sum_{n=0}^6 h(n)e^{-j\omega n}$$

$$\begin{aligned} H(e^{j\omega}) &= h(0) + h(1)e^{-j\omega} + h(2)e^{-j2\omega} + h(3)e^{-j3\omega} \\ &\quad + h(4)e^{-j4\omega} + h(5)e^{-j5\omega} + h(6)e^{-j6\omega} \\ &= \left\{ (h(0)e^{j3\omega} + h(6)e^{-j3\omega}) + (h(1)e^{j2\omega} + h(5)e^{-j2\omega}) \right. \\ &\quad \left. + (h(2)e^{j\omega} + h(4)e^{-j\omega}) + h(3) \right\} e^{-j3\omega} \end{aligned}$$

$$H(e^{j\omega}) = e^{-j3\omega} [0.75 + 0.3466 \cos \omega - 0.0986 \cos 2\omega + 0.012 \cos 3\omega]$$

Q.4 (b) (i) Solution:

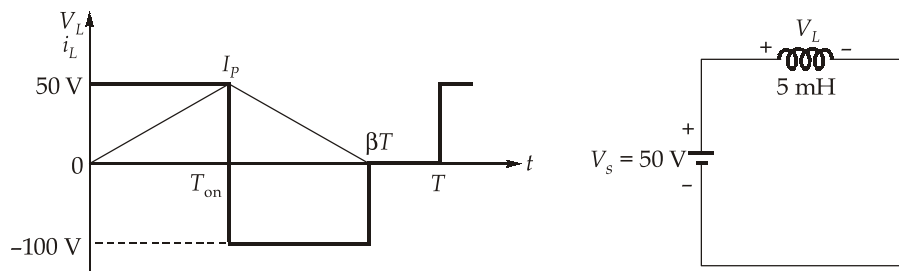

During T_{on} the circuit behaves as,

$$V_s = L \frac{di}{dt}$$

$$di = \frac{V_s}{L} dt$$

Integrating on both sides, we get

$$I_P = \frac{V_s}{L} T_{on}$$

$$T_{on} = \alpha T = \frac{\alpha}{f} = \frac{0.4}{5 \times 10^3} = 80 \times 10^{-6} \text{ s}$$

$$I_P = \frac{50}{5 \times 10^{-3}} \times (80 \times 10^{-6}) = 0.8 \text{ A}$$

During T_{off} , it is $T_{on} \leq t \leq \beta T$

Apply KVL in the circuit,

$$V_L = V_s - V_0$$

$$(V_L)_{avg} = 0$$

$$V_s T_{on} + (V_s - V_0) (\beta T - T_{on}) = 0$$


$$V_s \beta T = V_0 (\beta T - T_{on})$$

$$\frac{V_0}{V_s} = \frac{\beta}{\beta - \alpha}$$

$$\beta = 0.6$$

From the graph of I_L
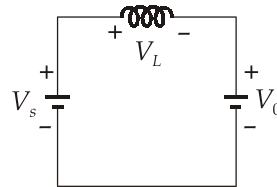
$$I_{L(avg)} = \frac{\frac{1}{2} \times b \times h}{T}$$



$$= \frac{\frac{1}{2} \times \beta T \times I_P}{T} = \frac{1}{2} \times 0.6 \times 0.8 = 0.24 \text{ A}$$

Q.4 (b) (ii) Solution:

Given, rotor induced emf at standstill = 700 V line

$$\text{Per phase, } E_2 = \frac{700}{\sqrt{3}} \text{ V}$$

$$\text{Slip, } s = \frac{1500 - 1200}{1500} = 0.2$$

Voltage drop in diode, $V_{Diode} = 0.7 \text{ V}$

Voltage drop in thyristor, $V_{th} = 1.5 \text{ V}$

DC voltage across the diode rectifier is

$$V_d = \frac{3\sqrt{6}E_2}{\pi} - 2 \times V_{Diode} = \frac{3\sqrt{2} \times 0.2 \times 700}{\pi} - 1.4$$

$$= 187.67 \text{ V}$$

With no voltage drop in inductor,

$$V_{dc} = V_d$$

$$\text{Inverter DC voltage} = - \left(\frac{3\sqrt{6} \times V_s}{\pi} \cos \alpha - V_{th} \times 2 \right)$$

DC voltage across the diode rectifier without voltage drop in inductor = Inverter DC voltage

$$-\frac{3\sqrt{2} \times 415}{\pi} \cos \gamma + 3 = \frac{3\sqrt{2} \times 0.2 \times 700}{\pi} - 1.4$$

$$\gamma = \cos^{-1} \left[\frac{-184.67 \times \pi}{3\sqrt{2} \times 415} \right] = 109.24^\circ$$

Firing advance angle of inverter = $180^\circ - \gamma$

$$180^\circ - 109.24^\circ = 70.76^\circ$$

Q.4 (c) Solution:

(i) Condition for the desired response

1. system must be controllable.
2. system must be observable.

The state transition matrices,

$$A = \begin{bmatrix} 2 & 3 \\ -1 & 4 \end{bmatrix}, B = \begin{bmatrix} 0 \\ 1 \end{bmatrix} \text{ and } C = [1 \quad 0]$$

For controllability

$$|Q_c| \neq 0$$

We know that,

$$Q_c = [B \quad AB]$$

$$AB = \begin{bmatrix} 2 & 3 \\ -1 & 4 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 3 \\ 4 \end{bmatrix}$$

$$|Q_c| = \begin{vmatrix} 0 & 3 \\ 1 & 4 \end{vmatrix}$$

\therefore $|Q| = 0 - 3 \neq 0$ so, system is controllable.

For observability, $|Q_0| \neq 0$

We know that, $Q_0 = \begin{bmatrix} C \\ CA \end{bmatrix}$

$$CA = [1 \ 0] \begin{bmatrix} 2 & 3 \\ -1 & 4 \end{bmatrix} = [2 \ 3]$$

$$|Q_0| = \begin{vmatrix} 1 & 0 \\ 2 & 3 \end{vmatrix}$$

\therefore $|Q_0| = 3 - 0 \neq 0$ so, the system is observable.

So, the desired response is possible.

(ii) Given: Settling time, $T_s = 0.5$ sec, damping frequency $\omega_d = 6$ rad/sec

We know that, $T_s = \frac{4}{\xi\omega_n} \Rightarrow \xi\omega_n = \frac{4}{0.5} = 8$

We know that, $\omega_d = \omega_n \sqrt{1 - \xi^2} = \sqrt{\omega_n^2 - (\omega_n \xi)^2}$
 $6 = \sqrt{\omega_n^2 - 8^2} \Rightarrow \omega_n = 10$ rad/sec

\therefore $\xi = \frac{8}{\omega_n} = \frac{8}{10} = 0.8$

The second order characteristic equation,

$$s^2 + 2\xi\omega_n s + \omega_n^2 = 0$$

$$s^2 + 16s + 100 = 0$$

...(i)

Let the observer gain matrix be,

$$K = \begin{bmatrix} K_1 \\ K_2 \end{bmatrix}$$

The desired response is given by,

$$\dot{x} = (A - KC)x + Bu$$

Characteristic equation,

$$q(s) = |sI - (A - KC)| = 0$$

$$(A - KC) = \begin{bmatrix} 2 & 3 \\ -1 & 4 \end{bmatrix} - \begin{bmatrix} K_1 \\ K_2 \end{bmatrix} \begin{bmatrix} 1 & 0 \end{bmatrix}$$

$$(A - KC) = \begin{bmatrix} 2 & 3 \\ -1 & 4 \end{bmatrix} - \begin{bmatrix} K_1 & 0 \\ K_2 & 0 \end{bmatrix} = \begin{bmatrix} 2 - K_1 & 3 \\ -1 - K_2 & 4 \end{bmatrix}$$

$$\begin{aligned}
 [sI - (A - KC)] &= \begin{bmatrix} s & 0 \\ 0 & s \end{bmatrix} - \begin{bmatrix} 2 - K_1 & 3 \\ -1 - K_2 & 4 \end{bmatrix} \\
 &= \begin{bmatrix} s - 2 + K_1 & -3 \\ 1 + K_2 & s - 4 \end{bmatrix}
 \end{aligned}$$

Characteristic equation,

$$q(s) = |sI - (A - KC)| = \begin{vmatrix} s - 2 + K_1 & -3 \\ 1 + K_2 & s - 4 \end{vmatrix}$$

$$(s - 2 + K_1)(s - 4) + 3(1 + K_2) = 0$$

$$s^2 - 4s + (-2 + K_1)s + 8 - 4K_1 + 3 + 3K_2 = 0$$

$$s^2 + (-6 + K_1)s + (11 - 4K_1 + 3K_2) = 0 \quad \dots(ii)$$

On comparing equation (i) and (ii),

$$-6 + K_1 = 16$$

$$\therefore K_1 = 16 + 6 = 22$$

$$11 - 4K_1 + 3K_2 = 100$$

$$11 - 4 \times 22 + 3K_2 = 100$$

$$3K_2 = 100 - 11 + 88 = 177$$

$$\therefore K_2 = 59$$

The observer gain matrix,

$$\begin{bmatrix} K_1 \\ K_2 \end{bmatrix} = \begin{bmatrix} 22 \\ 59 \end{bmatrix}$$

Section-B

Q.5 (a) Solution:

$$\text{M.D} = 20 \text{ MW, LF} = 75\%, \text{PCF} = 50\%$$

$$\text{Plant use factor} = 80\%$$

$$\text{Average load} = \text{MD} \times \text{LF} = 20 \times 0.75 = 15 \text{ MW}$$

$$(i) \text{ Daily Energy Generates} = 15 \times 24 = 360 \text{ MWh}$$

$$(ii) \text{ Plant Reserve capacity} = \text{Plant capacity} - \text{Max. Demand}$$

$$\text{Plant capacity} = \frac{\text{Avg. load}}{\text{PCF}} = \frac{15}{0.5} = 30 \text{ MW}$$

$$\text{Plant reserve} = \text{P.C} - \text{M.D} = 30 - 20 = 10 \text{ MW}$$

(iii) Max. Energy that can be produced daily if the plant running all the time

$$= \frac{\text{Actual Energy Generated}}{\text{PCF}} = \frac{360}{0.5} = 720 \text{ MWh}$$

Q.5 (b) Solution:

Let X_1 , X_2 and X_3 be the positive negative and zero sequence reactances respectively of the alternator.

For 3-phase fault,

$$\text{Fault current} = \frac{E_{ph}}{X_1}$$

$$2000 = \frac{11000 / \sqrt{3}}{X_1}$$

$$\therefore X_1 = \frac{11000}{\sqrt{3} \times 2000} = 3.175 \Omega$$

For line-to-line fault, we have

$$\text{Fault current} = \frac{\sqrt{3}E_{ph}}{X_1 + X_2}$$

$$2600 = \frac{\sqrt{3} \times \frac{11000}{\sqrt{3}}}{X_1 + X_2}$$

$$X_1 + X_2 = \frac{11000}{2600} = 4.231 \Omega$$

$$X_2 = 4.231 - X_1 = 4.231 - 3.175 = 1.056 \Omega$$

For line-to-ground fault, we have,

$$\text{Fault current} = \frac{3E_{ph}}{X_1 + X_2 + X_0}$$

$$4200 = \frac{3 \times \frac{11000}{\sqrt{3}}}{X_1 + X_2 + X_0}$$

$$X_1 + X_2 + X_0 = \frac{3 \times 11000}{\sqrt{3} \times 4200} = 4.536 \Omega$$

$$X_0 = 4.536 - X_1 - X_2$$

$$= 4.536 - 3.175 - 1.056 = 0.305 \Omega$$

Q.5 (c) Solution:

Assembly language program for the given problem is as follows:

```

LXI H, XX60H ; source pointer
LXI D, XX80H ; Destination pointer.
MVIC, N      ; Number of readings
LOOP: INX H   ; Skip high byte
      MOV A, M ; Skip low byte
      XCHG
      MOV A, M ; Store low byte
      XCHG
      INX H   ; Move to next reading
      INXD   ; Mark Next Destination
      DCR C
      JNZ LOOP
      HLT
    
```

Q.5 (d) Solution:

(i) We may redraw the block diagram as shown in Figure (1).

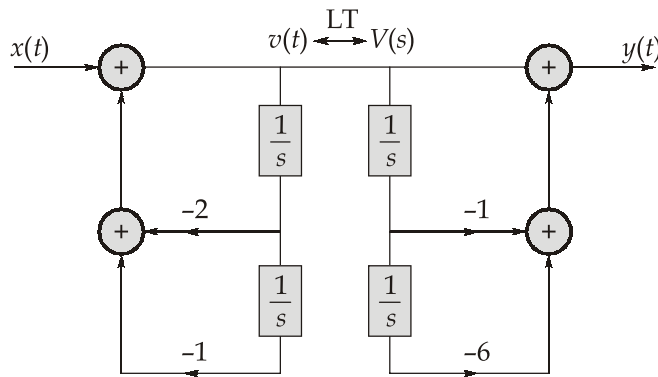


Figure (1)

Let $H_1(s) = \frac{V(s)}{X(s)}$ and $H_2(s) = \frac{Y(s)}{V(s)}$

$\therefore H(s) = H_1(s) \cdot H_2(s)$... (i)

Now, consider the left half section of the Figure (1).

$$V(s) = X(s) + \frac{1}{s} V(s)(-2) + (-1) \frac{V(s)}{s^2}$$

$$V(s) \left[1 + \frac{2}{s} + \frac{1}{s^2} \right] = X(s)$$

$$\frac{V(s)}{X(s)} = \frac{s^2}{(s^2 + 2s + 1)}$$

$$\frac{V(s)}{X(s)} = H_1(s) = \frac{s^2}{s^2 + 2s + 1} \quad \dots(\text{ii})$$

Now, from the right half section of Figure (1).

$$Y(s) = V(s) + \frac{1}{s}V(s)(-1) + \frac{1}{s^2}V(s)(-6)$$

$$Y(s) = V(s) \left[1 - \frac{1}{s} - \frac{6}{s^2} \right]$$

$$\frac{Y(s)}{V(s)} = H_2(s) = \frac{(s^2 - s - 6)}{s^2} \quad \dots(\text{iii})$$

Now, from equation (i), (ii) and (iii), we get

$$H(s) = \frac{s^2}{(s^2 + 2s + 1)} \times \frac{(s^2 - s - 6)}{s^2}$$

$$H(s) = \frac{(s^2 - s - 6)}{(s^2 + 2s + 1)} = \frac{Y(s)}{X(s)}$$

$$Y(s)[s^2 + 2s + 1] = X(s)[s^2 - s - 6]$$

The inverse Laplace transform of the above equation yields the differential equation of the system relating $x(t)$ and $y(t)$.

$$\frac{d^2y(t)}{dt^2} + \frac{2dy(t)}{dt} + y(t) = \frac{d^2x(t)}{dt^2} - \frac{dx(t)}{dt} - 6x(t)$$

$$\text{(ii)} \quad H(s) = \frac{(s^2 - s - 6)}{(s+1)^2} = \frac{(s-3)(s+2)}{(s+1)^2}$$

We know that for a system to be stable, all the poles must lie in the left half of the s -plane. The two poles of the system are at $s = -1$. We may conclude that this system is stable.

Q.5 (e) Solution:

$$\text{Armature circuit resistance, } r_a = \frac{xz}{a^2}$$

Here,

x = individual resistance of conductor

z = number of conductors

a = number of parallel paths

$$r_a = 1000 \times 2 \times 10^{-3} \times \frac{1}{2^2} = 0.5 \Omega$$

Let I_f be shunt field current.

The generated emf at 1055 rpm is given by

$$\begin{aligned} E_{a1} &= V_t + (I_L + I_f) \times 0.5 \\ &= 100 + (10 + I_f) \times 0.5 \end{aligned}$$

At 1105 rpm

$$E_{a2} = 100 + (20 + I_f) \times 0.5$$

But

Generated emf \propto field current \times speed

and

$$E_{a1} \propto I_f \times 1055$$

$$E_{a2} \propto I_f \times 1105$$

\therefore

$$I_f \times 1055 \propto 100 + (10 + I_f) \times 0.5$$

and

$$I_f \times 1105 \propto 100 + (20 + I_f) \times 0.5$$

$$\frac{I_f \times 1055}{I_f \times 1105} = \frac{100 + (10 + I_f) \times 0.5}{100 + (20 + I_f) \times 0.5}$$

Its solution gives

$$I_f = 1 \text{ A.}$$

\therefore

$$\begin{aligned} E_{a1} &= 100 + (10 + 1) \times 0.5 \\ &= 105.5 \text{ volts at 1055 rpm} \end{aligned}$$

Now

$$E_{a1} = \frac{\phi Z n P}{a}$$

or

$$105.5 = \frac{\phi \times 1000 \times 1055 \times 2}{60 \times 2}$$

$$\phi = \frac{105.5 \times 60}{1000 \times 1055} = 0.006 \text{ Wb}$$

\therefore

$$\text{Field circuit resistance} = \frac{V_t}{I_f} = \frac{100}{1} = 100 \Omega$$

$$\text{Flux per pole} = \frac{6}{2} = 3 \text{ mWb}$$

Q.6 (a) (i) Solution:

$$P_1 + P_2 = 210 \quad \dots(i)$$

For ELD without losses $I_{C1} = I_{C2}$

$$0.15P_1 + 50 = 0.2P_2 + 40$$

$$0.15P_1 - 0.02P_2 = -10$$

$$\Rightarrow 15P_1 - 20P_2 = -1000 \quad \dots(ii)$$

By solving to the equations $P_1 = 91.4$ MW, $P_2 = 118.6$ MW

Total cost or production with ELD.

$$I_{C1} = (0.15 \times 91.4 + 50) + (0.2 \times 118.6 + 40) = 127.43 \text{ Rs/hr}$$

Total cost of production when $P_1 = P_2 = 105$ MW

$$I_{C2} = (0.15 \times 105 + 50) + (0.2 \times 105 + 40)$$

$$C_1 = 0.075P_1^2 + 50P_1 + K_1$$

$$C_2 = 0.1P_2^2 + 40P_2 + K_2$$

$$\begin{aligned} F_1 = C_1 + C_2 &= (0.075(91.4)^2 + 50 \times 91.4 + K_1) + (0.1(118.6)^2 + 40(118.6) + K_2) \\ &= 5196.547 + K_1 + 6150.596 + K_2 = 11347.136 + K_1 + K_2 \end{aligned}$$

$$\begin{aligned} F_2 = C'_1 + C'_2 &= (0.075(105)^2 + 50 \times 105 + K_1 + 0.1(105)^2 + 40(105) + K_2) \\ &= 6076.875 + K_1 + 5302.5 + K_2 = 11379.375 + K_1 + K_2 \end{aligned}$$

Additional cost with the scheduling of $P_1 = P_2 = 105$ is

$$\begin{aligned} &= (11379.375 + K_1 + K_2) - (11347.136 + K_1 + K_2) \\ &= 32.24 \text{ Rs/hr} \end{aligned}$$

Q.6 (a) (ii) Solution:

$$\text{Load power rating } P_L = \sqrt{3}V_L I_2 \cos \phi$$

$$P_L = \sqrt{3} \times 500 \times 20 \times 0.8 = 13.856 \text{ kW}$$

$$\phi_1 = \cos^{-1}(0.8) = 36.80^\circ, \quad \phi_2 = \cos^{-1}(1.0) = 0.0$$

$$\text{KVAR Raised} = P(\tan \phi_1 - \tan \phi_2)$$

$$= 13.856(\tan 36.86 - \tan 0) = 10388.26 \text{ KVAR}$$

$$\text{Power rating of motor} = \frac{10 \times 746}{0.8} = 9.325 \text{ kW}$$

$$\text{The KVA rating of the motor} = \sqrt{9.325^2 + 10.388^2} = 13.9 \text{ kVA}$$

$$\phi = \tan^{-1}\left(\frac{10.388}{9.325}\right) = 48.08^\circ$$

$$P.F = \cos 48.08 = 0.67 \text{ lead}$$

Q.6 (b) Solution:

State table:

Present state			Next state			F.F Inputs				
A	B	C	A ⁺	B ⁺	C ⁺	J _A	K _A	T _B	S _C	R _C
0	0	1	0	1	1	0	X	1	X	0
0	1	1	1	0	0	1	X	1	0	1
1	0	0	0	1	0	X	1	1	0	X
0	1	0	0	0	0	0	X	1	0	X
0	0	0	0	0	1	0	X	0	1	0

K-map for J_A:

		BC			
		00	01	11	10
A	0	0	0	1	0
	1	X	X	X	X

$$J_A = BC$$

K-map for K_A:

		BC			
		00	01	11	10
A	0	X	X	X	X
	1	1	X	X	X

$$K_A = 1$$

K-map for T_B:

		BC			
		00	01	11	10
A	0	0	1	1	1
	1	1	X	X	X

$$T_B = A + B + C$$

K-map for S_C :

	BC			
A	00	01	11	10
0	1	X	0	0
1	0	X	X	X


$$S_C = \bar{A}\bar{B} \text{ or } S_C = \overline{A+B}$$

K-map for R_C :

	BC			
A	00	01	11	10
0	0	0	1	X
1	X	X	X	X

$$R_C = B$$

Circuit

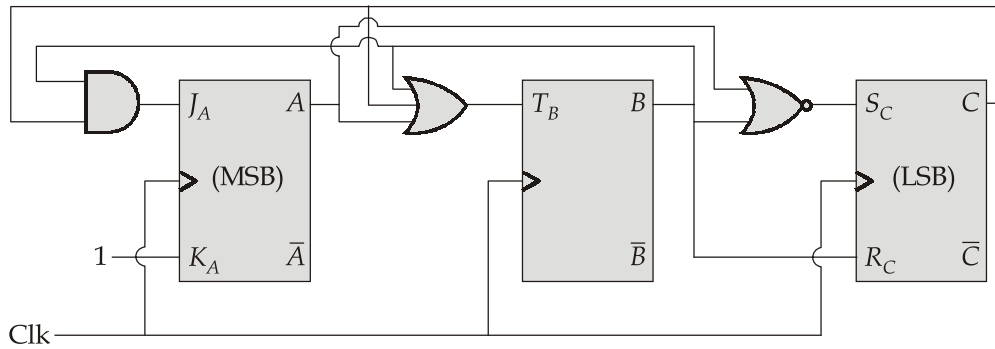


Q.6 (c) Solution:


There are four feedback amplifier topologies:

1. Voltage series feedback
2. Current series feedback
3. Current shunt feedback
4. Voltage shunt feedback


1. Voltage series feedback:

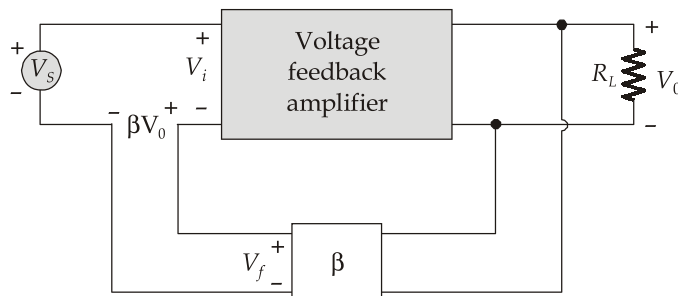


2. Current series feedback:

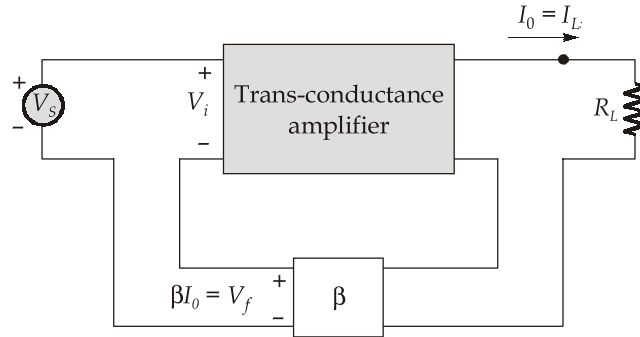


3. Current shunt feedback:

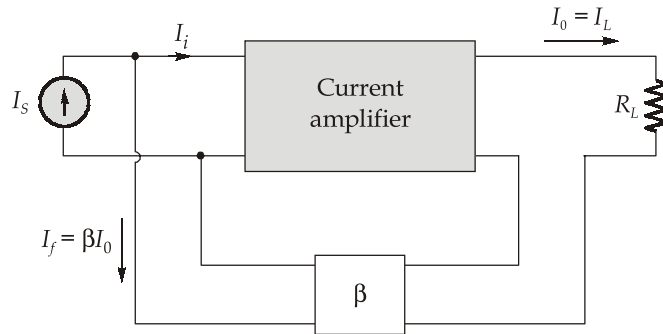

4. Voltage shunt feedback:

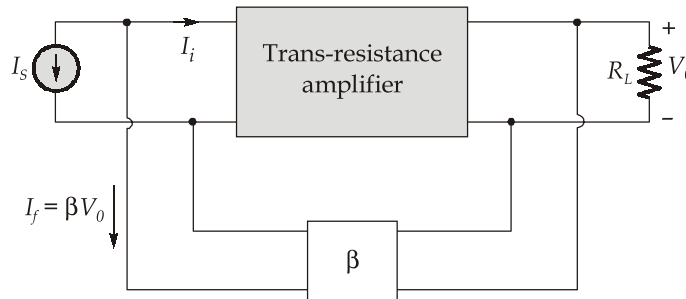

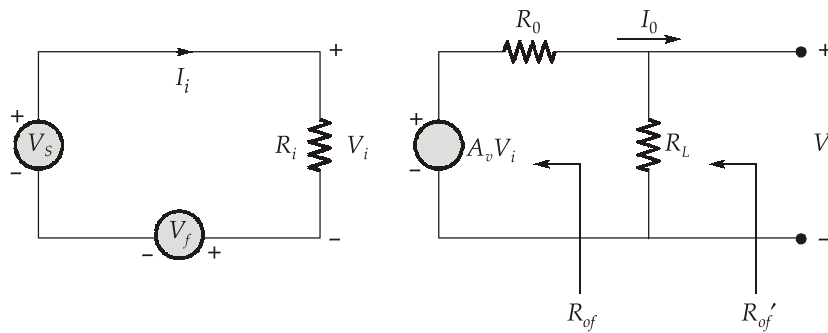Voltage series feedback circuit is shown in figure below:



$$V_s = I_i R_i + V_f = I_i R_i + \beta V_0 \quad \dots(i)$$

and

$$V_0 = \frac{A_v V_i R_L}{R_0 + R_L} = A_v I_i R_i \quad \dots(ii)$$

So,


$$A_{vf} = \frac{A_v R_L}{R_0 + R_L} \quad \dots(iii)$$

From equations (i) and (ii),

$$V_s = I_i R_i + \beta(A_v I_i R_i)$$

$$\frac{V_s}{I_i} = R_{if} = R_i(1 + \beta A_v)$$

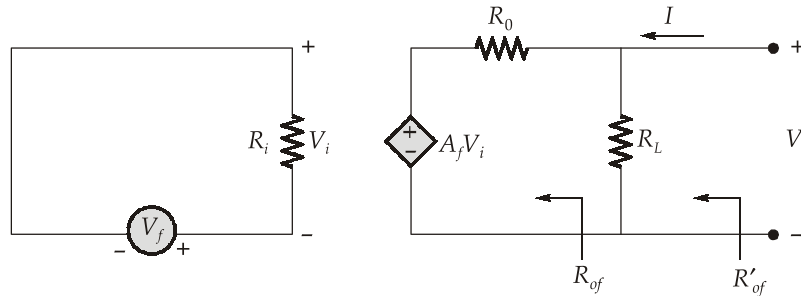For R_{of} taking $V_s = 0$ means $V_i = -V_f = -\beta V_0$



We have,

$$I = \frac{V_0}{R_L} + \frac{V_0 - A_v V_i}{R_0}$$

$$I = V_0 \left[\frac{1}{R_0} + \frac{1}{R_L} \right] + \frac{A_v V_f}{R_0} \quad \dots(iv)$$

$$= V_0 \left[\frac{1}{R_0} + \frac{1}{R_L} \right] + \frac{A_v \beta V_0}{R_0} = V_0 \left[\frac{1}{R_L} + \frac{1 + A_v \beta}{R_0} \right]$$

$$\frac{1}{R'_{of}} = \frac{I}{V_0} = \frac{1}{R_L} + \frac{1}{\frac{R_0}{1 + A_v \beta}}$$

$$R'_{of} = R_L || R_{of} = R_L || \frac{R_0}{1 + A_v \beta} = \frac{R_L || R_0}{1 + A_v \beta} = \frac{R'_0}{1 + A_v \beta}$$

where,

$$R_{of} = \frac{R_0}{1 + A_v \beta}$$

$$R'_0 = R_0 || R_L$$

Q.7 (a) Solution:

$$\begin{aligned} \text{Given, } S_{G1} &= P_{G1} + jQ_{G1} \\ S_{D1} &= P_{D1} + jQ_{D1} = 2 + j1 \\ S_{G2} &= P_{G2} + jQ_{G2} = 0.5 + j1 \\ S_{D2} &= P_{D2} + jQ_{D2} = 0 + j0 \end{aligned}$$

Using nominal π -method for transmission line

$$\begin{aligned} y_{\text{series}} &= \frac{1}{0.02 + j0.08} = 2.941 - j11.764 \\ &= 12.13 \angle -75.96^\circ \text{ p.u.} \end{aligned}$$

\therefore Each off diagonal term = $-2.941 + j11.764$ p.u.

$$\begin{aligned} \text{Each self term} &= (2(2.941 - j11.764) + j0.01) \\ &= 5.882 - j23.528 \\ &= 24.23 \angle -75.95^\circ \text{ p.u.} \end{aligned}$$

$$Y_{\text{bus}} = \begin{bmatrix} 24.23 \angle -75.95^\circ & 12.13 \angle 104.04^\circ & 12.13 \angle 104.04^\circ \\ 12.13 \angle 104.04^\circ & 24.23 \angle -75.95^\circ & 12.13 \angle 104.04^\circ \\ 12.13 \angle 104.04^\circ & 12.13 \angle 104.04^\circ & 24.23 \angle -75.95^\circ \end{bmatrix} \text{ } \Omega$$

Also given, $V_2^0 = 1 + j0$ and $\delta_3^0 = 0$

$$\begin{aligned} P_2 &= |V_2| |V_1| |Y_{21}| \cos(\theta_{21} + \delta_1 - \delta_2) + |V_2|^2 |y_{22}| \cos(\theta_{22}) \\ &\quad + |V_2| |V_3| |Y_{23}| \cos(\theta_{23} + \delta_3 - \delta_2) \end{aligned}$$

$$\begin{aligned} P_3 &= |V_3| |V_1| |Y_{31}| \cos(\theta_{31} + \delta_1 - \delta_3) \\ &\quad + |V_3| |V_2| |Y_{32}| \cos(\theta_{32} + \delta_2 - \delta_3) + V_3^2 |Y_{33}| \cos(\theta_{33}) \end{aligned}$$

$$\begin{aligned} Q_2 &= \left[-|V_2| |V_1| |Y_{21}| \sin(\theta_{21} + \delta_1 - \delta_2) - V_2^2 |Y_{22}| \sin(\theta_{22}) \right. \\ &\quad \left. - |V_2| |V_3| |Y_{23}| \sin(\theta_{23} + \delta_3 - \delta_2) \right] \end{aligned}$$

$$\begin{aligned} P_2^0 &= [(1.04)(1)(12.13) \cos(104.04 + 0 - 0) + (1)^2 (24.23) \cos(-75.95^\circ) \\ &\quad + (1)(1.04)(12.13) \cos(104.04^\circ + 0 - 0)] \\ &= -3.064 + 5.8822 - 3.0604 \\ &= -0.2385 \text{ p.u.} \end{aligned}$$

$$\begin{aligned} P_3^0 &= [(1.04)(1.04)(12.13) \cos(104.04 + 0 - 0) + (1.04) \times 12.13 (\cos 104.04) \\ &\quad + (1.04)^2 (24.23) \cos(-75.95)] \end{aligned}$$

$$\begin{aligned}
 &= -3.18285 - 3.0604 + 6.3622 \\
 &= 0.119 \text{ p.u.}
 \end{aligned}$$

Similarly, $Q_2^0 = -0.9715 \text{ p.u.}$

Checking for Q_3 range

$$\begin{aligned}
 Q_3 &= -|V_3|V_1Y_{31} \sin(\theta_{31} + \delta_1^{(0)} - \delta_3^{(0)}) - |V_3|^2 Y_{33} \sin(\theta_{33}) \\
 &\quad - V_3V_2Y_{32} \sin(\theta_{32} + \delta_2^{(0)} - \delta_3^{(0)}) \\
 &= -12.7278 + 25.423 - 12.238 = 0.2686
 \end{aligned}$$

$$Q_{G3}^{(0)} = Q_{D3} + \Delta Q_3^{(0)} = 0.6 + 0.2686 = 0.8686 \text{ p.u.}$$

Power residual,

$$\begin{aligned}
 \Delta P_2^0 &= P_2 \text{ (specified)} - \Delta P_2^0 \text{ (Calculated)} = 0.5 - (-0.235) \\
 &= 0.7385 \text{ p.u.}
 \end{aligned}$$

$$\Delta P_3^0 = -1.5 - (0.119) = -1.619 \text{ p.u.}$$

$$\Delta Q_2^0 = 1 - (-0.9715) = 1.9715 \text{ p.u.}$$

So matrix equations for the solution of load flow by FDLF method,

$$\begin{bmatrix} \frac{\Delta P_2^{(0)}}{|V_2^{(0)}|} \\ \frac{\Delta P_3^{(0)}}{|V_3^{(0)}|} \end{bmatrix} = \begin{bmatrix} -B_{22} & -B_{23} \\ -B_{32} & -B_{33} \end{bmatrix} \begin{bmatrix} \Delta \delta_2^{(0)} \\ \Delta \delta_3^{(0)} \end{bmatrix}$$

and
$$\begin{bmatrix} \frac{\Delta Q_2^{(0)}}{|V_2^{(0)}|} \end{bmatrix} = [-B_{22}] \begin{bmatrix} \Delta |V_2^{(0)}| \end{bmatrix}$$

Here B_{22} and B_{33} are the imaginary parts of Y_{22} and Y_{33}

$$\begin{bmatrix} \frac{0.7385}{1} = 0.7385 \\ \frac{-1.619}{1.04} = -1.5567 \end{bmatrix} = \begin{bmatrix} 23.528 & -11.764 \\ -11.764 & 23.528 \end{bmatrix} \begin{bmatrix} \Delta \delta_2^{(0)} \\ \Delta \delta_3^{(0)} \end{bmatrix}$$

Solving above equation,

$$\Delta\delta_2^{(0)} = -0.0023 \text{ rad}$$

$$\Delta\delta_3^{(0)} = -0.0673 \text{ rad}$$

$$\delta_2^{(1)} = 0 - 0.0023 = -0.0023 \text{ rad or } -0.13178^\circ$$

$$\delta_3^{(1)} = 0 - 0.0673 = -0.0673 \text{ rad or } -3.856^\circ$$

$$Q_2^{(0)} = \left(-1.04 \times 1 \times 12.13 \sin \left(104.04^\circ + 0 + 0.0023 \times \frac{180}{\pi} \right) - (24.23) \sin(-75.95^\circ) \right.$$

$$\left. - (1.04) \left(12.13 \sin \left(104.04 + 0.0023 \times \frac{180}{\pi} - 0.0673 \times \frac{180}{\pi} \right) \right) \right)$$

$$= -12.231 + 23.50 - 12.411 = -1.14227 \text{ p.u.}$$

$$\Delta Q_2^{(0)} = 1 - (-1.14227) = -2.14227 \text{ p.u.}$$

$$-2.14227 = 23.528 \left(\Delta V_2^{(0)} \right)$$

$$\Delta |V_2^0| = 0.091$$

$$|V_2^{(1)}| = |V_2^{(0)}| + \Delta |V_2^{(0)}| = 1 + 0.091 = 1.091 \text{ p.u.}$$

Q.7 (b) Solution:

Let 7500 kVA be the base kVA.

% Reactance of generator A on the base kVA

$$= 7 \times \frac{7500}{3000} = 17.5\%$$


% reactance of generator B on the base kVA

$$= 8 \times \frac{7500}{4500} = 13.34\%$$

% Reactance of transformer on the base kVA

$$= 7.5 \times \frac{7500}{7500} = 7.5\%$$

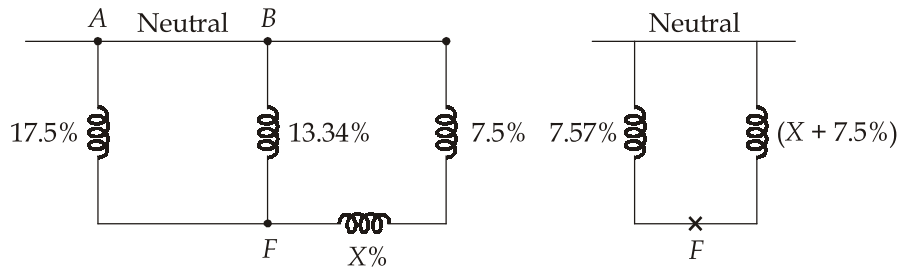Let the percentage reactance of the bus-bar reactor be X%. Then for 3-phase short-circuit fault on an outgoing feeder, the reactance diagram at the selected base kVA will be as shown in figure



Total % reactance from generator neutral to fault point F

$$\begin{aligned}
 &= 7.57\% \parallel (X + 7.5)\% \\
 &= \frac{7.57(X + 7.5)}{X + 15.07}\%
 \end{aligned}$$

$$\text{Short-circuit kVA} = 7500 \times 100 \times \frac{X + 15.07}{7.57(X + 7.5)}$$

But the short-circuit kVA should not exceed 150×10^3 kVA, the rupturing capacity of the breaker.

$$150 \times 10^3 = \frac{7500 \times 100 \times (X + 15.07)}{7.57(X + 7.5)}$$

$$7.57(X + 7.5) = 5(X + 15.07)$$

$$7.57X + 56.77 = 5X + 75.35$$

$$X = \frac{75.35 - 56.77}{7.57 - 5} = 7.23\%$$

The %age reactance can be converted into reactance in ohm by the following expression:

$$\%X = \frac{(\text{kVA})X}{10(\text{kV})^2}$$

$$7.23 = \frac{7500X}{10(3.3)^2}$$

$$X = \frac{7.23 \times 10 \times (3.3)^2}{7500} = 0.105 \Omega$$

Q.7 (c) Solution:

(i) Given differential equation,

$$x''(t) - 2x'(t) + 4x(t) = u(t)$$

Taking Laplace transform,

$$s^2X(s) - sx(0^-) - x'(0^-) - 2[sX(s) - x(0^-)] + 4X(s) = \frac{1}{s}$$

$$X(s)[s^2 - 2s + 4] - 4 = \frac{1}{s}$$

$$X(s)[s^2 - 2s + 4] = \frac{1}{s} + 4 = \frac{(4s + 1)}{s}$$

$$X(s) = \frac{(4s + 1)}{s(s^2 - 2s + 4)}$$

Using partial fraction expansion,

$$X(s) = \frac{A}{s} + \frac{Bs + C}{(s^2 - 2s + 4)} \quad \dots(i)$$

$$A = \frac{(4s + 1)}{(s^2 - 2s + 4)} \Big|_{s=0} = \frac{1}{4}$$

$$\therefore A = \frac{1}{4}$$

and

$$(4s + 1) = A(s^2 - 2s + 4) + (Bs + C)s$$

$$(4s + 1) = (A + B)s^2 + (C - 2A)s + 4A$$

Comparing coefficients of power of 's' on both sides, we get

$$A + B = 0 \quad , \quad C - 2A = 4$$

$$B = -A = -\frac{1}{4} \quad , \quad C - \frac{2}{4} = 4$$

$$\therefore B = -\frac{1}{4} \quad C = 4 + \frac{1}{2}$$

$$\therefore C = \frac{9}{2}$$

Substituting all the values in equation (i), we get

$$X(s) = \frac{1}{4s} + \frac{\left(-\frac{1}{4}s + \frac{9}{2}\right)}{(s^2 - 2s + 4)}$$

$$\begin{aligned} X(s) &= \frac{1}{4s} - \frac{s}{4(s^2 - 2s + 4)} + \frac{9}{2(s^2 - 2s + 4)} \\ &= \frac{1}{4s} - \frac{s}{4[(s-1)^2 + (\sqrt{3})^2]} + \frac{9}{2[(s-1)^2 + (\sqrt{3})^2]} \end{aligned}$$

$$= \frac{1}{4s} - \frac{(s-1)}{4[(s-1)^2 + (\sqrt{3})^2]} - \frac{1}{4[(s-1)^2 + (\sqrt{3})^2]} + \frac{9}{2[(s-1)^2 + (\sqrt{3})^2]}$$

$$= \frac{1}{4s} - \frac{(s-1)}{4[(s-1)^2 + (\sqrt{3})^2]} + \frac{17 \times \sqrt{3}}{4[(s-1)^2 + (\sqrt{3})^2](\sqrt{3})}$$

Taking inverse Laplace transform,

$$x(t) = \frac{1}{4}u(t) - \frac{1}{4}e^t \cos(\sqrt{3}t) + \frac{17}{4\sqrt{3}}e^t \sin(\sqrt{3}t); t \geq 0$$

$$x(t) = \frac{1}{4} \left[1 - e^t \cos(\sqrt{3}t) + \frac{17}{\sqrt{3}} e^t \sin(\sqrt{3}t) \right] u(t)$$

(ii) Given, frequency, $f = 2 \text{ Hz}$


$$\therefore \omega = 2\pi f = 2\pi \times 2$$

$$= 4\pi \text{ rad/sec}$$

Given input, $x(t) = \cos[\omega t]u(t) = \cos(4\pi t)u(t)$

Given transfer function,
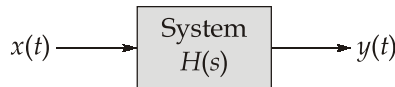
$$H(s) = \frac{10}{(s+10)} \quad \dots(i)$$



$$y(t) = |H(j\omega)|_{\omega=4\pi} \cos \left[4\pi t + \angle H(j\omega)|_{\omega=4\pi} \right] \quad \dots(ii)$$

Now put, $s = j\omega$ in equation (i)

$$H(j\omega) = \frac{10}{(j\omega + 10)}$$

$$|H(j\omega)| = \frac{10}{\sqrt{\omega^2 + 10^2}}$$

$$|H(j\omega)|_{\omega=4\pi} = \frac{10}{\sqrt{(4\pi)^2 + 10^2}} = 0.623$$


$$\angle H(j\omega)|_{\omega=4\pi} = -\tan^{-1} \left(\frac{\omega}{10} \right) \Big|_{\omega=4\pi} = -\tan^{-1} \left(\frac{4\pi}{10} \right) = -0.899 \text{ rad}$$

Substituting all the values in equation (ii), we get

$$y(t) = 0.623 \cos(4\pi t - 0.899); t > 0$$

Q.8 (a) (i) Solution:

Voltage commutated chopper circuit,

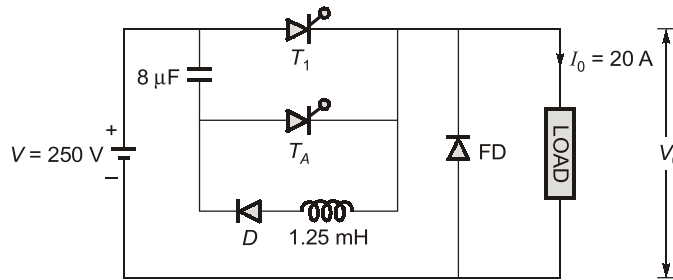

Commutation circuit turnoff time,

$$t_c = \frac{CV_s}{I_0} = \frac{8 \times 10^{-6} \times 250}{20} = 1 \times 10^{-4} \text{ s}$$

The minimum on period for this chopper is,

$$t_1 = \frac{\pi}{\omega_0} = \pi\sqrt{LC}$$

$$= \pi\sqrt{1.25 \times 10^{-3} \times 8 \times 10^{-6}} = 3.1416 \times 10^{-4} \text{ s}$$

The minimum average output voltage of the circuit is,


$$V_{0, \min} = fV_s[t_1 + 2t_c]$$

$$= 250 \times 250 [3.1416 \times 10^{-4} + 2 \times 10^{-4}]$$

$$V_{0, \min} = 32.135 \text{ V}$$

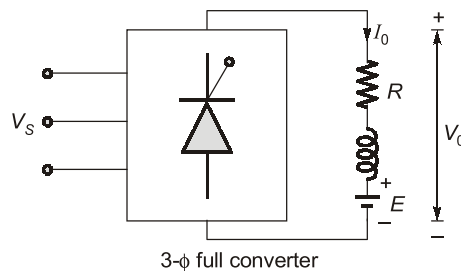Q.8 (a) (ii) Solution:

Average output voltage of 3-φ full converter,



$$V_0 = \frac{3V_{ml}}{\pi} \cos \alpha = E + I_0R$$


$$\frac{3 \times \sqrt{2} \times 220}{\pi} \cos \alpha = 110 + (10 \times 0.2)$$

$$297.1043 \cos \alpha = 112$$

$$\alpha = \cos^{-1} \left(\frac{112}{297.1043} \right)$$

Firing angle, $\alpha = 67.85^\circ$

SCR conducts for 120° .

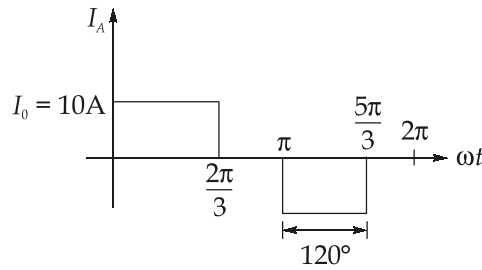

For constant load current, $I_0 = 10 \text{ A}$,

Supply current i_A is of square wave of amplitude 10 A. As i_A flows for 120° over every half cycle of 180° , the rms supply current, I_s is ,

$$I_s = 10 \sqrt{\frac{120^\circ}{180^\circ}} = 8.1649 \text{ A}$$

Power delivered to the load = $P_0 = V_0 I_0$

$$= \left[\frac{3 \times \sqrt{2} \times 220}{\pi} \cos(67.85^\circ) \right] \times 10 = 1120.18 \text{ W}$$

$$\text{Input supply power factor} = \frac{V_0 I_0}{\sqrt{3} V_s I_s} = \frac{1120.18}{\sqrt{3} \times 220 \times 8.1649} = 0.36 \text{ (lag)}$$


or input supply power factor for 3- ϕ full converter

$$= \frac{3}{\pi} \cos \alpha = \frac{3}{\pi} \cos(67.85^\circ) = 0.36 \text{ (lag)}$$

Q.8 (b) Solution:

Given, The phase voltage, $V_{ph} = \frac{440}{\sqrt{3}} = 254 \text{ V}$

and slip, $s = 0.025$

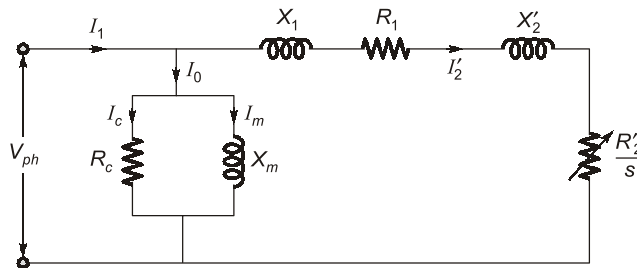

Equivalent per phase circuit diagram of induction motor

From equivalent circuit diagram, the rotor per phase current referred to stator side is

$$\bar{I}'_2 = \frac{V_{ph}}{R_1 + \left(\frac{R'_2}{s}\right) + j(X_1 + X'_2)}$$

$$\begin{aligned}\bar{I}'_2 &= \frac{254}{0.25 + \left(\frac{0.25}{0.025}\right) + j(0.75 + 0.75)} \\ &= \frac{254}{10.25 + j1.50} = 24.52 \angle -8.33^\circ \text{ A}\end{aligned}$$

$$\bar{I}'_2 = 24.52 \angle -8.33^\circ = (24.26 - j3.55) \text{ A}$$

The no-load current is

$$I_c = \frac{254}{100} = 2.54 \text{ A}$$

$$I_m = \frac{254}{j1000} = -j0.254 \text{ A}$$

$$\bar{I}_0 = 2.54 - j0.254 \text{ A}$$

The input line current is,

$$\begin{aligned}\bar{I}_1 &= \bar{I}_0 + I'_2 \\ &= (2.54 - j0.254) + (24.26 - j3.55) \\ &= 26.8 - j3.804 = 27.07 \angle -8.1^\circ \text{ A}\end{aligned}$$

The power factor is $\cos 8.01^\circ = 0.99$

Synchronous speed can be given as

$$N_s = \frac{120f}{p} = \frac{120 \times 50}{6} = 1000 \text{ RPM}$$

The rotational speed is,

$$\omega_s = \frac{2\pi N_s}{60} = \frac{2\pi \times 1000}{60} = 104.72 \text{ rad/s}$$

The developed torque is,

$$T = \frac{P_g}{\omega_s} = \frac{3I_2'^2 R'_2}{s\omega_s} = \frac{3 \times (24.52)^2 \times 0.25}{0.025 \times 104.72} = 172.24 \text{ Nm}$$

The power output is,

$$\begin{aligned}P_0 &= P_{\text{mech}} - \text{Rotational loss} \\ &= (1-s) \frac{3I_2'^2 R'_2}{s} - \text{Rotational loss} \\ &= (1-0.025) \frac{3 \times (24.52)^2 \times 0.25}{0.025} - 450 = 17136 \text{ W}\end{aligned}$$

$$\begin{aligned}\text{Rotor copper loss} &= 3I_2'^2 \times R_2' \\ &= 3 \times (24.52)^2 \times 0.25 = 450.92 \text{ W}\end{aligned}$$

The efficiency can be given as

$$\begin{aligned}\eta &= \frac{\text{Output}}{\text{Input}} \times 100 = \frac{\text{Output}}{\text{Output} + \Sigma \text{ Losses}} \times 100 \\ &= \frac{17136 \times 100}{17136 + 800 + 450 + 450.92} = 90.97\%\end{aligned}$$

Q.8 (c) Solution:

(i) Given:

Open loop transfer function,

$$G(s)H(s) = \frac{8s}{(s-1)(s-2)}$$

Open loop poles : $s = 1, s = 2$

There are two open loop poles on the right half of s -plane i.e., $P = 2$.

There are no open loop poles on the $j\omega$ -axis. So, the Nyquist contour includes $j\omega$ axis.

$$\text{Put } s = j\omega, \quad G(j\omega)H(j\omega) = \frac{j8\omega}{(j\omega-1)(j\omega-2)}$$

$$|G(j\omega)H(j\omega)| = \frac{8\omega}{\sqrt{\omega^2+1}\sqrt{\omega^2+4}}$$

$$\begin{aligned}\angle G(j\omega)H(j\omega) &= 90^\circ - (180^\circ - \tan^{-1}(\omega)) - \left(180^\circ - \tan^{-1}\left(\frac{\omega}{2}\right)\right) \\ &= 90^\circ + \tan^{-1}(\omega) + \tan^{-1}\left(\frac{\omega}{2}\right)\end{aligned}$$

$$G(j\omega)H(j\omega) = \frac{8\omega}{\sqrt{\omega^2+1}\sqrt{\omega^2+4}} \angle 90^\circ + \tan^{-1}(\omega) + \tan^{-1}\left(\frac{\omega}{2}\right)$$

ω	$ G(j\omega)H(j\omega) \angle G(j\omega)H(j\omega)$
0	0 $\angle 90^\circ$
0.1	0.3975 $\angle 98.57^\circ$
1	2.53 $\angle 161.56^\circ$
1.5	2.662 $\angle 183.18^\circ$
2	2.53 $\angle 198.44^\circ$
10	0.78 $\angle 252.98^\circ$
∞	0 $\angle 270^\circ$

Intercept with real-axis will occur at ω where,

$$\angle G(j\omega)H(j\omega) = -180^\circ$$

$$-180^\circ = 90^\circ + \tan^{-1}(\omega) + \tan^{-1}\left(\frac{\omega}{2}\right)$$


$$-90^\circ = \tan^{-1}\left(\frac{\omega + \frac{\omega}{2}}{1 - \frac{\omega^2}{2}}\right)$$

$$1 - \frac{\omega^2}{2} = 0$$

$$\Rightarrow \omega = \sqrt{2} \text{ rad/sec}$$

$$\therefore G(j\omega)H(j\omega)|_{\omega=\sqrt{2}} = \frac{8}{3} \angle 180^\circ$$

Nyquist plot,

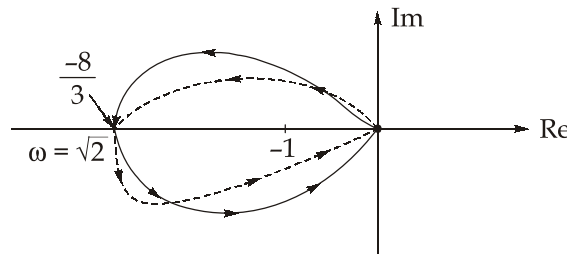

There are two encirclements of $(-1, 0)$ in anti-clockwise.

i.e., $N = +2$

We know, $N = P - Z \Rightarrow Z = P - N$

$$Z = 2 - 2 = 0$$

Hence, there are no closed loop poles on right side.

So, the system is stable.

(ii) Given, open loop transfer function,

$$G(s)H(s) = \frac{8s}{(s-1)(s-2)}$$

Characteristic equation,

$$1 + G(s)H(s) = 0$$

$$1 + \frac{8s}{(s-1)(s-2)} = 0$$

$$s^2 - 3s + 2 + 8s = 0$$

$$s^2 + 5s + 2 = 0$$

R-H Table:

$$\begin{array}{l|ll} s^2 & 1 & 2 \\ s^1 & 5 & \\ s^0 & 2 & \end{array}$$

Since all the coefficients of 1st column of R-H table is positive. So, the system is stable.

○○○○