



**MADE EASY**  
Leading Institute for ESE, GATE & PSUs

Detailed Solutions

**ESE-2026  
Mains Test Series**

**Electrical Engineering  
Test No : 15**

**Section-A**

**Q.1 (a) Solution:**

(i)

$$V_d = 295 - 325 \text{ V}$$

Peak of the fundamental frequency component in the output voltage is,

$$V_{01\text{peak}} = m_a V_d = 1 \times 295 = 295 \text{ V}$$

$$V_{\text{rms}, 01} = \frac{V_{01\text{peak}}}{\sqrt{2}} = \frac{295}{\sqrt{2}} = 208.6 \text{ V}$$

(ii)

$$I_0 = \frac{2000}{208.6} = 9.6 \text{ A}$$

$$I_{0\text{peak}} = \sqrt{2} \times I_0 = \sqrt{2} \times 9.6 \\ = 13.57 \text{ A}$$

Switch voltage rating,

$$V_T = V_{d, \text{max}} = 325 \text{ V}$$

Switch current rating,

$$I_T = I_{0\text{peak}} = 13.57 \text{ A} \approx 13.6 \text{ A}$$

Number of switches,

$$q = 4$$

$$\therefore \text{Combined switch utilization ratio} = \frac{\text{Rated volt amperes}}{q V_T I_T} \\ = \frac{2000}{4 \times 325 \times 13.6} = 0.113$$

## Q.1 (b) Solution:

Given :

$$V_t = 220 \text{ V}, P = 8$$


Lap winding,

$$Z = 1200 \text{ conductors,}$$

$$R_{sh} = 220 \Omega,$$

$$I_{L1} = 50 \text{ A,}$$

$$N_1 = N_{\text{rated}}$$

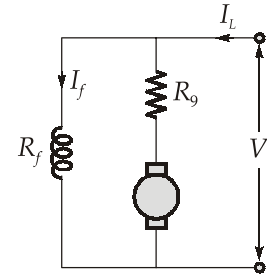

Since winding is LAP, so number of parallel path in armature circuit is 8.

$$\text{Number of conductors per path} = \frac{Z}{A} = \frac{1200}{8} = 150$$

$$\text{Resistance of each conductor} = 50 \text{ m}\Omega$$

$$\text{So, resistance of each parallel path} = \frac{Z}{A} \times r_{\text{each}} = 150 \times 50 \times 10^{-3} = 7.5 \Omega$$

$$I_{a1} = I_L - I_{sh} = 50 - 1 = 49 \text{ A}$$

$$E_{b1} = V_t - I_{a1} r_a = 220 - 49 \times 0.9375 = 174.06 \text{ V}$$

Since torque is constant,

$$\frac{T_2}{T_1} = \frac{E_{b2} \cdot I_{a2}}{E_{b1} \cdot I_{a1}} \times \frac{N_1}{N_2}$$

$$(E_{b1} I_{a1}) \times \frac{N_2}{N_1} = E_{b2} \cdot I_{a2}$$

$$(174.06 \times 49) \times 1.4 = (V_t - I_{a2} \cdot r_a) I_{a2}$$

$$11940.68 = (220 - I_{a2} \times 0.9375) I_{a2}$$

$$0.9375 I_{a2}^2 - 220 I_{a2} + 11940.68 = 0$$

On solving,

$$I_{a2} = 149.43 \text{ A, } 85.23 \text{ A}$$

We will choose  $I_{a2} = 85.23 \text{ A}$ , otherwise Cu-losses will increase and efficiency of machine will deteriorate.

As we know,

$$N \propto \frac{E_b}{\phi}$$

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{\phi_1}{\phi_2}$$

$$\phi \propto I_{sh}$$

$$\frac{\phi_1}{\phi_2} = \frac{I_{sh1}}{I_{sh2}}$$

$$\frac{I_{sh2}}{I_{sh1}} = \frac{E_{b2} \times N_1}{E_{b1} \times N_2} = \frac{(220 - 0.9375 \times 85.23) \times N_1}{174.06 \times 1.4 N_1}$$

$$\frac{I_{sh2}}{I_{sh1}} = 0.5749$$

$$I_{sh2} = I_{sh1} \times 0.5749 = 0.5749 \text{ A } [\because I_{sh1} = 1 \text{ A}]$$

$$R_{\text{ext}} + R_{sh} = \frac{V_t}{I_{sh2}} = 382.66 \Omega$$

So, required value of external resistance to be added in field winding is

$$R_{\text{ext}} = 382.66 - 220 = 162.66 \Omega$$

to increase speed by 1.4 times of rated speed.

### Q.1 (c) Solution:

Sending end phase voltage,  $V_S = \frac{230}{\sqrt{3}} = 132.79 \text{ kV}$

When the load is disconnected,

$$I_R = 0 \text{ A}$$

$\therefore$  sending end phase voltage,

$$\begin{aligned} V_S &= AV_R + BI_R \\ &= AV_R \end{aligned}$$

$$\therefore V_R = \frac{V_S}{A} = \frac{132.79}{0.938 \angle 1.2} = 141.57 \angle -1.2^\circ \text{ kV}$$

Receiving end line voltage,

$$\therefore V_{RL} = \sqrt{3}V_R = \sqrt{3} \times 141.57 = 245.2 \text{ kV}$$

Line charging current,

$$\begin{aligned} I_C &= CV_R = 0.001 \angle 90^\circ \times 141.57 \angle -1.2^\circ \\ &= 141.57 \angle 88.8^\circ \text{ A} \end{aligned}$$

Maximum power that can be transmitted for  $V_{RL} = 220 \text{ kV}$  and  $V_S = 230 \text{ kV}$

$$A = 0.938, \quad B = 131.2,$$

$$\alpha = 1.2^\circ, \quad \beta = 72.3^\circ$$

$$P_R = \frac{V_S V_R}{B} \cos(\beta - \delta) - \frac{AV_R^2}{B} \cos(\beta - \alpha)$$

For  $P_R = P_{R \text{ max}}$ ,

$$\delta = \beta = 72.3^\circ$$

$$P_{R \text{ (max)}} = \frac{V_S V_{RL}}{B} - \frac{A}{B} V_{RL}^2 \cos(\beta - \alpha)$$

$$= \frac{(230)(220)}{131.2} - \frac{0.938}{131.2} \times 220^2 \cos(72.3 - 1.2)$$

$$= 272.58 \text{ MW}$$

Corresponding reactive power required at the receiving end,

$$Q_R = -\frac{A}{B} V_{RL}^2 \sin(\beta - \alpha) = \frac{-0.938}{131.2} \times 220^2 \sin(72.3^\circ - 1.2^\circ)$$

$$= -327.37 \text{ MVAR}$$

**Q.1 (d) Solution:**

(i) When a converter circuit is working in an inverter mode,

$$V_0 = -E + I_0 R$$

for 3-pulse converter, output voltage  $V_0$  is,

$$V_0 = \frac{3V_{mL}}{2\pi} \cos \alpha$$

Therefore, 
$$\frac{3V_{mL}}{2\pi} \cos \alpha = -230 + 10 \times 2$$

$$\frac{3V_{mL}}{2\pi} \cos \alpha = -210$$

$$\frac{3 \times 400\sqrt{2}}{2\pi} \cos \alpha = -210$$

$$\text{Firing angle, } \alpha = 141.033^\circ$$

(ii) Source inductance is responsible for reduction in output voltage of converter.

Reduction in output voltage,

$$\Delta V_d = 3fL_s I_0$$

$$\Delta V_d = 3 \times 50 \times 2 \times 10^{-3} \times 10 = 3\text{V}$$

Now, 
$$V_0 = \frac{3V_{mL}}{2\pi} \cos \alpha - \Delta V_d = -E + I_0 R$$

$$\frac{3V_{mL}}{2\pi} \cos \alpha - \Delta V_d = -230 + 10 \times 2$$

$$\frac{3V_{mL}}{2\pi} \cos \alpha = -210 + 3$$

$$\frac{3 \times 400\sqrt{2}}{2\pi} \cos \alpha = -207$$

$$\text{Firing angle, } \alpha = 140.03^\circ$$

For 3-pulse converter, reduction in output voltage in terms of overlap angle is given by,

$$\Delta V_d = \frac{3V_{mL}}{4\pi} [\cos \alpha - \cos(\alpha + \mu)]$$

$$\frac{3V_{mL}}{4\pi} \cos(\alpha + \mu) = \frac{3V_{mL}}{4\pi} \cos \alpha - \Delta V_{d0}$$

$$\frac{3 \times 400\sqrt{2}}{4\pi} \cos(\alpha + \mu) = \frac{3 \times 400\sqrt{2}}{4\pi} \cos 140.03^\circ - 3 = -106.50$$

$$\cos(\alpha + \mu) = -0.7886$$

$$\alpha + \mu = 142.055^\circ$$

$$\text{Overlap angle } \mu = 2.025^\circ$$

### Q.1 (e) Solution:

For phase lead controller,

$$G_c(s) = \frac{1 + aTs}{1 + Ts}, \quad \text{Put } s = j\omega$$

$$G_c(j\omega) = \frac{1 + jaT\omega}{1 + jT\omega}$$

$$\phi = \angle G_c(j\omega) = \tan^{-1}(a\omega T) - \tan^{-1}(\omega T) \quad \dots(i)$$

$$\tan \phi = \frac{a\omega T - \omega T}{1 + a\omega T \cdot \omega T}$$

$$\tan \phi = \frac{\omega T(a - 1)}{1 + a\omega^2 T^2} \quad \dots(ii)$$

For getting maximum value of phase angle,

From equation (i), at  $\omega = \omega_m$

$$\frac{d\phi}{d\omega} = 0 = \frac{aT}{1 + (a\omega_m T)^2} - \frac{T}{1 + (\omega_m T)^2}$$

$$a[1 + (\omega_m T)^2] = 1 + (a\omega_m T)^2$$

$$a + a(\omega_m T)^2 = 1 + a^2(\omega_m T)^2$$

$$a - 1 = (\omega_m T)^2 [a^2 - a]$$

$$(a - 1) = (\omega_m T)^2 a(a - 1)$$

$$(\omega_m T)^2 = \frac{1}{a}$$

$$\omega_m^2 = \frac{1}{aT^2}$$

$$\omega_m = \frac{1}{T\sqrt{a}}$$

Now put this value in equation (ii),

$$\tan \phi_m = \frac{\omega T(a-1)}{1+a\omega^2 T^2} \Bigg|_{\omega=\omega_m} = \frac{1 \times T(a-1)}{T\sqrt{a} \left[ 1 + a \times \frac{1}{a} \right]}$$


$$\tan \phi_m = \frac{(a-1)}{2\sqrt{a}}$$

Maximum phase,  $\phi_m = \tan^{-1} \left[ \frac{(a-1)}{2\sqrt{a}} \right]$

**Q.2 (a) Solution:**

(i)  $G(s)H(s) = \frac{s+2}{(s+1)(s-1)}$

The Nyquist contour in s-plane is

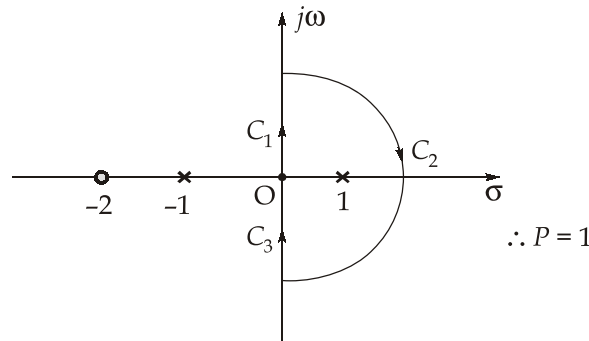

Nyquist plot in  $G(s)H(s)$  plane is obtained as below,

Corresponding to  $C_1 : s = j\omega ; \omega : 0 \rightarrow \infty$

$$G(j\omega)H(j\omega) = \frac{j\omega+2}{(j\omega+1)(j\omega-1)}$$

We have,  $M = \frac{\sqrt{\omega^2+4}}{\omega^2+1}$

and  $\phi = \tan^{-1} \left( \frac{\omega}{2} \right) - \tan^{-1}(\omega) - 180^\circ + \tan^{-1}(\omega)$

Angular frequency	M	$\angle G(j\omega)H(j\omega)$
$\omega = 0^+$	2	$-180^\circ$
$\omega = \infty^+$	0	$-90^\circ$

Corresponding to  $C_3 : s = -j\omega ; \omega: \infty \rightarrow 0$

$$G(-j\omega)H(-j\omega) = \frac{2 - j\omega}{(1 - j\omega)(-1 - j\omega)}$$

Here, 
$$M = \frac{\sqrt{4 + \omega^2}}{(\omega^2 + 1)}$$

and 
$$\phi = -\tan^{-1}\left(\frac{\omega}{2}\right) + \tan^{-1}(\omega) - 180^\circ - \tan^{-1}(\omega)$$

Angular frequency	M	$\angle G(j\omega)H(j\omega)$
$\omega = 0^-$	2	$-180^\circ$
$\omega = \infty^-$	0	$-270^\circ$

Corresponding to  $C_2 :$


$$G(s)H(s) = \lim_{R \rightarrow \infty} R e^{j\theta}; \theta \text{ varies from } +90^\circ \text{ to } -90^\circ$$

So, 
$$G(s)H(s) = \lim_{R \rightarrow \infty} \frac{(R e^{j\theta} + 2)}{(R e^{j\theta} + 1)(R e^{j\theta} - 1)}$$

$$G(s)H(s) = \lim_{R \rightarrow \infty} \frac{1}{R} e^{-j\theta}$$

Thus,  $M = 0 ; \phi = -\theta$  and thus, varies from  $-90^\circ$  to  $90^\circ$ .

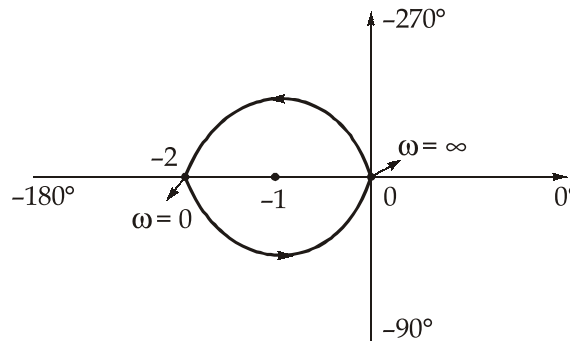The Nyquist plot in  $G(s)H(s)$  plane is obtained as below:



Number of encirclement, of  $(-1 + j0)$  point in anticlockwise direction ( $N$ ) = 1

Number of open loop poles on right half of  $s$ -plane ( $P$ ) = 1

So, 
$$N = P - Z$$

or 
$$Z = 0$$

where,  $Z$  is the number of closed loop poles on the right hand side of  $s$ -plane. Thus, the closed loop system is stable.

(ii) The observability matrix for a control system is given by,

$$Q_0 = [C^T A^T C^T \dots (A^T)^{n-1} C^T]$$

where  $n$  = number of states = 3 (given). We have,

$$A = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -6 & -11 & -6 \end{bmatrix}$$

$$A^T = \begin{bmatrix} 0 & 0 & -6 \\ 1 & 0 & -11 \\ 0 & 1 & -6 \end{bmatrix}$$

$$C^T = \begin{bmatrix} 1 \\ 1 \\ 0 \end{bmatrix}$$

$$A^T C^T = \begin{bmatrix} 0 \\ 1 \\ 1 \end{bmatrix}$$

$$A^T(A^T C^T) = \begin{bmatrix} -6 \\ -11 \\ -5 \end{bmatrix}$$

$$\text{Observability Matrix, } Q_0 = \begin{bmatrix} 1 & 0 & -6 \\ 1 & 1 & -11 \\ 0 & 1 & -5 \end{bmatrix}$$

$$\begin{aligned} |Q_0| &= 1[(1 \times -5) - (1 \times -11) - 0 + (-6)(1 - 0)] \\ &= -5 + 11 - 6 = 0 \end{aligned}$$

Since determinant is zero, rank is not 3 and hence, the system is not completely observable.

The roots of the characteristic equation are given by  $|\lambda I - A| = 0$  i.e.

$$\begin{vmatrix} \lambda & -1 & 0 \\ 0 & \lambda & -1 \\ 6 & 11 & \lambda+6 \end{vmatrix} = 0$$

$$\Rightarrow \lambda^3 + 6\lambda^2 + 11\lambda + 6 = 0$$

$$\Rightarrow (\lambda + 1)(\lambda + 2)(\lambda + 3) = 0$$

Thus, Eigen values are -1, -2 and -3.

The Vandermonde matrix formed by the eigen values is,

$$M = \begin{bmatrix} 1 & 1 & 1 \\ -1 & -2 & -3 \\ 1 & 4 & 9 \end{bmatrix} = \text{Vandermonde matrix}$$

$$X = CM = [1 \ 1 \ 0] \begin{bmatrix} 1 & 1 & 1 \\ -1 & -2 & -3 \\ 1 & 4 & 9 \end{bmatrix} = [0 \ -1 \ -2]$$

$$y = CMZ = [0 \ -1 \ -2] \begin{bmatrix} z_1 \\ z_2 \\ z_3 \end{bmatrix}$$

$z_1(t)$  is not observable, a mode due to eigen value  $\lambda = -1$ .

**Q.2 (b) Solution:**

Pre-fault,  $z_{pre} = j0.3 + (j0.55) \parallel (j0.55) + j0.15 = j0.725 \text{ pu}$

Equivalent circuit during fault,

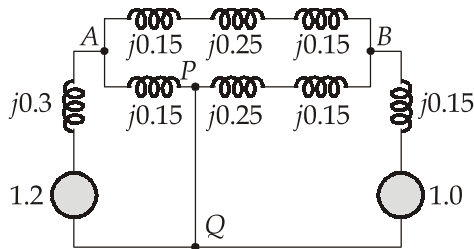


Fig. (i)


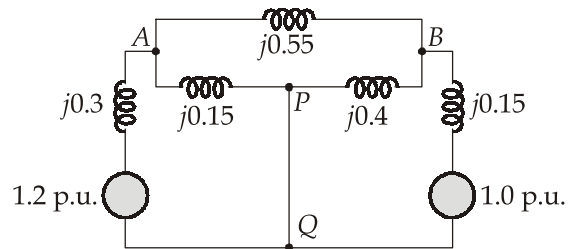


Fig. (ii)

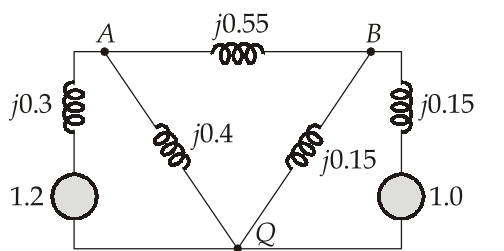

( $\Delta$  -  $Y$ ) Transformation  
Fig. (iii)


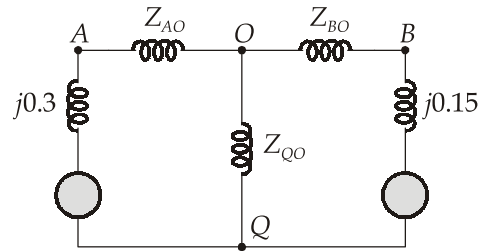


Fig. (iv)

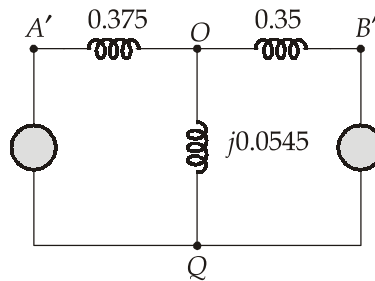
$$Z_{AO} = \frac{Z_{AB} \times Z_{AQ}}{Z_{AB} + Z_{AQ} + Z_{BQ}} = \frac{j0.15 \times j0.55}{j0.15 + j0.55 + j0.4} = j0.075$$



( $\Delta$  -  $\Upsilon$ ) Transformation

$$Z_{BO} = \frac{Z_{AB} \times Z_{BQ}}{Z_{BA} + Z_{BQ} + Z_{QA}} = j0.2$$
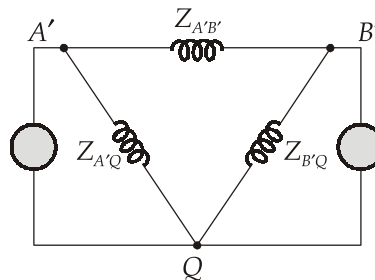
$$Z_{QO} = \frac{Z_{QA} \times Z_{QB}}{Z_{QA} + Z_{QB} + Z_{AB}} = j0.0545$$



$$Z_{A'B'} = \frac{j0.375 \times j0.35 + j0.35 \times j0.0515 + j0.0545 \times i}{j0.0545}$$

$$= j3.133 \text{ p.u.}$$

$$\text{During fault, } z_f = j3.133 \text{ pu} = Z_{A'B'}$$


$$\text{Post fault } z_{\text{post}} = j0.3 + j0.15 + j0.55 = j1.0 \text{ pu}$$

Maximum power output is  $\frac{E_1 E_2}{X}$

$$\text{Before fault } P_{\text{pre(max)}} = \frac{1.2 \times 1.0}{0.725} = 1.66 \text{ pu}$$

$$\text{During fault } P_{f(\text{max})} = \frac{1.2 \times 1.0}{3.133} = 0.383 \text{ pu}$$
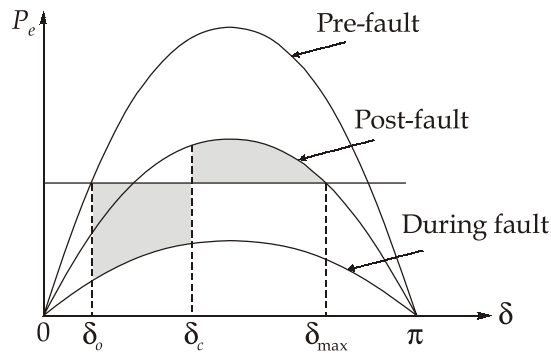
$$\text{Post fault } P_{\text{post(max)}} = \frac{1.2 \times 1.0}{1} = 1.2 \text{ pu}$$



Using equal - area criterion,  $\int_{\delta_0}^{\delta_{\max}} P_e d\delta = 0$

$$\delta_o = \sin^{-1} \left[ \frac{P_e}{P_{\text{pre(max)}}} \right] = \sin^{-1} \left[ \frac{1}{1.66} \right]$$

$$= 37.17^\circ \text{ or } 0.648 \text{ rad}$$

$$\text{Ratio, } r_1 = \frac{P_{f(\text{max})}}{P_{\text{pre(max)}}} = \frac{0.383}{1.66} = 0.23$$

$$r_2 = \frac{P_{\text{post(max)}}}{P_{\text{pre(max)}}} = \frac{1.2}{1.66} = 0.725$$

$$\delta_m = \pi - \sin^{-1} \left[ \frac{P_e}{P_{\text{pre(max)}}} \right] = \sin^{-1} \left( \frac{1}{1.2} \right)$$

$$= 123.6^\circ \text{ or } 2.157 \text{ rad}$$

$$\delta_c = \cos^{-1} \left[ \frac{\sin \delta_o (\delta_m - \delta_o) + r_2 \times \cos \delta_m - r_1 \cos \delta_o}{r_2 - r_1} \right]$$

$$= \cos^{-1} (0.66) = 48.7^\circ \text{ or } 0.85 \text{ rad}$$

**Q.2 (c) Solution:**

- (i) Using the open-loop poles and zeros, we represent the open-loop system whose root locus is given as

$$G(s)H(s) = \frac{k(s-3)(s-5)}{(s+1)(s+2)} = \frac{k(s^2 - 8s + 15)}{(s^2 + 3s + 2)}$$

But for all points along the root locus,

$$kG(s)H(s) = -1, \text{ and along the real axis, } s = \sigma$$

$$\text{Hence, } \frac{k(\sigma^2 - 8\sigma + 15)}{(\sigma^2 + 3\sigma + 2)} = -1$$

$$k = \frac{-(\sigma^2 + 3\sigma + 2)}{(\sigma^2 - 8\sigma + 15)}$$

$$\text{For break points, } \frac{dk}{d\sigma} = 0$$

$$\frac{dk}{d\sigma} = \frac{-[(2\sigma + 3)(\sigma^2 - 8\sigma + 15) - (\sigma^2 + 3\sigma + 2)(2\sigma - 8)]}{(\sigma^2 - 8\sigma + 15)^2} = 0$$

$$\frac{dk}{d\sigma} = \frac{11\sigma^2 - 26\sigma - 61}{(\sigma^2 - 8\sigma + 15)^2} = 0$$

$$11\sigma^2 - 26\sigma - 61 = 0$$

$$\sigma = \frac{26 \pm \sqrt{26^2 + 4 \times 61 \times 11}}{2 \times 11}$$

$$\therefore \sigma = -1.45; 3.82$$

\(\therefore\) The breakaway point is,

$$\sigma_p = -1.45$$

The break-in point,  $\sigma_z = 3.82$

$$\text{(ii) Transfer function} = \frac{Y(s)}{U(s)} = \frac{10(s+1)}{s(s+1)(s+5)+10} = \frac{10(s+1)}{s^3+6s^2+5s+10}$$

Transfer function decouposition,

$$0(s) \rightarrow \frac{10}{s^3+6s^2+5s+10} X(s) \rightarrow (s+1) \rightarrow Y(s)$$

$$\frac{Y(s)}{U(s)} = \frac{10}{s^3+6s^2+5s+10}$$

$$\text{and } Y(s) = (s+1)X(s)$$

$$X(s)(s^3+6s^2+5s+10) = 10 U(s)$$

\(\downarrow\uparrow\) I.L.T.

$$\frac{d^3x}{dt^3} + \frac{6d^2x}{dt^2} + 5\frac{dx}{dt} + 10x = 10u \quad \dots(i)$$

$$\text{and } Y(s) = (s+1)X(s)$$

\(\downarrow\uparrow\) I.L.T.

and 
$$y = \frac{dx}{dt} + x \quad \dots(\text{ii})$$

Let, 
$$x = x_1 \quad \dots(\text{iii})$$

$$\dot{x}_1 = \dot{x} = x_2 \quad \dots(\text{iii})$$

$$\dot{x}_2 = \ddot{x} = x_3 \quad \dots(\text{iv})$$

$$\dot{x}_3 = \ddot{\ddot{x}}$$

Putting the above values in equation (i) and (ii), we get

$$\dot{x}_3 = -10x_1 - 5x_2 - 6x_3 + 104 \quad \dots(\text{v})$$

and 
$$y = x_2 + x_1 \quad \dots(\text{vi})$$

Now from equation (iii), (vi), (v) and (vi)


$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \\ \dot{x}_3 \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -10 & -5 & -6 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 104 \end{bmatrix} u$$

$$y = \begin{bmatrix} 1 & 1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

**Q.3 (a) Solution:**

Minimum no. of flip-flops required = 3

**Sequence diagram:**

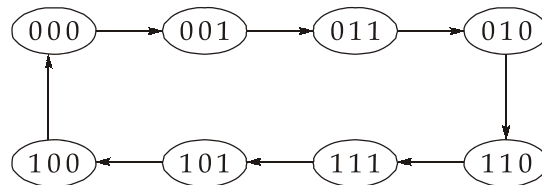

**Excitation table:**

Present State			Next State			Required Excitations					
$Q_2$	$Q_1$	$Q_0$	$Q_2^+$	$Q_1^+$	$Q_0^+$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	1	0	X	1	X	X	0
0	1	1	0	1	0	0	X	X	0	X	1
0	1	0	1	1	0	1	X	X	0	0	X
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	1	0	1	X	0	X	1	X	0
1	0	1	1	0	0	X	0	0	X	X	1
1	0	0	0	0	0	X	1	0	X	0	X

**Minimization**

**K-Map for  $J_2$**

$Q_1Q_0$	00	01	11	10
$Q_2$				1
0				1
1	X	X	X	X

$$J_2 = Q_1\bar{Q}_0$$

**K-Map for  $K_2$**

$Q_1Q_0$	00	01	11	10
$Q_2$				
0	X	X	X	X
1	1			

$$K_2 = \bar{Q}_1\bar{Q}_0$$

**K-Map for  $J_1$**

$Q_1Q_0$	00	01	11	10
$Q_2$				
0		1	X	X
1			X	X

$$J_1 = \bar{Q}_2Q_0$$

**K-Map for  $K_1$**

$Q_1Q_0$	00	01	11	10
$Q_2$				
0	X	X		
1	X	X	1	

$$K_1 = Q_2Q_0$$

**K-Map for  $J_0$**

$Q_1Q_0$	00	01	11	10
$Q_2$				
0	1	X	X	
1		X	X	1

$$J_0 = \bar{Q}_2\bar{Q}_1 + Q_2Q_1$$

$$J_0 = Q_2 \odot Q_1$$


**K-Map for  $K_0$**

$Q_1Q_0$	00	01	11	10
$Q_2$				
0	X		1	X
1	X	1		X


$$K_0 = Q_1\bar{Q}_2 + Q_2\bar{Q}_1$$

$$K_0 = Q_2 \oplus Q_1$$

**Logic Circuit:**

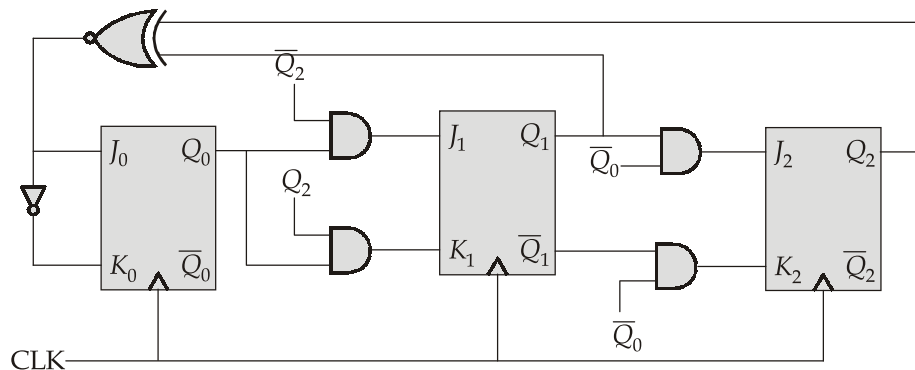

**Q.3 (b) Solution:**

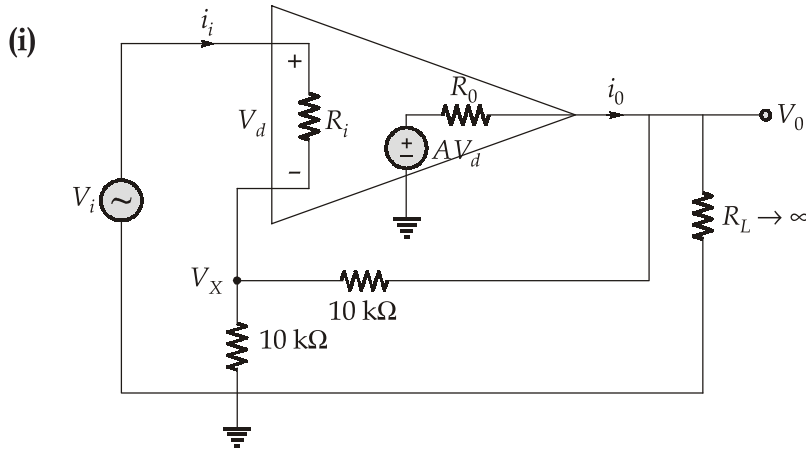

$$V_X = V_0 \cdot \frac{10}{10+10} = \frac{V_0}{2}$$

$$V_d = V_i - V_X = V_i - \frac{V_0}{2} \quad \dots(i)$$

$$\therefore V_0 = (A_v V_d) \cdot \frac{20}{20 + R_0} = A_v \left( V_i - \frac{V_0}{2} \right) \cdot \frac{20}{21}$$

$$\frac{V_0}{A_v} = \left( V_i - \frac{V_0}{2} \right) \frac{20}{21}$$

Given :  $A \rightarrow \infty$

$$0 = V_i - \frac{V_0}{2}$$

$$V_i = \frac{V_0}{2}$$

Hence,  $\frac{V_0}{V_i} = 2$

i.e.,  $A_f = 2$

(ii) We have;  $V_0 = 11 \sin \omega t \text{ V}$


$\therefore A_f = \frac{V_0}{V_i}$

$$V_i = \frac{V_0}{A_f} = \frac{11 \sin \omega t}{2} = 5.5 \sin \omega t \text{ V}$$

but,  $V_d = V_i - \frac{V_0}{2} = 5.5 \sin \omega t - 5.5 \sin \omega t = 0$

Hence, 
$$i_i = \frac{V_d}{R_i} = 0$$
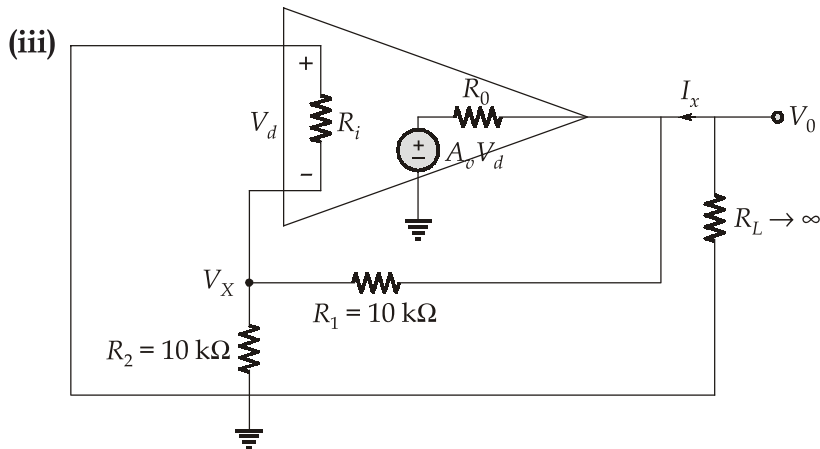
$$\therefore R_{if} = \frac{V_i}{i_i} = \text{Infinite}$$



Here, 
$$V_d = 0 - V_x = -\frac{V_o}{2}$$

KCL at output Node:

$$I_x = \frac{V_o - A_v V_d}{R_o} + \frac{V_o}{R_1 + R_2}$$

$$I_x = \frac{V_o - A_v \left( -\frac{V_o}{2} \right)}{R_o} + \frac{V_o}{R_1 + R_2}$$

$$I_x = \frac{V_o \left( 1 + \frac{A_v}{2} \right)}{R_o} + \frac{V_o}{R_1 + R_2}$$

$$I_x = V_o \left[ \frac{1 + \frac{A_v}{2}}{R_o} + \frac{1}{R_1 + R_2} \right]$$


$$\frac{V_o}{I_x} = \left[ \frac{R_o}{1 + A_v/2} \right] \parallel \left[ \frac{1}{R_1 + R_2} \right]$$

$$\therefore A_v \rightarrow \infty$$

$$R_{of} = \frac{V_o}{I_x} = R_1 + R_2 = 10 + 10 = 20 \text{ k}\Omega$$

**Q.3 (c) Solution:**

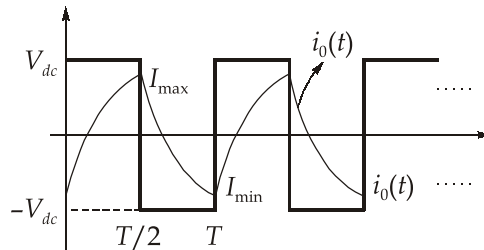(i) Waveform of steady state load current,



$$i_0(t) = \begin{cases} \frac{V_{dc}}{R} + \left( I_{\min} - \frac{V_{dc}}{R} \right) e^{-t/\tau} & 0 < t < \frac{T}{2} \quad \dots(i) \\ \frac{-V_{dc}}{R} + \left( I_{\max} + \frac{V_{dc}}{R} \right) e^{-\frac{(t-T/2)}{2}} & \frac{T}{2} < t < T \quad \dots(ii) \end{cases}$$

at  $t = \frac{T}{2}$ ,  $i_0\left(\frac{T}{2}\right) = I_{\max}$

$$I_{\max} = \frac{V_{dc}}{R} + \left( I_{\min} - \frac{V_{dc}}{R} \right) e^{-(T/2\tau)}$$

by symmetry,  $I_{\min} = -I_{\max}$

Substitute  $-I_{\max}$  for  $I_{\min}$  and solving for

$$I_{\max} = -I_{\min} = \frac{V_{dc}}{R} \left[ \frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}} \right]$$

From given data:

$$T = \frac{1}{f} = \frac{1}{60} = 0.0167 \text{ sec}$$

$$\tau = \frac{L}{R} = \frac{0.025}{10} = 0.0025 \text{ sec}$$

$$\frac{T}{2\tau} = 3.33$$

$$I_{\max} = -I_{\min} = \frac{100}{10} \left[ \frac{1 - e^{-3.33}}{1 + e^{-3.33}} \right] = 9.31 \text{ A}$$

From equation (i),

$$i_0(t) = \frac{100}{10} + \left( -9.31 - \frac{100}{10} \right) e^{-t/0.0025}$$

$$= (10 - 19.31e^{-t/0.0025})\text{A} \quad 0 < t < \frac{1}{120}$$

$$= \left( -10 + 19.31e^{-\frac{(t-0.0085)}{0.0025}} \right)\text{A} \quad \frac{1}{120} < t < \frac{1}{60}$$

(ii) Power is computed from  $I_{\text{rms}}^2 R$ , where  $I_{\text{rms}}$  is computed as

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i_0^2(t) dt}$$

$$= \sqrt{\frac{2}{T} \int_0^{T/2} \left[ \frac{V_{dc}}{R} + \left( I_{\text{min}} - \frac{V_{dc}}{R} \right) e^{-t/\tau} \right]^2 dt}$$

$$= \sqrt{\frac{1}{1/120} \int_0^{1/120} \left[ (10 - 19.31)e^{-t/0.0025} \right]^2 dt}$$

$$= 6.64 \text{ A}$$


Power absorbed by the load is

$$P = I_{\text{rms}}^2 R = (6.64)^2 \times (10) = 441 \text{ W}$$

(iii) Average source current can also be computed by equating source and load power

$$I_s = \frac{P_{dc}}{V_{dc}} = \frac{441}{100} = 4.41 \text{ A}$$

**Q.4 (a) Solution:**  
**(i)**

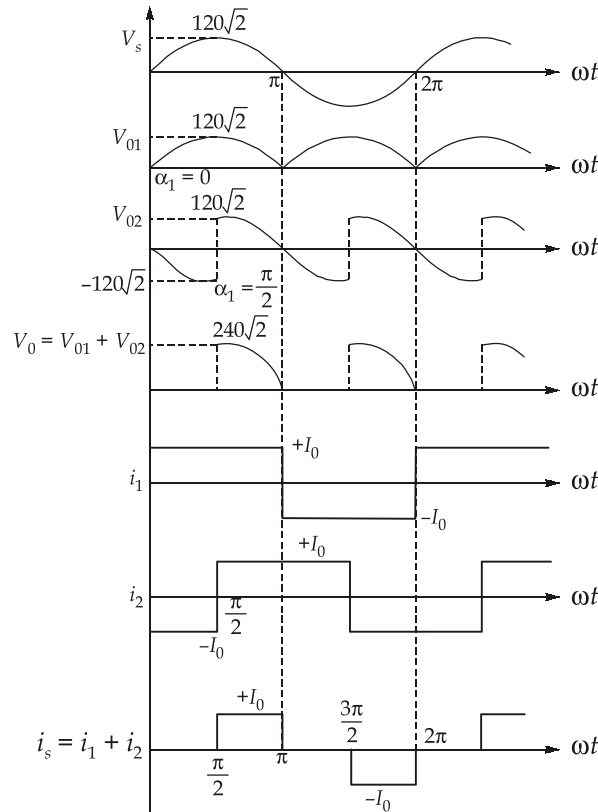

**(ii)** Average output voltage,  $V_o = \frac{2V_m}{\pi}(1 + \cos \alpha_2) = \frac{2 \times 120\sqrt{2}}{\pi} = 108.04 \text{ V}$

RMS output voltage,  $V_{rms} = \sqrt{2}V_m \left[ \frac{1}{\pi} \left( \pi - \alpha_2 + \sin \frac{2\alpha_2}{2} \right) \right]^{1/2} = V_m = 169.71 \text{ V}$

Fundamental current,  $I_1 = I_o \frac{2\sqrt{2}}{\pi} \cos \frac{\pi}{4} = 0.6366 I_o, \quad \phi_1 = -\frac{\pi}{4}$

RMS current,  $I_{rms} = 0.7071 I_o$

$DF = \cos \phi_1 = 0.7071$

$PF = \frac{I_1}{I_{rms}} \times DF = 0.6366 \text{ (lagging)}$

$HF = \left[ \left( \frac{I_{rms}}{I_1} \right)^2 - 1 \right]^{1/2} = 0.4835$

## Q.4 (b) Solution:

$$\begin{aligned}
 \text{(i) 1.} \quad X(s) &= \frac{1}{s^2} \frac{d}{ds} \left[ \frac{e^{-3s}}{s} \right], \text{ROC: } \sigma > 0 \\
 &= \frac{1}{s^2} \left[ \frac{-3e^{-3s}s - 1e^{-3s}}{s^2} \right] \\
 &= \frac{-3}{s^3} e^{-3s} - \frac{e^{-3s}}{s^4}; \sigma > 0 \quad \dots\text{(i)}
 \end{aligned}$$

Using the Multiplication by power of 't' property,

$$t^n u(t) \iff \frac{n!}{s^{n+1}}, \sigma > 0$$

Put  $n = 2$ :  $t^2 u(t) \iff \frac{2!}{s^3} = \frac{2}{s^3}, \sigma > 0$

$$\frac{t^2}{2} \cdot u(t) \iff \frac{1}{s^3}, \sigma > 0$$

Using the time-shifting property of Laplace Transform,

$$\frac{-3(t-3)^2}{2} u(t-3) \iff \frac{-3e^{-3s}}{s^3}, \sigma > 0$$

Put  $n = 3$ :  $t^3 u(t) \iff \frac{3!}{s^4}, \sigma > 0$

$$\frac{t^3}{6} u(t) \iff \frac{1}{s^4}, \sigma > 0$$

Using the time-shifting property of Laplace Transform,

$$\frac{(t-3)^3}{6} u(t-3) \iff \frac{e^{-3s}}{s^4}, \sigma > 0$$

By applying inverse Laplace transform on (i), we get

$$x(t) = \frac{-3}{2} (t-3)^2 u(t-3) - \frac{(t-3)^3}{6} \cdot u(t-3)$$

2.

$$\begin{aligned}
 X(s) &= s \left[ \frac{1}{s^2} - \frac{e^{-s}}{s^2} - \frac{e^{-2s}}{s} \right], \text{ROC: } \sigma > 0 \\
 &= \frac{1}{s} - \frac{e^{-s}}{s} - e^{-2s}; \sigma > 0 \quad \dots\text{(ii)}
 \end{aligned}$$

We know that,  $u(t) \xLeftrightarrow{s} \frac{1}{s}, \sigma > 0$

Using the time-shifting property of Laplace Transform,

$$u(t-1) \xLeftrightarrow{s} \frac{e^{-s}}{s}, \sigma > 0$$

Also,  $\delta(t-2) \xLeftrightarrow{s} e^{-2s}$

By applying inverse Laplace transform on (ii), we get

$$\begin{aligned} x(t) &= u(t) - u(t-1) - \delta(t-2) \\ \text{(ii)} \quad h(n) &= \alpha^n u(n) \text{ with } |\alpha| < 1 \\ H(z) &= \frac{1}{1-\alpha z^{-1}}, \text{ ROC: } |z| > |\alpha| \end{aligned}$$

Considering the unit step input i.e.

$$\begin{aligned} x(n) &= u(n) \\ \therefore X(z) &= \frac{1}{1-z^{-1}}, \text{ ROC: } |z| > 1 \end{aligned}$$

We have,  $Y(z) = X(z) \cdot H(z)$

$$\begin{aligned} \therefore Y(z) &= \frac{1}{1-z^{-1}} \cdot \frac{1}{1-\alpha z^{-1}}, \text{ ROC: } |z| > 1 \\ &= \frac{A}{1-z^{-1}} + \frac{B}{1-\alpha z^{-1}} \end{aligned}$$

$$\therefore Y(z) = \frac{1}{1-z^{-1}} - \frac{\alpha}{1-\alpha z^{-1}}$$

$$\begin{aligned} \Rightarrow y(n) &= \frac{1}{1-\alpha} u(n) - \frac{\alpha}{1-\alpha} (\alpha)^n u(n) \\ &= \frac{1}{1-\alpha} u(n) - \frac{\alpha^{n+1}}{1-\alpha} u(n) \end{aligned}$$

$$\therefore y(n) = \frac{1-\alpha^{n+1}}{1-\alpha} u(n)$$

When  $n \rightarrow \infty$ ,

$$\alpha^{n+1} = 0 \quad (\because |\alpha| < 1)$$

$\therefore$  Step response of the system

$$y(n) = \frac{1}{1-\alpha} \text{ when } n \rightarrow \infty$$

## Q.4 (c) Solution:

Given,

$$A(s) = \frac{1000}{\left(1 + \frac{s}{10^4}\right) \left(1 + \frac{s}{10^5}\right)^2}$$

and feedback factor  $\beta$  is independent of frequency

We have,

$$\angle A(j\omega) = -\tan^{-1}\left(\frac{\omega}{10^4}\right) - 2 \tan^{-1}\left(\frac{\omega}{10^5}\right)$$

When phase shift is  $180^\circ$ , then

$$180^\circ = -\tan^{-1}\left(\frac{\omega}{10^4}\right) - 2 \tan^{-1}\left(\frac{\omega}{10^5}\right)$$

Using:

$$2 \tan^{-1}(x) = \tan^{-1}\left(\frac{2x}{1-x^2}\right)$$

We get,

$$-180^\circ = \tan^{-1}\left(\frac{\omega}{10^4}\right) + \tan^{-1}\left(\frac{2(\omega/10^5)}{1-(\omega/10^5)^2}\right)$$

Taking the tangent on both sides,

$$0 = \tan^{-1} \left( \frac{\frac{\omega}{10^4} + \frac{2\left(\frac{\omega}{10^5}\right)}{1 - \left(\frac{\omega}{10^5}\right)^2}}{1 - \left(\frac{\omega}{10^4}\right) \left(\frac{2\left(\frac{\omega}{10^5}\right)}{1 - \left(\frac{\omega}{10^5}\right)^2}\right)} \right)$$

$$\frac{1}{10^4} + \frac{2}{10^5} \frac{1}{1 - \left(\frac{\omega}{10^5}\right)^2} = 0$$

$$1 - \left(\frac{\omega}{10^5}\right)^2 = -0.2$$

$$\omega^2 = 1.2 \times 10^{10} \Rightarrow \omega = \omega_{pc} = 1.1 \times 10^5 \text{ rad/sec}$$

For oscillations to occur

$$|A(j\omega_{pc})\beta| \geq 1$$

$$\frac{10^3 \beta}{\sqrt{1 + \left(\frac{\omega_{pc}}{10^4}\right)^2} \left(1 + \left(\frac{\omega_{pc}}{10^5}\right)^2\right)} \geq 1$$

$$\frac{\beta 10^3}{(\sqrt{1 + 11^2})(1 + 1.1^2)} \geq 1$$

$\Rightarrow \beta \geq 0.0244$

**Section-B**


**Q.5 (a) Solution:**

(i) As switching frequency is in MHz range and desired ratings are small. MOSFET can be used as a switch because it has highest switching frequency and diode should be compatible. Therefore schottkey diode can be used.

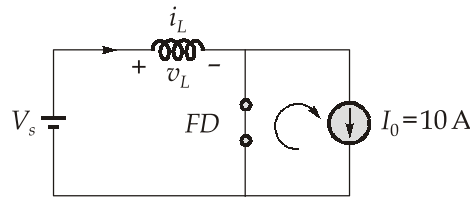(ii) Current through switch,

During  $0 < t < t_1$

The freewheeling diode is in on state, so the circuit will be



Applying KVL,  $V_L = L \frac{di_L}{dt}$


At  $t = t_1$

$i_L = I_0$

So freewheeling diode will stop conducting at

$$t = t_1 = \frac{LI_0}{V_s} = \frac{150 \times 10^{-6} \times 10}{20} = 75 \mu s$$

Now for  $t > t_1$

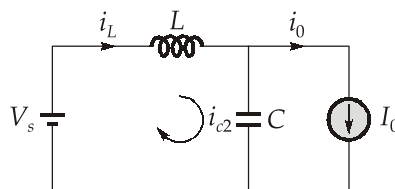

$i_L$  will be,

$$i_L = I_0 + i_{C2}$$

$$i_L = I_0 + I_p \sin \omega t$$


The peak current through switch will be

$$I_m = I_0 + I_p$$

$$I_m = I_0 + V_s \sqrt{\frac{C}{L}} = 10 + 20 \sqrt{\frac{0.05}{150}}$$

$$I_m = 10.37 \text{ A}$$


Current waveform will be

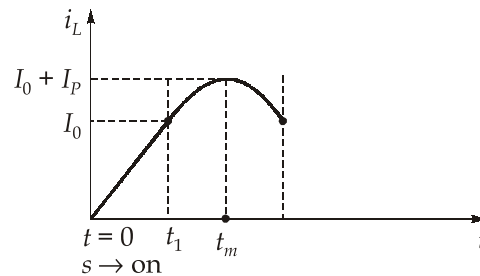

The peak value is obtained at  $t = t_m$

$$t_m = t_1 + \frac{\pi}{2} \sqrt{LC} = \left( 75 + \frac{\pi}{2} \sqrt{150 \times 0.05} \right) \times 10^{-6} = 79.3 \mu\text{s}$$

(iii) Capacitor voltage,

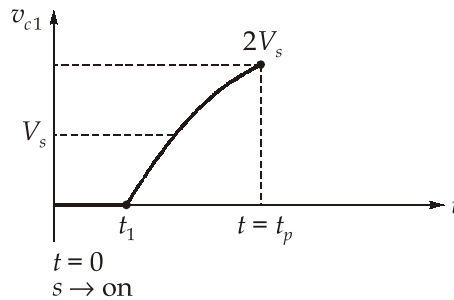

$v_c$  is given by,

$$v_c = 0; \text{ for } t < t_1$$

$$v_c = V_s(1 - \cos \omega t); \text{ for } t_1 < t < t_p$$

$v_c$  will be maximum at  $t = t_p$

$$t_p = t_1 + \pi \sqrt{LC}$$


$$t_p = \left( 75 + \pi \sqrt{150 \times 0.05} \right) \times 10^{-6} = 83.60 \mu\text{s}$$

Maximum capacitor voltage will be,

$$V_c \text{ max} = 2 V_s = 40 \text{ V}$$

**Q.5 (b) Solution:**

Type-A chopper

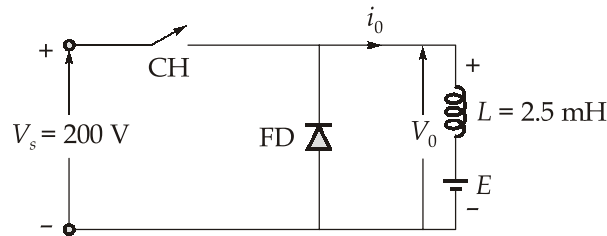

Average output voltage is given by,

$$V_0 = \alpha V_s$$

$$\alpha = \text{Duty ratio} = 0.25$$

$$V_0 = 0.25 \times 200 = 50 \text{ V}$$

As the average value of voltage drop across  $L$  is zero

$$E = V_0 = \alpha V_s = 50 \text{ V}$$

During  $T_{\text{on}}$ , the difference in source voltage  $V_s$  and load emf  $E$  appears across inductance  $L$ . Also during  $T_{\text{on}}$ , the current through  $L$  rises from  $I_{\text{min}}$  to  $I_{\text{max}}$ .

Therefore,

$$v_L = L \frac{di}{dt}$$

$$V_s - E = L \cdot \frac{\Delta I}{T_{\text{on}}}$$

$$T_{\text{on}} = \frac{L \cdot \Delta I}{(V_s - E)}$$

$$T_{\text{on}} = \frac{2.5 \times 8 \times 10^{-3}}{200 - 50}$$

and, duty ratio,  $\alpha = \frac{T_{\text{on}}}{T}$

$$\frac{\alpha}{T_{\text{on}}} = f$$

Chopping frequency,  $f = \frac{\alpha}{T_{\text{on}}}$

$$= \frac{0.25 \times 150}{2.5 \times 8 \times 10^{-3}} = 1.875 \text{ kHz}$$

## Q.5 (c) Solution:

As we know efficiency of a transformer

$$\eta = \frac{P_{\text{output}}}{P_{\text{input}}} = \frac{VI \cos \phi}{VI \cos \phi + 2P_c}$$

$$0.985 = \frac{125 \times 0.8}{125 \times 0.8 + P_{cu} + P_c}$$

$$(P_{cu})_{\text{at max efficiency}} = P_c = 761 \text{ W}$$

We know

$$P_{cu} \propto S^2$$

$$\Rightarrow \frac{(P_{cu})_{\text{rated}}}{(P_{cu})_{\text{max}}} = \frac{S_{\text{rated}}^2}{S_{\text{max}}^2}$$

$$\Rightarrow (P_{cu})_{\text{rated}} = \left(\frac{150}{125}\right)^2 \times 0.761 = 1.096 \text{ kW}$$

$$P_{h1} = P_{e1} = \frac{0.761}{2} = 0.3805 \text{ kW}$$

As we know

$$P_e \propto (f\beta_m)^2 \propto V^2 \text{ (same)}$$

$$P_h \propto f\beta_m^m = P_h \propto f \left(\frac{V}{f}\right)^n$$

$$P_h \propto \frac{1}{f^{n-1}} \Rightarrow P_h \propto \frac{1}{f^{1.6-1}} \Rightarrow P_h \propto \frac{1}{f^{0.6}}$$

$$\frac{P_{h1}}{P_{h2}} = \left(\frac{f_2}{f_1}\right)^{0.6}$$

$$\Rightarrow \frac{P_{h2}}{P_{h1}} = \left(\frac{50}{40}\right)^{0.6}$$

$$\Rightarrow P_{h2} = \left(\frac{50}{40}\right)^{0.6} \times 0.3805$$

$$\Rightarrow P_{h2} = 0.4352 \text{ kW}$$

$$\text{So, } P_{c2} = P_{h2} + P_{c2} = 0.4352 + 0.3805 = 0.816 \text{ kW}$$

$$\text{So, transformer efficiency, } \eta = \frac{150 \times 1}{150 \times 1 + P_{cu2} + P_{c2}} \times 100$$

$$\eta = \frac{150 \times 1}{150 \times 1 + 1.096 + 0.816} \times 100 = 98.74\%$$

**Q.5 (d) Solution:**

The delay produced by the given subroutine program can be calculated by determining the total number of T-states required to execute the given program.

Total number of T-states required to execute the program can be determined by analyzing the given program as shown in table.

	Instruction	No. of times executed	No. of T-state for one time execution
Delay	MVI B, 02H	1	7
LOOP 2	MVI C, FFH	1 × 2 = 2	7
LOOP 1	DCR C	255 × 2 = 510	4
	JNZ LOOP 1	254 × 2 = 508 ⇒ True 1 × 2 = 2 ⇒ False	10 ⇒ True 7 ⇒ False
	DCR B	2	4
	JNZ LOOP 2	1 ⇒ True 1 ⇒ False	10 ⇒ True 7 ⇒ False
	RET	1	10

⇒ Total delay produced by the program in terms of T-state can be given by,

$$\begin{aligned}
 \text{Delay} &= (1 \times 7T) + (2 \times 7T) + (510 \times 4T) + (508 \times 10T) \\
 &\quad + (2 \times 7T) + (2 \times 4T) + (10T + 7T) + 10T \\
 &= 7T + 14 T + 2040 T + 5080 T + 14T + 8T + 17T + 10T \\
 &= 7190 T
 \end{aligned}$$

Therefore, total delay produced =  $7190 \times \frac{1}{f} = \frac{7190}{2 \times 10^6} = 3595 \mu\text{sec}$

**Q.5 (e) Solution:**

Given: Open loop transfer function (OLTF) as  $G(s)H(s) = \frac{K}{(s+2)^2(s+3)}$

To determine the value of K:

(i) Position error constant  $K_p \geq 2$

As we know, position error constant  $K_p$  is given by

$$K_p = \lim_{s \rightarrow 0} G(s)H(s)$$

So, 
$$K_p = \lim_{s \rightarrow 0} \frac{K}{(s+2)^2(s+3)} = \frac{K}{12}$$

$$\begin{aligned} \text{As given,} & \quad K_p \geq 2 \\ \Rightarrow & \quad \frac{K}{12} \geq 2 \\ \text{So,} & \quad K \geq 24 \end{aligned}$$

(ii) Gain margin  $\geq 3$

$$G(s)H(s) = \frac{K}{(s^2 + 4s + 4)(s + 3)} = \frac{K}{s^3 + 7s^2 + 16s + 12}$$

Substituting  $s = j\omega$ ,

$$\Rightarrow G(j\omega)H(j\omega) = \frac{K}{-j\omega^3 - 7\omega^2 + j16\omega + 12} = \frac{K}{j(16\omega - \omega^3) + (12 - 7\omega^2)}$$

For imaginary part to be zero,

$$16\omega - \omega^3 = 0$$

$$\omega(16 - \omega^2) = 0$$

$$\Rightarrow \omega = 0, 4 \text{ rad/sec}$$

So,  $\omega = 4$  rad/sec is phase cross-over frequency,  $\omega_{pc}$ .

$$\text{Now, } G(j\omega)H(j\omega)|_{\omega=\omega_{pc}=4 \text{ rad/sec}} = \frac{K}{12 - 7(4)^2} = -\frac{K}{100}$$

$$|G(j\omega)H(j\omega)|_{\omega=\omega_{pc}} = \frac{K}{100}$$

$$\text{Gain margin, } GM = \frac{1}{|G(j\omega)H(j\omega)|_{\omega=\omega_{pc}}} = \frac{1}{K/100} = \frac{100}{K}$$

$$\text{As per question, } GM \geq 3$$

$$\Rightarrow \frac{100}{K} \geq 3 \Rightarrow K \leq \frac{100}{3} = 33.33$$

$$\Rightarrow K \leq 33.33$$

So, the value of  $K$  satisfying above both conditions is given by

$$24 \leq K \leq 33.33$$

### Q.6 (a) Solution:

Since  $R_{EE} = 200 \text{ k}\Omega$  is very high, the current through  $R_{EE}$  can be neglected. Thus, the collector current in  $Q_1$  and  $Q_2$  are


$$I_{C1} = I_{C2} = \frac{I}{2} = \frac{1}{2} = 0.5 \text{ mA}$$

The small signal parameters of the transistors can be obtained as below,

$$g_m = \frac{I_C}{V_T} = \frac{0.5 \times 10^{-3}}{25 \times 10^{-3}} = 20 \text{ m}\Omega$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{20} = 5 \text{ k}\Omega$$

**(i) Differential mode Analysis**

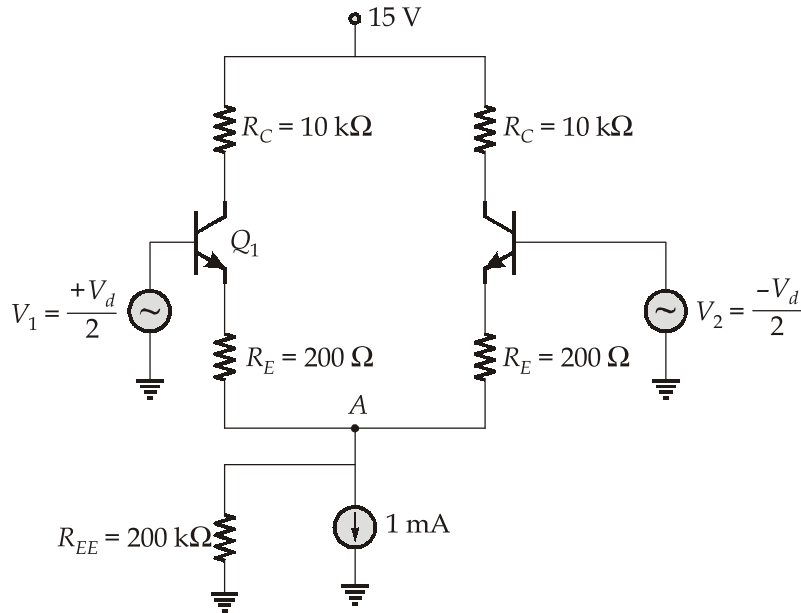


In differential mode analysis,

We assume input as

$$V_1 = \frac{V_d}{2} \text{ and } V_2 = \frac{-V_d}{2}$$

As the circuit is symmetric and  $V_1 = -V_2$ . In differential mode analysis, Node A can be assumed as AC ground.

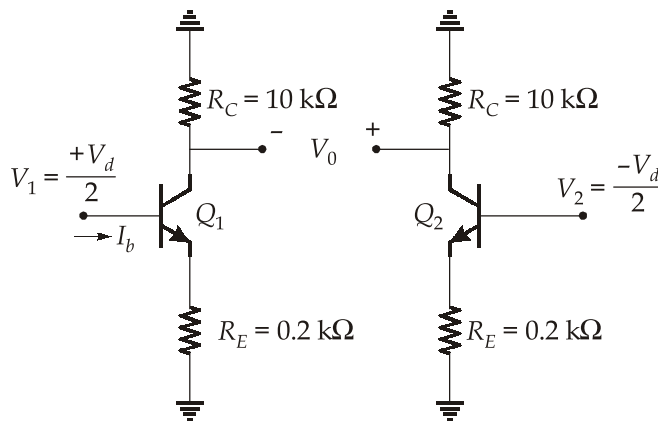For AC analysis, 1 mA current source is considered as open-circuit dc voltage source 15 V is considered as short circuit and since  $V_A = 0$ ,  $R_{EE}$  would be dead resistor.



Replacing  $Q_1$  with  $\pi$ -model.

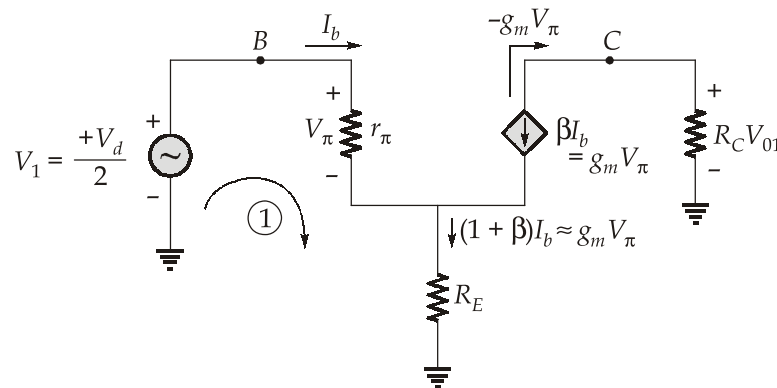


Fig. 1

KVL in base-emitter loop:

$$V_1 = I_b r_\pi + (1 + \beta) I_b R_E$$

$$\frac{V_1}{I_b} = r_\pi + (1 + \beta) R_E$$

We have,

$$V_1 = \frac{+V_d}{2}$$

$$\frac{V_d}{2} = r_\pi + (1 + \beta) R_E$$

$$R_{id} = \frac{V_d}{I_b} = 2[r_\pi + (1 + \beta) R_E]$$

$R_{id}$ : Differential input resistance

Substituting the values

$$R_{id} = 2[5 + 101 \times 0.2]$$

$$R_{id} \cong 50 \text{ k}\Omega$$

(ii) Differential voltage gain  $\left[ A_{DM} = \frac{V_0}{V_d} \right]$

From fig. (1),

$$V_{01} = -g_m V_\pi R_C \quad \dots(1)$$

and

$$V_1 = V_\pi + g_m V_\pi R_E \quad \dots(2)$$

From (1)  $\div$  (2), we get  $\frac{V_{01}}{V_1} = \frac{-g_m V_\pi R_C}{V_\pi (1 + g_m R_E)}$

$$\Rightarrow \frac{V_{01}}{V_1} = \frac{-g_m R_C}{1 + g_m R_E}$$

$$\text{As } V_1 = \frac{V_d}{2},$$

$$\frac{V_{01}}{\frac{V_d}{2}} = \frac{-g_m R_C}{1 + g_m R_E}$$

$$\frac{V_{01}}{V_d} = \frac{-g_m R_C}{2(1 + g_m R_E)}$$

$\frac{V_{01}}{V_d}$  : Differential gain when o/p is unbalanced

$$\text{Similarly when } V_2 = \frac{-V_d}{2}$$

$$\frac{V_{02}}{V_2} = \frac{-g_m R_C}{1 + g_m R_E}$$

$$\frac{V_{02}}{V_d} = \frac{g_m R_C}{2(1 + g_m R_E)}$$

$\frac{V_{01}}{V_d}$  and  $\frac{V_{02}}{V_d}$  are differential mode gain for unbalanced output or single ended output.

$\frac{V_0}{V_d}$  is difference mode gain for balanced output. We can write,

$$A_{DM} = \frac{V_0}{V_d} = \frac{V_{02}}{V_d} - \frac{V_{01}}{V_d}$$

$$\text{Hence, } A_{DM} = \frac{g_m R_C}{1 + g_m R_E}$$

Putting the values, we get

$$A_{DM} = \frac{20 \times 10}{1 + 20 \times 0.2} = 40$$


(iii) Common mode analysis:

We assume input as  $V_1 = V_2 = V_{CM}$

and Common mode gain,

$$A_{CM} = \frac{V_0}{V_{CM}} = \frac{V_{02} - V_{01}}{V_{CM}}$$

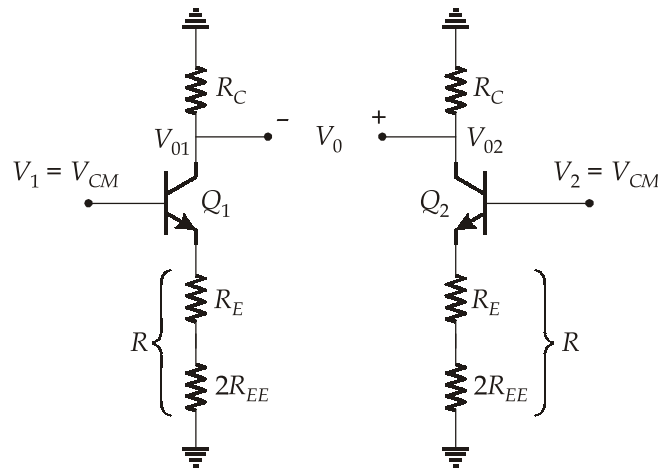In common mode analysis, we apply symmetry property



$Q_1$  and  $Q_2$  are CE amplifier with unbypassed emitter resistance  $R$ .

$$\frac{V_{01}}{V_{CM}} = \frac{V_{02}}{V_{CM}} = \frac{-g_m R_C}{1 + g_m R}$$

$$= \frac{-g_m R_C}{1 + g_m (R_E + 2R_{EE})}$$

$$\frac{V_{01}}{V_{CM}} \cong \frac{V_{02}}{V_{CM}} \cong \frac{-R_C}{R_E + 2R_{EE}}$$

$$A_{CM} = \frac{V_0}{V_{CM}} = \frac{V_{02} - V_{01}}{V_{CM}}$$

$$A_{CM} = \frac{V_{02}}{V_{CM}} - \frac{V_{01}}{V_{CM}}$$

If  $R_C$  values are perfectly equal, then  $A_{CM} = 0$ .

In the question, it is given that there is some mismatch. Hence, common mode gain of differential amplifier becomes non-zero, because of mis-match in the value of  $R_C$ .

Now,

$$\frac{V_{02}}{V_{CM}} = \frac{-R_{C2}}{R_E + 2R_{EE}} \text{ and } \frac{V_{01}}{V_{CM}} = \frac{-R_{C1}}{R_E + 2R_{EE}}$$

Common mode gain in worst case is equal to maximum possible common mode gain.  $A_{CM}$  is maximum if

$$R_{C1} = R_C + \Delta R$$

$$R_{C2} = R_C - \Delta R$$

$$A_{CM} = \frac{R_{C1} - R_{C2}}{R_E + 2R_{EE}}$$

$$A_{CM} = \frac{2\Delta R}{R_E + 2R_{EE}}$$

Given,

$$\Delta R = 1\% \text{ of } R_C$$

$$= 1\% \text{ of } 10 \text{ k}\Omega$$

$$= 0.1 \text{ k}\Omega$$

$$A_{CM} = \frac{2 \times 0.1}{0.2 + 2 \times 200}$$

$$A_{CM} \cong 0.5 \times 10^{-3}$$

$$(iv) \quad (CMRR)_{dB} = 20 \log_{10} \left| \frac{A_{DM}}{A_{CM}} \right|$$

$$= 20 \log_{10} \left| \frac{40}{0.5 \times 10^{-3}} \right|$$

$$= 98 \text{ dB}$$

Hence, CMRR is 98 dB.

#### Q.6 (b) Solution:

(i) For sinusoidal signal  $m(t) = A \cos(2\pi ft)$ . To avoid slope overload distortion,

$$\frac{\sigma}{T_s} \geq \left| \frac{d}{dt} m(t) \right|_{\max} = 2\pi f A_{\max} = \omega A_{\max}$$

$$A_{\max} = \frac{\sigma f_s}{\omega}$$

or,

$$\sigma = \frac{\omega A_{\max}}{f_s} = \frac{2\pi \times 3.4 \times 10^3}{64000},$$

$$\sigma = 0.3337$$


$$(ii) \quad N_0 = \frac{\sigma^2 B}{3 f_s} = \frac{(0.3337)^2 (3.4 \times 10^3)}{3(64000)} = 0.00197$$

$$(iii) \text{ For sinusoidal signal, } S_0 = \frac{A^2}{2} = 0.5$$

$$SNR = \frac{S_0}{N_0} = \frac{0.5}{0.00197} = 253.80 = 24.04 \text{ dB}$$

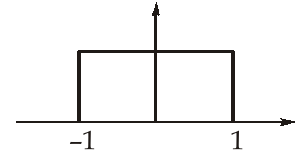(iv) For uniform distribution,  $S_0 = \frac{(1 - (-1))^2}{12} = \frac{1}{3}$

So,  $\frac{S_0}{N_0} = \frac{0.333}{0.00197} = 22.28 \text{ dB}$



(v) The minimum transmission bandwidth  $B_T$  for a baseband signal (using Nyquist criterion) is:

$$B_T = \frac{R_b}{2} = \frac{64 \text{ kHz}}{2} = 32 \text{ kHz}$$

**Q.6 (c) Solution:**

The sequence networks are shown in figure below:

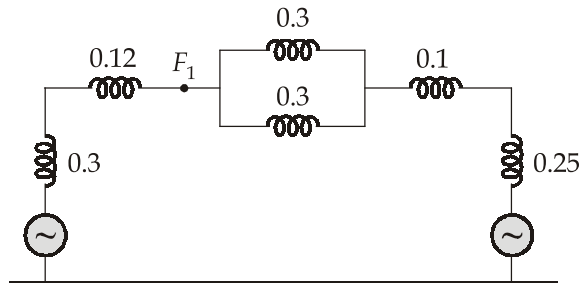


Fig. (a)

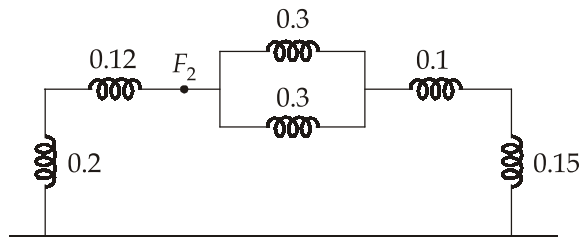


Fig. (b)

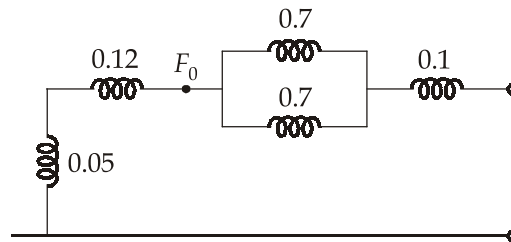


Fig. (c)

From the positive-sequence network of figure (a), the equivalent impedance upto the point of the fault is given by

$$\begin{aligned}
 Z_1 &= j \left[ (0.3 + 0.12) \parallel \left( 0.25 + 0.1 + \frac{0.3}{2} \right) \right] \\
 &= j [(0.42) \parallel (0.5)] = j \frac{0.42 \times 0.5}{0.42 + 0.5} = j0.22826 \text{ pu}
 \end{aligned}$$

From the negative-sequence network of Fig. (b), the equivalent impedance upto  $F$  is given by

$$\begin{aligned}
 Z_2 &= j \left[ (0.2 + 0.12) \parallel \left( 0.15 + 0.1 + \frac{0.3}{2} \right) \right] \\
 &= j(0.32) \parallel (0.4) = j \frac{0.32 \times 0.4}{0.32 + 0.4} = j0.1778 \text{ pu}
 \end{aligned}$$

From the zero-sequence network of Fig. (c), the equivalent impedance upto  $F$  is given by

$$Z_0 = j(0.05 + 0.12) = j0.17 \text{ pu}$$

**(i) LLG Fault at  $F$**

If phase  $a$  is assumed to be the reference phasor and phases  $b$  and  $c$  are shorted at the fault.

$$\begin{aligned}
 I_{a1} &= \frac{V_f}{Z_{a1} + \frac{Z_{a0}Z_{a2}}{Z_{a0} + Z_{a2}}} = \frac{1 \angle 0^\circ}{j \left( 0.22826 + \frac{0.17 \times 0.1778}{0.17 + 0.1778} \right)} \\
 &= -j3.1729 \text{ pu} = 3.1729 \angle -90^\circ \text{ pu}
 \end{aligned}$$

If we put  $Z_f = 0$  and  $Z_g = 0$  then by current division rule

$$\begin{aligned}
 I_{a0} &= -I_{a1} \frac{Z_{a2}}{Z_{a0} + Z_{a2}} = j \left( 3.1729 \times \frac{0.1778}{0.17 + 0.1778} \right) \\
 &= j1.622 \text{ pu} = 1.622 \angle 90^\circ \text{ pu}
 \end{aligned}$$

Check

$$\begin{aligned}
 I_a &= I_{a0} + I_{a1} + I_{a2} = j1.622 - j3.1729 + j1.551 \simeq 0 \\
 I_b &= I_{a0} + \alpha^2 I_{a1} + \alpha I_{a2} \\
 &= j1.622 + (1 \angle 240^\circ)(3.1729 \angle -90^\circ) + (1 \angle 120^\circ)(1.551 \angle 90^\circ)
 \end{aligned}$$

$$\begin{aligned}
 &= j1.622 + 3.1729 \angle 150^\circ + 1.551 \angle 210^\circ \\
 &= j1.622 - 2.7478 + j1.5864 - 1.3432 - j0.7755 \\
 &= -4.091 + j2.4729 \\
 I_c &= I_{a0} + \alpha I_{a1} + \alpha^2 I_{a2} \\
 &= j1.622 + (1 \angle 120^\circ)(3.1729 \angle -90^\circ) + (1 \angle 240^\circ)(1.551 \angle 90^\circ) \\
 &= j1.622 + 2.7478 + j1.5864 + 1.3432 - j0.7755 \\
 &= 4.091 + j2.4729 \\
 |I_b| &= |I_c| = \sqrt{(4.091)^2 + (2.4729)^2} = 4.78 \text{ pu}
 \end{aligned}$$

**(ii) LL Fault at F**

If the line-to-line fault is between phases  $b$  and  $c$ .

$$\begin{aligned}
 I_{a1} &= \frac{V_f}{Z_{a1} + Z_{a2}} = \frac{1 \angle 0^\circ}{j(0.22826 + 0.1778)} \\
 &= -j2.4627 \text{ pu} = 2.4627 \angle -90^\circ \text{ pu}
 \end{aligned}$$

The phase  $a$  negative-sequence current is given by

$$I_{a2} = -I_{a1} = +j2.4627 \text{ pu} = 2.4627 \angle 90^\circ \text{ pu}$$

The phase  $a$  fault current

$$I_a = I_{a0} + I_{a1} + I_{a2} = 0 - j2.4627 + j2.4627 = 0$$

The phase  $b$  fault current

$$\begin{aligned}
 I_b &= I_{a0} + \alpha^2 I_{a1} + \alpha I_{a2} \\
 &= 0 + (1 \angle 240^\circ)(2.4627 \angle -90^\circ) + (1 \angle 120^\circ)(2.4627 \angle 90^\circ) \\
 &= 2.4627 \angle 150^\circ + 2.4627 \angle 210^\circ \\
 &= -2.133 + j1.231 - 2.133 - j1.231 = -4.266 \text{ pu}
 \end{aligned}$$

The phase  $c$  fault current

$$\begin{aligned}
 I_c &= I_{a0} + \alpha I_{a1} + \alpha^2 I_{a2} \\
 &= 0 + (1 \angle 120^\circ)(2.4627 \angle -90^\circ) + (1 \angle 240^\circ)(2.4627 \angle 90^\circ) \\
 &= 2.4627 \angle 30^\circ + 2.4627 \angle 330^\circ \\
 &= 2.133 + j1.231 + 2.133 - j1.231 = 4.266 \text{ pu}
 \end{aligned}$$

Thus, it is calculated that

$$I_b = -I_c = -4.266 \text{ pu}$$

**Q.7 (a) Solution:**

Since the load is at the bus of plant 2, therefore, the line loss will not be affected by variation of  $P_2$ . Thus,

$$B_{12} = B_{21} = 0 \text{ and } B_{22} = 0$$

For a 2-plant system

$$P_L = P_1^2 B_{11} + P_2^2 B_{22} + 2P_1 P_2 B_{12}$$

When  $P_1 = 125 \text{ MW}$ ,  $P_L = 12.5 \text{ MW}$

$$\text{we have } 12.5 = (125)^2 B_{11} + 0 + 0$$

$$\text{or } B_{11} = \frac{12.5}{(125)^2} = 8 \times 10^{-4} \text{ MW}^{-1}$$

$$\text{Therefore, } P_L = 8 \times 10^{-4} P_1^2; \quad \frac{\partial P_L}{\partial P_1} = 16 \times 10^{-4} P_1$$

We are also given  $\lambda = 70 \text{ Rs/MWh}$ .

**(i) Use of coordinates equation**

The coordination equation for plant 1 is given by

$$\frac{dC_1}{dP_1} + \lambda \frac{\partial P_L}{\partial P_1} = \lambda$$

Substituting the values of  $\frac{dC_1}{dP_1}$ ,  $\lambda$  and  $\frac{\partial P_L}{\partial P_1}$  we have

$$0.25P_1 + 40 + 70 \times 16 \times 10^{-4} P_1 = 70$$

$$(0.25 + 0.112)P_1 = 30, P_1 = 82.8729 \text{ MW}$$

The coordination equation for plant 2 is given by

$$\frac{dC_2}{dP_2} + \lambda \frac{\partial P_L}{\partial P_2} = \lambda$$

$$\text{or } 0.20P_2 + 50 + 0 = 70, P_2 = 100 \text{ MW}$$

The line loss is given by

$$P_L = 8 \times 10^{-4} P_1^2 = 8 \times 10^{-4} \times (82.8729)^2 = 5.494 \text{ MW}$$

$$\begin{aligned} \text{Therefore, the total load, } P_R &= P_1 + P_2 - P_L \\ &= 82.8729 + 100 - 5.494 \\ &= 177.3789 \text{ MW} \end{aligned}$$

**(ii) Use of penalty factor**

The penalty factor for plant 1 is given by

$$L_1 = \frac{1}{1 - \frac{\partial P_L}{\partial P_1}} = \frac{1}{(1 - 16 \times 10^{-4} P_1)}$$

For optimal dispatch

$$L_1 \frac{dC_1}{dP_1} = \lambda; \quad \frac{1}{(1 - 16 \times 10^{-4} P_1)} \times (0.25 P_1 + 40) = 70$$

or  $0.25 P_1 + 40 = 70 - 70 \times 16 \times 10^{-4} P_1$

or  $P_1 = \frac{30}{0.25 + 0.112} = 82.8729 \text{ MW}$

Penalty factor for plant 2,

$$L_2 = \frac{1}{1 - \frac{\partial P_L}{\partial P_2}} = \frac{1}{1 - 0} = 1$$

For optimal dispatch,


$$L_2 \frac{dC_2}{dP_2} = \lambda; \quad 1 \times (0.20 P_2 + 50) = 70$$

$$P_2 = \frac{20}{0.20} = 100 \text{ MW}$$

It is seen that both the methods give identical results. This is due to the fact that the penalty factor has been derived from the coordination equation.

**Q.7 (b) Solution:****(i) Part 1:**

Given waveform of  $x(t)$  is

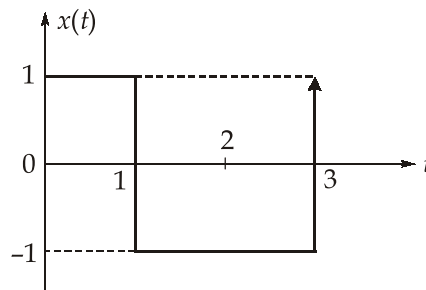

We can express  $x(t)$  as:

$$x(t) = u(t) - 2u(t - 1) + u(t - 3) + \delta(t - 3)$$


Let

$$z(t) = \int_{-\infty}^t x(\tau) d\tau$$

then

$$z(t) = \int_{-\infty}^t u(\tau) d\tau - 2 \int_{-\infty}^t u(\tau - 1) d\tau + \int_{-\infty}^t u(\tau - 3) d\tau + \int_{-\infty}^t \delta(\tau - 3) d\tau$$

$$z(t) = r(t) - 2r(t - 1) + r(t - 3) + u(t - 3)$$

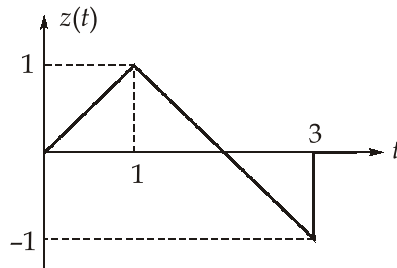

**Part 2:**

We can express  $y(t)$  as,


$$y(t) = u(t) - \sum_{n=1}^{\infty} \delta(t - n)$$

Let

$$f(t) = \int_{-\infty}^t y(\tau) d\tau$$

$$f(t) = \int_{-\infty}^t u(\tau) d\tau - \sum_{n=1}^{\infty} \left[ \int_{-\infty}^t \delta(\tau - n) d\tau \right]$$
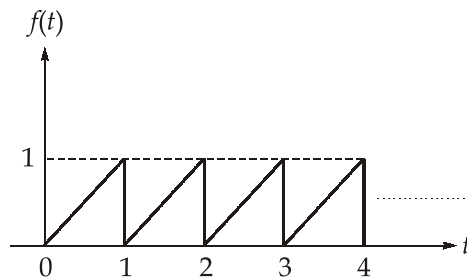
$$\begin{aligned} f(t) &= r(t) - \sum_{n=1}^{\infty} u(t - n) \\ &= r(t) - u(t - 1) - u(t - 2) - u(t - 3) - \dots \end{aligned}$$



(ii) Given : 
$$K_1 = \frac{1}{2}, K_2 = \frac{1}{4}$$

The transfer function of a lattice filter of order 'm' is given by

$$A_m(z) = A_{m-1}(z) + K_m z^{-m} A_{m-1}(z^{-1})$$

with initial condition,  $A_0(z) = 1$

We have, 
$$A_1(z) = A_0(z) + K_1 z^{-1} A_0(z^{-1}) = 1 + \frac{1}{2} z^{-1} \times 1$$

$$= 1 + \frac{1}{2} z^{-1} \quad (\because A_0(z) = 1; \text{ thus } A_0(z^{-1}) = 1)$$

$$A_2(z) = A_1(z) + K_2 z^{-2} A_1(z^{-1})$$

$$= \left(1 + \frac{1}{2} z^{-1}\right) + \frac{1}{4} z^{-2} \left(1 + \frac{1}{2} z\right)$$

$$\left(\because A_1(z^{-1}) = A_1(z) \Big|_{z \rightarrow z^{-1}} = 1 + \frac{1}{2} z\right)$$


$$= 1 + \frac{1}{2} z^{-1} + \frac{1}{4} z^{-2} + \frac{1}{8} z^{-1}$$

$$A_2(z) = 1 + \frac{5}{8} z^{-1} + \frac{1}{4} z^{-2}$$

We have, 
$$A_2(z) = \sum_{i=0}^2 a_2(i) z^{-i}$$

thus impulse response,
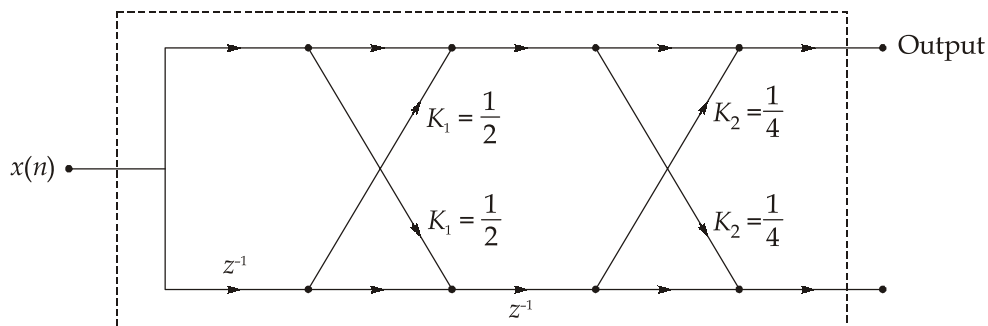
$$a_2(0) = 1, a_2(1) = \frac{5}{8}, a_2(2) = \frac{1}{4}$$



## Q.7 (c) Solution:

- (i) When  $\alpha$  is greater than  $90^\circ$ , then average output voltage is negative. If load circuit emf (DC source) is reserved, then this battery will feed power back to AC source.

$$V_0 = \frac{3V_{mL}}{\pi} \cos \alpha = I_0 R - E$$

$$\frac{3 \times \sqrt{2} \times 4160}{\pi} \times \cos 120^\circ = (I_0 \times 2) - 3000$$

$$I_0 = 95.5 \text{ A}$$

The power absorbed by the bridge and transferred back to the AC system

$$P_{ac} = I_0 V_0 = 95.5 \times (-2808.98) = 268.26 \text{ kW}$$

Power supplied by the DC source,

$$P_{dc} = I_0 V_{dc} = 95.5 \times 3000$$

$$P_{dc} = 286.5 \text{ kW}$$

- (ii) Hence this is a six pulse converter, the normalized harmonic voltage is given,

$$\frac{V_6}{V_m} = 0.28$$

$$V_6 = 0.28 \times V_m = 0.28 \times \sqrt{2} \times 4160 = 1647 \text{ V}$$

The peak to peak variation of 10 percent corresponds to a zero to peak amplitude of

$$0.05 \times 95.5 = 4.8 \text{ A}$$

$$Z_6 = \frac{V_6}{I_6} = \frac{1647}{4.8} = 343.125 \Omega$$

$$Z_6 = \sqrt{R^2 + (6\omega L)^2}$$

$$\frac{(343.125)^2 - 4}{(6 \times 2\pi \times 50)^2} = L^2$$

$$L = \sqrt{0.033135} = 0.18 \text{ H}$$

## Q.8 (a) Solution:

(i) Using Routh's array table,

$$\begin{array}{r}
 s^4 \quad \quad \quad b_0 \quad \quad \quad b_2 \quad b_4 \\
 s^3 \quad \quad \quad b_1 \quad \quad \quad b_3 \\
 s^2 \quad \quad \quad \frac{b_1 b_2 - b_0 b_3}{b_1} \quad \quad \quad b_4 \\
 s^1 \quad \quad \quad \frac{\left[ \frac{b_1 b_2 - b_0 b_3}{b_1} \right] b_3 - b_1 b_4}{\left[ \frac{b_1 b_2 - b_0 b_3}{b_1} \right]} \\
 s^0 \quad \quad \quad b_4
 \end{array}$$

For system to be stable, there should be no sign change in the first column of Routh Array. Thus, the stability conditions are given by

$$b_0 > 0; b_1 > 0; b_1 b_2 - b_0 b_3 > 0;$$

$$(b_1 b_2 - b_0 b_3) b_3 - b_1^2 b_4 > 0$$

and  $b_4 > 0$

(ii) For the given characteristic equation, Routh's Array can be drawn as below,

$$\begin{array}{r}
 s^5 \quad 1 \quad 1 \quad 4 \\
 s^4 \quad 1 \quad 1 \quad 4 \\
 \boxed{s^3 \quad 0(4) \quad 0(2)} \\
 s^2 \quad \frac{4-2}{4} = \frac{1}{2} \quad 4 \\
 s^1 \quad \frac{1-16}{0.5} = -30 \\
 s^0 \quad 4
 \end{array}$$

Using Auxiliary equation, we get

$$A(s) = s^4 + s^2 + 4 = 0$$

$$\frac{dA(s)}{ds} = 4s^3 + 2s$$

From the Routh-Hurwitz table, since sign change occurs in the first column of Routh Array. Hence, the system is unstable. Further, we conclude that

- two poles are in right side of s-plane [since there are two sign changes in the first column of Routh Array].

- four poles are complex in nature [as  $s^3$  row is zero].

Complex poles are given by:

$$s^4 + s^2 + 4 = 0 \Rightarrow s^2 = -0.5 \pm 1.936i = 2\angle\pm 104.48^\circ$$

We get  $s = \pm 1.414\angle\pm 52.24^\circ$ . Therefore,

$$s = (0.866 + 1.117i); (0.866 - 1.117i)$$

$$s = (-0.866 + 1.117i); (-0.866 - 1.117i)$$

Now,

the characteristic equation can be represented as

$$(s + a)(s^4 + s^2 + 4) = 0$$

$$s^5 + s^3 + 4s + as^4 + as^2 + 4a = 0$$

$$s^5 + as^4 + s^3 + as^2 + 4s + 4a = 0$$

and on comparing with the given characteristic equation, we get,  $a = 1$


Thus, Fifth pole lies at  $s = -a$  i.e. at

$$s = -1$$

Hence, poles are at

$$s = (0.866 + 1.117i), (0.866 - 1.117i), (-0.866 + 1.117i), (-0.866 - 1.117i) \text{ and } -1$$

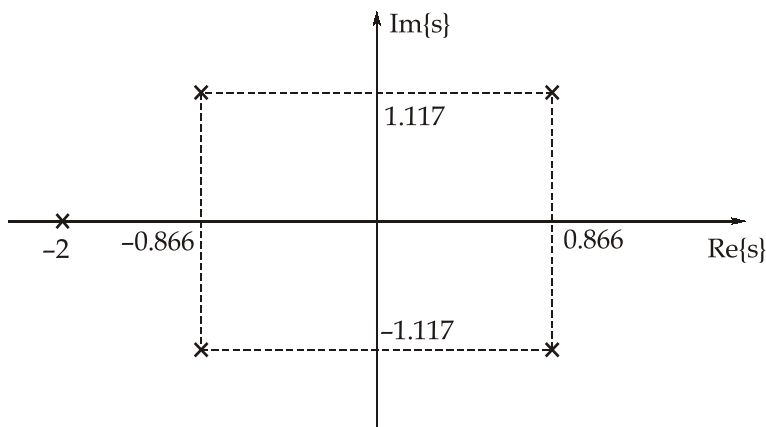Thus, the poles can be represented in the s-plane as below:



### Q.8 (b) Solution:

(i) 1. Given information are:

(a)  $x(n)$  is right-sided.

(b)  $X(z)$  has single pole.

(c)  $x(0) = 4, x(2) = \frac{1}{4}$

From (b), 
$$X(z) = \frac{K}{1-az^{-1}}$$

By applying inverse z-transform

$$x(n) = K(a)^n u(n) \quad \dots(i)$$

as  $x(n)$  is right sided.

Put  $n = 0$ :  $x(0) = K = 4$  ...from information (c)

$\Rightarrow K = 4$

Put  $n = 2$ :

$$x(2) = K \cdot a^2 = \frac{1}{4}$$

$$a^2 = \frac{1}{4K} = \frac{1}{16}$$

$\Rightarrow a = \frac{1}{4}$

From (i),  $x(n) = K(a)^n u(n)$

$$= 4 \left( \frac{1}{4} \right)^n u(n)$$

2. Given information are:

(a) Poles:  $P_1 = \frac{1}{4}, P_2 = -1$

(b) ROC includes  $|z| = \frac{1}{2}$

(c)  $x(1) = 1, x(-1) = 1$

From (a), 
$$X(z) = \frac{K}{(z-P_1)(z-P_2)}$$

$$= \frac{K}{\left(z - \frac{1}{4}\right)(z+1)} = \left[ \frac{K \cdot z^2}{\left(z - \frac{1}{4}\right)(z+1)} \right] z^{-2}$$

$$= \left[ \frac{K}{\left(1 - \frac{1}{4}z^{-1}\right)(1+z^{-1})} \right] z^{-2}$$

$\Rightarrow X(z) = F(z)z^{-2} \quad \dots(i)$

where,

$$F(z) = \frac{K}{\left(1 - \frac{1}{4}z^{-1}\right)(1 + z^{-1})}$$

$$F(z) = K \left[ \frac{A}{1 - \frac{1}{4}z^{-1}} + \frac{B}{1 + z^{-1}} \right]$$

Residue calculation:

$$A = \left( \frac{1}{1 + z^{-1}} \right) \Big|_{z^{-1}=4} = \frac{1}{1+4} = \frac{1}{5}$$

$$B = \left( \frac{1}{1 - \frac{1}{4}z^{-1}} \right) \Big|_{z^{-1}=-1} = \frac{1}{1 + \frac{1}{4}} = \frac{4}{5}$$

Thus,

$$F(z) = K \left[ \frac{1}{5} \cdot \frac{1}{1 - \frac{1}{4}z^{-1}} + \frac{4}{5} \cdot \frac{1}{1 + z^{-1}} \right] \quad \dots(ii)$$

From information (b), since ROC includes  $|z| = \frac{1}{2}$ . Thus, ROC:  $\frac{1}{4} < |z| < 1$

i.e.,  $x(n)$  will be a both sided signal.

By applying inverse z-transform on (ii)

$$F(z) = K \left[ \frac{1}{5} \cdot \left(\frac{1}{4}\right)^n u(n) - \frac{4}{5} \cdot (-1)^n u(-n-1) \right]$$

From (i),  $X(z) = F(z)z^{-2}$

By using time shifting property of z-transform,

$$x(n) = f(n-2)$$

$$\Rightarrow x(n) = K \left[ \frac{1}{5} \left(\frac{1}{4}\right)^{n-2} u(n-2) - \frac{4}{5} (-1)^{n-2} u(-(n-2)-1) \right]$$

$$x(n) = K \left[ \frac{1}{5} \left(\frac{1}{4}\right)^{n-2} u(n-2) - \frac{4}{5} (-1)^{n-2} u(-n+1) \right]$$

Put  $n = 1$ :  $x(1) = K \left[ \frac{-4}{5} (-1)^{-1} \right] = 1 \quad \dots\text{from information (c)}$

$$\Rightarrow K = \frac{5}{4}$$

Using the above value of  $K$  and substituting  $n = -1$ , we can verify,

$$x(-1) = K \left[ \frac{-4}{5} (-1)^{-3} \right] = 1 \quad \dots \text{from information (c)}$$

$$\text{Thus, } x(n) = \frac{5}{4} \left[ \frac{1}{5} \left( \frac{1}{4} \right)^{n-2} u(n-2) - \frac{4}{5} (-1)^{n-2} u(-n+1) \right]$$

$$\Rightarrow x(n) = \left( \frac{1}{4} \right)^{n-1} u(n-2) - (-1)^{n-2} u(-n+1)$$

(ii) 1. The complex Fourier series coefficient is given by

$$C_n = \frac{1}{T} \int_0^T f(t) e^{-jn\omega_0 t} dt$$

The given signal is periodic with time period  $T = 1$  and  $f(t) = t$  for  $0 \leq t \leq 1$

$$= \frac{1}{1} \int_0^1 t e^{-jn \cdot \frac{2\pi}{1} t} dt = \left[ t \times \frac{e^{-j2\pi n t}}{-j2\pi n} \right]_0^1 - \int_0^1 \frac{e^{-j2\pi n t}}{-j2\pi n} dt$$

$$\text{Now, } e^{-jn\pi} = (-1)^n$$

$$\therefore e^{-j2n\pi} = (-1)^2 = 1$$

$$\therefore C_n = \frac{1}{-j2\pi n} - \left[ \frac{e^{-j2\pi n t}}{(-j2\pi n)^2} \right]_0^1 = \frac{1}{-j2\pi n} + \frac{1}{(2\pi n)^2} - \frac{1}{(2\pi n)^2}$$

$$C_n = \frac{j}{2\pi n}$$

but  $C_n$  becomes  $\infty$  when we put  $n = 0$ , so again calculate  $C_n$  at  $n = 0$

$$\text{We have, } C_n = \frac{1}{T} \int_0^T f(t) e^{-jn\omega_0 t} dt$$

$$\text{putting, } n = 0$$

$$\therefore C_0 = \frac{1}{T} \int_0^T f(t) dt = \frac{1}{1} \int_0^1 t dt = \left[ \frac{t^2}{2} \right]_0^1$$

$$\therefore C_0 = \frac{1}{2}$$

$$\therefore C_n = \begin{cases} \frac{1}{2} & \text{when } n = 0 \\ \frac{j}{2\pi n} & \text{when } n \neq 0 \end{cases}$$

Thus, the complex Fourier series representation of a signal is given by


$$x(n) = \sum_{n=-\infty}^{\infty} C_n e^{jn\omega_0 t} = \sum_{n=-\infty}^{\infty} C_n e^{j2\pi n t}$$

2. Magnitude,  $C_0 = \frac{1}{2}$


and  $|C_n| = \left| \frac{j}{2\pi n} \right| = \frac{1}{2\pi n}$

Phase,  $\angle C_n = +j = \frac{\pi}{2}$  when  $n > 0$   
 $= -j = \frac{-\pi}{2}$  when  $n < 0$   
 $= 0$  when  $n = 0$


**Magnitude plot:**

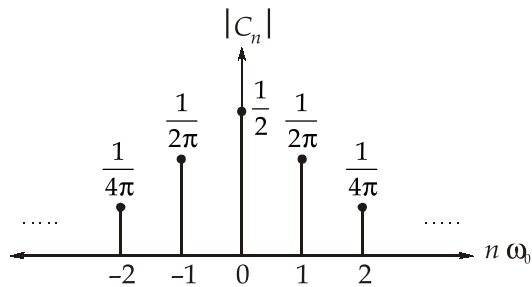

**Phase plot:**

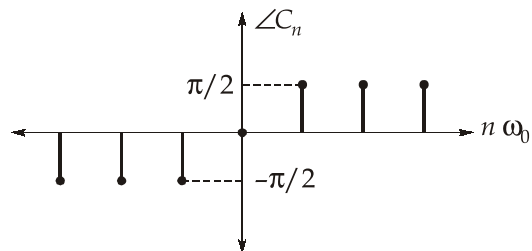

Q.8 (c) Solution:

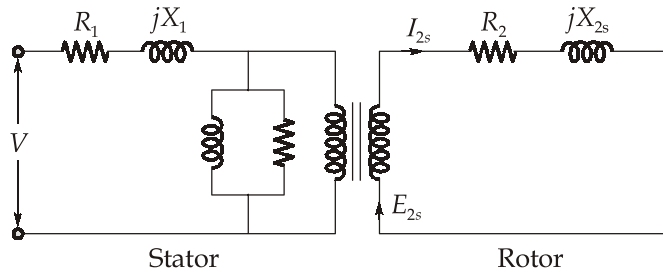

Equivalent circuit of an induction motor

(i) Power generated in the rotor = 3 × 1 phase power

$$\begin{aligned}
 &= 3E_{2s} I_{2s} \cos\phi_{2s} = 3E_{2s} \frac{E_{2s}}{Z_{2s}} \times \frac{R_2}{Z_{2s}} = 3 \frac{E_{2s}^2 R_2}{Z_{2s}^2} \\
 &= 3s^2 \frac{E_{20}^2 R_2}{R_2^2 + (sX_{20})^2} \quad \left[ \begin{array}{l} E_{2s} = sE_{20} \\ X_{2s} = sX_{20} \end{array} \right]
 \end{aligned}$$

All this power will be lost as copper losses.

$$\Rightarrow sP_g = \frac{3s^2 E_{20}^2 R_2}{R_2^2 + (sX_{20})^2} \quad [P_g = \text{Airgap power}]$$

$$\Rightarrow (s2\pi n_s \tau) = \frac{3s^2 E_{20}^2 R_2}{R_2^2 + (sX_{20})^2} \quad \left[ \begin{array}{l} n_s = \text{speed in rps} \\ \tau = \text{torque} \end{array} \right]$$

$$\Rightarrow \tau = \left( \frac{3}{2\pi n_s} \right) \frac{sE_{20}^2 R_2}{R_2^2 + (sX_{20})^2} = \frac{3E_{20}^2 R_2}{\text{constant}} \times \frac{1}{\frac{R_2^2}{s} + sX_{20}^2}$$

Maximum torque will occur when,

$$\frac{R_2^2}{s} = sX_{20}^2$$

$$\Rightarrow s = \frac{R_2}{X_{20}}$$

To have maximum starting torque, the maximum torque will have to occur at  $s = 1$ 

$$\Rightarrow \frac{R_2}{X_{20}} = 1$$

$$\Rightarrow R_2 = X_{20}$$

⇒ Condition for maximum starting torque

(ii) Given,  $P = 4$  ;  $f = 50$  Hz

$\therefore$  Synchronous speed,  $N_s = \frac{120f}{p}$

$\Rightarrow N_s = 120 \times \frac{50}{4} = 1500$  rpm

Let,  $s_M$  = slip of maximum torque ;  $s_{fl}$  = slip at full load ;  $s = 1$  at starting

Torque, 
$$\tau = \frac{3E_{20}^2 R_2}{2\pi n_s} \times \frac{1}{R_2 X_{20}} \times \frac{1}{\frac{R_2}{sX_{20}} + \frac{sX_{20}}{R_2}}$$

$\Rightarrow \tau = k \times \frac{1}{\frac{s_M}{s} + \frac{s}{s_M}} \left[ k = \frac{3E_{20}^2}{2\pi X_{20}^2 n} \right]$

1.  $\tau_{fl}$  = Full load torque

$\tau_s$  = Starting torque

Now, 
$$\frac{\tau_{fl}}{\tau_s} = \frac{\frac{1}{\frac{s_{fl}}{s_M} + \frac{s_M}{s}}}{\frac{1}{\frac{s_M}{1} + \frac{1}{s_M}}}$$

$\Rightarrow \frac{1}{1.6} = \frac{1}{\frac{1}{\frac{2s_{fl}}{2} + 2s_{fl}}} \quad [s_M = 2 \text{ from part (b)}]$

$\Rightarrow \frac{2}{84} = \frac{1}{\frac{1}{2s_{fl}} + 2s_{fl}}$

$\Rightarrow 4 = 2s_{fl} + \frac{1}{2s_{fl}}$

$\Rightarrow 8s_{fl} = 4s_{fl}^2 + 1$

$\Rightarrow 4s_{fl}^2 - 8s_{fl} + 1 = 0$

$s_{fl} = 0.134$

$\therefore$  Full load speed =  $N_{fl} = 1299$  rpm

2. Let,  $\tau_M =$  Maximum torque

$$\frac{\tau_s}{\tau_M} = \frac{1}{\frac{s_M + \frac{1}{s_M}}{1/2}}$$

$$\Rightarrow \frac{1.6}{2} = \frac{2}{s_M + \frac{1}{s_M}}$$

$$\Rightarrow s_M + \frac{1}{s_M} = \frac{5}{2}$$

$$\Rightarrow 2s_M^2 - 5s_M + 2 = 0$$

$$\Rightarrow s_M = \frac{1}{2}$$

$\therefore$  Speed at maximum torque

$$= N_M = N_s(1 - s_M) = 750 \text{ rpm}$$

○○○○