



# MADE EASY

India's Best Institute for IES, GATE & PSUs

## ESE 2019 : Mains Test Series

UPSC ENGINEERING SERVICES EXAMINATION

### Electronics & Telecommunication Engineering

#### Test-5: Analog Circuits + Materials Science

#### Electronic Devices & Circuits-1 + Advanced Electronics Topics-1

#### Analog and Digital Communication Systems-2

Name : Sakshi Singh

Roll No : E C 1 9 M T D L A 0 0 3

#### Test Centres

Delhi  Bhopal  Noida  Jaipur  Indore   
Lucknow  Pune  Kolkata  Bhubaneswar  Patna   
Hyderabad

#### Student's Signature

Sakshi

#### Instructions for Candidates

1. Do furnish the appropriate details in the answer sheet (viz. Name & Roll No).
2. Answer must be written in English only.
3. Use only black/blue pen.
4. The space limit for every part of the question is specified in this Question Cum Answer Booklet. Candidate should write the answer in the space provided.
5. Any page or portion of the page left blank in the Question Cum Answer Booklet must be clearly struck off.
6. Last two pages of this booklet are provided for rough work. Strike off these two pages after completion of the examination.

#### FOR OFFICE USE

Question No.	Marks Obtained
Section-A	
Q.1	38
Q.2	35
Q.3	38
Q.4	-
Section-B	
Q.5	34
Q.6	-
Q.7	41
Q.8	-
<b>Total Marks Obtained</b>	<b>186</b>

Signature of Evaluator

Meh


Cross Checked by

Jha



Section A : Analog Circuits + Materials Science

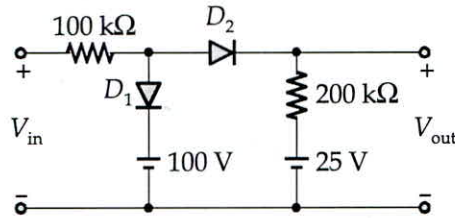
a) Consider the circuit shown in the figure below:




By assuming that the diodes are ideal, develop the transfer characteristic curve of the above circuit.

[12 marks]

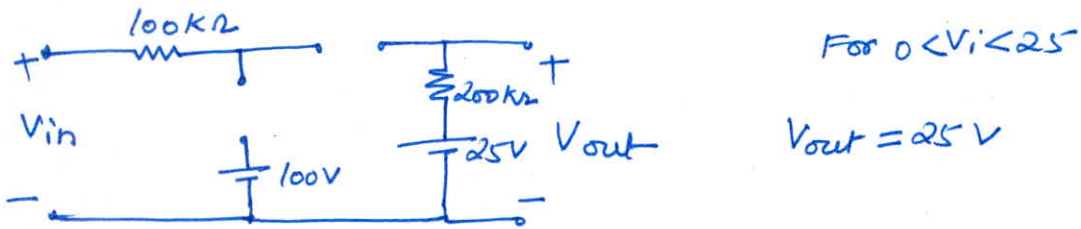When Both diodes are open ( $D_1$  and  $D_2$  off)



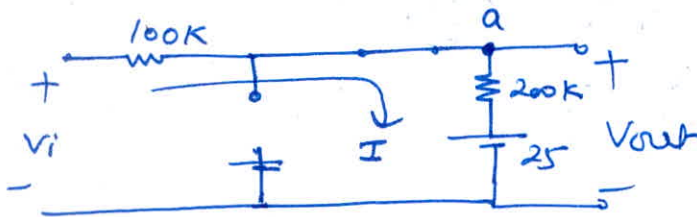Considering  $D_2$  on and  $D_1$  off when  $V_i > 25$



$$-V_i + I(300) + 25 = 0 \quad I = \frac{V_i - 25}{300} \quad V_{out} = \frac{2}{3}V_i - \frac{50}{3} + 25$$

$$V_a = \frac{25 \times 100 + 200V_i}{300} = \frac{25 + 2V_i}{3} = \frac{2}{3}V_i + \frac{25}{3}$$


Diode  $D_1$  on when  $\frac{25 + 2V_i}{3} > 100$

$$2V_i > 275$$


$$V_i \geq 137.5 \text{ Volts.}$$

For  $25 < V_i < 137.5$  Diode  $D_1$  off and  $D_2$  on

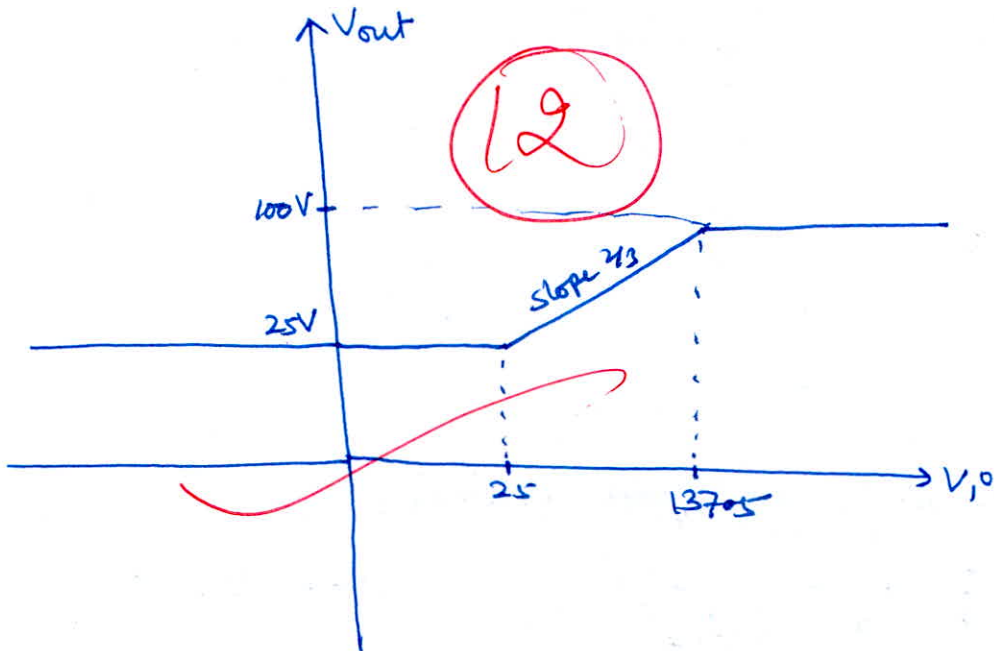$V_i > 137.5$  both diodes are on  $V_{out} = 100V$



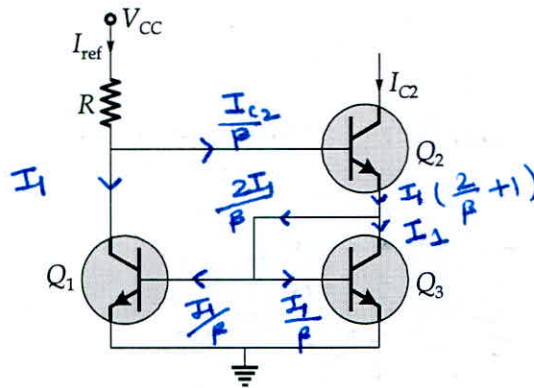Q.1 (b) Consider the Wilson current mirror circuit as shown in the figure below:



Assume that the three transistors to be matched with  $V_{BE1} = V_{BE3}$  and  $\beta_1 = \beta_2 = \beta_3 = \beta$ . Derive an expression for  $I_{C2}$  in terms of  $I_{ref}$ .

[12 marks]

$$I_{ref} = \frac{V_{cc} - 2V_{BE}}{R}$$

$$I_{ref} = I_1 + \frac{I_{C2}}{\beta}$$

$$\frac{I_{C2}}{\beta} + I_{C2} = I_1 \left( \frac{2}{\beta} + 1 \right)$$

$$I_1 = \frac{I_{C2} \left( \frac{1}{\beta} + 1 \right)}{\frac{2}{\beta} + 1}$$



$$I_{ref} = \frac{I_{c2} \left( \frac{1}{\beta} + 1 \right)}{\frac{2}{\beta} + 1} + \frac{I_{c2}}{\beta}$$

$$= \frac{I_{c2} (1 + \beta)}{2 + \beta} + \frac{I_{c2}}{\beta}$$

$$= I_{c2} \left\{ \frac{1 + \beta}{2 + \beta} + \frac{1}{\beta} \right\}$$

$$= I_{c2} \left\{ \frac{\beta^2 + \beta + 2 + \beta}{2(\beta + 2)} \right\}$$

$$I_{ref} = I_{c2} \left\{ \frac{\beta^2 + 2\beta + 2}{2(\beta + 2)} \right\}$$

||

$$I_{ref} = I_{c2} \left\{ \frac{(\beta + 1)^2 + 1}{2(\beta + 2)} \right\}$$

- Q.1 (c) A long narrow rod (having cubic structure) has an atomic density of  $5 \times 10^{28}$  atoms/m<sup>3</sup>. Each atom has a polarizability of  $10^{-40}$  F-m<sup>2</sup>. Calculate the internal electric field in the rod when an external axial field of 1 V/m is applied.

[12 marks]

$$E_i = E + \frac{\gamma P}{\epsilon_0}$$

For cubic structure  $\gamma = \frac{1}{3}$

$$\rho = \text{density} = 5 \times 10^{28} \text{ atoms/m}^3$$

$$p_{\text{each atom}} = 10^{-40} \text{ F-m}^2$$

$$P = 10^{-40} \times 5 \times 10^{28}$$

$$E = 1 \text{ V/m}$$

$$= 5 \times 10^{-12} \frac{\text{F}}{\text{m}}$$

$$E_i = \frac{1 + \frac{10^{-40} \times 5 \times 10^{28}}{3 \times 8.85 \times 10^{-12}}}{1}$$

$$= \frac{1 + \frac{10^{-40+12} \times 5 \times 10^{28}}{26.55}}{1}$$

$$= \frac{1 + 0.03766 \times 10^{-28} \times 5 \times 10^{28}}{1}$$

$$= \frac{1 + 0.1883}{1}$$

$$E_i = 1.1833 \text{ V/m}$$

1) Explain Silsbee's rule for superconductors. Also give some applications of superconductors.

[12 marks]

### Superconductor

It is a state of Material in which it has zero resistivity and have perfect diamagnetism. Below critical Temperature ( $T_c$ ) and certain Magnetic field called as critical field ( $H_c$ ) superconductivity is shown by material at low or DC freq. on increasing Magnetic field above  $H_c$  and/or temperature and current above  $I_c$  it loses its superconductivity and behave as Normal Conductor.

Silsbee's Rule → To make superconductor behave as Normal Conductor it is not necessary that direct Magnet field above critical field ( $H_c$ ) is applied it can be in form of critical Current  $I_c$  (  $I > I_c$  ) such that superconductivity destroy.



Ampere circuital law,

$$\oint H \cdot dl = I$$

$$H_c \cdot 2\pi r = I_c$$


$$H_c = \frac{I_c}{2\pi r} \quad ; \quad r = \text{radius of cond}^r$$

$$H_c = H_0 \left[ 1 - \left( \frac{T}{T_c} \right)^2 \right]$$

9

$H_0$  = critical field at  $0^\circ$  Kelvin

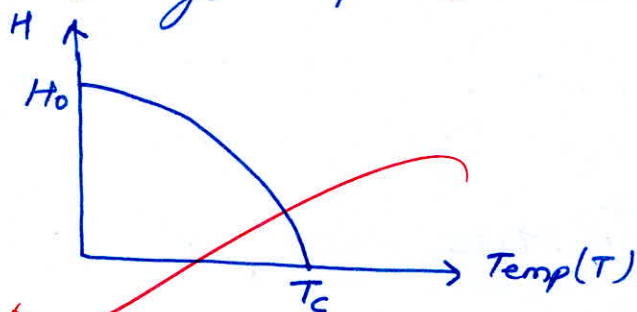On increasing temp  $H_c$  can be reduced.



application

- used in Magnetically Levitated Trains (Maglev)
- MRI
- Used in storage devices
- Used in computers



3) Write short notes on the following nanomaterials:

- (i) Quantum dots
- (ii) Carbon nanotubes

[6 + 6 marks]

(ii) Carbon Nanotubes

Nanomaterial, designing and engineering of a material of dimension in 1-100 nm are called Nanomaterial.


Nanomaterials acquires less space, faster and much more efficient than conventional devices.

In the era of Miniaturization, we are developing lot many materials in nano size. Carbon nanotube is one of them, it is 1-D Nanomaterial in which one dimension is large and other two are in range of nm.

4



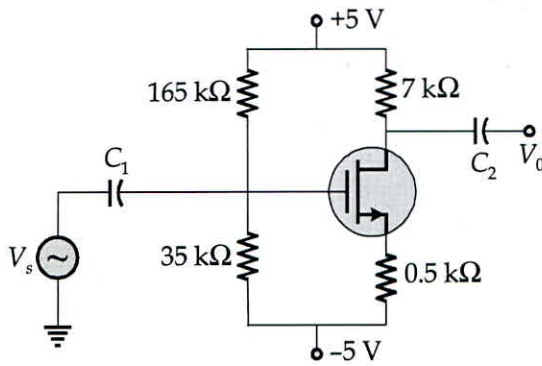(i) Consider the common source transistor circuit shown in the figure below:




The transistor parameters are  $V_{TN} = 0.8 \text{ V}$ ,  $K_n = \frac{\mu_n C_{ox} W}{2L} = 1 \text{ mA/V}^2$  and  $\lambda = 0$ .

Calculate the value of small signal voltage gain  $V_0/V_s$  of the circuit.

(ii) A differential amplifier has input voltages  $V_1 = 1 \text{ mV}$  and  $V_2 = 3 \text{ mV}$ . The amplifier has differential gain  $A_d = 5 \times 10^3$  and CMRR = 1000. Calculate the output voltage of the amplifier.

[15 + 5 marks]

DC analysis

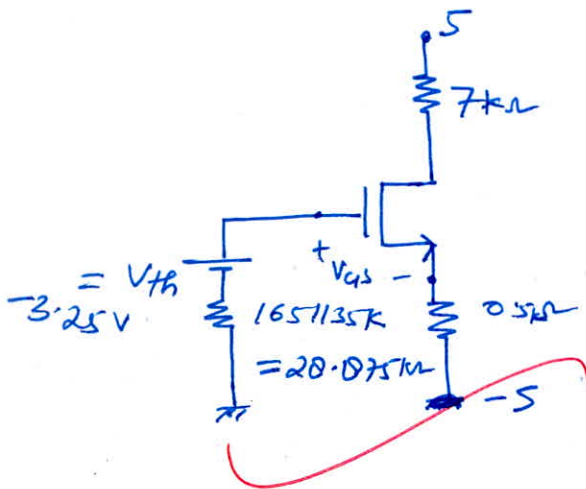

$$V_{th} = \frac{165 \times -5 + 35 \times 5}{200}$$

$$= \frac{-825 + 175}{200}$$

$$= \frac{-650}{200}$$

$$= -3.25 \text{ V}$$

$$R_{th} = \frac{165 \times 35}{200}$$

$$= 28.875 \text{ k}\Omega$$

Considering in saturation

$$I_D = 1 (V_{gs} - 0.8)^2$$

$$-V_{th} + V_{gs} + I_D \cdot 0.5 - 5 = 0$$

$$0.5 I_D + V_{gs} = -3.25 + 5$$

$$I_D = \frac{-3.25 - V_{gs}}{0.5} = -6.5 - 2V_{gs}$$

$$I_D = 2(1.75 - V_{gs}) = 3.5 - 2V_{gs}$$

$$-6.5 - 2V_{gs} = (V_{gs} - 0.8)^2$$

$$-6.5 - 2V_{gs} = V_{gs}^2 + 0.64 - 1.6V_{gs}$$

$$V_{gs}^2 + 0.4V_{gs} + 7.14 = 0$$

$$\Rightarrow 3.5 - 2V_{gs} = (V_{gs} - 0.8)^2$$


$$\Rightarrow 3.5 - 2V_{gs} = V_{gs}^2 + 0.64 - 1.6V_{gs}$$

$$V_{gs}^2 + 0.4V_{gs} - 2.86 = 0$$

$$V_{gs} = 1.502$$

$$I_D = 1(1.502 - 0.8)^2$$

$$I_D = 0.4928 \text{ mAmp}$$

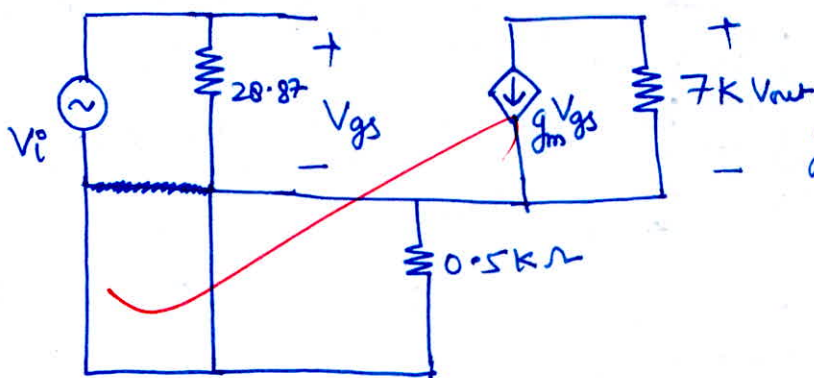

$$g_m = \frac{I_D}{V_T}$$

$$= \frac{0.4928}{0.025}$$

$$g_m = 0.0197$$

$$V_i = V_{gs} + g_m V_{gs} \cdot 0.5$$

$$V_{out} = -g_m V_{gs} \cdot 7$$

$$\frac{V_{out}}{V_i} = \frac{-g_m \cdot 7}{1 + g_m \cdot 0.5} = \frac{-7 g_m}{1 + g_m \cdot 0.5} = \frac{-0.1326 \times 1000}{10.45} = -12.68$$



$$(ii) \quad V_1 = 1 \text{ mV} \quad V_2 = 3 \text{ mV}$$

$$A_d = 5 \times 10^3 \quad \text{CMRR} = 1000$$

$$V_o = A_d (V_1 - V_2) + A_{cm} \left( \frac{V_1 + V_2}{2} \right)$$

$$\text{CMRR} = \frac{A_d}{A_{cm}} = \frac{5 \times 10^3}{A_{cm}} = \underline{1000}$$


$$A_{cm} = 5$$

$$V_o = 5 \times 10^3 (3 - 1) \times 10^{-3} + 5 \times \left( \frac{1 + 3}{2} \right) \times 10^{-3}$$

$$= 10 + 10 \times 10^{-3}$$

$$V_o = 10.01 \text{ Volts}$$

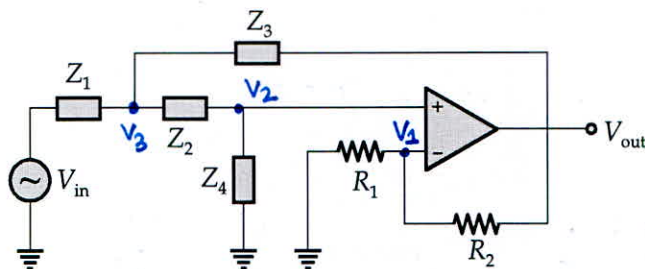Q.2 (b) Consider the circuit shown in the figure below:



The figure represents a second order active filter system.

- (i) Derive an expression for  $V_{out}/V_{in}$ .
- (ii) If each of the impedance elements  $Z_1$  through  $Z_4$  are replaced by a resistor of value  $R$ , then find the value of  $V_{out}/V_{in}$ .

[20 marks]

$$(i) V_1 = \frac{V_{out} R_1}{R_1 + R_2}$$

$$V_1 = V_2$$

$$\frac{V_3 - V_{in}}{Z_1} + \frac{V_3 - V_2}{Z_2} + \frac{V_3 - V_{out}}{Z_3} = 0 \quad \text{--- (1)}$$

$$\frac{V_2 - V_3}{Z_2} + \frac{V_2}{Z_4} = 0$$

$$V_2 \left( \frac{1}{Z_2} + \frac{1}{Z_4} \right) = \frac{V_3}{Z_2}$$

$$V_3 = V_2 \left( 1 + \frac{Z_2}{Z_4} \right)$$

$$V_3 = V_1 \left( 1 + \frac{Z_2}{Z_4} \right)$$

$$V_3 = V_{out} \left( \frac{R_1}{R_1 + R_2} \right) \left( 1 + \frac{Z_2}{Z_4} \right)$$

$$\frac{V_{out} \left( \frac{R_1}{R_1+R_2} \right) \left( 1 + \frac{Z_2}{Z_4} \right) - V_{in}}{Z_1} + \frac{V_3 - V_2}{Z_2} + \frac{V_3 - V_{out}}{Z_3} = 0$$

From eqn. ①

$$V_3 \left( \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right) = \frac{V_{in}}{Z_1} + \frac{V_2}{Z_2} + \frac{V_{out}}{Z_3}$$

$$= \frac{V_{in}}{Z_1} + \frac{V_1}{Z_2} + \frac{V_{out}}{Z_3}$$

$$= \frac{V_{in}}{Z_1} + \frac{V_{out} R_1}{R_1+R_2} + \frac{V_{out}}{Z_3}$$

$$V_{out} \left( \frac{R_1}{R_1+R_2} \right) \left( 1 + \frac{Z_2}{Z_4} \right) = \frac{V_{in}}{Z_1} + V_{out} \left( \frac{R_1}{R_1+R_2} + \frac{1}{Z_3} \right)$$

$$V_{out} \left\{ \frac{R_1}{R_1+R_2} + \frac{Z_2 R_1}{Z_4 (R_1+R_2)} - \frac{R_1}{R_1+R_2} - \frac{1}{Z_3} \right\} = \frac{V_{in}}{Z_1}$$

$$V_{out} \left\{ \frac{Z_2 Z_3 R_1 - Z_4 R_1 - Z_4 R_2}{Z_3 Z_4 (R_1+R_2)} \right\} = \frac{V_{in}}{Z_1}$$

$$\frac{V_{out}}{V_{in}} = \frac{Z_3 Z_4 (R_1+R_2)}{Z_1 Z_2 Z_3 R_1 - Z_1 Z_4 R_1 - Z_1 Z_4 R_2}$$

$$ii) \frac{V_{out}}{V_{in}} = \frac{R^2 (R_1+R_2)}{R^3 R_1 - R^2 R_1 - R^2 R_2} = \frac{R_1+R_2}{R R_1 - R_1 - R_2}$$

$$V = \frac{R_1 + R_2}{R_1 - (R_1 + R_2)}$$

$$V = \frac{R_1 + R_2}{R_1(R-1) - R_2}$$

7

- Q.2 (c) (i) For a dielectric, establish an expression for the relationship between the polarizability and permittivity. How does this relation lead to Clausius-Mossotti equation?
- (ii) When an NaCl crystal is subjected to an electric field of 1000 V/m, the resulting polarization is  $4.3 \times 10^{-8}$  C/m<sup>2</sup>. Calculate the relative permittivity of NaCl.

[15 + 5 marks]

$$P = N \alpha E_i$$

$$D = \epsilon E = \epsilon_0 E + P = \epsilon_0 \epsilon_r E$$

$$P = \epsilon_0 (\epsilon_r - 1) E$$

$$P = \epsilon_0 \chi_c E$$

$$E_i = E + \frac{\gamma P}{\epsilon_0} \quad ; \quad \begin{array}{l} E_i = \text{internal electrical field} \\ E = \text{applied external field} \end{array}$$

$$\gamma = \text{For cubic lattice} = \frac{1}{3}$$

$$E_i = E + \frac{\gamma \epsilon_0 (\epsilon_r - 1) E}{\epsilon_0}$$

$$E_i = E + \frac{(\epsilon_r - 1) E}{3} = E \left\{ 1 + \frac{\epsilon_r - 1}{3} \right\} = E \left\{ \frac{2 + \epsilon_r}{3} \right\}$$



$$P \Rightarrow N \propto E \left( \frac{2 + \epsilon_r}{3} \right) = \epsilon_0 (\epsilon_r - 1) E$$

$$= \cancel{N \propto \left( \frac{2 + \epsilon_r}{3} \right)} = \epsilon_0 (\epsilon_r - 1)$$

$$\neq \frac{\alpha N}{3\epsilon_0} = \frac{\epsilon_r - 1}{\epsilon_r + 2}$$

Clausius Mossotti eqn.

14

$$E = 1000 \text{ V/m}$$

$$P = 4.3 \times 10^{-8} \text{ C/m}^2$$

$$\epsilon_r = ?$$

$$P = \cancel{\epsilon_0 (\epsilon_r - 1) E}$$

4

$$4.3 \times 10^{-8} = 8.85 \times 10^{-12} (\epsilon_r - 1) 1000$$


$$(\epsilon_r - 1) = \frac{4.3 \times 10^{-8}}{8.85 \times 10^{-9}} = 0.4858 \times 10$$

$$\epsilon_r - 1 = 4.858$$

$$\epsilon_r = 5.858$$



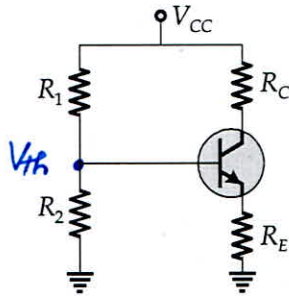Consider the voltage divider biasing circuit shown in the figure below:




For this circuit,

- (i) Derive an expression for stability factor  $S$  [i.e., the variation of  $I_C$  w.r.t.  $I_{CO}$ ].
- (ii) Derive an expression for stability factor  $S'$  [i.e., the variation of  $I_C$  w.r.t.  $V_{BE}$ ].
- (iii) Derive a relation between  $S$  and  $S'$ .

[20 marks]

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$R_B = \frac{R_1 R_2}{R_1 + R_2}$$

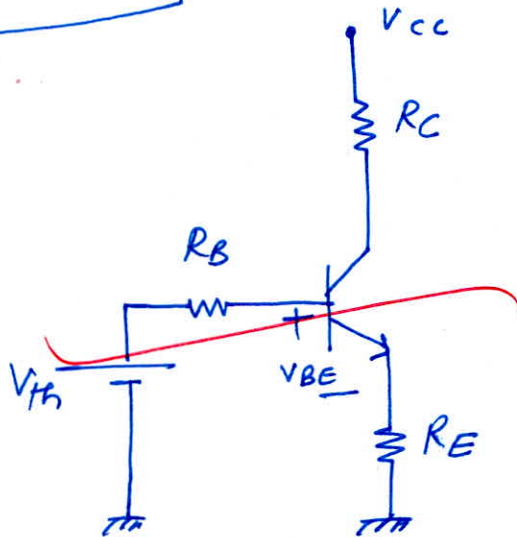

$$I_C = \beta I_B + (1 + \beta) I_{CO}$$

$$I_E = (1 + \beta) I_B$$

$$-V_{TH} + I_B (R_B) + V_{BE} + I_E R_E = 0$$

$$\frac{I_C - (1 + \beta) I_{CO}}{\beta} R_B + V_{BE} + (1 + \beta) \left( \frac{I_C - (1 + \beta) I_{CO}}{\beta} \right) R_E = V_{TH}$$

$$\frac{I_C R_B}{\beta} - \frac{(1 + \beta) I_{CO} R_B}{\beta} + V_{BE} + \frac{R_E (1 + \beta)}{\beta} I_C - \frac{(1 + \beta)^2 I_{CO} R_E}{\beta} = V_{TH} \quad (1)$$

Differentiating above eqn. wrt  $I_{C0}$

$$\frac{\partial I_C}{\partial I_{C0}} \frac{R_B}{\beta} - \frac{(1+\beta)R_B}{\beta} + \frac{R_E(1+\beta)}{\beta} \frac{\partial I_C}{\partial I_{C0}} - \frac{(1+\beta)^2}{\beta} R_E = 0$$

$$\frac{\partial I_C}{\partial I_{C0}} \left( \frac{R_B}{\beta} + \frac{R_E(1+\beta)}{\beta} \right) = \frac{(1+\beta)R_B}{\beta} + \frac{(1+\beta)^2}{\beta} R_E$$

$$\frac{\partial I_C}{\partial I_{C0}} = \frac{(1+\beta)(R_B + R_E)}{R_B + R_E(1+\beta)}$$

$$S = \frac{\partial I_C}{\partial I_{C0}} = \frac{(1+\beta)(R_B + R_E)}{(R_B + R_E) + R_E \beta} = \frac{(1+\beta)}{1 + \frac{R_E \beta}{R_E + R_B}}$$

$$(ii) S' = \frac{\partial I_C}{\partial V_{BE}}$$

Diff. eqn. (i) wrt  $V_{BE}$

$$\frac{\partial I_C}{\partial V_{BE}} \frac{R_B}{\beta} + 1 + \frac{(1+\beta)R_E}{\beta} \frac{\partial I_C}{\partial V_{BE}} = 0$$

$$\frac{\partial I_C}{\partial V_{BE}} \left( \frac{R_B}{\beta} + \frac{(1+\beta)R_E}{\beta} \right) + 1 = 0$$

$$\frac{\partial I_C}{\partial V_{BE}} = \frac{-\beta}{R_B + R_E + \beta R_E} = \frac{-\beta / (R_E + R_B)}{1 + \beta \frac{R_E}{R_E + R_B}}$$

2



$$S = \frac{(1+\beta)(R_E + R_B)}{(R_E + R_B) + \beta R_E}$$

$$S' = \frac{-\beta}{(R_E + R_B) + \beta R_E}$$

For much larger  $\beta$ ,  $1 + \beta \approx \beta$

$$\frac{S}{S'} \approx -(R_E + R_B)$$

17


- (b) What are the types of cubic crystal structure? Derive the atomic packing factor of all the cubic crystal structures.

[20 marks]

There are 3 types of Cubic Crystal Structure.

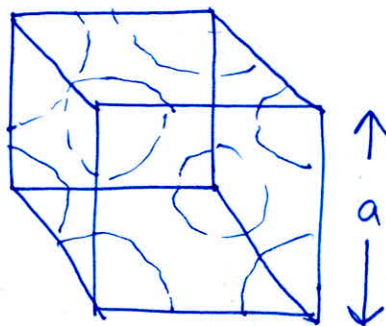- i) Simple cubic

In this at each corner of cube  $\frac{1}{8}$ <sup>th</sup> part of atom is occupied.



$r$  = radius of atom

$$2r = a$$

$$r = a/2$$

$$\text{Total No. of atoms} = \frac{1}{8} \times 8 = 1 \text{ atom}$$


$$\text{Packing factor} = \frac{1 \times \frac{4}{3} \pi r^3}{a^3} = \frac{\frac{4}{3} \pi (a/2)^3}{a^3}$$

$$\text{packing fraction} = \frac{\frac{4}{3} \pi a^3}{8 a^3} \times 100\%$$

$$= 0.52 \text{ or } 52\%$$

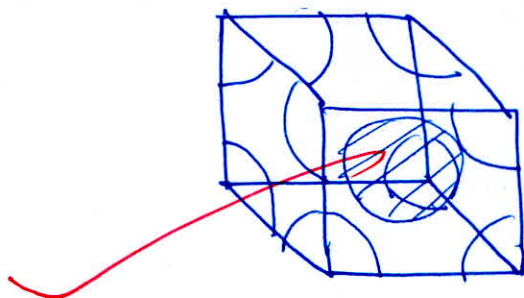
(ii) Body centered cube

In this along with corner atoms (contribution is  $\frac{1}{8}$  of whole atom) an atom at center of cube is present.



$$\text{effective atoms} = \frac{1}{8} \times 8 + 1$$

$$= 2 \text{ atoms.}$$

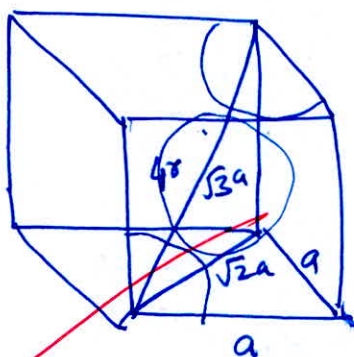

$$\sqrt{3}a = 4r$$

$$r = \frac{\sqrt{3}}{4}a$$


$$\text{packing fraction} = \frac{\text{Vol. of atoms occupied}}{\text{cube volume.}}$$

$$= \frac{\frac{4}{3} \pi r^3 \times 2}{a^3} = \frac{\frac{4}{3} \pi \left(\frac{\sqrt{3}}{4} a\right)^3 \times 2}{a^3}$$

$$= 0.68 \text{ or } 68\%$$
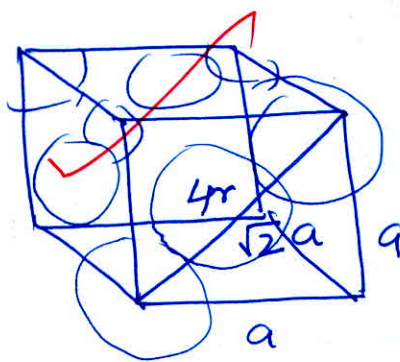
### (ii) Face centered cube

In this crystal atom is present at all faces of cube with contribution of  $\frac{1}{2}$  of whole atom along with  $\frac{1}{8}$  th of atom at each corner.



$$4r = \frac{\sqrt{2}a}{2}$$

$$\text{effective atoms} = \frac{1}{2} \times 6 + \frac{1}{8} \times 8$$

$$= 3 + 1 = 4 \text{ atoms.}$$

$$\text{packing fraction} = \frac{4 \times \frac{4}{3} \pi \left(\frac{a}{2\sqrt{2}}\right)^3}{a^3}$$

18

$$= 0.74 \text{ or } 74\%$$

- Q.3 (c) Electron drift mobility in indium (In) has been measured to be  $6 \text{ cm}^2 \text{ V}^{-1} \text{ s}^{-1}$ . At room temperature ( $27^\circ\text{C}$ ), the resistivity of In is  $8.37 \times 10^{-8} \Omega \text{ m}$  and its atomic mass and density are  $114.82 \text{ g mol}^{-1}$  and  $7.31 \text{ g cm}^{-3}$  respectively.
- (i) Based on the resistivity value, determine the effective number of free electrons donated by each In atom in the crystal.
- (ii) If the mean speed of conduction electrons in In is  $1.74 \times 10^8 \text{ cm s}^{-1}$ , what is the mean free path?
- (iii) Calculate the thermal conductivity of In at room temperature.

[20 marks]

$$\mu = 6 \text{ cm}^2 \text{ V}^{-1} \text{ s}^{-1}$$

$$\rho = 8.37 \times 10^{-8} \Omega \text{ m} = \frac{1}{qn\mu}$$

$$m = 114.82 \text{ g/mol}$$

$$\text{density} = 7.31 \text{ g/cm}^3$$

$$8.37 \times 10^{-8} \times 10^2 = \frac{1}{1.6 \times 10^{-19} \times n \times 6}$$

$$n = \frac{1}{1.6 \times 10^{-19} \times 8.37 \times 10^{-6} \times 6}$$

$$= \frac{1}{80.352 \times 10^{-25}}$$

$$= 124.4 \times 10^{24}$$

$$n = 1.244 \times 10^{23}$$


$$\mu = \frac{q\tau}{m}$$

$$\tau = \frac{\mu m}{q} = \frac{6 \times 114.82}{1.6 \times 10^{-19}} = 4.3 \times 10^{19}$$





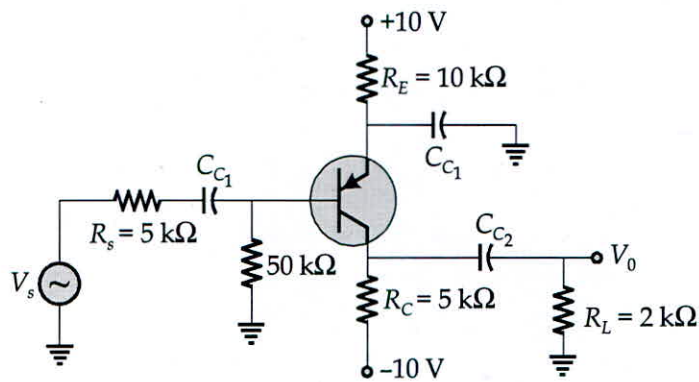
- Q.4 (a) Consider a  $p-n-p$  transistor shown in the figure below. The transistor has  $V_{EB(on)} = 0.7\text{ V}$ ,  $\beta = 150$  and  $V_A = \infty$ . Draw a neat and labelled graph for DC and AC load line. Mark the Q-point on the graph.



[20 marks]



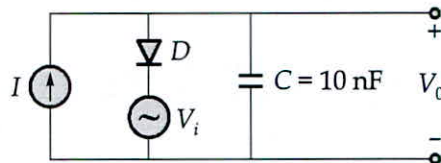Q.4 (b) Consider the circuit shown in the figure below:



$I$  is DC current and  $V_i$  is a sinusoidal signal with small amplitude and frequency of 100 kHz. Thus for small signal input and output voltages  $V_i$  and  $V_0$ , calculate:

- (i) Phase angle difference between  $V_i$  and  $V_0$ .
- (ii) The value of DC current  $I$  for which the phase shift between  $V_i$  and  $V_0$  is  $-45^\circ$ .  
(Assume  $V_T = 25$  mV)
- (iii) The range of phase shift that is achieved as  $I$  is varied over the range of 0.1 to 10 times of the value obtained in part (ii).

[20 marks]







- c) (i) What do you understand by magnetic hysteresis? Differentiate between hard and soft magnetic materials?
- (ii) In a magnetic material, the field strength is found to be  $10^6$  A/m. If the magnetic susceptibility of the material is  $0.5 \times 10^{-5}$ , calculate the intensity of the magnetization and the magnetic flux density in the material.

[12 + 8 marks]





**Section B : Electronic Devices & Circuits-1 + Advanced Electronics Topics-1  
+ Analog and Digital Communication Systems-2**

(a) With neat diagrams, explain the Local Oxidation of Silicon (LOCOS) isolation technique used in IC fabrication.

[12 marks]


LOCOS

\* It is a isolation technique used in fabrication to separate the devices so as to avoid malfunctioning of the devices.


Steps involved

2

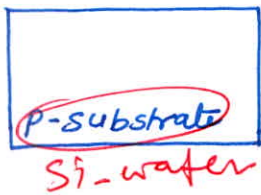
\* Take substrate (p or N according to requirement)



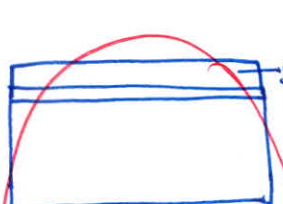\* grow pad oxide (thin oxide) using dry oxidation or wet




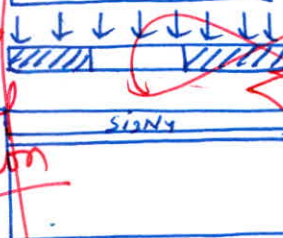\* grow layer of  $Si_3N_4$  for better protection.




\* using Mask and UV ray perform photolithography to etch the unwanted layers using HF or  $H_2SO_4$  (dilute acid)

2

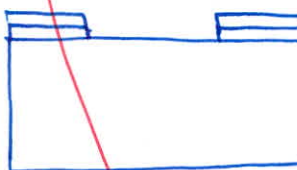

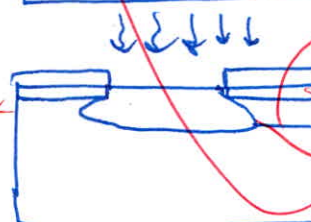\* Then perform oxidation process using suitable reactants.



In this ~~typ~~ process of oxide formation there is formation of Bird's beak like structure which is unwanted and leads to Malfunction in the device ~~is~~ (case of small devices). Therefore Now a day shallow trench isolation is preferred.

label the diagrams properly with sequences.

- Q.5 (b)
- (i) The oxide removal rate and the removal rate of a layer underneath the oxide (called a stop layer) are  $r$  and  $0.1r$  respectively. To remove  $1 \mu\text{m}$  of oxide and a  $0.01 \mu\text{m}$  stop layer, the total removal time is 5.5 minutes. Find the oxide removal rate ( $r$ ).
  - (ii) Calculate the Al average etch rate and etch rate uniformity on a 200 mm diameter silicon wafer, assuming the etch rates at the center, left, right, top and bottom of the wafer are 750, 812, 765, 743 and 798 nm/min respectively.


[6 + 6 marks]



Q.5 (c)

A source emits seven symbols with probabilities 0.35, 0.3, 0.2, 0.1, 0.04, 0.005, 0.005. Give Huffman coding for these symbols and calculate average bits of information and average binary digits of information per symbol.

[12 marks]

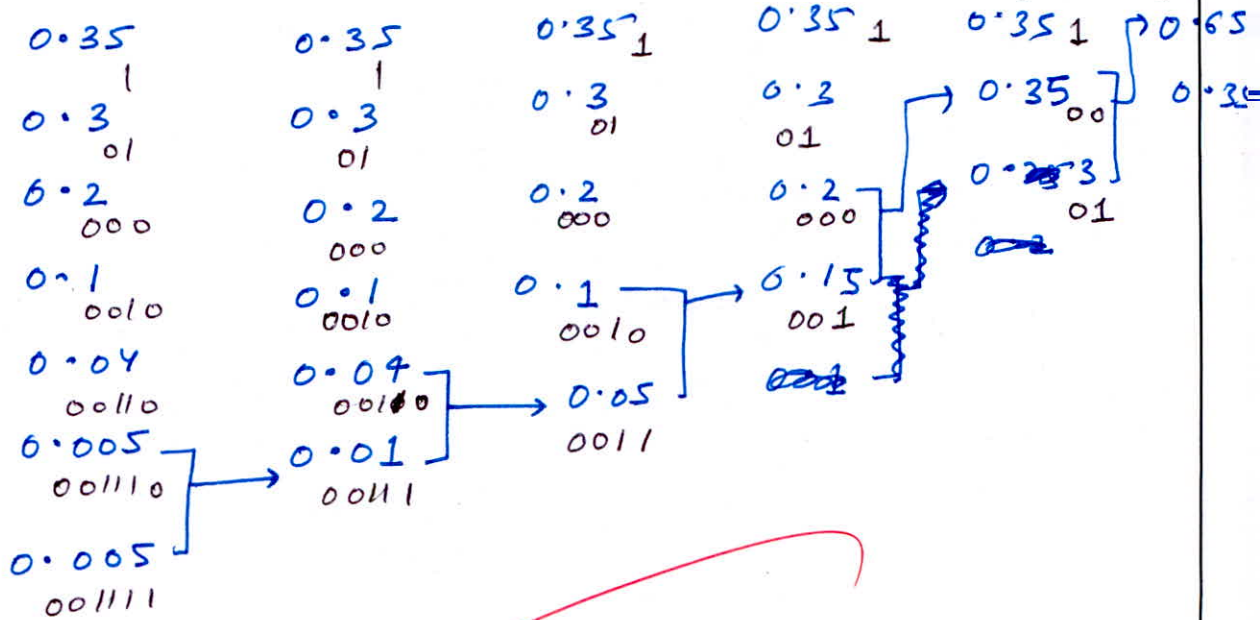

$$H(x) = - \left( 0.35 \log_2 0.35 + 0.3 \log_2 0.3 + 0.2 \log_2 0.2 \right.$$

$$\left. + 0.1 \log_2 0.1 + 0.04 \log_2 0.04 + 0.005 \log_2 0.005 + 0.005 \log_2 0.005 \right)$$

$$= 0.53 + 0.521 + 0.4643 + 0.332$$

$$+ 0.1857 + 0.03821 + 0.03821$$

$$H(x) \approx 2.1094 \text{ bits/symbol}$$

$$L = 0.35 \times 1 + 0.3 \times 2 + 0.2 \times 3 + 0.1 \times 4$$

$$+ 0.04 \times 5 + 0.005 \times 6 + 0.005 \times 6$$

$$= 0.35 + 0.6 + 0.6 + 0.4 + 0.20$$

$$+ 0.03 + 0.03$$



$$L = 2.21 \text{ bits/symbol.}$$

$$\eta = \frac{H(x)}{L} = \frac{2.1094}{2.21}$$

$$= 0.9544$$



95.44% efficiency

- (d) The distribution (with respect to energy) of electron concentration in the conduction band is given by density of allowed quantum states times the probability that state being occupied by an electron. i.e.,  $n(E) = g_c(E) f(E)$  where,  $g_c(E)$  = Density of allowed states,  $f(E)$  = probability of state being occupied. Assuming that Boltzmann approximation in a semiconductor is valid, calculate the ratio of  $n(E)$  at  $E = E_c + 4kT$  to that at  $E = E_c + (kT/2)$ . Here,  $k$  = Boltzmann constant,  $E_c$  = edge of the conduction band and  $T$  = temperature in  $^{\circ}\text{K}$ .

[12 marks]

$$f_E = \frac{1}{1 + e^{(E-E_c)/kT}}$$

$$f_{E_1} = \frac{1}{1 + e^{4kT/kT}}$$

$$= \frac{1}{1 + e^4} = \frac{1}{27.55} = 0.03629$$

Probability of  $e^-$  at  $E = E_c + 4kT$  is 0.03629

$$f_{E2} = \frac{1}{1 + e^{(kT/2)/kT}}$$

$$= \frac{1}{1 + e^{1/2}}$$


7

$$f_{E2} = \frac{1}{2.5066} = 0.3989$$

$$\frac{f_{E1}}{f_{E2}} = \frac{0.03629}{0.3989} = 0.0909$$

0.0854

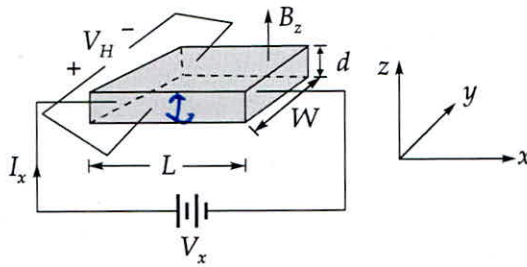e) Consider a silicon Hall effect device which is used for the experiment as shown below:



The device has dimensions  $d = 5 \times 10^{-3}$  cm,  $W = 5 \times 10^{-2}$  cm and  $L = 0.5$  cm. The electrical parameters measured as the result of the experiment are  $I_x = 0.5$  mA,  $V_x = 1.25$  V and  $B_z = 6.5 \times 10^{-2}$  T. If the induced Hall electric field is  $E_{Hy} = -16.5$  mV/cm, then determine:

- (i) Hall voltage ( $V_H$ )
- (ii) The type of semiconductor
- (iii) The majority carrier concentration

[12 marks]

$$V_H = \frac{I_x R_H B_z}{d}$$

$$\frac{V_x}{I_x} = R = \frac{1.25}{0.5 \times 10^{-3}}$$

$$R = 2.5 \text{ k}\Omega$$

$$E_{Hy} = -16.5 \times 10^{-3} \frac{\text{V}}{\text{cm}}$$

$$V_H = E_{Hy} \times W$$

$$= -16.5 \times 10^{-3} \times 5 \times 10^{-2}$$

$$= -82.5 \times 10^{-5} \text{ volts.}$$

$$= -0.825 \text{ mV volts.}$$

10

since  $V_H$  is negative therefore it is

N type semiconductor.


$$n = \frac{1}{2R_H} = 4.96 \times 10^{21}$$

unit?

$$R_H = \frac{V_H d}{I_x B_z} = \frac{-0.825 \times 10^{-3} \times 5 \times 10^{-5}}{0.5 \times 10^{-3} \times 6.5 \times 10^{-2}}$$

$$R_H = 1.2692 \times 10^{-3} = \frac{1}{nq}$$

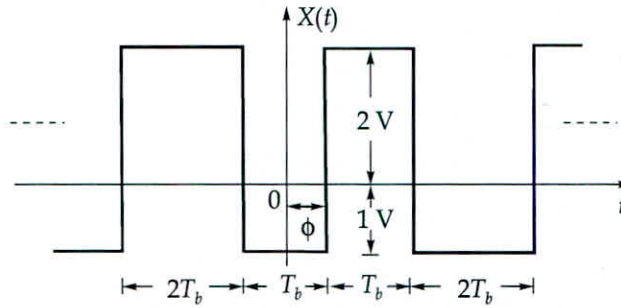Q.6 (a) Consider the random binary wave shown below:



In this binary wave, logic-1 is represented with positive rectangular pulse and logic-0 is represented with negative rectangular pulse, both with different amplitudes.  $\phi$  is an independent random variable uniformly distributed in the range  $[0, T_b]$ , where  $T_b$  is the bit duration. Determine and sketch the auto-correlation function of  $X(t)$ . Assume that logic-1 and logic-0 are occurring with equal probability.

[20 marks]





- Q.6 (b)** A 1 cm long bar of *n*-type Ge has a cross section of 1 mm × 1 mm. The resistivity of material is 20 Ω-cm and the lifetime of the carriers is 100 microseconds. (Assume  $\mu_n = 3800 \text{ cm}^2/\text{V-s}$ ,  $\mu_p = 1800 \text{ cm}^2/\text{V-s}$  and intrinsic carrier concentration  $n_i = 2.5 \times 10^{13}/\text{cm}^3$ ).
- (i) Calculate the resistance of the bar.
  - (ii) Calculate the donor concentration.
  - (iii) Calculate the resistance of the bar when it is illuminated such that excess electron-hole pairs are generated at a rate of  $10^{15} \text{ cm}^{-3} \text{ s}^{-1}$ , uniformly all over the bar.

**[20 marks]**





- (i) Binary data (equiprobable bits) with a rate of 1 Mbps is transmitted through an AWGN channel using different modulation schemes. The two sided power spectral density of the channel noise is  $0.5 \times 10^{-11}$  W/Hz and the carrier signal used in the transmitters is  $5\cos(2\pi f_c t)$  mV. In each case of different modulation schemes, the signals are received by their respective correlator receivers with exact phase synchronisation and with optimum threshold detection. Find the average symbol error probability for modulation schemes BASK, BFSK and BPSK.
- (ii) Suppose that two signals  $s_1(t)$  and  $s_2(t)$  are orthogonal over the interval  $(0, T)$ . A sample function  $n(t)$  of a zero-mean white noise process is correlated with  $s_1(t)$  and  $s_2(t)$  separately, to yield the following variables:

$$n_1 = \int_0^T s_1(t)n(t)dt \quad \text{and} \quad n_2 = \int_0^T s_2(t)n(t)dt$$

Prove that  $n_1$  and  $n_2$  are orthogonal.


[15 + 5 marks]








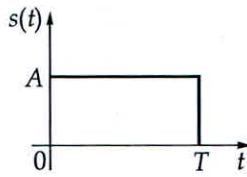Q.7 (a) Consider the signal shown in the figure below:





This signal is passed through a channel and applied to a filter matched to the signal  $s(t)$  at the receiving end. If the channel is not ideal, but has an impulse response  $c(t) = \delta(t) + \frac{1}{2}\delta(t - \frac{T}{2})$ , then determine and sketch the output of the matched filter.


[20 marks]


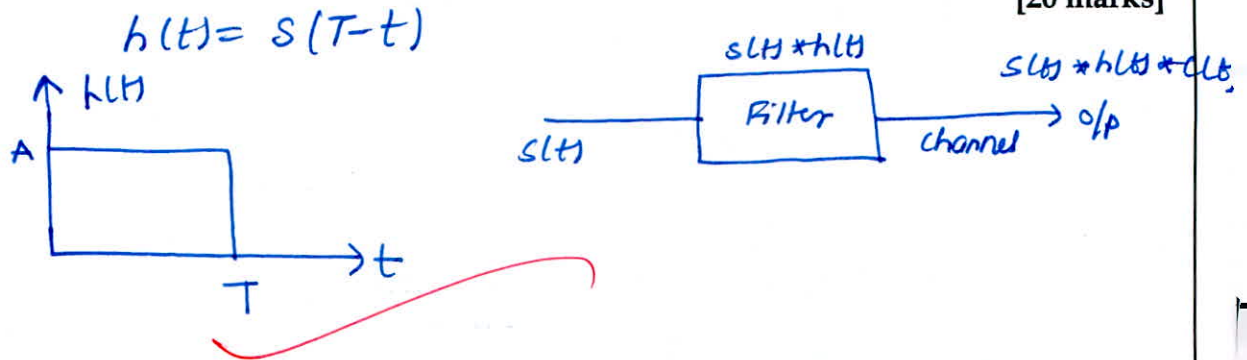


$s(t) * h(t)$

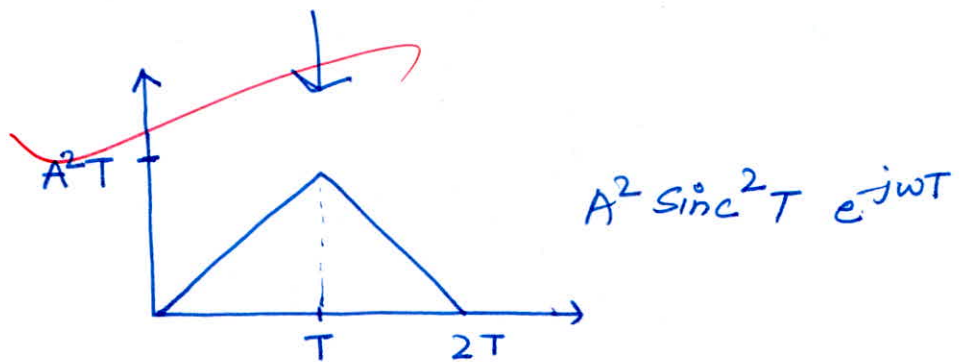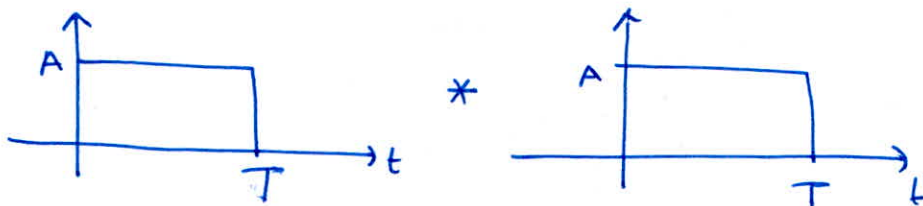

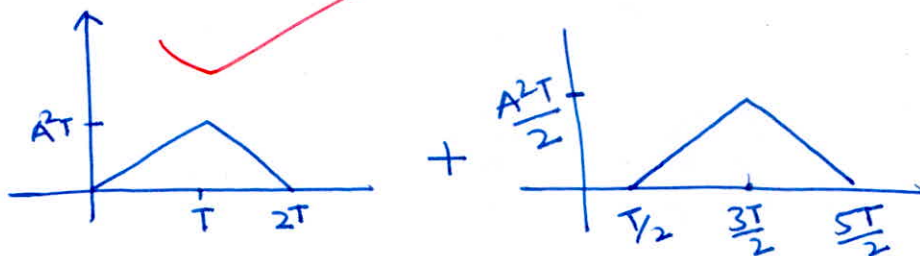passed through channel  $c(t)$   
 $s(t) + \frac{1}{2}\delta(t - T/2)$



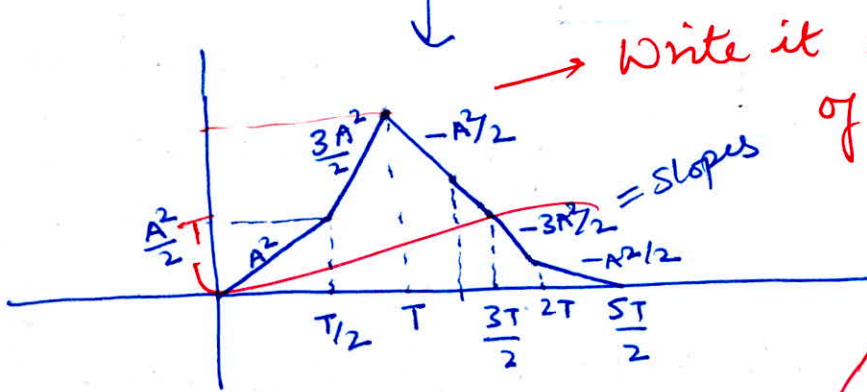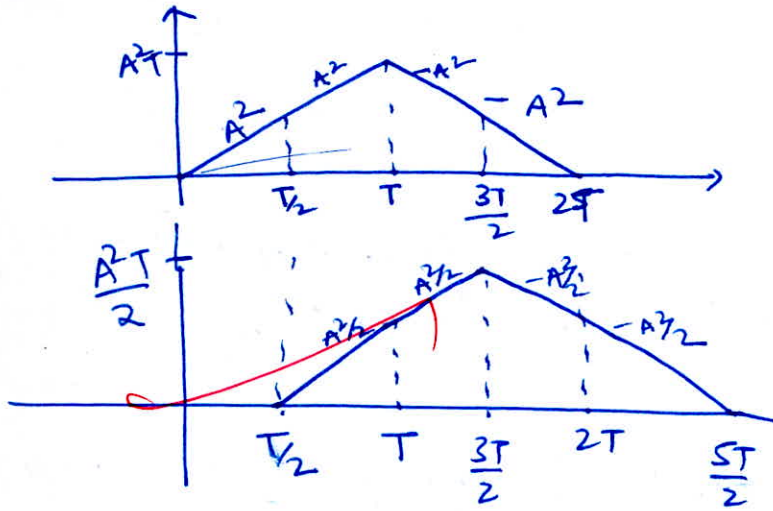

Write it in the form of equations also.


15




Q.7 (b) Explain the basic steps involved in the fabrication of a CMOS transistor using silicon on sapphire (SOS) process.

[20 marks]

Steps

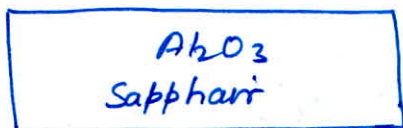


Take sapphire substrate ( $Al_2O_3$ )

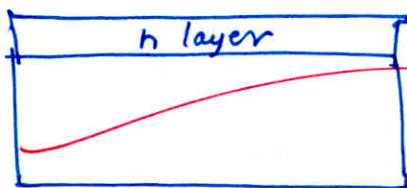


deposit (grow) n type layer




perform lithography

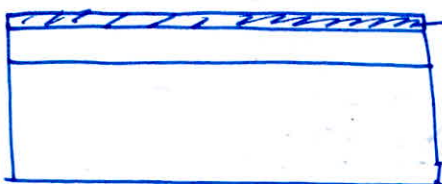

$SiO_2$  to etch out undesired layer


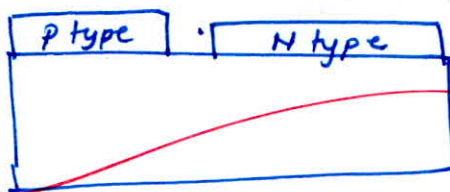


grow n and p well using oxidation

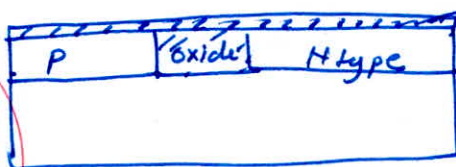


Poly silicon

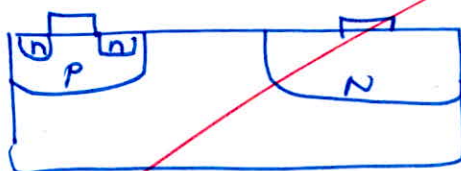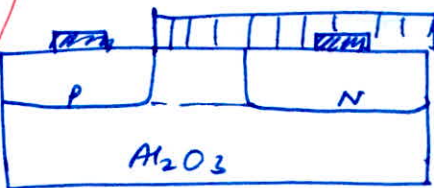grow polysilicon layer for self alignment of gate






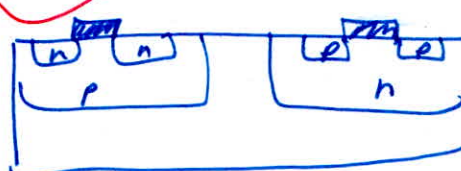Make (grow) source and drain using doping of n/p



required accordingly

9

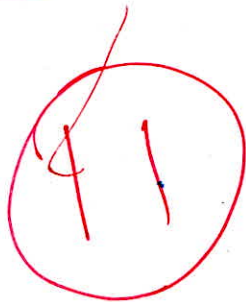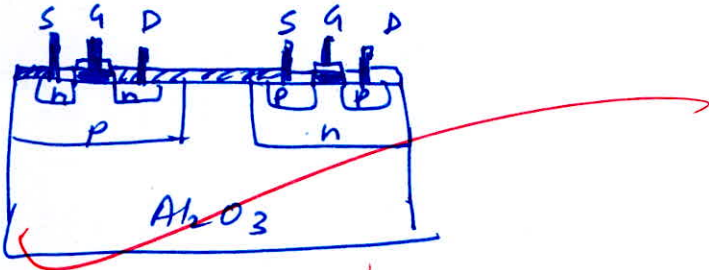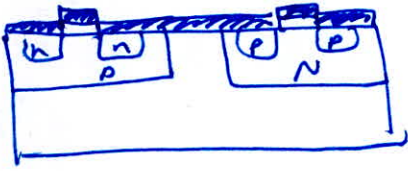



- Q.7 (c) A  $p$ -type lightly doped semiconductor has electron mobility  $\mu_n$ , hole mobility  $\mu_p$ , intrinsic carrier concentration  $n_i$  and the acceptor impurity concentration  $N_A$ .
- Derive an expression for the hole concentration ' $p$ ' in terms of  $n_i$ ,  $\mu_n$  and  $\mu_p$ , such that the conductivity of the semiconductor is minimum.
  - Derive an expression for the minimum conductivity of the semiconductor.
  - If  $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$ ,  $\mu_n = 1300 \text{ cm}^2/\text{V-sec}$  and  $\mu_p = 500 \text{ cm}^2/\text{V-sec}$ , then calculate the value of minimum conductivity.
  - If there is 100% ionization of doping atoms, then calculate the value of acceptor impurity concentration ( $N_A$ ).

[20 marks]

$$np = n_i^2$$

$$n + N_A = p + N_A$$

$$\sigma = qn\mu_n + qp\mu_p$$

$$\sigma = q \frac{n_i^2}{p} \mu_n + qp\mu_p$$

For min conductivity,

$$\frac{\partial \sigma}{\partial p} = 0$$

$$\frac{\partial \sigma}{\partial p} = - \frac{q h_i^2 \mu_n}{p^2} + q \mu_p = 0$$

$$p = h_i \sqrt{\frac{\mu_n}{\mu_p}}$$

Similarly,

$$n = h_i \sqrt{\frac{\mu_p}{\mu_n}}$$

$$\sigma = q n \mu_n + q p \mu_p$$

Using previous result for min conductivity,

$$\sigma = q h_i \sqrt{\frac{\mu_p}{\mu_n}} \mu_n + 2 h_i \sqrt{\frac{\mu_n}{\mu_p}} \mu_p$$

$$= q h_i \sqrt{\mu_n \mu_p} + 2 h_i \sqrt{\mu_n \mu_p}$$

$$= 2 q h_i \sqrt{\mu_n \mu_p}$$

13

$$\sigma_{\min} = 2 \times 1.6 \times 10^{-19} \times 1.5 \times 10^{10} \sqrt{1300 \times 500}$$

$$= 4.8 \times 10^{-9} \sqrt{650000}$$

$$= 3869.88 \times 10^{-9}$$

$$= 3.869 \times 10^{-6} \text{ cm}^{-1} \text{ V}^{-1} \text{ sec}^{-1}$$


$$3.869 \times 10^{-6} = \frac{1}{1.6 \times 10^{-19} \times N_A \times 500 + 1.6 \times 10^{-19} \frac{1.5 \times 10^{10}}{N_A}}$$

$$N_A = ?$$

Write formula  
then put the  
values!



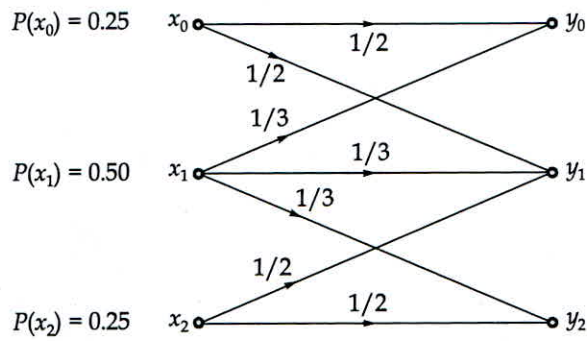Consider the discrete memoryless channel shown below:



Determine the mutual information  $I(X; Y)$ .

[20 marks]







- Q.8 (b) For a boron diffusion in silicon at  $1000^{\circ}\text{C}$ , the surface concentration is maintained at  $10^{19} \text{ cm}^{-3}$  and the diffusion time is 1 hour. Assume that the diffusivity ( $D$ ) of Boron in Silicon at  $1000^{\circ}\text{C}$  is  $2 \times 10^{-14} \text{ cm}^2/\text{s}$ . Determine:
- The total number of dopant atoms per unit area of semiconductor.
  - The distance of the location from the surface where the dopant concentration reaches  $10^{15} \text{ cm}^{-3}$ . Assume that  $\text{erfc}^{-1}(10^{-4}) = 2.75$ .
  - The gradient of the diffusion profile at the surface.
  - The gradient of the diffusion profile at the distance from the surface obtained in part (ii).

[20 marks]



- Q.8 (c) (i) Find the expression for reverse saturation current  $I_0$  in a  $p-n$  junction diode in terms of intrinsic carrier concentration  $n_i$ .
- (ii) Find an expression for the reverse saturation current in terms of the conductivity of

the device and prove that,  $I_0 = AV_T \frac{b\sigma_i^2}{(1+b)^2} \left[ \frac{1}{L_p\sigma_n} + \frac{1}{L_n\sigma_p} \right]$  where,  $b = \frac{\mu_n}{\mu_p}$

[20 marks]







Space for Rough Work

---

**Space for Rough Work**

---