

2020

RANK Improvement **WORKBOOK**



**Detailed Explanations of
Objective & Conventional Questions**

Electronics Engineering
Digital Circuits



MADE EASY
Publications

1

Boolean Algebra, Logic Gates

LEVEL 1 Objective Solutions

1. (c)

2. (c)

3. (c)

LEVEL 2 Objective Solutions

4. (1)

5. (c)

6. (d)

7. (a)

8. (c)

9. (b)

■ ■ ■ ■


© Copyright: Subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced or utilised in any form without the written permission.

LEVEL 3 Conventional Solutions

Solution : 1

$$\begin{aligned}
 \text{(i)} \quad AB + AC + B\bar{C} &= AB(C + \bar{C}) + AC + B\bar{C} & (\because C + \bar{C} = 1) \\
 &= ABC + AC + AB\bar{C} + B\bar{C} \\
 &= (B + 1)AC + (A + 1)B\bar{C} & (\because A + 1 = 1) \\
 &= AC + B\bar{C} \\
 \text{(ii)} \quad \overline{AB + BC + CA} &= (\overline{AB})(\overline{BC})(\overline{CA}) \\
 &= (\bar{A} + \bar{B})(\bar{B} + \bar{C})(\bar{C} + \bar{A}) \\
 &= (\bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B}\bar{C})(\bar{C} + \bar{A}) \\
 &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B} + \bar{A}\bar{C} + \bar{A}\bar{C} + \bar{B}\bar{C} + \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} \\
 &= \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{C}\bar{A} + \bar{A}\bar{B}\bar{C} \\
 &= \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{C}\bar{A}(1 + \bar{B}) \\
 &= \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{C}\bar{A} & (\because 1 + \bar{B} = 1)
 \end{aligned}$$


Solution : 2

 

Solution : 3

$$\begin{aligned}
 \text{(i)} \quad &\text{Prime implicants: } \bar{w}\bar{x}\bar{z}, x\bar{y}\bar{z}, \bar{w}xy, w\bar{x}\bar{z} \\
 \text{(ii)} \quad &\text{Minimal representation: } \bar{w}\bar{x}\bar{z} + w\bar{x}\bar{z} + x\bar{y}\bar{z} + \bar{w}xy \\
 &= \underbrace{\bar{x}\bar{z}} + \underbrace{x\bar{y}\bar{z}} + \underbrace{\bar{w}xy}
 \end{aligned}$$

 (iii) Two-level realization using NAND Gates only,



■■■■■

2

Combinational Circuits

LEVEL 1 Objective Solutions

1. (a)

2. (c)

LEVEL 2 Objective Solutions

3. (a)

4. (a)

5. (12)

6. (a)

7. (50)

8. (a)


■■■■

© Copyright: Subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced or utilised in any form without the written permission.

LEVEL 3 Conventional Solutions

Solution : 1

(i)

 

(ii) $\therefore$

$$P_1 = \bar{a}b$$

$$P_2 = ac$$

$$P_3 = b\bar{c}$$

If


$$P_4 = \bar{a}\bar{b}, \quad \text{then } P_5 = bc$$

and if


$$P_4 = bc, \quad \text{then } P_5 = \bar{a}\bar{b}$$

Solution : 2



(i)

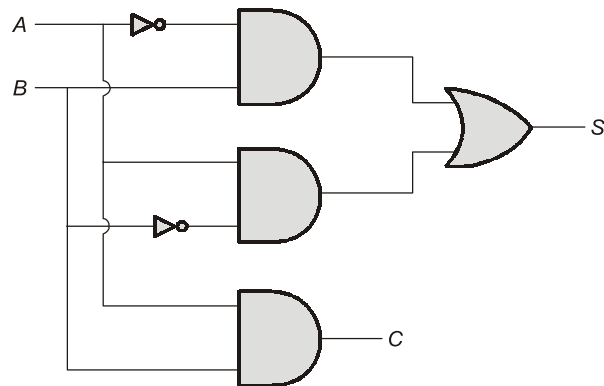


(ii)

 



(iii)

  **Solution : 3**

 


Solution : 4

 

 Solution : 5**Solution : 6**

(a)

 

(b) It can not be realized with a 4 to 1 multiplexer as 5th and 7th lines are being used.

■■■■■

3

Sequential Circuits

LEVEL 1 Objective Solutions

1. (d)

2. (10)

LEVEL 2 Objective Solutions

3. (0.8415)

4. (b)

5. (c)

6. (6)


7. (b)

8. (a)


9. (d)

■ ■ ■ ■


© Copyright: Subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced or utilised in any form without the written permission.

 LEVEL 3 Conventional Solutions**Solution : 1**


Logic Diagram

 Solution : 2**Solution : 3**


Realizations of counter using above results:

  **Solution : 4**

The diagram of a 4-bit shift register using JK flip-flops is shown below:




 The output waveforms of all flip-flops as for the given data are shown below




Solution : 5

Johnson counter is twisted ring counter

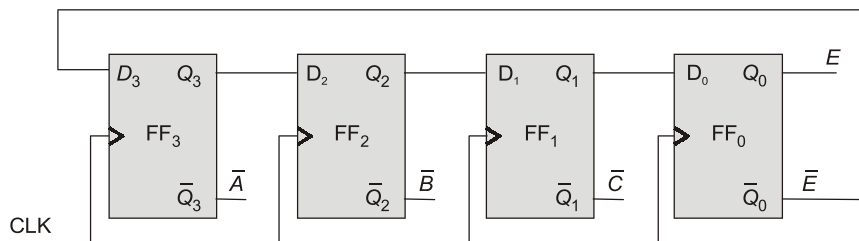


4 bit Ring counter using D flip-flop

 

4 bit Ring counter using J-K flip-flop

Solution : 6

 

4

A/D and D/A Converters

LEVEL 1 Objective Solutions

1. (a)

LEVEL 2 Objective Solutions

2. (a)

3. (a)

■ ■ ■ ■


© Copyright: Subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced or utilised in any form without the written permission.

Solution : 1

This type of ADC uses an array of comparators connected in parallel, each comparator switching on in a definite ratio of the reference voltage.

Simultaneous 3-bit A/D converter: "Flash type Converter"

 
The block diagram of simultaneous 3-bit A/D converter is shown below:



- ⇒ The simultaneous 3-bit A/D converter uses 7 comparators to convert an analog input voltage into the digital output. The reference voltages used are $\frac{V}{8}$, $\frac{2V}{8}$, ..., $\frac{7V}{8}$ for any input voltage between 0 and $+V$.
- ⇒ If the analog input voltage (V_i) exceeds the reference voltage of a comparator, the output of the comparator goes high. i.e. 1 and vice-versa.
- ⇒ The outputs of the comparators are fed into a coding network which gets stored in register of 3 bit and provide the digital output of 3-bit corresponding to the input analog voltage.

Solution : 2

The 8-bit successive approximation A/D converter is shown below

 **Solution : 3**

Dual-slope < single-slope < successive approximation < flash


maximum conversion time for converting n -bit

$$= n \times T_{\text{CLK}} = 8 \times \frac{1}{f_{\text{CLK}}} = 8 \times 10^{-6} \text{ second} = 8 \mu\text{-sec.}$$

Solution : 4

- (i) Resolution = 1 mV as transducer is able to distinguish a minimum change of 1 mV in its signal input.
- (ii) Total number of quantized levels = $\frac{10}{1 \times 10^{-3}} = 10000$
So, minimum number of bits required = 14 [As $2^{13} < 10000$, $2^{14} > 10000$]
- (iii) Quantization interval = $\frac{1}{2^{(\text{Number of bits})}} = \frac{1}{2^{14}} = 6.1 \times 10^{-5} \text{ V}$
- (iv) Number of decision levels = $2^n - 1 = 2^{14} - 1 = 16383$

Solution : 5

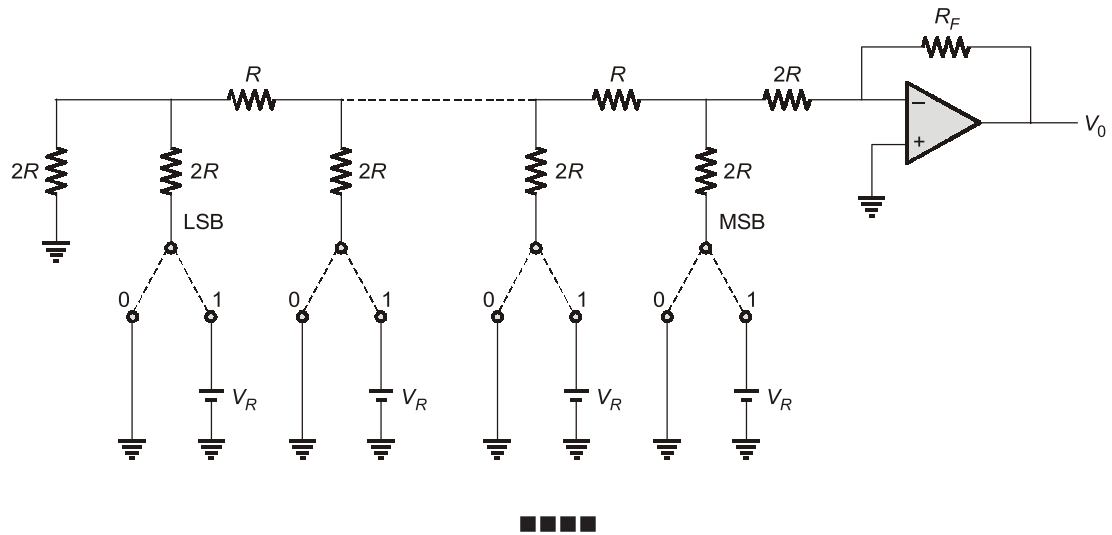

LEVEL 1 Objective Solutions

1. (b)

LEVEL 2 Objective Solutions

2. (0.63)

3. (b)

4. (c)

■ ■ ■ ■

© Copyright: Subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced or utilised in any form without the written permission.

Solution : 1

Differences between ECL and TTL are as follows:

1. In ECL, the positive end of the supply is connected to ground while in TTL, the negative end of the supply is connected to ground.
2. In TTL, the inputs are connected to emitter while in ECL the inputs are connected to bases
3. ECL uses transistors in difference amplifier configuration while TTL uses a multiple emitter transistor.

Merits and demerits of TTL:

Merits:

1. Current drawn from the input source is very small.
2. It has high output drive capability.
3. No damage is done to TTL devices if inputs are left unconnected.

Demerits:

1. High power consumption.
2. High current drain.

Merits and demerits of ECL:

Merits:

1. It is the fastest of all logic families.
2. Input impedance is high.
3. Output impedance is low
4. High fanout.
5. Outputs of ECL gates can be connected to obtain additional logic.


Demerits:

1. High power consumption.
2. ECL gates are not readily compatible with other logic families.

Solution : 2


(i)

$$Y = A \cdot B$$

 


(ii)

$$Y = A + B$$

 


(iii)

$$Y = A \oplus B$$

 

(iv)

$$Y = A \odot B$$

 

Solution : 3

As single NMOS acts as an inverter, implementing $\bar{f}$ would realize $f(a, b, c)$

