

2020

RANK *Improvement* **WORKBOOK**



**Answer key and Hint of
Objective & Conventional Questions**

Electronics Engineering
Network Theory



MADE EASY
Publications

1

Basics of Network Analysis

LEVEL 1 Objective Solutions

1. (b)
2. (b)
3. (a)
4. (a)
5. (80)
6. (c)
7. (b)
8. (25)

© Copyright: Subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced or utilised in any form without the written permission.

LEVEL 2 Objective Solutions

9. (100)
10. (c)
11. (1.71)
12. (a)
13. (a)
14. (a)
15. (c)
16. (0.196)

■■■■

LEVEL 3 Conventional Solutions

Solution : 1

$$\frac{P_{\text{out}}}{P_{\text{in}}} = 1.064 \times 10^6 \text{ W}$$

Solution : 2

$$I_1 = 0.25 \text{ A}, I_2 = -0.417 \text{ A}$$

Independent sources delivering the power and dependent sources absorbing the power.

Solution : 3


$$\frac{V_L}{V_S} = 0.9375$$

Solution : 4

$$P_{12\Omega} = 192 \text{ W}, P_{8\Omega} = 288 \text{ W and } P_{16\Omega} = 144 \text{ W}$$

Solution : 5

Constant current source

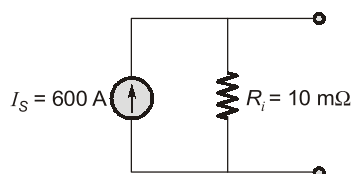

Solution : 6

$$\alpha = \frac{I_2}{I_1} = -0.786$$

Solution: 7

$$P = 100 \text{ mW}$$



2

Steady State Sinusoidal Analysis

LEVEL 1 Objective Solutions

1. (d)
2. (1)
3. (a)
4. (a)
5. (c)
6. (b)
7. (b)

© Copyright: Subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced or utilised in any form without the written permission.

LEVEL 2 Objective Solutions

8. (a)
9. (c)
10. (c)
11. (d)
12. (c)
13. (89.44)
14. (b)
15. (b)
16. (1)

■ ■ ■ ■

LEVEL 3 Conventional Solutions

Solution : 1

$$R = 1 \text{ k}\Omega$$

Solution : 2

$$C = \frac{L}{R^2 + (\omega L)^2}$$


Solution : 3

$$\text{Voltmeter reading} \approx 152 \text{ V}$$

Solution : 4

$$Q \text{ factor} = 0.03 \text{ and } \omega_0 = 1414 \text{ rad/sec.}$$

Solution : 5

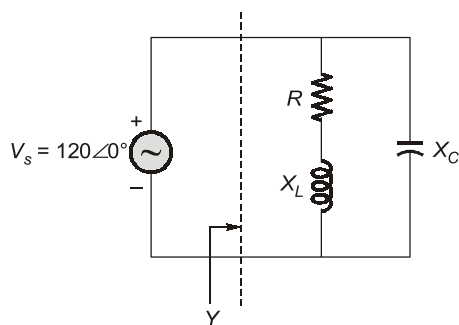

Y = equivalent admittance of the parallel circuit

Hint:

For unity power factor resonance, imaginary term must be zero

$$\frac{1}{X_C} - \frac{X_L}{R^2 + X_L^2} = 0$$

$$X_L^2 - X_C X_L + R^2 = 0$$

Minimum value of the current drawn from the supply $I_{s1} = 3 \text{ A}$.

Solution : 6

$$\tan \theta = \frac{\left(\omega L - \frac{1}{\omega C} \right)}{R}$$

(i) $f = 19.57 \text{ Hz}$

(ii) $f = 21.56 \text{ Hz}$

Solution : 7

$$L = 0.2481 \text{ mH}$$


$$R = 222.73 \, \Omega \text{ and } R_g = 11.13 \text{ k}\Omega$$

Solution : 8

- | | |
|--------------------------------|------------------------------------|
| (i) Resonant frequency | $\omega_0 = 10.05 \text{ rad/sec}$ |
| (ii) Q factor | $Q = 5.02$ |
| (iii) Bandwidth | $\beta = 2$ |
| (iv) Impedance under resonance | $Z_0 = R = 40 \, \Omega$ |

Solution : 9

- | | |
|------|--|
| (i) | $\omega_0 = \frac{1}{\sqrt{LC}}$ |
| (ii) | $Z_{xy} = R_1 + R_2$ |
| | $i(t) = \frac{V}{R_1 + R_2} \sin \omega t$ |

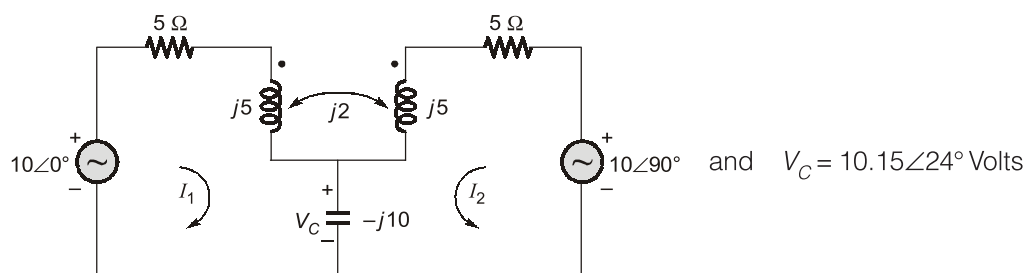Solution : 10

■ ■ ■ ■

3

Network Theorems

LEVEL 1 Objective Solutions


1. (b)
2. (a)
3. (160)
4. (5)
5. (b)
6. (d)

© Copyright: Subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced or utilised in any form without the written permission.

LEVEL 2 Objective Solutions

7. (257.99)
8. (1)
9. (c)
10. (b)
11. (1.797)
12. (c)
13. (c)
14. (0.8)

■■■■

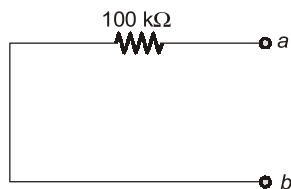LEVEL 3 Conventional Solutions**Solution : 1****Solution : 2**

$$R_L = R_N = 2.5 \, \Omega \text{ and } P_{\max} = 15.625 \, \text{W}$$

Solution : 3

$$i_0 = -0.4706 \, \text{A}$$

Solution : 4

$$I_L = \frac{V_{0.c}}{R_{Th} + R_L} = -46.15 \, \text{mA} \quad (\text{i.e., } 46.15 \, \text{mA anticlockwise})$$

Solution : 5

$$\text{Meter current} = 0.255 \, \text{mA}$$

Solution : 6

$$i_L(t) = (82.848 - 84.50e^{-0.243t} + 1.654e^{-12.418})u(t) \, \text{A}$$

Solution : 7

$$P_{R_L} = 4.05 \, \text{W}, \, P_{R_L/2} = 8.1 \, \text{W} \text{ and } P_{R_L/3} = 12.15 \, \text{W}$$

Solution : 8

$$I = \frac{4}{3} \, \text{A}$$



4

Transient State Analysis

LEVEL 1 Objective Solutions

1. (b)
2. (b)
3. (a)
4. (b)
5. (c)
6. (d)
7. (b)
8. (d)
9. (b)
10. (6.99)

© Copyright: Subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced or utilised in any form without the written permission.

LEVEL 2 Objective Solutions

11. (2.54)
12. (a)
13. (5.41)
14. (54.14)
15. (b)
16. (b)
17. (c)
18. (c)
19. (d)
20. (1)
21. (0.25)
22. (c)

■■■■

LEVEL 3 Conventional Solutions**Solution : 1**

$$v_o(t) = 80 \sin(2t) \text{ V}$$

Solution : 2

$$i(t) = 5te^{-2t} u(t) \text{ A}$$

Solution : 3

$$i = e^{-200t} (2.04 \sin 979.8 t) \text{ Amp}$$

Solution : 4

$$\frac{di(0^+)}{dt} = -40 \text{ A/s} \quad \text{and} \quad \frac{d^2i(0^+)}{dt^2} = 800 \text{ A/s}^2$$

Solution : 5

$$V_C(t) = (e^{-(t-1)} + e^{-t}) \text{ V}$$

Solution : 6

$$I(s)_{ss} = 2 \text{ mA} \quad \text{and} \quad \tau = 0.3125 \text{ msec.}$$

Solution : 7

$$V_o(t) = 75e^{-10(t-t_0)} \text{ V}$$

At $t = t_0$,

$$V_o = 75 \text{ V}$$

At $t = 25 \text{ m sec}$,

$$V_o = 75e^{-10(25 \times 10^{-3} - t_0)} \text{ V}$$

At $t \rightarrow \infty$,

$$V_o = 0 \text{ V}$$

Solution : 8

$$i_1(t) = (5 - e^{-t/5}) u(t) \text{ A}$$

Solution : 9

$$i_R(t) = 0.1 e^{-2000t} \text{ for } t > 0$$

Solution : 10

$$V_C(0^+) = V_C(0^-) = 2 \text{ V}$$

$$i_L(0^-) = i_L(0^+) = 0 \text{ A}$$

$$\frac{dV_C(0^+)}{dt} = 16 \text{ V/S}$$

$$\frac{di_L(0^+)}{dt} = 2 \text{ A/S}$$

■■■■

5

Two-Port Network Parameters

LEVEL 1 Objective Solutions

1. (a)
2. (4)
3. (85)
4. (0.5)
5. (d)
6. (c)
7. (d)
8. (c)

© Copyright: Subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced or utilised in any form without the written permission.

LEVEL 2 Objective Solutions

9. (d)
10. (c)
11. (d)
12. (11.11)
13. (d)
14. (b)
15. (c)
16. (b)
17. (3)
18. (c)

■ ■ ■ ■

LEVEL 3 Conventional Solutions**Solution : 1**

$$R_{11} = 13 \, \Omega$$

Solution : 2

$$y_{11} = 0.233 \, \text{S}$$

Solution : 3

Reciprocal network : A network is reciprocal when the ratio of response at port 2 to the excitation at port '1' is same as the ratio of response at port 1 to the excitation at port 2.

$$Y = \begin{bmatrix} 2 & -\frac{1}{2} \\ -\frac{1}{2} & +\frac{1}{2} \end{bmatrix}$$

Here,

$$Y_{12} = Y_{21} \quad (\text{Given network is reciprocal})$$

Solution : 4


$$h_{12} = 1.2, \, Z_{12} = 9.6 \, \Omega \text{ and } Y_{12} = -0.24 \, \text{S}$$

Solution : 5

$$[h] = \begin{bmatrix} 0.375 & 3 \\ -0.25 & 0.667 \end{bmatrix}$$

Solution : 6

$$I_1 = 24 \, \text{A}, \, I_2 = 1.5 \, \text{A} \text{ and } I_3 = 6.5 \, \text{A}$$

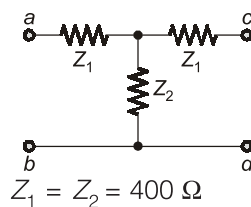Solution : 7**Solution : 8**

Parameter	Condition for reciprocal
Z	$Z_{12} = Z_{21}$
Y	$y_{12} = y_{21}$
h	$h_{12} = -h_{21}$
$ABCD$	$AD - BC = 1$

Solution : 9

$$v_2(t) = (0.037 + 0.0456 e^{-1.902t} - 0.083 e^{-7.098t})u(t)$$

Solution : 10

$$[Z_n] = \begin{bmatrix} 1.72 & 1.22 \\ 1.22 & 2.22 \end{bmatrix}$$

Solution : 11

$$[y] = \begin{bmatrix} \frac{5s}{3} & -\frac{4s}{3} \\ -\frac{4s}{3} & \frac{5s}{3} \end{bmatrix}$$

■■■■

6

Network Synthesis and Graph Theory

LEVEL 1 Objective Solutions

1. (c)
2. (b)
3. (d)
4. (c)
5. (c)

© Copyright: Subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced or utilised in any form without the written permission.

LEVEL 2 Objective Solutions


6. (c)
7. (a)
8. (c)
9. (b)
10. (c)

■ ■ ■ ■

LEVEL 3 Conventional Solutions


Solution : 1

The Tie-set matrix is shown below:

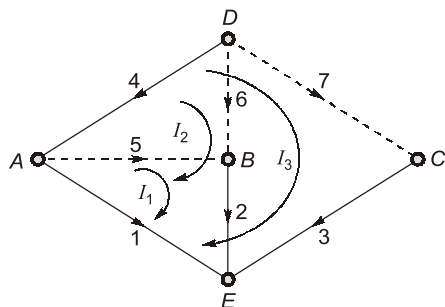


Loop currents	Branches						
	1	2	3	4	5	6	7
I_1	-1	1	0	0	1	0	0
I_2	-1	1	0	-1	0	1	0
I_3	-1	0	1	-1	0	0	1

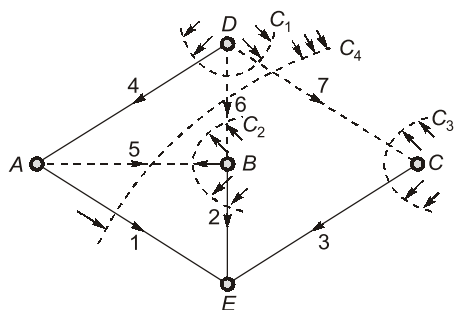The necessary cut-set matrix is shown below:



Cut-Sets	Branches						
	1	2	3	4	5	6	7
C_1	0	0	0	1	0	1	1
C_2	0	1	0	0	-1	-1	0
C_3	0	0	1	0	0	0	-1
C_4	1	0	0	0	1	1	1

Solution : 2

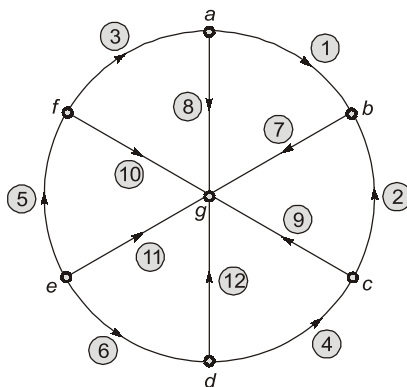

Fundamental cut set matrix:

f cut set	Branches											
	1	2	3	4	5	6	7	8	9	10	11	12
$f-1$	1	0	-1	0	0	0	0	1	0	0	0	0
$f-2$	-1	-1	0	0	0	0	1	0	0	0	0	0
$f-3$	0	1	0	-1	0	0	0	0	1	0	0	0
$f-4$	0	0	0	1	0	-1	0	0	0	0	0	1
$f-5$	0	0	0	0	1	1	0	0	0	0	1	0
$f-6$	0	0	1	0	-1	0	0	0	0	1	0	0

Solution : 3

$$I(t) = 2t - 12e^{-2t} + 24e^{-3t} \text{ A}$$

Solution : 4

$$Y_{12}(s) = -\left(\frac{R_1 + R_2 + Ls}{R_1 R_2}\right)$$

$$Z_{12}(s) = -\frac{(R_2 + Ls)}{R_1}$$

$$Z_{11}(s) = \frac{R_1(R_2 + Ls)}{R_1 + R_2 + Ls}$$

$$Z_{22}(s) = -R_2$$

■■■■