

# 2020

## **RANK** *Improvement* **WORKBOOK**



**Answer key and Hint of  
Objective & Conventional *Questions***

---

**Electrical Engineering**  
Power Electronics



**MADE EASY**  
Publications

# 1

## Power Semiconductor Devices

### LEVEL 1 Objective Questions

1. (a)

2. (b)

3. (b)

4. (a)

5. (d)

6. (d)

7. (c)

8. (b)

9. (b)

10. (b)

11. (b)

12. (a)

13. (c)

© Copyright: Subject matter to MADE EASY Publications, New Delhi: No part of this book may be reproduced or utilised in any form without the written permission.

### LEVEL 2 Objective Questions

14. (d)

15. (1.51)

16. (c)

17. (d)

18. (b)

19. (0.67)

20. (2.93)

21. (c)

22. (34.17)

23. (7)

■■■■


**LEVEL 3** Conventional Questions

**Solution : 1**

Before the initiation of turn-off process, a GTO carries a steady current  $I_a$ . This figure shows a typical turn-off dynamic characteristic for a GTO. The total turn off time  $t_q$  is subdivided into three different periods; namely the storage period ( $t_s$ ), the fall period ( $t_f$ ) and the tail period ( $t_t$ ). In other words,

$$t_q = t_s + t_f + t_t$$

Initiation of turn-off process starts as soon as negative gate current begins to flow after  $t = 0$ . The rate of rise of this gate current depends upon the gate circuit inductance and the gate voltage applied. During the storage period, anode current  $I_a$  and anode voltage (equal to on-state voltage drop) remain constant. Termination of the storage period is indicated by a fall in  $I_a$  and rise in  $V_a$ .

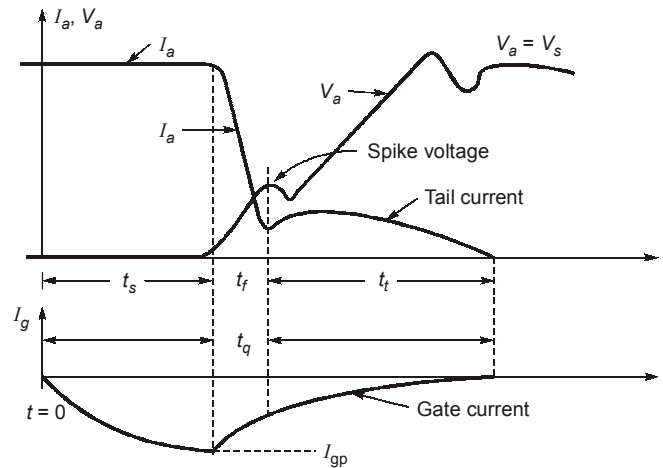

During  $t_s$ , excess charges, i.e. holes in p-base are removed by negative gate current and the centre junction comes out of saturation. In other words, during storage time  $t_s$ , the negative gate current rises to a particular value and prepares the GTO for turning-off (or commutation) by flushing out of the stored carriers. After  $t_s$ , anode current begins to fall rapidly and anode voltage starts rising. As shown in figure, the anode current falls to a certain value and then abruptly changes its rate of fall. Interval during which anode current falls rapidly is the fall time  $t_f$  figure and is of the order of 1  $\mu\text{sec}$  [4]. The fall period  $t_f$  is measured from the instant gate current is maximum negative to the instant anode current falls to its tail current.

At the time  $t = t_s + t_f$  there is a spike in voltage due to abrupt current change. After  $t_f$ , anode current  $I_a$  and anode voltage  $V_a$  keep moving towards their turn-off values for a time  $t_t$  called tail time. After  $t_t$ , anode current reaches zero value.

A GTO has the following disadvantage as compared to a conventional thyristor:


- (i) Magnitude of latching and holding currents is more in a GTO.
- (ii) On state voltage drop and the associated loss is more in a GTO.
- (iii) Due to the multicathode structure of GTO, triggering gate current is higher than that required for a conventional SCR.
- (iv) Gate drive circuit losses are more
- (v) Its reverse-voltage blocking capability is less than its forward-voltage blocking capability. But this is no disadvantage so far as inverter circuits are concerned.

In spite of all these demerits, GTO has the following advantages over an SCR:

- (i) GTO has faster switching speed.
- (ii) Its surge current capability is comparable with an-SCR.
- (iii) It has more  $di/dt$  rating at turn-on.
- (iv) GTO circuit configuration has lower size and weight as compared to SCR circuit unit.
- (v) GTO unit has higher efficiency because an increase gate-drive power loss and on-state loss is more than compensated by the elimination of forced commutation losses.
- (vi) GTO unit has reduced acoustical electromagnetic noise due to elimination of commutation chokes.

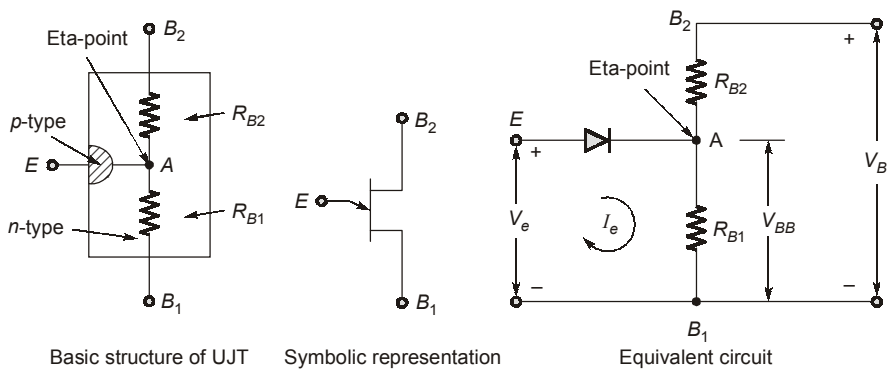**Solution : 2**

An UJT is made up of an n-type silicon (Si) base to which p-type emitter is embedded. It has three terminals the emitter (E), base one  $B_1$  and base two  $B_2$  between bases  $B_1$  and  $B_2$ , the Unijunction behave like ordinary resistance.




In figure (a), when source voltage  $V_{BB}$  is applied, capacitor  $C$  begins to charge through  $R$  exponentially towards  $V_{BB}$ . During this charging, emitter circuit of UJT is an open circuit.

The capacitor voltage  $v_c$ , equal to emitter voltage  $v_e$ , is given by

$$v_c = v_e = V_{BB} (1 - e^{-t/RC})$$

The time constant of the charge circuit is  $\tau_1 = RC$ .

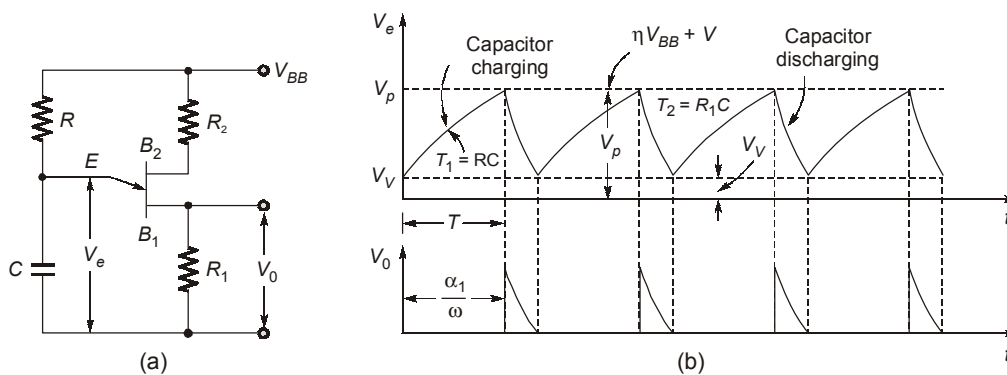

**Fig. (2) UJT oscillator (a) Connection diagram and (b) Voltage waveforms**

When this emitter voltage  $v_e$  (or  $v_c$ ) reaches the peak-point voltage  $V_p (= \eta V_{BB} + V_D)$ , the Unijunction between  $E-B_1$  breaks down. As a result, UJT turns on and capacitor  $C$  rapidly discharge through low resistance  $R_1$  with a time constant  $\tau_2 = R_1 C$ . Here  $\tau_2$  is much smaller than  $\tau_1$ . When the emitter voltage decays to the valley-point voltage  $V_v$ , UJT turns off. The time  $T$  required for capacitor  $C$  to charge from initial voltage  $V_v$  to peak-point voltage  $V_p$ , through large resistance  $R$ , can be obtained as under:

Assuming,

$$V_p = \eta V_{BB} + V_D = V_v + V_{BB}(1 - e^{-T/RC})$$

$$V_D = V_v, \eta = (1 - e^{-T/RC})$$

$$T = \frac{1}{f} = RC \ln\left(\frac{1}{1-\eta}\right)$$

In case  $T$  is taken as the time period of output pulse duration (neglecting small discharge time), then the value of firing angle  $\alpha_1$  is given by

$$\alpha_1 = \omega T = \omega RC \ln \frac{1}{1-\eta}$$


where 'ω' is the angular frequency of UJT oscillator.

**Solution : 3**

The power-generated in the junction region of a thyristor in a normal operation consists of the following components of dissipation:

1. Forward-conduction
2. Turn-off or commutation
3. Turn-on switching
4. Forward and Reverse blocking
5. Gate pulse triggering

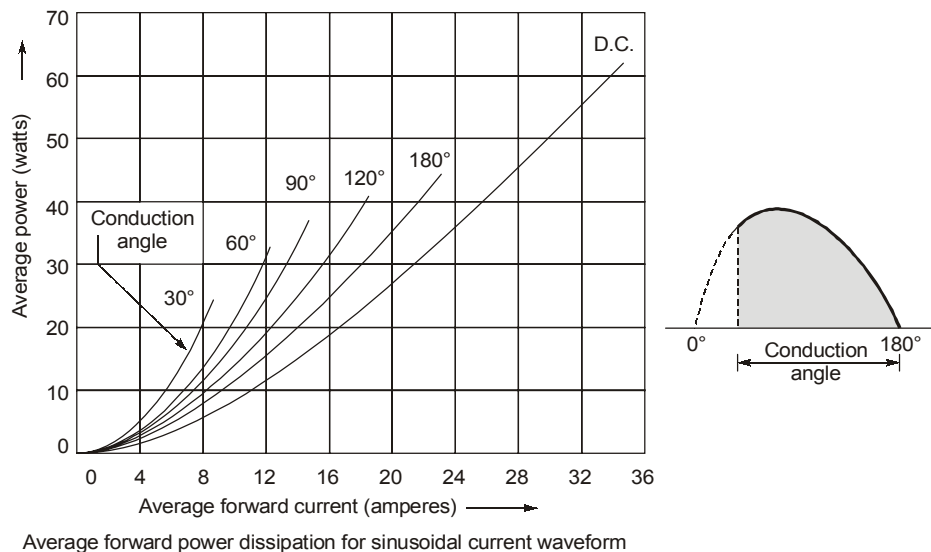**1. Forward Conduction Loss:** The average anode current multiplied by the forward voltage drop across the SCR is the average power dissipated in the thyristor. ON state conduction losses are the major source of junction heating for normal duty cycle and power-frequencies. figure shown below illustrates the variation of the ON state average conduction loss in watts with the average current in amperes for various conduction angles for operation on from 50 Hz to 400 Hz. This type of information is generally supplied by the manufacturer. The curve marked d.c. is applicable for continuous direct-current. These curves are based on the current waveform which is the remainder of the half-sine wave which results when delayed angle triggering is used in a single phase resistive load circuit. These power curves are integrated product of the instantaneous anode current and ON state voltage drop. This integration can be performed graphically or analytically for conduction angles other than those listed, using the ON state voltage-current characteristic curves for the specific device. In the line commutated converters and a.c. regulator circuits, the forward conduction loss is the major source of junction heating.



2. **Turn-on Losses:** Since the switching process takes a finite time, there is a relatively high voltage across the thyristor while a current flows. Therefore, this loss is rather higher than the turn-off loss. For example, by the time the current has reached 90 per cent of its final value, there may still be 10 percent of the supply voltage across the device. Accordingly, appreciable power may be dissipated during this turn-on interval. Above 400 Hz switching, additional circuitry is used to reduce the switching losses or else some derating of the normal forward current is made to allow for the extra dissipation.
3. **Turn-off Losses:** The turn-off power losses arises during the time of decay of reverse current, according to the product of the instantaneous values of reverse current and reverse voltage, may reach high peak values up to several kilowatts. It is possible during rapid turn-off for the reverse current to rise to a value comparable to the forward current. When the thyristor impedance starts to increase, dissipation occurs as the current falls and the reverse voltage builds up. To limit the rate of change of current at turn-off and hence the energy to be dissipated, circuit inductance is used. This also limits the rate of rise of forward current which is an advantage but the inductance can give rise to high reverse voltage transients during turn-off. In high frequency inverters, where the thyristors arc switched ON and OFF several times in each supply cycle, the turn-on and turn-off losses may also have to be taken into consideration while selecting the device ratings since the switching loss may constitute a significant portion of the total loss.
4. **Forward and Reverse Blocking Losses:** As mentioned in the previous section, a thyristor has different regions of operation. In the forward blocking region, anode is made positive with respect to cathode and the anode current is the small forward leakage current. Therefore, the forward blocking power loss is the integration of product of the forward blocking voltage and forward leakage current. Similarly, reverse power loss occurs in reverse blocking region. The forward power loss is generally small compared to the conduction-loss.
5. **Gate Power Loss:** The gate power loss is the mean power loss due to gate current between the gate and main terminals. Gate losses are negligible for pulse types of triggering signals. Losses may become more significant for gate signals with a high duty cycle.


**Solution : 4**

Average energy loss in the transistor = Average energy loss during turn-off + Average energy loss during turn on

$$\begin{aligned}
 \text{Average energy loss during turn on} &= \int_0^{t_{\text{on}}} i_c v_{CE} dt \\
 i_C &= \frac{100}{50 \times 10^{-6}} (t) = m_1 t \\
 v_{CE} &= m_2 t + C = -\frac{200}{40 \times 10^{-6}} t + 200 \\
 &= \int_0^{t_{\text{on}}} \left[ \frac{100}{50 \times 10^{-6}} t \right] \left[ 200 - \frac{200t}{40 \times 10^{-6}} \right] dt \\
 &= \int_0^{t_{\text{on}}} [2 \times 10^6 t] [200 - 5 \times 10^6 t] dt
 \end{aligned}$$

$$\begin{aligned}
 &= \left[ \frac{400 \times 10^6 t^2}{2} \right]_0^{t_{\text{on}}=40 \mu\text{s}} - \left[ \frac{10 \times 10^{12} t^3}{3} \right]_0^{t_{\text{on}}} \\
 &= \frac{400 \times 10^6 \times (40)^2 \times 10^{-12}}{2} - \left[ \frac{10 \times 10^{12} \times (40)^3 \times (10^{-6})^3}{3} \right] \\
 &= 40 \times 8000 \times 10^{-6} - \left[ \frac{10 \times 64 \times 10^3 \times 10^{-6}}{3} \right] \\
 &= 320000 \times 10^{-6} - \frac{64}{3} \times 10^{-2} \\
 &= \left[ 32 - \frac{64}{3} \right] \times 10^{-2} = \frac{32}{3} \times 10^{-2} = 0.1067 \text{ Watt-sec}
 \end{aligned}$$

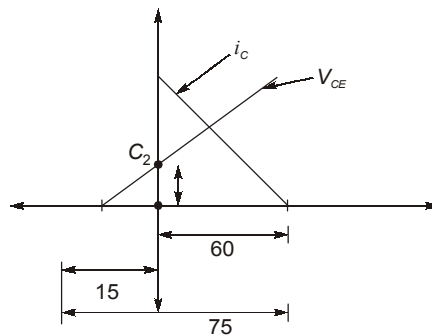Average power loss during turn-off =  $\int_0^{t_{\text{off}}} i_C V_{CE} dt$



$$\begin{aligned}
 C_2 &= m_2 \times 15 \times 10^{-6} \\
 &= \frac{200 \times 15 \times 10^{-6}}{75 \times 10^{-6}} = 40
 \end{aligned}$$

$$i_C = m_1 t + C = \left[ -\frac{100}{60 \times 10^{-6}} t + 100 \right]$$

$$V_{CE} = m_2 t + C_2 = \left[ \frac{200}{75} \times 10^6 t + 40 \right]$$

$$= \int_0^{t_{\text{off}}=60 \mu\text{s}} \left[ 100 - \frac{100t \times 10^6}{60} \right] \left[ 40 + \frac{200 \times 10^6 t}{75} \right] dt$$

$$= [4000t]_0^{t_{\text{off}}} + \left[ \frac{200 \times 10^6 t^2}{75 \times 2} \times 100 \right]_0^{t_{\text{off}}} - \left[ \frac{40 \times 100 \times 10^6 t^2}{60 \times 2} \right]_0^{t_{\text{off}}} - \left[ \frac{100 \times 10^6 \times 200 \times 10^6 t^3}{60 \times 75 \times 3} \right]_0^{t_{\text{off}}}$$

$$= 0.24 + 0.48 - 0.12 - 0.32$$

$$= 0.28 \text{ Watt-sec}$$

Total energy loss in one cycle = 0.1067 + 0.2800

$$= 0.3867 \text{ Watt-sec}$$

Average power loss in transistor = Switching frequency  $\times$  Average energy loss in one cycle


$$f = \frac{300}{0.3867} = 775.79 \text{ Hz}$$

**Solution : 5**

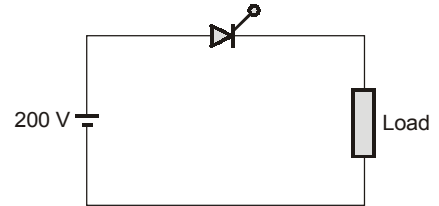(a) 
$$E = L \frac{di}{dt} \Rightarrow 200 = 0.2 \frac{di}{dt}$$

$$\Rightarrow 200 = 0.2 \frac{I_{latch}}{t_{gate\ width}}$$

$$\Rightarrow t_{gate\ width} = \frac{0.2 \times 100 \times 10^{-3}}{200} = 100 \mu\ sec$$



(b) 
$$E = Ri + L \frac{di}{dt}$$

$$i = \frac{E}{R} (1 - e^{-\frac{R}{L}t})$$


$$\Rightarrow 0.100 = \frac{200}{20} (1 - e^{-100t}) \Rightarrow 0.01 = 1 - e^{-100t}$$

$$\Rightarrow e^{-100t} = 0.99 \Rightarrow -100t = -0.010050$$
  
$$t = 100.503 \mu\ s$$

(c) 
$$i = \frac{E}{R} \left[ 1 - e^{-\frac{R}{L}t} \right]$$

$$0.100 = \frac{200}{20} (1 - e^{-10t})$$
  
$$t = 1005.03 \mu\ -sec$$

**Solution : 6**

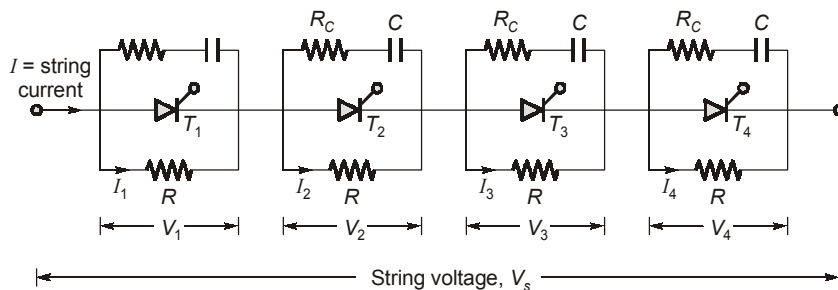

$I$  = string current in off state

$R$  = state equalizing resistance

$R_C$  = Dynamic equalizing resistance

$C$  = Dynamic equalizing capacitance

$I_1, I_2, I_3, I_4$  = Currents through  $R$

(a) **During static conditions:**

- Capacitors will be out of circuit and hence no current will flow through  $R_C$  and  $C$ .
- Leakage currents will flow through SCRs.



$$\text{Voltage across } T_1 = (I - 0.022) \times 25000 = V_1$$

$$\text{Voltage across } T_2 = (I - 0.026) \times 25000 = V_2$$

$$\text{Voltage across } T_3 = (I - 0.020) \times 25000 = V_3$$

$$\text{Voltage across } T_4 = (I - 0.018) \times 25000 = V_4$$

$$V_1 + V_2 + V_3 + V_4 = V_5$$

$$25000(4I - 0.085) = 10000$$

$$4I - 0.085 = 0.4$$

$$I = 0.121 \text{ A}$$

$$V_1 = 25000 \times (0.121 - 0.022) = 2475 \text{ V}$$

$$V_2 = 25000 \times (0.121 - 0.026) = 2375 \text{ V}$$

$$V_3 = 25000 \times (0.121 - 0.020) = 2525 \text{ V}$$

$$V_4 = 25000 \times (0.121 - 0.018) = 2575 \text{ V}$$

(b) **During dynamic conditions:**

At time of turn-on capacitors will short-circuit.

$$I_{C1} = \text{Discharge current through capacitor 1} = \frac{V_1}{R_1} = \frac{2475}{50} = 49.5 \text{ A}$$

$$I_{C2} = \text{Discharge current through capacitor 2} = \frac{V_2}{R_2} = \frac{2375}{50} = 47.5 \text{ A}$$

$$I_{C3} = \text{Discharge current through capacitor 3} = \frac{V_3}{R_3} = \frac{2525}{50} = 50.5 \text{ A}$$

$$I_{C4} = \text{Discharge current through capacitor 4} = \frac{V_4}{R_4} = \frac{2575}{50} = 51.5 \text{ A}$$

(c)

Derating factor = 1 – string efficiency

$$= 1 - \frac{(\text{Actual voltage of whole string})}{(\text{Number of SCR} \times \text{Individual rating})}$$

$$= 1 - \frac{10000}{4 \times 3000} = 1 - \frac{10000}{12000}$$

$$= 1 - 0.833 = 0.1667 \text{ or } 16.67\%$$



# 2

## Controlled & Uncontrolled Rectifiers

### LEVEL 1 Objective Questions

1. (c)
2. (c)
3. (b)
4. (0.70)
5. (a)
6. (147.51)
7. (1.66)
8. (0.0170)
9. (a)
10. (b)
11. (b)
12. (a)
13. (11.99)
14. (170)
15. (b)
16. (c)
17. (c)

© Copyright: Subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced or utilised in any form without the written permission.


### LEVEL 2 Objective Questions

18. (b)
19. (19.96)
20. (9.28)
21. (0.955)
22. (b)
23. (b)
24. (d)
25. (d)
26. (b)
27. (10)
28. (c)
29. (5.03)
30. (17.25)

■■■■

**LEVEL 3** Conventional Questions

**Solution : 1**

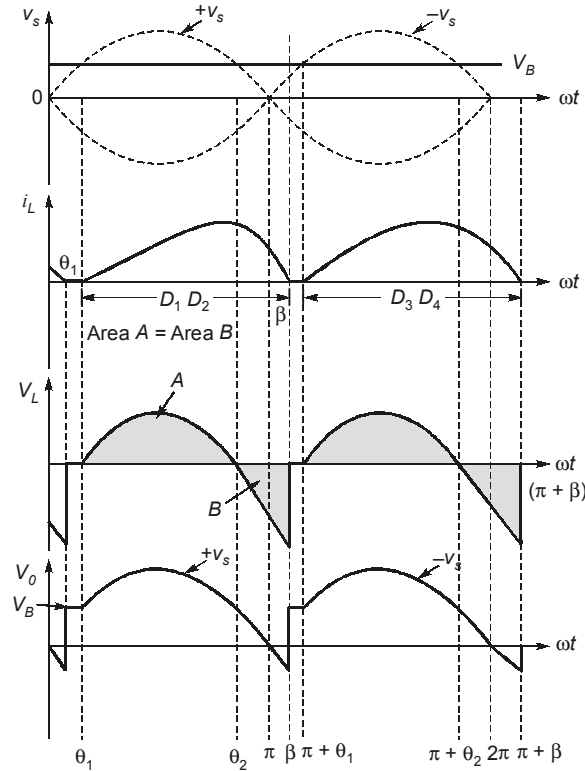

$$\theta_1 \leq \omega t \leq \beta$$

KVL :  $D_1 D_2 \rightarrow$  ON

$$\begin{aligned} -V_S + V_L + V_B &= 0 \\ V_L &= V_S - V_B \\ V_L &= V_m \cdot \sin \omega t - V_B \end{aligned}$$

$$L \frac{di_L}{dt} = V_m \sin \omega t - V_B$$

$$\int di_L = \frac{1}{L} \int [V_m \sin \omega t - V_B] \cdot dt$$

$$i_L = \frac{-V_m}{\omega L} \cos \omega t - \frac{V_B \cdot t}{L} + K$$

Use initial conditions to find K.

At  $\omega t = \theta_1$ ,

$$i_L = 0$$


$$0 = \frac{-V_m}{\omega L} \cos \theta_1 - \frac{V_B \cdot \theta_1}{\omega L} + K$$

$$K = \frac{1}{\omega L} [V_m \cos \theta_1 + V_B \theta_1]$$

$$I_{L \text{ avg}} = \frac{1}{\pi} \int_{\theta_1}^{\beta} i_L \cdot d(\omega t)$$

**Solution : 2**

Single-phase diode bridge rectifier:

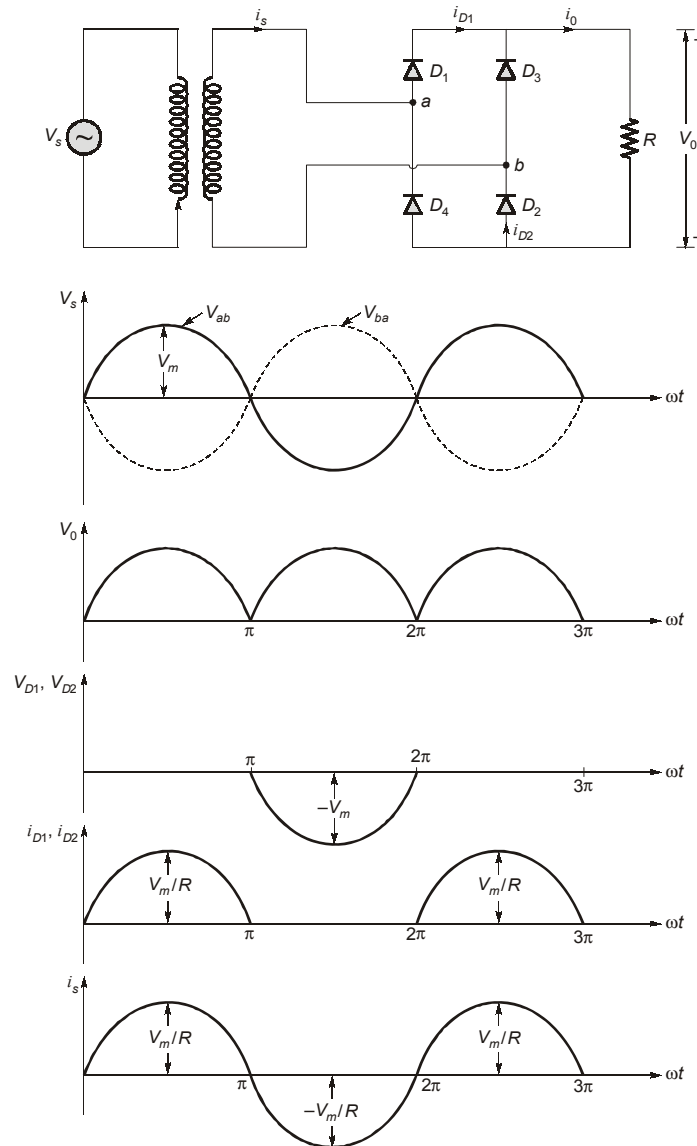

When 'a' is positive with respect to 'b' diode  $D_1$ ,  $D_2$  conduct together so that output voltage is  $V_{ab}$ . Each of the diodes  $D_3$  and  $D_4$  is subjected to a reverse voltage of  $V_s$ .

When 'b' is positive with respect to 'a', diodes  $D_3$ ,  $D_4$  conduct together and output voltage is  $V_{ba}$ . Each of the two diodes  $D_1$  and  $D_2$  experience a reverse voltage of  $V_s$ .

Average value of output voltage,

$$V_0 = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d(\omega t) = \frac{2V_m}{\pi}$$

Average output current,

$$I_0 = \frac{V_0}{R}$$

Rms value of output voltage,

$$V_{or} = \left[ \frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t d(\omega t) \right]^{1/2} = \frac{V_m}{\sqrt{2}} = V_s$$

Rms value of load current,

$$I_{or} = \frac{V_s}{R}$$

Form factor,

$$FF = \frac{V_{or}}{V_0} = \frac{V_m/\sqrt{2}}{2V_m/\pi} = \frac{\pi}{2\sqrt{2}} = 1.11$$

Ripple voltage,

$$V_r = \sqrt{V_{or}^2 - V_0^2} = \left[ \left( \frac{V_m}{\sqrt{2}} \right)^2 - \left( \frac{2V_m}{\pi} \right)^2 \right]^{1/2} = 0.30776 V_m$$

Voltage ripple factor,

$$VRF = \frac{V_r}{V_0} = \frac{0.30776 V_m}{2V_m/\pi} = 0.4834$$

Transformer utilization factor,  $TUF = \frac{P_{dc}}{\text{VA rating of transformer}}$

Rms value of source voltage,  $V_s = \frac{V_m}{\sqrt{2}}$

Rms value of source current,  $I_s = \frac{I_m}{\sqrt{2}}$


$$\text{VA rating of transformer} = V_s I_s = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = \frac{V_m I_m}{2}$$

$$P_{dc} = V_0 I_0 = \frac{2V_m}{\pi} \cdot \frac{2I_m}{\pi} = \left( \frac{2}{\pi} \right)^2 \cdot V_m I_m$$


So, 
$$TUF = \frac{P_{dc}}{\text{VA rating of transformer}} = \frac{\frac{4}{\pi^2} V_m I_m}{V_m I_m / 2} = \frac{8}{\pi^2} = 0.81057$$

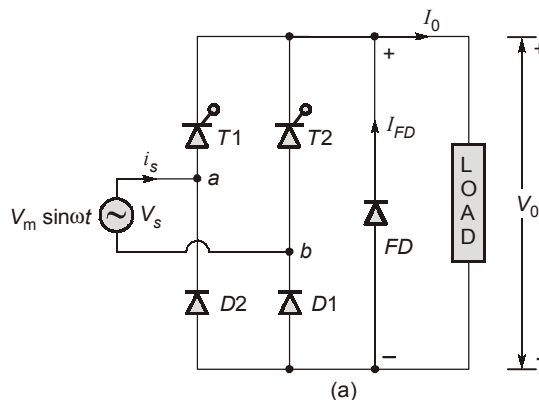**Solution : 3**

1- $\phi$  semiconverter circuit is shown in figure (a).



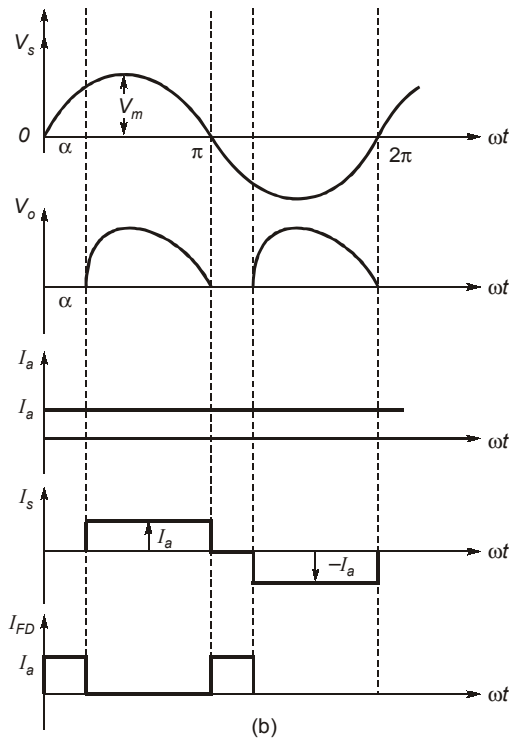- The load current is assumed to be continuous and ripple free.
- The various waveforms  $V_s$ ,  $V_0$ ,  $I_a$  and  $I_s$  are shown in figure (b).



- The instantaneous input current  $i_s(t)$  can be expressed in Fourier series as:

$$i_s(t) = a_0 + \sum_{n=1,2,3}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$$

where,

$$a_0 = \frac{1}{2\pi} \int_0^{2\pi} i_s(t) d(\omega t)$$

$$a_n = \frac{1}{\pi} \int_0^{2\pi} i_s(t) \cdot \cos n\omega t \cdot d(\omega t)$$

and

$$b_n = \frac{1}{\pi} \int_0^{2\pi} i_s(t) \cdot \sin n\omega t \cdot d(\omega t)$$

$$a_0 = \frac{1}{2\pi} \left[ \int_{\alpha}^{\pi} i_a \cdot d(\omega t) - \int_{\pi+\alpha}^{2\pi} I_a \cdot d(\omega t) \right] = 0$$

$$a_n = \frac{1}{\pi} \left[ \int_{\alpha}^{\pi} i_a \cos n\omega t \cdot d(\omega t) - \int_{\pi+\alpha}^{2\pi} I_a \cos n\omega t \cdot d(\omega t) \right]$$

$$= \frac{I_a}{n\pi} \left[ \left| \sin n\omega t \right|_{\alpha}^{\pi} \right] - \left[ \left| \sin n\omega t \right|_{n+\alpha}^{2\pi} \right]$$

$$= -\frac{2I_a}{n\pi} \sin n\alpha \dots \dots \dots \text{for } n = 1, 3, 5 \dots \dots$$

$$= 0 \dots \dots \dots \text{for } n = 2, 4, 6 \dots \dots$$

$$b_n = \frac{1}{\pi} \left[ \int_{\alpha}^{\pi} I_a \sin n\omega t \cdot d(\omega t) - \int_{n+\alpha}^{2\pi} I_a \sin n\omega t \cdot d(\omega t) \right]$$

$$= \frac{2I_a}{n\pi} (1 + \cos n\alpha) \dots\dots\dots \text{for } n = 1, 3, 5 \dots\dots\dots$$

$$= 0 \dots\dots\dots \text{for } n = 2, 4, 6$$

$$C_n = \left[ \left( -\frac{2I_a}{n\pi} \sin n\alpha \right)^2 + \left( \frac{2I_a}{n\pi} (1 + \cos n\alpha) \right)^2 \right]^{1/2} = \frac{2\sqrt{2}I_a}{n\pi} (1 + \cos n\alpha)^{1/2}$$

as we know,  $1 + \cos\theta = 2\cos^2 \frac{n\theta}{2}$

$$C_n = \frac{2\sqrt{2}I_a}{n\pi} \left[ 2\cos^2 \frac{n\alpha}{2} \right]^{1/2} = \frac{4I_a}{n\pi} \cos \frac{n\alpha}{2}$$

$$\theta_n = \tan^{-1} \left( \frac{a_n}{b_n} \right) = \tan^{-1} \left[ -\frac{\sin n\alpha}{1 + \cos n\alpha} \right] = \tan^{-1} \left[ -\frac{2\sin \frac{n\alpha}{2} \cdot \cos \frac{n\alpha}{2}}{2\cos^2 \frac{n\alpha}{2}} \right] = -\frac{n\alpha}{2}$$

Hence, 
$$i_s(t) = \sum_{n=1,3,5}^{\infty} \frac{4I_a}{n\pi} \cos \frac{n\alpha}{2} \cdot \sin \left( n\omega t - \frac{n\alpha}{2} \right)$$

Rms value of nth harmonic input current,

$$I_{sn} = \frac{4I_a}{\sqrt{2}n\pi} \cos \frac{n\alpha}{2} = \frac{2\sqrt{2}}{n\pi} I_a \cdot \cos \frac{n\alpha}{2}$$

Hence, Rms value of the fundamental current,

$$I_{s1} = \frac{2\sqrt{2}}{n\pi} I_a \cdot \cos \frac{\alpha}{2} \quad \text{for } n = 1$$

Rms value of total input current,

$$I_s = \left[ \frac{I_a^2(\pi - \alpha)}{\pi} \right]^{1/2} = I_a \left[ \frac{\pi - \alpha}{\pi} \right]^{1/2}$$

$$CDF = \frac{I_{s1}}{I_s} = \left( \frac{2\sqrt{2}}{\pi} I_a \cos \frac{\alpha}{2} \right) \times \left( \frac{\sqrt{\pi}}{I_a \sqrt{\pi - \alpha}} \right) = \frac{2\sqrt{2} \cos \frac{\alpha}{2}}{\sqrt{\pi(\pi - \alpha)}}$$

$$\text{Harmonic factor} = \left[ \frac{1}{CDF^2} - 1 \right]^{1/2} = \left[ \frac{\pi(\pi - \alpha)}{8\cos^2 \frac{\alpha}{2}} - 1 \right]^{1/2} = \left[ \frac{\pi(\pi - \alpha)}{4(1 + \cos \alpha)} - 1 \right]^{1/2}$$

Hence, harmonic factor of input current for  $\alpha = \pi/2$

$$= \left[ \frac{\pi(\pi - \pi/2)}{4(1 + \cos \pi/2)} - 1 \right]^{1/2} = 0.4834$$

**Solution : 4**

The given circuit is a three-phase three-pulse converter.

**Case-I:**  $\alpha \leq \frac{\pi}{6}$ , free wheeling diode will not conduct

$$i_R = I_0$$

$$i_R = 0$$

when  $T_1$  is ON

when  $T_1$  OFF

$$i_R = a_1 \cos \omega t + b_1 \sin \omega t$$

$$a_1 = \frac{1}{\pi} \int_0^{2\pi} f(\omega t) \cdot \cos \omega t \cdot d(\omega t)$$

$$= \frac{1}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} I_0 \cos \omega t \cdot d(\omega t) \quad \left[ \because T_{ON} \text{ from } \left( \frac{\pi}{6} + \alpha \right) \text{ to } \left( \frac{5\pi}{6} + \alpha \right) \right]$$

$$a_1 = \frac{\sqrt{3} I_0}{\pi} \sin \alpha$$

$$b_1 = \frac{1}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} I_0 \sin \omega t \cdot d(\omega t) = \frac{\sqrt{3} I_0}{\pi} \cos \alpha$$

$$c_1 = \sqrt{a_1^2 + b_1^2} = \frac{\sqrt{3} I_0}{\pi}$$

$$\phi_1 = \tan^{-1} \left( \frac{a_1}{b_1} \right) = \alpha$$

$$i_{R1} = c_1 \sin(\omega t + \phi_1) = \frac{\sqrt{3} I_0}{\pi} \sin(\omega t + \alpha)$$

Fundamental displacement factor = FDF =  $\cos \phi_1 = \cos \alpha$

$$\text{Distortion factor} = g = \frac{I_{R1 \text{ rms}}}{I_{R \text{ rms}}} = \frac{\frac{\sqrt{3} I_0}{\pi}}{I_0 / \sqrt{3}} = \frac{3}{\sqrt{2} \pi}$$

$$\text{Power factor} = g \times \text{FDF} = \frac{3}{\sqrt{2} \pi} \cos \alpha$$

**Case-II:**  $\alpha > \frac{\pi}{6}$  freewheeling diode will conduct

$T_1$  will conduct from  $\left( \frac{\pi}{6} + \alpha \right)$  to  $\pi$

$$i_{R1} = a_1 \cos \omega t + b_1 \sin \omega t$$

$$a_1 = \frac{1}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\pi} I_0 \cos \omega t \cdot d(\omega t) = -\frac{I_0}{\pi} \sin \left( \frac{\pi}{6} + \alpha \right)$$



$$b_1 = \frac{1}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\pi} I_0 \sin \omega t \cdot d(\omega t) = \frac{I_0}{\pi} \left[ 1 + \cos \left( \frac{\pi}{6} + \alpha \right) \right]$$

$$c_1 = \sqrt{a_1^2 + b_1^2} = \frac{I_0}{\pi} \sqrt{\sin^2 \left( \frac{\pi}{6} + \alpha \right) + \left[ 1 + \cos \left( \frac{\pi}{6} + \alpha \right) \right]^2} = \frac{2I_0}{\pi} \cos \left( \frac{\pi}{12} + \frac{\alpha}{2} \right)$$

$$I_{R_1(\text{rms})} = \frac{\sqrt{2} I_0}{\pi} \cos \left( \frac{\pi}{12} + \frac{\alpha}{2} \right)$$

$$\phi_1 = \tan^{-1} \left( \frac{a_1}{b_1} \right) = \tan^{-1} \left( -\tan \left( \frac{\frac{\pi}{6} + \alpha}{2} \right) \right) = - \left( \frac{\frac{\pi}{6} + \alpha}{2} \right)$$


$$\text{FDF} = \cos \phi_1 = \cos \left( \frac{\pi}{12} + \frac{\alpha}{2} \right)$$

$$\text{Distortion factor} = \frac{I_{s_1}}{I_s} = \frac{\frac{\sqrt{2} I_0}{\pi} \cos \left( \frac{\pi}{12} + \frac{\alpha}{2} \right)}{I_{Ox} \sqrt{\frac{5\pi - \alpha}{6}} \cdot \frac{1}{2\pi}}$$

$$\text{Digital factor} = \frac{2 \cos \left( \frac{\alpha}{2} + \frac{\pi}{12} \right)}{\sqrt{\pi \left( \frac{5\pi}{6} - \alpha \right)}}$$

$$\text{Power factor} = \frac{2 \cos^2 \left( \frac{\alpha}{2} + \frac{\pi}{12} \right)}{\sqrt{\pi \left( \frac{5\pi}{6} - \alpha \right)}}$$

**Solution: 5**

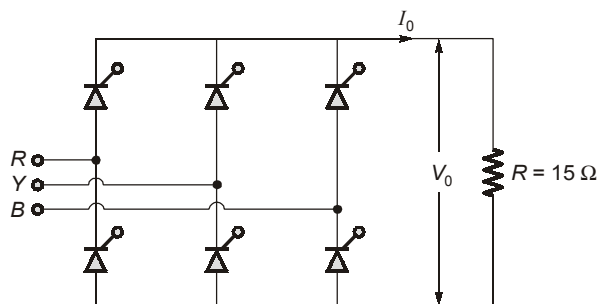

$$V_0 = \frac{1}{\pi} \int_{\frac{\pi}{3} - \left(\frac{\pi}{6} - \alpha\right)}^{\left(\frac{\pi}{6} + \alpha\right)} V_m \cos \omega t d(\omega t) = \frac{3V_m}{\pi} \cos \alpha$$

$$\alpha = 75^\circ, \quad = \frac{3\sqrt{3}V_m}{\pi} \cos 75^\circ = 0.428 V_m$$

$$\text{Power consumed by load} = 6 \text{ kW} = \frac{V_0^2}{R}$$

$$6 \times 10^3 = \frac{(0.428V_m)^2}{15}$$


$$V_m = \frac{\sqrt{6 \times 10^3 \times 15}}{0.428} = 700.9345 \text{ V}$$

**Solution : 6**


The generation of gating signals for thyristors of ac to dc converters involves the following steps:

1. Zero crossing detection of input voltage.
2. Phase shifting of the signals to the required value.
3. Pulse shaping to generate pulses of short duration.
4. Pulse isolation through pulse transformers.

**Block diagrams:**

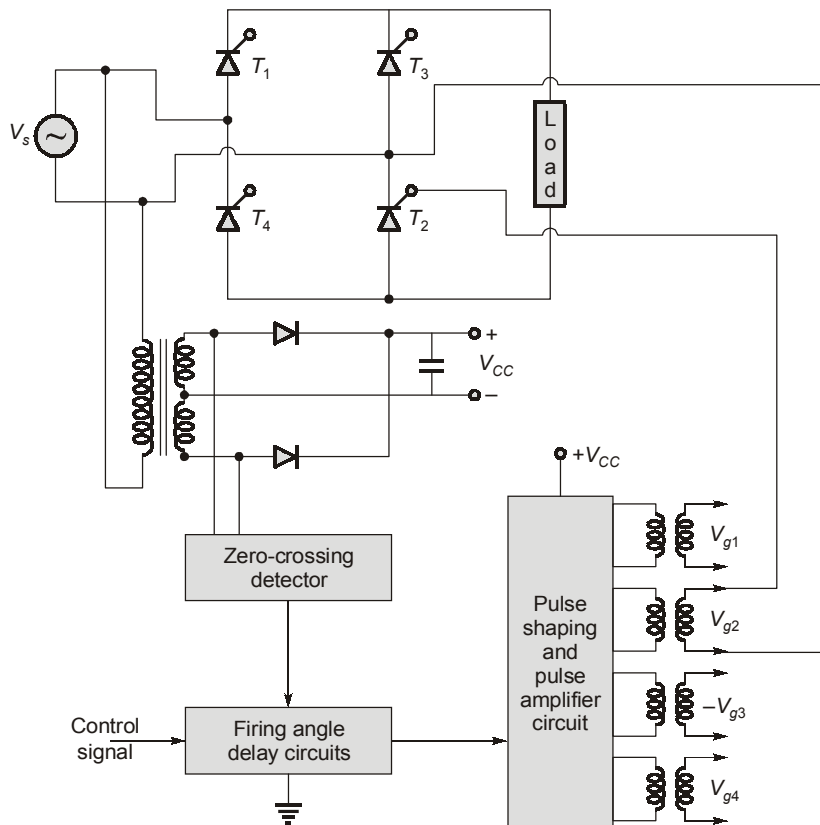

**Solution : 7**

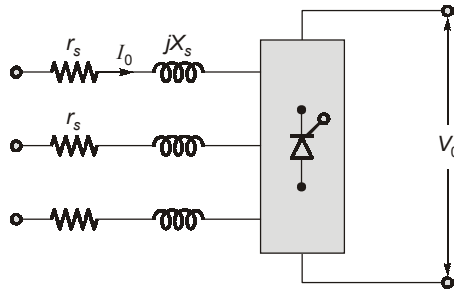

Power circuit diagram above shows that source resistance  $r_s$  will lead to a voltage drop of  $2I_0r_s$ . Two thyristors, one from positive and other from negative group will conduct together. Thus there would be a constant voltage drop of  $2V_T$ . The source reactance leads to overlap and it will lead to a drop of  $= \frac{3\omega L_s I_0}{\pi}$ .

Hence, 
$$V_0 = \frac{3V_{ml}}{\pi} \cos \alpha - 2I_0r_s - 2V_T - \frac{3\omega L_s I_0}{\pi}$$

As converter is working in inverter mode polarities of output voltage would be reversed,

$$-V_0 = \frac{3V_{ml} \cos \alpha}{\pi} - 2I_0r_s - 2V_T - \frac{3\omega L_s I_0}{\pi}$$

$$V_0 = \frac{3V_{ml} \cos \alpha}{\pi} + 2I_0r_s + 2V_T + \frac{3\omega L_s I_0}{\pi}$$

$$= \frac{3(440\sqrt{2}) \cos 35^\circ}{\pi} + (2 \times 60 \times 0.05) + (2 \times 2) + \frac{3 \times 0.3 \times 60}{\pi}$$

$$= 486.75 + 6 + 4 + 17.18 = 513.9 \text{ V}$$

**Solution : 8**

For a fully controlled three-phase bridge with source inductance,.

Change in output voltage, 
$$\Delta V = 6fL_s I_0 = \frac{V_{d0}}{2} (\cos \alpha - \cos(\alpha + \mu)) \quad \dots(1)$$

where,

$$f = 50 \text{ Hz}$$

$$L_s = 0.32 \text{ mH}$$

$I_0$  = Maximum current

$\mu$  = Overlap angle or recovery angle =  $5^\circ$

$\alpha$  = Firing angle

$$= 180^\circ - 30^\circ = 150^\circ$$

( $\therefore$  as it is firing advance angle)

$$V_{d0} = \frac{3V_{ml}}{\pi} = \frac{3 \times 220\sqrt{6}}{\pi} = 514.59 \text{ V}$$

By equation (i),

$$6 \times 50 \times 0.32 \times 10^{-3} \times I_0 = 257.295 (\cos 150^\circ - \cos 155^\circ)$$

$$I_0 = \frac{10.364 \times 10^3}{6 \times 50 \times 0.32} = 107.9 \text{ A}$$



**LEVEL 1** Objective Questions

1. (a)
2. (b)
3. (d)
4. (d)
5. (d)
6. (c)
7. (c)
8. (54)
9. (4.9)
10. (a)
11. (a)
12. (a)
13. (d)
14. (a)

© Copyright: Subject matter to MADE EASY Publications, New Delhi: No part of this book may be reproduced or utilised in any form without the written permission.

**LEVEL 2** Objective Questions

15. (c)
16. (b)
17. (38.47)
18. (c)
19. (c)
20. (a)
21. (40.00)
22. (0.13)
23. (171.52)


■■■■

**LEVEL 3** Conventional Questions

**Solution : 1**

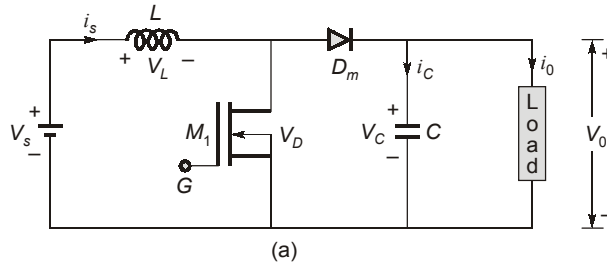**Boost regulator:**


In boost regulator the output voltage is greater than input voltage hence the name 'boost'.




The circuit operation is divided into two modes.

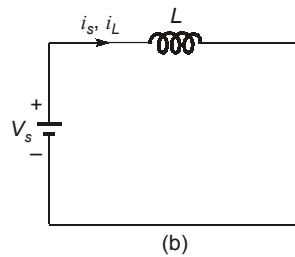**Mode-1:**

Begin when MOSFET  $M_1$  is switched on at  $t = 0$



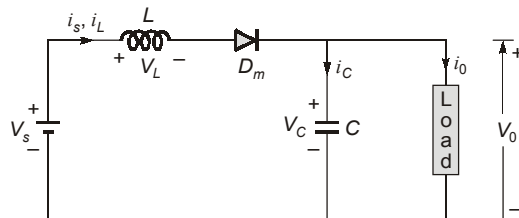The input current, which rises flows through inductor  $L$  and MOSFET  $M_1$ . Mode 2 begins when MOSFET  $M_1$  is switched-off at  $t = t_1$ .



The current that was flowing through the MOSFET would now flow through  $L$ ,  $C$  load and diode  $D_m$ . The inductor current will flow until MOSFET  $M_1$  is turned-on again in the next cycle. Assuming that the inductor current rises linearly from  $I_1$  to  $I_2$  in time  $t_1$ .

$$V_s = \frac{L(I_2 - I_1)}{t_1} = L \frac{\Delta I}{t_1} \quad \dots(1)$$

$$t_1 = T_{ON} = \frac{\Delta I_L}{V_s} \quad \dots 1 (a)$$

and the inductor current falls linearly from  $I_2$  to  $I_1$  in time  $t_2$ ,

$$V_s - V_0 = \frac{-L \Delta I}{t_2}$$

$$T_{\text{OFF}} = t_2 = \frac{\Delta I L}{V_0 - V_s} \quad \dots(2)$$

where,  $\Delta I = I_2 - I_1$  is peak to peak ripple current of inductor  $L$ .

From equation (1) and (2),

$$\Delta I = \frac{V_s T_{\text{ON}}}{L} = \frac{(V_0 - V_s) T_{\text{OFF}}}{L} \quad \dots(3)$$

Substituting,

$$\begin{aligned} T_{\text{ON}} &= \alpha T \\ T_{\text{OFF}} &= (1 - \alpha) T \quad \text{[in equation (3)]} \\ \frac{V_s \alpha T}{L} &= \frac{(V_0 - V_s)(1 - \alpha) T}{L} \\ \alpha V_s &= V_0 - \alpha V_0 - V_s + \alpha V_s \\ V_s &= V_0(1 - \alpha) \\ V_0 &= \frac{V_s}{1 - \alpha} = \text{Average output voltage} \quad \text{[Ans. (i)]} \end{aligned}$$

For voltage ripple:

When switch 's' is on, capacitor supplies the load current for  $t = T_{\text{on}}$ . The average capacitor current during time  $T_{\text{ON}}$  is  $I_C = I_0$  and peak to peak ripple voltage of capacitor is

$$\begin{aligned} \Delta V_C &= V_C(\text{at } t = T_{\text{ON}}) - V_C(\text{at } t = 0) \\ &= \frac{1}{C} \int_0^{T_{\text{ON}}} I_C dt = \frac{1}{C} I_0 T_{\text{ON}} \quad \dots(4) \\ &= \frac{1}{C} I_0 \alpha T = \frac{I_0 \alpha}{fC} \quad \text{[Ans. (iii)]} \end{aligned}$$

For minimum inductance for continuous current:

If  $I_L$  is the average inductor current, the inductor ripple current is

$$\Delta I = 2I_L \quad \dots(5)$$

From equation (3),

$$\Delta I = \frac{V_s \alpha}{fL} \quad \text{as } T_{\text{ON}} = \frac{\alpha}{f} \quad \dots(6)$$

$$I_L = I_0 = \frac{V_0}{R} = \frac{V_s}{(1 - \alpha)R} \quad \dots(7)$$

Putting equation (6) and (7) in (5),

$$\begin{aligned} \frac{V_s \alpha}{fL} &= \frac{2V_s}{(1 - \alpha)R} \\ L &= \frac{\alpha(1 - \alpha)R}{2f} \quad \text{[Ans. (ii)]} \end{aligned}$$

For critical capacitance:

If  $V_C$  = average capacitor voltage, the capacitor voltage ripple,


$$\begin{aligned} \Delta V_C &= 2 V_0 \quad \dots(8) \\ \Delta V_C &= \frac{I_0 \alpha}{fC} \end{aligned}$$

Putting  $\Delta V_C$  and  $V_0$  in equation (8),

$$\frac{I_0 \alpha}{fC} = 2I_0 R$$

$$C = \frac{\alpha}{2fR} \quad \text{[Ans. (iv)]}$$

Output waveforms:

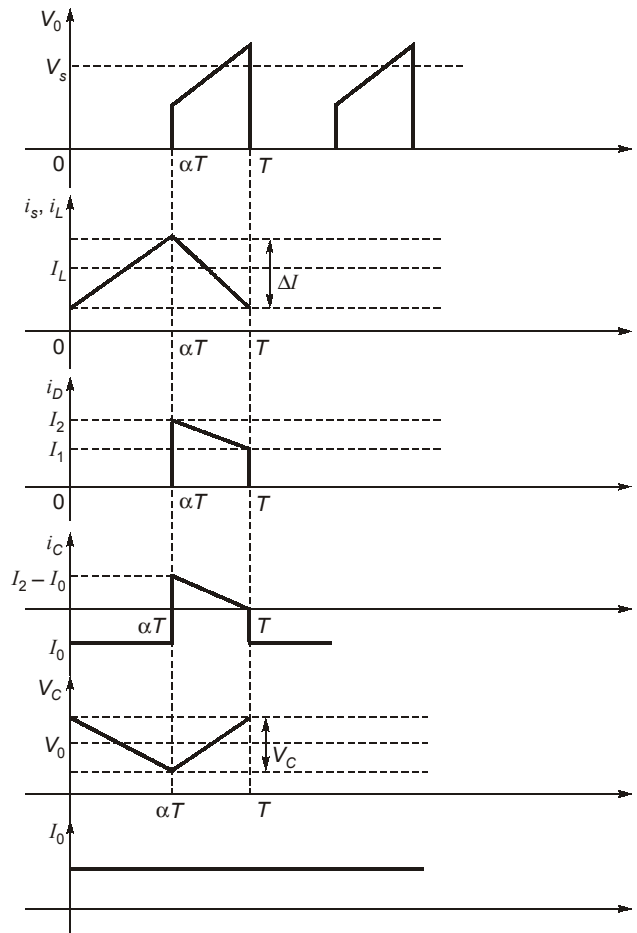

**Solution : 2**

- (a) Limit of continuous conduction is reached when  $I_{mn}$  goes to zero. The value of duty cycle  $\alpha$  at the limit of continuous conduction is obtained by equating  $I_{mn}$  to zero. Therefore,

$$I_{mn} = \frac{V_s}{R} \left[ \frac{e^{T_{ON}/T_a} - 1}{e^{T/T_a} - 1} \right] - \frac{E}{R} = 0$$

$$\Rightarrow \frac{e^{T_{ON}/T_a} - 1}{e^{T/T_a} - 1} = \frac{E}{V_s} = m \Rightarrow e^{T_{ON}/T_a} = 1 + m(e^{T/T_a} - 1)$$

$$\Rightarrow \alpha' = \frac{T_{ON}}{T} = \frac{T_a}{T} \ln[1 + m(e^{T/T_a} - 1)]$$

$$T_a = \frac{L}{R} = 5 \times 10^{-3} \text{ sec}$$

$$\frac{T_a}{T} = \frac{5 \times 10^{-3}}{2000 \times 10^{-6}} = 2.5$$

$$\frac{T}{T_a} = 0.4$$

$$m = \frac{E}{V_s} = \frac{24}{220} = 0.11$$

$$\alpha = \frac{600}{2000} = 0.3$$

$$\frac{T_{ON}}{T_a} = \frac{600}{5000} = 0.12$$

$$\begin{aligned} \alpha' &= \frac{T_{ON}}{T} = \frac{T_a}{T} \times \ln[1 + m(e^{T/T_a} - 1)] \\ &= 2.5 \ln[1 + 0.11(e^{0.4} - 1)] = 0.13172 \end{aligned}$$

As actual value of duty cycle  $\alpha = 0.3$  is greater than  $\alpha'$ , load current is continuous.

$$(b) \quad I_0 = \frac{\alpha V_s - E}{R} = \frac{0.3 \times 220 - 24}{1} = 42 \text{ A}$$

$$(c) \quad \begin{aligned} I_{mx} &= \frac{V_s}{R} \left[ \frac{1 - e^{-T_{ON}/T_a}}{1 - e^{-T/T_a}} \right] - \frac{E}{R} \\ &= \frac{220}{1} \left[ \frac{1 - e^{-0.12}}{1 - e^{-0.4}} \right] - \frac{24}{1} = 51.46 \text{ A} \end{aligned}$$

$$I_{mn} = \frac{V_s}{R} \left[ \frac{e^{T_{ON}/T} - 1}{e^{T/T_a} - 1} \right] - \frac{E}{R} = \frac{220}{1} \left[ \frac{e^{0.12} - 1}{e^{0.4} - 1} \right] - 24 = 33.031 \text{ A}$$

$$(d) \quad V_n = \frac{2V_s}{n\pi} \sin n\pi d \sin(n\omega t + \theta_n)$$

Rms value of 1<sup>st</sup> harmonic,

$$V_1 = \frac{2V_s}{\sqrt{2}\pi} \sin(\pi \times 0.3) = \frac{2 \times 220}{\sqrt{2}\pi} \sin 54^\circ = 80.121 \text{ V}$$

$$Z_1 = \sqrt{R^2 + (\omega L)^2} = \sqrt{1^2 + (2\pi \times 500 \times 5 \times 10^{-3})^2} = 15.739 \Omega$$

$$I_1 = \frac{V_1}{Z_1} = \frac{80.121}{15.739} = 5.0903 \text{ A}$$

$$\begin{aligned} I_2 &= \frac{2 \times 200}{2 \times \sqrt{2}\pi} \sin 108^\circ \times \frac{1}{\sqrt{1 + (2\pi \times 500 \times 2 \times 5 \times 10^{-3})^2}} \\ &= 1.498 \text{ A} \end{aligned}$$



$$I_3 = \frac{2 \times 200}{3\sqrt{2} \pi} \sin 162^\circ \times \frac{1}{\sqrt{1 + (2\pi \times 500 \times 3 \times 5 \times 10^{-3})^2}} = 0.21643 \text{ A}$$

$$I_{av} = \frac{\alpha(V_s - E)}{R} - \frac{L}{RT}(I_{mx} - I_{mn}) = 12.7275 \text{ A}$$

(e) Input power =  $E \times$  average supply current  
 $= 220 \times 12.7275 = 2800.05 \text{ Watts}$

Power absorbed by load emf =  $E \times$  Average load current  
 $= 24 \times 42 = 1008 \text{ Watts}$

Power loss in resistor =  $2800.05 - 1008 = 1792.05 \text{ Watts}$

(f) 
$$I_{or} = \sqrt{I_{av}^2 + I_1^2 + I_2^2 + I_3^2}$$


$$= \sqrt{42^2 + (5.0903)^2 + (1.4983)^2 + (0.2164)^2} = 42.31 \text{ A}$$

Power loss in resistor =  $I^2 R = 1792.05 \text{ W}$

$$I_{or} = \sqrt{\frac{1792.05}{1}} = 42.33 \text{ A}$$

**Solution : 3**

Voltage commutated chopper circuit,

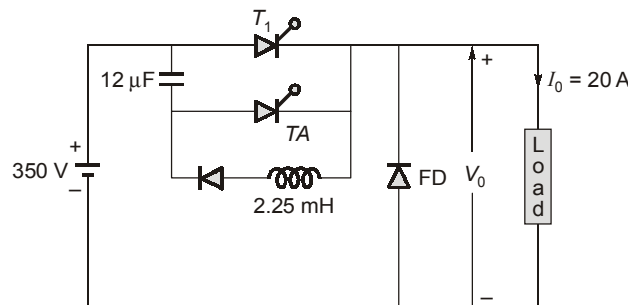

Circuit turn-off time:

$$t_c = \frac{CV_s}{I_0} = \frac{12 \times 10^{-6} \times 350}{30} = 140 \times 10^{-6} = 1.4 \times 10^{-4} \text{ s}$$

Minimum on-period for this chopper is

$$t_1 = \frac{\pi}{\omega_0} = \pi\sqrt{LC}$$

$$= \pi\sqrt{2.25 \times 10^{-3} \times 12 \times 10^{-6}}$$

$$= \pi\sqrt{27 \times 10^{-9}} = \pi \times 10^{-4} \sqrt{2.7}$$

$$= 5.162 \times 10^{-4} \text{ s}$$

The minimum average output voltage of the circuit is

$$V_{0, \min} = f V_s [t_1 + 2t_c]$$

$$= 250 \times 350 [5.162 \times 10^{-4} + 2 \times 1.4 \times 10^{-4}]$$

$$= 8.75 \times 7.962 = 69.67 \text{ V}$$

**Solution : 4**

$$C = \frac{t_c I_0}{V_s}$$

By the question,

$$t_c = \frac{CV_s}{I_0} = \frac{30 \times 10^{-6} \times 150}{I_0}$$

(i) Peak current through main thyristor =  $I_0 + V_s \sqrt{\frac{C}{L}}$

$$2I_0 = I_0 + V_s \sqrt{\frac{C}{L}}$$

$$I_0 = V_s \sqrt{\frac{C}{L}} = 150 \sqrt{\frac{30}{35}} = 138.87 \text{ A}$$

(ii)  $t_c = \frac{CV_s}{I_0} = \frac{30 \times 10^{-6} \times 150}{138.87} = 32.40 \mu\text{s}$

(iii) Minimum value of duty cycle:

$$\alpha_{mn} = \pi f \sqrt{LC} = \pi \times 300 \sqrt{30 \times 35 \times 10^{-6} \times 10^{-6}} = 0.0305$$

Minimum value of output voltage

$$\begin{aligned} &= V_s (\alpha_{mn} + 2ft_c) \\ &= 150(0.0305 + 2 \times 300 \times 32.40 \times 10^{-6}) \\ &= 150(0.0305 + 194.4 \times 10^{-4}) \\ &= 150(0.0305 + 0.0194) \\ &= 7.485 \text{ V} \end{aligned}$$

Maximum value of output voltage = 150 V

**Solution : 5**

(i) 
$$L = \frac{V_s t_c}{x I_0 \left[ \pi - 2 \sin^{-1} \left( \frac{1}{x} \right) \right]} = \frac{230 \times 60 \times 10^{-6}}{2 \times 200 \left[ \pi - 2 \sin^{-1} \left( \frac{1}{2} \right) \right]} = 16.473 \mu\text{H}$$

$$C = \frac{x I_0 t_c}{V_s \left[ \pi - 2 \sin^{-1} \left( \frac{1}{x} \right) \right]} = \frac{2 \times 200 \times 60 \times 10^{-6}}{230 \left[ \pi - 2 \sin^{-1} \left( \frac{1}{2} \right) \right]} = 49.822 \mu\text{F}$$

(ii) Peak capacitor voltage,  $V_{cp} = V_s + I_0 \sqrt{\frac{L}{C}}$

$$= 230 + 200 \sqrt{\frac{16.473}{49.822}} = 345 \text{ Volts}$$

(iii) Peak commutating current =  $x I_0 = 2 \times 200 = 400 \text{ A}$

**Solution : 6**

(a) Peak commutating current, is

$$I_{CP} = C_s \sqrt{\frac{C}{L}} = 230 \sqrt{\frac{50}{20}} = 363.66 \text{ A}$$

$$x = \frac{I_{CP}}{I_0} = \frac{363.66}{200} = 1.8183$$

Turn-off time of main SCR, is

$$\begin{aligned} t_c &= \left[ \pi - 2 \sin^{-1} \left( \frac{1}{x} \right) \right] \sqrt{LC} \\ &= \left[ \pi - 2 \sin^{-1} \left( \frac{1}{1.8183} \right) \right] \sqrt{20 \times 50 \times (10^{-6})^2} \\ &= 62.52 \mu\text{s} \end{aligned}$$

(b) 
$$\theta_1 = \sin^{-1} \left( \frac{I_0}{I_{CP}} \right) = \sin^{-1} \left( \frac{200}{363.66} \right) = 33.656^\circ$$

Total commutation interval is

$$\begin{aligned} &= \left( \frac{5\pi}{2} - \theta_1 \right) \sqrt{LC} + CV_s \frac{(1 - \cos \theta_1)}{I_0} \\ &= \left( \frac{5\pi}{2} - \frac{33.365 \times \pi}{180^\circ} \right) \sqrt{1000 \times 10^{-6}} + 50 \times 10^{-6} \times 230 \left( \frac{1 - \cos 33.6}{200} \right) \\ &= 229.95 \times 10^{-6} + 9.477 \times 10^{-6} \\ &= 239.427 \mu\text{s} \end{aligned}$$

(c) Turn-off time of auxiliary thyristor

$$\begin{aligned} &= (\pi - \theta_1) \sqrt{LC} \\ &= \left[ \pi - \frac{33.365 \times \pi}{180^\circ} \right] \sqrt{1000 \times 10^{-6}} = 80.931 \mu\text{s} \end{aligned}$$

**Solution : 7**

$V_s = 18 \text{ V}$ ,  $V_0 = 45 \text{ V}$ ,  $I_a = 1.5 \text{ A}$ ,  $f = 20 \text{ kHz}$ ,  $L = 300 \mu\text{H}$ ,  $C = 450 \mu\text{F}$

(a) 
$$V_a = \frac{V_s \alpha}{(1 - \alpha)}$$

$$\Rightarrow 45 = \frac{18 \alpha}{1 - \alpha}$$

$$\Rightarrow 45 - 45\alpha = 18\alpha$$

$$\Rightarrow \alpha = \frac{45}{63} = 0.714$$

(c) Ripple voltage, 
$$\Delta V_C = \frac{\alpha I_0}{fC} = \frac{0.714 \times 1.5}{20 \times 10^3 \times 450 \times 10^{-6}} = 119 \text{ mV}$$

(b) Ripple current, 
$$\Delta I = \frac{\alpha V_s}{fL} = \frac{0.714 \times 18}{20 \times 10^3 \times 300 \times 10^{-6}} = 2.142 \text{ A}$$

(d) Peak current of transistor,

$$I_s = \frac{I_a \alpha}{1 - \alpha} = \frac{1.5 \times 0.714}{(1 - 0.714)} = 3.74 \text{ A}$$

$$I_P = \frac{I_s}{\alpha} + \frac{\Delta I}{2} = \frac{3.74}{0.714} + \frac{2.142}{2} = 6.309 \text{ A}$$

(e) 
$$R = \frac{|V_a|}{|I_a|} = \frac{45}{1.5} = 30 \ \Omega$$

$$L_C = \frac{(1 - \alpha)\alpha R}{2f}$$

$$= \frac{(1 - 0.714)(0.714) \times 30}{2 \times 20 \times 10^3} = 0.153 \times 10^{-3} = 153 \ \mu\text{H}$$

$$C_C = \frac{\alpha}{2fR} = \frac{0.714}{2 \times 20 \times 10^3 \times 30} = 0.595 \ \mu\text{H}$$

### Solution : 8

(a) 
$$V_a = kV_s$$

$$k = \frac{V_a}{V_s} = \frac{5}{12} = 0.4167$$

(b) 
$$\Delta I = \frac{V_a(V_s - V_a)}{fLV_s}$$

$$L = \frac{5(12 - 5)}{0.8 \times 25000 \times 12} = 145.83 \ \mu\text{H}$$

(c) 
$$\Delta V_C = \frac{\Delta I}{8fC}$$

$$C = \frac{0.8}{8 \times 20 \times 10^{-3} \times 25000} = 200 \ \mu\text{F}$$

(d) 
$$L_C = \frac{(1 - K)R}{2f} = \frac{(1 - 0.4167) \times 500}{2 \times 25 \times 10^3} = 5.83 \ \text{mH}$$

$$C_C = \frac{1 - K}{16Lf^2} = \frac{(1 - 0.4167)}{16 \times 5.83 \times 10^{-3} (25 \times 10^3)^2} = 1500 \ \mu\text{F}$$

### Solution : 9

$$\frac{T_{\text{OFF}}}{T_{\text{ON}}} = \frac{1}{4}$$

$$\frac{T_{OFF}}{T_{ON}} + 1 = \frac{5}{4}$$

$$\frac{T}{T_{ON}} = \frac{5}{4} \Rightarrow \frac{T_{ON}}{T} = \alpha = \frac{4}{5}$$


Average value of load voltage =  $V_0$

$$V_0 = \alpha V_s = \frac{4}{5} \times 100 = 80 \text{ V}$$

Chopping period,  $T = 2 \text{ m-sec}$

$$T_{ON} = \frac{4}{5} \times 2 = 1.6 \text{ ms}$$

Hence,

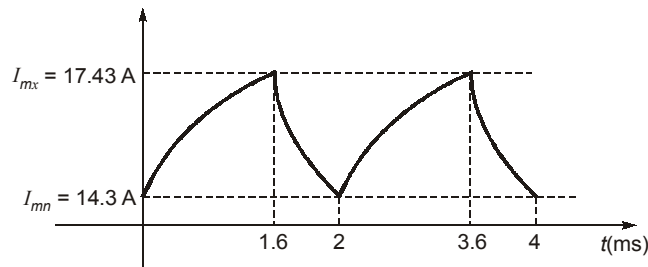

During  $T_{ON}$ :

$$V_s = L \frac{di}{dt} + iR$$

Taking Laplace transform:

$$\frac{V_s}{s} = L(sI(s) - I_{mn}) + I(s)R$$

$$\frac{V_s}{s} + LI_{mn} = I(s) + (sL + R)I(s)$$

$$I(s) = \frac{V_s}{s(sL + R)} + \frac{LI_{mn}}{sL + R}$$

$$I(s) = \frac{V_s}{Ls \left( s + \frac{R}{L} \right)} + \frac{I_{mn}}{s + \frac{R}{L}} = \frac{V_s}{R} \left[ \frac{1}{s} - \frac{1}{s + \frac{R}{L}} \right] + \frac{I_{mn}}{s + \frac{R}{L}}$$

$$i(t) = \frac{V_s}{R} (1 - e^{-\frac{Rt}{L}}) + I_{mn} e^{-Rt/L}$$

$$= 20 [1 - e^{-500t}] + I_{mn} e^{-500t}$$

During  $T_{OFF}$ :

$$0 = L \frac{di}{dt} + iR$$

$$\frac{di}{dt} = -\frac{R}{L}(i)$$

$$\int_{i_{mn}}^i \frac{di}{i} = -\int_0^t \frac{R}{L} dt$$

$$\ln \frac{i}{i_{mx}} = -\frac{Rt}{L}$$

$$i = i_{mx} e^{-Rt/L}$$

$$i = i_{mx} e^{-500t}$$

at  $t = T_{ON}$ :

$$\begin{aligned} I_{mx} &= 20(1 - e^{-0.8}) + I_{mn} e^{-0.8} \\ I_{mx} - 0.45I_{mn} &= 11.01 \end{aligned} \quad \dots(1)$$

at  $t = T_{OFF}$ :

$$\begin{aligned} I_{mn} &= I_{mx} e^{-0.2} \\ I_{mn} &= 0.82 I_{mx} \end{aligned} \quad \dots(2)$$

Solving,

$$\begin{aligned} I_{mx} &= 17.43 \text{ A} \\ I_{mn} &= 14.3 \text{ A} \end{aligned}$$



**LEVEL 1** Objective Questions

1. (b)
2. (d)
3. (18.08)
4. (b)
5. (b)
6. (c)
7. (b)
8. (a)
9. (c)
10. (a)
11. (b)
12. (a)

© Copyright: Subject matter to MADE EASY Publications, New Delhi: No part of this book may be reproduced or utilised in any form without the written permission.

**LEVEL 2** Objective Questions

13. (b)
14. (60)
15. (d)
16. (2.78)
17. (2.25)
18. (b)
19. (0.122)
20. (72.92)
21. (b)
22. (c)
23. (a)
24. (b)
25. (121.54)
26. (710.46)
27. (c)

■■■■



## LEVEL 3 Conventional Questions

## Solution : 1

PWM (pulse width modulation) is a internal voltage control of inverter. In this method, a fixed dc input voltage is given to the inverter and a controlled output voltage is obtained by, adjusting the on and off periods of the inverter components. In Sine modulation [Sin  $M$ ] the pulse width is a sinusoidal function of the angular position of the pulse in a cycle as shown in figure.

For realizing sin  $M$ , a high-frequency triangular carrier wave  $V_c$  is compared with a sinusoidal reference wave  $V_r$  of the desired frequency. The intersection of  $V_c$  and  $V_r$  waves determines the switching instants and commutation of the modulated pulse. In figure  $V_c$  is the peak value of triangular carrier wave and  $V_r$  that of the reference, or modulating signal.

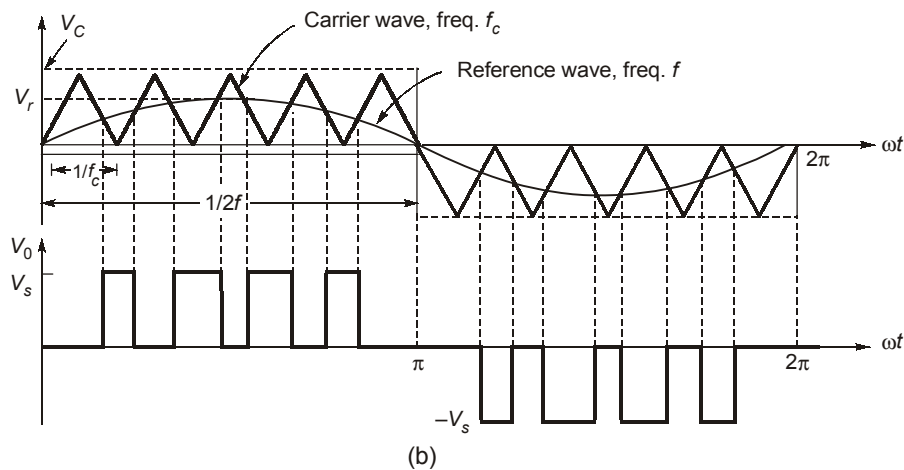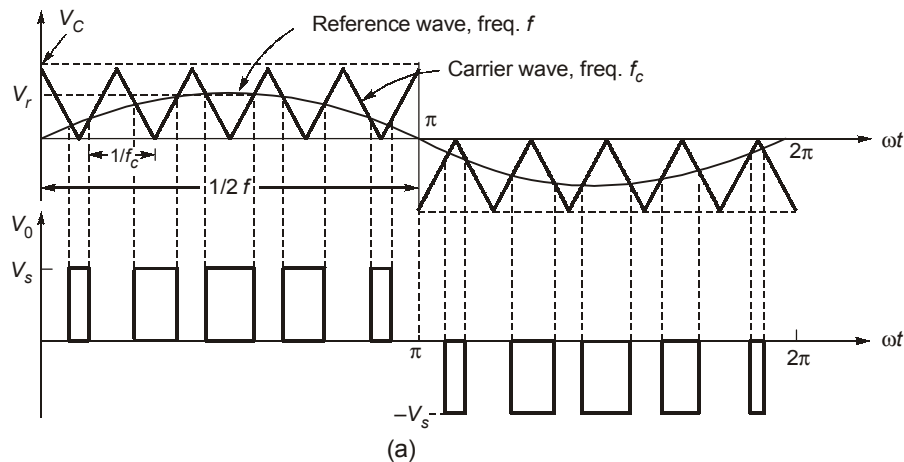The carrier and reference waves are mixed in a comparator. When sinusoidal wave has magnitude higher than the triangular wave, the comparator output is high, otherwise it is low. The comparator output is processed in a trigger pulse generator in such a manner that the output voltage wave of the inverter has a pulse width in agreement with the comparator output pulse width.



Output voltage waveforms with sinusoidal pulse modulation



When triangular carrier wave has its peak coincident with zero of the reference sinusoid, there are  $N = f_c/2f = \frac{f_c}{2f}$  pulses per half cycle ; Fig. (a) has five pulses. In case zero of the triangular wave coincides with zero of the reference sinusoid, there are  $(N - 1)$  pulses per half cycle ; Fig. (b) has  $(f_c/2f - 1)$ , i.e. four, pulses per cycle.

The ratio of  $V_r/V_c$  is called the modulation index (MI) and it controls the harmonic content of the output voltage waveform. The magnitude of fundamental component of output voltage is proportional to MI, but MI can never be more than unity. Thus the output voltage is controlled by varying MI.


Harmonic analysis of the output modulated voltage wave reveals that  $\sin M$  has the following important features:

- (i) For MI less than one, largest harmonic amplitudes in the output voltage are associated with harmonics of order  $f_c/f \pm 1$  or  $2N \pm 1$ , where  $N$  is the number of pulses per half cycle. Thus, by increasing the number of pulses per half cycle, the order of dominant harmonic frequency can be raised, which can then be filtered out easily.

It is observed from above that as  $N$  is increased, the order of significant harmonic increases and the filtering requirements are accordingly minimised. But higher value of  $N$  entails higher switching frequency of thyristors. This amounts to more switching losses and therefore an impaired inverter efficiency. Thus a compromise between the filtering requirements and inverter efficiency should be made.

- (ii) For MI greater than one, lower order harmonics appear, since for  $MI > 1$ , pulse width is no longer a sinusoidal function of the angular position of the pulse.

**Solution : 2**

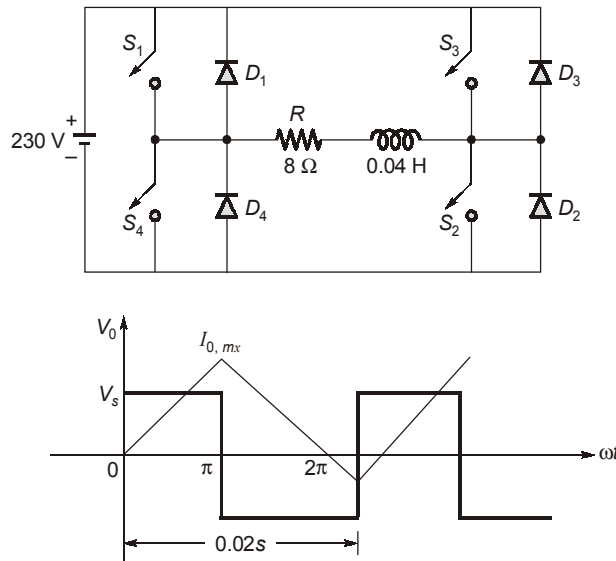

For the first-half cycle:

$$0 < t < \frac{T}{2}$$

The voltage equation for RL load is

$$V_s = Ri_0 + L \frac{di_0}{dt}$$

$$i(t) = \frac{V_s}{R} \left( 1 - e^{-\frac{t}{\tau}} \right) = \frac{220}{8} (1 - e^{-200t}) \quad \left[ \text{where, } \tau = \frac{L}{R} = 0.005 \right]$$

$$= 27.5 (1 - e^{-200t})$$

During second half cycle:

$$I_0 = I_{\text{initial}} = \frac{V_s}{R}$$

$$I_\infty = I_{\text{field}} = -\frac{V_s}{R}$$

$$I(t) = (I_\infty - (I_\infty - I_0)e^{-t/\tau})$$

$$= \left[ -\frac{V_s}{R} - \left( -\frac{V_s}{R} - \frac{V_s}{R} \right) e^{-t/\tau} \right] = -\frac{V_s}{R} + \frac{2V_s}{R} e^{-t/\tau}$$

$$= -\frac{220}{8} + \frac{2 \times 220}{8} e^{-200t} = -27.5 + 55 e^{-200t}$$

### Solution : 3

#### Sinusoidal Pulse-Width Modulation:

$$m_A = \frac{A_{\text{Reference}}}{A_{\text{carrier}}}$$

$$m_F = \frac{f_{\text{carrier}}}{f_{\text{Reference}}}$$

Instead of maintaining the width of all pulses the same as in the case of multiple-pulse modulation, the width of each pulse is varied in proportion to the amplitude of a sine wave evaluated at the center of the same pulse. The DF and LOH are reduced significantly. The gating signals are generated by comparing a sinusoidal reference signal with a triangular carrier wave of frequency  $f_c$ . This sinusoidal pulse-width modulation (SPWM) is commonly used in industrial applications. The frequency of reference signal  $f_r$  determines the inverter output frequency  $f_0$ ; and its peak amplitude  $A_r$  controls the modulation index  $M$ , and then in turn the rms output voltage  $V_0$ . The rms output voltage can be varied by varying the modulation index  $M_A$ . It can be observed that the area of each pulse corresponds approximately to the area under the sine wave between the adjacent midpoints of off periods on the gating signals. The harmonic profile is shown in figure for five pulses per half-cycle. The DF is significantly reduced compared with that of multiple-pulse modulation.

The output voltage of an inverter contains harmonics. The PWM pushes the harmonics into a high-frequency range around the switching frequency  $f_c$  and its multiples, that is around harmonics  $m_f$ ,  $2m_f$ ,  $3m_f$ , and so on. The frequencies at which the voltage harmonics occur can be related by

$$f_n = (jm_f \pm k) f_c$$

where the  $n^{\text{th}}$  harmonic equals the  $k^{\text{th}}$  sideband of  $j^{\text{th}}$  times the frequency to modulation ratio  $m_f$ .

$$n = jm_f \pm k$$


$$= 2jp \pm k$$

For  $j = 1, 2, 3, \dots$  and  $k = 1, 3, 5, \dots$

The peak fundamental output voltage for PWM and SPWM control can be found approximately from

$$V_{m1} = m_A V_s \text{ for } 0 \leq m_A \leq 1.0$$

For  $m_A = 1$ , equation gives the maximum peak amplitude of the fundamental output voltage as  $V_{m1(\max)} = V_s$ . According to equation,  $V_{m1(\max)}$  could be as high as  $4V_s/\pi = 1.273 V_s$  for a square-wave output. To increase the fundamental output voltage,  $m_A$  must be increased beyond 1.0. The operation beyond  $m_A = 1.0$  is called overmodulation. The value of  $m_A$  at which  $V_{m1(\max)}$  equals  $1.273 V_s$  is dependent on the number of pulses per half-cycle  $p$  and is approximately 3 for  $p = 7$ , as shown in figure. Overmodulation basically leads to a square-wave operation and adds more harmonics as compared with operation in the linear range (with  $m_A \leq 1.0$ ). Overmodulation is normally avoided in applications requiring low distortion (e.g. uninterruptible power supplies [UPS]).

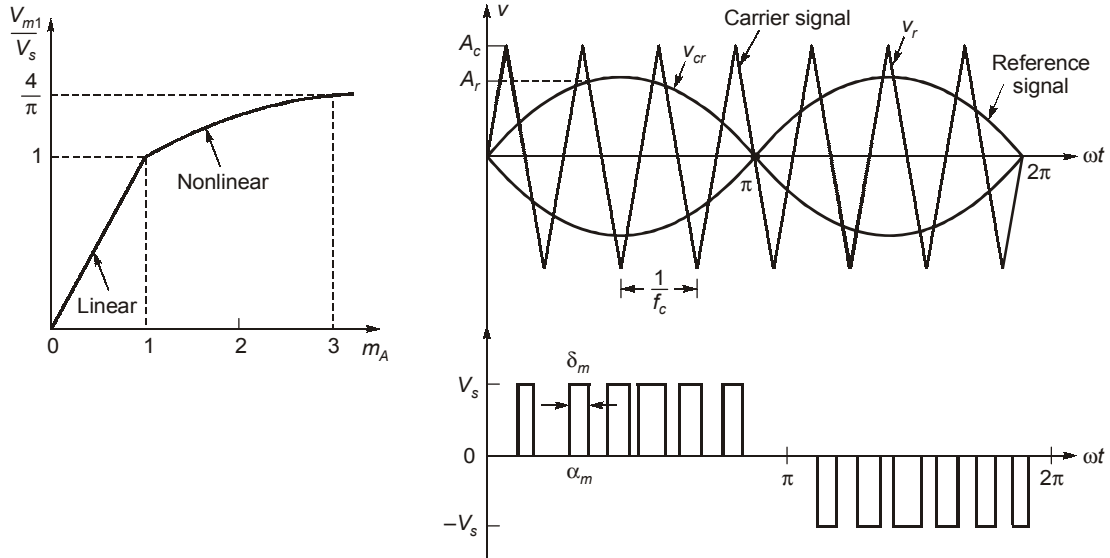

**Solution : 4**

The voltage waveform of the given figure is symmetrical about  $\pi$  as well as  $\pi/2$ . As this voltage waveform has quarter wave symmetry,

$$a_n = 0$$

and

$$b_n = \frac{4V_s}{\pi} \left[ \int_0^{\alpha_1} \sin \omega t \cdot d\omega(t) - \int_{\alpha_1}^{\alpha_2} \sin n\omega t \cdot d\omega(t) + \int_{\alpha_2}^{\pi/2} \sin n\omega t \cdot d\omega(t) \right]$$

$$b_n = \frac{4V_s}{\pi} \left[ \left( -\frac{\cos n\omega t}{n} \right) \Big|_0^{\alpha_1} - \left( -\frac{\cos n\omega t}{n} \right) \Big|_{\alpha_1}^{\alpha_2} + \left( -\frac{\cos n\omega t}{n} \right) \Big|_{\alpha_2}^{\pi/2} \right]$$

$$= \frac{4V_s}{\pi} \left[ \frac{1 - \cos n\alpha_1}{n} + \frac{\cos n\alpha_2 - \cos n\alpha_1}{n} + \frac{\cos n\alpha_2}{n} \right]$$

$$b_n = \frac{4V_s}{\pi} \left[ \frac{1 - 2\cos n\alpha_1 + 2\cos n\alpha_2}{n} \right]$$

Now, for the values of  $\alpha_1 = 23.62^\circ$  and  $\alpha_2 = 33.30^\circ$   
The amplitude of 7<sup>th</sup> harmonics

$$b_7 = \frac{4V_s}{\pi} \left[ \frac{1 - 2\cos(7 \times 23.62^\circ) + 2\cos(7 \times 33.30^\circ)}{7} \right] = 0.3154 V_s$$

The amplitude of 9<sup>th</sup> harmonics

$$b_9 = \frac{4V_s}{\pi} \left[ \frac{1 - 2\cos(9 \times 23.62^\circ) + 2\cos(9 \times 33.30^\circ)}{9} \right] = 0.5201 V_s$$

and the amplitude of 11th harmonics,

$$b_{11} = \frac{4V_s}{\pi} \left[ \frac{1 - 2\cos(11 \times 23.62^\circ) + 2\cos(11 \times 33.30^\circ)}{11} \right] = 0.3867 V_s$$

### Solution : 5

Rms value of fundamental component at the output of inverter,

$$V_1 = \frac{4 \times 12}{\pi} \times \frac{1}{\sqrt{2}} = \frac{48}{\sqrt{2}\pi} = 10.8 \text{ V}$$

$$(i) \quad \frac{V_1}{N_1} = \frac{V_2}{N_2}$$

$$\Rightarrow \quad N_2 = 230 \times \frac{10}{10.8} = 212.96 \text{ V}$$

(ii) Rms value of secondary current,

$$I_2 = \frac{230}{100} = 2.3 \text{ A}$$

$$I_1 N_1 = I_2 N_2$$

$$I_1 = \frac{2.3 \times 212.96}{10} = 48.98 \text{ A}$$

$$(iii) \text{ Rms value of thyristor current} = \frac{\text{Rms value of primary current}}{\sqrt{2}} = \frac{48.98}{\sqrt{2}} = 34.634 \text{ A}$$



# 5

## Resonant Converters and Power Electronics Applications (Drives, SMPS)

### LEVEL 1 Objective Questions

1. (d)
2. (a)
3. (d)
4. Sol.
5. (b)
6. (b)
7. (c)
8. (a)
9. (d)

© Copyright: Subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced or utilised in any form without the written permission.

### LEVEL 2 Objective Questions

10. (a)
11. (b)
12. (d)
13. (180)
14. (b)
15. (d)
16. (c)
17. (c)
18. (b)
19. (98.72)
20. (c)

■■■■

**LEVEL 3** Conventional Questions
**Solution : 1**

From the question:

$$i(0) = 10 \text{ A}$$

To calculate  $i(10^{-3})$

During ON condition:

$$V_s = iR_a + L \frac{di}{dt} + E_b$$

$$180 = 0.4i + 8 \times 10^{-3} \frac{di}{dt} + 80$$

$$100 = 0.4i + 8 \times 10^{-3} \frac{di}{dt}$$

$$\int_0^t dt = 8 \times 10^{-3} \int_0^i \frac{di}{100 - 0.4i}$$

$$t = \frac{8 \times 10^{-3}}{-0.4} \ln \left( \frac{100 - 0.4i}{96} \right)$$

$$-50t = \ln \left( \frac{100 - 0.4i}{96} \right)$$



$$100 - 0.4i = 96 e^{-50t}$$

$$i = \frac{1}{0.4} [100 - 96 e^{-50t}] = 5[50 - 48 e^{-50t}]$$

$$= 250 - 240 e^{-50t}$$

At  $t = 10^{-3}$  sec.,

$$i = 250 - 240 e^{-\frac{50}{1000}} = 21.705 \text{ A}$$

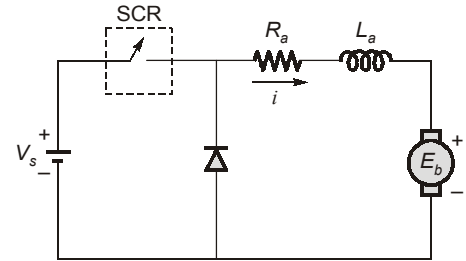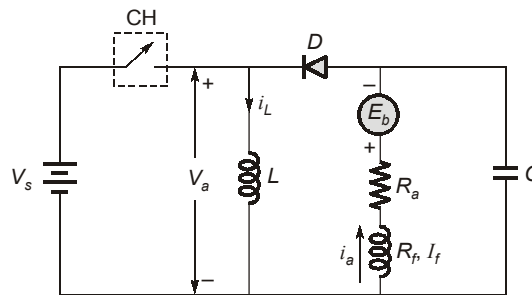**Solution : 2**

$$V_a = \frac{\alpha V_s}{1 - \alpha}$$

$$[\alpha = \text{Duty cycle} = T_{\text{ON}}/T]$$

Now,

$$V_a = E_b + I_a (R_a + R_f)$$

$$= E_b + I_a R$$


$$\Rightarrow V_a = k_1 N I_a + I_a R \quad [E_b \propto N \phi \propto N I_a]$$

$$\Rightarrow N = \frac{V_a - I_a R}{k_1 I_a}$$


$$\Rightarrow N = \frac{V_a}{k_1 I_a} - \frac{R}{k_1}$$

For constant  $I_a$  [i.e. constant torque as torque  $\propto I_a^2$ ],

$$N \propto V_a$$

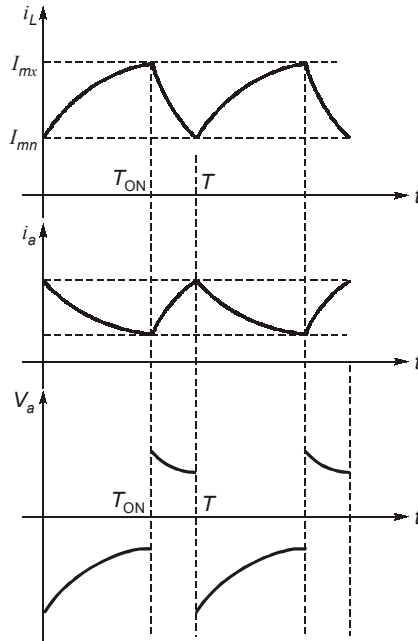

**Solution : 3**

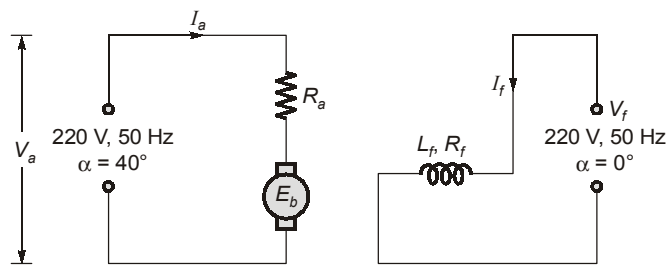

(i)  $E_b = K \omega I_f$  ...(1)

$$I_f = \frac{V_f}{R_f}$$

$$V_f = \frac{2V_m \cos 0}{\pi} = \frac{2 \times 220 \times \sqrt{2}}{\pi} = 198.069 \text{ V}$$

$$= \frac{198.069}{150} = 1.32 \text{ A}$$

Further,

$$V_a = I_a R_a + E_b$$

$$E_b = V_a - I_a R_a$$

$$V_a = \frac{2V_m}{\pi} \cos 40^\circ = 151.73 \text{ V}$$

$$= 151.73 - (40 \times 0.6) = 127.73 \text{ V}$$

Putting in equation (1),  $\omega = \frac{E_b}{kI_f} = \frac{127.73}{0.6 \times 1.32} = 161.275 \text{ rad/sec.}$

$$N = \omega \times \frac{60}{2\pi} = 1540.06 \text{ rpm}$$

(ii) Power factor of armature current

$$= \frac{I_a^2 R_a + E_b I_a}{220 I_a} = \frac{I_a R_a + E_b}{220}$$

$$= \frac{151.73}{220} = 0.6869 \text{ lag}$$

(iii) Power factor of driving scheme

$$= \frac{I_a^2 R_a + E_b I_a + I_f^2 R_f}{220 \sqrt{I_a^2 + I_f^2}}$$

$$= \frac{40^2(0.6) + 127.73 \times 40 + 1.32^2 + 150}{220 \sqrt{(40)^2 + (1.32)^2}} = 0.7189 \text{ lag}$$

#### Solution : 4

At rated operation:

$$E = V_a - I_a R_a$$

$$= 200 - 150 \times \frac{6}{100} = 191 \text{ V}$$

(i)  $E$  at 750 rpm:

$$\frac{E_1}{N_1} = \frac{E_2}{N_2}$$

$$\Rightarrow E_2 = \frac{E_1}{N_1} \times N_2 = 191 \times \frac{750}{875} = 163.7 \text{ V}$$

$$V_a = E + I_a R_a$$

$$= 163.7 + (150 \times 0.06) = 172.7 \text{ V}$$

$$\frac{2V_m}{\pi} \cos \alpha = V_a$$

$$\cos \alpha = \frac{\pi V_a}{2V_m} = \frac{\pi \times 172.7}{2 \times \sqrt{2} \times 220} = 0.872$$

$$\alpha = 29.3^\circ$$



(ii)  $E$  at  $-500$  rpm:

$$E = -\frac{500}{875} \times 191 = -109 \text{ V}$$

$$V_a = E + I_a R_a = -109 + (150 \times 0.06) = -100 \text{ V}$$

$$\frac{2V_m}{\pi} \cos \alpha = V_a$$

$$\cos \alpha = -\frac{100\pi}{2 \times \sqrt{2} \times 220} = -0.504$$

$$\alpha = 120^\circ$$

(iii)  $\alpha = 160^\circ$ :

$$V_a = \frac{2V_m}{\pi} \cos \alpha = \frac{2 \times 220\sqrt{2} \cos 160^\circ}{\pi} = -186 \text{ V}$$



$$V_a = E + I_a R_a$$

$$-186 = E + 150 \times 0.06$$

$$E = -195 \text{ V}$$

$$N_2 = -\frac{195}{191} \times 875 = -893.2 \text{ rpm}$$

**Solution : 5**

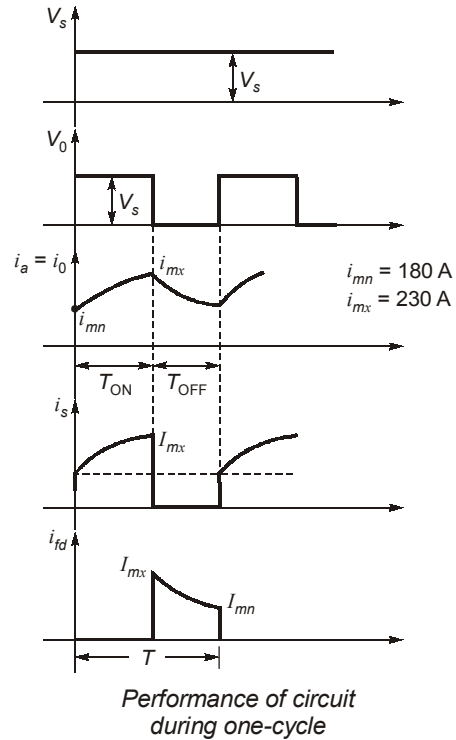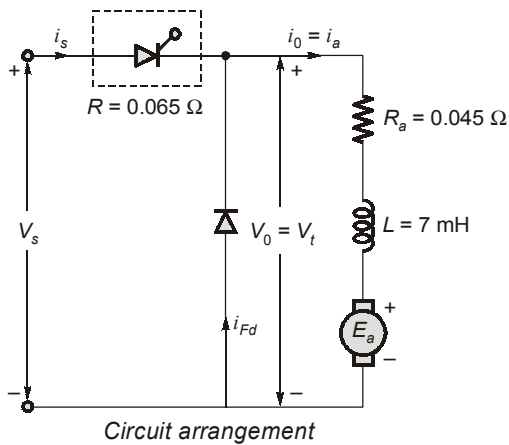

For a separately-excited DC motor:

$$V_t = V_0 = E_a + I_a r_a$$

$$72 = kN + (200 \times 0.045)$$

$$k = \frac{72 - 9}{2500} = \frac{63}{2500} \text{ V/rpm}$$

At 1000 rpm, counter emf of motor:

$$E_a = k \times 1000$$

$$= \frac{63}{2500} \times 1000 = 25.2 \text{ V}$$

$$I_{mx} = \frac{V_s - E}{R} (1 - e^{-T_{ON}/T_a}) + I_{mn} e^{-T_{ON}/T_a} \quad \dots(1)$$

$$T_a = \frac{L}{R} = \frac{7 \times 10^{-3}}{0.045 + 0.065} = 0.064 \text{ s}$$

Putting in equation (1),

$$230 = \frac{72 - 25.2}{0.11} [1 - e^{-T_{ON}/0.064}] + 180 - e^{-T_{ON}/0.064}$$

$$\Rightarrow 245.45 e^{-T_{ON}/0.064} = 195.45$$

$$T_{ON} = 0.01458 \text{ s}$$

During free wheeling period:

$$I_{mn} = -\frac{E}{R} (1 - e^{-T_{OFF}/T_a}) + I_{mx} e^{-T_{OFF}/T_a}$$

$$T_a = \frac{L}{R} = \frac{7 \times 10^{-3}}{0.045} = 0.1556 \text{ s}$$

$$180 = -\frac{25.2}{0.045} (1 - e^{-T_{OFF}/0.1556}) + 230 e^{-T_{OFF}/0.1556}$$

$$T_{OFF} = 0.1556 \ln \frac{790}{740} = 0.01017 \text{ s}$$

$$\begin{aligned} \text{Chopping period} &= T = T_{ON} + T_{OFF} \\ &= 0.01458 + 0.01017 \\ &= 0.02475 \text{ s} \end{aligned}$$

$$\text{Chopping frequency, } f = \frac{1}{T} = \frac{1}{0.02475} = 40.40 \text{ Hz}$$

$$\text{Duty cycle} = \frac{T_{ON}}{T} = \frac{0.01458}{0.024754} = 0.589 = 58.9\%$$

### Solution : 6

(a) Motor constant = 0.5 V-sec/rad = 0.5 Nm/A =  $K_m$

Motor torque,  $T = K_m I_a$

$$I_a = \frac{15}{0.5} = 30 \text{ A}$$

Motor emf, 
$$E_a = K_m \omega_m = 0.5 \times \frac{2\pi}{60} \times 1000 = 52.36 \text{ V}$$

For a 1-phase, half wave converter feeding a dc motor,

$$\begin{aligned} V_t &= \frac{V_m}{2\pi}(1 + \cos \alpha) = E_a + I_a r_a \\ &= \frac{\sqrt{2} 230}{2\pi}(1 + \cos \alpha) = 52.36 + (30 \times 0.7) = 73.36 \text{ V} \end{aligned}$$

Firing angle of armature converter,

$$\alpha = 65.336^\circ$$

(b) Rms value of thyristor current,

$$I_{\text{Thyristor}} = I_a \sqrt{\frac{\pi - \alpha}{2\pi}} = 30 \sqrt{\frac{180 - 65.336}{360}} = 16.931$$

Rms of free wheeling diode current,

$$I_{fd} = I_a \sqrt{\frac{\pi + \alpha}{2\pi}} = 30 \sqrt{\frac{180 + 65.336}{360}} = 24.766 \text{ A}$$

(c) Input power factor of armature converter =  $\frac{V_t I_a}{V_s I_{sr}}$

$$\begin{aligned} I_{sr} &= I_{\text{Thyristor}} \\ &= \frac{73.36 \times 30}{230 \times 16.931} = 0.5651 \text{ lag} \end{aligned}$$

**Solution : 7**

(a) Motor terminal voltage =  $\frac{3V_m}{\pi} \cos 30^\circ = \frac{3 \times 400 \times \sqrt{2}}{\pi} \frac{\sqrt{3}}{2} = 467.75 \text{ V}$

$$\begin{aligned} V_t &= E_a + I_a r_a + 2 \\ 467.75 &= K_m \omega_m + (21 \times 0.1) + 2 \end{aligned}$$

$$\text{No-load motor speed} = \frac{467.75 - 4.1}{1.6} = 289.78 \text{ rad/sec.}$$

(b) At rated armature current and at 2000 rpm

$$V_0 = K_m \omega_m + I_a r_a + 2$$

$$\frac{3\sqrt{2} \times 400}{\pi} \cos \alpha = \left( 1.6 \times \frac{2\pi}{60} \times 2000 \right) + (210 \times 0.1) + 2 = 358.1 \text{ V}$$

$$\cos \alpha = \frac{358.1 \times \pi}{3\sqrt{2} \times 400} = 0.663$$

$$\alpha = 48.47^\circ$$

Rms value of source current,

$$I_{sr} = I_a \sqrt{\frac{2}{3}} = 210 \sqrt{\frac{2}{3}} = 171.46$$

$$\text{Supply p.f.} = \frac{V_t I_a}{\sqrt{3} V_s I_{sr}} = \frac{358.10 \times 210}{\sqrt{3} \times 400 \times 171.46} = 0.633 \text{ lag}$$

- (c) At rated load, speed is 2000 rpm, armature voltage  $V_t = 358.1$  V and firing angle is  $48.47^\circ$ .  
If load reduced to zero then,

$$V_t = K_m \omega_m + I_a r_a + 2$$

$$358.1 = K_m \omega_m + (21 \times 0.1) + 2$$

$$\omega_m = \frac{358.1 - 4.1}{1.6} = 221.25 \text{ rad/sec. or } 2112.8 \text{ rpm}$$

$$\text{Speed regulation} = \frac{2112.8 - 2000}{2000} \times 100 = 5.64\%$$

**Solution : 8**

Rotor induced emf at stand still = 700 V (line)

$$E_2 = \frac{700}{\sqrt{3}} \text{ V}$$

$$s = \frac{1500 - 1200}{1500} = 0.2$$

DC voltage across diode rectifier is

$$V_d = \frac{3\sqrt{6} s E_2}{\pi} - 2 \times 0.7 = \frac{3\sqrt{2} \times 0.2 \times 700}{\pi} - 1.4$$

Inverter dc voltage is given by

$$V_{dc} = - \left[ \frac{3\sqrt{2} \times 415}{\pi} \cos \alpha - 2 \times 1.5 \right]$$

With no voltage drop in inductor,

$$V_{dc} = V_d$$

$$-\frac{3\sqrt{2} \times 415}{\pi} \cos \alpha + 3 = \frac{3\sqrt{2} \times 0.2 \times 700}{\pi} - 1.4$$

$$\alpha = \cos^{-1} \left[ \frac{-184.6379 \times \pi}{3\sqrt{2} \times 415} \right] = 109.24^\circ$$

Firing advance angle of inverter =  $180^\circ - \alpha = 70.76^\circ$

