

1.(a)

when $\eta = 98.5\% = 0.985$

$$\eta = \frac{\text{Output}}{\text{Input}} = \frac{\text{Output}}{\text{Output} + \text{losses}}$$

$$0.985 = \frac{1 \times 0.8}{1 \times 0.8 + P_i + P_{\text{CuFe}}}$$

$P_i \rightarrow$ iron loss

$P_{\text{CuFe}} \rightarrow$ full load copper loss

$$P_i + P_{\text{CuFe}} = \frac{12}{985} \quad \text{--- (1)}$$

Now when $\eta = 99\% = 0.99$

$$0.99 = \frac{0.5 \times 1.0}{0.5 \times 1.0 + P_i + (0.5)^2 P_{\text{CuFe}}}$$

$$P_i + (0.5)^2 P_{\text{CuFe}} = \frac{1}{198} \quad \text{--- (2)}$$

Solving (1) & (2)

$$P_i = 2.6731 \times 10^{-3} \text{ pu}$$

at base of 100 KVA

$$P_{\text{CuFe}} = 9.50965 \times 10^{-3} \text{ pu}$$

$$P_i = 2.6731 \times 10^{-3} \times 100 \times 10^3 = 267.31 \text{ Watts.}$$

$$P_{\text{CuFe}} = 9.50965 \times 10^{-3} \times 100 \times 10^3 = 950.965 \text{ Watts.}$$

for maximum efficiency $\Rightarrow$ Core loss = Cu loss


$$2.6731 \times 10^{-3} = x^2 \times 9.50965 \times 10^{-3}$$

$$x = 0.53018 \text{ pu of full load current}$$

$$\text{Value of load current} = 0.53018 \times \frac{100 \times 10^3}{11000}$$

$$\rightarrow \boxed{I = 4.82 \text{ A}}$$

1. (b)

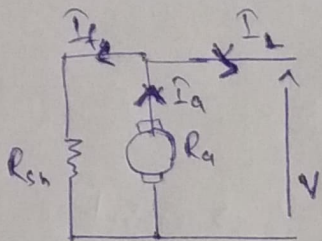Shunt generator

$$V = 200$$

$$P_{out} = V I_L = 30 \text{ kW}$$

$$I_L = \frac{30 \times 10^3}{200} = 150 \text{ A}$$

$$I_f = \frac{V}{R_{sn}} = \frac{200}{50} = 4 \text{ A}$$

$$I_a = I_L + I_f = 150 + 4 = 154 \text{ A}$$

$$E_g = \text{generated emf} = V + I_a R_a$$

$$= 200 + 154 \times 0.05$$

$$E_g = 207.7 \text{ Volts}$$

$$C_{losses} = I_a^2 R_a + I_f^2 R_{sn}$$

$$= (150)^2 \times 0.05 + (4)^2 \times 50$$

$$C_{losses} = 1925 \text{ watts}$$

$$\eta = \frac{\text{Output}}{\text{Input}} \times 100 = \frac{\text{Output}}{\text{Output} + \text{Losses}} \times 100$$

$$= \frac{30 \times 10^3}{30 \times 10^3 + 1925 + 1000} \times 100$$


$$\eta = 91.16 \%$$

1(c)

Equivalent circuit of induction motor

During No load test $\Rightarrow$ $s \approx 0$

$$R_1 = 1.5 \Omega$$

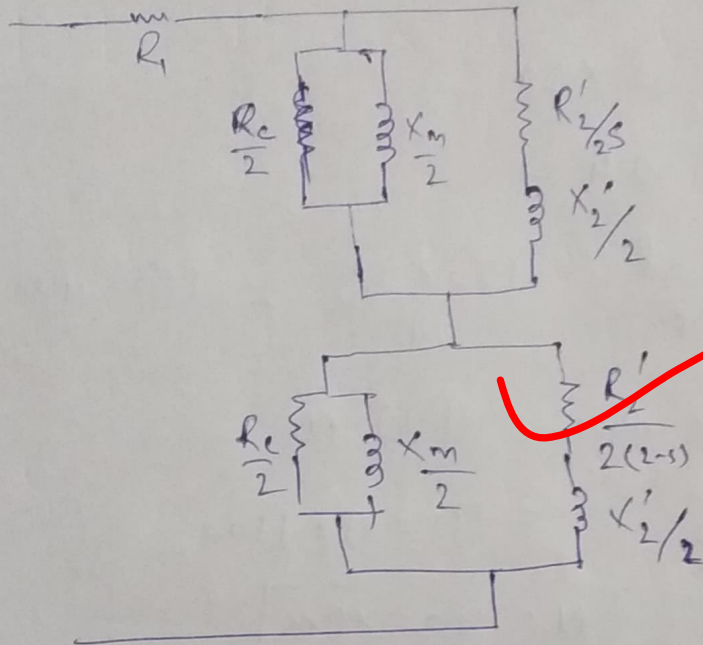

1.(d) (i) At rotor the frequency is slip time the frequency of supply.

$$\therefore f_r = s f$$

$$20 = s \times 50$$

$$\Rightarrow s_1 = 0.4 \text{ pu}$$

$$\text{So, } N_s = \frac{120 f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

$$\begin{aligned} \text{Speed of prime mover} &= (1-s) N_s \\ &= (1-0.4) \times 1500 \end{aligned}$$

$$\boxed{N_1 = 900 \text{ rpm}}$$

we can obtain 20 Hz frequency at rotor by moving motor at greater than N_s $\therefore$

Slip becomes negative, so at

$$s_2 = -0.4 \text{ pu}$$

$$\begin{aligned} N_2 &= [1 - (-0.4)] N_s \\ &= [1 + 0.4] \times 1500 \end{aligned} \Rightarrow \boxed{N_2 = 2100 \text{ rpm}}$$

(ii) Voltage at slip ring of motor $\propto s$

$$\therefore \frac{V_1}{V_2} = \frac{s_1}{s_2}$$

$$\frac{V_1}{V_2} = \frac{0.4}{-0.4} \Rightarrow$$

$$\boxed{\frac{V_1}{V_2} = -1}$$

1.e)

$$P = 0.9 \text{ pu}$$


$$V = 1 \text{ pu} \quad \cos \phi = 0.8$$

$$P = V I \cos \phi$$

$$0.9 = 1 \times I \times 0.8$$

$$\Rightarrow I = 1.125 \text{ pu}$$

axis

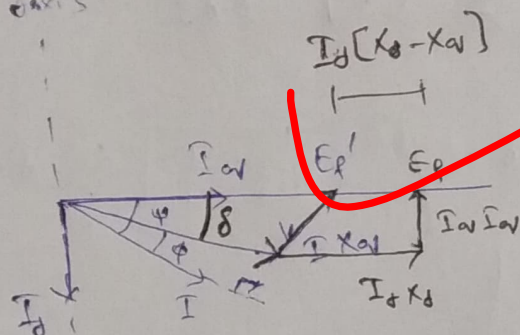

$$I_d = I \sin \phi$$

$$I_q = I \cos \phi$$

Let $V = 1 \angle 0^\circ$
for reference.

$$E_f' = V + j I X_a$$

$$E_f' = 1 \angle 0^\circ + j 0.6 \times 1.125 \angle -\cos^{-1} 0.8$$

$$E_f' = 1.5052 \angle 21.02$$

$\therefore$ load angle

$$\delta = 21.02$$

$$\psi = \delta + \phi = 21.02 + 36.87 = 57.89$$

$$I_d = I \sin \phi = 1.125 \sin 57.89 = 0.953 \text{ pu}$$

$$E_f = 1.5052 + I_d (X_d - X_a)$$

$$= 1.5052 + 0.953 (1 - 0.6)$$

$$\boxed{\text{excitation voltage} = E_f = 1.886 \text{ pu}}$$

Power delivered by Salient pole alternator

$$P = \frac{VE_f}{X_d} \sin \delta + \frac{V^2}{2} \left[\frac{1}{X_q} - \frac{1}{X_d} \right] \sin 2\delta$$

for max. power $\frac{dP}{d\delta} = 0$

$$\frac{dP}{d\delta} = \frac{VE_f}{X_d} \cos \delta + \frac{V^2}{2} \left[\frac{1}{X_q} - \frac{1}{X_d} \right] \times 2 \cos 2\delta$$

$$\frac{dP}{d\delta} = 0 \Rightarrow \frac{1 \times 1.886}{1} \cos \delta + 1^2 \left[\frac{1}{0.6} - \frac{1}{1} \right] \cos 2\delta = 0$$

$$\boxed{\delta = 72.84^\circ}$$

$$P_{\max} = \frac{1 \times 1.886}{1} \sin 72.84 + \frac{1^2}{2} \left[\frac{1}{0.6} - \frac{1}{1} \right] \sin 2(72.84)$$

$$\boxed{P_{\max} = 1.9708 \text{ pu}}$$

This much power it can deliver without losing synchronization before the excitation is reached to zero gradually.

4.(a)

$$X_s = 0.8 \text{ pu}$$

$$V = 1 \text{ pu}, E_f = 1.2 \text{ pu}$$

$$S = 1 \text{ pu}$$

$$E_f = V + I j X_s$$

$$1.2 \angle \delta = 1 \angle 0^\circ + j 0.8 \times I \angle -\phi$$

$$1.2 = 1 + 0.8 I \angle 90 - \phi$$

Equating the magnitudes

$$(1.2)^2 = [1 + 0.8 I \cos(90 - \phi)]^2 + [-0.8 I \sin(90 - \phi)]^2$$

$$(1.2)^2 = 1 + (0.8 I)^2 + 1.6 I \sin \phi$$

$$(0.8 I)^2 + 1.6 I \sin \phi - 0.44 = 0$$

$$\text{as } |S| = 1 \quad \& \quad |S| = |V I|$$

$$\Rightarrow 1 = 1 \times I \Rightarrow |I| = 1 \text{ pu}$$

$$\therefore (0.8)^2 + 1.6 \sin \phi - 0.44 = 0$$

$$\phi = +7.18^\circ$$

~~cos ϕ~~
mechanical Power delivered by motor = $V I \cos \phi$

$$P_m = 1 \times 1 \times (\cos 7.18^\circ)$$

$$\boxed{P_m = 0.9921 \text{ pu}}$$

Now for same load $P_m = 0.9921 \text{ pu}$, $E_f = 1 \text{ pu}$

$$E_f = V - j I_a X_s$$

$$1 \angle 0^\circ = 1 \angle 0^\circ - j 0.8 \times I_a \angle \phi$$

$$P_m = V I_a \cos \phi$$

$$0.9921 = 1 \times I_a \cos \phi$$

$$I_a \cos \phi = 0.9921$$

Equating magnitudes

$$1^2 = (1 + 0.8 I_a \sin \phi)^2 + (0.8 I_a \cos \phi)^2$$

$$1 = 1 + (0.8 I_a)^2 + 1.6 I_a \sin \phi$$

$$0.8^2 I_a^2 + 1.6 I_a \sin \phi = 0$$

$$0.8^2 \times \left(\frac{0.9921}{\cos \phi} \right)^2 + 1.6 \times 0.9921 \tan \phi = 0$$


$$\phi = -26.2653$$


$$I_a = \frac{0.9921}{\cos \phi} = \frac{0.9921}{\cos(26.2653)} = 1.1063$$

$$\text{Input KVA } |S| = |V I_a| = |1 \times 1.1063|$$

$$S = 1.1063 \text{ Pu}$$


$$S = 110.63 \%$$

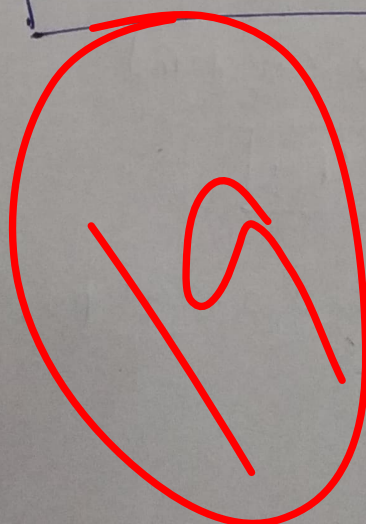

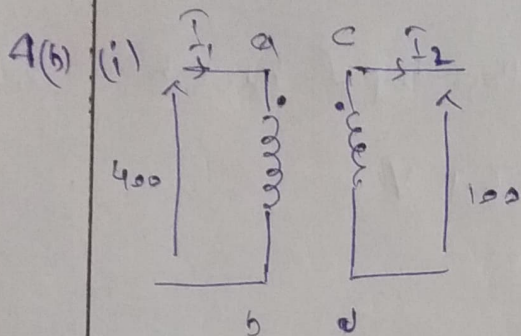

$$I_1 = \frac{5 \times 10^3}{400} = 12.5 \text{ A}$$

$$I_2 = 50 \text{ A}$$

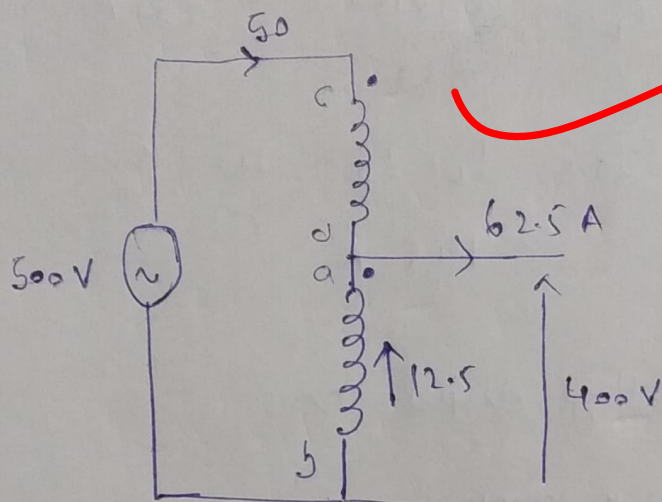

← auto transformer
Supply power at
400V from
500V source.

Output KVA = 400×62.5
= 25 KVA

(11) $P_{out} = 50 \text{ kW}$, $V = 250 \text{ V}$ $N = 400 \text{ rpm}$

$R_a = 0.02 \Omega$, $R_f = 50 \Omega$

as generator

$$I_f = \frac{V}{R_f} = \frac{250}{50} = 5 \text{ A}$$

$$P_{out} = V I_L \Rightarrow 50 \times 10^3 = 250 \times I_L$$

$$I_L = 200 \text{ A}$$

$$I_a = I_L + I_f = 200 + 5 = 205 \text{ A}$$

$$E'_g = V + I_a R_a = 250 + 205 \times 0.02 = 254.1 \text{ V}$$

Generator EMF $E_g = E'_g + \text{Voltage drop of brush}$

$$= 254.1 + 2 \times 1 = 256.1 \text{ V}$$

Now when it is working as motor

$$P_{in} = 50 \text{ kW}, \quad I_L = \frac{50 \times 10^3}{250} = 200 \text{ A}$$

$$I_f = 5 \text{ A}, \quad I_a = I_L - I_f = 200 - 5 = 195 \text{ A}$$

$E_b = V - I_a R_a - \text{Voltage drop of brush}$

$$= 250 - 195 \times 0.02 - 2 \times 1$$

$$E_b = 244.1$$

$$\text{As, } E \propto N \phi$$

$$\propto N$$


$$\text{as } \phi = \text{Constant}$$

$$\therefore \frac{E_g}{E_b} = \frac{N_g}{N_m}$$

$N_m \rightarrow \text{Speed of motor}$

$$\frac{256.1}{244.1} = \frac{400}{N_m}$$

$$N_m = 381.257 \text{ rpm}$$

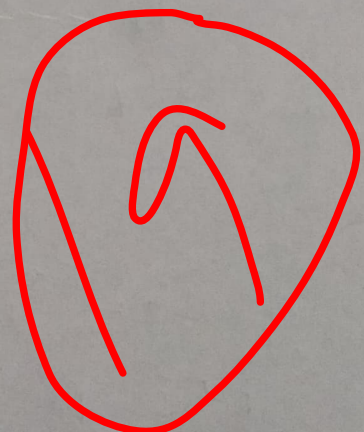

4(c)

As stator and rotor ~~losses~~ copper losses are equal

$$\therefore R_1 = R_2'$$

$$\text{and given } X_1 = 2X_2'$$

from load test. [S=0]

$$Z_{oc} = \frac{400/\sqrt{3}}{7.5} \angle (\cos^{-1} 0.135) = 30.792 \angle 82.2414^\circ \Omega$$

from blocked rotor test [S=1]

$$Z_{BR} = \frac{150/\sqrt{3}}{35} \angle (\cos^{-1} 0.44) = 4.2857/\sqrt{3} \angle 63.896^\circ \Omega$$

$$= 1.8857/\sqrt{3} + j 3.8485/\sqrt{3} \Omega$$

$$R_1 = R_2' = \frac{1.8857}{2\sqrt{3}} = \frac{0.94285}{\sqrt{3}} = 0.54435 \Omega$$

$$X_1 + 2X_2' = 3.48 \quad \frac{3.8485}{\sqrt{3}} \Rightarrow X_2' = 0.74064 \Omega$$


$$X_1 = 1.4813 \Omega$$

$$\text{Now } N = 960 \text{ rpm} \quad N_s = 1200 \text{ rpm}$$

Let no. of poles of motor = 6

$$N_s = \frac{120 \times f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$
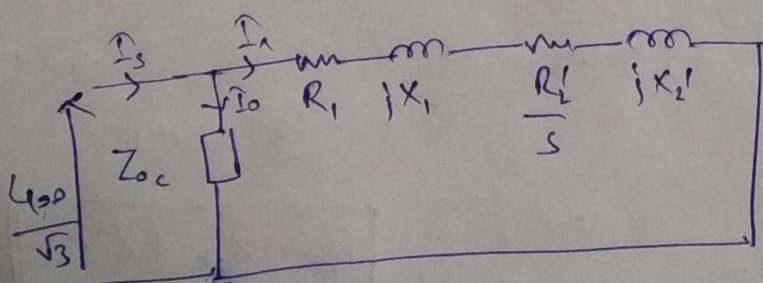
$$S = \frac{N_s - N}{N_s} = \frac{1000 - 960}{1000} = 0.04 \text{ pu}$$



$$I_a = \frac{400/\sqrt{3}}{0.54435 + \frac{0.54435}{0.24} + j \left[0.7404 + j14813 \right]}$$

$$I_a = 16.12 \angle -8.92^\circ \text{ A}$$

$$P_g = 3 \times 16.12^2 \times \frac{0.54435}{0.24}$$

$$[P_g = 3 I_a^2 \frac{R_2'}{s}]$$

$$P_g = 10608.88 \text{ Watts.}$$

$$\text{Rotor cu loss} = s P_g = 0.24 \times 10608.88 = 424.355$$

$$P_{out} = P_g - s P_g = 10184.525 \text{ W}$$

Net mechanical Power output

$$P_{out} = 10.18 \text{ kW}$$

net torque

$$T = \frac{P_g}{\omega_s} = \frac{10608.88 \times 60}{2\pi \times 1000}$$


$$T = 101.3 \text{ Nm}$$

$$\eta = \frac{\text{Output}}{\text{Output loss}} \times 100 = \frac{10.18 \times 10^3}{\sqrt{3} \times 400 \times I_a \times \cos \phi} \times 100$$

$$I_s = I_a + \frac{400/\sqrt{3}}{Z_{oc}} = 16.12 \angle -8.92^\circ + \frac{400/\sqrt{3}}{30.792 \angle 82.2414^\circ} = 19.634 \angle -30.384^\circ$$

$$\eta = \frac{10.18 \times 10^3}{\sqrt{3} \times 400 \times 19.634 \times \cos 30.384^\circ} \times 100 \Rightarrow \eta = 86.78\%$$


5(a)

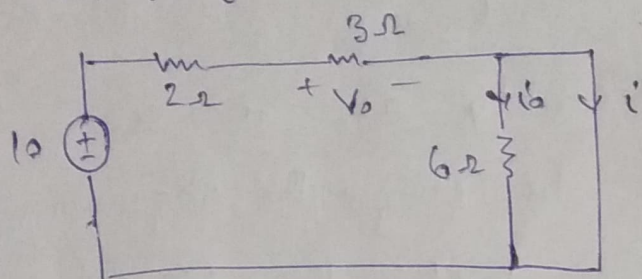At $t = 0^-$ 

$$i_0 = 0 \text{ A}$$

$$i = \frac{10}{2+3} = 2 \text{ A}$$

$$V_o = 2 \times 3 = 6 \text{ V}$$

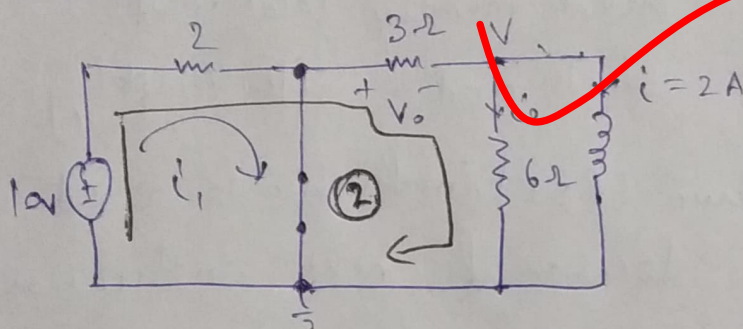At $t = 0^+$ Applying KVL in loop i_1

$$10 = 2i_1 \Rightarrow i_1 = 5 \text{ A}$$

$$\text{also, } V_o = -6i_1$$

KVL in loop 2

$$10 = 2i_1 -$$

KCL at V

$$\frac{V-0}{3} + \frac{V}{6} + 2 = 0$$

$$\frac{1}{2}V = -2$$


$$V = -4 \text{ V}$$

$$V_o = 0 - V$$

$$= 0 - (-4)$$

$$= 4 \text{ V}$$

$$i_0 = -\frac{4}{6} = -\frac{2}{3} \text{ A}$$

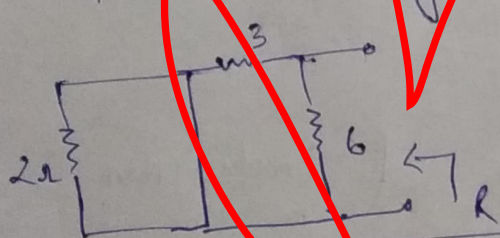So, Now calculating time constant $(\tau) = L/R$ 

$$R = 2 \Omega$$

$$\tau = \frac{2}{2} = 1 \text{ sec.}$$

$$i_0 = -\frac{2}{3} e^{-t/\tau} = -0.667 e^{-t} \text{ A}$$

$$V_o = 4 e^{-t} \text{ V} \quad i = 2 e^{-t} \text{ A}$$

Q6)

In writing a Program Stack and Subroutine Provides great deal of flexibility as in a Program if we require to change the Program Counter Sequence then to store the Present Sequence location we use Call instruction So it can store the Present memory location of Program Counter in Stack and after completing the Subroutine Return (RET) instruction is used to get back the location of next instruction that is to be executed Previously from the Stack. So, it is a quite flexible Process and microprocessor completes the Process without dealing much complications if Subroutine is not used.

Stack pointer Points to the location of memory which at is the top of Stack (TOS)

$$\text{Eg} \Rightarrow \text{SP} = 1000 \text{ H}$$

So it is pointing to location of 1000 H which is top of stack location.


Program Counter Points to the location of instruction

that is to be executed next after the Current instruction is Processed.

PUSH → instruction is used to push the data from Register Pair into top of stack.

Eg → PUSH H


$\boxed{H|L} \Rightarrow \boxed{21|00}$

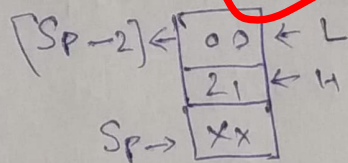

due to this SP changes to $SP-2$

POP → instruction is used to get the data present at top of stack into Register Pair

Eg POP R1

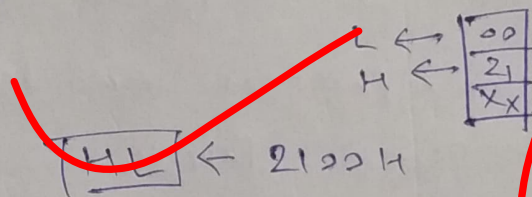

due to this SP changes to $SP+2$

CALL → instruction is used to Call Subroutines of interrupt or to change sequence of Program to deal great flexibility.

it pushes the present Program Counter value into TOS & changes sequence of Program to Subroutine address.

it changes SP to $SP-2$

RET → instruction is used at the end of subroutines to get back the value stored in TOS during CALL instruction to get back to Program which is being executed previously.

It changes SP to $[SP+2]$.

5. (c) Maskable Interrupt are those interrupt which can be masked when available i.e., if more than one interrupt occurs at same time then by using PIC (Priority Interrupt Controller) the interrupts having low priority are masked i.e., they will be ~~start~~ ~~to~~ processed when microprocessor is free.

Non maskable interrupts are those interrupts which can not be masked. They are highly prioritised interrupts. When they are triggered they have to be processed by microprocessor immediately after completing the present process.

Eg: Power Supply failure.

Maskable interrupts in 8085 are all software interrupts and RST 5.5, RST 6.5, RST 7.5, INTR

Nonmaskable interrupt in 8085 is TRAP [RST 4.5]
It is both level as well as edge triggered.

Handshake interrupt are the interrupts ~~where~~ which when triggered then is acknowledgment signal ~~back to~~ output from processor indicating that this interrupt is being triggered.

For eg: In 8085, if INTR interrupt is triggered then after receiving it INTA signal is sent

from the microprocessor in response of ~~int~~ INT. So it is like handshaking of microprocessor with interrupt signal. So they are handshake interrupts. And yes they refer to maskable interrupt because if they aren't masked there will be no acknowledgement signal which means they are masked.

5(a)

$$D = 3\text{m}, \quad \mu = \frac{0.58}{2} = 0.29\text{cm}$$

$$L = 2 \times 10^{-7} \times \ln\left(\frac{D}{\mu}\right) \text{ H/m}$$

$$= 2 \times 10^{-7} \times \ln\left(\frac{3 \times 100}{0.29 \times 100}\right)$$

$$= 14.383 \times 10^{-7} \text{ H/m}$$

$$= 14.383 \times 10^{-7} \times 10^3 \times 10^3 \times 1.609 \text{ mH/mile}$$

$$L = 2.314 \text{ mH/mile}$$

Due to internal flux linkage.

$$L = 0.05 \text{ mH/Km}$$

$$L = 0.05 \times 1.609 \text{ mH/mile}$$

$$L = 0.08045 \text{ mH/mile}$$

5.6)

$$P_R = 50 \text{ MW} \quad V_R = 220 \text{ KV} \quad \text{P.f}_R = 0.9 \text{ lag.}$$

$$I_R = \frac{50 \times 10^3}{\sqrt{3} \times 220} = 131.216 \text{ A}$$

$$V_S = AV_R + B I_R$$

$$V_S = [0.936 + j0.016] \times \frac{220}{\sqrt{3}} \angle 0^\circ + [33.5 + j138] \times 0.131216 \angle -\cos^{-1} 0.9$$

$$V_S = 131.763 \angle 7.1557 \text{ KV}$$

$$V_{SL} = 228.22 \text{ KV}$$

$$\text{Voltage Regulation} = \frac{\frac{V_S}{A} V_R}{V_R} \times 100 \quad [A = 0.9361]$$

$$= \frac{\frac{228.22}{0.9361} - 220}{220} \times 100$$

$$\boxed{\text{Voltage Regulation} = 10.817\%}$$

6.(a)
(i)

$$\frac{V_1}{V_2} = -\frac{1}{2} \quad \text{--- (1)}$$

$$\frac{\hat{I}_1}{\hat{I}_2} = -\frac{2}{1} \quad \text{--- (2)}$$

Applying KVL in input loop

$$120 \angle 0^\circ = [4 - j6] \hat{I}_1 + V_1 \quad \text{--- (3)}$$

Applying KVL in output loop

$$V_2 = 20 \hat{I}_2 \quad \text{--- (4)}$$

Using (1) & (2)

$$-2V_1 = 20 \left(-\frac{\hat{I}_1}{2} \right) \Rightarrow V_1 = 5\hat{I}_1 \quad \text{--- (5)}$$

Using (5) in (3)

$$120 \angle 0^\circ = [4 - j6 + 5] \hat{I}_1$$

$$\boxed{\hat{I}_1 = 11.094 \angle 33.69^\circ \text{ A}}$$

(a)

(b)

$$V_2 = -2V_1$$

using (1)

$$V_1 = 5\hat{I}_1$$

using (i)

$$V_2 = -10\hat{I}_1 \Rightarrow$$

$$\boxed{V_2 = V_o = 110.94 \angle -146.31^\circ \text{ V}}$$

$$V_2 = 20 \hat{I}_2$$

$$\hat{I}_2 = \frac{110.94 \angle -146.31^\circ}{20}$$

$$\boxed{\hat{I}_2 = 5.547 \angle -146.31^\circ \text{ A}}$$


6(a)(i)
6(c)

$$S = V I^*$$

$$= 120 \angle 0 \times 11.094 \angle -33.69$$

$$S = 1107.693 - j738.46 \text{ VA}$$

6(a)(ii)

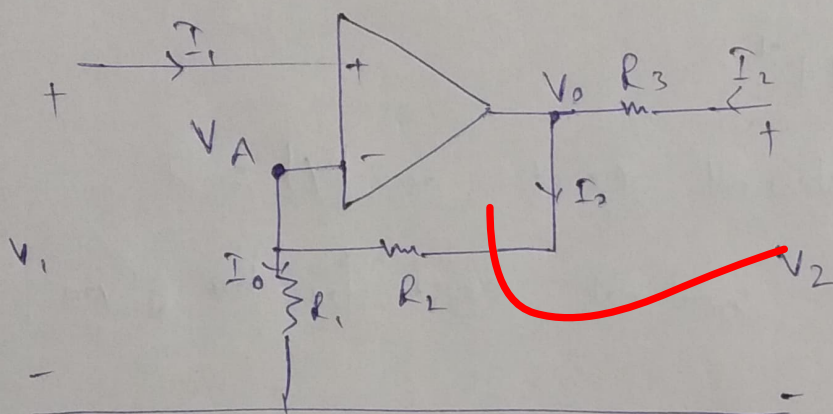

By virtual ground Concept $V_A = V_1$

Applying KCL at V_A

$$\frac{V_A}{R_1} + \frac{V_A - V_0}{R_2} = 0 \Rightarrow \frac{V_1}{R_1} + \frac{V_1 - V_0}{R_2} = 0 \quad \text{--- (1)}$$

$$I_2 = \frac{V_2 - V_0}{R_3} \Rightarrow I_2 = \frac{V_2}{R_3} - \frac{1}{R_3} \left[\frac{R_2}{R_1} V_1 + V_1 \right] \quad \text{Using (1)}$$

$$I_2 = -V_1 \left[\frac{R_2}{R_1 R_3} + \frac{1}{R_3} \right] + \frac{V_2}{R_3}$$

$$I_2 = -\frac{(R_2 + R_1)}{R_1 R_3} V_1 + \frac{V_2}{R_3}$$

and $I_1 = 0$

So Y parameter for the given circuit will be


$$[Y] = \begin{bmatrix} 0 & 0 \\ -\frac{(R_2 + R_1)}{R_1 R_3} & \frac{1}{R_3} \end{bmatrix}$$

As $[Z] = [Y]^{-1}$

But $[Y]^{-1}$ does not exist as $|Y| = 0$

So Z parameter will not exist for the given circuit.

6.(b)(i) At $t = 0^-$

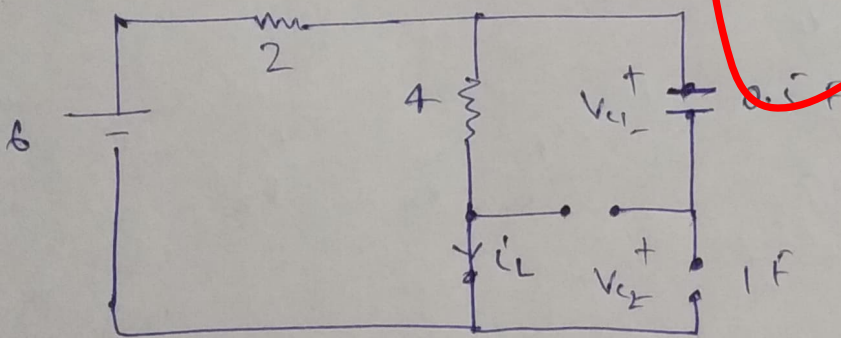

at steady state for DC excitation
inductor behaves like short circuit and
Capacitor behaves like open circuit
Using the above circuit

$$i_L(0^-) = \frac{6}{2+4} = 1 \text{ A}$$

Now

$$V_{c1}(0^-) = \frac{6 \times 4}{2+4} \times \frac{1}{1+0.5} = \frac{8}{3} \text{ V}$$

$$V_{c2}(0^-) = \frac{6 \times 4}{2+4} \times \frac{0.5}{1+0.5} = \frac{4}{3} \text{ V}$$


As inductor doesn't allow sudden change in current and capacitor doesn't allow sudden change in voltage.

$$\therefore i_L(0^-) = i_L(0^+) = 1 \text{ A} \rightarrow \text{behaves like current source}$$

$$V_{c1}(0^-) = V_{c1}(0^+) = \frac{8}{3} \text{ V} \left\{ \begin{array}{l} \text{behaves like voltage} \\ \text{source} \end{array} \right.$$

$$V_{c2}(0^-) = V_{c2}(0^+) = \frac{4}{3} \text{ V}$$

At $t=0^+$

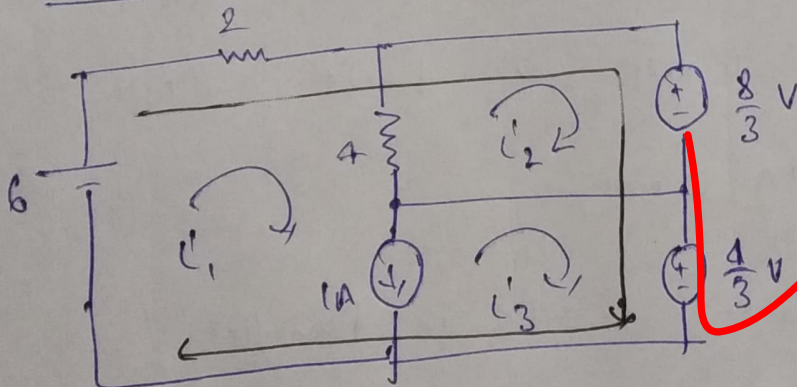

From the circuit

$$i_1 - i_3 = 1 \text{ A}$$

Apply KVL

$$6 = 2i_1 + \frac{8}{3} + \frac{4}{3}$$

$$\Rightarrow \boxed{i_1 = 1 \text{ A}}$$

KVL in loop i_2

$$i_2 = \frac{8}{3}$$

$$\boxed{i_2 = \frac{2}{3} \text{ A} = 0.667 \text{ A}}$$

KVL in loop 2

$$\frac{8}{3} = -4(i_2 - i_1) \Rightarrow \frac{8}{3} = -4[i_2 - 1]$$

$$i_2 = \frac{8}{3} \text{ A}$$

$$i_2 = 0.33 \text{ A}$$

Now as $i_1 - i_3 = 1$

$$1 - i_3 = 1$$

$$\Rightarrow i_3 = 0 \text{ A}$$

6. (b) (i)

When Connected in Series

$$L_{eq} = L_1 + L_2 + 2M = 12 \text{ mH}$$

$$L_{eq} = L_1 + L_2 - 2M = 4 \text{ mH}$$

$$\text{as } L_1 = L_2$$

$$\Rightarrow \text{So, } 2L + 2M = 12 \text{ mH} \Rightarrow L + M = 6 \text{ mH}$$

$$2L - 2M = 4 \text{ mH} \Rightarrow L - M = 2 \text{ mH}$$

$$L = 4 \text{ mH}, M = 2 \text{ mH}$$

maximum inductance when Connected in Parallel

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} = \frac{4 \times 4 - (2)^2}{4 + 4 - 2 \times 2} = 3 \text{ mH}$$

$$[L_{eq, \text{max}} = 3 \text{ mH}]$$

$$L_{eq, \text{min}} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} = \frac{4 \times 4 - (2)^2}{4 + 4 + 2 \times 2}$$

$$[L_{eq, \text{min}} = 1 \text{ mH}]$$

6(1)

$$f = 3 \text{ MHz}, \quad T_{\text{clk}} = \frac{1}{f} = \frac{1}{3} \text{ } \mu\text{sec.}$$

for 0.5 second delay

$$\text{No. of Tstates} = \frac{0.5}{T_{\text{clk}}} = 0.5 \times 3 \times 10^6 = 1.5 \times 10^6 \text{ Tstates required.}$$

Program

Tstates

LXI H, XXXX H	10
REPT: DCX H	6
MOV A, L	4
ORA H	4
JNZ REPT	10 / 7
RET	10

5. XXXX H $\rightarrow$ 16 bit number. Let it be x in decimal

~~Tstates~~ Tstates within the loop

$$[6 + 4 + 4 + 10]x + 7 - 10$$

$$T_{\text{WL}} = 24x - 3 \text{ Tstates}$$

Tstate ~~not~~ outside the loop

$$T_{\text{OL}} = 10 + 10 = 20 \text{ Tstates.}$$

$$T_{\text{WL}} + T_{\text{OL}} = 1.5 \times 10^6$$


$$24x - 3 + 10 + 10 = 1.5 \times 10^6$$

$$x = 62499.3$$

$$x \approx 62500$$

$$\Rightarrow \boxed{\text{XXXXH} = \text{F424 H}}$$

7(a)

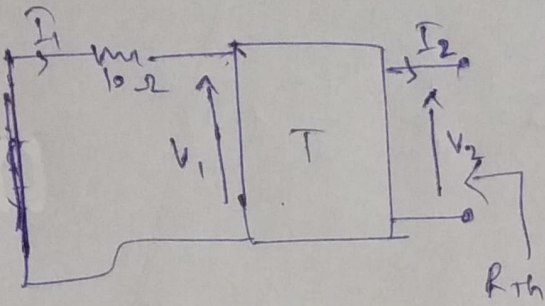

for maximum power transfer

$$R_L = R_{th} \quad (\text{using maximum power transfer theorem})$$

$$V_1 = 10 I_1 + V_{1'} \quad V_{1'} = -10 I_1 \quad - (1)$$

from ABCD Parameters

$$V_1 = 4 V_2 + 20 I_2 \quad - (2) \Rightarrow -10 I_1 = 4 V_2 + 20 I_2$$

$$I_1 = 0.1 V_2 + 2 I_2 \quad - (3)$$

$$R_{th} = \frac{V_2}{-I_2}$$

using (2) & (3)

$$\frac{-10 I_1}{I_1} = \frac{4 V_2 + 20 I_2}{0.1 V_2 + 2 I_2}$$


$$-V_2 - 20 I_2 = 4 V_2 + 20 I_2$$

$$5 V_2 = -40 I_2$$

$$\frac{V_2}{-I_2} = R_{th} = \frac{40}{5}$$

$$\Rightarrow R_L = R_{th} = 8 \Omega$$

Now V_{th}

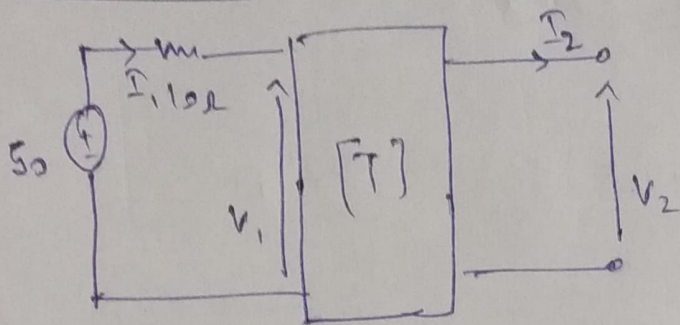

$$V_{th} = V_2$$

$$I_2 = 0$$

$$50 = 10I_1 + V_1 \quad \text{--- (1)}$$

$$I_1 = 0.1V_2 + 2I_2 \quad \text{--- (2)}$$

So,

$$50 = 10I_1 + 4V_2$$


$$[\because I_2 = 0]$$

$$\& \quad I_1 = 0.1V_2$$

$$50 = [10 \times 0.1 + 4] V_2$$

$$V_{th} = V_2 = 10V$$

Now circuit can be drawn as

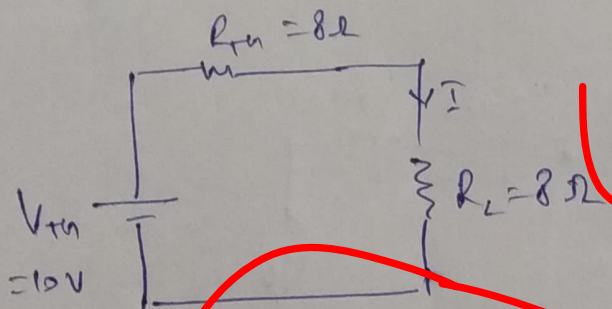

$$I = \frac{V_{th}}{R_{th} + R_L} = \frac{10}{8+8}$$

$$= 0.625A$$

max Power transferred to load

$$P_L = 0.625^2 \times R_L$$

$$P_L = 3.125W$$

7.(b) $S_B = 1000 \text{ MVA}, V_B = 20 \text{ KV}$

For G_1

$$X'' = 0.18 \times \frac{S_{\text{new}}}{S_{\text{old}}} = 0.18 \times \frac{1000}{750} = 0.24 \text{ pu}$$

For G_3

$$X'' = 0.13 \times \frac{1000}{1250} = 0.104 \text{ pu}$$

For T_1

$$X = 0.1 \times \frac{1000}{750} = 0.1333 \text{ pu}$$


For T_2

$$X = 0.08 \times \frac{1000}{1250} = 0.064 \text{ pu}$$


For line

$$X_l = \frac{50}{(500)^2} \times 1000 = 0.2 \text{ pu}$$

(i)

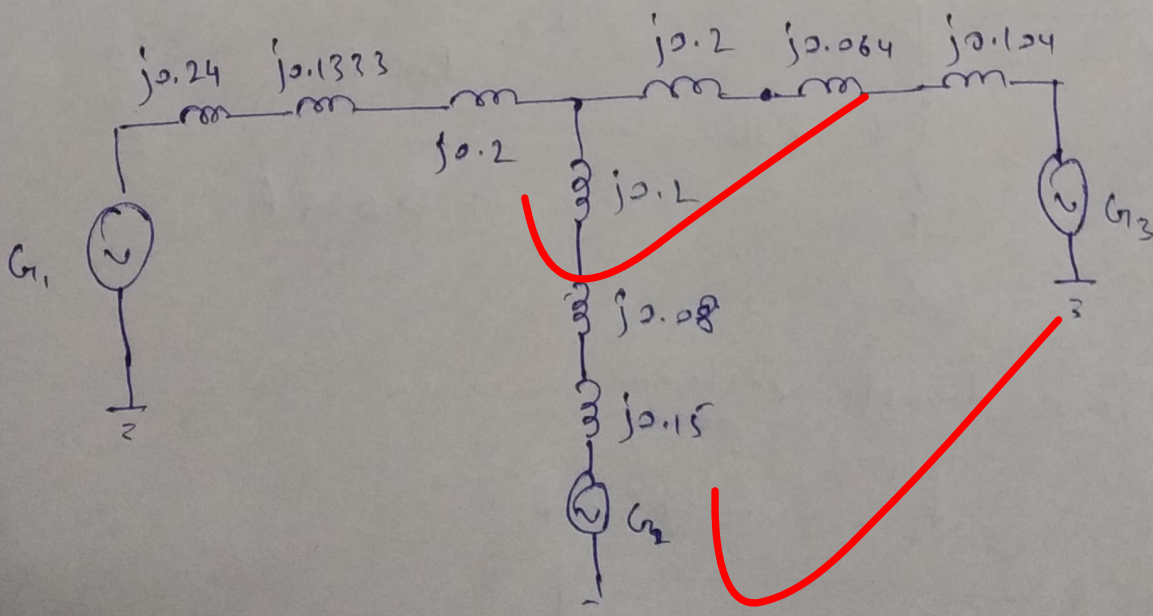


(i)

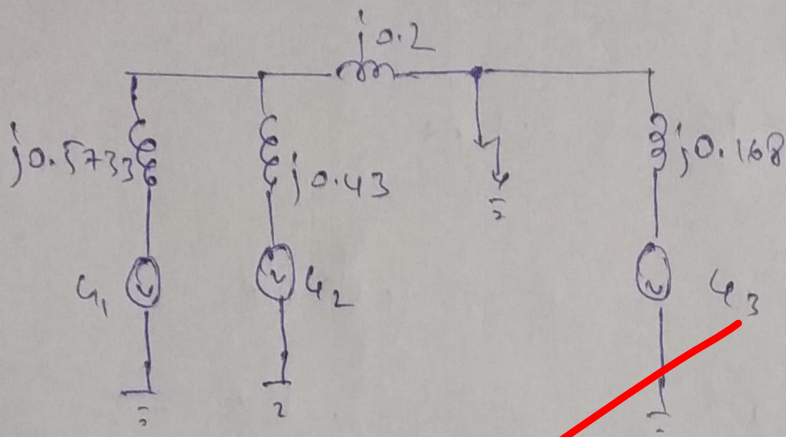

$$Z_{th} = j \left\{ \left[(0.5733 \parallel 0.43) + 0.2 \right] \parallel 0.168 \right\}$$

$$Z_{th} = j \left\{ 0.445708 \parallel 0.168 \right\}$$

$$Z_{th} = j0.12201 \text{ pu}$$

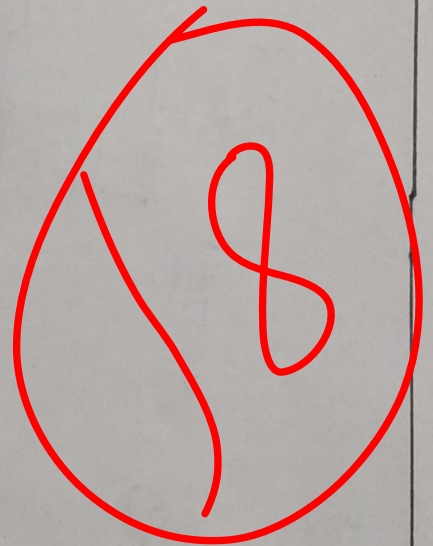

(iii)

$$\hat{I}_f = \frac{V}{Z_{th}} = \frac{485}{500} \times \frac{1}{j0.12201}$$

$$\hat{I}_f = 7.95 \angle -93^\circ \text{ pu}$$

$$\hat{I}_f = 7.95 \times \frac{1000}{\sqrt{3} \times 500} \text{ KA}$$

$$\hat{I}_f = 9.18 \angle -93^\circ \text{ KA}$$

7(c)



$$S_{\text{Base}} = 40 \text{ MVA}$$

$$\therefore X_T = 0.075 \times \frac{40}{30} = 0.1 \text{ pu}$$

Base Current on HV side of transformer

$$I_B = \frac{S_B}{\sqrt{3} \times V_B} = \frac{40}{\sqrt{3} \times 66} \text{ KA}$$

$$I_B = 349.91 \text{ A}$$

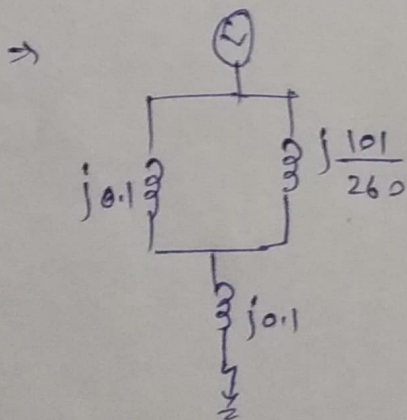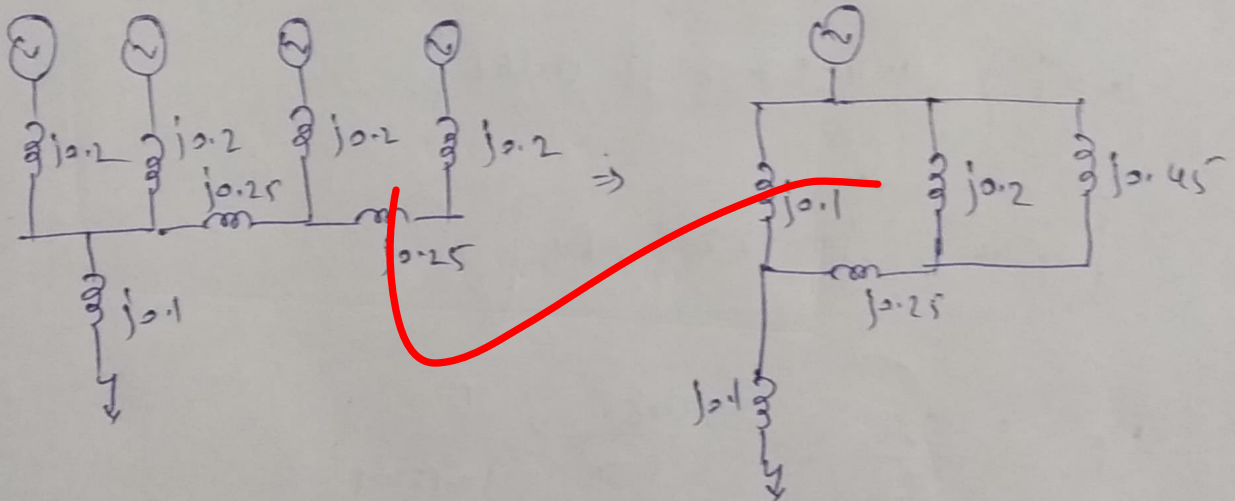

$$X_{th} = j0.17952 \text{ pu}$$

$$I_f = \frac{1}{X_{th}} = \frac{1}{j0.17952 \text{ pu}}$$

$$I_f = -j5.57 \text{ pu}$$

Current fed into the fault

$$I_f = -j5.57 \times I_B = -j1949.06 \text{ A}$$

$$\text{Fault MVA in PU} = I_f (\text{pu})$$

$$= 5.57 \text{ pu}$$

$$\text{Fault MVA (rms)} = \text{Fault MVA} \times S_{\text{Base}}$$

$$= 5.57 \times 40$$

$$\text{Fault MVA}_{\text{rms}} = 222.8 \text{ MVA}$$