

Q10 Given: Input Voltage, $V_s = 20V$


Duty ratio, $D = 0.6$

Inductance, $L = 100\mu H$

Resistance, $R = 50\Omega$

Capacitance, $C = 100\mu F$

Switching frequency, $f = 15kHz$

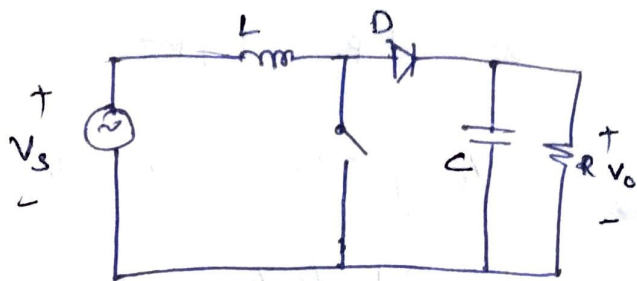

Boost converter

When SW is ON

$$V_s = L \frac{\Delta I}{\Delta T} = L \frac{\Delta I}{D} f \Rightarrow 20 = \frac{10^{-4} \times \Delta I \times 15 \times 10^3}{0.6}$$

$$\Delta I = 8A$$

$$\text{So, } \boxed{\frac{\Delta I}{2} = 4A}$$

Average inductor current, $i_{Lavg} = i_{in}$ (input current)

Considering continuous conduction -

~~Output Voltage~~, $\boxed{V_o = \frac{V_s}{1-D}} \Rightarrow \boxed{V_o = 40V}$

So, Output current, $\boxed{i_o = \frac{V_o}{R}} \Rightarrow \boxed{i_o = 1A}$


So, $V_o i_o = V_s i_{in} \Rightarrow 50 = 20 \times i_{in}$

$$\boxed{i_{in} = 2.5A} \quad \& \quad \boxed{i_{Lavg} = i_{in} = 2.5A}$$


So, $i_{Lavg} < \frac{\Delta I}{2}$ Hence ~~discontinuous~~ discontinuous conduction mode.

$$i_{Lavg} = \frac{1}{T} \times \left[\frac{1}{2} \times \Delta I_b \times BT \right]$$
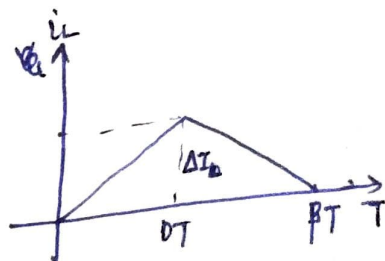
$$\boxed{i_{Lavg} = \frac{\Delta I_b}{2}} \Rightarrow \boxed{i_{Lavg} = 4A}$$


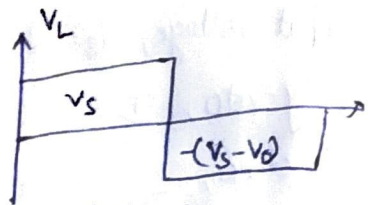
$$2.5 = 4\beta \Rightarrow \boxed{\beta = 0.625}$$



As, $V_{L\text{avg}} = 0$ ($V_{L\text{avg}}$ is inductor average voltage)

$$\Rightarrow [V_s D + (V_s - V_o)(\beta - D)] T \times \frac{1}{T} = 0$$

$$\Rightarrow V_s D + V_s \beta - V_s D - V_o \beta + V_o D = 0$$

$$\Rightarrow \cancel{V_o D} + V_s \beta - \cancel{V_s D} - V_o \beta + V_o D = 0$$

$$\boxed{V_o = V_s \left[\frac{\beta}{\beta - D} \right]}$$


$$\Rightarrow \boxed{V_o = 500V}$$

Maximum inductor current, $\boxed{I_{L\text{max}} = I_{\text{avg}} + \frac{\Delta I_L}{2}}$

$$I_{L\text{max}} = 2.5 + 4$$

$$\boxed{I_{L\text{max}} = 6.5A}$$

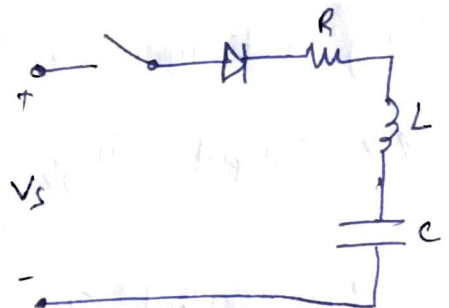(b) Given: Resistance, $R = 10\Omega$
 Inductance, $L = 1mH$
 Capacitance, $C = 5\mu F$
 Supply Voltage, $V_s = 230V$



$\Rightarrow \frac{V_s}{s} \Leftarrow$ By applying KVL & Laplace transform in equation 1 we get -

$$\frac{V_s}{s} = L s I(s) + \frac{I(s)}{Cs} + R I(s)$$

$$\Rightarrow \frac{V_s}{s} = I(s) \left[\frac{Lcs^2 + Rcs + 1}{cs} \right]$$

$$\Rightarrow I(s) = \frac{V_s}{L \left(s^2 + \frac{R}{L} s + \frac{1}{LC} \right)} = \frac{V_s}{L \left(s^2 + \frac{R}{L} s + \frac{1}{LC} \right)}$$

$$\Rightarrow I(s) = \frac{230}{10^{-3} [s^2 + 10^4 s + 2 \times 10^8]}$$

$$\Rightarrow I(s) = \frac{230 \times 10^3}{(s + 5 \times 10^3)^2 + ((1.75)^{1/2} \times 10^4)^2}$$

$$\Rightarrow i(t) = \frac{23 \times 10^4}{1.75^{1/2} \times 10^4} e^{-5 \times 10^3 t} \sin(1.323 \times 10^4 t)$$

$$\Rightarrow i(t) = 17.386366 e^{-5 \times 10^3 t} \sin(1.323 \times 10^4 t)$$

Conduction time of diode t_c , then,

$$1.323 \times 10^4 \times t_c = \pi \Rightarrow t_c = 0.2375 \text{ ms}$$

$$\frac{di(t)}{dt} = 17.386366 \times (-5 \times 10^3) e^{-5 \times 10^3 t} \sin(1.323 \times 10^4 t)$$

$$+ 17.386366 e^{-5 \times 10^3 t} \cos(1.323 \times 10^4 t)$$

$$\left. \frac{di(t)}{dt} \right|_{t=0} = 17.386366 \times 1.323 \times 10^4$$

$$\left. \frac{di(t)}{dt} \right|_{t=0} = 230621.6222 \text{ A/s}$$

①② Given: $5x + 3y + 7z = 4$
 $3x + 26y + 2z = 9$
 $7x + 2y + 10z = 5$

So,

$$[A] = \begin{bmatrix} 5 & 3 & 7 \\ 3 & 26 & 2 \\ 7 & 2 & 10 \end{bmatrix} \text{ \& } B = \begin{bmatrix} 4 \\ 9 \\ 5 \end{bmatrix}$$

$$[A:B] = \begin{bmatrix} 5 & 3 & 7 & | & 4 \\ 3 & 26 & 2 & | & 9 \\ 7 & 2 & 10 & | & 5 \end{bmatrix}$$

$$= \begin{bmatrix} 5 & 3 & 7 & | & 4 \\ 0 & 24.2 & -2.2 & | & 6.6 \\ 0 & -2.2 & 0.2 & | & -0.6 \end{bmatrix}$$

$$= \begin{bmatrix} 5 & 3 & 7 & | & 4 \\ 0 & 24.2 & -2.2 & | & 6.6 \\ 0 & 0 & 0 & | & 0 \end{bmatrix}$$

Hence, $\text{Rang}[A] = \text{Rank of } [A:B] \neq \text{Number of Variables}$
~~But~~ Hence, infinite solution.

①③ Given: $f(z) = \frac{z^3}{(z-1)^4 (z-2) (z-3)}$ C: $|z| = 2.5$

As, $z=3$ lies outside the contour C, So,

$$\oint f(z) dz = 2\pi i \left[\text{Res}(f(z)) \Big|_{z=1} + \text{Res}(f(z)) \Big|_{z=2} \right]$$

$$\text{Res}(f(z))|_{z=1} = \frac{1}{3!} \lim_{z \rightarrow 1} \frac{d^3}{dz^3} \frac{z^3}{(z-2)(z-3)(z-1)^4}$$

$$\text{Res}(f(z))|_{z=1} = \frac{1}{6} \lim_{z \rightarrow 1} \frac{d^3}{dz^3} \left[\frac{z^3}{z^2-5z+6} \right]$$

$$= \frac{1}{6} \lim_{z \rightarrow 1} \frac{d^3}{dz^3} \left[\frac{z^3}{z^2-5z+6} \right]$$

$$\frac{d}{dz} \left[\frac{z^3}{z^2-5z+6} \right] = \frac{3z^2(z^2-5z+6) - (2z-5)z^3}{(z^2-5z+6)^2}$$

$$= \frac{3z^4 - 15z^3 + 18z^2 - 2z^4 + 5z^3}{(z^2-5z+6)^2}$$

$$= \frac{z^4 - 10z^3 + 18z^2}{(z^2-5z+6)^2}$$

$$\frac{d^2}{dz^2} \left[\frac{z^3}{z^2-5z+6} \right] = \frac{(4z^3 - 30z^2 + 36z)(z^2-5z+6)^2 - 2(z^2-5z+6)(2z-5)(z^4-10z^3+18z^2)}{(z^2-5z+6)^4}$$

$$= \frac{(4z^3 - 30z^2 + 36z)(z^2-5z+6) - 2(2z-5)(z^4-10z^3+18z^2)}{(z^2-5z+6)^3}$$

$$= \frac{4z^5 - 50z^4 + 24z^3 + 150z^3 - 180z^2 + 36z^3 - 180z^2 + 216z - (4z-10)(z^4-10z^3+18z^2)}{z^2-5z+6}$$

$$= \frac{4z^5 - 56z^4 + 210z^3 - 360z^2 + 216z - 4z^5 + 40z^4 - 72z^3}{-10z^4}$$

$$\frac{d^3}{dz^3} [X] = 37.875$$

$$\operatorname{Res} f(z) \Big|_{z=2} = \lim_{z \rightarrow 2} (z-2) \frac{z^3}{(z-1)^4 (z-2)(z-3)}$$

$$= \frac{8}{-1} = -8$$

$$\boxed{\operatorname{Res} f(z) \Big|_{z=2} = -8}$$

$$\text{So, } \oint f(z) dz = 2\pi j [37.875 + (-8)]$$

$$\boxed{\oint f(z) dz = 187.71 j}$$

①② $x = a\sqrt{2}$

$$x = 2a \cos \theta$$

$$x^2 + y^2 = 2a^2$$


$$(x-a)^2 + y^2 = a^2$$

$$x^2 + y^2 = 2a^2$$

$$x^2 + a^2 - 2ax + y^2 = a^2$$

$$\Rightarrow 2a^2 = 2ax$$

$$\Rightarrow \boxed{x=a}$$

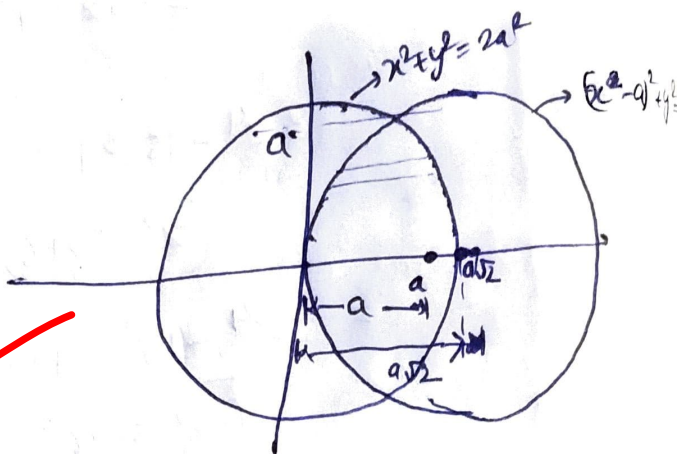

Area, $A = 2x \int_0^a \int_{\sqrt{2a^2-y^2}}^{\sqrt{a^2-y^2}+a} dx dy$

$$A = 2x \int_0^a \left(\sqrt{a^2-y^2} + a - \sqrt{2a^2-y^2} \right) dy$$


$$A =$$

Q) Given: $V_s = 120\sqrt{2} \sin(120\pi t)$

Resistance, $R = 10\Omega$

Inductance, $L = 20\text{mH}$

Firing angle, $\alpha = 60^\circ$

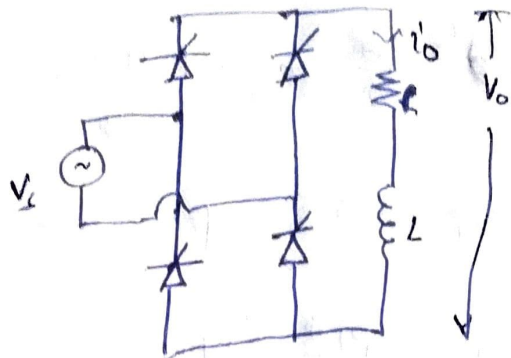

$$i_o = \frac{V_s}{|Z|} \sin(120\pi t - \phi) + A e^{-t/\tau}$$

$$\tau = \frac{L}{R} = \frac{20 \times 10^{-3}}{10} = 2 \times 10^{-3} = \frac{1}{500}$$

$$|Z| = [R^2 + (120\pi \times L)^2]^{1/2} \Rightarrow |Z| = 12.524\Omega$$

$$\phi = \tan^{-1} \left(\frac{120\pi \times L}{R} \right) = 37.0156^\circ$$

$$\Rightarrow i_o = 13.5504 \sin(120\pi t - 37.0156) + A e^{-t/1\text{ms}}$$

$$\Rightarrow i_o = 13.5504 \sin(120\pi t - 37.0156) + A e^{-500t} \text{ A}$$

at, $120\pi t = \pi/3$, $i_o = 0 \text{ A}$.

$$t = \frac{1}{120 \times 3} = \frac{1}{360}$$

$$-5.291167 = A e^{-500 \times \frac{1}{360}} \Rightarrow A = 21.21965$$

$$\Rightarrow i_o = 13.5504 \sin(120\pi t - 37.0156) + 21.21965 e^{-500t} \text{ A}$$

Considering, i_o at 200° as initial condition, $120\pi t = 200 \times \frac{\pi}{180}$

$$t = \frac{200}{120\pi} \times \frac{\pi}{180}$$

$$i_o = 4.1723 \text{ A} \Rightarrow i_o = 13.5504 \sin(\beta - 37.0156) + 21.21965 e^{-500t}$$

$$\beta_0' = \cancel{1000} \beta_0 + \frac{4.1723}{29.2841}$$

$$\cancel{i_0} \Rightarrow \cancel{0.6825} \quad \beta_1 = 3.6335 \text{ rad.}$$

$$\beta_2 = \beta_1 + \frac{f(\beta_1)}{f'(\beta_1)} \Rightarrow \beta_2 = 3.6335 + \frac{(-7.28367)}{11.2173}$$

$$\beta_2 = 2.984113 \text{ rad}$$

$$\beta_3 = 2.984113 + \frac{(-7.17806)}{}$$

$$i_0 = 13.5504 \sin(\beta - 0.646) + 21.21965 \times e^{-\frac{\beta \times 500}{120\pi}}$$

$$\boxed{i_0|_{\pi} = 8.486767 \text{ A.}}$$

$$i_0' = 13.5504 \cos(\beta - 0.646) - \frac{500 \times 21.21965}{120\pi} e^{-\frac{\beta \times 500}{120\pi}}$$

$$i_0'|_{\pi} = 11.255946 \text{ A.}$$

$$\beta_1 = \beta_0 + \frac{i_0|_{\pi}}{i_0'|_{\pi}} \Rightarrow \beta_1 = \pi + 0.753381$$

$$\Rightarrow \boxed{\beta_1 = 3.895574 \text{ rad}}$$

$$\beta_2 = \beta_1 - \frac{i_0|_{\beta_1}}{i_0'|_{\beta_1}} = 3.895574 + \frac{-1.93872}{13.63206}$$

$$\boxed{\beta_2 = 3.79787 \text{ rad}}$$

$$\beta_3 = 3.79787 + \frac{5.98 \times 10^{-3}}{13.432657} \Rightarrow \boxed{\beta_3 = 3.79978 \text{ rad}}$$

$$\boxed{\beta_3 = 217.5982^\circ}$$

where β_3 is extinction angle

Average load current, $I_0 = \frac{1}{\pi} \int i_0 d(\omega t)$

$$I_0 = 9.52054 \text{ A}$$

⑥ Single phase full bridge inverter.

Given: Supply voltage, $V_s = 230 \text{ V}$

Time, $T = 1 \text{ ms}$

frequency, $f = 1 \text{ kHz}$

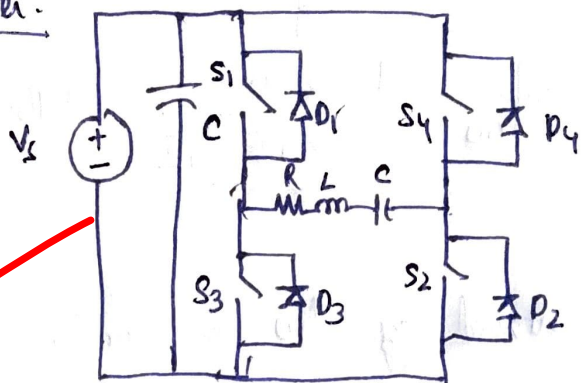


fig 1- ϕ full bridge inverter

Resistance, $R = 1 \Omega$

Inductive reactance, $X_L = \omega L = 6 \Omega$

Capacitive reactance, $X_C = \frac{1}{\omega C} = 7 \Omega$

$$V_o = a_0 + \sum_{n=1}^{\infty} a_n \cos n\omega t + b_n \sin n\omega t$$


$a_0 = a_n = 0$ (as odd symmetric signal)

$$b_n = \frac{2}{\pi} \int_0^{\pi} V_s \sin n\omega t d(\omega t)$$

$$b_n = \frac{2V_s}{n\pi} [-\cos n\omega t]_0^{\pi}$$

$$b_n = \frac{4V_s}{n\pi}$$
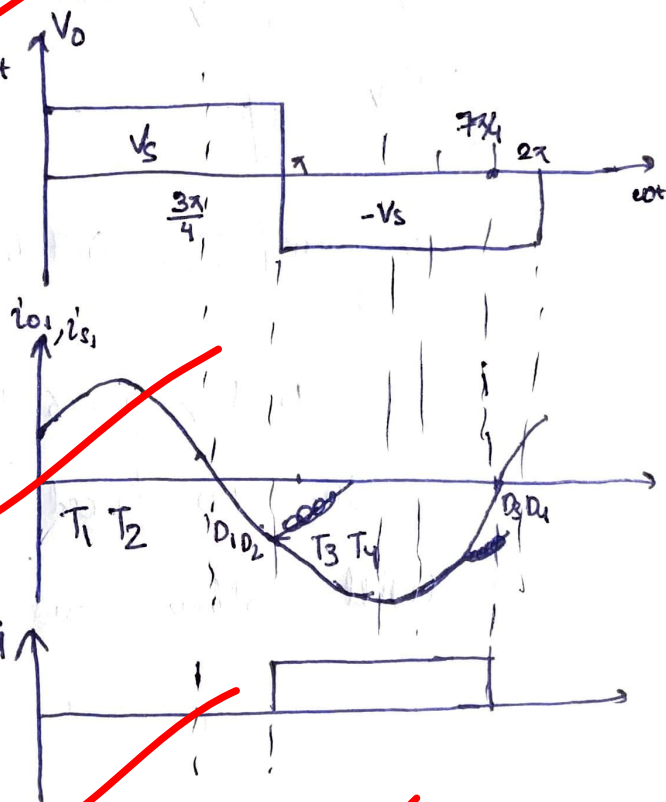
$$V_o = \sum_{n=1}^{\infty} \frac{4V_s}{n\pi} \sin n\omega t$$



Impedance (fundamental), $|Z_{01}| = \sqrt{1^2 + (6-7)^2} = \sqrt{2}$

$$\Rightarrow |Z_{01}| = \sqrt{2} \Omega$$

$$\phi = \tan^{-1}\left(\frac{7-6}{1}\right) = 45^\circ$$

$$i_{o1} = \frac{4 V_s}{\pi |Z_{o1}|} \sin(\omega t + 45^\circ)$$

$$\Rightarrow |i_{o1}|_{\text{rms}} = \frac{4 \times 280}{\pi \times \sqrt{2} \times \sqrt{2}} = 146.4225 \text{ A}$$

(ii) Power delivered by the fundamental component,

$$P_{o1} = i_{o1,\text{rms}}^2 \times R$$

$$P_{o1} = 21439.56246 \text{ W}$$

(iii)

$$\omega t_q = 2\pi f t_q = 2 \times \pi \times 10^3 \times 10^{-4}$$

$$\omega t_q = \frac{\pi}{5}$$

$$\Rightarrow \tan\left(\frac{\pi}{5}\right) = 0.72654$$

$$\text{as } 1 > 0.72654$$

So, no forced commutation, the circuit will follow load commutation.



Q. Given: $A = \begin{bmatrix} 3 & 1 & 4 \\ 0 & 2 & 6 \\ 0 & 0 & 5 \end{bmatrix}$

~~$[A - \lambda I] = \begin{bmatrix} 3-\lambda & 1 & 4 \\ 0 & 2-\lambda & 6 \\ 0 & 0 & 5-\lambda \end{bmatrix}$~~

$[A - \lambda I] = \begin{bmatrix} 3-\lambda & 1 & 4 \\ 0 & 2-\lambda & 6 \\ 0 & 0 & 5-\lambda \end{bmatrix}$

$= (3-\lambda) [(2-\lambda)(5-\lambda)] - 1[0-0] + 4[0-0]$

$\Rightarrow (\lambda-3)(\lambda-2)(\lambda-5) = 0$

Hence, Eigen Values, $\lambda = 2, 3, 5$

for $\lambda = 2$

$\begin{bmatrix} 3 & 1 & 4 \\ 0 & 0 & 6 \\ 0 & 0 & 3 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = 2 \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix}$

$\Rightarrow 3x_1 + x_2 + 4x_3 = 2x_1 \Rightarrow x_1 + x_2 + 4x_3 = 0 \quad \text{--- (1)}$

$2x_2 + 6x_3 = 2x_2 \Rightarrow x_3 = 0$

$5x_3 = 2x_3 \Rightarrow x_3 = 0$

$x_1 = -x_2$

from (1)

So, Eigen vector, $v_1 = \begin{bmatrix} 1 \\ -1 \\ 0 \end{bmatrix}$

for $\lambda = 3$

$\begin{bmatrix} 3 & 1 & 4 \\ 0 & 2 & 6 \\ 0 & 0 & 5 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = 3 \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix}$

$$3x_1 + 2x_2 + 4x_3 = 3x_1$$

$$\Rightarrow x_2 + 4x_3 = 0$$

$$2x_2 + 6x_3 = 0 \Rightarrow x_2 = -3x_3$$

$$5x_3 = 3x_3 \Rightarrow x_3 = 0$$

$$\Rightarrow x_2 = 0$$

$$\Rightarrow x_1 = K \text{ (any arbitrary constant)}$$

So, eigen vector, $v_2 = \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix}$

for $\lambda = 5$

$$\begin{bmatrix} 3 & 1 & 4 \\ 0 & 2 & 6 \\ 0 & 0 & 5 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = 5 \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix}$$

$$\Rightarrow 3x_1 + x_2 + 4x_3 = 5x_1$$

$$\Rightarrow 2x_1 = x_2 + 4x_3$$

$$2x_2 + 6x_3 = 5x_2 \Rightarrow 3x_2 = 6x_3 \Rightarrow x_2 = 2x_3$$

$$5x_3 = 5x_3$$

$$\text{Let } x_3 = 1$$

$$2x_1 = 6x_3 \Rightarrow x_1 = 3x_3$$

So, eigen vector, $v_3 = \begin{bmatrix} 3 \\ 2 \\ 1 \end{bmatrix}$

(ii) Given: $I = \int [(xy + y^2) dx + x^2 dy]$

$$C: y = x$$

$$y = x^2$$

$$\Rightarrow x(x-1) = 0$$


$$x = 0, 1$$

$$I = \int (xy + y^2) dx + \int x^2 dy$$

$$I = \int_C [(xy + y^2) \hat{a}_n + x^2 \hat{a}_y]$$

$$[dx \hat{a}_n + dy \hat{a}_y]$$

$$\Rightarrow x(x-1) = 0$$

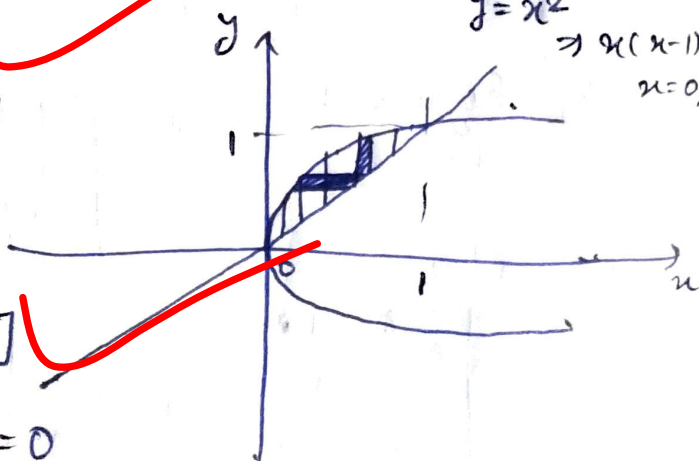

~~$$f(x,y) = (xy + y^2) \hat{a}_x + x^2 \hat{a}_y$$~~

[By using Stokes's theorem]

$$\vec{\nabla} \times \vec{f} = \begin{bmatrix} \hat{a}_x & \hat{a}_y & \hat{a}_z \\ \frac{\partial}{\partial x} & \frac{\partial}{\partial y} & \frac{\partial}{\partial z} \\ xy+y^2 & x^2 & 0 \end{bmatrix} = \hat{a}_z [2x - x - 2y]$$

$$= (x-2y) \hat{a}_z$$

$$I_1 = \iint_S (\vec{\nabla} \times \vec{f}) \cdot (dx dy \hat{a}_z) \quad (\text{By using Stokes's theorem})$$

$$\Rightarrow I_1 = \int_0^1 \int_x^{x^2} (x-2y) dy dx = \int_0^1 \int_x^{x^2} (x-2y) dy dx$$

~~$$\Rightarrow I = \int_0^1 [(x^2 - 2xy)]_{\frac{x}{2}}^{\frac{x}{2}} dy = \int_0^1 [(y^2 - 2y^2) - [y - 2y \cdot \frac{1}{2}]] dy$$~~
~~$$\Rightarrow I = \int_0^1 [-y^2 - y + 2y \cdot \frac{1}{2}] dy$$~~

~~$$\Rightarrow I_1 = \int_0^1 \cancel{[xy - y^2]}_x^{x^2} dx = \int_0^1 x^3 - x^4 - [x^2 - x^4] dx$$~~

~~$$\Rightarrow I_1 = \frac{1}{20}$$~~

Green's theorem

~~Let~~ Let $M = xy + y^2$ & $N = x^2$.

$$I_2 = \iint \left(\frac{\partial N}{\partial x} - \frac{\partial M}{\partial y} \right) dy dx$$

$$I_2 = \iint (2x - x - 2y) dy dx$$

$$I_2 = \int_0^1 \int_x^{x^2} (x-2y) dy dx$$

$$I_2 = \frac{1}{20}$$

As, $I_1 = I_2$, So, Green's theorem is verified.

③ ④ (i) Given: $[D^2 - 4D + 4]y = 8x^2 e^{2x} \sin 2x$

for complementary solution,

$$[D^2 - 4D + 4]y_{cm} = 0$$

$$\Rightarrow D^2 - 4D + 4 = 0 \Rightarrow (D-2)^2 = 0 \Rightarrow D = 2, 2$$

$$\Rightarrow y_{cm} = (A + Bx)e^{2x}$$

for particular solution:

$$[D^2 - 4D + 4]y_{PI} = 8x^2 e^{2x} \sin 2x$$

$$y_{PI} = \frac{8x^2 e^{2x} \sin 2x}{(D^2 - 4D + 4)}$$

$$\Rightarrow y_{PI} = e^{2x} \frac{8x^2 \sin 2x}{(D+2)^2 - 4(D+2) + 4} = e^{2x} \frac{8x^2 \sin 2x}{D^2 + 4D - 4D - 8 + 4}$$

$$\Rightarrow y_{PI} = 8e^{2x} \frac{x^2 \sin 2x}{D^2}$$

$$\Rightarrow y_{PI} = 8e^{2x} \frac{1}{D} \int x^2 \sin 2x$$

$$I = \int x^2 \sin 2x$$

$$I = \cancel{\frac{-x^2 \cos 2x}{2}} - \frac{x^2 \cos 2x}{2} + \frac{2}{2} \int x \cos 2x dx$$

$$I = \frac{-x^2 \cos 2x}{2} + \int x \cos 2x dx = \frac{-x^2 \cos 2x}{2} + \frac{x \sin 2x}{2} - \frac{1}{2} \int \sin 2x dx$$

$$I = \frac{-x^2 \cos 2x}{2} + \frac{x}{2} \sin 2x + \frac{1}{4} \cos 2x$$

$$y_{PI} = 8e^{2x} \left[\int \left(\frac{-x^2}{2} \cos 2x + \frac{x}{2} \sin 2x + \frac{1}{4} \cos 2x \right) dx \right]$$

$$\Rightarrow y_{PI} = 8e^{2x} \left[-\frac{1}{2} \int x^2 \cos 2x dx + \frac{1}{2} \int x \sin 2x dx + \frac{1}{8} \sin 2x \right]$$

$$I_1 = \int x^2 \cos 2x = \frac{x^2 \sin 2x}{2} - \int x \sin 2x dx$$

$$\Rightarrow y_{PI} = 8e^{2x} \left[-\frac{x^2 \sin 2x}{4} + \int x \sin 2x dx + \frac{1}{8} \sin 2x \right]$$

$$\Rightarrow y_{PI} = 8e^{2x} \left[-\frac{x^2 \sin 2x}{4} - \frac{x \cos 2x}{2} + \frac{1}{2} \int \cos 2x dx + \frac{1}{8} \sin 2x \right]$$

$$\Rightarrow y_{PI} = 8e^{2x} \left[-\frac{x^2 \sin 2x}{4} - \frac{x \cos 2x}{2} + \frac{3}{8} \sin 2x \right]$$

$$\Rightarrow y_{PI} = [3 \sin 2x - 4x \cos 2x - 2x^2 \sin 2x] e^{2x}$$

$$y = y_{CM} + y_{PI}$$

$$(ii) \quad y = (A+Bx)e^{2x} + e^{2x} (3 \sin 2x - 4x \cos 2x - 2x^2 \sin 2x)$$

Given: ~~for~~ $3x = \cos x + 1$

$$\Rightarrow \cos x + 1 - 3x = f(x)$$

$$\Rightarrow f'(x) = -\sin x - 3$$

Let, initial assumption, $x_0 = 0$

$$x_1 = 0 - \frac{f(x_0)}{f'(x_0)} = x_0 - \frac{f(x_0)}{f'(x_0)}$$

$$\Rightarrow x_1 = 0 + \frac{2}{3} \Rightarrow x_1 = \frac{2}{3}$$

$$x_2 = x_1 - \frac{f(x_1)}{f'(x_1)} = 0.607493$$

$$x_3 = x_2 - \frac{f(x_2)}{f'(x_2)} = 0.607101$$

$$x_4 = x_3 - \frac{f(x_3)}{f'(x_3)} = 0.607101$$

Hence, the root of the given equation is

$$x = 0.607101$$

⑥ (i) Given: $f(x) = \begin{cases} Kx; & 0 \leq x \leq 2 \\ 2K; & 2 \leq x < 4 \\ -Kx + 6K; & 4 \leq x < 6 \end{cases}$

$$\int_{-\infty}^{\infty} f(x) dx = 1 \Rightarrow \int_0^2 Kx dx + \int_2^4 2K dx + \int_4^6 (-Kx + 6K) dx = 1$$

$$\Rightarrow 2K + 2K[2] + K + 2K = 1$$

$$\Rightarrow 8K = 1 \Rightarrow K = \frac{1}{8}$$

Mean of $f(x)$, $\bar{x} = \int_0^6 x f(x) dx$

$$f(x) = \int_0^2 \frac{x^2}{8} dx + \int_2^4 \frac{2}{8} x dx + \int_4^6 \frac{1}{8} (6-x) x dx$$

$$\therefore f(x) = \frac{1}{8} \left[\int_0^2 x^2 dx + 2 \int_2^4 x dx + \int_4^6 (6x - x^2) dx \right]$$


$$f(x) = \frac{1}{8} \left[\frac{8}{3} + 12 + \frac{28}{3} \right] \Rightarrow \boxed{f(5) = 3}$$

(ii) probability of having 0 child in a family, $p_0 = 0.2$

probability of having 1 child in a family, $p_1 = 0.3$

probability of having 2 children in a family, $p_2 = 0.5$

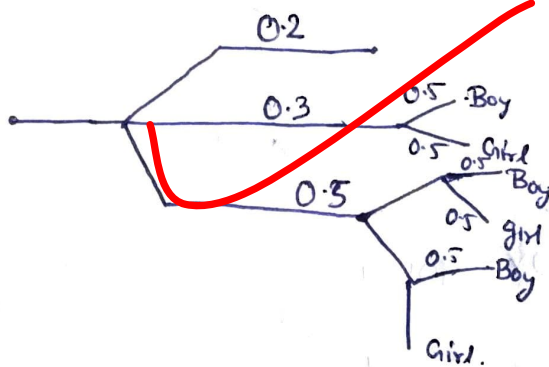probability of being boy or girl, $p = 0.5$



probability of having no boy, $p_{nb} = p_0 + p_1 \times 0.5 + p_2 \times 2 \times \left(\frac{1}{2}\right)^2$


$$p_{nb} = 0.2 + 0.5 \times 0.3 + 0.5 \times \frac{1}{4}$$

$$\boxed{p_{nb} = 0.475}$$

③ ④ Given: $V_s = 240 \sqrt{2} \sin(120\pi t)$

Resistance, $R = 8 \Omega$

Inductance, $L \rightarrow \infty$

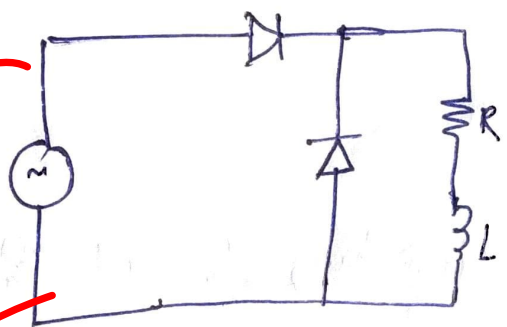

Average Output Voltage,

$$\boxed{V_0 = \frac{1}{2\pi} \int_0^{2\pi} V_s \sin(\omega t) d(\omega t)}$$

$$V_0 = \frac{240\sqrt{2}}{2\pi} [-\cos \omega t]_0^\pi$$

$$V_0 = \frac{240\sqrt{2}}{2\pi} \times 2 \Rightarrow V_0 = 108.038 \text{ V}$$

$$I_0 = \frac{V_0}{R} \Rightarrow I_0 = 13.504745 \text{ A}$$

Power absorbed by source,

$$P_0 = V_0 I_0$$

$$P_0 = 108.038 \times 13.504745$$





$$\Rightarrow P_0 = 1459.02564 \text{ W}$$

power factor,

$$\cos \phi = \frac{P_0}{V_0 I_0}$$

$$= \frac{1459.02564}{108.038 \times 13.504745}$$
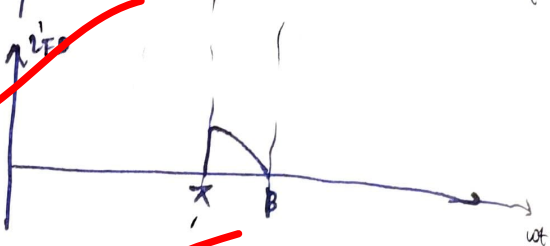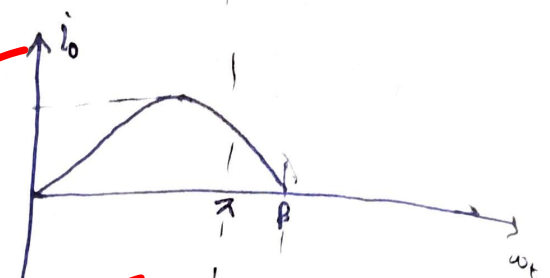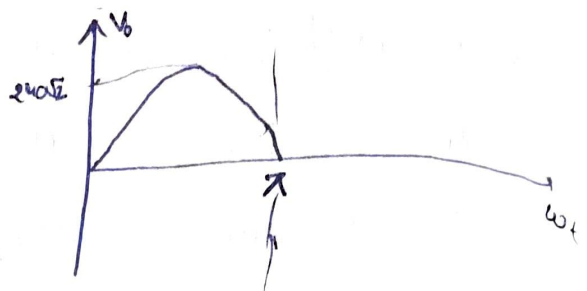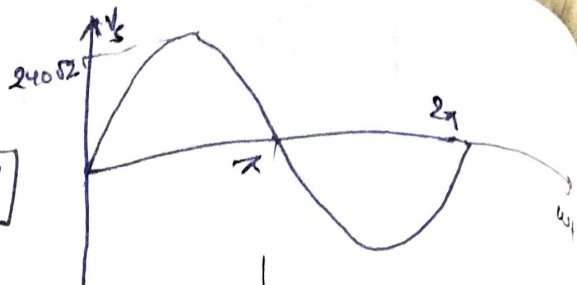
$$\cos \phi = 0.63662 \text{ (lagging)}$$



10

(iii) Considering for 2nd harmonic component only,

$$V = V_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$$

$$q_2 = \frac{2}{\pi} \int_0^\pi 240\sqrt{2} \sin \omega t \cos 2\omega t d(\omega t)$$

~~2nd harmonic content~~

$$a_2 = -144.0506$$

(Considering only for

2nd harmonic content)

$$b_2 = \frac{2}{\pi} \int_0^{\pi} 240 \sin \omega t \sin(2\omega t) d(\omega t)$$

$$b_2 = 0$$

$$|I_2| = \frac{-144.0506}{\sqrt{8^2 + (240\pi \times L)^2}} \times 82006 \text{ mA}$$

$$|I_2| = \frac{144.0506}{\sqrt{64 + (240\pi \times L)^2}} \leq 0.1 \times 13.504745$$

$$106.666^2 \leq 64 + (240\pi \times L)^2$$

$$L \geq 0.1410726 \text{ H}$$

50 for region 1
Electric field, $\vec{E}_1 = 5 \text{ V/m}$

$$\text{polarization, } \vec{P}_1 = 20 \text{ pC/m}^2$$

$$\text{polarization of region 2, } \vec{P}_2 = 50 \text{ pC/m}^2$$

$$\text{thickness, } t = 4 \text{ cm}$$

$$\vec{P}_1 = \frac{\vec{P}_1}{\vec{E}_1 t} \Rightarrow \frac{E_0 \epsilon_r}{t} = \frac{20 \times 10^{-12}}{5 \times t}$$

$$\Rightarrow 8.854 \times 10^{-12} \epsilon_r = 4 \times 10^{-12}$$

$$\text{Polarization, } \vec{P}_1 = \epsilon_0 (\epsilon_r - 1) \vec{E}_1 \Rightarrow 20 \times 10^{-12} = 8.854 (\epsilon_r - 1) \times 5$$

$$\epsilon_r = 1.451793$$

ϵ_r is relative permeability of region 1.

$$\vec{P}_2 = \epsilon_0 (\epsilon_r - 1) \vec{E}_1$$

where ϵ_r is relative permittivity of region 2.

$$\Rightarrow 50 \times 10^{-12} = 8.854 \times 10^{-12} \times 5 \times (\epsilon_r - 1)$$

$$\Rightarrow \epsilon_r = 2.9294$$

⑥ Registers → These are the memory elements present inside the CPU for its internal operation and for arithmetic and logic operation.

- They have the least latency time as compared to all other memories (main memory, secondary memory etc).
- Some of the registers present are general purpose register, accumulator, memory buffer register etc.

function of registers

① Accumulator is mainly used in arithmetic and logic operation. It behaves as primary data and also after evaluation the output is stored at the accumulator. Example → ADD C, SUB B etc.

② Memory register → These registers directly point to the memory location or it stores the memory address. Ex → CMP M. CM means data at memory.

③ General purpose register → These are generally used to hold secondary data and can be used as counters.

Purpose of Memory buffer register

- ① There are two buffer registers, MAR (Memory Address Register) and MBR (Memory Buffer Register).
- ② MAR is a 16 bit register used to hold the ~~data~~ memory address before it is placed on address lines.
- ③ MBR is a 8 bit register used to hold the data ^{before} ~~what~~ it is placed on the data lines or before it is retrieved by the ^{internal} ~~instruction~~ register of CPU.

③ Given $\rightarrow$ Double order pole at $s = -a$
Zero at, $s = -b$

$$b - a = B$$
$$h(\infty) = 2.$$

$$H(s) = K \frac{(s+a)^2}{(s+b)^2} \Rightarrow H(s) = K \left[\frac{A}{(s+b)} + \frac{C}{(s+b)^2} \right]$$

$$K \frac{(s+a)^2}{(s+b)^2} = K \left[\frac{A(s+b) + C}{(s+b)^2} \right]$$

$$As + bA + C = s + a$$

$$\Rightarrow \cancel{As} \quad As = s \Rightarrow \boxed{A=1}$$

$$bA + C = a \Rightarrow C = a - b \Rightarrow C = -B.$$

$$H(s) = K \left[\frac{1}{s+b} - \frac{B}{(s+b)^2} \right]$$

$$h(t) = K [e^{-bt} - B t e^{-bt}] u(t)$$

$$h(0^+) = K \Rightarrow \boxed{K=2}$$

$$h(t) = 2 [e^{-bt} - Bt e^{-bt}] u(t)$$

⑤ ① $R_2 = 400\Omega$ (Given)

$$R_3 = 600\Omega$$

$$R_4 = 1000\Omega$$


$$C_4 = 0.5\mu F$$

frequency, $f = 1000\text{Hz}$

$$Z_4 = R_4 \parallel \left(\frac{1}{j\omega C_4} \right)$$

$$= R_4 \times \frac{1}{j\omega C_4} \div \left(R_4 + \frac{1}{j\omega C_4} \right)$$
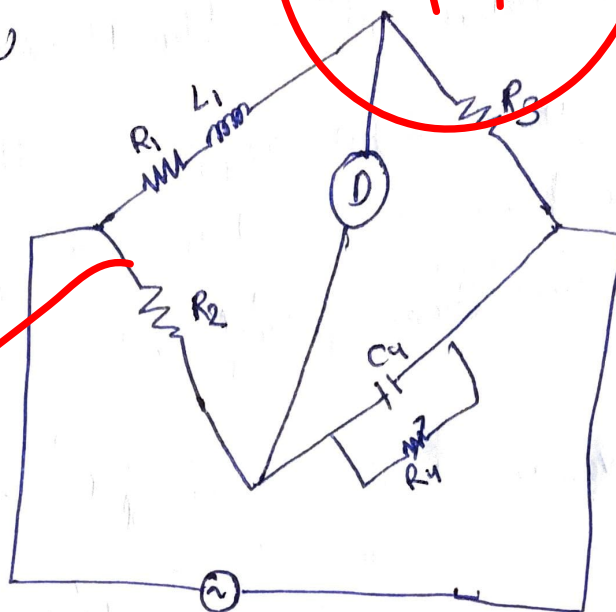
$$\boxed{Z_4 = \frac{R_4}{j\omega R_4 C_4 + 1}}$$



At bridge balance condition: $Z_1 Z_4 = Z_2 Z_3$

$$\Rightarrow [R_1 + j\omega L_1] \frac{R_4}{j\omega R_4 C_4 + 1} = R_2 R_3$$

$$\Rightarrow R_1 R_4 + j\omega L_1 R_4 = R_2 R_3 + R_2 R_3 j\omega R_4 C_4$$

By comparing real and imaginary parts

$$R_1 R_4 = R_2 R_3 \Rightarrow \boxed{R_1 = R_2 \frac{R_3}{R_4}}$$

$$\Rightarrow R_1 = 400 \times \frac{600}{1000} \Rightarrow \boxed{R_1 = 240\Omega}$$

And, $R_2 R_3 j\omega R_4 C_4 = j\omega L_1 R_4$

$$L_1 = R_2 R_3 C_4$$

$$\Rightarrow L_1 = 0.12 \text{ H}$$

Quality factor of coil, $Q = \frac{\omega_0 L}{R} \Rightarrow \omega_0 = 2\pi f$

$$Q = \pi \Rightarrow Q = 3.1416$$

Advantages

- ① The value of L_1 and R_1 in the expression are frequency independent.
- ② It can be used to find inductance of coils at wide range of audio frequency.

Disadvantages

- ① The Variable Capacitor increases the cost of the bridge.
- ② It can be used for coils having quality factor,
$$1 \leq Q \leq 10$$

⑤ ⑥ Given: $x_c(t) = 10 \cos[2\pi \times 10^6 t + 0.1 \sin(10^3 \pi t)]$

$$K_p = 10 \text{ rad/V}$$

$$K_f = 10\pi \text{ rad/s-volt}$$

$$\theta_i = 2\pi \times 10^6 t + 0.1 \sin(10^3 \pi t) = \text{instantaneous angle}$$
$$\frac{d\theta_i}{dt} = \Delta\omega_i = 2\pi \times 10^6 + 0.1 \times 10^3 \pi \cos(10^3 \pi t)$$

ω_i is instantaneous frequency. divides

Maximum frequency deviation, $\Delta f|_{\max} = (10^6 + 50) \text{ Hz}$

for FM signal

$$x_c(t) = 10 \cos[2\pi \times 10^6 t + K_f \int m(t) dt]$$

$m(t)$ is message signal

$$K_f \int m(t) dt = 0.1 \sin(10^3 \pi t)$$

$$\Rightarrow \int m(t) dt = \frac{0.1}{10\pi} \sin 10^3 \pi t$$

$$\Rightarrow m(t) = \frac{0.1}{10\pi} \frac{d \sin(10^3 \pi t)}{dt} = \frac{0.1}{10\pi} \times 10^3 \pi \cos 10^3 \pi t$$

$$\Rightarrow \boxed{m(t) = 10 \cos(10^3 \pi t) \text{ V}}$$

frequency deviation, $\Delta f = \frac{K_f A_m}{2\pi} \Rightarrow \boxed{\Delta f = 50 \text{ kHz}}$

for PM signal

$$x_c(t) = 10 \cos[2\pi \times 10^6 t + K_p m(t)]$$

$$K_p m(t) = 0.1 \sin(10^3 \pi t)$$

$$\boxed{m(t) = 10^{-2} \sin(10^3 \pi t)}$$

So,

frequency deviation,

$$\Delta \omega = K_p A_m \omega_m$$

$$\Rightarrow \boxed{\Delta f = K_p A_m f_m}$$

$$\Rightarrow \Delta f = 10 \times 10^{-2} \times \frac{10^3 \pi}{2\pi}$$

$$\boxed{\Delta f = 50 \text{ kHz}}$$

7) ① Program development cycle → It is used for developing a program for real life problem or application. It consist of various steps which result in the development of program.

It is a set standard of how to proceed for developing a program for given real life problem.

Steps involved in developing a program

① Retriving input data → The data that has to be taken by the user as input should be retrived or gathered from the user in a proper format


② Logic development → Developing the proper logic for the ~~execution of~~ execution of the program for its proper functioning.

③ Initialization ~~Initiation~~ → ~~It is used for~~ The variables used in the program should be initialized with their type and value (if applicable).

④ Execution → The program should be written in proper format so, that program runs as per the logic formed.

⑤ Output generation and display → Output should be displayed in a manner, so, that it is easily understandable by the user.

(ii) flow chart ~~code~~

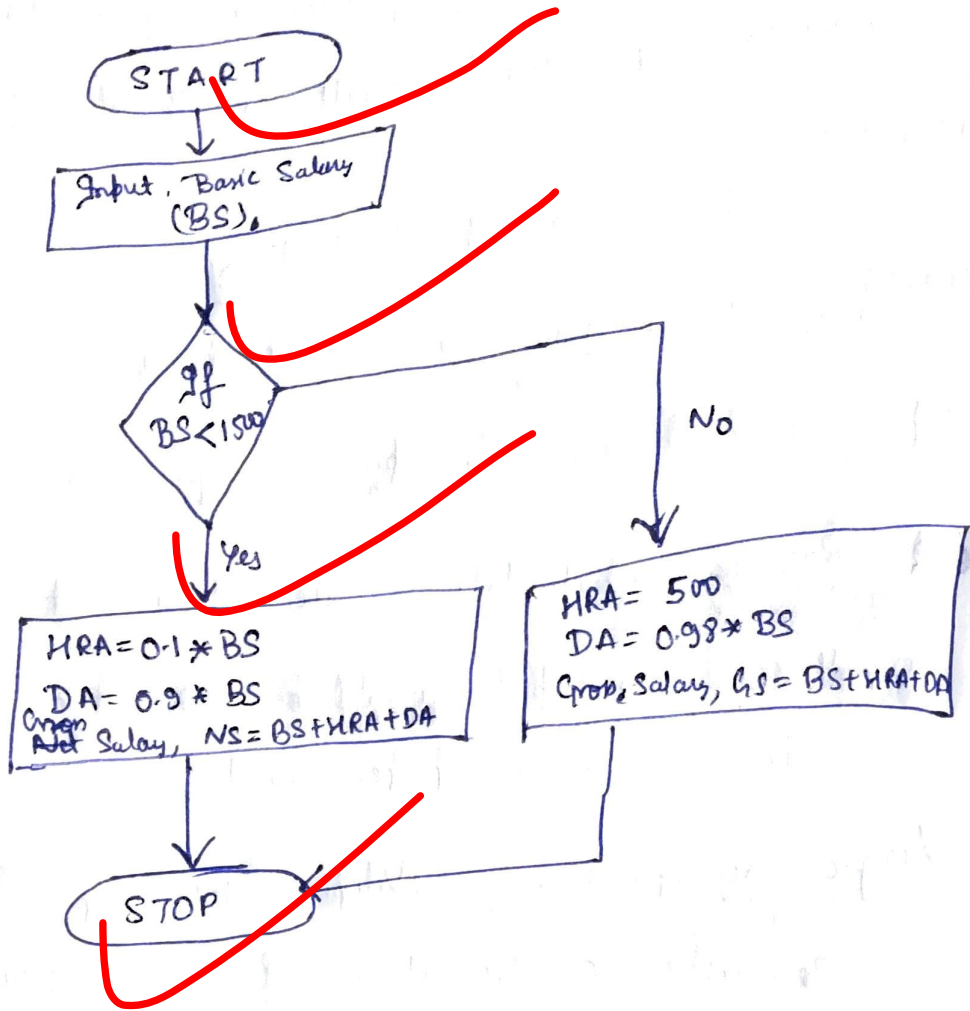

C-Program

```
#include <stdio.h>
#include <conio.h>

Void main ( )
{
    float int HRA, DA, NS;
    int BS;
    printf ("Enter the basic Salary");
    scanf ("%d", &BS);

    if ( BS < 1500 )
    {
        HRA = 0.1 * BS;
        DA = 0.9 * BS;
        NS = BS + HRA + DA;
    }
    else
    {
        HRA = 500
        DA = 0.98 * BS;
```


$$NS = BS + HRA + DA$$

7

printf("added Gross salary %d", &NS)

}

$$\textcircled{7} \textcircled{b} \quad X(k) = \sum_{n=0}^{N-1} x(n) e^{-j \frac{2\pi}{N} n k}$$

$$x(n) = \frac{1}{N} \sum_{k=0}^{N-1} X(k) e^{+j \frac{2\pi}{N} k n}$$

$$\Rightarrow x_1(n) = \frac{1}{N} \sum_{k=0}^{N-1} X_1(k) e^{+j \frac{2\pi}{N} k n}$$

$$x_2(n) = \frac{1}{N} \sum_{k=0}^{N-1} X_2(k) e^{+j \frac{2\pi}{N} k n}$$

$$\Rightarrow x_1(n) \cdot x_2(n) = \frac{1}{N^2} \left(\sum_{k=0}^{N-1} X_1(k) e^{+j \frac{2\pi}{N} k n} \right) \left(\sum_{k=0}^{N-1} X_2(k) e^{+j \frac{2\pi}{N} k n} \right)$$

~~from~~ we know that -

$$x_1(n) * x_2(n) = X_1(k) X_2(k)$$

By using duality property

$$\frac{1}{N} [X_1(k) * X_2(-k)] = x_1(n) x_2(n)$$

As, it is a circular convolution, $X_1(-k) = X_1(k)$
 $X_2(-k) = X_2(k)$

$$\Rightarrow x_1(k) x_2(k) = \frac{1}{N} [X_1(k) * X_2(k)] \quad (\text{By interchanging variables})$$

$$\Rightarrow x(n) = \frac{1}{N} [X_1(k) * X_2(k)]$$

⑦ ③ To prove!

$$\sum_{n=0}^{N-1} x_1(n) x_2^*(n) = \frac{1}{N} \sum_{k=0}^{N-1} X_1(k) X_2^*(k)$$

$$x(n) \equiv \sum_{k=0}^{N-1} x(k) \delta(n-k)$$

$$x_1(n) x_2(n) = \frac{1}{N} [X_1(k) * X_2(k)]$$


$$x_2^*(n) \xrightarrow{\text{DFT}} X_2^*(e^{j2\pi k/N}) \quad i \text{ is any arbitrary index}$$

$$x_1(n) x_2^*(n) = \frac{1}{N} [X_1(k) * X_2^*(e^{j2\pi k/N})]$$

$$= \frac{1}{N} X_1(k) * X_2^*(e^{j2\pi k/N})$$

$$\Rightarrow \sum_{n=0}^{N-1} x_1(n) x_2^*(n) = \frac{1}{N} \sum_{k=0}^{N-1} X_1(k) * X_2^*(e^{j2\pi k/N})$$
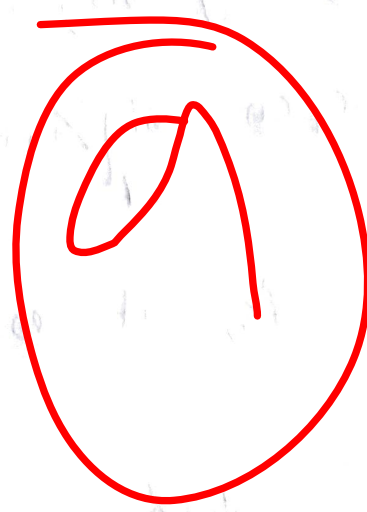
$$\Rightarrow \sum_{n=0}^{N-1} x_1(n) x_2^*(n) = \frac{1}{N} \sum_{k=0}^{N-1} X_1(k) X_2^*(k)$$



7) (i) ~~Resistance~~ Resistance, $R = \frac{\rho L}{A}$

Area, $A = \frac{\pi D^2}{4}$

$$\frac{\partial A}{\partial D} = \frac{2\pi D}{4} = \frac{\pi D}{2}$$

$$\ln R = \ln \left(\frac{\rho L}{A} \right)$$

$$\Rightarrow \ln R = \ln(\rho) + \ln(L) - \ln(A)$$

$$\Rightarrow \frac{\partial R}{R} = \frac{\partial \rho}{\rho} + \frac{1}{L} \partial L - \frac{1}{A} \frac{\partial A}{\partial D} \partial D$$

$$\Rightarrow \frac{\partial R}{R} = \frac{\partial \rho}{\rho} + \frac{1}{L} \partial L - \frac{4}{\pi D^2} \times \frac{\pi D}{2} \partial D$$

$$\Rightarrow \frac{\partial R}{R} = \frac{\partial \rho}{\rho} + \frac{1}{L} \partial L - \frac{2}{D} \partial D$$

$$\Rightarrow \frac{\Delta R}{R} = \frac{\Delta \rho}{\rho} + \frac{\Delta L}{L} - \frac{2 \Delta D}{D}$$

$$\Rightarrow \frac{\frac{\Delta R}{R}}{\frac{\Delta L}{\Delta L}} = 1 + \frac{\frac{\Delta \rho}{\rho}}{\frac{\Delta L}{\Delta L}} - 2 \frac{\frac{\Delta D}{D}}{\frac{\Delta L}{\Delta L}}$$

Let $\boxed{\frac{\Delta L}{L} = \epsilon \text{ (Strain)}}$

$$\Rightarrow \frac{\frac{\Delta R}{R}}{\frac{\Delta L}{L}} = 1 + \frac{\Delta \rho}{\epsilon \rho} + 2 \left(-\frac{\frac{\Delta D}{D}}{\frac{\Delta L}{L}} \right)$$

$$\boxed{Y = -\frac{\frac{\Delta \rho}{\rho}}{\frac{\Delta L}{L}} = \text{Poisson's ratio}}$$

$$2 \frac{\frac{\Delta R}{R}}{\frac{\Delta L}{L}} = \text{Gauge factor (Gf)}$$

$$\Rightarrow Gf = 1 + 2\nu + \frac{\Delta P}{\epsilon P}$$

(ii) Given: Nominal resistance, $R_f = 500 \Omega$

Gauge factor, $Gf = 4$

Other resistances, $R_2, R_3, R_4 = 500 \Omega$

Strain, $\epsilon = 100 \times 10^{-6} \text{ m/m} = 10^{-4} \text{ m/m}$

$$Gf = \frac{\frac{\Delta R_1}{R_1}}{\epsilon}$$

ΔR_1 is change in resistance.

$$4 = \frac{\frac{\Delta R_1}{500}}{10^{-4}} \Rightarrow 4 \times 10^{-4} \times 500 = \Delta R_1$$

$$\Delta R_1 = 0.2 \Omega$$


Supply voltage, $V = 5 \text{ V}$ (Given)

$$V_b = V \times \frac{R_2}{R_1 + \Delta R_1 + R_2}$$

(By voltage division rule)

$$V_b = 5 \times \frac{500}{100.2}$$

$$V_b = 2.495001 \text{ V}$$

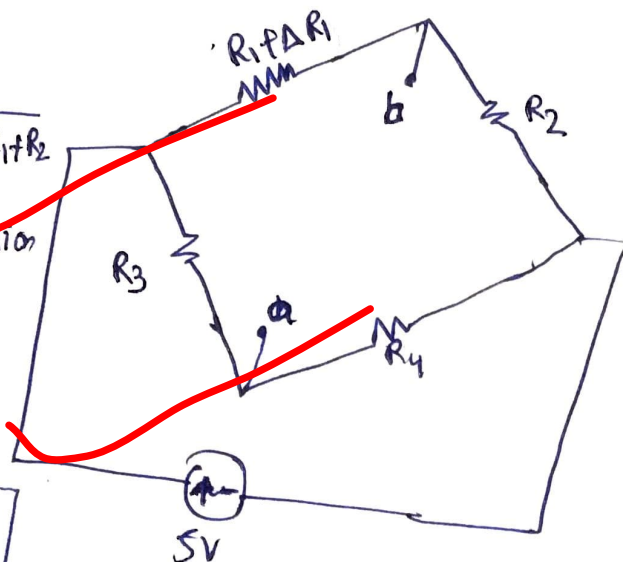

$$V_a = V \times \frac{R_4}{R_3 + R_4} \quad (\text{By using Voltage divider rule})$$

$$\Rightarrow V_a = 5 \times \frac{500}{1000} \Rightarrow \boxed{V_a = 2.5 \text{ V}}$$

So, $V_{ab} = V_a - V_b$

$$\boxed{V_{ab} = 0.4999 \text{ mV}}$$

If the voltmeter is connected across ab, we get,

Output voltage, $\boxed{V_{ab} = V_b = 0.4999 \text{ mV}}$

