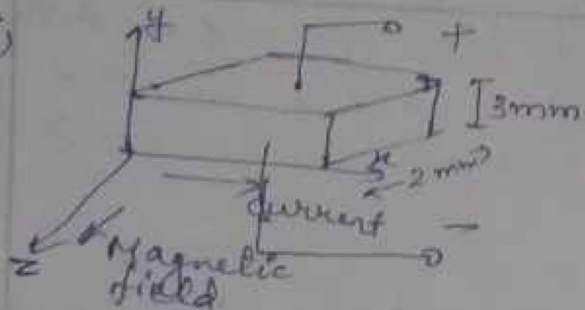


NAME :
 ROLL NUMBER :
 TEST NO : 14
 SUBJECT :

1(a)(i)



Force is applied on the electron moving inside the specimen.

This specimen The majority carriers experience a force due to transverse magnetic field present.

This force is $f = q v_x \times B_z$
 This force is acting in downward direction.

As a result majority carriers electrons accumulate on lower surface, to counterbalance this a force applied in upward direction so that charge carriers attain equilibrium.

$$f_y = q v_x B_z$$

this f_y is due to hall voltage developed

$$f_y = q \cdot E_y$$

$$q E_y = q v_x B_z \Rightarrow E_y = v_x B_z$$

$$\text{Hall voltage } V_H = \frac{E_y}{d}$$

$$\text{Current density } J_x = n e v_x = \sigma E_x$$

$$v_x = \frac{\sigma E_x}{n e} = \frac{n e \mu_n E_x}{n e} = \mu_n E_x$$

$$E_y = \mu_n E_x B_z$$

$$V_H = \frac{\mu_n E_x B_z}{d}$$

6



$$V_H = 3500 \times \frac{6}{10^2} \times \frac{0.3 \times 0.1}{3 \times 10^{-3}} \times 10^{-4}$$

$$V_H = 21 \text{ KV.}$$

(ii) If p-type bar ~~used~~ force still acts in downward direction, as a result ~~positive~~ ~~sigma~~ lower surface becomes positive w.r.t top surface as a result ~~no~~ polarity of Hall voltage reverses.

1(b) Initially assume both diodes to be off.

$$V_{P1} = V_i \quad V_{P2} = 75$$

$$V_{N1} = 25V \quad V_{N2} = 25V$$

So D_2 can be assumed to be ON first.

As a result D_2 short circuit.

$$V_o(t) = \frac{25 \times 5 + 75 \times 5}{25 + 25} = 50V$$

when $V_i > 50V$, D_1 becomes ON. and D_2 already ON so $V_o = V_i$

for $V_i < 50V$, D_1 off & D_2 ON so $V_o = 50V$.

Consider case when D_1 ON & D_2 off. Output cut off from input & $V_o = 75V$. We need to check if this happens.



when D_2 cut off. $V_{N2} = 75V$.

$$V_{P2} = V_i$$

So when $V_i > 75V$, D_2 cut off and $V_o = 75V$.

$$V_o = \begin{cases} 50 & V_i < 50 \\ V_i & 50 < V_i < 75 \\ 75 & V_i > 75 \end{cases}$$


Transfer characteristic

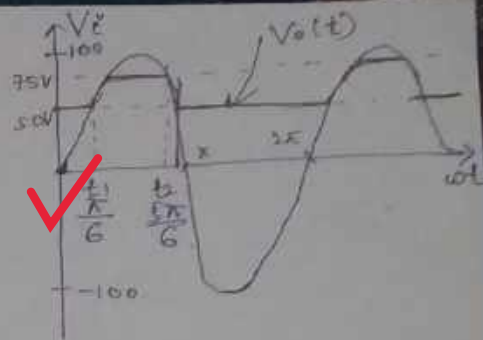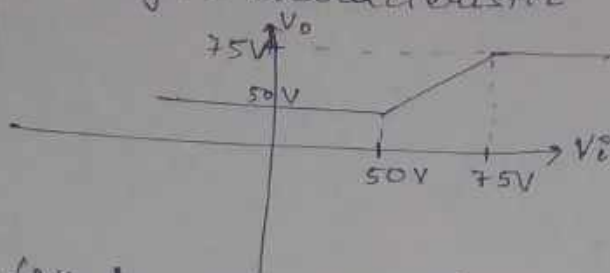

for t_1 , $50 = 100 \sin(\omega t_1)$
 $\omega t_1 = \pi/6$
 $\omega t_2 = \pi - \pi/6 = \frac{5\pi}{6}$

12

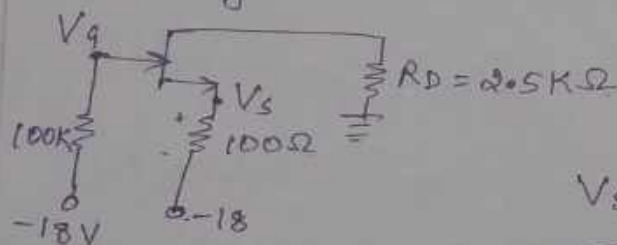1 (c) For voltage gain we need g_m , for this DC analysis has to be done



$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$V_{G1} = -18V$$

$$V_S - I_D \times 100 + 18 = 0$$

$$100 I_D = V_S + 18$$

$$\Rightarrow V_{GS} = -100 I_D \Rightarrow I_D = \frac{-V_{GS}}{100}$$

$$\frac{-V_{GS}}{100} = 8 \times 10^{-3} \left(1 - \frac{V_{GS}}{-3}\right)^2$$

$$-V_{GS} = 0.8 \left(1 + \frac{V_{GS}^2}{9} + 2 \frac{V_{GS}}{3}\right)$$

$$\frac{-9 V_{GS}}{0.8} = 9 + V_{GS}^2 + 6 V_{GS}$$

$$V_{GS}^2 + 17.25 V_{GS} + 9 = 0$$

$$V_{GS} = -0.66 \quad V_{GS} = -13.56$$

as $V_{GS} < V_P$ desired hence $V_{GS} = -0.66$

$$I_D = -\left(\frac{-0.66}{100}\right) = 6.6 \text{ mA}$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{2 I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right) = 2 I_{DSS} \sqrt{\frac{I_D}{I_{SS}}}$$


$$g_m = \frac{2 \sqrt{I_D I_{DSS}}}{V_P}$$

$$g_m = \frac{2}{1.31} \cdot \sqrt{6.6 \times 8} = 4.844 \text{ mS}$$

Now for AC analysis.



Replacing by equivalent π model.

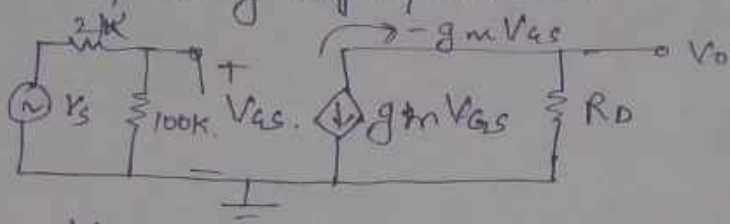

12


$$V_{gs} = \frac{V_s \times 100k}{100k + 2k} = \frac{V_s \times 100k}{102k} = 0.98 V_s$$

$$V_o = -g_m V_{gs} R_D = -g_m \times 0.98 V_s R_D$$

$$\frac{V_o}{V_s} = -g_m \times 0.98 \times R_D = -4.844 \times 0.98 \times 2.5$$

$$\boxed{\frac{V_o}{V_s} = -11.87}$$

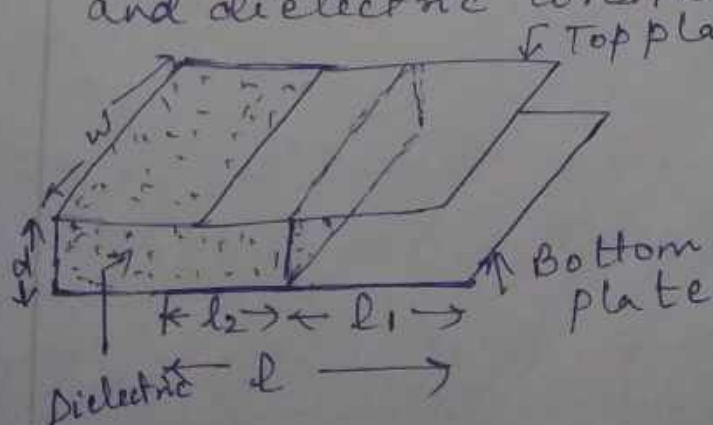1(d) For the measurement of displacement through capacitive transducer we can either change overlap area, plate separation, and dielectric constant.



The plates of the capacitor are fixed. However a moving object having dielectric constant ϵ_r is moving into the plate. We are willing to measure displacement of object

At any intermediate stage, let l_2 length of object is inside the plates. Therefore, upto l_2 length, the capacitor filled with dielectric having dielectric constant ϵ_r whereas for l_1 length we have air. Capacitance of combination can be found as

$$C = C_1 + C_2$$

$$C = \frac{\epsilon_0 w l_1}{d} + \frac{\epsilon_0 w l_2 \epsilon_r}{d}$$

$$C = \frac{\epsilon_0 w}{d} (l_1 + \epsilon_r l_2)$$


As object moves into capacitor, the value of l_2 increases and capacitance C also increases. By measuring this capacitance, linear displacement can also be measured.

Let full length is l & penetration be x .

$$C = \frac{\epsilon_0 w}{d} [(l-x) + \epsilon_r x]$$

$$\frac{\partial C}{\partial x} = \frac{\epsilon_0 w}{d} [-1 + \epsilon_r] = \frac{\epsilon_0 w}{d} (\epsilon_r - 1)$$

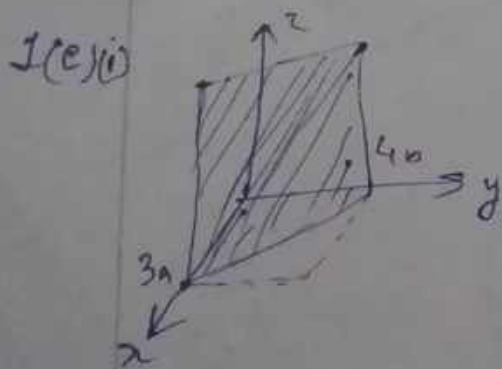Hence can be used to measure linear displacements.



x	y	z	
3a	4b	∞	- intercept
3	4	∞	- simple ratios
$\frac{1}{3}$	$\frac{1}{4}$	0	- Reciprocal.
4	3	0	- Ratios.

Miller indices $(4 \ 3 \ 0)$

(ii) from Bragg's law we have

$$n\lambda = 2d \sin \theta$$

for 1st order reflection $n=1$

$$1 \times 0.175 = 2d \times \sin 30$$

$$0.175 = 2 \times d \times \frac{1}{2} \Rightarrow d = 0.175 \text{ nm}$$

This d is interplanar separation between two planes having miller indices (h, k, l)

$$d = \frac{a}{\sqrt{h^2 + k^2 + l^2}} \quad ; \text{ here } a \text{ is interatomic separation \& } h, k, l \text{ are miller indices.}$$

$$0.175 = \frac{a}{\sqrt{1^2 + 1^2 + 1^2}} \Rightarrow a = 0.175 \times \sqrt{3} \text{ nm}$$

$$\boxed{a = 0.303 \text{ nm}}$$

4(a) Atomic polarisability is given as

$$P = \alpha E. \Rightarrow \alpha = \frac{P}{E}$$

here P is atomic dipole moment.

let us first move towards finding electric field E .

As from gauss law. $\oint \vec{D} \cdot d\vec{s} = Q_{enc}$

We are given the charge density

$$Q = \int_V \rho(r) dV = \int_V \frac{q}{4\pi a^3} e^{-2r/a} dV$$

$$= \int \int \int \frac{q}{4\pi a^3} e^{-2r/a} r^2 \sin \theta d\theta d\phi dr$$
$$= \frac{q}{4\pi a^3} \int_0^r r^2 e^{-2r/a} dr \int_0^\pi \sin \theta d\theta \int_0^{2\pi} d\phi$$

$$= \frac{q}{4\pi a^3} \times 2\pi \times 2 \int_0^r r^2 e^{-2r/a} dr$$

$$\begin{aligned}
 Q &= \frac{q}{4\pi a^3} \times 4\pi \left[\frac{r^2 e^{-2r/a}}{-2/a} + \frac{a}{2} \int 2r e^{-2r/a} dr \right] \quad (4) \\
 &= \frac{q}{a^3} \left[\frac{-ar^2}{2} e^{-2r/a} + a \left[\frac{r e^{-2r/a}}{-2/a} + \frac{a}{2} \frac{e^{-2r/a}}{-2/a} \right] \right] \\
 &= \frac{q}{a^3} \cdot \left[\frac{-ar^2}{2} e^{-2r/a} + \frac{-a^2}{2} r e^{-2r/a} + \frac{-a^3}{4} e^{-2r/a} \right]_0^r \\
 &= \frac{q}{a^3} \left[\frac{a^3}{4} - \frac{a}{4} (2r^2 - 2ar + a^2) e^{-2r/a} \right]
 \end{aligned}$$

$$Q = \frac{q}{a^3} \left[1 - \frac{e^{-2r/a}}{4} (2r^2 - 2ar + a^2) \right]$$

$$e^{-2r/a} = 1 - \frac{2r}{a} + \frac{1}{2} \left(\frac{2r}{a} \right)^2 - \frac{1}{6} \left(\frac{2r}{a} \right)^3 + \dots$$

$$Q = q \left[1 - \left(1 - \frac{2r}{a} + \frac{1}{2} \left(\frac{2r}{a} \right)^2 - \frac{1}{6} \left(\frac{2r}{a} \right)^3 + \dots \right) \left(\frac{2r^2}{a^2} - \frac{2r}{a} + 1 \right) \right]$$

$$\oint D \cdot ds = Q \Rightarrow D \cdot 4\pi r^2 = Q$$

$$D = \frac{Q}{4\pi r^2}$$

15

$$D = \epsilon E \Rightarrow E = \frac{Q}{4\pi \epsilon r^2}$$

$$E = \frac{q}{4\pi \epsilon r^2} \left[1 - \left(1 - \left(\frac{2r}{a} \right) + \frac{1}{2} \left(\frac{2r}{a} \right)^2 - \frac{1}{6} \left(\frac{2r}{a} \right)^3 + \dots \right) \left(\frac{2r^2}{a^2} - \frac{2r}{a} + 1 \right) \right]$$


$$= \frac{q}{4\pi \epsilon r^2} \cdot \frac{4}{3} \left(\frac{r}{a} \right)^3 \quad \left[\text{neglecting higher terms as } r \gg a \right]$$

$$= \frac{q}{4\pi \epsilon} \cdot \frac{4}{3} \frac{r}{a^3} = \frac{qr}{3\pi \epsilon a^3}$$


$qr = p$ = atomic polarisation

$$E = \frac{p}{3\pi \epsilon a^3} \Rightarrow \boxed{\frac{p}{E} = 3\pi \epsilon a^3 = \alpha}$$

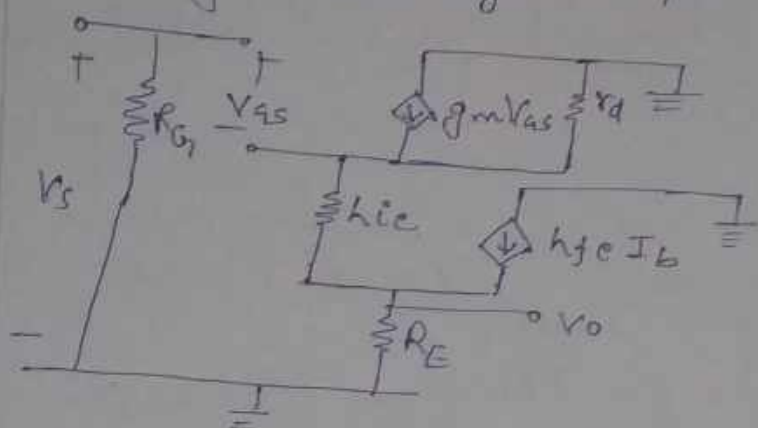4(b) Drawing small signal equivalent circuit. (5)



Simplifying the arrangement.

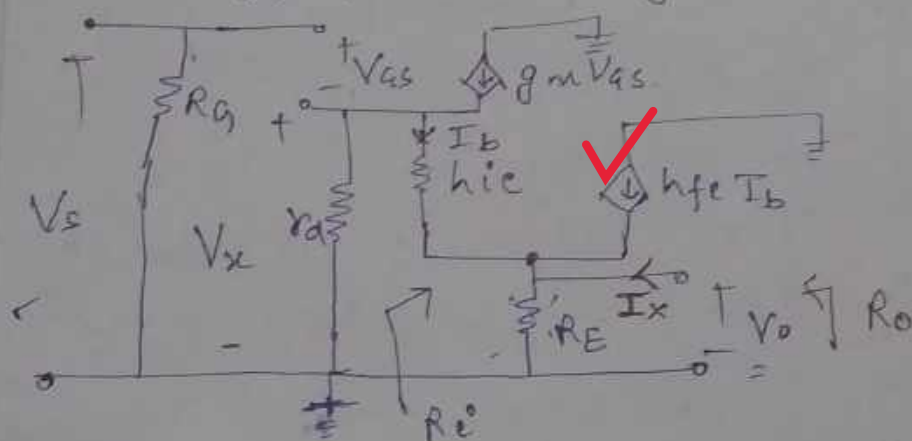

$$V_i = h_{ie} I_b + R_E (1 + h_{fe}) I_b$$

$$R_i^o = \frac{V_i}{I_b} = h_{ie} + (1 + h_{fe}) R_E \quad \text{--- (1)}$$

$g_m V_{as}$ divided b/w r_d & R_i^o as they appear in parallel.

$$V_s = V_{as} + V_x = V_{as} + g_m V_{as} (r_d || R_i^o) \quad \text{--- (2)}$$

$$V_o = I_b (1 + h_{fe}) R_E \quad \text{--- (3)}$$

$$I_b = g_m V_{as} \frac{r_d}{r_d + R_i^o} \quad \text{--- (4)}$$

$$(4) \text{ in } (3) \quad V_o = g_m V_{as} \frac{r_d (1 + h_{fe}) R_E}{r_d + R_i^o} \quad \text{--- (5)}$$

from (2)

$$V_s = V_{as} + g_m V_{as} \frac{r_d R_i}{r_d + R_i}$$

$$V_s = V_{as} (r_d + R_i) + g_m V_{as} r_d R_i \quad \text{--- (6)}$$

(5) $\div$ (6)

$$\frac{V_o}{V_s} = \frac{g_m V_{as} \frac{r_d (1+h_{fe}) R_E}{r_d + R_i}}{V_{as} (r_d + R_i) + g_m V_{as} r_d R_i}$$

$$\begin{aligned} \frac{V_o}{V_s} &= \frac{g_m r_d (1+h_{fe}) R_E}{(r_d + R_i) + g_m r_d R_i} \\ &= \frac{g_m r_d (1+h_{fe}) R_E}{r_d + h_{ie} + (1+h_{fe}) R_E + g_m r_d (h_{ie} + (1+h_{fe}) R_E)} \end{aligned}$$

$g_m = \frac{\mu}{r_d}$ (as μ and r_d given in question).

$$\boxed{\frac{V_o}{V_s} = \frac{\mu (1+h_{fe}) R_E}{r_d + h_{ie} + (1+h_{fe}) R_E + \mu (h_{ie} + (1+h_{fe}) R_E)}}$$

This is required voltage gain.

For output resistance, V_s removed from eqn (2) $V_{as} + g_m V_{as} (r_d || R_i) = 0$
 $g_m (r_d || R_i) = -1$

KCL at emitter junction

$$\frac{V_o}{R_E} + I_x + (1+h_{fe}) I_b = 0$$

$$V_{as} + V_x = 0$$

$$V_x = I_b h_{ie} + V_o \quad \text{--- (7)}$$

13

$$V_o = [(1+h_{fe})I_b + I_x] R_E \quad (8)$$

(6)

$$V_x = I_b h_{ie} + [(1+h_{fe})I_b + I_x] R_E$$

At source terminal KCL eqn.

$$g_m V_{as} = I_b + \frac{V_x}{r_d}$$

$$g_m (-V_x) = I_b + \frac{V_x}{r_d}$$

$$I_b = -V_x \left(g_m + \frac{1}{r_d} \right) \quad (9)$$

eqn (9) in (7)

$$V_x = -V_x h_{ie} \left(g_m + \frac{1}{r_d} \right) + V_o$$

$$V_x \left[1 + h_{ie} \left(\frac{1}{g_m} \parallel r_d \right) \right] = V_o$$

$$I_x = (1+h_{fe}) I_b$$

$$I_x = (1+h_{fe}) \left(g_m + \frac{1}{r_d} \right) (-V_x)$$

$$I_x = (1+h_{fe}) \left(g_m + \frac{1}{r_d} \right) \frac{V_o}{1 + h_{ie} \left(\frac{1}{g_m} \parallel r_d \right)}$$

$$\frac{V_o}{I_x} = R_o' = \frac{1 + h_{ie} \left(\frac{1}{g_m} \parallel r_d \right)}{(1+h_{fe}) \left(\frac{1}{g_m} \parallel r_d \right)}$$

$$R_o = \frac{1 + h_{ie} \left(\frac{1}{g_m} \parallel r_d \right)}{(1+h_{fe}) \left(\frac{1}{g_m} \parallel r_d \right)} \parallel R_E \approx \frac{h_{ie}}{1+h_{fe}} \parallel R_E$$

4(c) For linearly graded junction charge density given as $\rho_v = q x e \quad -\frac{w}{2} \leq x \leq \frac{w}{2}$

as this is charge consisting region, so we apply Poisson relation.

$$\nabla^2 V = -\frac{\rho_v}{\epsilon} = -\frac{q x e}{\epsilon}$$

Integrating both sides

$$\nabla V = -\frac{q x^2 e}{2 \epsilon} + C$$

This is equation of Electric field
as $E = -\nabla V = 0$ at $x = -w/2$

$$0 = -\frac{ge(-\frac{w}{2})^2}{2\epsilon} + C_1 \Rightarrow C_1 = \frac{gew^2}{8\epsilon}$$

$$\frac{dV}{dx} = -\frac{gex^2}{2\epsilon} + \frac{gew^2}{8\epsilon}$$

Integrating both sides.

$$V = -\frac{gex^3}{6\epsilon} + \frac{gew^2x}{8\epsilon} + C_2$$

$$\text{at } x = 0 ; V = 0 \Rightarrow C_2 = 0$$



$$V = -\frac{gex^3}{6\epsilon} + \frac{gew^2x}{8\epsilon}$$

$$\text{at } x = -w/2 \quad V = V_p.$$

$$V_p = -\frac{ge(-\frac{w}{2})^3}{6\epsilon} + \frac{gew^2(-\frac{w}{2})}{8\epsilon} = -\frac{gew^3}{24\epsilon}$$

$$\text{at } x = w/2 \quad V = V_n. \Rightarrow V_n = \frac{gew^3}{24\epsilon}$$

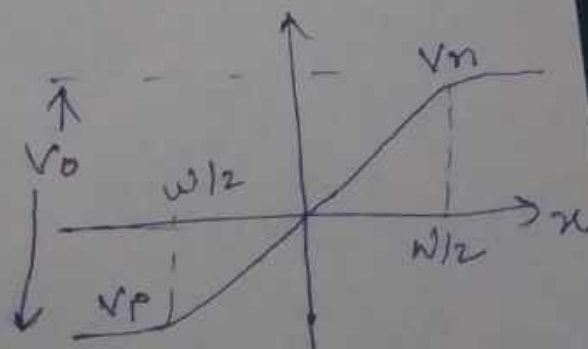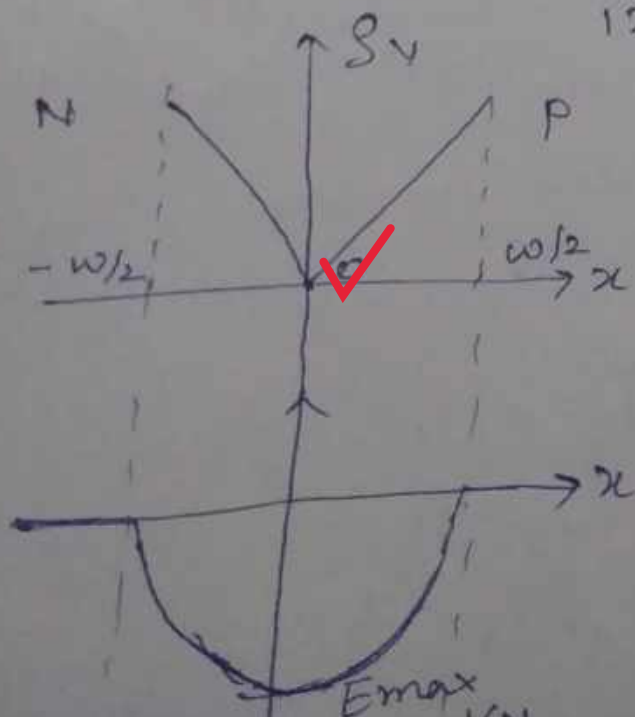
$$V_0 = V_n - V_p = \frac{gew^3}{12\epsilon}$$



15

4(d) $R_m = 20 \Omega$; $I_m = 1 \text{ mA}$

(7)

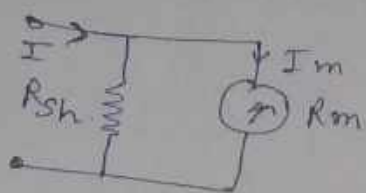


$$\frac{I}{I_m} = m = \frac{100}{1} = 100$$

$$R_{sh} = \frac{R_m}{m-1}$$

$$R_{sh} = \frac{20}{100-1} = 0.202 \Omega$$

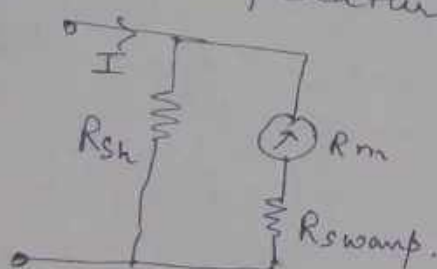Now 75Ω resistance connected in series for temperature compensation



$$R_{sh \text{ new}} = \frac{R_m + R_{swamp}}{m-1}$$

$$= \frac{20 + 75}{100-1} = 0.9596 \Omega$$

for 20°C rise in temp.

$$R_m' = R_m (1 + \alpha T) = 20 (1 + 0.005 \times 20) = 22 \Omega$$

$$R_{swamp}' = 75 (1 + 0.0002 \times 20) = 75.3 \Omega$$

$$R_{\text{meter arm}} = 22 + 75.3 = 97.3 \Omega$$

$$R_{sh \text{ new}} = 0.9596 (1 + 0.0002 \times 20) = 0.9634 \Omega$$

$$I_m = I \times \frac{R_{sh}}{R_{sh} + R_{\text{meter arm}}}$$

$$I_m = I \times \frac{0.9634}{0.9634 + 97.3} = 0.9804 \text{ mA}$$


Error due to temperature rise

$$= MV - TV = 0.9804 - 1 = -0.0196 \text{ mA}$$

$$\% \text{ error} = \frac{-0.0196}{1} \times 100 = -1.96 \%$$

14

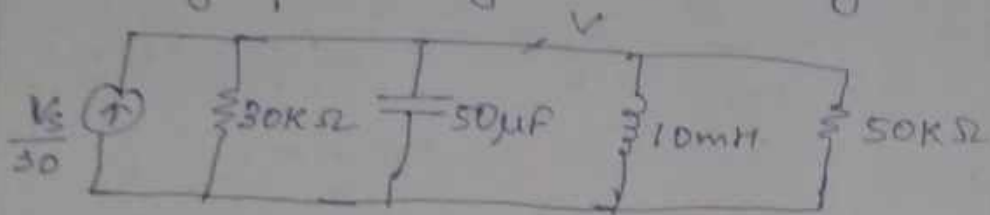5a) changing voltage source by current source



At resonance $\frac{V_s}{30} = \frac{V}{30} + \frac{V}{50} + \frac{V}{j\omega L} + \frac{V}{1/j\omega C}$

$$\frac{V_s}{30} = V \left(\frac{1}{30} + \frac{1}{50} \right) + \frac{V}{j\omega L} + j\omega C V$$

at resonance all current flows through resistor & L & C form OC.

$$\frac{1}{j\omega L} + j\omega C = 0 \Rightarrow 1 + j^2 \omega_0^2 LC = 0$$

$$\omega_0^2 LC = 1 \Rightarrow \boxed{\omega_0 = \frac{1}{\sqrt{LC}}} \Rightarrow f \neq \omega$$

This is required resonant frequency.

Quality factor $Q = \frac{1}{\omega_0 CR}$

3

$$R = 30 // 50 = 18.75 K\Omega$$


~~Q = 1/(\omega_0 CR)~~ $\omega_0 = \frac{1}{\sqrt{10 \times 10^{-3} \times 50 \times 10^{-6}}}$

$$\boxed{\omega_0 = 1.414 \text{ Krad/sec}}$$

$$Q = \frac{1}{1.414 \times 10^3 \times 50 \times 10^{-6} \times 18.75 \times 10^3}$$

$$Q = 7.5436 \times 10^{-4}$$

5(b)
(i)

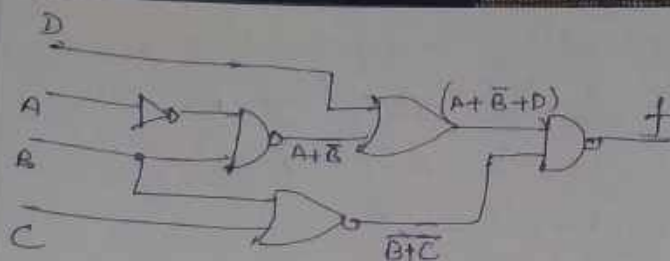

$$\begin{aligned} f &= \overline{(A+B+D) \cdot (B+C)} \\ &= \overline{A+B+D} + \overline{(B+C)} \\ &= \overline{A} \overline{B} \overline{D} + \overline{B} + \overline{C} \\ &= B(\overline{A} \overline{D} + 1) + C = B + C \end{aligned}$$



10

(ii)

$$\begin{aligned} F(P, Q, R) &= P(P' + Q)(P' + Q + R') \\ &= (PP' + PQ)(P' + Q + R') \\ &= PQP' + PQ + PQR' \\ &= PQ + PQR' = PQ(1 + R') = PQ. \end{aligned}$$

P \ Q	00	01	11	10
0	0	0	0	0
1	0	0	1	1

$$F = (P + Q + R)(P + Q + \overline{R})(P + \overline{Q} + \overline{R})(P + \overline{Q} + R)(\overline{P} + Q + R)(\overline{P} + Q + \overline{R}).$$

$$F = \Pi M(0, 1, 2, 3, 4, 5).$$

5(c) Let two variables are A & B.
with n variables number of Boolean expressions are 2^{2^n}
here $n=2$
hence number of Boolean expressions
 $= 2^{2^2} = 2^4 = 16$

Let us write those expression

- | | |
|--------------------------|-------------------------------|
| 1. $Y = AB$ | 9. $Y = AB + \bar{A}\bar{B}$ |
| 2. $Y = A+B$ | 10. $Y = A\bar{B} + \bar{A}B$ |
| 3. $Y = \bar{A}B$ ✓ | 11. $Y = 0$ |
| 4. $Y = A\bar{B}$ | 12. $Y = \bar{A}$ |
| 5. $Y = \bar{A}+B$ | 13. $Y = B$ |
| 6. $Y = A+\bar{B}$ | 14. $Y = A$ |
| 7. $Y = \bar{A}+\bar{B}$ | 15. $Y = B$ |
| 8. $Y = \bar{A}\bar{B}$ | 16. $Y = 1$ |

9

5(d)

Output mechanical power = $VI \cos \phi$

$$7.46 = 500 \times I \times 0.9 \Rightarrow \boxed{I_a = 16.577 \text{ A}}$$

$$\text{Copper loss} = I_a^2 R_a = (16.577)^2 \times 0.8 = 219.86 \text{ W}$$

$$\begin{aligned} \text{Total losses} &= 1500 + 219.86 \\ &= 1719.86 \text{ W} \end{aligned}$$

Commercial efficiency

$$\eta = \frac{\text{O/P}}{\text{O/P} + \text{losses}}$$

$$\eta = \frac{7460}{7460 + 1719.86} = 81.265\%$$


2

5(e)


$R_L C$ large means charging & discharging times can be neglected.

$V_{in} > V_r$ ✓, Diode forward biased and capacitor charges through diode D upto voltage $V_{in} - V_r$
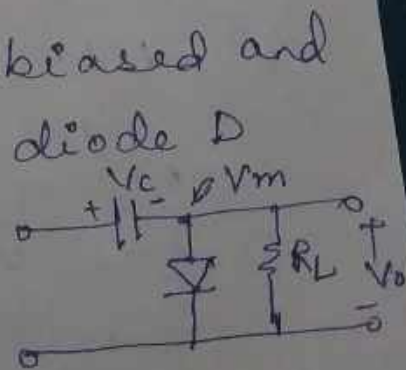
$$\begin{aligned} \text{i.e. } V_c &= V_{in} - V_r = 5 - 0.8 \\ &= 4.2 \text{ V} \end{aligned}$$




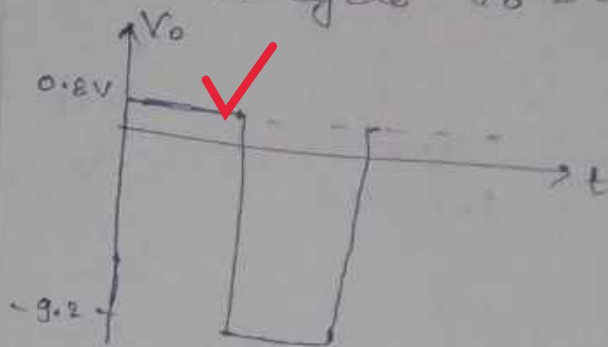$V_o = V_{in} - V_e$
 for +ve cycle $V_o = 5 - 4.2 = 0.8 \text{ V}$.
 for -ve cycle $V_o = -5 - 4.2 = -9.2 \text{ V}$



8

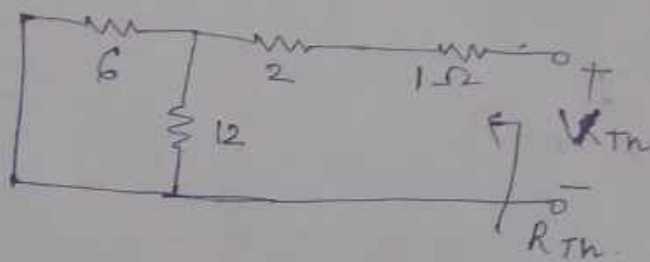5(+) for maximum power transfer $R_L = R_{Th}$
 here R_{Th} is thevenin's equivalent resistance
 for this we deactivate source.



Open circuit
 current source
 and short
 circuit voltage
 source.


$$R_{Th} = 1 + 2 + 12 \parallel 6$$

$$= 1 + 2 + 4 = 7 \Omega$$

$R_L = 7 \Omega$ for maximum power transfer.

5

6(a)

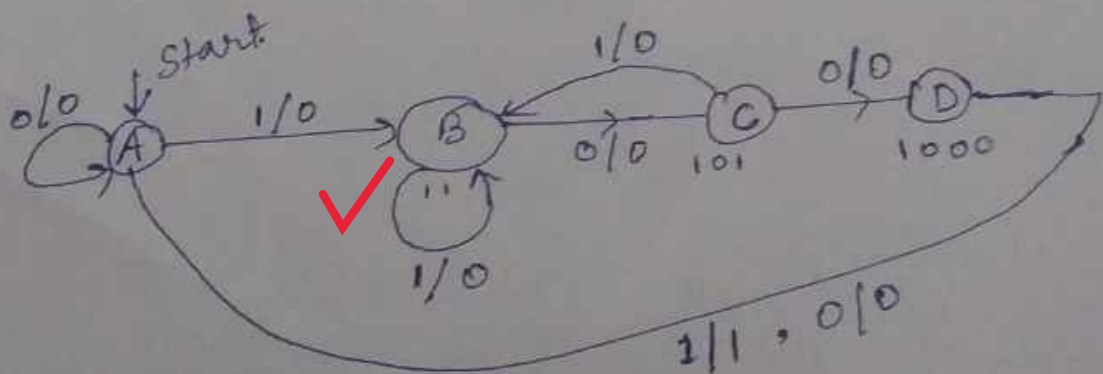

A: 00
B: 01
C: 10
D: 11

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

(10)

P S	X	NS	Y	$J_1 K_1$	$J_0 K_0$
$Q_1 Q_0$	X	$Q_1 + Q_0 + 1$	Y	$J_1 K_1$	$J_0 K_0$
0 0	0	0 0	0	0 X	0 X
0 0	1	0 1	0	0 X	1 X
0 1	0	1 0	0	1 X	X 1
0 1	1	0 1	0	0 X	X 0
1 0	0	1 1	0	X 0	1 X
1 0	1	0 0	0	X 1	1 X
1 1	0	0 0	1	X 1	X 1
1 1	1	0 0	1	X 1	X 1

J_1 Q_0 X

Q_1	00	01	11	10
0				1
1	X	X	X	X

$J_1 = Q_0 \bar{X}$

K_1 Q_0 X

Q_1	00	01	11	10
0				
1	X	X	X	X

$K_1 = X + Q_0$

J_0 Q_1 X

Q_0	00	01	11	10
0				
1	1	X	X	X


$J_0 = X + Q_1$

K_0 Q_1 X

Q_0	00	01	11	10
0	X	X		
1	X	X	1	X

$K_0 = \bar{X} + Q_1$

$Y = Q_1 Q_0 X$

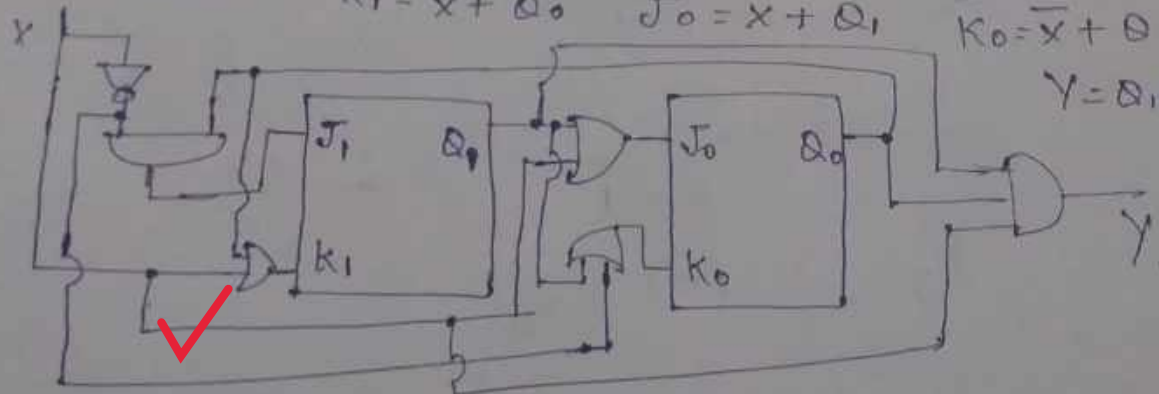


$J_1 = Q_0 \bar{X}$ $K_1 = X + Q_0$ $J_0 = X + Q_1$ $K_0 = \bar{X} + Q_1$

$Y = Q_1 Q_0 X$

18


Q.6(i)

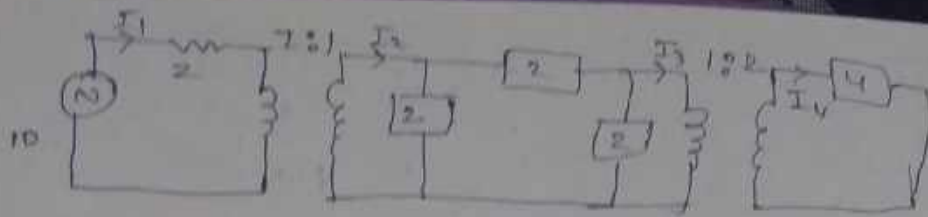


$$I_1 = \frac{10}{2} = 5A$$

$$\frac{I_1}{I_2} = \frac{1}{2} \Rightarrow I_2 = 5 \times 2 = 10A$$

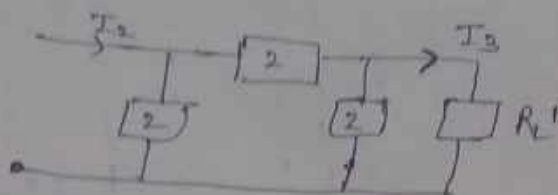for finding I_3 we move 4Ω of load into its branch.



$$R_L' = \frac{4}{(2)^2} = 1\Omega$$

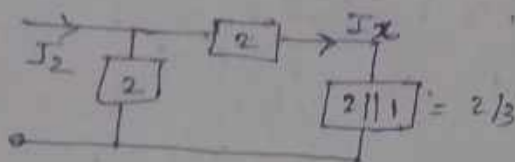

$$I_x = \frac{I_2 \times 2}{2 + \frac{2}{3} + 2} = \frac{I_2 \times 2}{\frac{14}{3}}$$

$$I_x = \frac{6}{14} I_2 = \frac{3}{7} I_2$$

$$I_3 = \frac{I_x \times 2}{2 + 1} = \frac{\frac{3}{7} I_2 \times 2}{3} = \frac{2 I_2}{7}$$

$$I_3 = \frac{2}{7} (10) = \frac{20}{7}$$

4

$$I_4 = \frac{I_3}{2} = \frac{20}{7} \times \frac{1}{2} = \frac{10}{7} = 1.428A$$

Power delivered $P_L = I_4^2 R_L$

$$P_L = \left(\frac{10}{7}\right)^2 \times 4 = 8.16 \text{ Watts}$$

(ii) $V_b = V_i + I_1 \times 1K \Rightarrow V_f$

~~AV~~

6(b)(ii) $V_2 = -2000 I_2$ — (1)

(11)

$$V_1 = 100 I_1 + 0.0025 V_2$$

$$V_1 = 100 I_1 + 0.0025 \times 2000 I_2 = 100 I_1 + 5 I_2$$

$$I_2 = 20 I_1 + 10^{-3} V_2$$
 — (2)

$$I_2 = 20 I_1 + 10^{-3} \times 2 \times 10^3 (-I_2) \quad [(1) \text{ in } (2)]$$

$$3 I_2 = 20 I_1 \Rightarrow I_1 = \frac{3}{20} I_2$$
 — (3)

$$V_1 = 100 \left(\frac{3}{20} I_2 \right) + 5 I_2 = 20 I_2$$
 — (4)

$$\frac{V_2}{V_1} = \frac{-2000 I_2}{20 I_2} = -100 \Rightarrow \boxed{\frac{V_2}{V_1} = -100}$$

6(c) Torque Power delivered $= 3 I_2^2 \frac{R_2}{s}$ — (1)

$$I_2 = \frac{E_2}{\sqrt{\left(\frac{R_2}{s}\right)^2 + \left(\frac{X_2}{s}\right)^2}} = \frac{s E_2}{\sqrt{(R_2)^2 + (X_2)^2}}$$
 — (2)

(2) in (1)

$$P_g = 3 \frac{s^2 E_2^2}{(s R_2)^2 + (R_2)^2} \times \frac{R_2}{s}$$

$$P_g = \frac{3 s E_2^2 R_2}{(s R_2)^2 + (R_2)^2}$$

Torque generated $T = \frac{P}{\omega}$

$$T = \frac{3}{\frac{2\pi \times 50}{60}} \cdot \frac{s E_2^2 R_2}{(s R_2)^2 + (R_2)^2}$$

$$T = \frac{3 E_2^2}{\frac{2\pi N_s}{60}} \frac{R_2}{(\sqrt{3} X_2)^2 + \left(\frac{R_2}{\sqrt{3}}\right)^2}$$

$$T = \frac{K R_2}{\left(\frac{\sqrt{3} R_2}{\sqrt{3}}\right)^2 + 2 R_2 X_2 - 2 R_2 X_2 + (\sqrt{3} X_2)^2}$$

$$T = \frac{K R_2}{\left(\frac{R_2}{\sqrt{3}} - \sqrt{3} X_2\right)^2 + 2 R_2 X_2}$$

for maximum torque. $\frac{R_2}{\sqrt{3}} - \sqrt{3} X_2 = 0$

$$\boxed{R_2 = 3 X_2}$$

↑
This is condition for maximum torque

$$T_{max} = \frac{K R_2}{2 R_2 X_2} = \frac{K}{2 X_2}$$

$$T_{max} = \frac{3 E_2^2}{\frac{2\pi N_s}{60} 2 X_2} = \frac{3}{\frac{2\pi N_s}{60}} \frac{E_2^2}{2 X_2}$$

(ii)

$$T_{max} = 110 \text{ Nm}$$

$$N_{rmax} = 1360 \text{ rpm}$$

$$N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

$$s_{max} = \frac{N_s - N}{N_s} = \frac{1500 - 1360}{1500} = 0.093$$

$$R_2 = 0.25 \text{ (star connected)}$$

$$X_2 = \frac{R_2}{s} = \frac{0.25}{0.093} = 2.688 \Omega$$

$$T = \frac{P_g}{\omega} \Rightarrow P_g = T \omega = T \cdot \frac{2\pi N_s}{60}$$

$$P_g = 110 \times \frac{2\pi \times 1500}{60} = 17.2787 \text{ kW.}$$

$$P_g = 3 I_{2ph}^2 \frac{R_2}{s}$$

$$17.2787 = 3 I_{2ph}^2 \times \frac{0.25}{0.093} \Rightarrow I_{2ph} = 46.2874$$

$$\text{Now required } T_{st} = \frac{1}{2} T_{FL} \Rightarrow T_{st} = \frac{110}{2}$$

$$\frac{T_{st}}{T_{FL}} = \frac{2}{s_s}$$

$$T_{st} = 55 \text{ Nm}$$

$s_s = 1 \leftarrow$ slip at starting

$$E_2 = I_2 \sqrt{\left(\frac{R_2}{s}\right)^2 + (X_2)^2}$$

$$= 46.287 \sqrt{\frac{0.25}{0.093} + (2.688)^2}$$

$$E_{2ph} = 175.95 \text{ V.}$$

$$\text{for case 2. } P_g = 8.63935 \text{ kW}$$

$$P_g = 3 I_{2ph}'^2 \frac{R_2}{s}$$

$$8.63935 = 3 I_{2ph}'^2 \times (0.25 + R_{ext})$$

$$I_{2ph}' = \frac{E_2}{\sqrt{(R_2 + R_{ext})^2 + (2.688)^2}}$$

$$\frac{8.63935 \times 10^3}{3} = \frac{(175.95)^2}{(0.25 + R_{ext})^2 + (2.688)^2}$$

$$(0.25 + R_{ext})^2 + (2.688)^2 = 10.75 (0.25 + R_{ext})$$

$$0.0625 + R_{ext}^2 + 0.5 R_{ext} + 2.688^2 = 2.6875 + 10.75 R_{ext}$$

$$R_{ext}^2 - 10.25 R_{ext} + 4.6 = 0$$

$$R_{ext} = 0.47 \Omega, 9.7796 \Omega$$

$$R_{ext} = 0.47 \Omega$$

12

7(a) Voltage across capacitor given as

$$V = \frac{1}{C} \int i dt = \frac{I}{C f_0}$$

$$V_{co} = \frac{10^{-3}}{20 \times 10^{-6} \times 4 \times 10^3} = 0.0125 \text{ V}$$

This is the voltage that can be sampled in one instant or can be called as resolution.

When $V_A > V_{co}$ then counter enabled and starts to count until $V_A \leq V_{co}$. when it is cleared.


$$\text{No of steps} = \frac{2}{0.0125} = 160$$

So counter counts from 0 to 159 in 160 clock pulses.

when it stops it has $(159)_{10} = (10011111)_2$

Q_7	Q_6	Q_5	Q_4	Q_3	Q_2	Q_1	Q_0
1	0	0	1	1	1	1	1

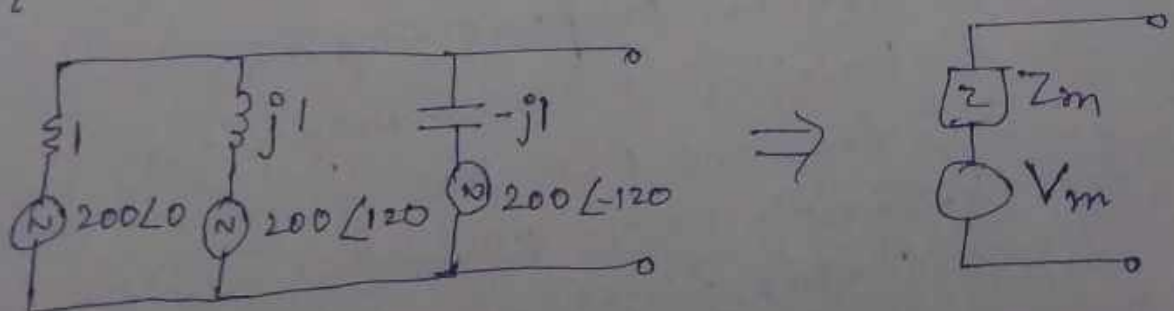7(b) From millman theorem when a network consists of parallel voltage sources then it is can be replaced by equivalent voltage & current source & equivalent resistance.




$$V_m = \frac{\cancel{200} \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$V_m = \frac{\frac{200}{1} + \frac{200 \angle 120}{1 \angle 90} + \frac{200 \angle 120}{1 \angle -90}}{\frac{1}{1} + \frac{1}{j} + \frac{1}{-j}}$$

$$= \frac{200 + 200 \angle 30 + 200 \angle -30}{1 - j + j} = 546.41 \angle 0$$
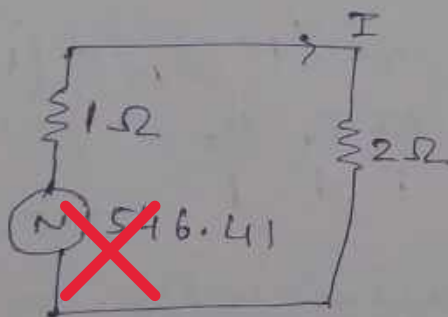
$$R_m = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{1} + \frac{1}{j} + \frac{1}{-j}} = 1$$



$$I = \frac{546.41}{2 + 1}$$

$$I = 182.1367 \text{ A}$$

7(c) Intel 8086 contains the following registers -

1. General purpose register
2. Pointer & Index registers
3. Segment Register.
4. Instruction pointer
5. Status flags -

AH	AL
BH	BL
CH	CL
DH	DL
SP	
BP	
SI	
DI	
CS	
DS	
SS	
ES	
IP	
Flags	

General Purpose register

Pointer

Index registers

Segment registers

(12)

Acc - AX
 Base - BX
 Counter - CX
 Data - DX
 Stack pointer - SP
 Base pointer - BP
 Source Index - SI
 Destination Index - DI
 Code segment - CS
 Data segment - DS
 Stack segment - SS
 Extra segment - ES
 Instruction Pointer - IP
 Status Register - flags

General Purpose register : 16 bit registers further classified as two 8 bit

Pointer & Index Register : SP holds address of top of stack. BP, SS, DI are used in memory address computation.

Segment Registers : Code segment of memory holds instruction codes of a program. Data, variables constants in data segment. Stack segment holds content of subroutine. Extra segment holds destination address of some data.

Instruction Pointer (IP) : Holds address of next instruction to be executed. Its content automatically incremented while program execution

7(c)

Resistance drop of 10%

$$\frac{\% R}{R} = 10\%$$

$$\cos \phi = 0.5$$

$$\sin \phi = 0.866$$

Impedance drop 20%

$$\frac{\% X}{X} = 20\%$$

Voltage regulation

$$VR = \frac{I R_{eq} \cos \phi + I X_{eq} \sin \phi}{V} \times 100.$$

$$\frac{R_{eq}}{V/I} = 10\%$$

$$\frac{X_{eq}}{V/I} = 20\%$$

$$VR = 10 \times 0.5 + 20 \times 0.866$$

$$[VR = 22.32\%]$$

3