

GATE

MADE EASY **WORKBOOK 2026**



**Detailed Explanations of
Try Yourself *Questions***

Computer Science & IT
Digital Logic



1

Number Systems and Binary Codes



Detailed Explanation of Try Yourself Questions

T2 : Solution

(c)

$$\begin{aligned}(44)_7 &= (32)_{10}; (44)_5 = (24)_{10} \\ (44)_7 - (44)_5 &= (32)_{10} - (24)_{10} = (8)_{10} \\ &= 00001000 \leftarrow \text{It is in 2's complement form}\end{aligned}$$

T3 : Solution

(d)

$$\begin{aligned}(34)_8 &= (28)_{10} = (11100)_2 \\ &= 10010 \leftarrow \text{Gray code}\end{aligned}$$

T4 : Solution

(424)

\therefore

$$\begin{aligned}A &= 10, \quad B = 11 \\ r &= 12 \\ (2B4)_{12} &= 2 \times (12)^2 + 11 \times (12) + 4 \\ &= 288 + 132 + 4 = (424)_{10}\end{aligned}$$

T9 : Solution

(1101)

Let number N is given to the system.

$$\text{Output after 1's complement} = 15 - N$$

$$\text{Output after 2's complement} = 16 - 15 + N = N + 1$$

3 such systems are connected in cascade.

$$\begin{aligned}\text{So,} \quad \text{Final output} &= \text{Input} + (3)_{10} \\ &= 1010 + 0011 = 1101\end{aligned}$$

■■■■

2

Boolean Algebra, Logic Gates and K-Maps



Detailed Explanation of Try Yourself Questions


T1 : Solution

Let the 3 locks are A, B, C

0 - key not inserted

1 - key inserted

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	X

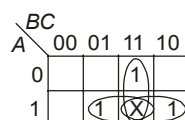

$$Y = AB + BC + AC$$

The expression for Y is similar to carry in full adder circuit.

So, Number of NAND Gates required are = 6.

T2 : Solution

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

F	CD				
		00	01	11	10
AB	00			1	1
	01			1	1
	11	1	1		
	10	1	1		


$$F = \bar{A}C + A\bar{C} = A \oplus C$$

**T3 : Solution**

(d)

Consider left side EX-OR gate as G_1 and right side EX-OR gate as G_2 .

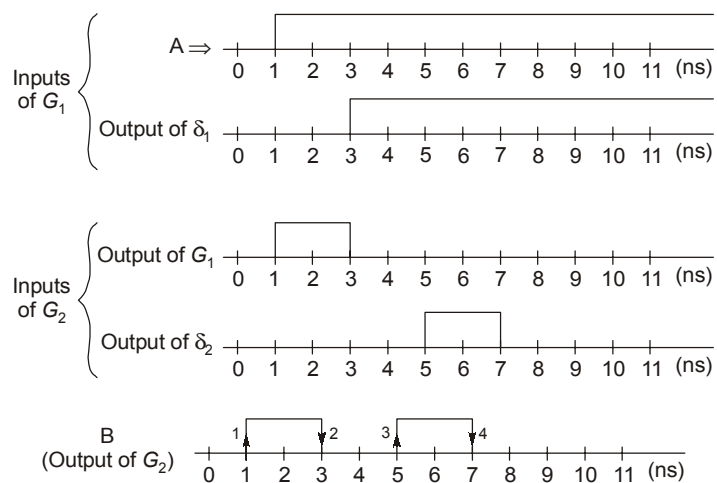
1. To find number of transitions at B i.e. the output of gate G_2 , it is required to identify the inputs of gate G_2 .
2. To identify gate G_2 inputs it is required to find gate G_1 output waveform.
3. To find gate G_1 output waveform, it is required to identify δ_1 output waveform.



Total numbers of transitions at B during interval from 0 to 10 ns are '4'.
Hence option (d).

T6 : Solution

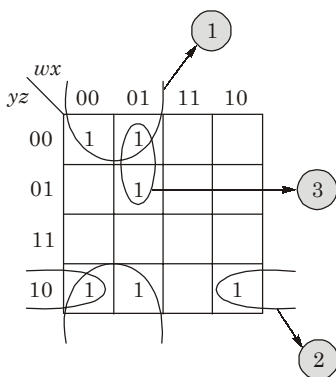
$$f(w, x, y, z) = \sum(0, 2, 4, 5, 6, 10)$$



\therefore 3 prime implicants.

T7 : Solution

(c)

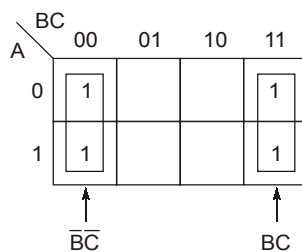

$$= \overline{B}\overline{C} + BC = B \odot C = \overline{B \oplus C}$$

■■■■

3

Combinational Logic Circuits



Detailed Explanation of Try Yourself Questions

T2 : Solution

(a)

$$Z = PRS + PQR\bar{S} + \bar{P}RS + (P + \bar{Q})\bar{R}\bar{S}$$

Mapping above terms in Karnaugh map

		RS			
		00	01	11	10
PQ	00	1			
	01				
	11	1	1	1	1
	10	1	1		

$$Z = PQ + \bar{P}\bar{Q}S + \bar{Q}\bar{R}\bar{S}$$

T5 : Solution

(b, c)

(b) $X = 1001$ and $C_{in} = 1$
then

$$\begin{array}{r} 9 \\ + 2's \text{ of } BCD \end{array} \Bigg\} \Rightarrow \begin{array}{r} 9 \\ -BCD \\ \hline 9's \text{ of } BCD \end{array}$$


- (c) $X = 1010$ and $C_{in} = 0$
then

$$\left. \begin{array}{c} 10 \\ + 1\text{'s of BCD} \end{array} \right\} \Rightarrow \left. \begin{array}{c} 9 \\ + 2\text{'s of BCD} \end{array} \right\} \Rightarrow \begin{array}{c} 9 \\ -BCD \\ \hline 9\text{'s of BCD} \end{array}$$

\therefore Answer is option (b) and (c).

T6 : Solution

(a)

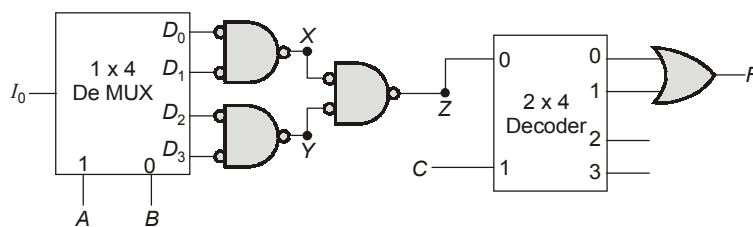

$$\begin{aligned} X &= \overline{D_0} \overline{D_1} I_0 = (D_0 + D_1) I_0 \\ &= (\overline{A} \overline{B} + \overline{A} B) I_0 = \overline{A} I_0 \\ Y &= \overline{D_2} \overline{D_3} I_0 = (D_2 + D_3) I_0 \\ &= (A \overline{B} + A B) I_0 = A I_0 \\ Z &= \overline{(X \cdot Y)} = X + Y \\ &= \overline{A} \cdot I_0 + A I_0 = I_0 \\ F &= (\overline{Z} \overline{C} + Z \overline{C}) = \overline{C} (\overline{I_0} + I_0) \\ &= \overline{C} \end{aligned}$$

■■■■

4

Sequential Circuits



Detailed Explanation of Try Yourself Questions

T1 : Solution

(a)

When

$$A = 1 \text{ and } B = 1$$

$$X = \bar{Y}$$

$$Y = \bar{X}$$

Now

$$A = 1 \text{ and } B = 0$$

$$Y = 1$$

$$X = 0$$

Now

$$A = 1 \text{ and } B = 1$$

$$X = \bar{Y} = 0$$

$$Y = \bar{X} = 1$$

So, the outputs x and y will be fixed at 0 and 1 respectively.

T2 : Solution

(c)

	A	B	C_i	S	C_o
After 1 st CP	1	1	0	0	1
After 2 nd CP	1	1	1	1	1

■■■■