



MADE EASY

India's Best Institute for IES, GATE & PSUs

Test Centres: Delhi, Hyderabad, Bhopal, Jaipur, Pune, Kolkata

ESE 2024 : Prelims Exam
CLASSROOM TEST SERIES

**ELECTRICAL
ENGINEERING**

Test 20

Full Syllabus Test 4 : Paper-II

- | | | | | | |
|---------|---------|---------|----------|----------|----------|
| 1. (d) | 26. (a) | 51. (d) | 76. (b) | 101. (d) | 126. (a) |
| 2. (c) | 27. (b) | 52. (b) | 77. (c) | 102. (b) | 127. (d) |
| 3. (d) | 28. (d) | 53. (b) | 78. (d) | 103. (d) | 128. (a) |
| 4. (b) | 29. (c) | 54. (c) | 79. (a) | 104. (b) | 129. (d) |
| 5. (c) | 30. (d) | 55. (c) | 80. (c) | 105. (a) | 130. (d) |
| 6. (c) | 31. (d) | 56. (b) | 81. (d) | 106. (a) | 131. (a) |
| 7. (c) | 32. (d) | 57. (c) | 82. (b) | 107. (b) | 132. (d) |
| 8. (c) | 33. (a) | 58. (c) | 83. (a) | 108. (a) | 133. (a) |
| 9. (b) | 34. (b) | 59. (a) | 84. (a) | 109. (a) | 134. (c) |
| 10. (a) | 35. (a) | 60. (d) | 85. (a) | 110. (d) | 135. (a) |
| 11. (b) | 36. (b) | 61. (d) | 86. (b) | 111. (a) | 137. (d) |
| 12. (b) | 37. (a) | 62. (b) | 87. (d) | 112. (d) | 136. (d) |
| 13. (b) | 38. (c) | 63. (d) | 88. (c) | 113. (b) | 138. (a) |
| 14. (a) | 39. (a) | 64. (a) | 89. (a) | 114. (d) | 139. (c) |
| 15. (a) | 40. (b) | 65. (b) | 90. (b) | 115. (c) | 140. (a) |
| 16. (b) | 41. (b) | 66. (c) | 91. (c) | 116. (d) | 141. (b) |
| 17. (a) | 42. (b) | 67. (a) | 92. (c) | 117. (a) | 142. (d) |
| 18. (a) | 43. (d) | 68. (c) | 93. (b) | 118. (b) | 143. (b) |
| 19. (a) | 44. (d) | 69. (b) | 94. (c) | 119. (d) | 144. (d) |
| 20. (c) | 45. (c) | 70. (b) | 95. (a) | 120. (a) | 145. (a) |
| 21. (b) | 46. (a) | 71. (c) | 96. (b) | 121. (d) | 146. (a) |
| 22. (d) | 47. (b) | 72. (a) | 97. (c) | 122. (c) | 147. (a) |
| 23. (d) | 48. (b) | 73. (c) | 98. (a) | 123. (d) | 148. (b) |
| 24. (d) | 49. (c) | 74. (b) | 99. (d) | 124. (d) | 149. (c) |
| 25. (a) | 50. (c) | 75. (d) | 100. (c) | 125. (a) | 150. (a) |

Note: In Q. no. 83 answer key has been updated.

DETAILED EXPLANATIONS

1. (d)


Let the voltage across current source be V . Using nodal analysis,

$$\frac{V-2}{1} + (-1) + \frac{V}{3} = 0$$

$$\frac{4V}{3} = 3$$

$$V = \frac{9}{4}$$

$$V = 2.25 \text{ Volt}$$

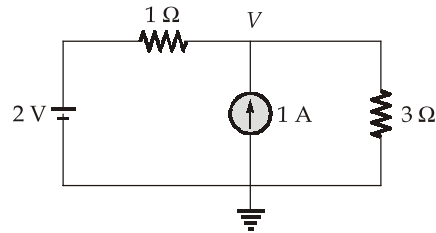

2. (c)

We have, $I = 2 \text{ A}$, $t = 10 \text{ sec}$, $V = 115 \text{ Volt}$

$$\begin{aligned} \text{Charge } (q) &= I \times t \\ &= 2 \times 10 = 20 \text{ Coulomb} \end{aligned}$$


$$\begin{aligned} \text{Since, Energy } (E) &= qV \\ &= 20 \times 115 = 2300 \text{ J} = 2.3 \text{ kJ} \end{aligned}$$

3. (d)

In the given circuit,

 6Ω and 3Ω resistors are in parallel.
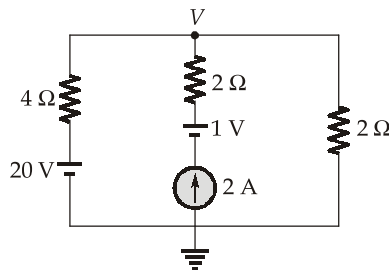
$$\therefore R' = \frac{6 \times 3}{6 + 3} = \frac{18}{9} = 2 \Omega$$



Using nodal analysis,


$$\frac{V-20}{4} - 2 + \frac{V}{2} = 0$$

$$\frac{V}{4} + \frac{V}{2} = 2 + 5$$

$$\frac{3V}{4} = 7$$

$$V = \frac{28}{3} \text{ volt}$$
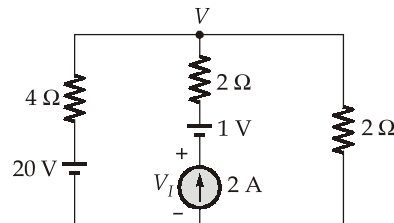
$$V = 1 + V_I - 2 \times 2 \quad (\text{where, } V_I \text{ is voltage across current source})$$



$$V = V_I - 3$$

$$V_I = \frac{28}{3} + 3 = \frac{37}{3} \text{ volt}$$

Power delivered by current source = $V_I \cdot 2$


$$= 2 \times \frac{37}{3} = \frac{74}{3} = 24.67 \text{ W}$$

4. (b)

Conductance: "It is the ability of an element to conduct electric current."

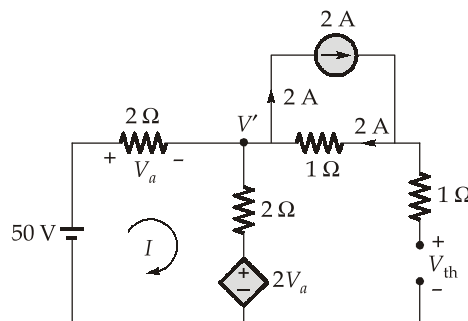5. (c)

Disconnecting the load resistance, we calculate the Thevenin voltage across the open circuit terminals.



$$2I = V_a$$

by using KVL, $50 - 2V_a = 4I$

$$50 = 4I + 4I$$

$$8I = 50$$

$$I = \frac{50}{8} = \frac{25}{4} \text{ A}$$

$$V' = 2I + 2V_a = 2I + 4I = 6I$$

$$V' = \frac{25}{4} \times 6 = 37.5 \text{ volt}$$

$$V_{th} = 2 + V' = 2 + 37.5$$

$$V_{th} = 39.5 \text{ V}$$

6. (c)

We have,

$$V = -2\sin(314t + 10^\circ) = 2\cos(314t + 10^\circ + 90^\circ)$$

$$V = 2\cos(314t + 100^\circ) \text{ Volt}$$

$$V = 2\angle 100^\circ \text{ Volt}$$

Now,

$$I = 5\cos(314t + 160^\circ) = 5\angle 160^\circ \text{ Amp}$$


Here ; $\theta = \theta_V - \theta_I = 100 - 160 = -60^\circ$

Power factor $\Rightarrow \cos\theta = \cos(-60^\circ) = 0.5(\text{leading})$

Note: Leading because current is leading with voltage.

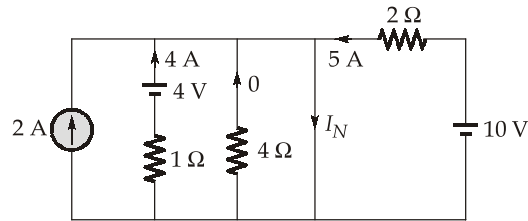7. (c)

For Norton current, I_N load R_L is short circuited.



by using KCL,

$$I_N = 2 + 4 + 5$$

$$I_N = 11 \text{ A}$$

8. (c)

For a two port network to be symmetrical, in transmission parameter matrix, $\begin{bmatrix} A & B \\ C & D \end{bmatrix}$

$$A = D \quad \dots(i)$$


For a two port network to be bilateral, in transmission parameter matrix, $\begin{bmatrix} A & B \\ C & D \end{bmatrix}$

$$AD - BC = 1 \quad \dots(ii)$$

\therefore Option (c) will satisfy the above two conditions.

9. (b)

Given, Circuit

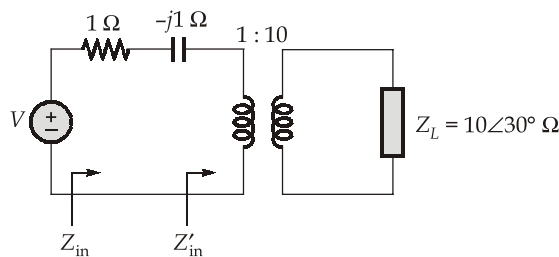

The impedance seen by the source,

$$Z_{in} = 1 - j1 + Z'_{in}$$

where,

$$Z'_{in} = \left(\frac{N_1}{N_2} \right)^2 Z_L = \left(\frac{1}{10} \right)^2 10 \angle 30^\circ$$

$$Z'_{in} = 0.087 + j0.05$$

$$Z_{in} = 1 - j1 + 0.087 + j0.05$$

$$\therefore Z_{in} = 1.087 - j0.95 \Omega$$

10. (a)

When all the nodes are connected to each other and there is no repeated path existing between any two node then;

Total number of possible tress = N^{N-2}

$$N = \text{Number of nodes} = 4$$

$$\text{Total number of possible tress} = 4^{4-2} = 16$$


11. (b)

Duality means, the mathematical representation of both the networks should be identical (KVL and KCL).

\therefore For dual networks, Loop equations of one network are analogous to the node equations of the other.

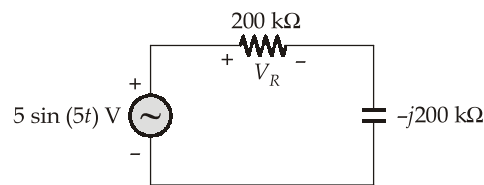12. (b)

$$X_C = \frac{1}{\omega C} = \frac{1}{5 \times 10^{-6}} = 200 \text{ k}\Omega$$



$$\begin{aligned} \therefore V_R &= \frac{5 \angle 0^\circ}{(200 - j200)} \times 200 \\ &= \frac{5 \angle 0^\circ}{(1 - j)} = \frac{5 \angle 0^\circ}{\sqrt{2} \angle -45^\circ} \\ &= 2.5\sqrt{2} \angle 45^\circ \\ V_R &= 2.5\sqrt{2} \sin(5t + 0.25\pi) \text{ volt} \end{aligned}$$

13. (b)

We know,

$$\text{Quality factor } (Q) = \frac{\text{Resonant frequency } (\omega_0)}{\text{Bandwidth}}$$

$$\text{Here, Resonance frequency } (\omega_0) = \sqrt{\omega_1 \cdot \omega_2} = 2\omega_1$$

$$\text{Bandwidth (B.W.)} = \omega_2 - \omega_1 = 3\omega_1$$

$$\therefore Q = \frac{2\omega_1}{3\omega_1} = \frac{2}{3}$$

14. (a)

$$\begin{aligned}\text{Load factor} &= \frac{\text{Average load}}{\text{Maximum demand}} \\ &= \frac{15 \times 8 + 10 \times 8 + 5 \times 8}{24 \times 15} = \frac{240}{15 \times 24} = \frac{10}{15} \\ \text{Load factor} &= 0.667\end{aligned}$$

15. (a)

$$\text{Total load, } P_{G_1} + P_{G_2} = 250 \text{ MW}$$

For optimum load sharing,

$$\begin{aligned}\frac{dC_1}{dP_{G_1}} &= \frac{dC_2}{dP_{G_2}} \\ 0.20 P_{G_1} + 40.0 &= 0.25 P_{G_2} + 30.0 \\ 5 P_{G_1} - 4 P_{G_2} &= 200 \quad \dots(i) \\ P_{G_1} + P_{G_2} &= 250 \quad \dots(ii)\end{aligned}$$

On solving equations (i) and (ii), we obtain

$$P_{G_1} = \frac{350}{3} \text{ MW}$$

$$\text{and } P_{G_2} = \frac{400}{3} \text{ MW}$$

16. (b)

Nuclear power stations have very high capital cost and very low fuel cost. Thus they are considered as base load power stations.

17. (a)

$$\text{Geometric mean radius} = \text{GMR} = D_s$$

$$\begin{aligned}D_s &= \sqrt[4]{D_{aa} \cdot D_{ab} \cdot D_{ac} \cdot D_{ad}} \\ &= \sqrt[4]{r' \times 2r \times 2r \times 2\sqrt{2} \times r} \\ D_s &= \sqrt[4]{8.8} r\end{aligned}$$

18. (a)

The distance between the phase conductors in underground cable is very small as the result of which proximity effect is dominant.

19. (a)

$$\begin{aligned}\text{Let } \Delta V &= \text{Voltage fluctuation} \\ \Delta Q &= \text{Reactive power variation (i.e. the size of the compensator)} \\ S_{s/c} &= \text{System short circuit capacity}\end{aligned}$$

Then,
$$\Delta V = \frac{\Delta Q}{S_{s/c}}$$

or,
$$\begin{aligned}\Delta Q &= \Delta V \times S_{s/c} \\ &= \pm (0.05 \times 5000) \\ &= \pm 250 \text{ MVAR}\end{aligned}$$

\therefore The capacity of the static VAR compensator is 250 MVAR.

20. (c)

Corona effects can be minimized in a transmission line by using large diameter conductors which may be accomplished by using hollow conductors.

21. (b)

Since the generators are in parallel, they will operate at same frequency at steady load.

Let,

$$\text{load on generator 1 (200 MW)} = x \text{ MW}$$

$$\text{load on generator 2 (400 MW)} = (600 - x) \text{ MW}$$

$$\text{Reduction in frequency} = \Delta f$$

Then,
$$\frac{\Delta f}{x} = \frac{0.04 \times 50}{200}$$

$$\frac{\Delta f}{600 - x} = \frac{0.05 \times 50}{400}$$

Also, Equating $\Delta f = \frac{0.04 \times 50}{200}(x) = \frac{0.05 \times 50}{400}(600 - x)$, we have

$$x \approx 231 \text{ MW (load on generator 1)}$$

$$\therefore \text{System frequency} = 50 - \left(\frac{0.04 \times 50}{200} \right) \times 231 = 47.69 \text{ Hz}$$

22. (d)

Three phase fault current is given as

$$(I_f)_{3-\phi} = \frac{V_3^0}{Z_{33}} = \frac{1}{j0.3} = -j 3.33 \text{ p.u.}$$

23. (d)

The diagonal element Y_{22} of Y_{bus} is obtained by,

$$\begin{aligned}Y_{22} &= y_{12} + y_{23} + y_{20} \\ &= \frac{1}{Z_{12}} + \frac{1}{Z_{23}} + \frac{1}{Z_{20}} \\ &= \frac{1}{j0.1} + \frac{1}{j0.1} + \frac{1}{-j20} = -j19.95 \text{ p.u.}\end{aligned}$$

24. (d)

In general for a n bus system having p -number of pV buses the size of the Jacobian matrix will be

$$\begin{aligned}
 &= (2n - 2 - p) \times (2n - 2 - p) \\
 &= (2 \times 15 - 2 - 3) \times (2 \times 15 - 2 - 3) \\
 &= 25 \times 25
 \end{aligned}$$

25. (a)

Insulation resistance is inversely proportional to length of the line

$$\begin{aligned}
 R &\propto \frac{1}{l} \\
 \frac{R_1}{R_2} &= \frac{l_2}{l_1} \\
 \frac{200}{R_2} &= \frac{5}{1} \\
 R_2 &= 40 \text{ M}\Omega
 \end{aligned}$$

26. (a)

$$\begin{aligned}
 I_S &= CV_r + DI_R \\
 V_r &= \frac{220}{\sqrt{3}}, \quad I_r = 0 \\
 \therefore I_S &= 0.5 \times 10^{-4} \times \frac{220}{\sqrt{3}} \times 10^3 \\
 I_S &= \frac{11}{\sqrt{3}} \text{ A}
 \end{aligned}$$

27. (b)

Kinetic energy = GH

If Kinetic energy is constant then $G \propto \frac{1}{H}$

$$\begin{aligned}
 \therefore \frac{G_1}{G_2} &= \frac{H_2}{H_1} \\
 \text{or, } \frac{100}{50} &= \frac{H_2}{5} \\
 H_2 &= 10 \text{ MJ/MVA}
 \end{aligned}$$

28. (d)

Steady state error due to unit step input for type-0 system:

$$e_{ss} = \frac{1}{1 + K_p}$$

where,
$$K_p = \lim_{s \rightarrow 0} G(s)H(s) = \lim_{s \rightarrow 0} \frac{K}{(s+1)(0.1s+1)} = K$$

given
$$e_{ss} = \frac{1}{1+K} = 0.1$$

$$1+K = \frac{1}{0.1} = 10$$

$$K = 9$$

29. (c)

For a state transition matrix:



$$\phi(0) = I$$

and

$$[\phi(t)]^{-1} = \phi(-t)$$

only option (c) satisfies above conditions.

30. (d)

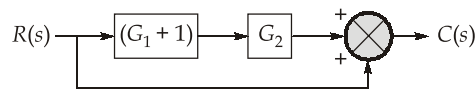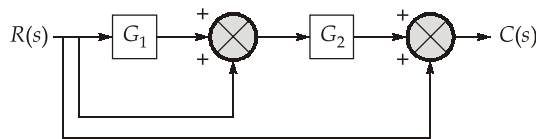

$$R(s) \longrightarrow \boxed{G_1 G_2 + G_2 + 1} \longrightarrow C(s)$$

$$\frac{C(s)}{R(s)} = 1 + G_2 + G_1 G_2$$

31. (d)

Output $Y(s)$ is given as,
$$Y(s) = \left[[R(s) - Y(s)]K + X(s) \right] \frac{1}{(s+1)}$$

$$Y(s) + \frac{K}{(s+1)} Y(s) = \frac{KR(s) + X(s)}{(s+1)}$$

$$Y(s) = \frac{K[R(s)]}{(s+K+1)} + \frac{X(s)}{s+(K+1)}$$

Output due to disturbance, $Y_1(s)$

$$Y_1(s) = \frac{X(s)}{s+K+1}$$

Let

$$X(s) = \frac{A}{s}$$

$$\lim_{t \rightarrow \infty} y_1(t) = \lim_{s \rightarrow 0} s Y_1(s) = \frac{A}{(K+1)}$$

As K increases, value of output due to disturbance decreases.

$\therefore K$ should be very high value.

32. (d)

Here, $A = \begin{bmatrix} 0 & 1 \\ -3 & -a \end{bmatrix}$, $B = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$, $C = [1 \quad 1]$

By using characteristic equation,

$$q(s) = |[sI - A]| = 0$$

$$\left| \begin{bmatrix} s & 0 \\ 0 & s \end{bmatrix} - \begin{bmatrix} 0 & 1 \\ -3 & -a \end{bmatrix} \right| = 0$$

$$\begin{vmatrix} s & -1 \\ 3 & (s+a) \end{vmatrix} = 0$$

$$s(s+a) + 3 = 0$$

$$s^2 + as + 3 = 0 \dots (i)$$

Comparing it with standard second order characteristic equation, we get

$$\omega_n = \sqrt{3}$$

$$2\xi\omega_n = a \quad \xi = 0.5, \quad \text{given } a = \sqrt{3}$$

$$a = 1.732$$

33. (a)

Open loop transfer function $G(s) = \frac{25}{s(s+5)}$

Characteristic equation $= 1 + G(s)H(s)$

$$q(s) = \frac{25}{s(s+5)} + 1 = 0$$

$$s^2 + 5s + 25 = 0$$

Comparing it with standard 2nd order system characteristic equation, we get,

$$\omega_n = 5 \text{ rad/sec}$$

$$\xi = 0.5$$

$$\text{Quality factor, } Q = \frac{1}{2\xi} = \frac{1}{2 \times 0.5}$$

$$Q = 1$$

34. (b)

Using R-H criterion for characteristic equation:

$$s^2(s+2)(s+5) + K(2s+1) = 0$$

$$(s^3 + 2s^2)(s+5) + K(2s+1) = 0$$

$$s^4 + 5s^3 + 2s^3 + 10s^2 + 2sK + K = 0$$

$$s^4 + 7s^3 + 10s^2 + 2sK + K = 0$$

$$s^4 \quad 1 \quad 10 \quad K$$

$$s^3 \quad 7 \quad 2K \quad 0$$

$$s^2 \quad \frac{70-2K}{7} \quad K$$

$$s^1 \quad \frac{\left(\frac{70-2K}{7}\right)2K - 7K}{\left(\frac{70-2K}{7}\right)}$$

$$s^0 \quad K$$

For stable system,

$$K > 0,$$

$$\frac{70-2K}{7} > 0$$

$$K < 35$$

and

$$\frac{\left(\frac{70-2K}{7}\right)2K - 7K}{\left(\frac{70-2K}{7}\right)} > 0$$

$$(70-2K)2K - 49K > 0$$

$$K < \frac{91}{4}$$

$$K < 22.75$$

 \therefore Range of K ,

$$0 < K < 22.75$$

35. (a)

$$\text{Angle of asymptotes} = 180^\circ$$

$$\therefore P - Z = 1$$

Only option (a) satisfies this condition.

36. (b)

$$G(s) = \frac{1}{s(2s+1)(s+1)}$$

For phase cross over frequency; phase should be -180°

$$-180^\circ = \angle G(j\omega) = -90^\circ - \tan^{-1}(2\omega_{pc}) - \tan^{-1}(\omega_{pc})$$

$$90^\circ = \tan^{-1}(2\omega_{pc}) + \tan^{-1}(\omega_{pc})$$

$$90^\circ = \tan^{-1}\left(\frac{3\omega_{pc}}{1-2\omega_{pc}^2}\right)$$

$$1-2\omega_{pc}^2 = 0$$

$$2\omega_{pc}^2 = 1$$

$$\omega_{pc} = \pm \frac{1}{\sqrt{2}}$$

$$\begin{aligned} \therefore \text{Gain margin} &= \frac{1}{|G(j\omega)|_{\omega=\omega_{pc}}} \\ &= \frac{1 \times 1 \times \sqrt{(4\omega_{pc}^2 + 1)} \times \sqrt{\omega_{pc}^2 + 1}}{1 \times \sqrt{2} \times 1} \\ &= \frac{1}{\sqrt{2}} \times \sqrt{3} \times \frac{\sqrt{3}}{\sqrt{2}} = \frac{3}{2} \end{aligned}$$

37. (a)

Initial slope = 6 dB/oct = 20 dB/dec

$$\frac{a-0}{\log_{10} 20 - \log_{10} 2} = 20$$

$$\frac{a}{\log_{10}\left(\frac{20}{2}\right)} = 20$$

$$\frac{a}{\log_{10} 10} = 20$$

$$a = 20 \text{ dB}$$

38. (c)

Primary bonds are interatomic bonds, these bonds are stable and strong.

39. (a)

The dielectric strength for different dielectric materials in decreasing order is given below:
Mica > Glass > Bakelite > Rubber > Polystyrene > Impregnated paper > Mineral oil > Air

40. (b)

- Burger's vector of an edge dislocation is perpendicular to dislocation line.
- Burger's vector of an screw dislocation is parallel to screw dislocation line.

41. (b)

Properties of hard magnetic materials:

- High value of residual flux density.
- High permeability.
- High coercive force.
- High curie temperature.
- Broad hysteresis loop.

42. (b)

$$\begin{aligned}
 \text{The area of B-H curve} &= \text{Hysteresis loss per cycle} \\
 &= \text{Area of parallelogram} \\
 &= \text{Base} \times \text{Height} \\
 &= 400 \times 10^3 \times 2 = 8 \times 10^5 \text{ J/m}^3
 \end{aligned}$$


43. (d)

Atomic radius of FCC = r

In right angle triangle at any face

$$(r + 2r + r)^2 = s^2 + s^2 = 2s^2$$

$$r = \frac{s\sqrt{2}}{4}$$

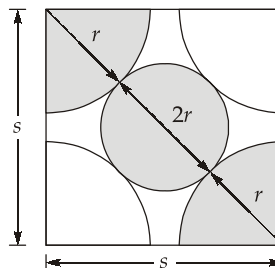

$$\text{Atomic packing factor} = \frac{\text{Total volume of atom}}{\text{Volume of unit cell}}$$

Number of atoms in unit cell = 4

$$\text{Volume of each sphere} = \frac{4}{3}\pi r^3 = \frac{4}{3}\pi \left(\frac{s\sqrt{2}}{4}\right)^3$$

$$\text{Volume of unit cell} = s^3$$

$$\therefore \text{Atomic packing factor} = \frac{4 \times \frac{4}{3}\pi \left(\frac{s\sqrt{2}}{4}\right)^3}{s^3} = \frac{\pi}{3\sqrt{2}}$$

44. (d)

Soft magnetic material have low eddy current losses, narrow hysteresis loop, low coercive force and can be easily demagnetized in other direction.

45. (c)

We know, Dielectric loss = $\frac{E^2 f \epsilon_r \tan \delta}{1.8 \times 10^{12}} \text{ W/cm}^3$

Given,

$$E = 50 \text{ kV/cm},$$

$$f = 50 \text{ Hz},$$

$$\tan \delta = 0.001$$

$$\text{Dielectric loss} = 0.48 \text{ mW/cm}^3 = 0.48 \times 10^{-3} \text{ W/cm}^3$$

$$0.48 \text{ mW/cm}^3 = \frac{60^2 \times 10^6 \times 50 \times \epsilon_r \times 0.001}{1.8 \times 10^{12}}$$

$$\epsilon_r = \frac{0.48 \times 10^{-3} \times 1.8 \times 10^{12}}{60 \times 60 \times 10^6 \times 50 \times 0.001}$$

$$= \frac{48 \times 18}{36 \times 5} = \frac{24}{5} = 4.8$$

46. (a)

Silsbee's rule suggest that current cannot exceed a critical value to maintain the superconducting state. If current goes higher to this critical value the superconductivity is lost and normal state of material appears.

47. (b)

$$arr = \begin{array}{|c|c|c|c|c|c|c|c|c|c|} \hline M & a & d & e & e & a & s & y & \% \\ \hline 1000 & 1001 & 1002 & 1003 & 1004 & 1005 & 1006 & 1007 & 1008 \\ \hline \end{array}$$

$$* \text{str} \begin{array}{|c|} \hline 1000 \\ \hline 2000 \\ \hline \end{array}$$

$$= \text{str} + \text{str} [3] - \text{str} [1]$$

$$= 1000 + \text{ASCII} [e] - \text{ASCII} [a]$$

$$= 1000 + 101 - 97$$

$$= 1000 + 4$$

$$= 1004$$

printf function print string from address 1004 to 1008 i.e., easy.

48. (b)

$$\text{Number of sets} = 64/8 = 8 = 3 \text{ bits required}$$

$$\text{Number of blocks in main memory} = 2$$

$$1 \text{ block} = 512 \text{ words} = 9 \text{ bits required}$$

Tag	Set	Word
8	3	9

$$\text{Tag} = \text{Total} - (\text{Set} + \text{Word})$$

$$\text{Tag bits} = 20 - (9 + 3) = 8 \text{ bits for Tag}$$

49. (c)

From at	1 bit	8 bit	23 bit
	Sign	Exponent	Mantissa
	32		
	1	10000011	11110000 ... 0

$$\begin{aligned}
 &= (-1)^s (1.E) \times 2^{E-127} \\
 &= (-1)^1 (1.1111) \times 2^{131-127} \\
 &= -(1.1111) \times 2^4 \\
 &= -[2^0 \times 1 + 2^{-1} \times 1 + 2^{-2} \times 1 + 2^{-3} \times 1 + 2^{-4} \times 1] \times 2^4 \\
 &= -[2^4 + 2^3 + 2^2 + 2^1 + 2^0] \\
 &= -(31)_{10}
 \end{aligned}$$

50. (c)

$$\text{Execution time for pipeline} = (k + n - 1) \times t_p$$

where

k = Number of stages

n = Number of instruction

t_p = Execution time = Max (all stages)

$$P_1 = [8 + 500 - 1] \times 8 = 4056$$

$$P_2 = [5 + 500 - 1] \times 5 = 2520$$

$$\text{Time saved using } P_2 = 4056 - 2520 = 1536 \text{ nsec} = 1.536 \mu\text{sec}$$

51. (d)

All the above statements are correct.

S1: Reference bit some times called access bit used in page table entry to show if page is replaced or not.

S2: In hierarchial memory access, CPU perform read and write operation only on level 1 memory. If miss occur then data is first transferred to level 1 then CPU access data.

S3: In simultaneous memory access, CPU perform read and write operation on any level of memory i.e. not necessary to take data first into level 1 memory then access it.

52. (b)

FCFS is non pre-emptive algorithm.

53. (b)

In horizontal form signals are present in decoded form. So number of signal bits

$$= 20 + 70 + 2 + 10 + 23$$

$$= 125 \text{ bits}$$

In vertical form signals are present in encoded form. So, number of signal bits

$$= \log_2(20) + \log_2(70) + \log_2(2) + \log_2(10) + \log_2(23)$$

$$= 5 + 7 + 1 + 4 + 5 = 22$$

So, total bits saved using vertical form

$$= 125 - 22 = 103 \text{ bits}$$

54. (c)

Size of instruction 24 bits

Starting address of the program is 300. The size of instruction is 3 byte long So the address is always the multiple of 3 byte next address is 600 it is also the next instruction of the program.

55. (c)

Under maximum efficiency condition

$$P_{cu} = P_i$$

$$\text{Total loss} = 2 P_i ;$$

$$= 2 \times 300$$

$$= 600 \text{ W}$$

56. (b)

If the incoming alternator is running slower, then soon after the synchronizing switch is closed, the already loaded alternator gets loaded still further and the incoming alternator starts operating as a synchronous motor, which is undesirable.

57. (c)

$$T_{st} = x^2 \left(\frac{I_{sc}}{I_{fl}} \right)^2 S_{fl} \cdot T_{fl}$$

$$0.4 T_{fl} = x^2 [5]^2 \times 0.035 \times T_{fl}$$

$$x^2 = 0.457$$

Current drawn from supply

$$I_{\text{Line}} = x^2 I_{sc} = 0.457 \times 5 \times I_{fl}$$

$$I_{\text{Line}} = 2.28 I_{fl}$$

58. (c)

- Voltage regulation is less important in power transformer and less important in distribution transformer.
- Magnetizing current has dominant 3rd harmonics.
- Magnetizing inrush current has dominant 2nd harmonic.

59. (a)

Under maximum efficiency condition

$$W_i = W_{Cu}$$

$$\text{So, } W_{Cu \text{ } fL} = 2000 \text{ W}$$

Cu loss at $\frac{3}{4}$ full load.

$$= \left(\frac{3}{4}\right)^2 \times \text{Full load Cu loss}$$

$$= \frac{9}{16} \times 2000 = 1125 \text{ W}$$

60. (d)

All statements are correct.

61. (d)

$$\text{generated voltage: } E = \frac{Z\phi NP}{60A}$$

$$\text{for lap } \Rightarrow A = P$$


$$E = \frac{Z\phi N}{60}$$

$$500 = \frac{(12 \times 40) \times 50 \times 10^{-3} \times N}{60}$$

$$N = 1250 \text{ rpm}$$

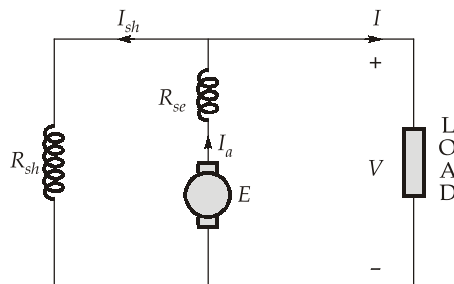62. (b)

The circuit diagram for long shunt compound D.C generator is shown:



Here,

$$I = 50 \text{ A; } V = 500 \text{ Volt; } R_a = 0.05 \Omega; R_{se} = 0.03 \Omega;$$

and

$$R_{sh} = 250 \Omega$$

$$\text{Brush contact drop, } V_b = 2 \times 1 = 2 \text{ V}$$

$$I_{sh} = \frac{V_{sh}}{R_{sh}} = \frac{500}{250} = 2 \text{ A}$$

$$I_a = I_{sh} + I = 2 + 50 = 52 \text{ A}$$

Using KVL:

$$\begin{aligned} E &= V + I_a R_a + I_a R_{se} + V_b \\ &= 500 + (52 \times 0.05) + (52 \times 0.03) + 2 \\ E &= 506.16 \text{ Volt} \end{aligned}$$

63. (d)

At $V = 250 \text{ V}$; $I_{a1} = 50 \text{ A}$; $R_a = 0.25 \Omega$, $N_1 = 750 \text{ rpm}$;

$$E_{b1} = V - I_{a1} R_a = 250 - 50 \times 0.25 = 237.5 \text{ V}$$

after reducing the flux,

$$\phi_2 = 0.9 \phi_1$$

load torque remains same,

$$\begin{aligned} T_1 &= T_2 \\ \phi_1 I_{a1} &= \phi_2 I_{a2} \\ \frac{50}{0.9} &= I_{a2} \end{aligned}$$

$$I_{a2} = 55.56 \text{ A}$$

Back Emf at I_{a2} ,

$$E_{b2} = V - I_{a2} R_a = 250 - (55.56)(0.25) = 236.1 \text{ Volt}$$

for DC machine:

$$\begin{aligned} E_b &\propto N\phi \\ \frac{E_{b1}}{E_{b2}} &= \frac{N_1}{N_2} \times \frac{\phi_1}{\phi_2} \\ \frac{237.5}{236.1} &= \frac{750}{N_2} \times \frac{1}{0.9} \\ N_2 &= 828.5 \text{ rpm} \end{aligned}$$

64. (a)

$$N \propto \frac{E_b}{\phi} \propto \frac{V - I_a R_a}{\phi}$$

By varying flux, we can increase the speed more than its base speed.

65. (b)

Stator teeth of various stack differ by angular displacement of

$$\theta = \frac{360^\circ}{\eta T}$$

$\eta \rightarrow$ no. of stacks

$T \rightarrow$ no. of teeth

for $\theta = 6^\circ$ and $T = 15$

$$6^\circ = \frac{360^\circ}{\eta \times 15}$$

$$\eta = 4$$

67. (a)

If field excitation is such that $E_f \cos \phi > V$ the motor is said to be over-excited and it draws leading current.

68. (c)

Given: rotor frequency = 1.5 Hz = f_2

$$f_2 = f_1$$

$$\text{slip, } s = \frac{1.5}{50} = 3\%$$

$$\text{synchronous speed: } N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

$$\text{rotor speed} = N = N_s(1 - s) = 1500(1 - 0.03) = 1455 \text{ rpm}$$


69. (b)

- GTO thyristor 

It can be switched-off by a negative gate pulse.

- Triac 

Bidirectional device

- IGBT 

Advantage of both MOSFET and BJT. High input impedance and low on-state power loss.

70. (b)

$$\begin{aligned} \left(\frac{di}{dt} \right)_{\max} &= \frac{V_m}{L} \\ &= \frac{230\sqrt{2}}{20\mu\text{H}} = 16.26 \text{ A}/\mu\text{ sec} \end{aligned}$$

71. (c)

The peak to peak ripple voltage of the capacitor is,

$$\Delta V_c = \frac{V_0(1 - \alpha)}{8LCf^2}$$

73. (c)

The given circuit is a Boost regulator,

$$V_0 = \frac{V_s}{1 - \alpha}$$

$$15 = \frac{5}{1 - \alpha}$$

$$\alpha = 0.6667$$

or,

$$\Delta I = \frac{V_s \alpha}{fL}$$

$$\Delta I = \frac{5 \times 0.6667}{25 \times 10^3 \times 150 \times 10^{-6}} = 0.89 \text{ A}$$

74. (b)

A Cycloconverter is used to step up or step down the frequency.
This operation is not possible with four quadrant chopper.

75. (d)

$$V_r = 4 \text{ V}$$

$$V_c = 6 \text{ V}$$

$$\text{Total pulse width} = 2d$$

$$\frac{2d}{N} = \left(1 - \frac{V_r}{V_c}\right) \frac{\pi}{N} \quad (\text{Where } N \text{ is number of pulses per half cycle})$$

$$2d = \left(1 - \frac{V_r}{V_c}\right) \pi = \left(1 - \frac{4}{6}\right) 180^\circ = 60^\circ$$

76. (b)

For single phase full bridge controlled converter,

$$\begin{aligned} \text{Fundamental displacement factor} &= \cos \alpha \\ &= \cos 45^\circ = 0.707 \end{aligned}$$

77. (c)

$$\begin{aligned} \text{Peak Inverse Voltage across } FD &= 2 V_s \\ &= 2 \times 230 = 460 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{Peak Inverse Voltage across main thyristor} \\ &= V_s = 230 \text{ V} \end{aligned}$$

78. (d)

In quadrant-II it is working in forward braking mode.

In quadrant-III it is working in reverse motoring mode.

In quadrant-IV it is working in reverse braking mode.

79. (a)

Using multiple pulse modulation (MPM) lower ordered harmonics are reduced but higher ordered harmonics are increased.

80. (c)

$$\beta = 135^\circ/\text{m}$$

$$\pi = 180^\circ$$

$$\beta = \frac{\pi}{180} \times 135 \text{ rad/m}$$

$$\text{Electrical length} = \beta l = \frac{135\pi}{180} \times 5$$

$$= \frac{15\pi}{4} = 3.75\pi \text{ rad}$$

81. (d)

$$\text{Charge density, } \rho_V = \vec{\nabla} \cdot \vec{D}$$

$$\rho_V = \frac{\partial}{\partial x}(x^3 y^2) + \frac{\partial}{\partial y}(x^2 z) + \frac{\partial}{\partial z}(x^2 y^2)$$

$$\rho_V = 3x^2 y^2 \text{ C/m}^3$$

Charge enclosed by the cube,


$$Q = \int_{-1}^1 \int_{-1}^1 \int_{-1}^1 \rho_V dx dy dz$$

$$Q = \int_{-1}^1 \int_{-1}^1 \int_{-1}^1 3x^2 y^2 dx dy dz$$

$$Q = \frac{3(x^3)_{-1}^1}{3} \left(\frac{y^3}{3} \right)_{-1}^1 (z)_{-1}^1 = \frac{1}{3} \times 2 \times 2 \times 2$$

$$Q = \frac{8}{3} \text{ C}$$

82. (b)

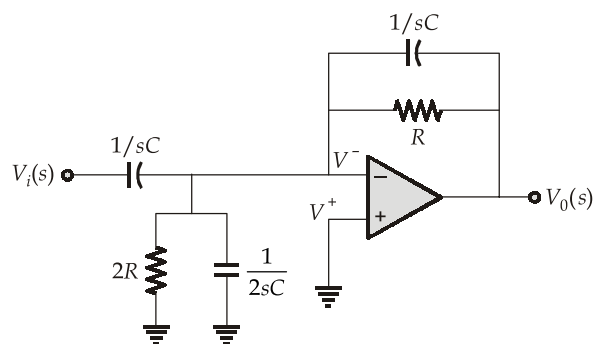

Due to virtual ground,

$$V^+ = V^- = 0 \text{ V}$$

KCL at node V^-

$$\frac{0 - V_i(s)}{1/Cs} + \frac{0 - V_0(s)}{R} + \frac{0 - V_0(s)}{1/Cs} = 0$$

$$V_0(s) \left[\frac{1 + sCR}{R} \right] = -sC V_i(s)$$

$$\frac{V_0(s)}{V_i(s)} = \frac{-sCR}{1 + sCR}$$

Putting $s = j\omega$

$$\frac{V_0(j\omega)}{V_i(j\omega)} = \frac{-j\omega CR}{(1 + j\omega CR)}$$

When $\omega = 0$;

$$V_0(j\omega) = 0$$

When $\omega = \infty$;

$$V_0(j\infty) \neq 0$$

So, it is a HPF

83. (a)

The Thevenin voltage, $V_{Th} = \frac{30}{30+70} \times 20 = 6 \text{ V}$

The Thevenin resistance $R_{Th} = 30 \parallel 70 = 21 \text{ k}\Omega$

Since, large value of β is given therefore current $I_B = 0$


The equivalent circuit,

Applying KVL in loop-1, we get

$$\frac{6 - 0.7}{0.5} = I_C$$


\therefore

$$I_C = 10.6 \text{ mA}$$

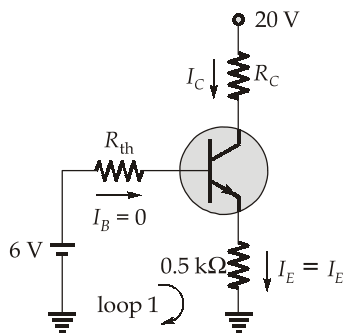

84. (a)

For positive half cycle,

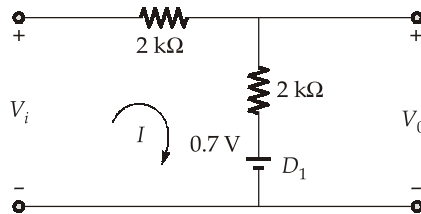 D_1 ON, D_2 OFF

Maximum input voltage = 5 V

$$I = \frac{5 - 0.7}{4k}$$

$$I = \frac{4.3}{4k} \text{ A}$$


$$V_0 = 2kI + 0.7$$

$$= 2k \left(\frac{4.3}{4k} \right) + 0.7$$

$$V_0 = 2.15 + 0.7$$

$$V_{0 \text{ max}} = 2.85 \text{ V}$$

For negative half cycle,

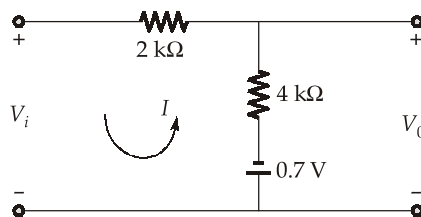 D_1 OFF, D_2 ON

Minimum input voltage = -5 V

$$I = \frac{5 - 0.7}{6k} = \frac{4.3}{6k} \text{ A}$$

$$V_0 = -0.7 - 4kI$$

$$= -0.7 - 4k \left(\frac{4.3}{6k} \right) = -0.7 - \frac{8.6}{3} = -3.56 \text{ V}$$

85. (a)

$$\frac{dA_f}{A_f} \times 100 = \frac{1}{(1 + A\beta)} \left(\frac{dA}{A} \times 100 \right)$$

$$2 = \frac{10}{1 + A\beta}$$

$$1 + A\beta = 5$$

$$\text{Closed loop gain, } A_f = \frac{A}{1 + A\beta} = \frac{100}{5}$$

$$A_f = 20$$


Closed loop gain is having variation of $\pm 2\%$

$$\therefore \frac{2}{100} \times 20 = 0.4$$

$$\therefore A_f = 20 \pm 0.4$$

86. (b)

Using small-signal analysis,

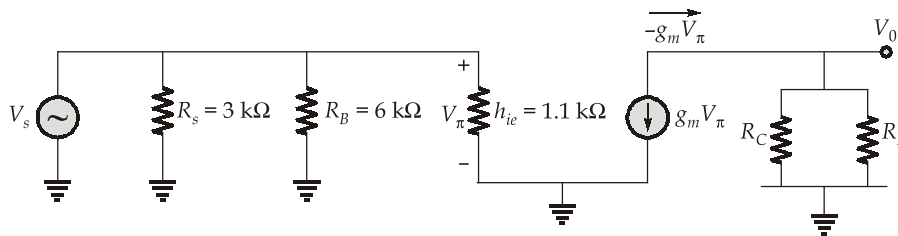

$$V_0 = -g_m V_\pi (R_C \parallel R_L)$$

$$R_C \parallel R_L = 4 \text{ k}\Omega \parallel 4 \text{ k}\Omega = \frac{4 \times 4}{4 + 4} = \frac{16}{8}$$

$$= 2 \text{ k}\Omega$$

$$V_\pi = V_s$$

$$g_m h_{ie} = h_{fe}$$

$$g_m = \frac{50}{1.1 \text{ K}} \text{ A/V}$$

$$V_0 = -g_m V_s (2 \text{ K})$$

$$= \frac{-50}{1.1 \text{ K}} V_s (2 \text{ K})$$

$$\frac{V_0}{V_s} = \frac{-100}{1.1} = -90.9 \simeq -91$$

87. (d)

Let both the NMOS be in saturation.

Drain current is same for both MOSFETs,

$$I_{D1} = I_{D2}$$

$$\frac{k_n}{2} (8 - V_x - 1)^2 = \frac{k_n}{2} (3 - 1)^2$$

$$(7 - V_x)^2 = 4$$

$$49 + V_x^2 - 14V_x = 4$$

$$V_x^2 - 14V_x + 45 = 0$$

$$(V_x - 9)(V_x - 5) = 0$$

$$V_x \neq 9 \text{ V}, V_x = 5 \text{ V}$$

For $V_x = 5 \text{ V}, V_{DS2} = V_x = 5$

$$5 > V_{GS} - V_{TN}$$

$$5 > 3 - 1$$

$$5 > 2$$

\therefore Our assumption is true.

$$V_x = 5 \text{ V}$$

88. (c)

The base of the number is 7.

\therefore It can use digits from 0 to 6.

Hence, using 9 is invalid for this number system.

89. (a)

Six bit representation of +10 is 001010

Taking 2's complement \rightarrow 110101

$$\begin{array}{r} +1 \\ \hline 110101 \\ \hline \end{array}$$

90. (b)

$$Y = I_1 \overline{S_1} S_0 + I_2 S_1 \overline{S_0}$$

$$S_1 = A\overline{B}, \quad S_0 = \overline{A\overline{B}}$$

$$Y = \overline{A\overline{B}} \overline{A\overline{B}} + A\overline{B} \cdot A\overline{B}$$

$$Y = A\overline{B} + \overline{A\overline{B}}$$

$$Y = A\overline{B} + \overline{A} + B$$

$$Y = (\overline{A} + A)(\overline{A} + \overline{B}) + B$$

$$Y = 1(\overline{A} + \overline{B}) + B$$

$$Y = \overline{A} + \overline{B} + B$$

$$Y = \overline{A} + 1$$

$$Y = 1$$


91. (c)

When two numbers are added in excess-3 code and the sum is less than 9, then in order to get the correct answer, we need to subtract 0110 i.e. $(6)_{10}$ from the sum.

92. (c)

$$\begin{aligned}
 Y &= A[(A+B)(\bar{A}+B) + AB(A+\bar{B})] \\
 &= A[A\bar{A} + AB + \bar{A}B + B + AAB + AB\bar{B}] \\
 &= A[AB + B + \bar{A}B + 0] = A[B + \bar{A}B] \\
 Y &= AB
 \end{aligned}$$

Implementing using NOR gate only,

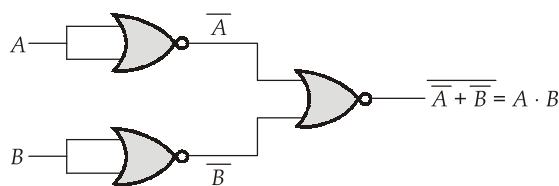

\therefore Minimum no. of 2 input NOR gates required is 3.

93. (b)

Non maskable interrupt in 8085 $\mu P \rightarrow$ TRAP (RST 4.5)

Starting address of RST 4.5

Step - I. $\rightarrow 4.5 \times 8 = (36)_{10}$

Step - II. $\rightarrow \begin{array}{c|c|c} 16 & 36 & \\ \hline & 2 & 4 \end{array} \uparrow = (0024)H$

Starting address $\rightarrow (0024)H$

Each interrupt occupies 8 bytes of memory

$$\begin{array}{r}
 \text{Ending address} = (0024)H \\
 + (0007)H \\
 \hline
 (002B)H
 \end{array}$$

94. (c)

Number of pins in 8085 = 27

95. (a)

For AND operation $\rightarrow AC = 1, CY = 0$

97. (c)

In CALL instruction

Instruction	Machine cycle	T-states
CALL	Opcode fetch	6
	Memory read	3
	Memory read	3
	Memory write	3
	Memory write	3
	5 Machine cycle	18 T-states

98. (a)

In asynchronous TDM, number of slots in each frame is less than that of number of signal sources.

99. (d)

The transmission efficiency of a standard AM signal can be given as,

$$\eta = \frac{k_a^2 P_m}{1 + k_a^2 P_m} \times 100$$

Where,

$$k_a = \text{amplitude sensitivity} = 2 \text{ V}^{-1}$$

$$P_m = \text{average power of message signal} = 6 \text{ W}$$

So,

$$\eta = \frac{24}{1 + 24} \times 100 = 96\%$$

100. (c)

From FM signal,

$$f_i = f_c + k_f m(t)$$

$$\theta_i = 2\pi f_c t + 2\pi k_f \int_{-\infty}^t m(t) dt$$

Maximum phase deviation,

$$\Delta\phi_{\max} = \left| 2\pi k_f \int_{-\infty}^t m(t) dt \right|_{\max}$$

$$\left| \int_{-\infty}^t m(t) dt \right|_{\max} = \text{Area under } m(t)$$


$$= 5 \times 10^{-3} \times 2 \text{ V-sec} = 10 \times 10^{-3} \text{ V-sec}$$

So,

$$\begin{aligned} \Delta\phi_{\max} &= 2\pi \times 2.5 \times 10^3 \times 10 \times 10^{-3} \text{ rad} \\ &= 50\pi \text{ rad} \end{aligned}$$

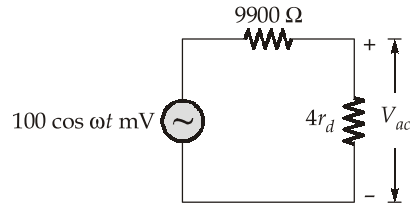103. (d)

$$I_{DC} = \frac{12.7 - (4 \times 0.7)}{9900} = 1 \text{ mA}$$



$$r_d = \frac{V_T}{I_{DC}} = \frac{25 \text{ mV}}{1 \text{ mA}} = 25 \Omega$$

Total resistance of diode,

$$4r_d = 100 \Omega$$

$$\begin{aligned} V_{ac} &= \frac{100 \cos \omega t \times 10^{-3} \times 4r_d}{9900 + 4r_d} \\ &= \frac{100 \times 10^{-3} \times \cos \omega t \times 100}{9900 + 100} = 1 \cos \omega t \text{ mV} \end{aligned}$$

104. (b)

$$\text{Ripple factor} = \sqrt{\left(\frac{I_{\text{rms}}}{I_{dc}}\right)^2 - 1}$$

$$I_{\text{rms}} = \sqrt{\frac{1}{\pi} \int_0^{\pi} I_m^2 \sin^2 \omega t \cdot d\omega t}$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

$$I_{\text{avg}} = \frac{1}{\pi} \int_0^{\pi} I_m \sin \omega t \cdot d\omega t = \frac{2I_m}{\pi}$$

$$\text{Ripple factor} = \sqrt{\left[\frac{\frac{I_m}{\sqrt{2}}}{\frac{2I_m}{\pi}}\right]^2 - 1} = 0.48$$

105. (a)

By applying KVL in base emitter loop,

$$-5 + I_B(200k) + 0.8 = 0$$

$$I_B = \frac{5 - 0.8}{200 \times 10^3} = 21 \mu\text{A}$$

$$I_C = \beta I_B = 100 \times 21 \times 10^{-6} = 2.1 \text{ mA}$$

$$R_C = \frac{10 - 0.2}{2.1 \times 10^{-3}} = 4667 \, \Omega$$

106. (a)

By applying KVL in the base emitter loop,

$$-6 + 0.7 + [(\beta + 1)I_B \times R_E] = 0$$

$$\beta = \frac{5.3}{0.5 \times 10^{-3} \times 530} - 1 = 19$$

By KVL in the collector emitter loop,

$$-10 + [19 \times 0.5 \times 10^{-3} \times 200] + V_{CE} + (20 \times 0.5 \times 10^{-3} \times 530) = 0$$

$$V_{CE} = 2.8 \text{ V}$$

108. (a)

$$I_B = \frac{V_{CC} - V_{BE}}{(\beta + 1)R_E + R_B} = \frac{10 - 0.7}{101 \times 1 + 270} \times 10^{-3}$$

$$= \frac{9.3}{371} \times 10^{-3} \text{ A} = 25.06 \, \mu\text{A}$$

now, $I_{C(\text{sat})} = \frac{10}{2} \times 10^{-3} = 5 \text{ mA}$

$$\therefore I_{C(\text{sat})} > \beta I_B$$

Hence, the transistor is in active mode.

109. (a)

$$\therefore \left| \frac{dv_0(t)}{dt} \right|_{\max} = V_m (2\pi f_m)$$

for distortionless $\left| \frac{dv_0(t)}{dt} \right|_{\max} \leq \text{SR}$

$$V_m \leq \frac{10^6}{2\pi \times 20 \times 10^3}$$

$$V_m \leq 7.96 \text{ V}$$

110. (d)

$$I_B = \frac{V_B}{R_B} = \frac{1.3}{50} \times 10^{-3} = 26 \, \mu\text{A}$$

$$V_E = 1.3 + 0.7 = 2 \text{ V}$$

$$I_E = \frac{10 - 2}{10} \times 10^{-3} = 0.8 \text{ mA}$$

$$\therefore \beta + 1 = \frac{I_E}{I_B} = \frac{0.8}{26 \times 10^{-3}} = 30.77$$

$$\beta = 29.77$$

Now,

$$\alpha = \frac{\beta}{1+\beta} = \frac{29.77}{30.77} = 0.968$$

111. (a)

$$\frac{dA_f}{A_f} = 0.2\% = \frac{0.2}{100}$$

$$dA = 150, \quad A = 2000$$

$$\therefore \frac{dA_f}{A_f} = \frac{1}{1+A\beta} \cdot \frac{dA}{A}$$

$$\frac{0.2}{100} = \frac{1}{1+A\beta} \cdot \frac{150}{2000}$$

$$1 + A\beta = 37.5$$

$$A_f = \frac{A}{1+A\beta} = \frac{2000}{37.5} = 53.33$$

112. (d)

Using virtual short concept

$$V_+ = V_-$$

$$\therefore I = \frac{V_1 - V_2}{1K} = \frac{4 - 6}{1K} = -2 \text{ mA}$$

As op-amp is ideal, input current to op-amp is zero.

$$\begin{aligned} V_0 &= 3K(I) \\ &= 3K(-2 \times 10^{-3}) \end{aligned}$$

$$V_0 = -6 \text{ V}$$

113. (b)

As

$$R_s = S \times \text{Range} - \text{Internal resistance}$$

and

$$S = \frac{1}{I_{fsd}} = \frac{1}{200\mu\text{A}} = 5 \text{ k}\Omega/\text{V}$$

The value of multiplier R_s is calculated as

$$\begin{aligned} R_s &= S \times \text{Range} - \text{internal resistance} \\ &= S \times V - R_m \\ &= 5k \times 50 - 100 \\ &= 249.9 \text{ k}\Omega \end{aligned}$$

114. (d)

$$R_x = \frac{C_1}{C_3} R_2 = \frac{0.5\mu\text{F}}{0.5\mu\text{F}} \times 2k = 2 \text{ k}\Omega$$

$$C_x = \frac{R_1}{R_2} C_3 = \frac{1k}{2k} \times 0.5 \mu\text{F} = 0.25 \mu\text{F}$$

The dissipation factor is given by,

$$\begin{aligned} D &= \omega C_x R_x \\ &= 2 \times \pi \times 1000 \times 2k \times 0.25 \mu F \\ &= \pi \end{aligned}$$

115. (c)

Most oscilloscopes use electrostatic deflection, since it permits high frequency operation and requires negligible power. Electromagnetic deflection is most common in TV picture tubes.

116. (d)

All statements are correct.

117. (a)

Limitations of thermistor:

- Non-linearity in resistance vs temperature characteristics.
- Unsuitable for wide temperature range.
- Very low excitation current to avoid self heating.
- Need of shielded power lines, filters etc due to high-resistance.

118. (b)

We know, Gauge factor = $1 + 2\nu + \frac{\Delta\rho/\rho}{\epsilon}$,

$$G_f = +3.6$$

If piezoresistive effect is neglected $G_f = 1 + 2\nu$

$$\text{Poisson's ratio, } \nu = \frac{G_f - 1}{2} = \frac{3.6 - 1}{2} = 1.3$$

120. (a)

An additional junction point in Anderson bridge increases difficulty of shielding for the bridge.

121. (d)

$$\text{Given, } \int_{-1}^1 t^2 \delta(3t+1) dt$$

From the scaling property of impulse,

$$= \frac{1}{3} \int_{-1}^1 t^2 \delta\left(t + \frac{1}{3}\right) dt$$

from sampling property of impulse,

$$\begin{aligned} &= \frac{1}{3} \left[\left(-\frac{1}{3} \right)^2 \right] \\ &= \frac{1}{3} \times \frac{1}{9} = \frac{1}{27} \end{aligned}$$

122. (c)

Given,
We know that,

$$x[k] = j \delta[K - 1] - j[K + 1] + \delta[K + 3] + \delta[K - 3]$$

$$x(t) = \sum_{k=-\infty}^{\infty} x(k) e^{jk\omega_0 t}$$

Where,

$$\omega_0 = 2\pi$$

 \therefore

$$x(t) = \sum_{k=-\infty}^{\infty} x(k) e^{jk2\pi t} = -je^{j2\pi t} + je^{-j2\pi t} + e^{j6\pi t} + e^{-j6\pi t}$$

$$x(t) = 2(\cos 6\pi t - \sin 2\pi t)$$

123. (d)

Given,

$$\sum_{n=-\infty}^{\infty} x_1(n) = 8$$

$$\sum_{n=-\infty}^{\infty} x_2(n) = 12$$

 \therefore

$$\begin{aligned} \sum_{n=-\infty}^{\infty} [x_1(n) * x_2(n)] &= \sum_{n=-\infty}^{\infty} x_1[n] \cdot \sum_{n=-\infty}^{\infty} x_2[n] \\ &= 8 \times 12 = 96 \end{aligned}$$

124. (d)

Given,

$$x[n] = 2 \delta[n]$$

$$Y(e^{j\omega}) = 3X(e^{j\omega}) - \frac{dX(e^{j\omega})}{d\omega}$$

$$X(e^{j\omega}) = 2$$

 \therefore

$$Y(e^{j\omega}) = 6 - 0 = 6$$

 \therefore

$$y[n] = 6 \delta[n]$$

125. (a)


FIR filters are sometimes called “all zero” because of the poles are always located at $z = 0$.

126. (a)

$$x(t) = u(t) - \delta(t - 1) - \delta(t - 2) - \delta(t - 3) - \delta(t - 4) \dots$$

$$\int_{-\infty}^t x(t) dt = r(t) - u(t - 1) - u(t - 2) - u(t - 3) \dots$$

The integration of $x(t)$ is shown as

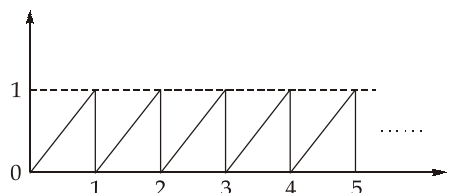

∴ From the figure,

$$\int_{-\infty}^t x(t) dt \Big|_{t=0.5} = 0.5$$

127. (d)

We know that,

$$e^{-a|t|} \leftrightarrow \frac{2a}{a^2 + \omega^2}$$

From duality property,

$$\frac{2a}{a^2 + t^2} \leftrightarrow 2\pi e^{-a|\omega|} = 2\pi e^{-a|\omega|}$$

For $a = 2$,

$$\frac{4}{4 + t^2} \leftrightarrow 2\pi e^{-2|\omega|}$$

$$\frac{2}{\pi(4 + t^2)} \leftrightarrow e^{-2|\omega|}$$

128. (a)

For signal $x(t)$

$$\omega_{NY} = NR = \omega_0$$

∴ $2\omega_m = \omega_0$ (Let ω_m is highest frequency component in $x(t)$)

and


$$Y(\omega) = j\omega X(\omega)$$

Maximum frequency component is decided by $X(\omega)$.

∴ $Y(\omega)$ will have maximum frequency component same as $X(\omega)$.

$$\therefore \text{NR of } y(t) = 2 \times \omega_m = 2 \times \frac{\omega_0}{2} = \omega_0$$

129. (d)

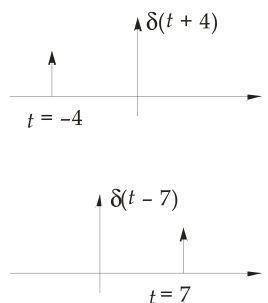

$$\therefore \delta(t + 4) \cdot \delta(t - 7) = \text{zero}$$

130. (d)

$$X(z) = \frac{z}{(z-1)(z-2)}$$

$$\frac{X(z)}{z} = \frac{1}{(z-1)(z-2)} = \frac{A}{(z-1)} + \frac{B}{(z-2)}$$

$$X(z) = \frac{-z}{(z-1)} + \frac{z}{(z-2)}$$

Inverse Z.T

$$x(n) = -u(n) + 2^n u(n) \quad \text{ROC: } |z| > 2$$

131. (a)

$$\begin{aligned} 6(13 \times 11 - 4 \times 37) - 3(32 \times 11 - 10 \times 37) + 7(32 \times 4 - 10 \times 13) \\ = -30 + 54 - 14 \\ = 10 \end{aligned}$$

132. (d)

$$I = \int_{-2}^2 |1-x^4| dx$$

The given function is an even function i.e.,

$$f(x) = f(-x)$$

$$I = 2 \int_0^2 |1-x^4| dx = 2 \left\{ \int_0^1 (1-x^4) dx + \int_1^2 (x^4-1) dx \right\}$$

$$= 2 \left\{ \left[x - \frac{x^5}{5} \right]_0^1 + \left[\frac{x^5}{5} - x \right]_1^2 \right\}$$

$$= 2 \left\{ \left[1 - \frac{1}{5} \right] + \left[\frac{32}{5} - 2 \right] - \left[\frac{1}{5} - 1 \right] \right\}$$

$$= 2 \times \left\{ \frac{4}{5} + \frac{22}{5} + \frac{4}{5} \right\} = 12$$

133. (a)

$$\frac{dx}{dy} = \frac{1}{x(1+y^2)}$$

$$\int \frac{dy}{1+y^2} = \int x dx$$

$$\tan^{-1} y = \frac{x^2}{2} + K$$

$$y = \tan \left(\frac{x^2}{2} + K \right)$$

134. (c)

$$P(x=r) = \frac{e^{-\lambda} \cdot \lambda^r}{r!}, \quad \text{where } \lambda = np$$

$$\lambda = 500 \times 0.006 = 3$$

$$\begin{aligned} P(x \leq 1) &= P(x=0) + P(x=1) \\ &= \frac{e^{-\lambda} \cdot \lambda^0}{0!} + \frac{e^{-\lambda} \cdot \lambda^1}{1!} \\ &= e^{-3} + e^{-3} \cdot 3 = 4e^{-3} \end{aligned}$$

135. (a)

To obtain maximum value of $f(x)$, first $f'(x)$ should be equated to zero

$$f'(x) = 6x^2 - 6x - 36 = 0$$

$$x^2 - x - 6 = 0$$

$$(x-3)(x+2) = 0$$

$$f'(x) = 0 \text{ at } x = 3 \text{ and } -2$$

Now,

$$f''(x) = 12x - 6$$

$$f''(3) = 30 > 0$$

at $x = 3$, there is local minima and

$$f''(2) = -30 < 0$$

\therefore at $x = -2$, a local maxima is observed.

137. (d)

$$\text{Nullity of } A = \text{No. of Columns of } A - \rho(A)$$

If Nullity of $A \neq 0$ then $\rho(A) < \text{order of } A$

$$\therefore \det A = 0$$

$$\Rightarrow \rho(A) < n.$$

136. (d)

$$A \cdot \vec{V} = \lambda \cdot \vec{V}$$

$$\begin{bmatrix} \omega & 2 & x \\ 1 & -3 & 0 \\ y & -1 & z \end{bmatrix} \begin{bmatrix} 4 \\ 4 \\ 1 \end{bmatrix} = \lambda \cdot \begin{bmatrix} 4 \\ 4 \\ 1 \end{bmatrix}$$

$$\begin{bmatrix} P \\ -8 \\ q \end{bmatrix} = \lambda \cdot \begin{bmatrix} 4 \\ 4 \\ 1 \end{bmatrix}$$

(P and q are unknown)

$$4 \cdot \lambda = -8$$

$$\lambda = -2$$

138. (a)

$$E_1 \rightarrow \text{Event of selection of fair win } P(E_1) = \frac{1}{3}$$

$$E_2 \rightarrow \text{Event of selection of two headed coin } P(E_2) = \frac{2}{3}$$

$A \rightarrow \text{Event of getting both times head}$

We require,

$$\begin{aligned} P(E_2/A) &= \frac{P(E_2)P(A/E_2)}{P(E_1)P(A/E_1) + P(E_2)P(A/E_2)} \\ &= \frac{\frac{1}{3} \times 1 \times 1}{\left(\frac{2}{3} \times \frac{1}{2} \times \frac{1}{2}\right) + \left(\frac{1}{3} \times 1 \times 1\right)} = \frac{2}{3} \end{aligned}$$

139. (c)

$$\frac{df}{dx} = \cos|x| \times \frac{|x|}{x}$$

at

$$x = \frac{-\pi}{4}$$

$$\frac{df}{dx} = \cos\left|\frac{-\pi}{4}\right| \times -1 = \frac{-1}{\sqrt{2}}$$

140. (a)

$$\nabla\phi = y^2 i + (2xy + z^3) j + 3yz^2 k$$

$$\nabla\phi|_{(2,-1,1)} = i - 3j - 3k$$

Given,

$$\vec{n} = i + 2j + 2k,$$

$$\hat{n} = \frac{i + 2j + 2k}{3}$$

$$\therefore \text{Directional derivative} = (\nabla\phi)_p \cdot \hat{n} = \frac{1}{3}(1 - 6 - 6) = \frac{-11}{3}$$

141. (b)

$$\frac{\sin z}{z^3} = \frac{1}{z^3} \left[z - \frac{z^3}{3!} + \frac{z^5}{5!} \dots \right]$$

$$= \frac{1}{z^2} - \frac{1}{3!} + \frac{1}{5!} z^2 \dots$$

$$\therefore z = 0 \text{ is a pole of order 2.}$$

143. (b)

$$A \odot B \odot C = A \oplus B \oplus C$$

144. (d)

The discrete time convolution follows associative commutative and distributive properties.

145. (a)

In CSI thyristor is subjected to large reverse voltage upto $-V$. Hence GTO cannot be used in CSI.

146. (a)

The reactance of bundle conductors is reduced because the self GMD of the conductors is increased

and as we know reactance $= K \ln \frac{\text{GMD}}{\text{GMR}}$ and as GMR is increased the reactance is reduced.

Self GMD is also called as geometrical mean radius (GMR).

147. (a)

Due to positive temperature coefficient of resistance, MOSFETs are best suitable for parallel operation.

148. (b)

For parallel resonance circuit,

$$Q = R \sqrt{\frac{C}{L}} \text{ and } \omega = \frac{1}{\sqrt{LC}}$$

So, Q increases as R increases.

149. (c)

Addition of open loop poles shifts the root locus towards the imaginary axis and the system response becomes more oscillatory.

150. (a)

The power factor angle,

$$\phi = \cos^{-1}(\text{p.f.})$$

As power factor decreases, power factor angle increases and since,

angular deflection $\theta \propto VI \cos \phi$

$\theta \rightarrow 0$ as pf decreases.

