



GATE 2026

Electronics Engineering

Forenoon Session

**Memory Based
Questions & Solutions**

Exam held on 15-02-2026

MADE EASY Corporate Office:

44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016

Centres : Delhi, Hyderabad, Jaipur, Bhopal, Pune | www.madeeasy.in | Ph: 9021300500



GET UPTO

100%

SCHOLARSHIP

NATIONAL SCHOLARSHIP TEST **NST-2**



Scan to register

Test Mode : **Online**

Last date to Register :

20 FEB

Test Date :

22 FEB

For details, visit : nst.madeeasy.in

For **ESE 2027** & **GATE 2027**

Offline Batches

Delhi	19 Feb & 5 Mar 2026
Bhopal	19 Feb & 16 Mar 2026
Jaipur	9 Mar 2026
Hyderabad	20 Feb & 19 Mar 2026
Pune	26 Feb 2026

Live-Online Batches

20 Feb 2026 &
11 Mar 2026

Admissions Open

More Batches to be
announced soon.



Delhi

Ph : 9021300500

Hyderabad

Ph : 9440695415

Bhopal

Ph : 7290068507

Jaipur

Ph : 7290068512

Pune

Ph : 7290068508



Web : www.madeeasy.in



Helpline : 9021300500

If $AB = 2.5$, $BC = 1$, $CD = DE = 2$ and $EF = FC = 3$, then the ratio of area of land (L) and to water (W) is _____


- (a) 0.75 (b) 0.25
 (c) 0.45 (d) 1.00

Ans. (a)

$$\begin{aligned}
 AB &= r_1 = 2.5, & AC &= r_2 = 3.5 \\
 AD &= r_3 = 5.5, & AE &= r_4 = 7.5 \\
 AF &= r_5 = 10.5, & AG &= r_6 = 13.5 \\
 L &= L_1 + L_2 + L_3 \\
 &= \pi r_1^2 + \pi(r_3^2 - r_2^2) + \pi(r_5^2 - r_4^2) \\
 &= \pi(2.5)^2 + \pi(5.5^2 - 3.5^2) + \pi(10.5^2 - 7.5^2) \\
 &= 78.25\pi \\
 W &= W_1 + W_2 + W_3 \\
 &= \pi(r_2^2 - r_1^2) + \pi(r_4^2 - r_3^2) + \pi(r_6^2 - r_5^2) \\
 &= \pi(3.5^2 - 2.5^2) + \pi(7.5^2 - 5.5^2) + \pi(13.5^2 - 10.5^2) \\
 &= 104\pi \\
 \frac{L}{W} &= \frac{78.25\pi}{104\pi} = 0.75
 \end{aligned}$$

End of Solution

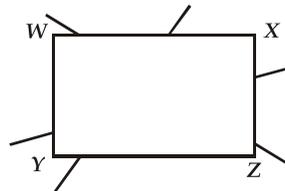4. Find the remaining part of the given diagram:



- (a) (b) (c) (d)

Ans. (a)

End of Solution


GENERAL ENGLISH

5. Find the antonym of nocturnal.
- (a) normal (b) abnormal
 (c) diurnal (d) exceptional

Ans. (c)

ANALOG CIRCUITS

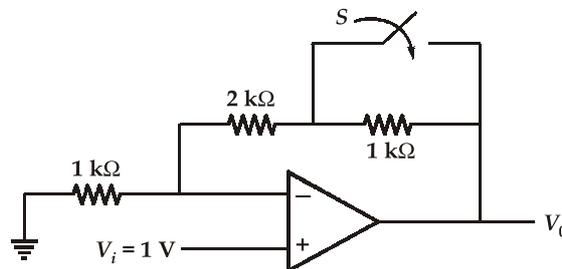6. Consider the op-amp shown in figure below:



If V_0 is 'x' when switch is open after closed the switch, the output V_0 is

- (a) x (b) $\frac{3x}{4}$
 (c) $\frac{x}{2}$ (d) $2x$

Ans. (b)

Given, $V_{01} = x$

$$\text{Switch open} = V_{01} = \left(1 + \frac{3}{1}\right) \times 1 = 4 \text{ V} = x$$

$$\text{Switch closed} = V_{02} = \left(1 + \frac{2}{1}\right) \times 1 = 3 \text{ V}$$

$$\frac{V_{02}}{V_{01}} = \frac{3}{4}$$

$$V_{02} = \frac{3}{4} \times V_{01}$$

$$V_{02} = \frac{3}{4} x$$

End of Solution



Announcing
**Classroom Courses &
Live-Online Courses** for

**GATE
2027**

**ESE
2027**

Salient Features :

- ✓ Classes by experienced & renowned faculties.
- ✓ Systematic subject sequence & timely completion.
- ✓ Comprehensive & updated books (Optional).
- ✓ Efficient teaching with comprehensive coverage.
- ✓ Regular performance assessment through class tests.
- ✓ Facility for doubt removal.
- ✓ Concept practice through workbook solving.
- ✓ Exam oriented learning ecosystem.
- ✓ Proper notes making & study concentration.
- ✓ Similar teaching pedagogy in offline & online classes.



**Classroom Courses
at Delhi**

**19 Feb 2026 &
05 Mar 2026**



**Live-Online
Courses**

**20 Feb 2026 &
11 Mar 2026**



Scan to enroll

Streams: CE, ME/PI, EE, EC/IN, CS

Admissions Open | More batches to be announced in Apr, May & June

Delhi Centre : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500


MADE EASY Centres : Delhi | Bhopal | Hyderabad | Jaipur | Pune www.madeeasy.in

$$I = \frac{6-2}{20\text{ K}} = \frac{4}{20\text{ K}} = 0.2\text{ mA}$$

$$\begin{aligned} V_{0\text{ max}} &= I \times 10\text{ K} + 2\text{ V} \\ &= 0.2\text{ mA} \times 10\text{ K} + 2\text{ V} \\ &= 4\text{ V} \end{aligned}$$


End of Solution

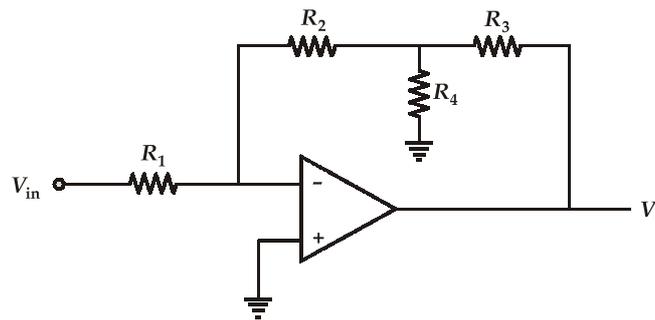11. Consider the op-amp circuit shown below:



If $R_1 = R_2 = R_3 = R_4 = 50\text{ k}\Omega$, then the magnitude of gain is _____.

Ans. (3)

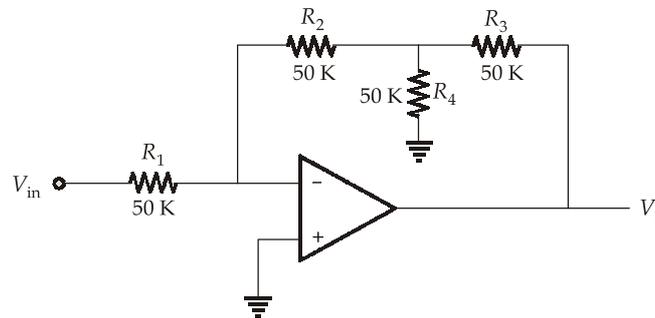

$$\begin{aligned} \frac{V_0}{V_i} &= \frac{-R_2}{R_1} \left[1 + \frac{R_3}{R_2} + \frac{R_3}{R_4} \right] \\ &= \frac{-50\text{ K}}{50\text{ K}} \left[1 + \frac{50\text{ K}}{50\text{ K}} + \frac{50\text{ K}}{50\text{ K}} \right] \\ &= -1[1 + 1 + 1] \\ &= -3 \end{aligned}$$

Hence, $\left| \frac{V_0}{V_i} \right| = 3$

End of Solution

COMMUNICATION SYSTEMS

12. For a 16 QAM system bit rate $R_b = 4$ Mbps. Find minimum BW (in MHz) of the system is _____.

Ans. (1)

$$\text{Minimum transmission BW} = \frac{R_b}{\log_2 M}$$

$$\text{Minimum BW} = \frac{4 \times 10^6}{\log_2 16} = 10^6 \text{ Hz} = 1 \text{ MHz}$$

End of Solution

13. If $\frac{E_b}{N_0} = 8.4$ dB, find probability of error for QPSK modulation.

- (a) 10^{-4} (b) 10^{-6}
(c) 10^{-2} (d) 10^{-3}

Ans. (c)

Given, $\frac{E_b}{N_0} = 8.4$ dB

We know that, $\text{erfc}(u) = \frac{e^{-u^2}}{u\sqrt{\pi}}$

$$\begin{aligned} P_e &= Q\left(\sqrt{\frac{2E_b}{N_0}}\right) \\ &= \frac{1}{2} \text{erfc}\left(\sqrt{\frac{E_b}{N_0}}\right) = \frac{1}{2} \text{erfc}(\sqrt{10^{-0.84}}) \\ &= \frac{1}{2} \text{erfc}(6.91) = \frac{1}{2} \frac{e^{-(6.91)^2}}{6.91 \times \sqrt{\pi}} = 0.01 = 10^{-2} \end{aligned}$$

End of Solution

14. Find the channel capacity of a system using Shannon Hartley Law of a signal whose bandwidth is 1 MHz, signal power is -80 dBm, $kT = -174$ dBm/Hz.

- (a) $C = B$ (b) $C = 2B$
(c) $C > 3B$ (d) $C < B$

Ans. (c)

Given, $B = 1$ MHz, $C = B \log_2 \left[1 + \frac{10^{-8} \times 10^{-3}}{KT B} \right]$ ($\because S = -80$ dBm = $10^{-8} \times 10^{-3}$)

$$= B \log_2 \left[1 + \frac{10^{-8} \times 10^{-3}}{KT B} \right] = B \log_2 \left[1 + \frac{10^{-11}}{10^{-17.4} \times 10^{-3} \times 10^6} \right]$$



Foundation Courses for

ESE 2027

GATE 2027



Tablet Course

- Pre-loaded full fledged recorded course
- Android OS based 10.5 inch Samsung tablet
- Internet access does not required
- Classes by senior faculties
- Validity: 2 Years
- Learn at your own pace
- Tablet is reusable for normal purpose after validity expires



Recorded Course

- Recorded Course
- Full fledged holistic preparation
- Classes by senior faculties
- Lectures can be watched anytime/ anywhere
- Courses are accessible on PC & Mac desktops/laptops/android/ iOS mobile devices.
- Learn at your own pace
- Validity: 1 year
- Internet connection required

Teaching Hours

- ✓ **GATE Exclusive** • CE, ME, EE : 800 to 900 Hrs.
• EC, IN, CS, CH : 650-700 Hrs.
- ✓ **GATE + ESE** • CE, ME, EE, EC : 1100 to 1200 Hrs.
- ✓ **GATE + SES-GS** • CE, ME, EE : 1150 to 1250 Hrs. ✓ **GATE + ESE + SES-GS** • CE, ME, EE, EC : 1450 to 1550 Hrs.
• EC, IN, CS, CH : 950-1050 Hrs.

Note : State Engineering Services Examination. • The course is offered with a validity options of 1 year and 2 years.

Low Cost EMI Facility Available

Admissions open



Scan to enroll

Delhi Centre : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

MADE EASY Centres : Delhi | Bhopal | Hyderabad | Jaipur | Pune

www.madeeasy.in

$$\begin{aligned}
 &= B \log_2 \left[1 + \frac{10^{-11}}{10^{-14.4}} \right] \\
 &= 1 \text{ M} \log_2 \left[1 + \frac{10^{-11}}{10^{-14.4}} \right] = 1 \text{ M} \log_2 [1 + 10^{3.4}] \\
 &= 11.29 \text{ Mbps}
 \end{aligned}$$

∴ $C > 3B$ would satisfy the above result.

End of Solution

15. **Given, (7, 4, 1) Hamming code and BER = 0.1**
Prove that decoder will fail to decode received codeword properly will be

Ans. (0.15)

Hamming code can correct upto one error only.

Probability of decoding received code word properly will be

$$\begin{aligned}
 \Rightarrow P_c &= P(\text{no error}) + P(\text{1-bit error}) \\
 &= {}^7C_0(0.1)^0(0.9)^7 + {}^7C_1(0.1)^1(0.9)^6
 \end{aligned}$$

∴ When n-bits transmitted, probability of getting error in r-bits will be ${}^nC_r P^r(1-P)^{n-r}$

$$\therefore P_c \cong 0.85$$

Probability of decoder failed to decode received codeword properly will be

$$\begin{aligned}
 P_e &= 1 - P_c \\
 &= 1 - 0.85 \\
 &= 0.15
 \end{aligned}$$

End of Solution

COMPUTER ORGANIZATION

16. **If the starting address of a 256KB memory is 2500H, then find the address of the final location.**

Ans. (424FFH)

Given, Memory capacity = 256 kB

Starting address = 2500 H

Final address = ?

Final address - Initial address + 1 = Capacity of memory

$$x - 2500 \text{ H} + 1 = 40000 \text{ H}$$

$$x = 40000 \text{ H} - 1 + 2500 \text{ H}$$

$$3\text{FFFFH}$$

$$x = +2500\text{H}$$

$$\underline{424\text{FFH}}$$

Hence, the final address location is 424FFH.

End of Solution

17. Find the 10's complement of $(47)_{10}$.

Ans. (53)

Using r 's complement = $(r - 1)$'s complement + 1

\therefore 9's complement of $(47)_{10}$

$$\begin{array}{r} 99 \\ -47 \\ \hline 52 \end{array} \text{ i.e., (9's complement)}$$

\therefore 10's complement


$$\begin{array}{r} 52 \\ +1 \\ \hline 53 \end{array}$$

Hence, the 10's complement of $(47)_{10}$ is 53.

End of Solution

CONTROL SYSTEMS

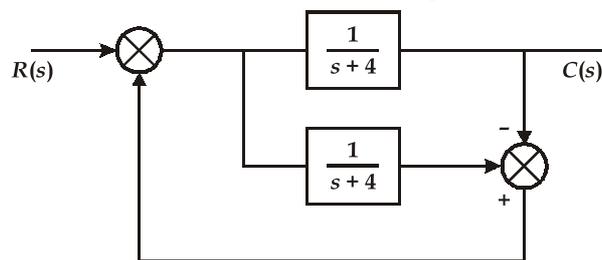18. Consider the closed loop system as shown in figure below:



The transfer function, $\frac{C(s)}{R(s)}$ of the system is

- | | |
|------------------------|-----------------------|
| (a) $\frac{1}{s+4}$ | (b) $\frac{s+4}{s+5}$ |
| (c) $\frac{1}{s^2+8s}$ | (d) $\frac{2}{s+4}$ |

Ans. (a)

Using Mason's gain formula, we get

$$\frac{C(s)}{R(s)} = \frac{\frac{1}{s+4}}{1 - \left[-\frac{1}{s+4} + \frac{1}{s+4} \right]} = \frac{1}{s+4}$$

End of Solution




Conventional Questions Practice Programme for ESE Mains 2026



Scan to enroll

Offline **Live-Online**

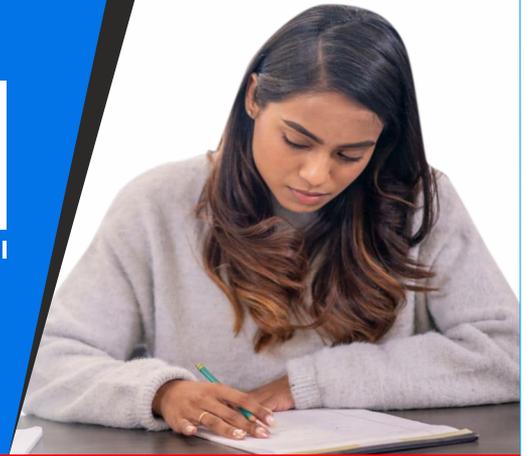- Batches Starting from 24 Feb, 2026
- Admissions Open



ESE Mains Test Series (15 tests) Starting from 15 March, 2026

Note : Solo Mains Test Series is also available.



Scan to enroll

This conventional course is offered in offline mode at Delhi Centre.

Key Features :

- Classes by MADE EASY senior faculties
- Beneficial to improve answer writing and presentation skills
- Updated Main exam workbooks containing diverse practice questions
- Highly useful for State Engineers Service examinations also.
- In-depth analysis and discussion on probable & potential questions
- Develops numerical questions solving techniques
- Weekly dynamic test series on every Sunday aligned with the course (optional).

Duration: 300-350 Hrs | **Streams:** CE, ME, EE, E&T

Fee Structure :

ESE Main Course Fees

- MADE EASY students : ₹13,000 + GST
- Non-MADE EASY students : ₹15,000 + GST

Main Course + Test Series Fee

- MADE EASY students : ₹16,500 + GST
- Non-MADE EASY students : ₹18,500 + GST

Test Series Fee

For all students : ₹4,500 + GST


Delhi Centre : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

MADE EASY Centres : Delhi | Bhopal | Hyderabad | Jaipur | Pune

www.madeeasy.in

DIGITAL CIRCUITS

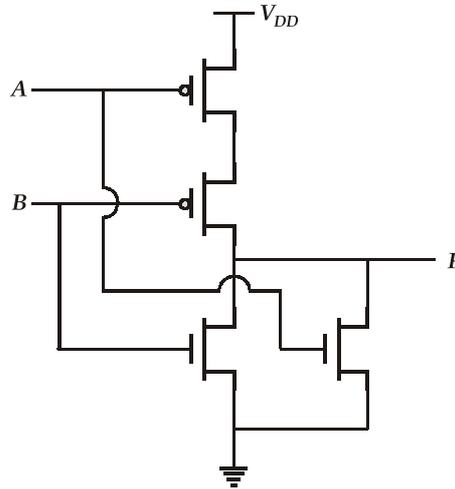23. Find the logic function performed by the below circuit:



- (a) NAND
- (b) NOR
- (c) AND
- (d) OR


Ans. (b)

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0


∴ The given circuit performs NOR operation.

End of Solution

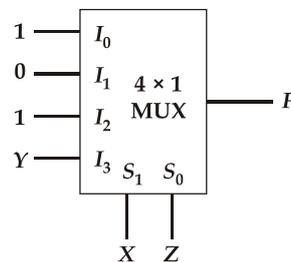24. Find the output of the following logic circuit.




Ans. $(XY + \bar{Z})$
 Given,

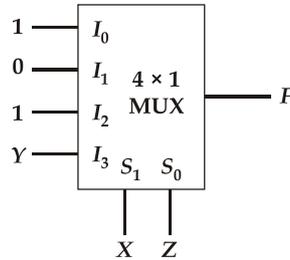

$$\begin{aligned}
 F &= \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3 \\
 &= \bar{X} \bar{Z}(1) + \bar{X} Z(0) + X \bar{Z}(1) + X Z Y \\
 &= \bar{X} \bar{Z} + X \bar{Z} + X Z Y \\
 &= \bar{Z}[X + \bar{X}] + X Z Y \\
 F &= \bar{Z} + X Z Y \\
 F &= X Y + \bar{Z}
 \end{aligned}$$

End of Solution

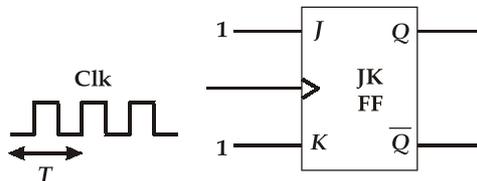25. Consider the JK flip-flop shown below,



where, $T = 10$ clocks per second. Find the output frequency (in Hz) of flip-flop.

Ans. (5)

When, $J = K = 1$,
 Then, JK-FF operate in toggle mode.

$$\therefore f_{out} = \frac{f_{in}}{2} = 5 \text{ Hz}$$

End of Solution

26. The number of flip-flops required to design MOD-64 ripple counter using

- (a) 4
- (b) 5
- (c) 6
- (d) 7

[MSQ]

Ans. (c, d)

Number flip-flops required should be

$$n \geq \log_2 M$$

where, M = Number of states.

Here, $M = 64$

Hence, $n \geq \log_2^{64}$

$$n \geq \log_2^{2^6}$$


$$n \geq 6$$

$$n = 6 \text{ and } 7$$

Hence, number of flip-flops required should be 6 or 7.

End of Solution

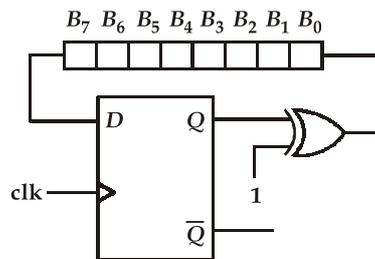27. The logic circuit shown below is composed of Left Shift Register (LSR) and D flip-flop.



Assuming all the circuits initially relaxed.

Find the output after 5 clock pulse.

Ans. (00011111)

CLK	Q	B_7	B_6	B_5	B_4	B_3	B_2	B_1	B_0
0	0	0	0	0	0	0	0	0	0
1 st	0	0	0	0	0	0	0	0	1
2 nd	0	0	0	0	0	0	1	1	1
3 rd	0	0	0	0	0	1	1	1	1
4 th	0	0	0	0	1	1	1	1	1
5 th	0	0	0	1	1	1	1	1	1

Hence, the output after 5 clock pulses is 0 0 0 1 1 1 1 1.

End of Solution

28. Find the simplified boolean expression for the following logic function

$$f[W, X, Y, Z] = \Sigma m(0, 2, 5, 7, 8, 10, 13, 15)$$

(a) $XZ + WXY + W\bar{X}\bar{Z} + \bar{W}XY\bar{Z}$

(b) $\bar{X}\bar{Z} + WXY + W\bar{X}\bar{Z} + \bar{W}XY\bar{Z}$


(c) $\bar{X}\bar{Z} + XZ + WY\bar{Z}$

(d) $\bar{X}\bar{Z} + XZ + WXY$

Ans. (c, d)

Given, $f(W, X, Y, Z) = \sum m(0, 2, 5, 7, 8, 10, 13, 14, 15)$

By using 4-variable K-map

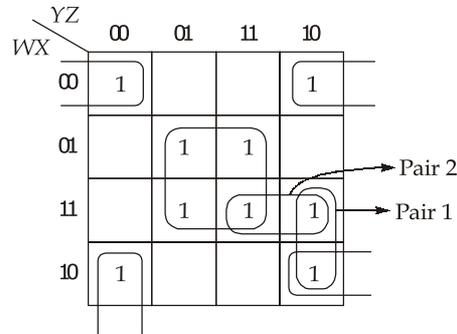

By forming pair 1, $f = XZ + \bar{X}Z + WY\bar{Z}$

If we form pair (2), $f = XZ + \bar{X}\bar{Z} + WXY$

End of Solution

ELECTROMAGNETICS

29. Find the cut-off frequency (in GHz) of rectangular waveguide supporting TE_{10} mode having dimensions 0.28×0.14 inches.

Ans. (21.09)

$$f_c|_{TE_{10}} = \frac{c}{2a} = \frac{3 \times 10^{10}}{2 \times 0.28 \times 2.54} \quad [\because 1 \text{ inch} = 2.54 \text{ cm}]$$

$$= 21.09 \text{ GHz}$$

End of Solution

30. Identify the type of polarisation for the EM value given,

$$E = E_0 [\cos(\omega t + kz)\hat{a}_x + \sin(\omega t + kz)\hat{a}_y]$$

- (a) Left circularly polarised
- (b) Right circularly polarised
- (c) Linearly polarised
- (d) Left elliptically polarised


Ans. (b)

$$\bar{E} = E_0 \cos(\omega t + kz)\hat{a}_x + E_0 \sin(\omega t + kz)\hat{a}_y$$

At $z = 0$, $\bar{E} = E_0 \cos \omega t + \hat{a}_x + E_0 \sin \omega t \hat{a}_y$; circularly polarized

At $t = 0$, $\omega t = 0$, $\bar{E} = E_0 \hat{a}_x$

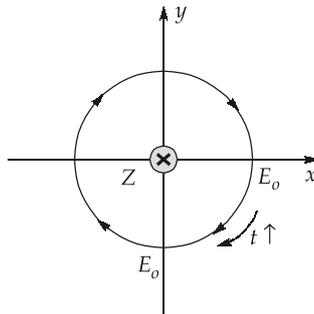At $t = \frac{T}{4}$, $\omega t = \frac{\pi}{4}$, $\bar{E} = E_0 \hat{a}_y$



End of Solution

ELECTRONIC DEVICES AND CIRCUITS

31. If N_d decreases linearly from $2 \times 10^{17} \text{ cm}^{-3}$ at $x = 1 \text{ } \mu\text{m}$ to $1 \times 10^{16} \text{ cm}^{-3}$ at $x = 4 \text{ } \mu\text{m}$. The region between $x = 1 \text{ } \mu\text{m}$ and $x = 4 \text{ } \mu\text{m}$ is labelled "linear". If electron mobility $\mu_n = 1400 \text{ cm}^2/\text{v-s}$, thermal voltage,

$$V_t = \frac{kT}{q} = 25 \text{ mV (at } T = 300 \text{ K)}$$

Then $J_{n(\text{diff})}$ _____ (in A/mm^2).

Ans. (35.47)


$$D_N = \mu_N \times V_T = 35 \text{ cm}^2/\text{sec}$$

$$\frac{dn}{dx} = \frac{\Delta n}{\Delta x} = \frac{2 \times 10^{17} - 1 \times 10^{16}}{3 \times 10^{-4} \text{ cm}} = 6.33 \times 10^{20} \text{ cm}^{-4}$$

$$J_{\text{Diff}} = qD_N \times \frac{dn}{dx} = 1.6 \times 10^{-19} \times 35 \times 6.33 \times 10^{20} \\ = 3547 \text{ A/cm}^2 = 35.47 \text{ A/mm}^2$$

End of Solution

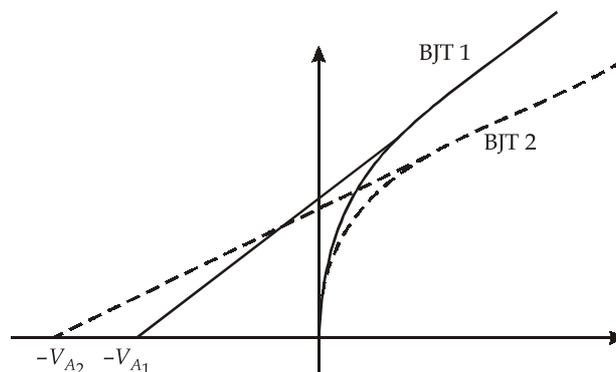32. The characteristics curve of two transistors are given as shown below:



If the early voltage of BJT 1 is V_{A1} and the early voltage of BJT 2 is V_{A2} , then which of the following options is/are correct?



POSTAL PACKAGES

- CSE
- ESE
- GATE
- PSUs
- SSC-JE
- RRB-JE
- UPPSC-AE
- BPSC-AE
- MPSC
- Other State Engineering Exams

Salient Features of Postal Study Package

Our Postal Book Packages cater to the needs of college-going students, working professionals, and individuals unable to join classroom courses. These books, offered by MADE EASY, are designed to be compact, comprehensive, and easily understandable. We have put our efforts to ensure error-free content, incorporating smart and shortcut techniques specifically tailored for solving numerical problems.

- Complete syllabus coverage aligned with latest pattern/syllabus.
- Detailed theory and practice exercises.
- Latest and updated study material
- Step by step solutions
- Ample no. of practice questions with PYQs.
- Emphasis on technical and non technical sections both.
- Subject-wise theory objective and conventional practice sets.
- Proven track record of student success.

For online purchase, visit :

www.madeeasypublications.org | Helpline : 8860378004

For offline purchase, visit in-person at any MADE EASY center.
Books will be sent to your provided address.




Scan to enroll

Address : 44-A/4, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016

9021300500


www.madeeasypublications.org

37.

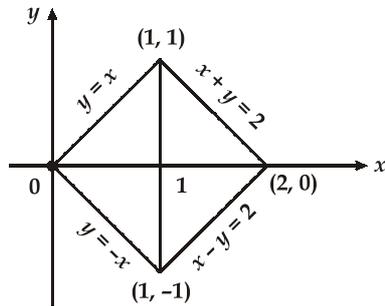

The value of $\iint_R (x^2 + y^2 - 1) dx dy$ is _____.

Ans. (0.66)

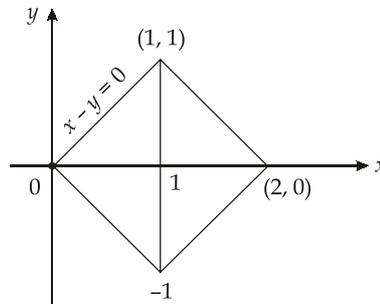

$$I = \iint_R (x^2 + y^2) dx dy - \iint_R dx dy$$

$$I = I_1 - I_2$$

$$I_1 = \int_0^1 \int_{-x}^x (x^2 + y^2) dy dx + \int_1^2 \int_{-(2-x)}^{2-x} (x^2 + y^2) dy dx$$

$$= 2 \int_0^1 \left(x^2 y + \frac{y^3}{3} \right)_0^x dx + 2 \int_1^2 \left(x^2 y + \frac{y^3}{3} \right)_0^{2-x} dx$$

$$= 2 \int_0^1 \frac{4}{3} x^3 dx + 2 \int_1^2 \left(x^2(2-x) + \frac{(2-x)^3}{3} \right) dx$$

$$= \frac{8}{3} \left(\frac{1}{4} \right) + 2 \left[\frac{2x^3}{3} - \frac{x^4}{4} + \frac{1}{3} \frac{(2-x)^4}{-4} \right]_1^2$$

$$= \frac{8}{12} + 2 \left[\left(\frac{16}{3} - 4 - \frac{1}{2}(0) \right) - \left(\frac{2}{3} - \frac{1}{4} - \frac{1}{12} \right) \right]$$

$$= \frac{2}{3} + 2 \left[\left(\frac{4}{3} - \frac{1}{3} \right) \right]$$

$$= \frac{2}{3} + 2$$

$$I_1 = \frac{8}{3}$$

$I_2 =$ Area of square

$$\therefore I = I_1 - I_2$$

$$I = \frac{8}{3} - \sqrt{2} \times \sqrt{2}$$

$$I = \frac{8}{3} - 2$$

$$I = \frac{2}{3}$$

End of Solution

38. The value of $\oint_c \frac{(z+4)^2}{(z-i)(z-2)} dz$

where $c : |z - 2 - i| = \frac{1}{3}$

Ans. (0)

$$\oint_c \frac{(z+4)^2}{(z-i)(z-2)} dz, \quad c : |z - 2 - i| = \frac{1}{3}$$

Poles are given by,

$$(z - i)(z - 2) = 0$$

$\Rightarrow z = i, 2$ are simple poles.

$z = i$

$$c : |i - 2 - i| = |-2| > \frac{1}{3} \Rightarrow \text{Lies outside 'c'}$$

$z = 2$

$$c : |2 - 2 - i| = |-i| = 1 > \frac{1}{3} \Rightarrow \text{lies outside 'c'}$$

\therefore Both lies outside 'c'.

By Cauchy theorem,

$$\int_c f(z) dz = 0$$

End of Solution

MADE EASY students top in ESE 2025

4 Streams 4 Toppers
all 4 MADE EASY Students

39 selections
in Top 10

434 selections out of
458 Vacancies (95% Selections)

CE 9 in Top 10	1 AIR MOHAMMAD SHAQUIB Live Online Foundation Course	2 AIR PRAKHAR SHRI Classroom Foundation Course	3 AIR ARJUN SHARMA Mains Online Course	4 AIR BOLLA U NANDAN Classroom Foundation Course	5 AIR KESHAV Test Series & IGP	7 AIR TUSHAR AGGARWAL Classroom Foundation Course	8 AIR AYUSH JAIN Classroom Foundation Course	9 AIR ADITYA P SINGH Test Series & IGP	10 AIR PUSHPENDRA RATHORE Test Series & IGP	
ME 10 in Top 10	1 AIR NIMESH CHANDRA Classroom Foundation Course	2 AIR ASHOK KUMAR Classroom Foundation Course	3 AIR HARI SINGH Mains Online Course	4 AIR SIDDESH RAO GS Online Course	5 AIR GOLLANGI SATEESH Mains Online Course	6 AIR AVINASH VERMA Mains Online Course	7 AIR PRASHANT SINGH Mains Offline Course	8 AIR MONU KUMAR Classroom Foundation Course	9 AIR NIKHIL KUMAR SAHA Test Series & IGP	10 AIR AMIT KUMAR SINGH Classroom Foundation Course
EE 10 in Top 10	1 AIR RAJAN KUMAR Classroom Foundation Course	2 AIR VISHNU SAINI Live Online Foundation Course	3 AIR OMPRAKASH RAJPUT Classroom Foundation Course	4 AIR TUSHAR CHAUDHARY Classroom Foundation Course	5 AIR RAM KUMAR Test Series & IGP	6 AIR PUNIT MEENA Classroom Foundation Course	7 AIR JYOTI K. PANDA Classroom Foundation Course	8 AIR D A SAI RAM REDDY Test Series & IGP	9 AIR DHURUV KAWAT Classroom Foundation Course	10 AIR AKSHIT PARASHARI Live Online Foundation Course
E&T 10 in Top 10	1 AIR UTKARSH PATHAK Live Online Foundation Course	2 AIR RAJESH TIWARI Live Online Foundation Course	3 AIR PRASHANT LAVANIA Classroom Foundation Course	4 AIR PRADEEP SHUKLA Mains Online Course	5 AIR ASHISH SINGH PATEL Classroom Foundation Course	6 AIR TANYA TYAGI Mains Online Course	7 AIR PALAK MISHRA Mains Online Course	8 AIR HAYAT ALI Classroom Foundation Course	9 AIR VIDHU SHREE Live Online Foundation Course	10 AIR RAM PAL SINGH Classroom Foundation Course

MADE EASY students top in GATE 2025

5 All India Rank 1
(CE, ME, IN, ES & EE)

45 Selections
in Top 10

399 Selections
in Top 100

1 AIR CE Abhay Singh Classroom Course	1 AIR ME Rajneesh Bijarniya Classroom Course	1 AIR EE Pradip Chauhan Test Series	1 AIR IN Kailash Goyal Classroom Course	1 AIR ES Yash Jain Classroom Course	2 AIR CE Harshvardhan Singh Classroom Course	2 AIR ME Gollangi Sateesh Online Course	2 AIR EE Kailash Goyal Classroom Course	2 AIR EC Ankush Philip John Postal Package & Test Series	
2 AIR IN S. Bhattacharya Test Series	2 AIR ES Jitesh Choudhary Classroom Course	2 AIR ES Tarun Yadav Classroom Course	3 AIR CE Pankaj Meena Classroom Course	3 AIR ME Nimesh Chandra Classroom Course	3 AIR PI Aditya Kr. Prasad Classroom Course	3 AIR XE Rohan Kr. Biswal Test Series	5 AIR CE Kartik Pokhriyal Classroom Course		
5 AIR PI Kuldeep Singh Naruka Classroom Course	5 AIR IN Sachin Yadav Test Series	5 AIR EC M. M. Nafeez Test Series	5 AIR ES Sachin Kumar Classroom Course	6 AIR PI Kaushal Kr. Kaushik Online Course	6 AIR CE Shivnand Chaurasia Online Course	6 AIR CE Nimish Upadhyay Online Course	6 AIR EE Puneet Soni Test Series	6 AIR EE Shivam Kr. Gupta Test Series	
6 AIR EC Pentela J. Bhavani Test Series	6 AIR IN Utkarsh P. Patil Classroom Course	7 AIR PI Waleed Shaikh Test Series	7 AIR ME Abhinn Online Course	7 AIR IN Dev J. Patel Test Series	7 AIR ES Ankit Kumar Classroom Course	8 AIR ME Goutam Kumar Test Series	9 AIR CE Tarun Yadav Classroom Course	9 AIR CS Omhari Test Series	9 AIR EC Chilukuri S. Charan Test Series
9 AIR XE Apar Harsh Chandra Classroom Course	10 AIR CE Adnan Quasain Classroom Course	10 AIR CE Rahul Singh Online Course	10 AIR ME Ashutosh Kumar Classroom Course	10 AIR ME Jetti Ganateja Test Series	10 AIR ME Muhammed Sinan K Test Series	10 AIR ME Pitchika Kr. Vasu Online Course	10 AIR PI M Gopu Ganesh Test Series	10 AIR EE Neelava Mukherjee Postal Package & Test Series	

Course-wise details of "top 100 rank holders of GATE 2025" and "selected candidates of ESE 2025 from MADE EASY" are available on our website.

Delhi Centre : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

MADE EASY Centres : Delhi | Bhopal | Hyderabad | Jaipur | Pune

www.madeeasy.in

39. $S_A \cdot \sum_{n=1}^{\infty} \left(\frac{n^2}{2^n} \right)$

$S_B \cdot S_n = 1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \dots + \frac{1}{512}$

Convergent (or) divergent?

- (a) S_A and S_B both are convergent
- (b) S_A convergent and S_B not convergent
- (c) S_A not convergent and S_B convergent
- (d) S_A and S_B are not convergent

Ans. (a)

By n^{th} root test

$$= \lim_{n \rightarrow \infty} \left(\frac{n^2}{2^n} \right)^{1/n}$$

$$= \lim_{n \rightarrow \infty} \frac{n^{2/n}}{2}$$

\therefore Given series is convergent

$$1 + \frac{1}{2} + \frac{1}{4} + \dots + \frac{1}{512}$$

$$S_n = \frac{a(1-r^n)}{1-r}, \quad r = \frac{1}{2}$$


$$S_8 = \frac{1 \left(1 - \left(\frac{1}{2} \right)^8 \right)}{1 - \frac{1}{2}} = \frac{1 - \frac{1}{512}}{\frac{1}{2}} = \frac{511}{256}$$

\therefore It is also convergent.

End of Solution

NETWORK THEORY

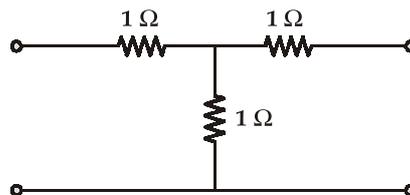40. Find the ABCD parameter of the following two port network




(a) $\begin{bmatrix} -2 & 3 \\ 1 & 2 \end{bmatrix}$

(b) $\begin{bmatrix} 2 & -3 \\ 1 & -2 \end{bmatrix}$

(c) $\begin{bmatrix} 2 & 3 \\ 1 & 2 \end{bmatrix}$

(d) $\begin{bmatrix} -2 & 3 \\ -1 & 2 \end{bmatrix}$

Ans. (c)
 Given, network

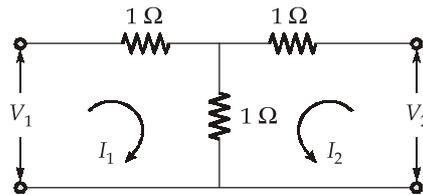

For ABCD parameter,

$$\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$

From the loop 1:

$$V_1 = 2I_1 + I_2 \quad \dots(1)$$

$$V_2 = I_1 + 2I_2 \quad \dots(2)$$

$$I_1 = V_2 - 2I_2 \quad \dots(3)$$

∴

$$V_1 = 2(V_2 - 2I_2) + I_2$$


$$V_1 = 2V_2 - 3I_2 \quad \dots(4)$$

From equation (3) and (4)

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 2 & +3 \\ 1 & +2 \end{bmatrix}$$

End of Solution


41. Find V_0 (in Volts).

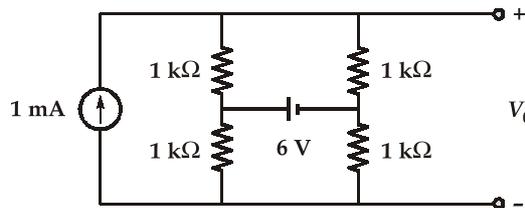


Ans. (1)

By using superposition theorem.

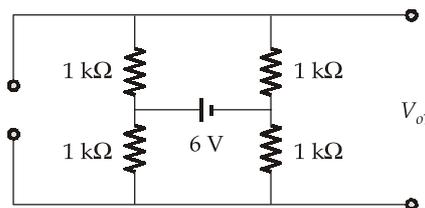
If 6 V source is active and 1 mA current source is open circuit.



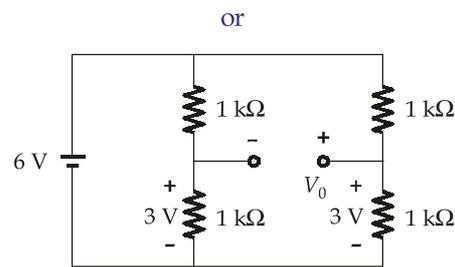

$$\therefore V_{o1} = 3 - 3 = 0 \text{ V}$$

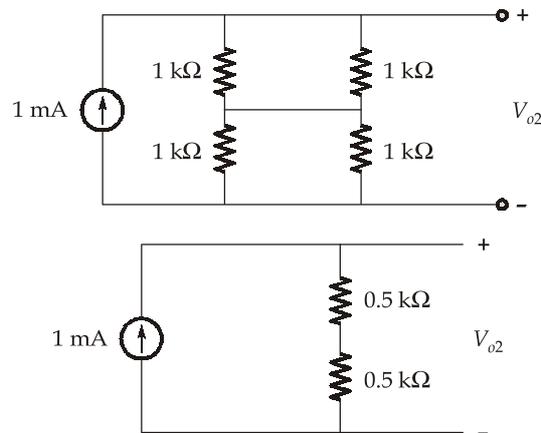If 1 mA current source is active and 6 V voltage source is short circuited.



$$\therefore V_{o2} = \left| \max \right| 1 \text{ k}\Omega = 1 \text{ V}$$


By superposition theorem,

$$V_0 = V_{o1} + V_{o2}$$

$$\therefore V_0 = 0 + 1 = 1 \text{ V}$$

End of Solution

42.

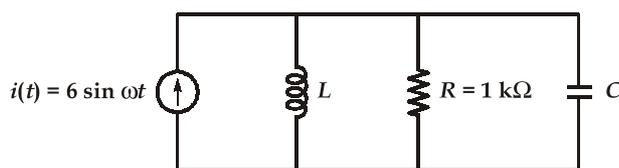

Find Average power (in kW) at resonance.


Ans. (18)

Since the given circuit is in resonance, $I_L + I_C = 0 \text{ A}$

$$\begin{aligned} \text{Power} &= I_{\text{rms}}^2 \times R \\ &= \left(\frac{6}{\sqrt{2}} \right)^2 \times 1 \text{ k}\Omega \\ &= \frac{36}{2} \times 1 \text{ k}\Omega = 18 \text{ kW} \end{aligned}$$

End of Solution

43.

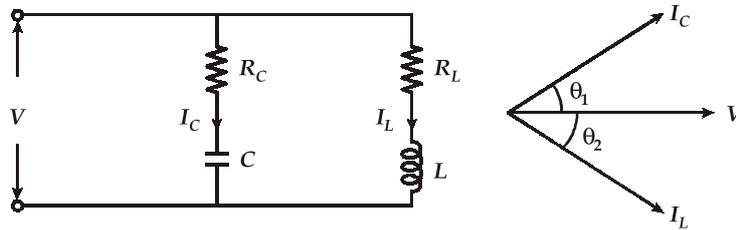

$$\theta_1 + \theta_2 = 90^\circ \text{ at } f = 159.15 \text{ Hz}$$

$$L = 1 \mu\text{H}, C = 1 \mu\text{F}$$

Find $R_L \times R_C$

Ans. (1)

$$\theta_1 = \tan^{-1}\left(\frac{X_C}{R_C}\right) + \tan^{-1}\left(\frac{X_L}{R_L}\right) = 90^\circ$$

$$\tan(A + B) = \frac{\tan A + \tan B}{1 - \tan A \tan B}$$

Here, $\tan A \cdot \tan B = 1$

i.e. $\tan^{-1}\left(\frac{X_C}{R_C}\right) \cdot \tan\left(\frac{X_L}{R_L}\right) = 1$

$$\frac{X_C}{R_C} \cdot \frac{X_L}{R_L} = 1$$

$$\frac{1}{\omega C R_C} \cdot \frac{\omega L}{R_L} = 1$$

i.e. $R_L \cdot R_C = \frac{L}{C}$

$\therefore R_L \cdot R_C = 1$

End of Solution

SIGNALS AND SYSTEMS

44. If $x(t)$ has energy E , then the ratio of energy of $\frac{E[x(t)]}{E[3x(-3t+5)]}$.

(a) 9 (b) $\frac{1}{3}$

(c) $\frac{1}{9}$ (d) 3

Ans. (b)

Energy of signal, $x(t) = E$ joule

$$x(-3t + 5) \rightarrow \frac{E}{3} \text{ joule}$$

47. The impulse-response of an LTI-system is given as $h(t) = e^{-2t} u(t)$. The system is
 (a) causal and unstable (b) causal and stable
 (c) non-causal and unstable (d) non-causal and stable

Ans. (b)

$$\because h(t) = 0, t < 0$$

\therefore System is causal.

Since, $h(t)$ is absolutely, integrable. Therefore, system is stable.

End of Solution

48. Consider a signal $x(t)$ given by

$$x(t) = e^{-2t} u(t)$$

If 99% of energy of $x(t)$ lies within 'B' Hz then the value of B is _____ Hz.

- (a) $\frac{126}{\pi} < B < \frac{128}{\pi}$ (b) $\frac{63}{\pi} < B < \frac{64}{\pi}$
 (c) $B < \frac{63}{\pi}$ (d) None of these

Ans. (b)

$$x(t) \Leftrightarrow X(w) = \frac{1}{2 + jw}$$

$$|X(w)| = \frac{1}{\sqrt{4 + w^2}}$$

For $x(t)$: Energy $\frac{1}{2 \times 2} = \frac{1}{4}$

Given that energy contained in the frequency range " $2\pi B$ " rad/sec is 99% of energy of $x(t)$.

i.e. $\frac{1}{2\pi} \int_{-2\pi B}^{2\pi B} |X(w)|^2 dw = \frac{0.99}{4}$

$$\Rightarrow \frac{1}{2\pi} \times 2 \times \int_0^{2\pi B} \frac{1}{4 + w^2} dw = \frac{0.99}{4}$$

$$\Rightarrow \frac{1}{\pi} \left[\frac{1}{2} \tan^{-1} \left(\frac{w}{2} \right) \right]_0^{2\pi B} = \frac{0.99}{4}$$

$$\frac{1}{\pi} \tan^{-1} \left[\frac{2\pi B}{2} \right] = \frac{0.99}{2}$$

$$\Rightarrow \tan^{-1}(\pi B) = \frac{0.99\pi}{2}$$

$$\Rightarrow \pi B = \tan \left(\frac{0.99\pi}{2} \right) = 63.56$$

$$\Rightarrow B = \frac{63.56}{\pi} = 20.26 \text{ Hz}$$

End of Solution

