



GATE 2026

Electronics Engineering

Forenoon Session

Detailed Solutions

Exam held on 15-02-2026

MADE EASY Corporate Office:

44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016

Centres : Delhi, Hyderabad, Jaipur, Bhopal, Pune | www.madeeasy.in | Ph: 9021300500

SECTION - A

GENERAL APTITUDE

- Q.1** Among the following options, the antonym of the word 'nocturnal' is _____.
- (a) normal (b) diurnal
(c) abnormal (d) exceptional

Ans. (b)

- Nocturnal-means active at night.
- Diurnal-means active during the day.

End of Solution

- Q.2** The statements (S1), (S2), and (S3) pertain to the scores obtained by students in an exam. The maximum possible marks in the exam is 150.
- (S1) The highest score is 100.
(S2) The fourth highest score is 76.
(S3) There are at least four students whose scores are within 25 of each other.
- Which one of the following options is necessarily correct?
- (a) (S1) and (S2) together imply (S3) (b) (S1) and (S3) together imply (S2)
(c) (S2) and (S3) together imply (S1) (d) (S1) implies (S3)

Ans. (a)

(S1) : Highest score = 100
(S2) : Fourth Highest Score = 76


So, the maximum difference among these four students is

$$100 - 76 = 24$$

Since, $24 \leq 25$, these four students are within 25 marks of each other.
Hence, (S3) must be true.

End of Solution

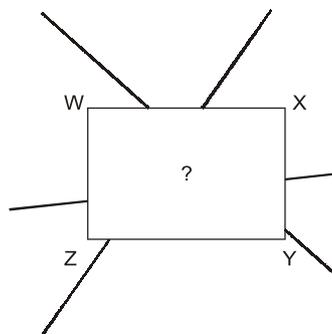- Q.3** The figure below has exactly three intersecting line segments with a rectangular portion WXYZ missing. Which one of the following options P, Q, R, and S is the missing portion WXYZ?





Announcing

Classroom Courses & Live-Online Courses for

**GATE
2027**

**ESE
2027**

Salient Features :

- ✓ Classes by experienced & renowned faculties.
- ✓ Systematic subject sequence & timely completion.
- ✓ Comprehensive & updated books (Optional).
- ✓ Efficient teaching with comprehensive coverage.
- ✓ Regular performance assessment through class tests.
- ✓ Facility for doubt removal.
- ✓ Concept practice through workbook solving.
- ✓ Exam oriented learning ecosystem.
- ✓ Proper notes making & study concentration.
- ✓ Similar teaching pedagogy in offline & online classes.



**Classroom Courses
at Delhi**

**19 Feb 2026 &
05 Mar 2026**



**Live-Online
Courses**

**20 Feb 2026 &
11 Mar 2026**



Scan to enroll

Streams: CE, ME/PI, EE, EC/IN, CS

Admissions Open | More batches to be announced in Apr, May & June

Delhi Centre : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

MADE EASY Centres : Delhi | Bhopal | Hyderabad | Jaipur | Pune www.madeeasy.in

Q.5 The following observation is made about the scores obtained by 100 students in an exam: 'For each student, there exists another student in the class such that their scores are at most ten marks away.'

If the above statement is **false**, which one of the following statements is necessarily true?

- (a) For each student, the scores of all the other students are more than 10 marks away.
- (b) There exists at least one student in the class for whom the scores of all the other students are more than 10 marks away.
- (c) There is exactly one student in the class for whom the scores of some students are more than 10 marks away.
- (d) For each student, the score of exactly one other student is more than 10 marks away.

Ans. (b)

End of Solution

Q.6 Each one of the following clues contains a keyword that is partially filled.

Clue 1: Synonym of recognize (8 letters): _ D _ NT_ FY

Clue 2: A story long enough to fill a book (5 letters): _ _ _ EL

Clue 3: Two of something (6 letters): _ _ _ PLE

Clue 4: A fraction of something, split equally into two parts (4 letters): _ _ _ F

The first letter of each of the keywords can be rearranged to form a four-letter word.

Which one of the options below is a possible choice for the four-letter word?

- (a) CHIN
- (b) COIN
- (c) ITCH
- (d) NOSE

Ans. (a)


① D E N T ① F Y	First letter I
① ② ③ E L	First letter N
① ② ③ P L E	First letter C
① ② ③ F	First letter H

Hence, option (a) CHIN is correct.

End of Solution

Q.7 Three children P, Q, R and two grown-ups X, Y play a badminton doubles tournament. X and Y are parents to two of the children playing. The child of X is not the same as the child of Y. Exactly one of the children does not have a parent playing in the tournament. The following rules are followed:

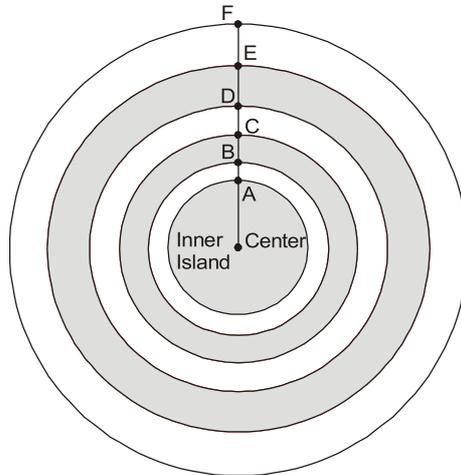- (i) A parent and his/her child cannot be on the same team.
- (ii) A match can feature at most one parent and his/her child, that is, a maximum of one parent-child pair can play in a match.



- (a) 0.45 (b) 0.60
 (c) 0.75 (d) 0.90

Ans. (c)

$$\begin{aligned}
 AB &= r_1 = 2.5, & AC &= r_2 = 3.5 \\
 AD &= r_3 = 5.5, & AE &= r_4 = 7.5 \\
 AF &= r_5 = 10.5, & AG &= r_6 = 13.5 \\
 L &= L_1 + L_2 + L_3 \\
 &= \pi r_1^2 + \pi(r_3^2 - r_2^2) + \pi(r_5^2 - r_4^2) \\
 &= \pi(2.5)^2 + \pi(5.5^2 - 3.5^2) + \pi(10.5^2 - 7.5^2) = 78.25\pi \\
 W &= W_1 + W_2 + W_3 \\
 &= \pi(r_2^2 - r_1^2) + \pi(r_4^2 - r_3^2) + \pi(r_6^2 - r_5^2) \\
 &= \pi(3.5^2 - 2.5^2) + \pi(7.5^2 - 5.5^2) + \pi(13.5^2 - 10.5^2) = 104\pi \\
 \frac{L}{W} &= \frac{78.25\pi}{104\pi} = 0.75
 \end{aligned}$$

End of Solution

Q.10 If Ref Fig \rightarrow 12 34 \rightarrow Ref Fig Then GATE - 2026 \rightarrow ?
 Aptitude Test

- (a) Test Aptitude (b) Aptitude Test
 GATE - 2026 2026 - GATE
 (c) Aptitude Test (d) Test Aptitude
 GATE - 2026 2026 - GATE

Ans. (c)

GATE - 2026 \rightarrow Aptitude Test
 Aptitude Test GATE - 2026

End of Solution

SECTION - B

TECHNICAL

Q.11 Consider the differential equation $\dot{\vec{w}} = A\vec{w}$, with $\vec{w}(t=0) = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$.

If $\vec{w}(t) = e^t\vec{u}_x + e^{-2t}\vec{u}_y$ be the solution to the equation where \vec{u}_x and \vec{u}_y are unit vectors along the positive x and y axes respectively, then which of the following options is the correct matrix representing A?

(a) $\begin{bmatrix} 1 & 0 \\ 0 & -2 \end{bmatrix}$

(b) $\begin{bmatrix} -1 & 0 \\ 0 & 2 \end{bmatrix}$

(c) $\begin{bmatrix} 0 & -2 \\ 1 & 0 \end{bmatrix}$

(d) $\begin{bmatrix} 0 & 2 \\ -1 & 0 \end{bmatrix}$

Ans. (a)

The problem gives the solution as

$$\vec{w}(t) = e^t\vec{u}_x + e^{-2t}\vec{u}_y$$

Since \vec{u}_x and \vec{u}_y are unit vectors along the x and y axis, we can write them in vector form.

Substituting these into the solution:

$$\vec{w}(t) = e^t \begin{bmatrix} 1 \\ 0 \end{bmatrix} + e^{-2t} \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$\vec{w}(t) = \begin{bmatrix} e^t \\ e^{-2t} \end{bmatrix}$$

The differential equation is given as

$$\dot{\vec{w}} = A\vec{w} \quad \dots(i)$$

$$\dot{\vec{w}} = \frac{d}{dt} \begin{bmatrix} e^t \\ e^{-2t} \end{bmatrix} = \begin{bmatrix} e^t \\ -2e^{-2t} \end{bmatrix}$$

Putting the value of $\vec{w}(t)$ and $\dot{\vec{w}}$ in equation (i)

$$\begin{bmatrix} e^t \\ -2e^{-2t} \end{bmatrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} e^t \\ e^{-2t} \end{bmatrix}$$

This gives us two linear equations:

$$e^t = ae^t + be^{-2t} \quad \dots(ii)$$

$$-2e^{-2t} = ce^t + de^{-2t} \quad \dots(iii)$$

For these equations to hold time for all value of t.

- From (2) : a = 1 and b = 0
- From (3) : c = 0 and d = -2

The resulting matrix A is:

$$A = \begin{bmatrix} 1 & 0 \\ 0 & -2 \end{bmatrix}$$

End of Solution

Q.12 A surface is given by $z^2 = 2x^2 - y^2$ and \vec{n} and $-\vec{n}$ are unit normal vectors to the surface at the point $\vec{P} = \hat{i} + \sqrt{2}\hat{k}$.

Which of the following vectors can be \vec{n} , where \hat{i}, \hat{j} and \hat{k} are the unit vectors along x, y and z axes, respectively?

- (a) $\hat{i} - \sqrt{2}\hat{k}$ (b) $\frac{2}{3}\hat{i} - \frac{1}{3}\hat{k}$
 (c) $\sqrt{2}\hat{i} - \sqrt{3}\hat{k}$ (d) $\frac{\sqrt{2}\hat{i} - \hat{k}}{\sqrt{3}}$

Ans. (d)

The given surface equation is $z^2 = 2x^2 - y^2$.

Rewriting this as a scalar function

$$f(x, y, z) = 0$$

$$f(x, y, z) = 2x^2 - y^2 - z^2$$

$$\nabla f = \frac{\partial f}{\partial x}\hat{i} + \frac{\partial f}{\partial y}\hat{j} + \frac{\partial f}{\partial z}\hat{k}$$

$$\nabla f = 4x\hat{i} - 2y\hat{j} - 2z\hat{k} \quad \dots(i)$$

The point is $\vec{P} = \hat{i} + \sqrt{2}\hat{k}$, which corresponds to $(x, y, z) = (1, 0, \sqrt{2})$.

Substituting these values into ∇f (i.e. equation (i))

$$\nabla f = 4(1)\hat{i} - 2(0)\hat{j} - 2(\sqrt{2})\hat{k}$$

$$\nabla f = 4\hat{i} - 2\sqrt{2}\hat{k}$$

The unit normal vector \vec{n} is given by

$$|\nabla f| = \sqrt{4^2 + (-2\sqrt{2})^2} = \sqrt{16 + 8} = \sqrt{24} = 2\sqrt{6}$$

$$\vec{n} = \frac{4\hat{i} - 2\sqrt{2}\hat{k}}{2\sqrt{6}} = \frac{2\hat{i} - \sqrt{2}\hat{k}}{\sqrt{6}}$$

$$\vec{n} = \frac{\sqrt{2}\hat{i} - \hat{k}}{\sqrt{3}}$$

End of Solution

Q.13 The Laplace Transform of the signal $x(t) = u(t - 2) * (tu(t))$ is given by which of the following expressions?

[“*” represents convolution operator]

- (a) $\frac{e^{-2s}}{s^2(s-2)}$ (b) $\frac{e^{-2(s-2)}}{s^3}$
 (c) $\frac{se^{-2s}}{(s-2)^2}$ (d) $\frac{e^{-2s}}{s^3}$

Ans. (d)

$$x(t) = r(t) * u(t - 2) = p(t - 2) = \frac{(t - 2)^2}{2} u(t - 2) \quad \dots(i)$$

$$p(t) = \frac{t^2}{2} u(t) \Rightarrow P(s) = \frac{1}{s^3}$$

From (i),
$$X(s) = P(s)e^{-2s} = \frac{1}{s^3} \cdot e^{-2s}$$

End of Solution

Q.14 Consider carrier transport in a Zener diode in the breakdown region. Which is the dominant transport mechanism for current flow in this case?

- (a) Drift (b) Diffusion
 (c) Tunneling (d) Ballistic transport

Ans. (c)

In Zener breakdown (heavily doped junction, low breakdown voltage), the strong electric field across the thin depletion region causes quantum mechanical tunneling of electrons from the valence band of p-side to the conduction band of n-side, dominating the current flow.

End of Solution

Q.15 Two analog signals $x_1(t)$ and $x_2(t)$ (t in second), are sampled at a rate $F_s = 40$ Hz, where $x_1(t) = \cos(20\pi t)$, $t \geq 0$, and $x_2(t) = \cos(100\pi t)$, $t \geq 0$.

The first ten samples (starting from $t = 0$) are considered for the analysis.

Which of the following statements is TRUE?

- (a) All of the first three samples of $x_1(t)$ are greater than the corresponding samples of $x_2(t)$.
 (b) All of the last three samples of $x_1(t)$ are greater than the corresponding samples of $x_2(t)$.
 (c) All of the samples of $x_2(t)$ are greater than the corresponding samples of $x_1(t)$.
 (d) All of the fourth to seventh samples of $x_1(t)$ are equal to the corresponding samples of $x_2(t)$.

Ans. (d)

$$x_1(t) = \cos 20\pi t$$

On sampling
$$t = nT_s = \frac{n}{f_s} = \frac{n}{40}$$

$$x_1(n) = x_1(nT_s) = \cos\left(20\pi \times \frac{n}{40}\right) = \cos\frac{\pi}{2}n$$

Similarly, for $x_2(t)$

$$x_2(t) = \cos 100\pi t$$

On sampling
$$t = nT_s = \frac{n}{40}$$



Foundation Courses for

ESE 2027

GATE 2027



Tablet Course

- Pre-loaded full fledged recorded course
- Android OS based 10.5 inch Samsung tablet
- Internet access does not required
- Classes by senior faculties
- Validity: 2 Years
- Learn at your own pace
- Tablet is reusable for normal purpose after validity expires



Recorded Course

- Recorded Course
- Full fledged holistic preparation
- Classes by senior faculties
- Lectures can be watched anytime/ anywhere
- Courses are accessible on PC & Mac desktops/laptops/android/ iOS mobile devices.
- Learn at your own pace
- Validity: 1 year
- Internet connection required

Teaching Hours

- ✓ **GATE Exclusive** • CE, ME, EE : 800 to 900 Hrs.
• EC, IN, CS, CH : 650-700 Hrs.
- ✓ **GATE + ESE** • CE, ME, EE, EC : 1100 to 1200 Hrs.
- ✓ **GATE + SES-GS** • CE, ME, EE : 1150 to 1250 Hrs. ✓ **GATE + ESE + SES-GS** • CE, ME, EE, EC : 1450 to 1550 Hrs.
• EC, IN, CS, CH : 950-1050 Hrs.

Note : State Engineering Services Examination. • The course is offered with a validity options of 1 year and 2 years.

Low Cost EMI Facility Available

Admissions open



Scan to enroll

Delhi Centre : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

MADE EASY Centres : Delhi | Bhopal | Hyderabad | Jaipur | Pune

www.madeeasy.in

$$x_2(n) = x_2(nT_s) = \cos\left(100\pi\frac{n}{40}\right) = \cos\left(\frac{5\pi}{2}n\right)$$

$$= \cos\left[\left(2\pi + \frac{\pi}{2}\right)n\right] = \cos\frac{\pi}{2}n$$

Therefore, $x_1(n) = x_2(n)$
 Hence, all of the fourth to seventh samples of $x_1(t)$ are equal to the corresponding samples of $x_2(t)$.

End of Solution

Q.16 The response of a discrete time system $y[n]$ obeys the following relation:

$$y[n] = \frac{5}{6}y[n-1] - \frac{1}{6}y[n-2] + x[n].$$

The input to the system is $x[n] = \delta[n] - \frac{1}{3}\delta[n-1]$.

Which of the following options is TRUE for $y[n]$?

- (a) Stable and causal response (b) Stable and non-causal response
 (c) Unstable and causal response (d) Unstable and non-causal response

Ans. (a)

The given difference equation is:

$$y(n) = \frac{5}{6}y(n-1) - \frac{1}{6}y(n-2) + x(n)$$

Taking the z-transform on both sides:

$$Y(z) = \frac{5}{6}z^{-1}Y(z) - \frac{1}{6}z^{-2}Y(z) + X(z)$$

$$Y(z)\left(1 - \frac{5}{6}z^{-1} + \frac{1}{6}z^{-2}\right) = X(z)$$

$$H(z) = \frac{Y(z)}{X(z)} = \frac{1}{1 - \frac{5}{6}z^{-1} + \frac{1}{6}z^{-2}}$$

On factoring the denominator, we get,

$$H(z) = \frac{1}{\left(1 - \frac{1}{2}z^{-1}\right)\left(1 - \frac{1}{3}z^{-1}\right)}$$

The input is given as

$$x[n] = \delta[n] - \frac{1}{3}\delta[n-1]$$

Its z-transform is: $X(z) = 1 - \frac{1}{3}z^{-1}$

The response $Y(z)$,

$$Y(z) = H(z) \cdot X(z)$$

$$Y(z) = \frac{1 - \frac{1}{3}z^{-1}}{\left(1 - \frac{1}{2}z^{-1}\right)\left(1 - \frac{1}{3}z^{-1}\right)}$$

$$Y(z) = \frac{1}{1 - \frac{1}{2}z^{-1}}$$

On taking inverse z-transform of $Y(z)$, we get


$$y(n) = \left(\frac{1}{2}\right)^n u(n)$$

- Since $y(n) = 0$ for $n < 0$. Hence, the response is causal.
- The pole of $Y(z)$ is at $z = \frac{1}{2}$. Since the magnitude of the pole (i.e. $\frac{1}{2}$) i.e. less than 1, the pole lies inside the unit circle in the z-plane, making the response stable.
- Hence, the response $y[n]$ is stable and causal.

End of Solution

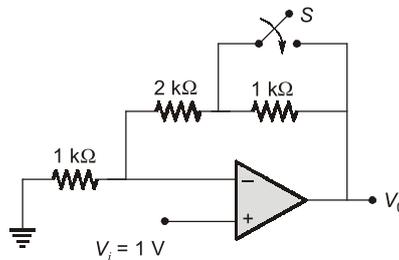Q.17 The ideal OP-AMP circuit shown in the Figure produces output voltage $V_o = x$ when the Switch, S, is open.

Which of the options represents the output voltage when S is closed?



- | | |
|--------------------|--------------------|
| (a) x | (b) $\frac{2}{3}x$ |
| (c) $\frac{3}{4}x$ | (d) $\frac{1}{2}x$ |


Ans. (c)

Given, $V_{o1} = x$

$$\text{Switch open} = V_{o1} = \left(1 + \frac{3}{1}\right) \times 1 = 4 \text{ V} = x$$

$$\text{Switch open} = V_{o2} = \left(1 + \frac{2}{1}\right) \times 1 = 3 \text{ V}$$

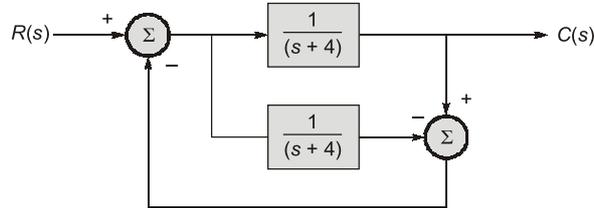Q.19 A control system is shown in the Figure.
 Which option represents the correct transfer function of the system?




- (a) $\frac{1}{(s+4)^2}$ (b) $\frac{1}{(s+4)}$
 (c) $\frac{2}{(s+4)}$ (d) $\frac{1}{(s^2+8s+17)}$

Ans. (b)
 Using Mason's gain formula, we get

$$\frac{C(s)}{R(s)} = \frac{\frac{1}{s+4}}{1 - \left[-\frac{1}{s+4} + \frac{1}{s+4} \right]} = \frac{1}{s+4}$$

End of Solution

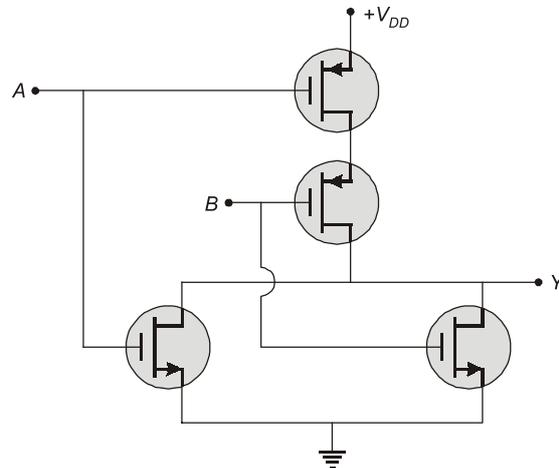Q.20 In the circuit shown in the Figure, A and B are logic inputs and Y is the logic output.
 Which of the following logic operations is realized by the circuit?



- (a) NOR (b) OR
 (c) XOR (d) AND

Ans. (a)

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

∴ The given circuit performs NOR operation.

End of Solution

Q.21 Consider the Friis' transmission equation $P_R = (P_T G_T G_R \lambda^2) / (4\pi D)^2$, where P_R and P_T are the received and the transmitted powers, respectively.

G_T and G_R are the gain of transmitting and receiving antennas, respectively, D is the distance between the transmitting and receiving antennas, and λ is the wavelength in free space.

Given: $G_T = G_R = 1.0$, $\lambda = 0.30$ m and $P_T = +10$ dBm.

Choose the distance (D), in km, from the following options at which the received power, $P_R = -90$ dBm?

- (a) $\frac{15}{4\pi}$ (b) $\frac{15}{2\pi}$
 (c) $\frac{75}{2\pi}$ (d) $\frac{3}{4\pi}$

Ans. (b)

Given data: $G_t = G_r = 1$; $\lambda = 0.30$; $P_t = 10$ dBm ; $P_r = -90$ dBm ; $r = ?$ (km)
 From Friis' transmission formula,

$$P_r = \frac{P_t G_{dt} G_{dr}}{\left(\frac{4\pi r}{\lambda}\right)^2}$$

$$\therefore P_r |_{\text{dBm}} = 10 \log_{10} \left(\frac{P_r}{1 \text{ mW}} \right)$$

$$\Rightarrow -90 = 10 \log_{10} \left(\frac{P_r}{1 \times 10^{-3}} \right)$$

$$\Rightarrow P_r = 10^{-12} \text{ W}$$

$$\text{Similarly, for } P_t \quad 10 = 10 \log_{10} \left(\frac{P_t}{1 \times 10^{-3}} \right) \Rightarrow P_t = 0.01 \text{ W}$$

On substituting, we get,

$$\left(\frac{4\pi r}{\lambda}\right)^2 = \frac{P_t G_{dt} G_{dr}}{P_r}$$

$$\Rightarrow r = \frac{\lambda}{4\pi} \sqrt{\frac{P_t G_{dt} G_{dr}}{P_r}}$$

$$r = \frac{0.30}{4\pi} \sqrt{\frac{0.01 \times 1 \times 1}{1 \times 10^{-12}}} = \frac{15}{2\pi} \text{ km}$$

End of Solution

Q.22 Consider a discrete memoryless source with an alphabet of four source symbols. $s(t)$ is a multi-level $(-1, 0, +1, +2)$ signal representing a long sequence of random symbols from the above source which is generating 10^4 symbols per second. Which of the following options is the correct value of equivalent Nyquist bandwidth of $s(t)$?

- (a) 10 kHz (b) 64 kHz
(c) 5 kHz (d) 20 kHz

Ans. (c)

Number of given symbols $\Rightarrow M = 4$

$$\text{Symbol rate } (R_s) = \frac{10^4 \text{ symbols}}{\text{sec}}$$

$$\text{Nyquist Bandwidth} = \frac{R_b}{2 \log_2 M}$$

$$\text{Symbol rate, } (R_s) = \frac{R_b}{\log_2 M}$$

$$\text{Nyquist Bandwidth} = \frac{R_s}{2} = \frac{10^4}{2} = 5 \text{ kHz}$$

End of Solution

Q.23 The relation between the input current (I) and the output voltage (V) of a circuit is governed by the equation: $C \frac{dV}{dt} = I(t) - m(t)$. The circuit is excited by $I(t) = q\delta(t)$, where

q is a real valued constant. V at $t = 0^-$ is V_0 .

Which of the following is an equivalent representation of the above case?

- (a) $C \frac{dV}{dt} = -m(t)$, with $V(t = 0^-) = V_0 + q/C$
 (b) $C \frac{dV}{dt} = -m(t)$, with $V(t = 0^-) = V_0 + q/C + m(t = 0^-)$
 (c) $C \frac{dV}{dt} = -m(t)$, with $V(t = 0^-) = V_0 - q/C + m(t = 0^-)$
 (d) $C \frac{dV}{dt} = -m(t)$, with $V(t = 0^-) = q/C$

Ans. (a)

The circuit is governed by the equation

$$C \frac{dV}{dt} = I(t) - m(t) \quad \dots(i)$$

The given conditions are:

Initial current: $I(t) = q\delta(t)$

Initial voltage: V at $t = 0^-$ is V_0

To understand the effect of impulse $q\delta(t)$,
 Integrating equation (i)

From $t = 0^-$ to $t = 0^+$

$$\int_{0^-}^{0^+} C \frac{dV}{dt} = \int_{0^-}^{0^+} [q\delta(t) - m(t)] \cdot dt$$

$$\Rightarrow C[V(0^+) - V(0^-)] = q$$

$$\Rightarrow V(0^+) - V_o = \frac{q}{C}$$

$$\Rightarrow V(0^+) = V_o + \frac{q}{C}$$

After the impulse has occurred (for $t > 0$), the input $I(t)$ become zero.
 The behaviour of system is then described by the original equation without the impulse term, but starting from the new initial state at $t = 0^+$

i.e. $C \frac{dV}{dt} = -m(t)$ with $V(t = 0^+) = V_o + \frac{q}{C}$

So, the equivalent representation shifts the effect of the impulse into the initial condition of the system. Hence, option (a) is correct.

End of Solution

Q.24 The electric field of a monochromatic plane wave travelling in a lossless isotropic and homogenous medium is given by

$$\vec{E}(z, t) = E_0 [\hat{x} \cos(\omega t - kz) + \hat{y} \sin(\omega t - kz)]$$

in a right-handed orthogonal co-ordinate system.

Which of the following is the correct polarization of the electromagnetic wave?

- (a) Right-handed circularly polarized (b) Left-handed circularly polarized
 (c) Linearly polarized (d) Linearly polarized with -45° angle to \hat{x}

Ans. (a)

Given, $\vec{E}(z, t) = E_0 [\cos(\omega t - kz)\hat{x} + \sin(\omega t - kz)\hat{y}]$

at $z = 0$,

$$\vec{E}(t) = E_0 \cos \omega t \hat{x} + E_0 \sin \omega t \hat{y}$$

As $|E_{x0}| = |E_{y0}| = E_0$


$$|\phi| = 90^\circ$$

\therefore it is a circularly polarized wave.

Now, at $t = 0$, $\omega t = 0$, $\vec{E} = E_0 \hat{x}$

at $t = T/4$, $\omega t = \pi/2$, $\vec{E} = E_0 \hat{y}$

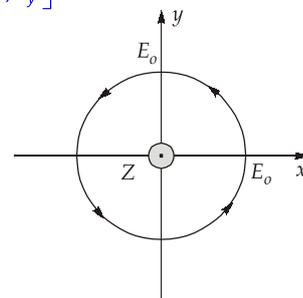Hence it is Right-handed circularly polarized.



End of Solution



Conventional Questions Practice Programme for ESE Mains 2026




Scan to enroll

Offline

Live-Online

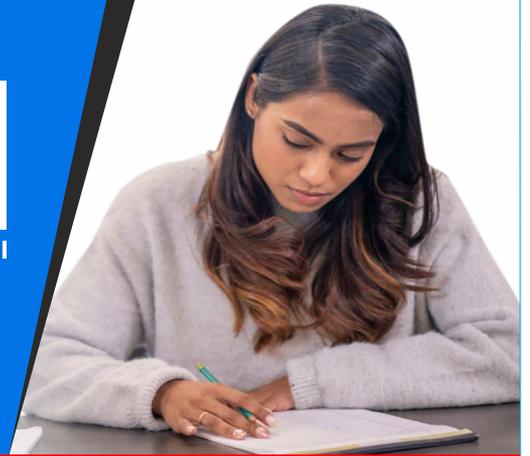- Batches Starting from 24 Feb, 2026
- Admissions Open



ESE Mains Test Series (15 tests) Starting from 15 March, 2026

Note : Solo Mains Test Series is also available.



Scan to enroll

This conventional course is offered in offline mode at Delhi Centre.

Key Features :

- Classes by MADE EASY senior faculties
- Beneficial to improve answer writing and presentation skills
- Updated Main exam workbooks containing diverse practice questions
- Highly useful for State Engineers Service examinations also.
- In-depth analysis and discussion on probable & potential questions
- Develops numerical questions solving techniques
- Weekly dynamic test series on every Sunday aligned with the course (optional).

Duration: 300-350 Hrs | Streams: CE, ME, EE, E&T

Fee Structure :

ESE Main Course Fees

- MADE EASY students : ₹13,000 + GST
- Non-MADE EASY students : ₹15,000 + GST

Main Course + Test Series Fee

- MADE EASY students : ₹16,500 + GST
- Non-MADE EASY students : ₹18,500 + GST

Test Series Fee

For all students : ₹4,500 + GST

Delhi Centre : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

MADE EASY Centres : Delhi | Bhopal | Hyderabad | Jaipur | Pune

www.madeeasy.in

Ans. (b)

A counter that counts from 0 to 64 must be able to represent a total of 65 distinct states. The maximum number of states (or the MOD number) that can be represented by n -flip-flops is given by:

$$\text{Total states} = 2^n$$

To accommodate 65 states, it must satisfy the following inequality:

$$2^n \geq 65$$

i.e. $n \geq \log_2^{65}$

$$n \geq 6.022$$

Hence, the minimum number of flip-flops required to design this counter is 7.

End of Solution

Q.28 Which option(s) represents/ represent the dielectric loss tangent of a substrate?

(a) Ratio of the real to imaginary parts of the total displacement current

(b) $\frac{(\omega\epsilon'' + \sigma)}{(\omega\epsilon')}$

(c) Ratio of the electric susceptibility to permittivity

(d) Ratio of the polarization vector \vec{P} to the displacement vector \vec{D}

Ans. (a, b)

The dielectric loss tangent ($\tan \delta$) measures energy loss in a dielectric substrate under AC fields. In electromagnetics it includes both polarization losses and conduction losses.

According to standard definition:

$$\tan \delta = (\omega\epsilon'' + \sigma) / (\omega\epsilon')$$

(where ϵ' = real permittivity, ϵ'' = imaginary part from dielectric loss, σ = conductivity, ω = angular frequency)

Hence, option (b) is correct.


Dielectric loss tangent of a substrate is the ratio of the real to imaginary parts of the total displacement current. Hence, option (a) is correct.

End of Solution

Q.29 Figure shows the output characteristics of two different Bipolar Junction

Transistors (BJT), BJT 1 with magnitude of Early voltage $|V_{A1}|$, and BJT 2 with magnitude of Early voltage $|V_{A2}|$.

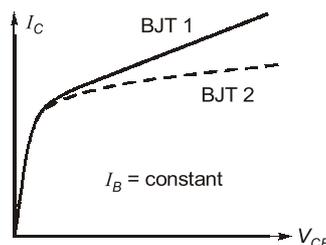Which of the following options is/are correct regarding the Early voltages?




- (a) $|V_{A1}| > |V_{A2}|$ (b) $|V_{A1}|$ is infinitely large
 (c) $|V_{A1}| < |V_{A2}|$ (d) $|V_{A2}|$ is infinite

Ans. (c, d)

BJT 2 has a smaller slope in the active region (flatter I_C vs V_{CE} curve). Hence $|V_{A2}|$ is greater than $|V_{A1}|$, so option (c) is correct, and since BJT 2 curve shows finite slope (not perfectly flat), V_{A2} is finite (and not ∞), so option (d) is also correct.

End of Solution

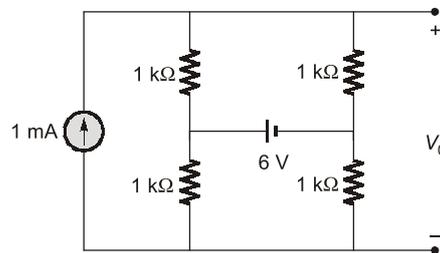
Q.30 The output voltage V_o (in Volt) for the network given in the Figure is _____.
 (rounded off to two decimal places)




Ans. (1) (0.95 to 1.05)

By using superposition theorem.

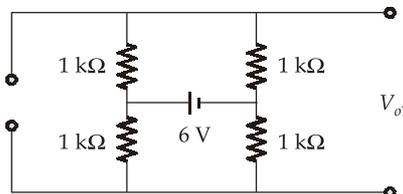If 6 V source is active and 1 mA current source is open circuit.





or

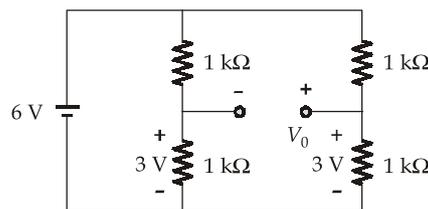

$$\therefore V_{o1} = 3 - 3 = 0 \text{ V}$$

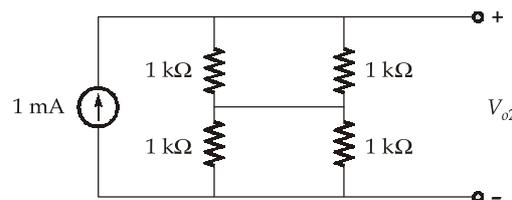If 1 mA current source is active and 6 V voltage source is short circuited.



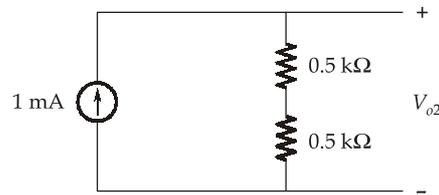

$$\therefore V_{o2} = | \max | 1 \text{ k}\Omega = 1 \text{ V}$$


By superposition theorem,

$$V_0 = V_{o1} + V_{o2}$$

$$\therefore V_0 = 0 + 1 = 1 \text{ V}$$

End of Solution

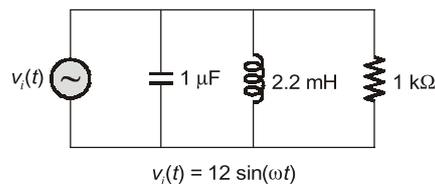- Q.31** Consider the circuit shown in the Figure, where the input $v_i(t)$ is in Volt. The average power (in mW) dissipated in the load resistance of $1 \text{ k}\Omega$ at the resonant frequency is _____.
 (rounded off to two decimal places)



Ans. (72) (71.50 to 72.50)

$$P = \frac{V^2}{R} = \frac{\left(\frac{12}{\sqrt{2}}\right)^2}{1 \times 10^3} = 72 \text{ mW}$$

End of Solution

- Q.32** A wireless digital transmission scheme is using 16-QAM over an additive white Gaussian noise channel and a maximum-likelihood receiver. Consider the information bit rate from source to be 4×10^6 bits per second. The minimum transmission bandwidth (in MHz) of the modulated signal necessary for optimum recovery of information at the receiver is _____.
 (rounded off to two decimal places)

Ans. (1) (0.95 to 1.05)

Given modulation scheme is 16 QAM
 $M = 16$

$$\text{Information bit rate } (R_b) = 4 \times 10^6 \frac{\text{bits}}{\text{sec}}$$

$$\text{Minimum transmission B.W} = \frac{R_b}{\log_2 M} = \frac{4 \times 10^6}{\log_2 16} = 10^6 = 1 \text{ MHz}$$

End of Solution

Q.33 The cutoff frequency (in GHz) for the dominant TE_{10} mode of an air-filled rectangular waveguide of inner dimension 0.28 inch \times 0.14 inch is _____.
 (rounded off to two decimal places).

Ans. (21.09) (20.50 to 21.50)

$$f_c|_{TE_{10}} = \frac{c}{2a} = \frac{3 \times 10^{10}}{2 \times 0.28 \times 2.54} \quad [\because 1 \text{ inch} = 2.54 \text{ cm}]$$

$$= 21.09 \text{ GHz}$$

End of Solution

Q.34 For a lossless passive two-port network, $|S_{11}|$ and $|S_{21}|$ intersect at -3 dB.
 For a lossy passive two-port network, $|S_{11}|$ and $|S_{21}|$ intersect at -4 dB.
 The percentage of power dissipated in the lossy network at the intersection frequency is _____.
 (rounded off to two decimal places)

Ans. (20.38) (20.00 to 21.00)

Given for the lossy passive two port network, at the intersection

$$|S_{11}| = |S_{21}| = -4 \text{ dB}$$

$$\therefore \text{Power ratio} = 10^{-0.4} = 0.3981$$

$$\therefore |S_{11}|^2 = |S_{21}|^2 = 0.3981$$

Further,

$$P_{in} = |S_{11}|^2 + |S_{21}|^2 + P_{loss}$$


$$\Rightarrow 1 = 0.3981 + 0.3981 + P_{loss}$$

$$\Rightarrow P_{loss} = 0.2038$$

$$\therefore \%P_{loss} = 20.38$$

End of Solution

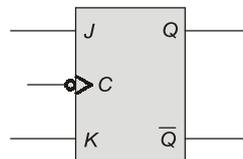Q.35 The negative edge triggered JK flip-flop in the Figure has J and K inputs tied to Logic High and a square wave of 10 cycles/second is applied to its clock (C) input.
 The frequency of the output Q (in cycles/second) is _____.
 (rounded off to two decimal places)



Ans. (5) (4.90 to 5.10)

When, $J = K = 1$,
 Then, JK-FF operate in toggle mode.

$$\therefore f_{out} = \frac{f_{in}}{2} = 5 \text{ Hz}$$

End of Solution

Q.36 Consider the two series, S_A and S_B , where

$$S_A = \sum_{n=1}^{\infty} \frac{n^2}{2^n}$$

$$S_A = 1 + \frac{1}{2} + \frac{1}{8} + \frac{1}{16} + \frac{1}{64} + \frac{1}{128} + \frac{1}{512} + \dots$$

Which of the following statements is correct for the two given series?

- (a) Both S_A and S_B converge.
- (b) Neither S_A nor S_B converges.
- (c) S_A converges but S_B does not converge.
- (d) S_B converges but S_A does not converge.

Ans. (a)

Case I :

$$S_A = \sum \frac{n^2}{2^n}$$

By n^{th} root test

$$= \lim_{n \rightarrow \infty} \left(\frac{n^2}{2^n} \right)^{1/n}$$

$$= \lim_{n \rightarrow \infty} \frac{n^{2/n}}{2} = \frac{1}{2} < 1$$

Hence, S_A is convergent

Case II :

Given $S_B = \sum_{n=1}^{\infty} \frac{1}{2^n}$ is GP series.

$$= 1 + \frac{1}{2} + \frac{1}{4} + \dots + \frac{1}{512}$$

$$S_{\infty} = \frac{1}{1 - \frac{1}{2}} = 2$$

$\therefore S_B$ is also convergent.

End of Solution

Q.37 The continuous time signal $x(t)$ is real, periodic with period T and satisfies the Dirichlet conditions.

The Fourier series representation of $x(t) = \sum_{n=-\infty}^{\infty} a_n e^{j\left(\frac{2\pi nt}{T}\right)}$ and $x(t)$ satisfies the following:

$$x\left(t - \frac{T}{2}\right) = -x(t).$$

For any integer m , which of the following options is correct?

- (a) $a_{2m} = 0$
- (b) $a_{2m} = 1$
- (c) $a_{2m} = a_{2m+1}$
- (d) $a_{2m} = -1$

Ans. (a)

Given that, $x\left(t - \frac{T}{2}\right) = -x(t)$ where 'T' is FTP.

Thus, $x(t)$ is half-wave symmetric signal.

For HWS: Even harmonics will be absent

i.e. $a_n = 0$ if n is even-integer.

$\Rightarrow a_{2m} = 0$ where $m = \text{integer}$

End of Solution

Q.38 Let X, N, Y and Z be random variables. The variables X and N are independent of each other. X is uniformly distributed between -1 and 1 ; N follows Normal distribution with zero mean and unity variance.

Y and Z are defined as, $Y = X + N$ and $Z = X^2 + N$.


Which of the following pairs represents the values of correlation between X and Y and that between X and Z ?

- (a) $1/3$ and 0 (b) $1/3$ and $1/9$
 (c) $1/3$ and $1/3$ (d) 1 and 0

Ans. (a)

Given,
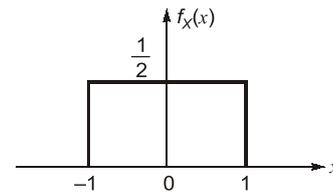
$$\begin{aligned} X &= U(-1, 1) \\ E[X] &= 0 \\ \text{var}[X] &= \frac{1}{3} \\ E[X^2] &= \frac{1}{3} \\ N &= N(0, 1) \\ E[N] &= 0 \\ \text{var}[N] &= 1 \\ E[N^2] &= 1 \end{aligned}$$



X and N are independent random variables.

Given $Y = X + N$ and $Z = X^2 + N$

Correlation between X and $Y \rightarrow \text{Cov}(X, Y)$

\therefore Co-variance is measure of correlation between two random variables.


$$\begin{aligned} \text{Cov}(X, Y) &= E[XY] - E[X] \cdot E[Y] \\ &= E[X^2 + XM] - E[X] \cdot E[X + N] \\ &= E[X^2] + E[X] \cdot E[M] - E[X] \cdot \{E[X] + E[N]\} \\ &= \frac{1}{3} + 0 - 0 = \frac{1}{3} \end{aligned}$$

Correlation between X and Z

$$\begin{aligned} \text{Cov}(X, Z) &= E[XZ] - E[X] \cdot E[Z] \\ &= E[X^3 + XM] - E[X] \cdot E[X^2 + N] \\ &= E[X^3] + E[XM] - 0 = E[X^3] \\ &= \int_{-1}^1 x^3 f_X(x) dx = 0 \end{aligned}$$

End of Solution

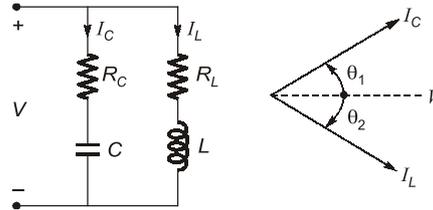Q.39 In the given circuit, $L = 1 \mu\text{H}$ and $C = 1 \mu\text{F}$. The phasor diagram for I_C and I_L is also shown. Assume that the phase $(\theta_1 + \theta_2)$ is 90° at a frequency of 159.15 kHz . Among the following options, what is the nearest integer value of $R_C \times R_L$?



- (a) 0
 (b) 1
 (c) 2
 (d) 10

Ans. (b)

$$\theta_1 = \tan^{-1}\left(\frac{X_C}{R_C}\right) + \tan^{-1}\left(\frac{X_L}{R_L}\right) = 90^\circ$$

$$\tan(A + B) = \frac{\tan A + \tan B}{1 - \tan A \tan B}$$

Here, $\tan A \cdot \tan B = 1$

i.e. $\tan^{-1}\left(\frac{X_C}{R_C}\right) \cdot \tan\left(\frac{X_L}{R_L}\right) = 1$

$$\frac{X_C}{R_C} \cdot \frac{X_L}{R_L} = 1$$

$$\frac{1}{\omega C R_C} \cdot \frac{\omega L}{R_L} = 1$$

i.e. $R_L \cdot R_C = \frac{L}{C}$


$\therefore R_L \cdot R_C = 1$

End of Solution

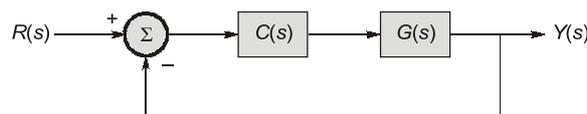Q.40 For the control system shown in the Figure, the transfer function of a plant,

$G(s) = \frac{1}{(s+1)(s+2)}$ is connected in cascade with a compensator $C(s) = K(s+\alpha)$, where K and α are positive real valued constants.

Which of the following pairs (K, α) represent the correct values for the closed loop system to have poles at $(-3 \pm j\sqrt{5})$?



- (a) 2, 3
 (b) 3, 4
 (c) 2, 4
 (d) 3, 3

Ans. (b)

We know that the characteristics equation is given as,

$$1 + G(s) H(s) = 1 + \frac{K(s + \alpha)}{(s + 1)(s + 2)}$$

or characteristics equation,

$$q(s) = s^2 + s(K + 3) + (2 + \alpha K) \quad \dots(1)$$

For $S = -3 \pm j\sqrt{5}$,

$$\begin{aligned} q(s) &= (s + 3)^2 + (\sqrt{5})^2 \quad \dots(2) \\ &= s^2 + 14 + 6s \end{aligned}$$

On comparing (1) and (2) we get,

$$K = 3 \text{ and } \alpha = 4$$

End of Solution

Q.41 The state and output equations for a control system are:

$$\begin{aligned} \dot{x} &= \begin{bmatrix} -4 & -1.5 \\ 4 & 0 \end{bmatrix} x + \begin{bmatrix} 2 \\ 0 \end{bmatrix} u \\ y &= [1.5 \quad 0.625]x \end{aligned}$$

Which of the following expressions correctly represents the transfer function $\frac{Y(s)}{U(s)}$ of the system with zero initial conditions?

- | | |
|-----------------------------------|-----------------------------------|
| (a) $\frac{3s}{s^2 + 4s - 6}$ | (b) $\frac{3s + 5}{s^2 + 4s - 6}$ |
| (c) $\frac{3s + 5}{s^2 + 4s + 6}$ | (d) $\frac{3s}{s^2 + 4s + 6}$ |

Ans. (c)

We know that,

Transfer Function of system, $TF = C[(sI - A)^{-1} B] + D$

On solving, we get

$$TF = \frac{3s + 5}{s^2 + 4s + 6}$$

End of Solution

Q.42 The address of the first location of a 256 kilo byte (KB) memory is $(2500)_H$.

Choose the correct address of the last location of the memory.

- | | |
|-----------------|-----------------|
| (a) $(2FFF)_H$ | (b) $(124FF)_H$ |
| (c) $(424FF)_H$ | (d) $(324FF)_H$ |

Ans. (c)

Given, Memory capacity = 256 kB

Starting address = 2500 H

Final address = ?

Final address – Initial address + 1 = Capacity of memory

$$\begin{aligned} x - 2500 \text{ H} + 1 &= 40000 \text{ H} \\ x &= 40000 \text{ H} - 1 + 2500 \text{ H} \\ &= 3\text{FFFFH} \\ x &= \underline{\underline{+2500\text{H}}} \\ &= \underline{\underline{424\text{FFH}}} \end{aligned}$$

Hence, the final address location is 424FFH.

End of Solution

- Q.43** Consider a real signal $x(t)$, $-\infty < t < \infty$, such that $x(t) = 0$ for $t < 0$, $x(t) = 2$ for $0 \leq t < 1$ and $x(t) = 0$ for $t \geq 1$.

$$\text{Let } E[x(t)] = \int_{-\infty}^{\infty} [x(t)]^2 dt.$$

Which of the following options correctly represents the ratio, $E[x(t)]/E[3x(-3t+)]$?

- (a) 3 (b) 1
 (c) 1/3 (d) 1/9

Ans. (c)

Energy of signal, $x(t) = E$ joule

$$x(-3t + 5) \rightarrow \frac{E}{3} \text{ joule}$$

$$3x[-3t + 5] \rightarrow 3^2 \times \frac{E}{3} = 3E \text{ joule}$$

$$\frac{E[x(t)]}{E[3x(-3t + 5)]} = \frac{E}{3E} = \frac{1}{3}$$

End of Solution

- Q.44** A QPSK modulated signal from an additive white Gaussian noise (AWGN) channel is received with an $E_b/N_o = 8.4$ dB at the input of a coherent QPSK demodulator. A maximum-likelihood reception method is used in the demodulator.

Assume the complimentary error function

$$\text{erfc}(u) \cong \left[\frac{1}{(u\sqrt{\pi})} \right] \exp(-u^2).$$

Which is the nearest bit error rate (BER) at the output of the demodulator?

- (a) 10^{-3} (b) 10^{-4}
 (c) 10^{-5} (d) 10^{-6}

Ans. (b)

Given, $\frac{E_b}{N_o} = 8.4 \text{ dB} = 10^{0.84}$

$$\text{erfc}(u) \simeq \frac{1}{u\sqrt{\pi}} e^{-u^2}$$



POSTAL PACKAGES

- CSE
- ESE
- GATE
- PSUs
- SSC-JE
- RRB-JE
- UPPSC-AE
- BPSC-AE
- MPSC
- Other State Engineering Exams

Salient Features of Postal Study Package

Our Postal Book Packages cater to the needs of college-going students, working professionals, and individuals unable to join classroom courses. These books, offered by MADE EASY, are designed to be compact, comprehensive, and easily understandable. We have put our efforts to ensure error-free content, incorporating smart and shortcut techniques specifically tailored for solving numerical problems.

- **Complete syllabus coverage aligned with latest pattern/syllabus.**
- **Detailed theory and practice exercises.**
- **Latest and updated study material**
- **Step by step solutions**
- **Ample no. of practice questions with PYQs.**
- **Emphasis on technical and non technical sections both.**
- **Subject-wise theory objective and conventional practice sets.**
- **Proven track record of student success.**

For online purchase, visit :

www.madeeasypublications.org | Helpline : 8860378004

For offline purchase, visit in-person at any MADE EASY center.
Books will be sent to your provided address.



Scan to enroll

Address : 44-A/4, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016

9021300500

www.madeeasypublications.org

$$\begin{aligned}
 \text{BER of QPSK} &= Q\left(\sqrt{\frac{2E_b}{N_0}}\right) \\
 &= \frac{1}{2} \operatorname{erfc}\left(\sqrt{\frac{E_b}{N_0}}\right) \\
 &= \frac{1}{2} \operatorname{erfc}(\sqrt{6.91}) \\
 &= \frac{1}{2} \operatorname{erfc}(2.63) \\
 &= \frac{1}{2} \times \frac{1}{2.63\sqrt{\pi}} e^{-(2.63)^2} \\
 &= 0.0001 \approx 10^{-4}
 \end{aligned}$$

End of Solution

- Q.45** What is the 10's complement of $(47)_{10}$?
 (a) 52 (b) 53
 (c) 54 (d) 55

Ans. (b)

Using r 's complement = $(r - 1)$'s complement + 1

\therefore 9's complement of $(47)_{10}$

$$\begin{array}{r}
 99 \\
 -47 \\
 \hline
 52
 \end{array}
 \quad \text{i.e., (9's complement)}$$

\therefore 10's complement

$$\begin{array}{r}
 52 \\
 +1 \\
 \hline
 53
 \end{array}$$

Hence, the 10's complement of $(47)_{10}$ is 53.

End of Solution

- Q.46** Consider a real baseband signal $x(t) = e^{-2t}$, for t (in seconds) ≥ 0 .
 If 99% of energy of $x(t)$ lies within B Hz, then which of the following options is TRUE for the value of B ?
 (a) $B > 1$ kHz (b) $63/\pi$ Hz $< B < 64/\pi$ Hz
 (c) $126/\pi$ Hz $< B < 128/\pi$ Hz (d) $B < 1$ Hz

Ans. (b)

$$\begin{aligned}
 x(t) \Leftrightarrow X(\omega) &= \frac{1}{2 + j\omega} \\
 |X(\omega)| &= \frac{1}{\sqrt{4 + \omega^2}}
 \end{aligned}$$

For $x(t)$: Energy $\frac{1}{2 \times 2} = \frac{1}{4}$

Given that energy contained in the frequency range " $2\pi B$ " rad/sec is 99% of energy of $x(t)$.

i.e. $\frac{1}{2\pi} \int_{-2\pi B}^{2\pi B} |X(\omega)|^2 d\omega = \frac{0.99}{4}$

$\Rightarrow \frac{1}{2\pi} \times 2 \times \int_0^{2\pi B} \frac{1}{4 + \omega^2} d\omega = \frac{0.99}{4}$

$\Rightarrow \frac{1}{\pi} \left[\frac{1}{2} \tan^{-1} \left(\frac{\omega}{2} \right) \right]_0^{2\pi B} = \frac{0.99}{4}$

$\frac{1}{\pi} \tan^{-1} \left[\frac{2\pi B}{2} \right] = \frac{0.99}{2}$

$\Rightarrow \tan^{-1}(\pi B) = \frac{0.99\pi}{2}$


$\Rightarrow \pi B = \tan \left(\frac{0.99\pi}{2} \right) = 63.56$

$\Rightarrow B = \frac{63.56}{\pi} = 20.26 \text{ Hz}$

End of Solution

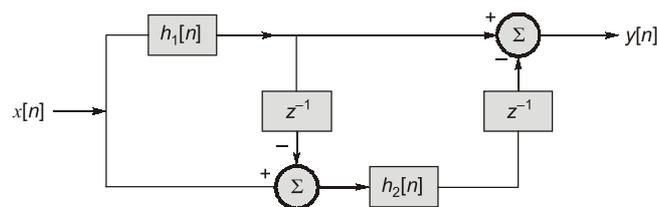Q.47 Consider the discrete time system (S) with input $x[n]$ and output $y[n]$ as shown in the Figure. The two sub-systems represented by their impulse responses $h_1[n]$ and $h_2[n]$ are linear and time invariant.

Which of the following statements is necessarily TRUE?




- (a) S is causal.
- (b) S is linear and time invariant.
- (c) S is linear and time varying.
- (d) S is non-linear.

Ans. (b)

The overall system S is composed of two sub-systems with impulse response $h_1[n]$ and $h_2[n]$.

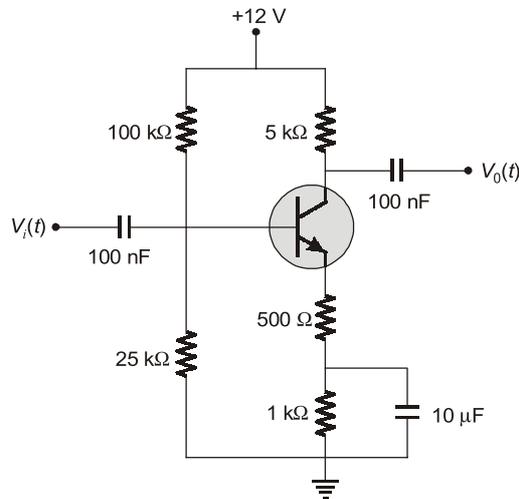- Given $h_1[n]$ and $h_2[n]$ is LTI system.
- The system uses adders (Σ), which are linear operation.
- The system uses unit delays (z^{-1}), which are linear and time-invariant operations.
- The sub-systems are connected in a combination of parallel and cascade (series) configuration.



- (a) $-9.1 [A \cos(10^5 t) + B \sin(10^7 t)]$ (b) $9.1 [A \cos(10^5 t) + B \sin(10^7 t)]$
 (c) $-190.4 [A \cos(10^5 t) + B \sin(10^7 t)]$ (d) $190.4 [A \cos(10^5 t) - B \sin(10^7 t)]$

Ans. (a)

For DC Analysis, $V_{th} = \frac{12 \times 25}{100 + 25} = 2.4 \text{ V}$

$R_{th} = 100 \parallel 25 = 20 \text{ k}\Omega$

$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta)R_E}$

$I_B = 0.01 \text{ mA}$

$I_C = \beta I_B = 0.99 \text{ mA}$

$V_{CE} \cong V_{CC} - I_C(R_C + R_E) = 5.56 \text{ V}$

$g_m = \frac{I_C}{V_T} = 39.6 \text{ mS}$

$r_\pi = \frac{\beta}{g_m} = 2.5 \text{ k}\Omega$

$r_o = \frac{V_A + V_{CE}}{I_C} = 106.6 \text{ k}\Omega$

If we neglect the effect of r_o then voltage gain expression is,


$A_V \cong \frac{-g_m R_C}{1 + g_m R_{E1}}, \quad R_{E1} = 0.5 \text{ k}\Omega$

$A_V \cong -9.5$

100 nF capacitors provide negligible reactance at given input frequencies. Hence both frequencies will appear in the output.


$V_0 = A_V \times V_i$

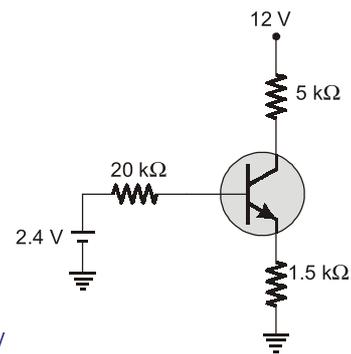$V_0 \cong -9.5 (A \cos 10^5 t + B \sin 10^7 t)$




End of Solution

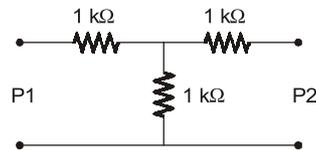Q.51 Consider the two-port network as shown in the Figure.
 Which of the following options provides the correct set of values of A , B , C and D parameters?



- (a) $A = \frac{1}{2}$, $B = 3 \times 10^3 \Omega$, $C = 10^{-3} \Omega^{-1}$, $D = \frac{1}{2}$
 (b) $A = 2$, $B = 3 \Omega$, $C = 1 \Omega^{-1}$, $D = 2$
 (c) $A = 2$, $B = 6 \times 10^3 \Omega$, $C = 2 \times 10^{-3} \Omega^{-1}$, $D = 2$
 (d) $A = 2$, $B = 3 \times 10^3 \Omega$, $C = 10^{-3} \Omega^{-1}$, $D = 2$

Ans. (d)

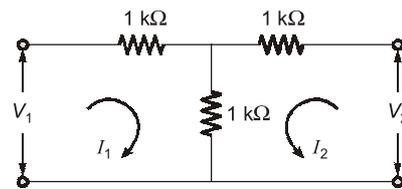

BY KVL1

$$V_1 = 2 \times 10^3 I_1 + 10^3 I_2 \quad \dots(1)$$

BY KVL2

$$V_2 = 10^3 I_1 + 2 \times 10^3 I_2 \quad \dots(2)$$

From eq. (2)

$$I_1 = \frac{V_2}{10^3} - \frac{2 \times 10^3}{10^3} I_2$$

$$I_1 = 10^{-3} V_2 - 2 I_2 \quad \dots(3)$$

$$I_1 = C V_2 - D I_2 \quad \dots(4)$$

By comparing eq. (3) and eq. (4)

$$C = 10^{-3}, D = 2$$

Substituting eq. (3) in eq. (1)

$$V_1 = 2 \times 10^3 (10^{-3} V_2 - 2 I_2) + 10^3 I_2$$

$$V_1 = 2 V_2 - 3 \times 10^3 I_2 \quad \dots(5)$$

$$V_1 = A V_2 - B I_2 \quad \dots(6)$$

By comparing eq. (5) and eq. (6)

$$A = 2, B = 3 \times 10^3$$

End of Solution

Q.52 A complex load (in Ω) is represented as $\Gamma_L = 0.5 \angle 30^\circ$ on the Smith chart. A co-axial cable with a characteristic impedance of 50Ω is connected to the load. The new input impedance of the load now moves to a diametrically opposite point on the same Γ circle on the Smith chart.

Which option is the nearest input impedance of the cable connected load (in Ω)?

- (a) $20.7 - j5.1$ (b) $17.7 - j11.8$
 (c) $97.5 - j65.0$ (d) $97.5 + j65.0$

Ans. (b)

Given: $\Gamma_L = 0.5 \angle 30^\circ$; $Z_o = 50 \Omega$

As point moves to a diametrically opposite point. So, there will be a phase change of 180° , the magnitude

$$\therefore \Gamma_{L|_{\text{new}}} = 0.5 [\angle 30^\circ + \angle 180^\circ] = 0.5 \angle 210^\circ = 0.5 \angle -150^\circ$$

$$\text{So, } \Gamma_{L|_{\text{new}}} = \frac{Z_{\text{in}} - Z_o}{Z_{\text{in}} + Z_o}$$

$$\Rightarrow Z_{\text{in}} = Z_o \left[\frac{1 + \Gamma_{L|_{\text{new}}}}{1 - \Gamma_{L|_{\text{new}}}} \right]$$

$$\Rightarrow Z_{\text{in}} = 50 \left[\frac{1 + 0.5 \angle -150^\circ}{1 - 0.5 \angle -150^\circ} \right] = 50 \times 0.426 \angle -33.7^\circ$$


$$\Rightarrow Z_{\text{in}} = 21.3 \angle 33.7^\circ$$

$$\Rightarrow Z_{\text{in}} = 17.72 - j11.82 \Omega$$

End of Solution

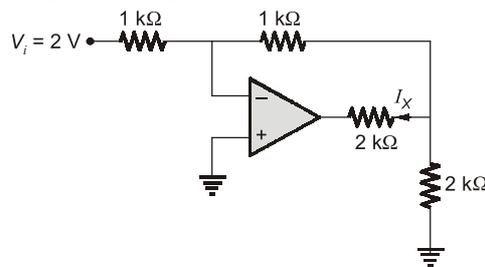
Q.53 A circuit using an ideal OP-AMP is shown in the Figure.

Which of the following options gives the correct value of the current I_x ?



- (a) 2.0 mA (b) 1.5 mA
 (c) 3.0 mA (d) 0 mA

Ans. (c)

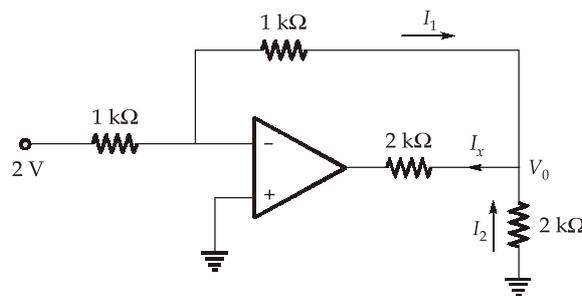

MADE EASY students top in ESE 2025

4 Streams 4 Toppers
all 4 MADE EASY Students

39 selections
in Top 10

434 selections out of
458 Vacancies (95% Selections)

CE 9 in Top 10	1 AIR MOHAMMAD SHAQUIB Live Online Foundation Course	2 AIR PRAKHAR SHRI Classroom Foundation Course	3 AIR ARJUN SHARMA Mains Online Course	4 AIR BOLLA U NANDAN Classroom Foundation Course	5 AIR KESHAV Test Series & IGP	7 AIR TUSHAR AGGARWAL Classroom Foundation Course	8 AIR AYUSH JAIN Classroom Foundation Course	9 AIR ADITYA P SINGH Test Series & IGP	10 AIR PUSHPENDRA RATHORE Test Series & IGP	
ME 10 in Top 10	1 AIR NIMESH CHANDRA Classroom Foundation Course	2 AIR ASHOK KUMAR Classroom Foundation Course	3 AIR HARI SINGH Mains Online Course	4 AIR SIDDESH RAO GS Online Course	5 AIR GOLLANGI SATEESH Mains Online Course	6 AIR AVINASH VERMA Mains Online Course	7 AIR PRASHANT SINGH Mains Offline Course	8 AIR MONU KUMAR Classroom Foundation Course	9 AIR NIKHIL KUMAR SAHA Test Series & IGP	10 AIR AMIT KUMAR SINGH Classroom Foundation Course
EE 10 in Top 10	1 AIR RAJAN KUMAR Classroom Foundation Course	2 AIR VISHNU SAINI Live Online Foundation Course	3 AIR OMPRAKASH RAJPUT Classroom Foundation Course	4 AIR TUSHAR CHAUDHARY Classroom Foundation Course	5 AIR RAM KUMAR Test Series & IGP	6 AIR PUNIT MEENA Classroom Foundation Course	7 AIR JYOTI K. PANDA Classroom Foundation Course	8 AIR D A SAI RAM REDDY Test Series & IGP	9 AIR DHURUV KAWAT Classroom Foundation Course	10 AIR AKSHIT PARASHARI Live Online Foundation Course
E&T 10 in Top 10	1 AIR UTKARSH PATHAK Live Online Foundation Course	2 AIR RAJESH TIWARI Live Online Foundation Course	3 AIR PRASHANT LAVANIA Classroom Foundation Course	4 AIR PRADEEP SHUKLA Mains Online Course	5 AIR ASHISH SINGH PATEL Classroom Foundation Course	6 AIR TANYA TYAGI Mains Online Course	7 AIR PALAK MISHRA Mains Online Course	8 AIR HAYAT ALI Classroom Foundation Course	9 AIR VIDHU SHREE Live Online Foundation Course	10 AIR RAM PAL SINGH Classroom Foundation Course

MADE EASY students top in GATE 2025

5 All India Rank 1
(CE, ME, IN, ES & EE)

45 Selections
in Top 10

399 Selections
in Top 100

1 AIR CE Abhay Singh Classroom Course	1 AIR ME Rajneesh Bijarniya Classroom Course	1 AIR EE Pradip Chauhan Test Series	1 AIR IN Kailash Goyal Classroom Course	1 AIR ES Yash Jain Classroom Course	2 AIR CE Harshvardhan Singh Classroom Course	2 AIR ME Gollangi Sateesh Online Course	2 AIR EE Kailash Goyal Classroom Course	2 AIR EC Ankush Philip John Postal Package & Test Series	
2 AIR IN S. Bhattacharya Test Series	2 AIR ES Jitesh Choudhary Classroom Course	2 AIR ES Tarun Yadav Classroom Course	3 AIR CE Pankaj Meena Classroom Course	3 AIR ME Nimesh Chandra Classroom Course	3 AIR PI Aditya Kr. Prasad Classroom Course	3 AIR XE Rohan Kr. Biswal Test Series	5 AIR CE Kartik Pokhriyal Classroom Course		
5 AIR PI Kuldeep Singh Naruka Classroom Course	5 AIR IN Sachin Yadav Test Series	5 AIR EC M. M. Nafeez Test Series	5 AIR ES Sachin Kumar Classroom Course	6 AIR PI Kaushal Kr. Kaushik Online Course	6 AIR CE Shivnand Chaurasia Online Course	6 AIR CE Nimish Upadhyay Online Course	6 AIR EE Puneet Soni Test Series	6 AIR EE Shivam Kr. Gupta Test Series	
6 AIR EC Pentela J. Bhavani Test Series	6 AIR IN Utkarsh P. Patil Classroom Course	7 AIR PI Waleed Shaikh Test Series	7 AIR ME Abhinn Online Course	7 AIR IN Dev J. Patel Test Series	7 AIR ES Ankit Kumar Classroom Course	8 AIR ME Goutam Kumar Test Series	9 AIR CE Tarun Yadav Classroom Course	9 AIR CS Omhari Test Series	9 AIR EC Chilukuri S. Charan Test Series
9 AIR XE Apar Harsh Chandra Classroom Course	10 AIR CE Adnan Quasain Classroom Course	10 AIR CE Rahul Singh Online Course	10 AIR ME Ashutosh Kumar Classroom Course	10 AIR ME Jetti Ganateja Test Series	10 AIR ME Muhammed Sinan K Test Series	10 AIR ME Pitchika Kr. Vasu Online Course	10 AIR PI M Gopu Ganesh Test Series	10 AIR EE Neelava Mukherjee Postal Package & Test Series	

Course-wise details of "top 100 rank holders of GATE 2025" and "selected candidates of ESE 2025 from MADE EASY" are available on our website.

Delhi Centre : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

MADE EASY Centres : Delhi | Bhopal | Hyderabad | Jaipur | Pune

www.madeeasy.in

Ans. (a, b, c)

Given Narrow band signal

$$x(t) = A(t)\cos[2\pi f_c t + \theta(t)]$$

- For suitable choices of $A(t)$ and $\theta(t)$; $x(t)$ represents an AM signals.

Ex.: Let $A(t) = 1 + m(t)$

$$\theta(t) = 0$$

$$x(t) = [1 + m(t)]\cos 2\pi f_c t,$$

It represents an AM signal.

- For suitable choices of $A(t)$ and $\theta(t)$; $x(t)$ represents PSK signal.

Ex.: Let $A(t)$ is a constant, $\theta(t)$ is 45° , 135° , 225° , 315° ;

Hence, $x(t)$ represents PSK signal.

- $x(t)$ represents a bandlimited Gaussian Noise process.

$$x(t) = x_i(t) \cos 2\pi f_c t - x_q(t) \sin 2\pi f_c t$$

where,

$$x_i(t) = A(t) \cos \theta(t)$$

$$x_q(t) = A(t) \sin \theta(t)$$

If $x_i(t)$ and $x_q(t)$ are Gaussian processes then $x(t)$ also represents Gaussian Process.

Hence, option (a, b, c) are correct.

- $x(t)$ can represents NBFM signal.

Ex:
$$x(t) = A(t)\cos[\underbrace{2\pi f_c t + \theta(t)}_{\theta_i(t)}]$$

$x(t)$ represents an angle modulated signal. So, can be considered as NBFM signal also. Hence option (d) is incorrect.

End of Solution

Q.58 Let $x_1(t) = \cos(2\pi nt)$ and $x_2(t) = 2\sin(4\pi nt)$ represent two sinusoids for a positive integer n and $-\infty < t < \infty$.

Which of the following statements about $x_1(t)$ and $x_2(t)$ is/are valid?

- $x_1(t)$ and $x_2(t)$ are orthogonal to each other over $0 \leq t < 1/n$.
- $x_1(t)$ and $x_2(t)$ are orthonormal to each other over $0 \leq t < 1/n$.
- $x_2(t)$ is a harmonic of $x_1(t)$.
- $x_1(t)$ and $x_2(t)$ are non-orthogonal to each other over $0 \leq t < 1/(2n)$.

Ans. (a, c, d)

$$x_1(t) = \cos 2\pi nt, x_2(t) = 2 \sin 4\pi nt$$

$$\begin{aligned} \int_0^{1/n} x_1(t) \cdot x_2(t) dt &= \int_0^{1/n} \cos 2\pi nt \cdot 2 \sin 4\pi nt dt \\ &= \int_0^{1/n} (\sin 6\pi nt + \sin 2\pi nt) dt \\ &= \left[\frac{-\cos 6\pi nt}{6\pi n} - \frac{\cos 2\pi nt}{2\pi n} \right]_0^{1/n} \\ &= \left[\frac{-\cos 6\pi + \cos 0}{6\pi n} \right] + \left[\frac{-\cos 2\pi + \cos 0}{2\pi n} \right] \end{aligned}$$

$$= \frac{-1+1}{6\pi n} + \frac{-1+1}{2\pi n} = 0$$

i.e., $x_1(t)$ and $x_2(t)$ are orthogonal over $0 \leq t < 1/n$.

Energy of $x_1(t)$ over $\left(0, \frac{1}{n}\right)$ interval is $\frac{1}{2n}$.


So, $x_1(t)$ and $x_2(t)$ are not orthonormal over $0 \leq t < 1/n$.

$$\begin{aligned} \int_0^{1/2n} x_1(t) \cdot x_2(t) dt &= \int_0^{1/2n} \cos 2\pi n t \cdot 2 \sin 4\pi n t dt \\ &= \left[\frac{-\cos 6\pi n t}{6\pi n} - \frac{\cos 2\pi n t}{2\pi n} \right]_0^{1/2n} \\ &= \left(\frac{-\cos 3\pi + \cos 0}{6\pi n} \right) + \left(\frac{-\cos \pi + \cos 0}{2\pi n} \right) \\ &= \frac{2}{6\pi n} + \frac{2}{2\pi n} = \frac{8}{6\pi n} = \frac{4}{3\pi n} \neq 0 \end{aligned}$$

i.e., $x_1(t)$ and $x_2(t)$ are non-orthogonal over $0 \leq t < \frac{1}{2n}$.

End of Solution

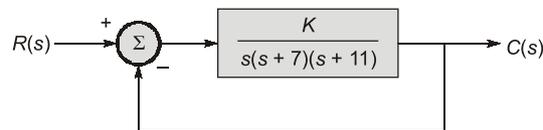- Q.59** Consider the unity negative feedback control system shown in the Figure. The value of gain $K (>0)$ at which the given system will remain marginally stable is _____. (Answer in integer)



Ans. (1386 to 1386)

We know that the characteristics equation is given as,

$$1 + G(s) H(s) = 1 + \frac{K}{s(s+7)(s+11)}$$

or $s(s^2 + 18s + 77) + K = 0$

or $s^3 + 18s^2 + 77s + K = 0$

Now using RH criteria we get

s^3	1	77
s^2	18	L
s^1	$\frac{18 \times 77 - K}{1s}$	
s^0	K	

For marginally stable system

$$18 \times 77 - K = 0$$


$$K = 18 \times 77 = 1386$$

End of Solution

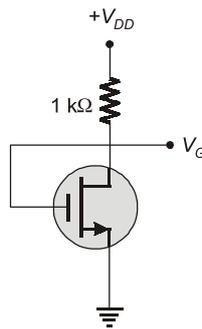
Q.60 An n -channel MOSFET is connected as shown in the Figure.

Assume $V_{TH} = 1$ V, $V_{DD} = 5$ V, and $\mu C_{ox} \left(\frac{W}{L} \right) = 2$ mA V⁻² and neglect channel length modulation effects.

The gate voltage (V_G) of the n -channel MOSFET (in Volt) is _____.
 (rounded off to two decimal places)



Ans. (2.56) (2.50 to 2.60)

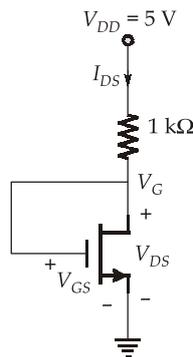

$$V_{GS} = V_{DS} = 5 - 1 \times I_{DS}$$

$$I_{DS} = 5 - V_{GS} \quad \dots(1)$$

$$I_{DS} = \frac{\mu_N C_{ox}}{2} \times \frac{W}{L} (V_{GS} - V_T)^2$$

$$5 - V_{GS} = \frac{2}{2} (V_{GS} - 1)^2$$

$$5 - V_{GS} = V_{GS}^2 + 1 - 2V_{GS}$$

$$V_{GS}^2 - V_{GS} - 4 = 0$$

$$\Rightarrow V_{GS} = 2.56 \text{ V}$$


Hence, $V_G = V_{GS} = 2.56 \text{ V}$

End of Solution


Q.61 Consider the square region R in the X - Y plane as shown with the dark shading in the

Figure. The value of $\iint_R (x^2 + y^2 - 1) dx dy$ is ____.

(rounded off to two decimal places)

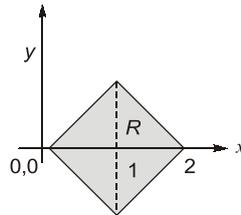

Ans. (0.66) (0.60 to 0.70)

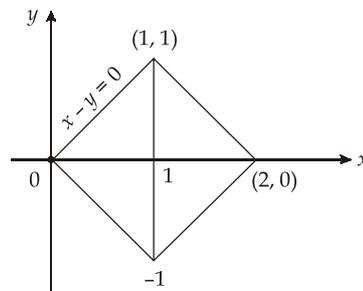

$$I = \iint_R (x^2 + y^2) dx dy - \iint_R dy dx$$

$$I = I_1 - I_2$$

$$I_1 = \int_{0-x}^1 \int_0^x (x^2 + y^2) dy dx + \int_1^2 \int_{1-(2-x)}^{(2-x)} (x^2 + y^2) dy dx$$

$$= 2 \int_0^1 \left(x^2 y + \frac{y^3}{3} \right)_0^x dx + 2 \int_1^2 \left(x^2 y + \frac{y^3}{3} \right)_0^{(2-x)} dx$$

$$= 2 \int_0^1 \frac{4}{3} x^3 dx + 2 \int_1^2 \left(x^2(2-x) + \frac{(2-x)^3}{3} \right) dx$$

$$= \frac{8}{3} \left(\frac{1}{4} \right) + 2 \left[\frac{2x^3}{3} - \frac{x^4}{4} + \frac{1}{3} \frac{(2-x)^4}{-4} \right]_1^2$$

$$= \frac{8}{12} + 2 \left[\left(\frac{16}{3} - 4 - \frac{1}{2}(0) \right) - \left(\frac{2}{3} - \frac{1}{4} - \frac{1}{12} \right) \right]$$


$$= \frac{2}{3} + 2 \left[\left(\frac{4}{3} - \frac{1}{3} \right) \right] = \frac{2}{3} + 2$$

$$I_1 = \frac{8}{3}$$


$$\begin{aligned} I_2 &= \text{Area of square} \\ \therefore I &= I_1 - I_2 \\ I &= \frac{8}{3} - \sqrt{2} \times \sqrt{2} \\ I &= \frac{8}{3} - 2 \\ I &= \frac{2}{3} \end{aligned}$$

End of Solution

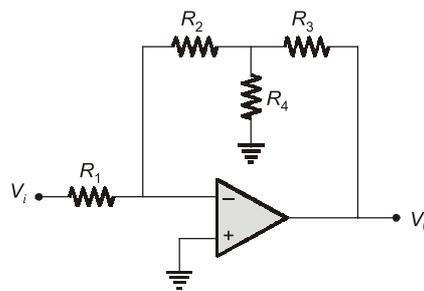- Q.62** Consider an ideal OP-AMP circuit as shown in the Figure.
 The resistances $R_1 = R_2 = R_3 = R_4 = 50 \text{ k}\Omega$.
 The magnitude of the closed loop gain is _____.
 (rounded off to two decimal places)



Ans. (2.90 to 3.10)

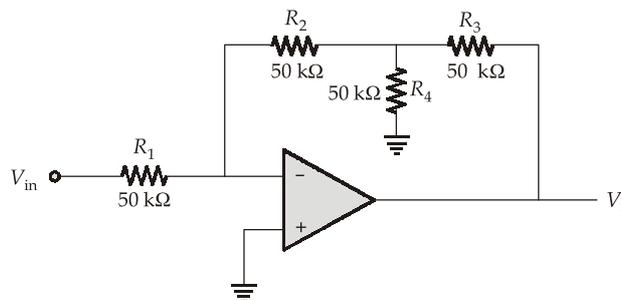

$$\begin{aligned} \frac{V_0}{V_i} &= \frac{-R_2}{R_1} \left[1 + \frac{R_3}{R_2} + \frac{R_3}{R_4} \right] \\ &= \frac{-50 \text{ k}\Omega}{50 \text{ k}\Omega} \left[1 + \frac{50 \text{ k}\Omega}{50 \text{ k}\Omega} + \frac{50 \text{ k}\Omega}{50 \text{ k}\Omega} \right] \\ &= -1[1 + 1 + 1] \\ &= -3 \end{aligned}$$

Hence, $\left| \frac{V_0}{V_i} \right| = 3$

End of Solution

Q.63 The average bit error rate at the input of a (7, 4, 1) Hamming decoder is 0.10. The probability that the decoder will fail to decode a received word correctly is _____. (rounded off to two decimal places)

Ans. (0.15) (0.10 to 0.20)

Hamming code can correct upto one error only.

Probability of decoding received code word properly will be

$$\Rightarrow P_c = P(\text{no error}) + P(\text{1-bit error}) \\ = {}^7C_0(0.1)^0(0.9)^7 + {}^7C_1(0.1)^1(0.9)^6$$

\therefore When n -bits transmitted, probability of getting error in r -bits will be ${}^nC_r P^r(1-P)^{n-r}$

$$\therefore P_c \cong 0.85$$

Probability of decoder failed to decode received codeword properly will be

$$P_e = 1 - P_c \\ = 1 - 0.85 \\ = 0.15$$

End of Solution

Q.64 Consider that the concentration of electrons in a semiconductor bar varies linearly from $2 \times 10^{17} \text{ cm}^{-3}$ at $x = 1 \mu\text{m}$ to $1 \times 10^{16} \text{ cm}^{-3}$ at $x = 4 \mu\text{m}$ along the x -direction. Assume that the concentration of electrons is not varying along other directions (that is along y and z -directions).

[Given: the mobility of electron is $1400 \text{ cm}^2 \text{ V}^{-1} \text{ s}^{-1}$, thermal voltage is 25 mV and electronic charge is $1.6 \times 10^{-19} \text{ Coulomb}$.]

The density of electron diffusion current (in A/mm^2) is _____. (rounded off to two decimal places)


Ans. (35.47) (34.50 to 36.50)

$$D_N = \mu_N \times V_T = 35 \text{ cm}^2/\text{sec} \\ \frac{dn}{dx} = \frac{\Delta n}{\Delta x} = \frac{2 \times 10^{17} - 1 \times 10^{16}}{3 \times 10^{-4} \text{ cm}} = 6.33 \times 10^{20} \text{ cm}^{-4} \\ J_{\text{Diff}} = qD_N \times \frac{dn}{dx} = 1.6 \times 10^{-19} \times 35 \times 6.33 \times 10^{20} \\ = 3547 \text{ A/cm}^2 = 35.47 \text{ A/mm}^2$$

End of Solution

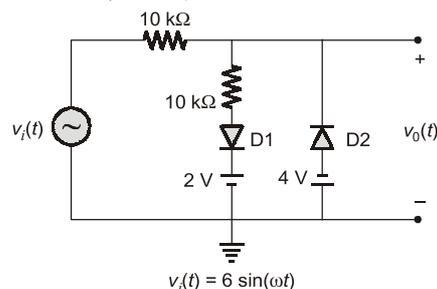
Q.65 Consider the ideal diodes D1 and D2 as shown in the Figure with cut-in voltage $V_Y = 0$ Volt and $v_i(t)$ is in Volt.

The maximum voltage (Volt) of the output $v_o(t)$ is _____. (rounded off to two decimal places)



Ans. (4) (3.70 to 4.30)

For maximum V_0
 D_1 ON and D_2 OFF

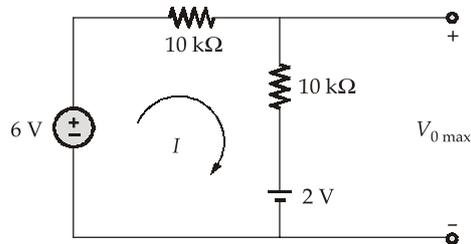

$$I = \frac{6-2}{20\text{ k}\Omega} = \frac{4}{20\text{ k}\Omega} = 0.2\text{ mA}$$

$$\begin{aligned} V_{0\text{ max}} &= I \times 10\text{ K} + 2\text{ V} \\ &= 0.2\text{ mA} \times 10\text{ K} + 2\text{ V} \\ &= 4\text{ V} \end{aligned}$$

End of Solution

