



MADE EASY

India's Best Institute for IES, GATE & PSUs

Test Centres: Delhi, Noida, Hyderabad, Bhopal, Jaipur, Lucknow, Bhubaneswar, Indore, Pune, Kolkata, Patna

ESE 2020 : Prelims Exam
CLASSROOM TEST SERIES

E & T
ENGINEERING

Test 2

Section A : Network Theory


Section B : Digital Circuits

- | | | | | |
|---------|---------|---------|---------|---------|
| 1. (d) | 16. (c) | 31. (b) | 46. (d) | 61. (c) |
| 2. (b) | 17. (a) | 32. (b) | 47. (c) | 62. (b) |
| 3. (b) | 18. (a) | 33. (c) | 48. (b) | 63. (a) |
| 4. (b) | 19. (d) | 34. (b) | 49. (b) | 64. (a) |
| 5. (c) | 20. (b) | 35. (d) | 50. (c) | 65. (b) |
| 6. (b) | 21. (b) | 36. (d) | 51. (d) | 66. (c) |
| 7. (c) | 22. (b) | 37. (b) | 52. (b) | 67. (a) |
| 8. (b) | 23. (d) | 38. (c) | 53. (c) | 68. (c) |
| 9. (a) | 24. (a) | 39. (c) | 54. (c) | 69. (c) |
| 10. (c) | 25. (b) | 40. (d) | 55. (c) | 70. (d) |
| 11. (b) | 26. (d) | 41. (d) | 56. (c) | 71. (b) |
| 12. (c) | 27. (a) | 42. (b) | 57. (a) | 72. (d) |
| 13. (b) | 28. (b) | 43. (b) | 58. (d) | 73. (d) |
| 14. (a) | 29. (b) | 44. (a) | 59. (b) | 74. (c) |
| 15. (d) | 30. (b) | 45. (b) | 60. (d) | 75. (b) |

DETAILED EXPLANATIONS
Section A : Network Theory

- (d)
 Superposition theorem can't be used for the given circuit, because while acting one source alone, the circuit violates KVL.

- (b)
 At $t = 0^-$:

 

At $t = 0^+$:

$$i_L(0^-) = \frac{10 \text{ V}}{4 \Omega} = 2.5 \text{ A}$$


$$v_C(0^-) = 0 \text{ V}$$

$$v_C(0^+) = v_C(0^-) = 0 \text{ V}$$

$$i_L(0^+) = i_L(0^-) = 2.5 \text{ A}$$

$$v_L(0^+) = -(4 \Omega) \frac{i_L(0^+)}{2}$$
 
$$= -4 \times \frac{2.5}{2} = -5 \text{ V}$$



- (b)
 Average power absorbed by a load depends only on fundamental components.

$$v(t) = 100\cos(\omega t) = 100\sin(\omega t + 90^\circ) \text{ V}$$


So,

$$P_{\text{avg(load)}} = \frac{V_1 I_1}{2} \cos \phi = \frac{100 \times 5}{2} \cos(90^\circ - 30^\circ) \text{ mW}$$

$$= 250 \cos(60^\circ) = 125 \text{ mW} = 0.125 \text{ W}$$

 - (b)
 From the given circuit, we have

$$V_1 = \frac{5 \times 10}{15} = \frac{50}{15} = \frac{10}{3} \text{ V}$$



$$\therefore V_{OC} = 3V_1 = 3 \times \frac{10}{3} = 10 \text{ V}$$

$$I_{SC} = \frac{10}{10} = 1 \text{ A}$$

$$\therefore R_{Th} = \frac{V_{OC}}{I_{SC}} = 10 \Omega$$

$$\text{so, } P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{V_{OC}^2}{4R_{Th}} = \frac{10 \times 10}{4 \times 10} = 2.5 \text{ W}$$


5. (c)

Using transmission parameters,

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$\therefore \text{parameter } D = \left. \frac{-I_1}{I_2} \right|_{V_2=0}$$

 

$$I_2 = -I_1 \times \frac{R}{R + (R/2)} = -I_1 \times \frac{2}{3}$$

$$D = \left. \frac{-I_1}{I_2} \right|_{V_2=0} = \frac{3}{2}$$


6. (b)

$$V = R_{eq} I_1$$

$$-I_1 + \frac{V}{4} + \frac{V - 2I_1}{2} = 0$$


$$\frac{V}{4} + \frac{V}{2} = 2I_1$$
 
$$\frac{V}{I_1} = R_{eq} = (8 \parallel 4) = \frac{8}{3} = 2.67 \Omega$$



 7. (c)

Redrawing the circuit after source transformation we get,




$$\frac{V_x - 10}{10} + \frac{V_x + 100}{10} + \frac{V_x}{10} = 0$$

$$3V_x + 90 = 0$$

$$V_x = -30 \text{ V}$$

$$\therefore I = -\frac{V_x}{10} = \frac{30}{10} = 3 \text{ A}$$

8. (b)

 

Let the current flowing into the circuit at the node 'a' will be I . Since the infinite network is symmetrical about 'a', the current I in going from 'a' to infinity, is divided equally along the branches aQ , aU , aP and ab as shown in the figure.

The current ' I ' then returns from infinity and is taken from the network at node 'b'.

Again by symmetry, the current flowing along the branches Rb , ab , Sb and Tb are $I/4$.

$$\therefore \text{Total current flowing along } ab \text{ is } I/4 + I/4 = I/2$$

$$\therefore V_{ab} = I/2 \times R$$

$$\therefore \text{Effective resistance } R_{ab} = R/2.$$

9. (a)

Initially,

$$C_1 = 5 \mu\text{F} \text{ and } Q_1 = 17 \mu\text{C}$$

$$C_2 = C \mu\text{F} \text{ and } Q_2 = 0$$

$$\therefore Q_T = Q_1 + Q_2 = 17 \mu\text{C} \quad \dots(i)$$

When C_1 is connected to C_2 parallelly, the charge is transferred from C_1 to C_2 . However the total charge remains equal to $17 \mu\text{C}$. Due to the law of conservation of charge, for the capacitors connected in parallel.

$$\therefore V_1 = V_2$$

$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2}$$

$$\frac{10}{5} = \frac{7}{C}$$

$$C = \frac{7}{2} = 3.5 \mu\text{F}$$

10. (c)

From z-parameter model,

$$V_1 = z_{11}I_1 + z_{12}I_2 \quad \dots(i)$$

$$V_2 = z_{21}I_1 + z_{22}I_2 \quad \dots(ii)$$

 \therefore Output port is short circuited

$$\therefore V_2 = 0$$

$$\therefore I_2 = \frac{-z_{21}}{z_{22}}I_1 \quad \dots(iii)$$

 \therefore From equation (i) and (iii),

$$V_1 = \left(z_{11} - \frac{z_{12} \times z_{21}}{z_{22}} \right) I_1$$

or

$$I_1 = \frac{V_1}{\left(z_{11} - \frac{z_{12} \times z_{21}}{z_{22}} \right)} = \frac{3}{27 - \frac{9 \times 9}{27}}$$

$$I_1 = \frac{3}{24} = \frac{1}{8} = 0.125 \text{ A} = 125 \text{ mA}$$

11. (b)

The total number of possible links are

$$l = B - n + 1$$


here,

$$B = 14$$

$$n = 8$$

$$\therefore l = 14 - 8 + 1 = 7$$

12. (c)

 At $t = 0^-$ the circuit will be drawn as

By KVL in the first loop,


$$2I + 3I - 20 = 0$$

$$I = \frac{20}{5} = 4 \text{ A}$$

$$\therefore v_C(0^-) = v_C(0^+) = 3 \times 4 = 12 \text{ V}$$

$$i_L(0^-) = i_L(0^+) = 0$$

 Now, at $t = 0^+$ the circuit can be redrawn as



$$V = \frac{3 \times 12}{2 + 3} = 7.2 \text{ V}$$

Also;

$$V = 3i(0^+) + \frac{2di(0^+)}{dt}$$

at $t = 0^+$,

$$i = 0$$

$$V = \frac{2di(0^+)}{dt}$$

or

$$\frac{di(0^+)}{dt} = \frac{V}{2} = \frac{7.2}{2} = 3.6 \text{ A/s}$$

13. (b)

The degree of each node in a fully connected graph is equal to $(n - 1)$

14. (a)

For the given circuit

$$L_{eq} = L_1 + L_2 \pm 2M$$

where

$$M \propto \sqrt{L_1 L_2}$$

and

$$L \propto N^2$$

when number of turns get halved,

$$L'_1 = \frac{1}{4}L_1$$

and

$$L'_2 = \frac{1}{4}L_2$$

$$L'_{eq} = \frac{1}{4}L_1 + \frac{1}{4}L_2 \pm \frac{1}{4} \times 2M$$

$$L'_{eq} = \frac{1}{4}(L_{eq})$$

\therefore

$$f'_0 = \frac{1}{2\pi\sqrt{L'_{eq}C}} = \frac{1}{2\pi\sqrt{\frac{1}{4}L_{eq}C}}$$


$$= \frac{2}{2\pi\sqrt{L_{eq}C}} = 2f_0$$

15. (d)

$$i(t) = \frac{1}{8}e^{-t/2}\text{A} \quad (\text{given})$$

$$\therefore I(s) = \frac{1}{8\left(s + \frac{1}{2}\right)} = \frac{2}{8(2s+1)} = \frac{1}{4(2s+1)} \quad \dots(\text{i})$$

as per the question,

 

The KVL equation in the loop

$$\frac{1}{s} = \left(R + \frac{1}{Cs}\right)I(s)$$

$$\frac{1}{s} = \left(\frac{1+RCs}{Cs}\right)I(s)$$

$$I(s) = \frac{C}{(1+RCs)} \quad \dots(\text{ii})$$

Comparing with equation (i), we get

$$C = \frac{1}{4} = 0.25 \text{ F}$$

and


$$RC = 2$$

$$R \times \frac{1}{4} = 2$$

$$R = 8 \Omega$$

16. (c)

The circuit can be redrawn as

 

By applying KVL in loop (i), we get,

$$3V_x = 6i_1 + 12i_1 + 6(i_1 - i_2)$$

$$3V_x = 24i_1 - 6i_2 \quad \dots(\text{i})$$

by applying KVL in loop (ii), we get

$$V_{ab} = 12i_2 + 3V_x + 6(i_2 - i_1)$$

$$\begin{aligned} V_{ab} &= 18i_2 + 3[12 \times i_1] - 6i_1 \\ &= 18i_2 + 36i_1 - 6i_1 \end{aligned}$$

$$V_{ab} = 18i_2 + 30i_1 \quad \dots(\text{ii})$$

∴ From equation (i) $3(12i_1) = 24i_1 - 6i_2$
 $36i_1 - 24i_1 = -6i_2$

or $i_1 = \frac{-6}{12}i_2 \quad \dots(\text{iii})$

∴ From equation (ii) and (iii)

$$V_{ab} = 18i_2 - 30\left(\frac{1}{2}\right)i_2 = (18 - 15)i_2$$

$$V_{ab} = 3i_2$$

or $\frac{V_{ab}}{i_2} = 3 \Omega$

17. (a)

From the given characteristics, it is clear that,


when $V = 0 \text{ V}$ (short circuit)

$$I = -3 \text{ A}$$

and when $V = 15 \text{ V}$

$I = 0 \text{ A}$ (open circuit)

∴ Network becomes,

 

$$V_{OC} = 15 \text{ V}$$

$$I_{SC} = -I = 3 \text{ A}$$

∴ $R_{Th} = \frac{15}{3} = 5 \Omega$

and maximum power transferred is

$$P_{\max} = \frac{V_{OC}^2}{4R_{Th}} = \frac{(15)^2}{4 \times 5} = \frac{15 \times 15}{20}$$

$$= \frac{45}{4} = 11.25 \text{ W}$$

18. (a)

Here

$$Z_L = j\omega L = j \times 1000 \times 10^{-3} = j$$


and

$$Z_C = \frac{1}{j\omega C} = \frac{-j}{1000 \times 10^{-3}} = -j$$

$$\begin{aligned} \therefore Z_{eq} &= 1 + (Z_L \parallel Z_C) \\ &= 1 + \frac{(j)(-j)}{-j+j} = 1 + \frac{1}{0} = \infty \\ \therefore I &= 0 \end{aligned}$$

 
19. (d)

In order to obtain Norton's equivalent across the terminals 'b' and 'c' the circuit can be redrawn as



$$\begin{aligned} \therefore I_{sc} &= \frac{17-5}{10} = 1.2 \text{ A} \\ \text{and} \\ R_{Th} &= \frac{10 \times 20}{20+10} = 6.67 \Omega \end{aligned}$$

20. (b)

 


22. (b)

The reciprocity theorem is not applicable to the circuits with time varying elements.

23. (d)

Considering the given circuit,

 

$$V_{Th} = -2R_3I_x + R_2I_x = (R_2 - 2R_3)I_x$$

V_{Th} will be equal to zero, when $R_2 = 2R_3$.

In option (a) $\Rightarrow R_2 = 15 \Omega$ and $R_3 = 30 \Omega \Rightarrow R_2 \neq 2R_3$

In option (b) $\Rightarrow R_2 = 15 \Omega$ and $R_3 = 10 \Omega \Rightarrow R_2 \neq 2R_3$

In option (c) $\Rightarrow R_2 = 20 \Omega$ and $R_3 = 40 \Omega \Rightarrow R_2 \neq 2R_3$


In option (d) $\Rightarrow R_2 = 20 \Omega$ and $R_3 = 10 \Omega \Rightarrow R_2 = 2R_3$

So, option (d) is correct.

25. (b)

Here, the 8Ω resistance in parallel with the 16 V source can be ignored.

\therefore the circuit can be redrawn as

 

By KVL in the outer loop, we get,

$$4I' - KI + 16 + 2(I' - 6) = 0$$

or
$$I' = \frac{KI - 4}{6} \quad \dots(i)$$

Also,
$$I = 6 - I' = 6 - \left(\frac{KI - 4}{6}\right) = \frac{40 - KI}{6}$$

or
$$I = \frac{40}{6 + K} \quad \dots(ii)$$

\therefore The power dissipated in the 2Ω resistor is 50 W .

\therefore
$$P_{2\Omega} = I^2 \times 2$$

$$50 = \left(\frac{40}{6 + K}\right)^2 \times 2$$

$$\frac{40}{6 + K} = \sqrt{25} = 5$$

or
$$40 = 30 + 5K$$

or
$$K = 2$$

26. (d)

For maximum power transfer

$$Z_L = Z_s^* = (R_s + jX_s)^* = R_s - jX_s$$

$$I = \frac{V_m \angle 0^\circ}{Z_s + Z_L} = \frac{V_m}{2R_s}$$

$$\therefore \text{Average power, } P_{\text{avg}} = \frac{1}{2} I^2 R = \frac{1}{2} \frac{V_m^2}{(2R_s)^2} \times R_s = \frac{V_m^2}{8R_s}$$

27. (a)

Here $v_0(t)$ is negative means current direction is opposite in the coils

$$\therefore v_0(t) = \frac{M di_1(t)}{dt}$$

$$M = \frac{|v_0(t)|}{\left| \frac{di_1(t)}{dt} \right|} = \frac{40}{16} = 2.5 \text{ H}$$

28. (b)

For a symmetrical two port network,

$$z_{11} = z_{22}$$

$$y_{11} = y_{22}$$


$$\Delta h = 1$$

and

$$A = D$$

29. (b)

The circuit can be redrawn as,

 When $I = 0$,

$$40 \text{ V} = 5R$$

$$R = 8 \Omega$$

30. (b)

At $t = 0^-$ when switch was closed.

The voltage across the capacitor is


$$v(0^-) = \frac{10 \times 2}{5} = 4 \text{ V}$$

 \therefore Capacitor does not allow the sudden changes in the voltage across it.

$$\therefore v(0^-) = v(0^+) = 4 \text{ V}$$

31. (b)

For a series RC circuit,

 

Here,

$$V_C = \frac{V_S}{R + \frac{1}{j\omega C}} \left(\frac{1}{j\omega C} \right) = \frac{V_S}{j\omega RC + 1}$$

Phase difference between V_S and V_C

$$\phi = \tan^{-1} \omega RC$$

As $\omega \uparrow \phi \uparrow$; $R \uparrow \phi \uparrow$; $C \uparrow \phi \uparrow$

As $\omega \downarrow \phi \downarrow$

32. (b)

The time constant for RC circuit is

$$\tau = R_{eq} C_{eq}$$

here,

$$R_{eq} = 2 \Omega$$

and

$$C_{eq} = \frac{(4 F + 4 F)(8 F)}{(4 F + 4 F) + 8 F} = \frac{8 F \times 8 F}{16 F} = 4 F$$

\therefore

$$\tau = 2 \times 4 = 8 \text{ sec}$$

33. (c)

$$H(s) = \frac{V_0(s)}{I(s)} = \frac{(s+1)}{(5s+8)(3s+2)}$$

\therefore

$$i(t) = 4u(t) \Rightarrow I(s) = 4/s$$

\therefore

$$V_0(s) = \frac{(s+1)}{(5s+8)(3s+2)} \times 4/s$$

\therefore Final value,

$$\begin{aligned} \lim_{s \rightarrow 0} sV_0(s) &= \lim_{s \rightarrow 0} \frac{(s+1)}{(5s+8)(3s+2)} \times 4 \\ &= \frac{1}{8 \times 2} \times 4 = \frac{4}{16} = \frac{1}{4} = 0.25 \end{aligned}$$

34. (b)

From h -parameter model,

$$V_1 = h_{11}I_1 + h_{12}V_2 \quad \dots(i)$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \quad \dots(ii)$$

From transmission parameter model,

$$V_1 = AV_2 - BI_2 \quad \dots(iii)$$

$$I_1 = CV_2 - DI_2 \quad \dots(\text{iv})$$

where,

$$B = \left. \frac{-V_1}{I_2} \right|_{V_2=0}$$

∴ From equation (i) and (ii), keeping $V_2 = 0$, we get,

$$B = \frac{-h_{11}}{h_{21}}$$

35. (d)

Power efficiency of the source can be more than 50%. But power efficiency will be 50% when maximum power is being delivered to R_L .

36. (d)

Power factor in any circuit is given by $\cos \phi$ where ϕ is the angle between voltage and current in the circuit.

∴ The voltage across and current through the capacitor are in phase quadrature.

$$\therefore \phi = 90^\circ$$

and $\cos 90^\circ = 0$ (Power factor)

38. (c)

Any combination and interconnection of network elements like resistor, capacitor, inductor or electrical energy sources are known as networks, however a closed energized network is known as a circuit. A network need not contain energy source but a circuit must contain energy source.

Section B : Digital Circuits

39. (c)

$$f(x_1 x_2 x_3) = \Pi M(0, 1, 5)$$

$x_2 x_3$	00	01	11	10
x_1	0	1	1	0
0	0	0	1	1
1	1	0	1	1

$$f(x_1 x_2 x_3) = x_2 + x_1 \bar{x}_3$$

40. (d)

$$\begin{aligned} f &= \bar{x}_1 \bar{x}_2 I_0 + \bar{x}_1 x_2 I_1 + x_1 \bar{x}_2 I_2 + x_1 x_2 I_3 \\ &= \bar{x}_1 \bar{x}_2 x_3 + \bar{x}_1 x_2 \bar{x}_3 + x_1 \bar{x}_2 \bar{x}_3 + x_1 x_2 x_3 \\ &= (x_1 \odot x_2) x_3 + (x_1 \oplus x_2) \bar{x}_3 \\ &= x_1 \oplus x_2 \oplus x_3 \end{aligned}$$

41. (d)

For $S = 1, f = (A + B) \Rightarrow$ OR gate
 for $S = 0, f = \bar{B} \Rightarrow$ NOT gate

42. (b)

For minimum value of 'y' the value of 'x' should be minimum
 \therefore minimum value of $x = 4$
 $\therefore (23)_4 + (21)_4 = (110)_4 = (4^2 + 4 + 0)_{10} = (20)_{10}$

43. (b)

$$f = (x\bar{y} + \bar{x}y) \oplus x = \bar{y} \oplus x$$


$$= \bar{x}\bar{y} + xy = x \odot y$$

44. (a)

$$Q^+ = Q \oplus X = Q\bar{X} + \bar{Q}X$$


Hence, it represents a T-flip-flop.

45. (b)

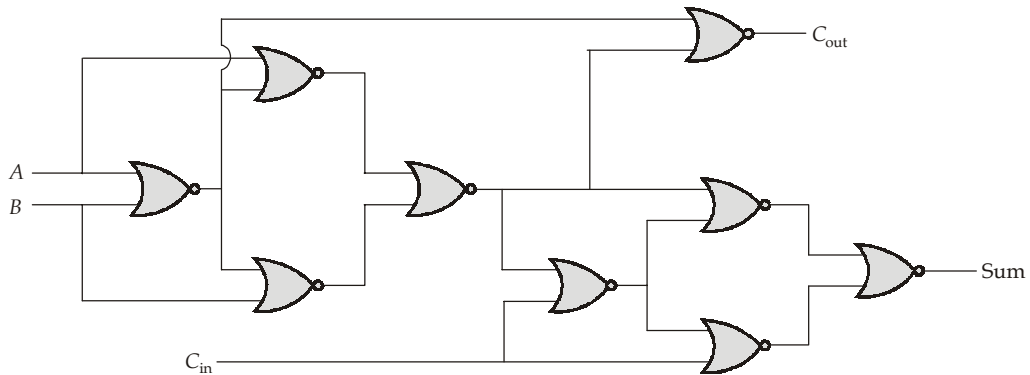

So, minimum 9 two-input NOR gates are required to design a full-adder circuit.

46. (d)

 

Therefore, the simplified expressions can be given as:

$$f(A,B,C,D) = \bar{A}\bar{B} + CD$$

$$= \bar{A}D + CD = \bar{A}\bar{B}D + CD$$

47. (c)

$$F(ABCD) = \bar{A} + \bar{B} + \bar{A}\bar{C}\bar{D} + \bar{A}\bar{B}C + \bar{A}C\bar{D} + \bar{B}C\bar{D}$$

$$= \bar{A}(1 + \bar{C}\bar{D} + \bar{B}C + C\bar{D}) + \bar{B}(1 + C\bar{D}) = \bar{A} + \bar{B} = \overline{AB}$$

thus, only one two-input NAND gate is required.


49. (b)

$$D = \bar{B}Q_n + A$$

which is equal to the excitation equation of a SR-flip flop

$$D = \bar{R}Q_n + S$$

50. (c)

 

$$f(A, B, C, D) = \bar{C}D + AD + \bar{B}D + A\bar{B}\bar{C}$$

51. (d)

$$f(w, x, y, z) = \Sigma m(4, 5, 7, 8, 10, 12, 15)$$

wx	$\bar{y}\bar{z}$	$\bar{y}z$	yz	$y\bar{z}$	
00	0	0	0	0	$I_0 = 0$
01	1	1	1	0	$I_1 = \bar{y} + z$
11	1	0	1	0	$I_3 = y \odot z$
10	1	0	0	1	$I_2 = \bar{z}$

∴

$$I_1(B) = \bar{y} + z$$

$$I_3(A) = y \odot z$$

52. (b)

Q_A	Q_B	T_A ($Q_A + Q_B$)	T_B ($\bar{Q}_A + Q_B$)	Q_A^+	Q_B^+
0	0	0	1	0	1
0	1	1	1	1	0
1	0	1	0	0	0
0	0	0	1	0	1

Thus, MOD = 3

53. (c)

$$f_i = 2 \text{ kHz}$$

$$f_0 = 256 \text{ kHz}$$

$$\therefore \text{MOD} = \frac{256}{2} = 128$$

$$\therefore n = \lceil \log_2(\text{MOD}) \rceil = 7$$

54. (c)

$$f_{\text{out}} = I_0 + I_1 + I_3 + I_6 + I_7$$

$$f_{\text{out}} = \bar{C}\bar{B}\bar{A} + \bar{C}\bar{B}A + \bar{C}BA + C\bar{B}\bar{A} + CBA$$

$$= \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + AB\bar{C} + \bar{A}BC + ABC$$

$$f_{\text{out}}(A, B, C) = \Sigma m(0, 4, 6, 3, 7) = \Sigma m(0, 3, 4, 6, 7)$$

55. (c)

$$Z = 1 \text{ thus } A > B$$

$$X = 1 \text{ thus } A = B$$

but if $X = 0$ and $Z = 0$, then $Y = 1$, and hence $A < B$.

56. (c)

$$\text{Total states} = 14$$

$$\therefore f_{\text{out}} = \frac{50 \times 10^3}{14} = 3.57 \text{ kHz}$$

58. (d)

$$2r + 3 + 4r + 4 + r + 4 + 3r + 2 = 2r^2 + 2r + 3$$

$$10r + 13 = 2r^2 + 2r + 3$$

$$2r^2 - 8r - 10 = 0$$

$$r^2 - 4r - 5 = 0$$

$$r = 5, -1$$

\therefore Radix cannot be negative

$$\therefore r = 5$$

59. (b)

3-bit gray code is

000

001

011


010

110

111

101

100

 


60. (d)

The circuit will combine two 4-bit ADC and will result in an 8-bit ADC circuit. It is used to reduced number of comparator in the circuit.

61. (c)

	CD			
	00	01	11	10
AB	00	01	11	10
	00	01	11	10
	01	01	11	10
	11	01	11	10
	10	01	11	10

62. (b)

 

$$Y = ABC + B\bar{C} \quad [\because \text{The nodes acts as wired OR logic}]$$

$$= B(AC + \bar{C}) = B(A + \bar{C})$$

63. (a)

$$F(A, B, C \dots) = A + \bar{A}B(1 + C + \bar{C}D + \bar{C}\bar{D}E + \dots)$$

$$= A + \bar{A}B$$

$$= A + B \Rightarrow \text{two NOR gates are required.}$$

65. (b)

Min decimal base $\Rightarrow x = 7$

$$\therefore (216)_7 = 2 \times 7^2 + 7 + 6$$

$$= 2 \times 49 + 7 + 6 = 98 + 7 + 6 = (111)_{10}$$

66. (c)

The decimal equivalent of number 44 can be represented as

$$(44)_{10} = (00101100)_2$$

Now, 2's complement representation of $(-44)_{10} = (11010100)_2$

67. (a)

	BC			
	00	01	11	10
A	0	0	1	1
	0	0	1	1
	1	0	0	1

F_1

	BC			
	00	01	11	10
A	0	1	0	1
	0	1	0	1
	1	0	1	1

F_2

∴

$$F_1 \times F_2 =$$

BC		00	01	11	10
A	0	0	0	0	1
A	1	0	0	0	1

∴

$$F_1 F_2 = B\bar{C}$$

68. (c)

$$F(A, B, C) = \bar{A}C + \bar{B}$$

The following function can be represented on a K-map as

	BC		00	01	11	10
A	0	1	1	1	0	
A	1	1	1	0	0	

To calculate the maxterms we just have to see the position of zeros.


∴

$$F(A, B, C) = \Pi M(2, 6, 7)$$

70. (d)

$$\begin{aligned}
 F &= (\overline{A\bar{B} + \bar{A}B + C})(\bar{C} + A\bar{B} + \bar{A}B) \\
 &= \overline{A\bar{B} + \bar{A}B} \cdot \bar{C} + (A\bar{B} + \bar{A}B) \cdot C \\
 &= (\bar{A}\bar{B} + AB)\bar{C} + A\bar{B}C + \bar{A}BC \\
 &= \bar{A}\bar{B}\bar{C} + AB\bar{C} + A\bar{B}C + \bar{A}BC
 \end{aligned}$$

71. (b)

 

J_1	K_1	J_0	K_0	$Q_1(t+1)$	$Q_0(t+1)$
Q_0	\bar{Q}_0	\bar{Q}_1	\bar{Q}_1	0	0
0	1	1	1	0	1
1	0	1	1	1	0
0	1	0	0	0	0

} 3 stable state
→ Repeat

Hence, the circuit is a mod-3 counter.

72. (d)
ROM is an example of a combinational circuit.
73. (d)
The time required for addition in a parallel adder does not depend upon the number of input bits.
74. (c)
In TDM, MUX can be used at transmitting end and DeMUX can be used at receiving end.

○○○○