

**MADE EASY**

India's Best Institute for IES, GATE & PSUs

Test Centres: Delhi, Noida, Hyderabad, Bhopal, Jaipur, Lucknow, Bhubaneswar, Indore, Pune, Kolkata, Patna**ESE 2020 : Prelims Exam**
CLASSROOM TEST SERIES**E & T**
ENGINEERING**Test 4****Section A :** Control Systems + Microprocessors and Microcontroller**Section B :** Network Theory-1**Section C :** Digital Circuits-1


- | | | | | |
|---------|---------|---------|---------|---------|
| 1. (a) | 16. (d) | 31. (a) | 46. (c) | 61. (b) |
| 2. (a) | 17. (c) | 32. (d) | 47. (c) | 62. (b) |
| 3. (d) | 18. (c) | 33. (d) | 48. (b) | 63. (c) |
| 4. (c) | 19. (b) | 34. (a) | 49. (d) | 64. (b) |
| 5. (b) | 20. (c) | 35. (d) | 50. (b) | 65. (b) |
| 6. (d) | 21. (a) | 36. (d) | 51. (c) | 66. (d) |
| 7. (c) | 22. (b) | 37. (b) | 52. (a) | 67. (c) |
| 8. (c) | 23. (c) | 38. (c) | 53. (a) | 68. (c) |
| 9. (c) | 24. (a) | 39. (a) | 54. (a) | 69. (b) |
| 10. (c) | 25. (a) | 40. (c) | 55. (d) | 70. (c) |
| 11. (a) | 26. (d) | 41. (d) | 56. (c) | 71. (a) |
| 12. (d) | 27. (d) | 42. (c) | 57. (b) | 72. (a) |
| 13. (c) | 28. (c) | 43. (b) | 58. (b) | 73. (c) |
| 14. (b) | 29. (c) | 44. (c) | 59. (a) | 74. (a) |
| 15. (a) | 30. (a) | 45. (d) | 60. (d) | 75. (b) |

DETAILED EXPLANATIONS

Section A : Control Systems + Microprocessors and Microcontroller


1. (a)

$$C_1 = \frac{10(s+1)}{(s+10)}$$

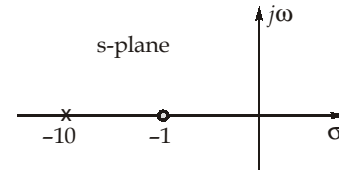zero at $s = -1$ pole at $s = -10$ 

As zero is closer to origin, zero dominates pole. Hence C_1 is a lead compensator.

$$C_2 = \frac{s+10}{10(s+1)}$$

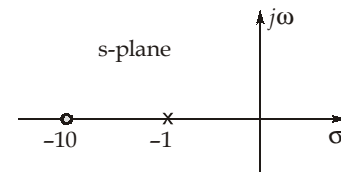zero at $s = -10$ pole at $s = -1$ 

As pole is closer to origin, pole dominates zero. Hence C_2 is a lag compensator.

2. (a)

Given,

$$G(s) = \frac{16}{s(s+8)}$$

Damped frequency, $\omega_d = \omega_n \sqrt{1 - \xi^2}$

Characteristic equation, $s^2 + 8s + 16 = 0$

$\therefore \omega_n = 4 \text{ rad/sec}$

$\xi = 1$

$\therefore \omega_d = 0$

4. (c)

Given,

$$G(s) = \frac{K(s+10)(s+20)}{s^2(s+2)}$$

characteristic equation,

$$s^2(s+2) + K(s+10)(s+20) = 0$$

$$s^3 + 2s^2 + Ks^2 + 200K + 30Ks = 0$$

$$s^3 + (K+2)s^2 + 30Ks + 200K = 0$$

For closed loop system to be stable,

$$(30K)(K+2) > 200K$$

$$K+2 > \frac{20}{3}$$

$$K > \frac{20}{3} - 2$$

$\therefore K > 4.67$

6. (d)

$$\begin{aligned} \therefore \frac{Y(s)}{R(s)} &= \frac{\frac{3K}{2s+1}}{1 + \frac{3K}{2s+1}} = \frac{3K}{2s+1+3K} \\ &= \frac{3K}{(1+3K)\left(1+s\frac{2}{1+3K}\right)} = \frac{\frac{3K}{1+3K}}{1+s\frac{2}{1+3K}} \end{aligned}$$

By comparing the above transfer function with $\frac{K}{1+s\tau}$ (1st order transfer function), we get,

$$\begin{aligned} \tau &= \frac{2}{1+3K} = 0.2 \\ 1+3K &= 10 \\ K &= 3 \end{aligned}$$

7. (c)

$$\begin{aligned} t_p &= \frac{\pi}{\omega_d} \\ 5 &= \frac{\pi}{\omega_d} \\ \therefore \omega_d &= \frac{\pi}{5} \end{aligned}$$

now, first undershoot occurs at $\frac{2\pi}{\omega_d}$

$$t_{\text{undershoot}} = \frac{2\pi}{\left(\frac{\pi}{5}\right)} = 10 \text{ sec}$$

8. (c)

From the given data,

$$G(s) = \frac{K}{s(s+2)} \text{ for type-1 system}$$

$$\frac{C(s)}{R(s)} = \frac{K}{s^2 + 2s + K}$$

$$2\xi\omega_n = 2 \Rightarrow \xi = \frac{1}{\omega_n} = \frac{1}{\sqrt{K}}$$

$$\therefore K = \left(\frac{1}{\xi}\right)^2 = \frac{1}{(0.4)^2} = 6.25$$

Steady state error for $r(t) = 4tu(t)$,

$$e_{ss} = \frac{4}{K_v}$$

where,

$$K_v = \lim_{s \rightarrow 0} sG(s) = \lim_{s \rightarrow 0} s \frac{6.25}{s(s+2)} = \frac{6.25}{2}$$

\therefore

$$e_{ss} = \frac{4}{K_v} = \frac{8}{6.25} = 1.28$$

10. (c)

Here,

Number of poles at RHS of s -plane = 1

$$N = P - Z$$

$$N = 1 - Z$$

and

$$N = -1$$

\therefore

$$-1 = 1 - Z$$

or

$$Z = 2$$

11. (a)

$$\frac{C(s)}{R(s)} = T(s) = \frac{G}{1+GH} = \frac{200}{5} = 40$$

$$\frac{\partial G}{G} = 10\% = 0.1$$

$$S_G^T = \frac{\partial T}{T} \times \frac{G}{\partial G} = \frac{1}{1+GH} = \frac{1}{5}$$

$$\frac{\partial T}{T} \times 100 = \frac{1}{5} \times 0.1 \times 100 = 2\%$$

12. (d)

Given,

$$G(s) = \frac{5(1+0.25s)}{(1+0.01s)}$$

By comparing with standard equation,

$$G(s) = \frac{\alpha(1+Ts)}{(1+\alpha Ts)}$$


We get,

$$T = 0.25 \text{ and } \alpha T = 0.01$$

Maximum phase compensation occurs at frequency,

$$\omega_m = \sqrt{\frac{1}{\alpha T} \times \frac{1}{T}} = \sqrt{\frac{1}{0.25} \times \frac{1}{0.01}} = \frac{1}{0.5 \times 0.1} = \frac{100}{5} = 20 \text{ rad/sec}$$

13. (c)

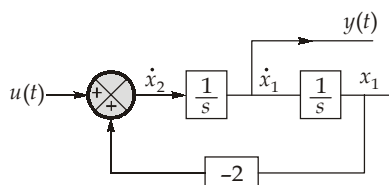

$$y = x_2$$

$$\dot{x}_1 = x_2$$

$$\dot{x}_2 = u - 2x_1$$

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -2 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u$$

$$[y] = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + [0]u$$

$$\therefore A = \begin{bmatrix} 0 & 1 \\ -2 & 0 \end{bmatrix}, B = \begin{bmatrix} 0 \\ 1 \end{bmatrix} \text{ and } C = \begin{bmatrix} 0 & 1 \end{bmatrix}$$

For controllability,

$$Q_C = [B \quad AB]$$

$$Q_C = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \Rightarrow |Q_C| \neq 0$$

Hence the given system is controllable.

For observability,

$$Q_O = \begin{bmatrix} C \\ CA \end{bmatrix}$$

$$Q_O = \begin{bmatrix} 0 & 1 \\ -2 & 0 \end{bmatrix} \Rightarrow |Q_O| \neq 0$$

Hence the given system is observable.

14. (b)

There are "6" poles symmetric about the origin. So, there exists a row of zeros in the RH table which causes an auxiliary equation of order 6. Hence, s^5 row will have all zeros in the RH table.

To have row of zeros in the s^5 row,

$$\frac{\alpha + 4}{(-6)} = -1$$

$$\alpha + 4 = 6$$

$$\alpha = 2$$

s^8	1	-2	-25	α	24
s^7	1	4	-1	-4	0
s^6	-6	-24	$(\alpha + 4)$	24	0
s^5					

15. (a)

Given,
$$\frac{C(s)}{R(s)} = \frac{Ks + \beta}{s^2 + s\alpha + \beta}$$

Open-loop transfer function,
$$G(s) = \frac{Ks + \beta}{s^2 + s\alpha + \beta - (Ks + \beta)}$$

$$= \frac{Ks + \beta}{s^2 + (\alpha - K)s} = \frac{Ks + \beta}{s[s + (\alpha - K)]}$$

The given system is type-1 system. So, e_{ss} due to step input is zero.

16. (d)

$$\frac{C(s)}{R(s)} = \frac{KG}{1 + KGH}$$

$$C(s) = \frac{KG}{1 + KGH} R(s)$$

$$C(s) = \frac{1}{\left(\frac{1}{KG} + H\right)} R(s)$$

If $KG \gg 1$, then

$$C(s) = \frac{R(s)}{H}$$

17. (c)

$$\frac{C(s)}{R(s)} = \frac{25}{s^2 + 6s + 25}$$

$$\omega_n = 5 \text{ rad/sec}$$

$$2\xi \omega_n = 6$$

∴

$$\xi = 0.6$$

$$t_p = \frac{\pi}{\omega_d}$$

$$= \frac{\pi}{\omega_n \sqrt{1 - \xi^2}} = \frac{\pi}{5\sqrt{1 - (0.6)^2}} = \frac{\pi}{4} = 0.79 \text{ sec}$$

18. (c)

The given system is type 1 and order 3 system having transfer function,

$$G(s) = \frac{K}{s(s+2)(s+3)}$$

$$[G(j\omega)]_{\omega=0} = \infty \angle -90^\circ$$

$$[G(j\omega)]_{\omega=\infty} = 0 \angle -270^\circ$$

Thus, option (c) is the correct choice.

19. (b)

When a zero is added to the system in LHS of s -plane,

- Root locus shifts away from $j\omega$ -axis.
- Damping improves, hence less oscillatory.
- Relative stability increases.
- Range of K for stable operation increases.

20. (c)

Since, the system is of minimum phase system, it has no poles or zeros in the right hand side of s -plane.

There are four corner frequencies for the transfer function $G(s)$.

- (i) Two poles at $\omega_1 = 5$ rad/sec as slope changes by -40 dB/dec.
- (ii) Two zeros at $\omega_2 = 20$ rad/sec as slope changes by $+40$ dB/dec.
- (iii) Two poles at $\omega_3 = 40$ rad/sec as slope changes by -40 dB/dec.
- (iv) A pole at $\omega_4 = 100$ rad/sec as slope changes here by -20 dB/dec.

Therefore open loop transfer function in time constant form;

$$G(s) = \frac{K \left(1 + \frac{s}{20}\right)^2}{\left(1 + \frac{s}{5}\right)^2 \left(1 + \frac{s}{40}\right)^2 \left(1 + \frac{s}{100}\right)}$$

\therefore Initial slope = 0 dB

then, $20 \log K = 40$ dB

or $K = 100$

Now open loop transfer function,

$$G(s) = \frac{100 \times 25 \times 40^2 \times 100(s+20)^2}{20^2(s+5)^2(s+40)^2(s+100)} = \frac{10^6(s+20)^2}{(s+5)^2(s+40)^2(s+100)}$$

21. (a)

Using Routh's array, we get,

s^4	1	15	K
s^3	25	20	0
s^2	$\frac{355}{25}$	K	0
s^1	$\frac{284 - 25K}{355/25}$	0	0
s^0	K	0	0

For the system to be marginally stable

$$\frac{284 - 25K}{355/25} = 0$$

or, $25K = 284$

or, $K = \frac{284}{25} = 11.36$

22. (b)

Point $s = (-1 + j)$ lie on the root locus, therefore the magnitude condition is

$$\left| \frac{K}{(-1+j)((-1+j)^2 + 7(-1+j) + 12)} \right| = 1$$

or,

$$\begin{aligned} K &= \left| (-1+j)((-1+j)^2 - 7 + 7j + 12) \right| \\ &= \left| (-1+j)[-1-2j+1-7+7j+12] \right| \\ &= \left| (-1+j)(5+5j) \right| = \left| -5 + 5j - 5j - 5 \right| \\ K &= \left| -10 \right| = 10 \end{aligned}$$

23. (c)

$$M_r = \frac{1}{2\xi\sqrt{1-\xi^2}} = \frac{1}{2 \times \frac{1}{\sqrt{2}} \times \sqrt{1-\frac{1}{2}}} = \frac{1}{2 \times \frac{1}{\sqrt{2}} \times \frac{1}{\sqrt{2}}} = 1$$

24. (a)

From figure (B), the closed loop transfer function,

$$\frac{C(s)}{R(s)} = \frac{G}{s+3} + 1$$

$$\text{From figure (A),} \quad \frac{C(s)}{R(s)} = \frac{(s+4)}{(s+3)}$$

$$\text{On equating both, we get,} \quad \frac{G}{s+3} + 1 = \frac{s+4}{s+3}$$

$$\frac{G+s+3}{s+3} = \frac{s+4}{s+3}$$

$$G+s+3 = s+4$$

$$G = 1$$

26. (d)

Forward paths:

$$P_1 = 2 \times 3 \times 4 = 24$$

$$P_2 = 8$$

Loops:

$$L_1 = -1, L_2 = -1, L_3 = -24, L_4 = -24,$$

Non touching loops:

$$L_1L_2 = 1 \text{ and } L_1L_3 = 24$$

$$\Delta_1 = 1$$

$$\Delta_2 = 1 - (L_1 + L_2) + L_1L_2 = 1 + 2 + 1 = 4$$

 \therefore

$$\begin{aligned} \frac{C(s)}{R(s)} &= \frac{P_1 \Delta_1 + P_2 \Delta_2}{1 - [L_1 + L_2 + L_3 + L_4] + [L_1L_2 + L_1L_3]} \\ &= \frac{24 \times 1 + 8 \times 4}{1 + 1 + 1 + 24 + 24 + 1 + 24} = \frac{24 + 32}{76} = \frac{56}{76} = \frac{14}{19} \end{aligned}$$

27. (d)

$$\text{Vector location of ISR} = 003\text{CH} = (3 \times 16 + 12)_{10} = (60)_{10}$$

$$\frac{60}{8} = 7.5$$

So, the interrupt is RST 7.5.

29. (c)

MVI C, 10H ; (7 T × 1 time) ⇒ 7 T
 LOOP: NOP ; (4 T × 16 times) ⇒ 64 T
 DCR C ; (4 T × 16 times) ⇒ 64 T
 JNZ LOOP ; (10 T × 15 times + 7 T) ⇒ 157 T
 NOP ; (4 T × 1 time) ⇒ 4 T

$$\text{Total number of T-states required} = 7 + 64 + 64 + 157 + 4 = 296$$

30. (a)

XTHL exchanges the contents of HL pair and stack top two locations.

Number of machine cycles = 5 (F, R, R, W, W)

$$\text{Number of T-states} = 4 + (4 \times 3) = 16$$

$$\text{Execution time} = \frac{16}{f_{\text{clk}}} = \frac{16}{2} = 8 \mu\text{s}$$

31. (a)

PUSH D, POP H require the access of stack memory.

SPHL loads the stack pointer (SP) with the contents of HL pair. SP is a 16-bit register present inside the microprocessor. So, it is not required to access the stack memory (which is external to the microprocessor) to update the contents of SP.

32. (d)

2000H : MVI B, 4FH ⇒ 2 Bytes (2000H, 2001H)
 2002H : MVI A, 78H ⇒ 2 Bytes (2002H, 2003H)
 2004H : SUB B ⇒ 1 Bytes (2004H)
 2005H : ANI 0FH ⇒ 2 Bytes (2005H, 2006H)
 2007H : STA 2020 H ⇒ 3 Bytes (2007H, 2008H, 2009H)
 200AH : HLT ⇒ 1 Byte (200AH)

34. (a)

A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀	Port	
1	0	0	0	1	1	0	0	A	8CH
1	0	0	0	1	1	0	1	B	8DH
1	0	0	0	1	1	1	0	C	8EH
1	0	0	0	1	1	1	1	Control register	8FH

35. (d)


STAX and LDAX must be used with either BC or DE pairs only but not with HL pair.

So, instruction given in option (d) is invalid.

36. (d)
 MVI A, 69H ; A = 69H
 ANI F0H ; A = 60H
 RRC ;
 RRC ;
 RRC ;
 RRC ; A = 06H = 0000 0110
 CMA ; A = 1111 1001 = F9H
37. (b)
 MUL AH; (AX) ← (AL) × (AH)
39. (a)
 During external memory access,
 • Port 0 acts as a multiplexed lower order address/data bus.
 • Port 2 acts as a higher order address bus.
40. (c)
 There are 4 independent channels in 8237 DMA controller.
41. (d)
 Gain margin alone is inadequate to indicate relative stability when system parameters other than the loop gain are subject to variation. Due to variation in some parameters, phase shift of the system can vary which may results instability. Hence, we must also consider the concept of phase margin for determining the relative stability of the system.
42. (c)
 The transient response in a closed loop system decays more quickly than in open loop system.
45. (d)
 In an 8085 microprocessor, PUSH operation requires more clock cycles than POP operation.

Section B : Network Theory-1

46. (c)

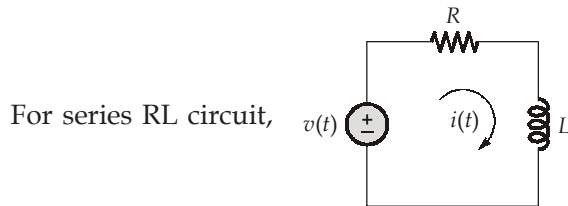

Using KVL,

$$v(t) = Ri(t) + L \frac{di(t)}{dt}$$

∴

$$6e^{-2t} = L \frac{d}{dt}(6e^{-2t} - 6e^{-3t}) + R(6e^{-2t} - 6e^{-3t})$$

$$6e^{-2t} = -12e^{-2t} + 18e^{-3t} + R(6e^{-2t} - 6e^{-3t})$$

$$(18e^{-2t} - 18e^{-3t}) = R(6e^{-2t} - 6e^{-3t})$$

$$18(e^{-2t} - e^{-3t}) = 6R(e^{-2t} - e^{-3t})$$

$$\text{or } R = 3 \Omega$$


47. (c)

$$\frac{1}{\sqrt{L_1 C_1}} = \frac{1}{\sqrt{250 \times 4 \times 10^{-9}}} = 1000 \text{ rad/sec}$$

$$\frac{1}{\sqrt{L_2 C_2}} = \frac{1}{\sqrt{2 \times 500 \times 10^{-9}}} = 1000 \text{ rad/sec}$$

The supply voltage is also oscillating at 1000 rad/sec.

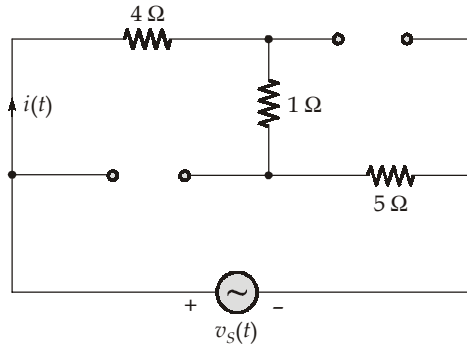So, both the parallel combinations of L and C act as open circuits, and the steady-state equivalent circuit can be drawn as,



$$i(t) = \frac{v_s(t)}{4 \Omega + 1 \Omega + 5 \Omega} = \frac{20 \cos(1000t)}{10} = 2 \cos(1000t) \text{ A}$$

So, the average power absorbed by the 4 Ω resistor will be,

$$P_{4\Omega} = \frac{(2)^2}{2} \times 4 = 8 \text{ W}$$

48. (b)

For an ideal transformer, $K = 1$

applying KVL in the primary and secondary loops, we get,

$$V_1 = (j\omega L_1)I_1 + j\omega MI_2$$

$$V_2 = (j\omega L_2)I_2 + j\omega MI_1$$

($\because I_1$ and I_2 both enters through the dots)

$$\frac{V_1}{V_2} = \frac{L_1 I_1 + MI_2}{L_2 I_2 + MI_1}$$

$$\therefore K = 1$$

$$\therefore M = \sqrt{L_1 L_2}$$

$$\frac{V_1}{V_2} = \sqrt{\frac{L_1}{L_2}} \left[\frac{\sqrt{L_1} \cdot I_1 + \sqrt{L_2} I_2}{\sqrt{L_1} I_1 + \sqrt{L_2} I_2} \right] = \sqrt{\frac{L_1}{L_2}}$$

49. (d)


The input impedance of the given circuit is given by,

$$\begin{aligned} Z_{\text{in}} &= 3 + \frac{j2 \times 2}{(2 + j2)} = 3 + \frac{j4}{(2 + j2)} \\ &= 3 + \frac{j4(2 - j2)}{8} \\ &= 3 + j + 1 = (4 + j) \end{aligned}$$

The input current will be in phase with the supply voltage provided the reactive part of the impedance does not exist. So, for the required series capacitor,

$$\begin{aligned} \frac{j}{\omega C} &= j \Rightarrow \omega C = 1 \\ C &= \frac{1}{2\pi f} = \frac{1}{100\pi} = \frac{10}{\pi} \text{ mF} \simeq 3.18 \text{ mF} \end{aligned}$$

50. (b)

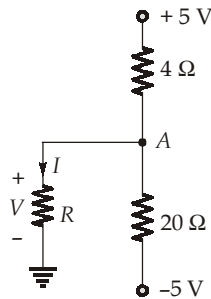


$$\therefore I = \frac{1}{4} \text{ A} \quad \therefore V = I \times R = R/4 \text{ V}$$

At Node 'A' by using KCL, we get,

$$\begin{aligned} \frac{5 - V}{4} + \frac{-V - 5}{20} &= I \\ \Rightarrow \frac{5 - R/4}{4} + \frac{-R/4 - 5}{20} &= \frac{1}{4} \\ 25 - \frac{5R}{4} - \frac{R}{4} - 5 &= 5 \\ 20 - \frac{6R}{4} &= 5 \\ \frac{6R}{4} &= 15 \\ R &= 10 \Omega \end{aligned}$$

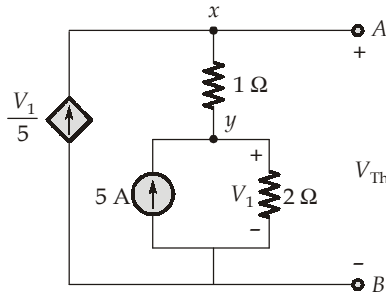51. (c)

In order to obtain Thevenin's voltage let us redraw the circuit with nodes x and y .



at node 'x'

$$\frac{V_1}{5} = \frac{V_{Th} - V_1}{1}$$

or

$$V_1 = 5 V_{Th} - 5 V_1$$

or

$$V_{Th} = \frac{6}{5} V_1 \quad \dots(i)$$

at node 'y'

$$5 = \frac{V_1 - V_{Th}}{1} + \frac{V_1}{2}$$

$$10 = 2V_1 - 2V_{Th} + V_1$$

$$10 = 3V_1 - 2V_{Th}$$

$$10 = 3 \times \frac{5}{6} V_{Th} - 2V_{Th}$$


$$20 = (5 - 4) V_{Th}$$

or

$$V_{Th} = 20 \text{ V}$$

53. (a)

The circuit can be redrawn as

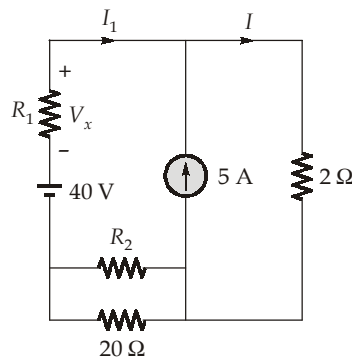

\therefore

$$V_x = -5 \text{ V}$$

\therefore

$$I_1 = \frac{-V_x}{R_1} = \frac{5}{R_1} \text{ A}$$

also

$$I_1 + 5 = I = 10 \text{ A}$$

or

$$I_1 = -5 + 10 = 5 \text{ A} \quad \dots(i)$$

$$\Rightarrow R_1 = \frac{5}{5} = 1 \Omega$$

By applying KVL, we get,

$$40 = -V_x + 2(I_1 + 5) + (20 \parallel R_2)I_1$$

$$40 = 5 + 2(10) + (20 \parallel R_2)I_1$$

$$40 - 25 = \frac{20 \times R_2}{20 + R_2} \times I_1$$

$$15 = \frac{20 \times R_2}{20 + R_2} \times I_1$$


From equation (i), by using the value of I_1 , we get,

$$R_2 = \frac{20 \times 3}{17} = \frac{60}{17} \approx 3.53 \Omega$$

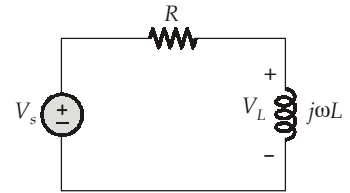54. (a)

Here,

$$\begin{aligned} V_L &= \left(\frac{j\omega L}{R + j\omega L} \right) V_s \\ &= \frac{V_s \omega L \angle 90^\circ}{\sqrt{R^2 + \omega^2 L^2} \angle \tan^{-1} \frac{\omega L}{R}} \end{aligned}$$




$$\therefore \phi = 90^\circ - \tan^{-1} \frac{\omega L}{R}$$

Thus, when R increases, $\tan^{-1} \left(\frac{\omega L}{R} \right)$ decreases and hence ϕ increases.

55. (d)

As per the question,

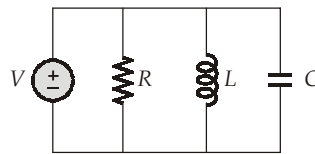


$$Q = R \sqrt{\frac{C}{L}} = \frac{1}{2\xi}$$

$$\xi = \frac{1}{2R} \sqrt{\frac{L}{C}} = \frac{1}{2 \times 100} \sqrt{\frac{0.8}{20 \times 10^{-6}}}$$

$$= \frac{1}{200} \sqrt{\frac{8}{2 \times 10^{-4}}} = \frac{1}{2} \sqrt{\frac{8}{2}} = 1$$

\therefore Critically damped response.

56. (c)

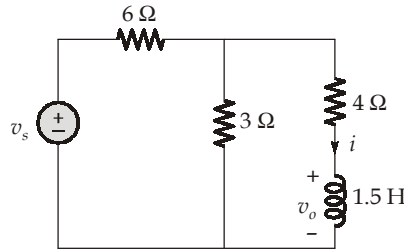

For $t < 0$,

$$V_s = 0, i(0) = 0$$

For $t > 0$

$$R_{eq} = (6 \parallel 3) + 4 = 2 + 4 = 6 \Omega$$

$$L_{eq} = 1.5 \text{ H}$$

$$\tau = \frac{L_{eq}}{R_{eq}} = 0.25 \text{ sec} \Rightarrow \frac{1}{\tau} = 4 \text{ sec}^{-1}$$

$$v_o(t) = v_o(0^+)e^{-t/\tau}u(t)$$

$v_o(0^+)$ = voltage across inductor at $t = 0^+$ (when inductor is open circuited)

$$v_o(0^+) = \frac{3 \Omega}{3 \Omega + 6 \Omega} \times 1 \text{ V} = \frac{1}{3} \text{ V}$$

So,

$$v_o(t) = \frac{1}{3}e^{-4t}u(t) \text{ V}$$

57. (b)

Here,

$$T = 2 \text{ and } v(t) = \begin{cases} 4; & 0 < t < 1 \\ 8; & 1 < t < 2 \end{cases}$$


$$V_{\text{rms}}^2 = \frac{1}{2} \left[\int_0^1 4^2 dt + \int_1^2 8^2 dt \right]$$

$$= \frac{1}{2} [16 + 64] = \frac{80}{2} = 40$$

$$V_{\text{rms}} = \sqrt{40} = 2\sqrt{10} \text{ V} = 2 \times 3.162 = 6.325 \text{ V}$$

58. (b)

From the given circuit,

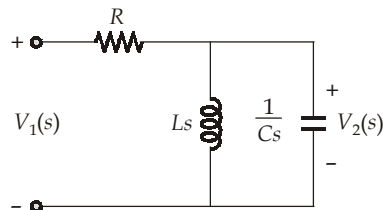

$$sL \parallel \frac{1}{sC} = \frac{sL}{1 + s^2LC}$$

$$\begin{aligned}\frac{V_2(s)}{V_1(s)} &= \frac{\frac{sL}{1+s^2LC}}{R + \frac{sL}{1+s^2LC}} = \frac{sL}{s^2RLC + sL + R} \\ &= \frac{s \cdot \frac{1}{RC}}{s^2 + s \cdot \frac{1}{RC} + \frac{1}{LC}}\end{aligned}$$

Comparing this with the given transfer function,

$$\frac{1}{RC} = 4$$

$$\frac{1}{LC} = 8$$

For

$$R = 1 \text{ k}\Omega$$

$$C = \frac{1}{4} \text{ mF} = 0.25 \text{ mF} = 250 \text{ }\mu\text{F}$$

and

$$LC = \frac{1}{8}$$

$$L = \frac{1}{8 \times 250 \times 10^{-6}} = 500 \text{ H}$$

60. (d)

A capacitor has one pole at $s = 0$ and driving point impedance is $Z(s) = \frac{1}{sC}$

Section C : Digital Circuits-1

61. (b)

$$\begin{aligned}\overline{f(A, B, C)} &= \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC \\ &= \overline{A}C(\overline{B} + B) + A\overline{C}(\overline{B} + B) \\ &= \overline{A}C + A\overline{C} = A \oplus C \\ f(A, B, C) &= \overline{A \oplus C} = A \odot C\end{aligned}$$

62. (b)


$$\begin{aligned}Z &= x \oplus [y \oplus xy] = x \oplus [y\overline{xy} + \overline{y}xy] \\ &= x \oplus [y(\overline{x} + \overline{y}) + 0] = x \oplus [y\overline{x} + 0] \\ &= x(\overline{y} + x) + \overline{x}y\overline{x} = x + \overline{x}y = x + y\end{aligned}$$

63. (c)

$$\text{Required number of 2 to 4 decoders} = \left\lceil \frac{256}{4} \right\rceil + \left\lceil \frac{64}{4} \right\rceil + \left\lceil \frac{16}{4} \right\rceil + \left\lceil \frac{4}{4} \right\rceil = 64 + 16 + 4 + 1 = 85$$

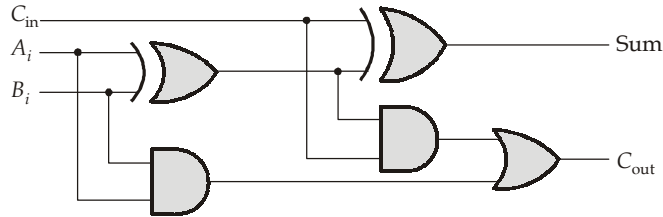64. (b)

In a full adder circuit, as shown in the following figure, the input carry has to propagate through 2 gates to produce output carry.



An n -bit ripple carry adder consists n -full adders. So, the carry has to propagate through $2n$ gates. In the given question, for a 6-bit binary ripple carry adder, input carry has to propagate through 12 gates.

65. (b)

$$Y = \bar{C}(A\bar{C} + BC) + C(\bar{B}\bar{C} + AC)$$

$$= A\bar{C} + AC = A$$

66. (d)

$$(199)_{12} = 12^2 + 9 \times 12 + 9 = (261)_{10}$$

$$(199)_{11} = 11^2 + 9 \times 11 + 9 = (229)_{10}$$

$$(199)_{12} + (199)_{11} = (490)_{10}$$

5	490		
5	98 - 0	0	↑ (LSB)
5	19 - 3	3	
	3 - 4	4	
		3	↑ (MSB)


∴

$$(490)_{10} = (3430)_5$$

67. (c)

$$f = A\{B + C(\overline{AB + AC})\} = AB + AC(\overline{AB} \cdot \overline{AC}) = AB$$

68. (c)

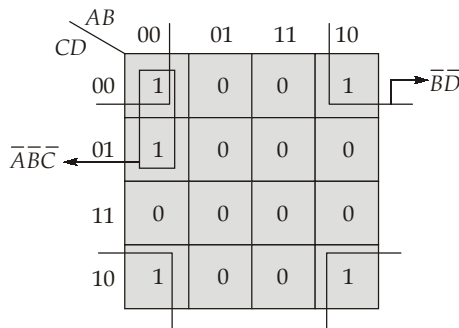

$$f = \bar{A}\bar{B}\bar{C} + \bar{B}\bar{D} = \bar{B}(\bar{A}\bar{C} + \bar{D})$$

70. (c)

$$\begin{aligned}
 \bar{f} &= \overline{(AB + \bar{B}C + AC)A} \\
 &= \overline{(AB + \bar{B}C + AC)} + \bar{A} \\
 &= (\bar{A}\bar{B})(\bar{B}\bar{C})(\bar{A}\bar{C}) + \bar{A} \\
 &= (\bar{A} + \bar{B})(B + \bar{C})(\bar{A} + \bar{C}) + \bar{A} \\
 &= (\bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B}\bar{C})(\bar{A} + \bar{C}) + \bar{A} \\
 &= \bar{A}\bar{B} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{B}\bar{C} + \bar{A} \\
 &= \bar{A}(B + \bar{B}\bar{C} + \bar{C} + \bar{B}\bar{C} + 1) + \bar{B}\bar{C} = \bar{A} + \bar{B}\bar{C}
 \end{aligned}$$

72. (a)

$$\begin{aligned}
 f &= \bar{A}\bar{B} + \bar{A}\bar{C}\bar{D} + \bar{A}\bar{B}D + \bar{A}\bar{B}C\bar{D} \\
 &= \bar{A} + \bar{B} + \bar{A}\bar{C}\bar{D} + \bar{A}\bar{B}D + (\bar{A} + \bar{B})C\bar{D} \\
 &= \bar{A} + \bar{B} + \bar{A}\bar{C}\bar{D} + \bar{A}\bar{B}D + \bar{A}C\bar{D} + \bar{B}C\bar{D} \\
 &= \bar{A}(1 + \bar{C}\bar{D} + \bar{B}D + C\bar{D}) + \bar{B}(1 + C\bar{D}) \\
 &= \bar{A} + \bar{B} \Rightarrow \text{Two literals}
 \end{aligned}$$

73. (c)


The expression can be written as

	BC			
A	00	01	11	10
0	0	1	0	0
1	0	1	1	1

$(A + \bar{B})$ is indicated by a box around the top row (0,0), (0,1), (0,11), (0,10).
 $(B + C)$ is indicated by a box around the bottom-left cell (1,00) and the bottom-right cells (1,01), (1,11), (1,10).

$$f = (A + \bar{B})(B + C)$$

Thus, the circuit can be drawn as

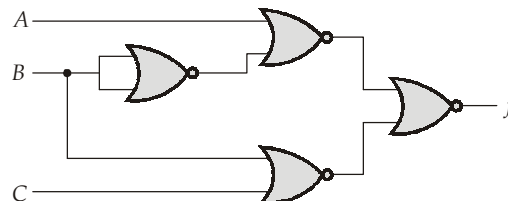

So, minimum 4 NOR gates are required.

○○○○