

# Electronics Engineering

## Analog Circuits

Comprehensive Theory

*with* Solved Examples and Practice Questions



**MADE EASY**  
Publications



## **MADE EASY Publications**

Corporate Office: 44-A/4, Kalu Sarai (Near Hauz Khas Metro Station), New Delhi-110016

E-mail: infomep@madeeasy.in

Contact: 011-45124612, 0-9958995830, 8860378007

Visit us at: [www.madeeasypublications.org](http://www.madeeasypublications.org)

## **Analog Circuits**

© Copyright, by MADE EASY Publications.

All rights are reserved. No part of this publication may be reproduced, stored in or introduced into a retrieval system, or transmitted in any form or by any means (electronic, mechanical, photo-copying, recording or otherwise), without the prior written permission of the above mentioned publisher of this book.

First Edition: 2015

Second Edition: 2016

Third Edition: 2017

Fourth Edition: 2018

Fifth Edition: 2019

**Sixth Edition: 2020**

# Contents

## Analog Circuits

### Chapter 1

#### Diode Circuits ..... 4

1.1	Introduction .....	4
1.2	Diode Circuits : DC Analysis and Models .....	4
1.3	Diode Logic Gates .....	11
1.4	Diode : The Small Signal Model.....	13
1.5	DC Power Supply .....	15
1.6	Rectifier .....	16
1.7	Half-wave Rectifier.....	16
1.8	Centre-Tapped Full-wave Rectifier .....	26
1.9	Bridge Rectifier.....	34
1.10	Comparison of Rectifier Circuits with Resistive Load .....	37
1.11	Filter .....	38
1.12	Inductor Filter .....	38
1.13	Capacitor Filter .....	40
1.14	LC Filter (L-Section Filter).....	43
1.15	CLC Filter (II-Section Filter) .....	47
1.16	Voltage Regulators .....	48
1.17	Zener Diode Shunt Regulator.....	49
1.18	Op-amp Controlled Series Regulator.....	50
1.19	Transistorized Series Regulator .....	52
1.20	Fixed Voltage IC Regulators .....	55
1.21	Wave Shaping.....	56
1.22	Clipper.....	56
1.23	Linear Wave Shaping.....	63
1.24	Clamper .....	70
1.25	Voltage Multiplier.....	74
	<i>Student's Assignments-1</i> .....	77
	<i>Student's Assignments-2</i> .....	80

### Chapter 2

#### BJT-Characteristics and Biasing..... 81

2.1	Introduction .....	81
2.2	Transistors Current Components.....	81
2.3	Early Effect .....	85
2.4	BJT Configuration.....	86
2.5	The Common Base Configuration.....	87
2.6	The Common-Emitter Configuration.....	89
2.7	The Common-Collector Configuration.....	92
	<i>Student's Assignments-1</i> .....	92
	<i>Student's Assignments-2</i> .....	94

### Chapter 3

#### Transistor Biasing and Thermal Stabilization ..... 96

3.1	Introduction .....	96
3.2	The Operating Point.....	96
3.3	Instability in Collector Current .....	98
3.4	BJT Biasing .....	101
3.5	Fixed Bias Circuit.....	101
3.6	Collector to Base Bias Circuit.....	103
3.7	Self-Bias, Emitter Bias, or Voltage-Divider Bias.....	104
3.8	Bias Compensation.....	107
3.9	Thermal Runaway .....	109
3.10	BJT Biasing in Integrated Circuits (ICs).....	113
3.11	Constant Current Source (Current Mirror).....	113
3.12	Widlar Current Source .....	114
3.13	Current Repeaters .....	116
3.14	Wilson Current Source.....	117
	<i>Student's Assignments-1</i> .....	119
	<i>Student's Assignments-2</i> .....	121

## Chapter 4

<b>BJT as an Amplifier .....</b>	<b>123</b>
4.1 Introduction .....	123
4.2 Graphical Analysis of BJT Amplifier .....	124
4.3 Transistor Hybrid Model .....	125
4.4 Analysis of Transistor Amplifier Circuit Using h-Parameters.....	127
4.5 Small Signal Hybrid- $\pi$ model of BJT.....	133
4.6 Hybrid- $\pi$ -Equivalent Circuit, by Considering Early Effect .....	135
4.7 Basic Transistor Amplifier Configurations.....	136
4.8 Common-Emitter Amplifiers.....	137
4.9 Common-Collector Amplifier .....	142
4.10 Common-Base Amplifier .....	146
4.11 Multistage Amplifiers.....	148
<i>Student's Assignments-1</i> .....	151
<i>Student's Assignments-2</i> .....	153

## Chapter 5

<b>Basic FET Amplifiers .....</b>	<b>155</b>
5.1 Introduction .....	155
5.2 The Common-Source Amplifier .....	155
5.3 Common-Drain (Source Follower) Amplifier..	160
5.4 The Common-Gate Configuration .....	162
<i>Student's Assignments-1</i> .....	167
<i>Student's Assignments-2</i> .....	169

## Chapter 6

<b>Frequency Response .....</b>	<b>170</b>
6.1 Introduction .....	170
6.2 Amplifier Frequency Response .....	170
6.3 Miller's Theorem .....	177
6.4 Frequency Response : BJT.....	179
6.5 High Frequency Response of Common-Emitter and Common-Source Circuits.....	184
6.6 High Frequency Response of Common-Base & Common-Gate Circuits.....	186
6.7 High Frequency Response of Emitter and Source Follower Circuits .....	188
<i>Student's Assignments-1</i> .....	192
<i>Student's Assignments-2</i> .....	193

## Chapter 7

<b>Differential Amplifiers .....</b>	<b>195</b>
7.1 Introduction .....	195
7.2 The Differential Amplifier .....	195
7.3 Basic BJT Differential Amplifier.....	196
7.4 FET Differential Amplifiers .....	202
7.5 Constant Current-Bias.....	203
7.6 Level Translator .....	205
<i>Student's Assignments</i> .....	207

## Chapter 8

<b>Feedback Amplifiers .....</b>	<b>208</b>
8.1 Introduction .....	208
8.2 Basic Feedback Concepts .....	208
8.3 General Block Diagram of Feedback Amplifier...212	
8.4 Four Basic Feedback Topologies .....	215
8.5 Series-Shunt Configuration .....	216
8.6 Shunt-Series Configuration .....	218
8.7 Series-Series Configuration .....	220
8.8 Shunt-Shunt Configuration .....	221
8.9 Summary of Results.....	221
<i>Student's Assignments-1</i> .....	224
<i>Student's Assignments-2</i> .....	226

## Chapter 9

<b>Large Signal Amplifier .....</b>	<b>227</b>
9.1 Introduction .....	227
9.2 Power Amplifier .....	227
9.3 Classification of Power Amplifiers.....	228
9.4 Direct Coupled Class-A Amplifier .....	229
9.5 Class-A Transformer Coupled Amplifier .....	231
9.6 Transformer Coupled Class-B Push Pull Amplifier .....	235
9.7 Cross-Over Distortion .....	238
9.8 Class-AB Push-Pull Amplifier .....	238
9.9 Class-A Push-Pull Amplifier.....	239
9.10 Transformerless Class-B Push-Pull Amplifier ..	239
9.11 Class-C Power Amplifier.....	240
9.12 Class-D Amplifiers .....	241
9.13 Class-S Power Amplifier .....	242
<i>Student's Assignments</i> .....	243

## Chapter 10

### Operational Amplifier .....245

10.1	Introduction .....	245
10.2	Block Diagram Representation of A Typical Op-Amp.....	245
10.3	Schematic Symbol.....	246
10.4	Operational Amplifier Characteristics.....	246
10.5	DC Characteristics .....	247
10.6	AC Characteristics.....	249
10.7	Characteristics of Ideal Op-Amp .....	252
10.8	Equivalent Circuit of an Op-Amp.....	252
10.9	Ideal Voltage Transfer Curve .....	253
10.10	Inverting Amplifier.....	254
10.11	Summing Amplifier.....	259
10.12	Non-inverting Amplifier .....	261
10.13	Voltage Follower .....	262
10.14	Current-to-Voltage Converter .....	263
10.15	Voltage-to-Current Converter.....	264
10.16	Differential Amplifier.....	265
10.17	Integrator and Differentiator.....	268
10.18	Instrumentation Amplifier.....	271
10.19	Log Amplifier.....	273
10.20	Antilog or Exponential Amplifier .....	275
10.21	Precision Diode.....	276
10.22	Half-Wave Rectifier .....	277
10.23	Full-Wave Rectifier.....	277
	<i>Student's Assignments-1</i> .....	279
	<i>Student's Assignments-2</i> .....	282

## Chapter 11

### Signal Generators and Waveform

### Shaping Circuits.....283

11.1	Introduction .....	283
11.2	Oscillators.....	283
11.3	The Phase-Shift Oscillator.....	285
11.4	Wien Bridge Oscillator .....	288
11.5	Colpitts Oscillator .....	290
11.6	Hartley Oscillator .....	293
11.7	Crystal Oscillators .....	293
11.8	Comparator.....	296
11.9	Zero-Crossing Detector .....	297
11.10	Sample-And-Hold Circuits.....	298
11.11	Basic Inverting Schmitt Trigger.....	299
11.12	Schmitt Trigger Oscillator .....	302
11.13	Monostable Multivibrator .....	304
11.14	The 555 Circuit.....	305
	<i>Student's Assignments</i> .....	312



# Analog Circuits

---

## Introduction to Analog Circuits

After studying the basic electronic devices and their characteristics, now we shall deal with more complex analog circuits, of which amplifiers is a very significant category. We shall start our analysis with applications of diode, a very fundamental component, in various circuit configurations such as clipper, clamper, regulator etc. Further, we shall proceed to applications of BJT and FET, particularly as an amplifier.

The other complex analog circuits, including circuits that form operational amplifiers, are also part of this book. These circuits are composed of fundamental configurations, such as differential amplifier, constant-current source, active load, and output stage, all of which have been discussed in detail.

The major emphasis throughout the book is on developing the reader's understanding for analyzing and designing various fundamental circuits, which are always an integral part of various competitive examinations. Throughout the book, a very sequential and comprehensive approach has been used, so that a beginner can also utilize the book in very efficient manner.

# Prelude to Analog Circuits

---

## Electronics

Electronics is defined as the science of motion of charges in a gas, vacuum, or semiconductor. Note that the charge motion in a metal is excluded from this definition.

This definition was used early in the 20<sup>th</sup> century to separate the field of electrical engineering, which dealt with motors, generators, and wire communications, from the new field of electronic engineering, which at that time dealt with the vacuum tubes.


## Microelectronics

Microelectronics refers to the integrated-circuit (IC) technology that is capable of producing circuits which contain millions of components in a small piece of silicon (known as a silicon chip) whose area is on the order of 100 mm<sup>2</sup>.
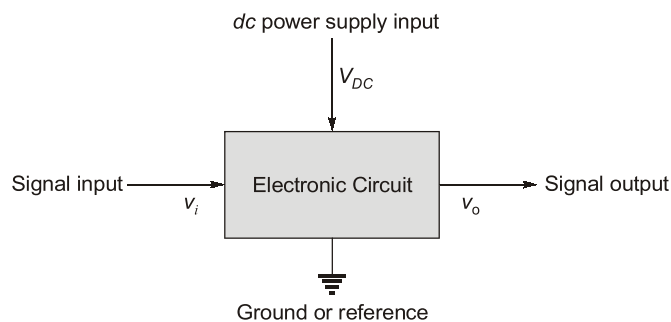
## Electronic Circuits

A circuit which consists of at least one electronic device (e.g. amplifier, rectifier, oscillator etc.) is known as an electronic circuit.



In most of the electronic circuits there are two inputs. One input is from power supply which provides dc voltages and currents to establish proper biasing for transistors. The second input is a signal that can be amplified by the circuit. Although the output signal can be larger than the input signal but the output power can never exceed the dc input power. Therefore, the magnitude of dc power supply is one limitation to the output signal response.



## Discrete and Integrated Circuits

Discrete electronic circuits contain discrete components, such as resistors, capacitors and transistors whereas an integrated circuit consists of a single crystal chip of silicon containing both active and passive elements and their interconnections. Such circuits are produced by the same processes used to fabricate individual transistors and diodes.

## Analog and Digital Signals

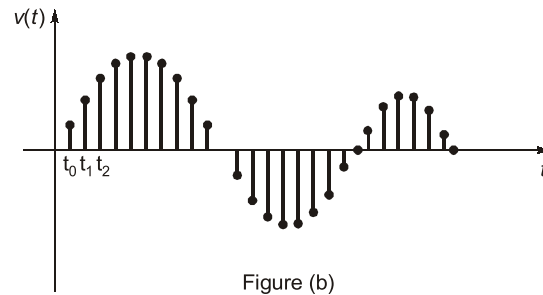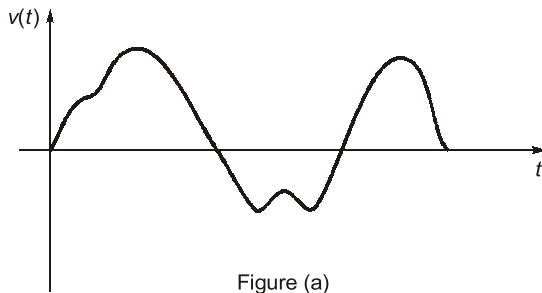

The voltage signal shown graphically in Fig. (a) is called an **analog signal**. The name derives from the fact that such a signal is analogous to the physical signal that it represents. The magnitude of an analog signal can take on any value; that is, the amplitude of an analog signal exhibits a continuous variation over its range of activity. Electronic circuits that process such signals are known as **analog circuits**.

An alternative form of signal representation is that of a sequence of numbers shown in Fig. (b), each number representing the signal magnitude at an instant of time. The resulting signal is called a **discrete signal**. When discrete signal is quantized in magnitude it becomes a **digital signal**. Electronic circuits that process digital signals are called **digital circuits**.

### Advantages of Analog Circuits

- Majority of signals in the “real world” are analog; so these signals can be directly processed in analog circuits whereas digital processing requires analog to digital and digital to analog conversion.
- Analog circuits can be designed to operate even at higher power levels.

### Advantages of Digital Circuits

- In digital circuits effect of noise is less.
- Digital circuits are easier to design.
- Digital circuits can be programmed.
- Digital data can be stored.






# Operational Amplifier

## 10.1 Introduction

Linear integrated circuits are being used in a number of electronic applications such as in fields like audio and radio communication, medical electronics, instrumentation control, etc. An important linear IC is operational amplifier which will be discussed in this chapter.

The operational amplifier (commonly referred to as op-amp) is a multi-terminal device which internally is quite complex. Fortunately, for the ordinary user, it is not necessary to know about the op-amp's internal make-up. The manufacturers have done their job so well that op-amp's performance can be completely described by its terminal characteristics and those of external components that are connected to it. However, the electronics of op-amp is described where various stages of op-amp are discussed.

## 10.2 Block Diagram Representation of A Typical Op-Amp

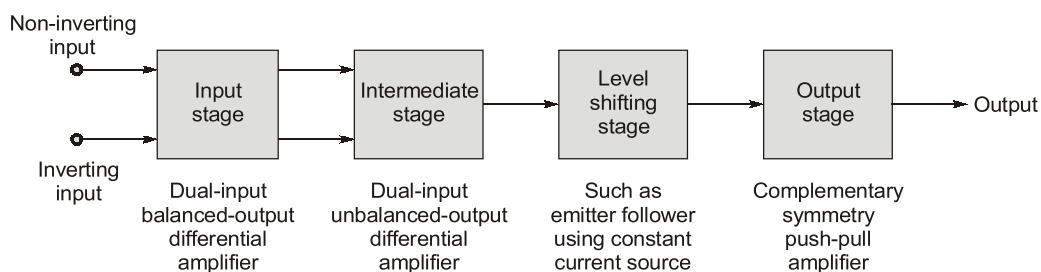

**Figure-10.1:** Block diagram of a typical op-amp

- An operational-amplifier is a direct-coupled high gain amplifier usually consisting of one or more differential amplifiers and usually followed by a level translator and an output.
- The input stage is the dual-input, balanced-output differential amplifier. This stage generally provides most of the voltage gain and also establishes the input resistance of the op-amp.
- The intermediate stage is usually another differential amplifier, which is driven by the output of the first stage. In most amplifiers the intermediate stage is dual input, unbalanced (single-ended) output.


- As direct coupling is used, so the DC voltage at the output of the intermediate stage is well above ground potential. Therefore, generally, the level translator (shifting) circuit is used after intermediate stage to shift the DC level at the output of intermediate stage downward to zero volts with respect to ground.
- The final stage is usually a push-pull complementary amplifier output stage. The output stage increases the output voltage swing and raises the current supplying capability of the op-amp. A well-designed output stage also provides low output resistance.

**NOTE**

The operational amplifier is a versatile device that can be used to amplify DC as well as AC input signals and was originally designed for computing such mathematical functions as addition, subtraction, multiplication, and integration. Thus the name **operational amplifier** stems from its original use for these mathematical operations.

### 10.3 Schematic Symbol

Given an op-amp schematic diagram, we can save time by using a schematic symbol for the entire op-amp circuit. Fig. (10.2) shows the most widely used symbol for a circuit with two inputs and one output. For simplicity, power supply and other pin connections are omitted. Since the input differential stage of the op-amp is designed to be operated in the differential mode, the differential inputs are designated by the (+) and (–) notations. The (+) input is non-inverting input. An AC signal or DC voltage applied to this input produces an inphase (or same polarity) signal at the output. On the other hand, the (–) input is inverting input because an AC signal or DC voltage applied to this input produces an 180° out-of-phase (or opposite polarity) signal at the output.

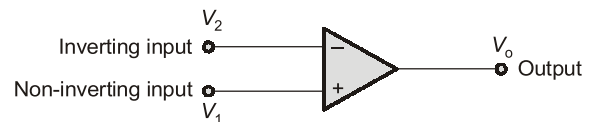

**Figure-10.2:** Schematic symbol for the op-amp

In figure

$V_1$  = Voltage at the non-inverting input (volts)

$V_2$  = Voltage at the inverting input (volts)

$V_0$  = Output voltage (volts)

Here

$$V_0 = A(V_1 - V_2) \quad \dots(10.1)$$

All these voltages are measured with respect to ground.

where,  $A$  = Large-signal voltage gain, which is specified on the data sheet for an op-amp.

### 10.4 Operational Amplifier Characteristics

In an ideal op-amp it is assumed that the op-amp responds equally well to both DC and AC input voltages. However, a practical op-amp does not behave this way. A practical op-amp has some DC voltage at the output even if both the inputs are grounded. The factors responsible for this and the suitable compensating techniques are discussed here.

## 10.5 DC Characteristics

An ideal op-amp draws no current from the source and its response is also independent of temperature. However, a real op-amp does not work this way. Current is taken from the source into the op-amp inputs. Also the two inputs respond differently to current and voltage due to mismatch in transistors. A real op-amp also shifts its operation with temperature. These non-ideal DC characteristics that add error components to the DC output voltage are:


- Input bias current.
- Input offset current.
- Input offset voltage.
- Thermal drift.

### 10.5.1 Input Bias Current

Input bias current  $I_B$  is the average of the currents that flow into the inverting and non-inverting input terminals of the op-amp. In equation form,

$$I_B = \frac{I_{B1} + I_{B2}}{2} \quad \dots(10.2)$$

- $I_B = 500$  nA maximum for the IC 741.
- Note that the two input currents  $I_{B1}$  and  $I_{B2}$  are actually the base currents of the first differential amplifier stage.

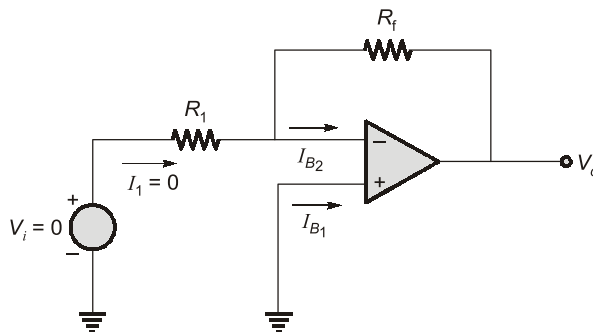


**Figure-10.3:** Inverting amplifier with bias currents

### 10.5.2 Input Offset Current

The algebraic difference between the currents into the inverting and non-inverting terminals is referred to as *input offset current*  $I_{io}$ .

$$I_{io} = |I_{B1} - I_{B2}| \quad \dots(10.3)$$

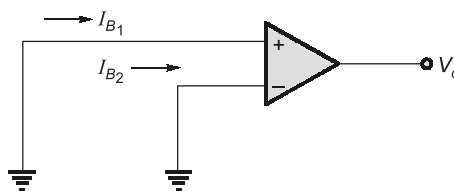

**Figure-10.4:** Defining input offset current  $I_{io}$

- The maximum input offset current for the IC741 is 200 nA. As matching between the two input terminals is improved, the difference between  $I_{B1}$  and  $I_{B2}$  becomes smaller; that is, the  $I_{io}$  value decreases further.

### 10.5.3 Input Offset Voltage

Input offset voltage is the voltage that must be applied between two input terminals of an op-amp to null the output, as shown in Fig. 10.5 (a). The smaller the value of  $V_{ios}$ , the better the input terminals are matched.

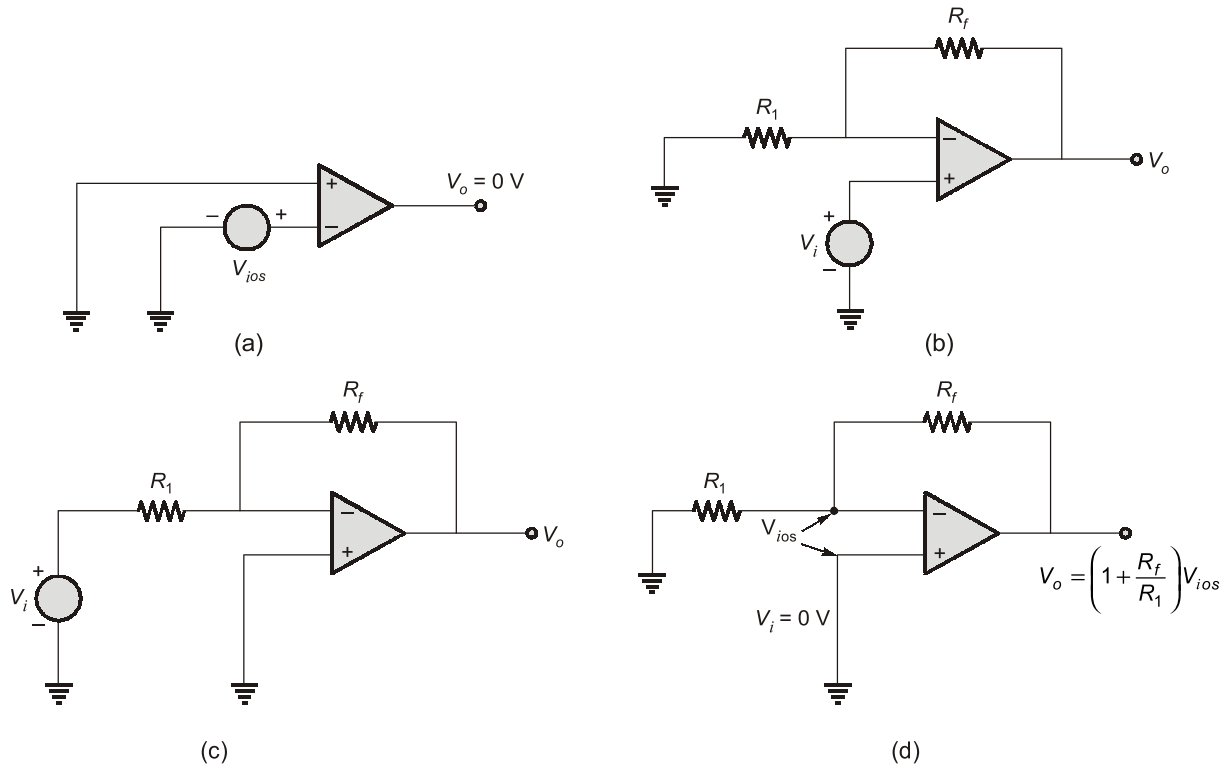


Figure-10.5 (a) Op-amp showing input offset voltage (b) Non-inverting amplifier (c) Inverting amplifier (d) Equivalent circuit for  $V_i = 0$

Let us now examine the effect of  $V_{ios}$  on the output of non-inverting and inverting op-amp as shown in Fig. 10.5 (b) and 10.5 (c). If  $V_i$  is set to zero, the circuits of Fig. 10.5 (b, c) become the same as in Fig. 10.5 (d). The voltage  $V_2$  at the (-) input terminal is given by

$$V_2 = \left( \frac{R_1}{R_1 + R_f} \right) V_o \quad \dots(10.4)$$

or

$$V_o = \left( \frac{R_1 + R_f}{R_1} \right) V_2 = \left( 1 + \frac{R_f}{R_1} \right) V_2 \quad \dots(10.5)$$

Since,  $V_{ios} = |V_i - V_2|$  and  $V_i = 0$

$$\Rightarrow V_{ios} = |0 - V_2| = V_2$$

or,

$$V_o = \left( 1 + \frac{R_f}{R_1} \right) V_{ios} \quad \dots(10.6)$$

Thus, the output offset voltage of an op-amp in closed-loop configuration (inverting or non-inverting) is given by equation (10.6).

### 10.5.4 Thermal Drift

Bias current, offset current and offset voltage change with temperature. A circuit carefully nulled at 25°C may not remain so when temperature rises to 35°C. This is called drift. Often, offset current drift is expressed in nA/°C and offset voltage drift in mV/°C. This indicates the change in offset for each degree Celsius change in temperature.

## 10.6 AC Characteristics

We have discussed so far the DC characteristics such as bias current, offset current offset voltage and thermal drift. These will affect the steady state (DC) response of the op-amp only. For small signal sinusoidal (AC) applications, one has to know the AC characteristics such as frequency response and slew-rate which will be discussed in this section.


### 10.6.1 Frequency Response

Since an op-amp is a direct coupled amplifier so ideally, it should have infinite bandwidth. But practically op-amp gain, however decreases (rolls-off) at higher frequencies. Actually, the op-amp acts as a low pass circuit i.e. its gain remains constant at low frequencies but it decreases at high frequencies.

The magnitude and the phase angle of the open loop voltage gain are function of frequency and can be written as

$$|A| = \frac{A_{OL}}{\sqrt{1 + \left(\frac{f}{f_1}\right)^2}} \quad \dots(10.7)$$

$$\phi = -\tan^{-1}\left(\frac{f}{f_1}\right) \quad \dots(10.8)$$

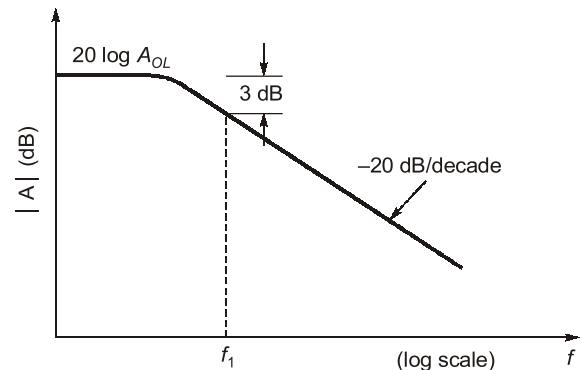

**Figure-10.6** Open loop magnitude characteristics

From **Fig. (10.6)**, we can observe that

- For frequency of  $f \ll f_1$ , the magnitude of the gain is  $20 \log A_{OL}$  in dB.
- At frequency  $f = f_1$ , the gain is 3 dB down from the DC value of  $A_{OL}$  in dB. This frequency  $f_1$  is called corner frequency.
- For  $f \gg f_1$ , the gain rolls-off at the rate of  $-20$  dB/decade or  $-6$  dB/octave.

**Remember**



- Frequency at which open loop gain of an op-amp becomes equal to 1, is called unity gain frequency or unity gain bandwidth (UGB).
- UGB is the product of open loop gain and bandwidth. It is also called gain bandwidth product.

**Example - 10.1** The first dominant pole encountered in the frequency response of a compensated op-amp is approximately at

- (a) 5 Hz (b) 10 kHz  
(c) 1 MHz (d) 100 MHz

**Solution: (a)**

**Example - 10.2** A 741-type op-amp has a gain-bandwidth product of 1 MHz. An non-inverting amplifier using this op-amp and having a voltage gain of 20 dB will exhibit a –3 dB bandwidth of

- (a) 50 kHz (b) 100 kHz  
(c)  $\frac{1000}{17}$  kHz (d)  $\frac{1000}{7.07}$  kHz

**Solution: (b)**

To find gain

$$\begin{aligned} \therefore 20 \log X &= 20 \\ X &= 10 \\ \therefore \text{Gain} \times \text{BW} &= 1 \times 10^6 \\ \Rightarrow \text{BW} &= \frac{1 \times 10^6}{\text{Gain}} = \frac{10^6}{10} = 100 \text{ kHz} \end{aligned}$$

### 10.6.2 Slew Rate

Slew rate (SR) is defined as the maximum rate of change in output voltage per unit of time and is expressed in volts per microseconds. In equation form,


$$SR = \left. \frac{dV_o}{dt} \right|_{\text{maximum}} \text{ V}/\mu\text{sec}$$

#### Remember



- Slew rate indicates how rapidly the output of an op-amp can change in response to change in the input frequency.
- The slew rate of an op-amp is fixed ; therefore, if the slope requirements of the output signal are greater than slew rate, then distortion occurs.

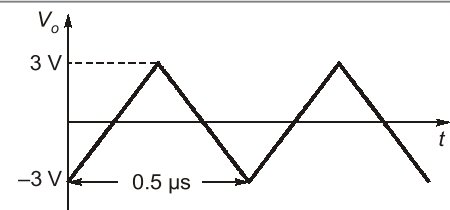**Example - 10.3** The output of an op-amp voltage follower is a triangular wave as shown in figure for a square wave input of frequency 2 MHz and 8 V peak to peak amplitude. What is the slew rate of the op-amp?



**Solution:**

Since slew rate is defined as the maximum rate of change of the output, so from given figure it can be seen that,

$$SR = \frac{6 \text{ V}}{(0.5/2) \mu\text{s}} = 24 \text{ V}/\mu\text{sec}$$