

Electrical Engineering

Digital Electronics

Comprehensive Theory

with Solved Examples and Practice Questions



MADE EASY
Publications



MADE EASY Publications

Corporate Office: 44-A/4, Kalu Sarai (Near Hauz Khas Metro Station), New Delhi-110016

E-mail: infomep@madeeasy.in

Contact: 011-45124612, 0-9958995830, 8860378007

Visit us at: www.madeeasypublications.org

Digital Electronics

© Copyright, by MADE EASY Publications.

All rights are reserved. No part of this publication may be reproduced, stored in or introduced into a retrieval system, or transmitted in any form or by any means (electronic, mechanical, photo-copying, recording or otherwise), without the prior written permission of the above mentioned publisher of this book.

First Edition: 2015

Second Edition: 2016

Third Edition: 2017

Fourth Edition: 2018

Fifth Edition: 2019

Sixth Edition: 2020

Contents

Digital Electronics

Chapter 1

Number Systems..... 1

- 1.1 Digital Number Systems (Positional Weight System)..... 2
- 1.2 Codes 7
- 1.3 Arithmetic Operations..... 11
- 1.4 Signed Number Representation 15
- 1.5 Over Flow Concept 19
- Student's Assignments* 20

Chapter 2

Boolean Algebra and Logic Gates21

- 2.1 Logic Operations 21
- 2.2 Laws of Boolean Algebra 22
- 2.3 Boolean Algebraic Theorems 23
- 2.4 Minimization of Boolean Functions 27
- 2.5 Representation of Boolean Functions 27
- 2.6 Karnaugh Map..... 32
- 2.7 Logic Gates 42
- Student's Assignments* 63

Chapter 3

Combinational Circuits.....65

- 3.1 Design Procedure for Combinational Circuit 65
- 3.2 Adders and Subtractors 73
- 3.3 Binary Adders 78
- 3.4 Code Converters..... 89
- 3.5 Parity Bit Generators and Checkers 91
- 3.6 Magnitude Comparators 93
- 3.7 Encoders 95
- 3.8 Decoders 98
- 3.9 Multiplexers..... 105
- 3.10 Demultiplexers..... 114
- 3.11 Hazards and Hazard-free Realization 114
- Student's Assignments* 122

Chapter 4

Flip-Flops and Registers..... 125

- 4.1 Latches and Flip-Flops..... 126
- 4.2 Conversion from One Type of Flip-Flop to Another Type... 136
- 4.3 Operating Characteristics of a Flip-Flop 139
- 4.4 Application of Latches and Flip-Flops 142
- 4.5 Registers 143
- Student's Assignments* 150

Chapter 5

Counters 152

- 5.1 Asynchronous Counters (or Ripple Counters) 154
- 5.2 Decoding Errors (Glitches or Spikes) 157
- 5.3 Synchronous Counters..... 160
- 5.4 Design of Synchronous Counters..... 171
- 5.5 Pulse Train Generation (Sequence Generators) 182
- Student's Assignments* 192

Chapter 6

Logic Families 194

- 6.1 Switching Circuits 195
- 6.2 Classification of Digital Logic Family..... 199
- 6.3 Characteristics of Digital Logic Family..... 200
- 6.4 Logic Families 206
- Student's Assignments* 240

Chapter 7

A/D and D/A Converters243

- 7.1 Digital to Analog Converter 243
- 7.2 Analog to Digital Converters..... 257
- Student's Assignments* 267



A/D and D/A Converters


Introduction

In practical world most of the physical variables are analog in nature and can take on any value within a continuous range of values for example temperature, pressure, light intensity, audio signals etc. However, the digital systems perform all of their internal operations using digital circuitry. Any information that has to be input to a digital system must first be converted into digital form and the outputs are always in digital form. Therefore, the interfacing of analog and digital systems requires the data (signal) to be converted from one form to other.

The process of converting an analog signal to a digital form involves the sequence of four processes:

 
1. Sampling
2. Holding
3. Quantizing
4. Encoding

Here, 'sampling' and 'holding' operations are done simultaneously using a circuit known as **sample-and-hold circuit (S/H)**. The 'Quantizing' and 'Encoding' processes are done simultaneously using a circuit referred to as an "Analog to digital converter" (A/D converter or ADC). Now, the digital output has to be converted back to the analog form referred to as a "digital to analog converter" (D/A converter or DAC).



 7.1 Digital to Analog Converter

- The digital to analog conversion is a process of taking a value represented in digital code and converting it to a voltage or current which is proportional to the digital value. The input given to the converter is an n -bit binary signal available in parallel form.



General block diagram of DAC

- The analog output voltage V_0 of an n -bit straight binary D/A converter is related to the digital input by the equation.

$$V_0 = K [2^{n-1}b_{N-1} + 2^{N-2}b_{N-2} + 2^{N-3}b_{N-3} + \dots + 2b_1 + b_0]$$

or, analog output = ($K \times$ Decimal equivalent of digital input)

Where,

K = Proportionality factor

$b_N = 1$; if the N^{th} bit of digital input is '1'

$b_N = 0$; if the N^{th} bit of digital input is '0'

Example - 7.1

What is the largest value of output from an 8 bit DAC that produces 1 V for a digital input of 00110010?

Solution:

$$(00110010) = (50)_{10}$$

$$\therefore 1 \text{ V} = K \times 50 \Rightarrow K = 20 \text{ mV}$$

The largest output will occur for an input of $(11111111)_2 = (255)_{10}$

$$V_{\text{out(max)}} = 20 \text{ mV} \times (255)_{10} = 5.10 \text{ V}$$


Type of D/A converters

There are two types of commonly used D/A converters. These are:

- (i) Weighted Resistor DAC
- (ii) $R-2R$ ladder DAC

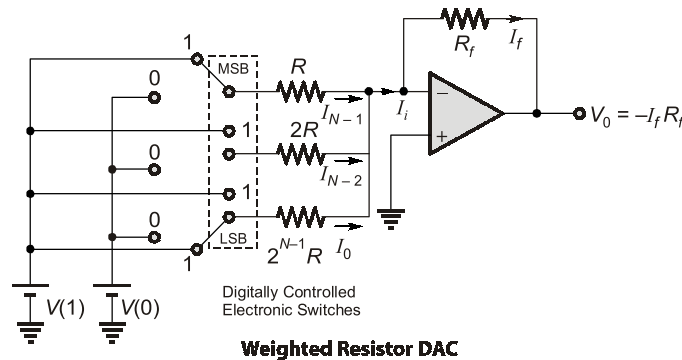7.1.1 Weighted Resistor D/A Converter

As the conversion from digital to analog signal involves a weighted sum corresponding to the input of the converter, the circuit given below can be used for the conversion.



In the circuit given above, since the resistance values are weighted in accordance with the binary weight, so it is called 'Weighted resistor D/A converter'. Here Op-amp is employed as 'summing amplifier'. In the above circuit the digital input (1 or 0) operate the switches. A switch is thrown to position 1 or 0 for a digital input corresponding to that bit being 1 or 0, respectively position '0'. The voltage applied to a resistor is $V(1)$ if the switch connected to it, in position '1' and $V(0)$ if it is in position '0'.

The current I_i is given by:

$$I_i = I_{N-1} + I_{N-2} + I_{N-3} + \dots + I_0$$

Where,

$$\left. \begin{aligned} I_{N-1} &= \frac{V_{N-1}}{2^0 \cdot R} \\ I_{N-2} &= \frac{V_{N-2}}{2^1 \cdot R} \\ I_{N-3} &= \frac{V_{N-3}}{2^2 \cdot R} \\ &\vdots \\ I_0 &= \frac{V_0}{2^{N-1} \cdot R} \end{aligned} \right\} \begin{aligned} &\text{Where,} \\ &V_N = V(1); \text{ if } b_1 = 1 \\ &= V(0); \text{ if } b_0 = 0 \end{aligned}$$

Since, Op-Amp output $V_0 = -I_i R_F$
for straight binary input, $V(0) = 0$ and $V(1) = -V_R$

\therefore The output voltage,
$$V_0 = -(-V_R) \left[\frac{R_F}{R} \cdot b_{N-1} + \frac{R_F}{2R} b_{N-2} + \dots + \frac{R_F}{2^{N-1}R} b_0 \right]$$

$$V_0 = \frac{R_F}{2^{N-1}R} \cdot V_R \cdot [b_{N-1} + b_{N-2} + b_{N-3} + \dots + b_0]$$

In the above equation the proportionality factor can be given as,

$$K = \frac{R_F}{2^{N-1} \cdot R} \cdot V_R$$

and

$$V_0 = \frac{R_F}{2^{N-1} \cdot R} (2^{N-1} V_{N-1} + 2^{N-2} V_{N-2} + \dots + 2^0 V)$$

- The Op-Amp in the above figure is operated in inverting mode to work as an excellent “**Current-to-Voltage Converter**”.

where,
$$I_i = \frac{V_R}{2^{N-1}R} \cdot [2^{N-1} b_{N-1} + 2^{N-2} b_{N-2} + \dots + 2^0 b_0]$$

or
$$I_i = \frac{V_R}{2^{N-1}R} \sum_{i=0}^{N-1} 2^i b_i$$

- The maximum output current will flow when all b_i coefficients are ‘1’.

i.e.
$$(I_i)_{\max} = \frac{V_R}{2^{N-1}R} \cdot (2^{N-1})$$

NOTE

- LSB Resistance = $(2^{N-1}) \times$ MSB Resistance.
- Typical value of resistance R ranges from 2.5 k Ω to 10 k Ω .

Disadvantage of Weighted-Resistor Type DAC

Weighted-resistor type DAC has several disadvantages which are as follows:

- When number of input bits is large, the resistance used for LSB has very large value.
- Due to the large difference in resistance values between the LSB and MSB, we cover a wide range of resistances tracking of which over a wide temperature range is difficult to produce.
- Due to the “Loading effect” (input impedance will not remain constant), accuracy of the system is less.
- Linearity is less.


7.1.2 R-2R Ladder DAC

The R-2R ladder DAC is further classified as:

- Normal ladder type
 - (i) Non-inverting OP-AMP Type
 - (ii) Inverting OP-AMP type
- Inverted ladder type
- Switch capacitor type

R-2R Ladder DAC by using Non-inverting OP-AMP

 - An R-2R ladder DAC uses resistors of only two values R and 2R. The input to the resistor is applied through digitally controlled switches.
- To analyze this circuit consider a 3-bit R-2R ladder DAC as shown in figure below.



R-2R Ladder DAC (using non-inverting Op-amp)

For a non-inverting op-amp

$$\text{Gain} = \frac{V_{out}}{V_{in}} = \left(1 + \frac{R_F}{R_1}\right)$$

The output analog voltage V_0 is given by


$$V_0 = \left(1 + \frac{R_F}{R_1}\right) \times \left(\frac{V_{ref}}{2^N}\right) \times \left(\sum_{i=0}^{N-1} 2^i b_i\right)$$

Therefore,

$$V_0 = (\text{Gain}) \times (\text{Resolution}) \times (\text{Decimal equivalent of binary input applied})$$

R-2R Ladder DAC by using Inverting Op-Amp

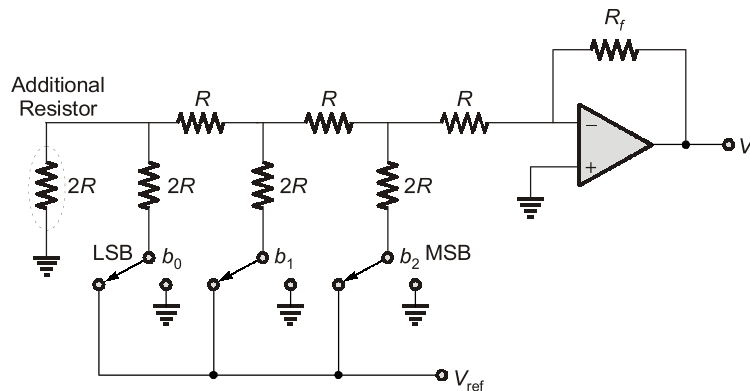R-2R ladder DAC with inverting Op-amp circuit is shown in the figure below.



R-2R Ladder DAC (using Inverting Op-amp)

In this circuit, we have assumed the digital input as '001' i.e. switch "S₀" is closed. This circuit is simplified using "Thevenin's theorem". Applying Thevenin's theorem at XX', YY' and ZZ', we get the circuits of Figure (a), (b) and (c) respectively.

 


Figure (a)

 


Figure (b)

 


Figure (c)

Here, digital input \Rightarrow equivalent voltage


$$001 \Rightarrow \frac{V_R}{2^3}$$

if,

$$010 \Rightarrow \frac{V_R}{2^2}$$

$$100 \Rightarrow \frac{V_R}{2^1}$$

 The value of the "input impedance" or "equivalent resistance" is 3R in each case. The equivalent circuit is given as,



$$V_0 = - \left(\frac{R_F}{3R} \cdot \frac{V_R}{2^3} \cdot b_0 + \frac{R_F}{3R} \cdot \frac{V_R}{2^2} b_1 + \frac{R_F}{3R} \cdot \frac{V_R}{2^1} b_2 \right)$$

$$V_0 = - \left(\frac{R_F}{3R} \right) \left(\frac{V_R}{2^3} \right) [4b_2 + 2b_1 + 1b_0]$$

\therefore The output voltage for n -bit DAC,

$$V_0 = (\text{Gain}) \times (\text{Resolution}) \times (\text{Decimal equivalent of binary input})$$

$$V_0 = \left(\frac{-R_F}{R_1 + R} \right) \times \left(\frac{V_{\text{ref}}}{2^N} \right) \times \left(\sum_{i=0}^{N-1} 2^i b_i \right)$$

Inverted R-2R Ladder DAC

In weighted resistor DAC and R-2R ladder DAC (Discussed above), the current flowing through the resistors changes as the applied input changes. Thus, more power dissipation causes the heating of the circuit, which in turn produces non linearity in DAC. To avoid this problem an inverted R-2R ladder type DAC is used in which current divides equally at each node irrespective of applied input. This is because the equivalent resistance to the right or to the left of any node is exactly 2R.

The figure below shows the circuit arrangement of inverted $R-2R$ ladder type DAC. This circuit works under the principle of summing currents.

from the figure

$$I_f = \frac{-V_0}{R_f}$$

where,


$$I_f = I_3 + I_2 + I_1 + I_0 = \frac{I}{2}b_3 + \frac{I}{4}b_2 + \frac{I}{8}b_1 + \frac{I}{16}b_0$$

Therefore,

$$I_f = \frac{I}{16} \sum_{i=0}^{N-1} 2^i b_i$$

$$\text{or } I_f = \frac{I}{2^N} \sum_{i=0}^{N-1} 2^i b_i$$
 
$$\text{and } V_0 = \left(-\frac{R_f}{R} \right) \left(-\frac{V_{ref}}{2^N} \right) \times \left(\sum_{i=0}^{N-1} 2^i b_i \right)$$



Inverted R-2R Ladder DAC

The most important feature of inverted $R-2R$ DAC is that, since all the switches are at the same potential even with changing input binary words. The stray capacitance is not able to produce slow down effects on the performance of the circuit. The $R-2R$ ladder DAC has following advantages over weighted resistor DAC:

- The $R-2R$ DACs have better linearity.
- It requires only two different type of resistors with values R and $2R$.

Note: A D/A converter which is used as a varying analog signal instead of fixed reference voltage is called a multiplying DAC.

Example - 7.2

(a) Design a 4-bit weighted resistor DAC whose full-scale output voltage is -5 V. The logic levels are $1 = +5$ V and $0 = 0$ V.

(b) In the above question what will be the value of output voltage when the input is 1101?

Solution:


The full-scale output voltage is the output voltage when the input voltage is maximum, i.e., 1111.

$$\therefore \text{Full scale output} = - \left[5V + \frac{5V}{2} + \frac{5V}{4} + \frac{5V}{8} \right] \times \frac{R_f}{R} = -5V$$

$$\therefore \frac{R_f}{R} = \frac{5}{9.357}$$

$$\therefore \text{Let } R_f = 10 \text{ k}\Omega$$

 - $R = 18.75 \text{ k}\Omega$
- $2R = 37.5 \text{ k}\Omega$
- $4R = 75 \text{ k}\Omega$
- $8R = 150 \text{ k}\Omega$




For input 1101 we will get,

$$\therefore V_{out} = -\left[5V + \frac{5V}{2} + 0 + \frac{5V}{8}\right] \times \frac{R_f}{R} = -8.125 \times \frac{10}{18.75} = -4.333V$$

Example - 7.3 Consider the circuit shown in the figure below:

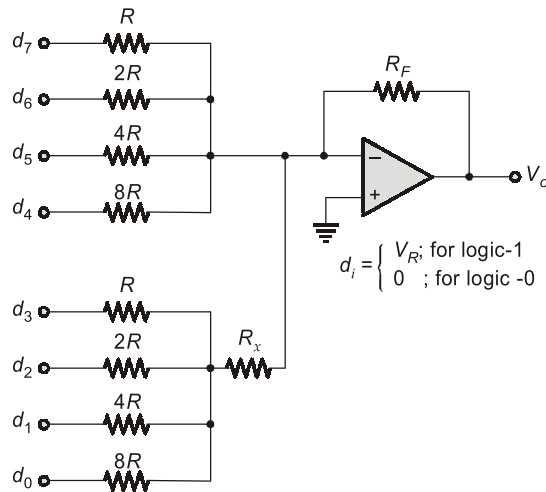- (i) If this circuit is to be used as an 8-bit (binary) digital-to-analog converter, then determine the relation between R_x and R .
- (ii) If the same circuit is to be used as a 2-decade BCD digital-to-analog converter, then determine the relation between R_x and R , by using the calculations obtained in part (i).



Solution:


- Let us assume that the binary logic values (1 or 0) are represented as $b_7, b_6, b_5, \dots, b_1, b_0$.

So,

$$d_i = \begin{cases} V_R i & \text{for } b_i = 1 \\ 0 & \text{for } b_i = 0 \end{cases}$$

$$d_i = V_R b_i$$

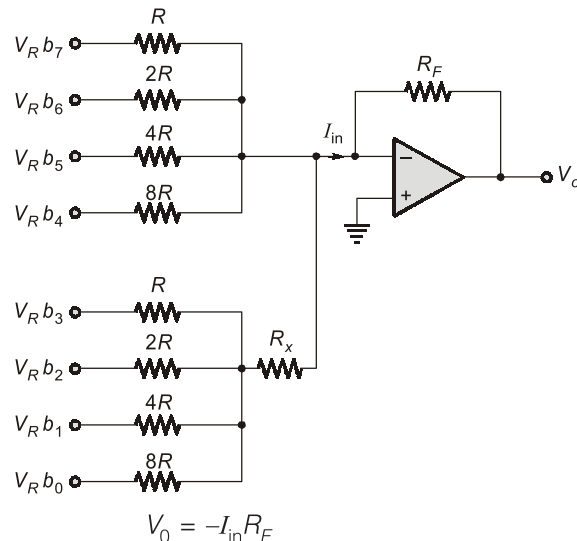- Considering the given circuit by modifying $d_i = V_R b_i$ as shown below.



- For a digital-to-analog converter,

$$V_0 \propto [\text{decimal equivalent of input binary code}]$$

$$V_0 = -I_{in}R_F$$

So,

$$I_{in} \propto [\text{decimal equivalent of input binary code}]$$

- Let, $I_{in} = I_0$ when $(b_7 \dots b_0) = (0000\ 0001)$

and $I_{in} = I_4$ when $(b_7 \dots b_0) = (0001\ 0000)$


$$(0000\ 0001)_2 = (1)_{10} \text{ and } (0001\ 0000)_2 = (16)_{10}$$

So,

$$I_4 = 16I_0 \quad \dots(i)$$

To calculate I_4 :

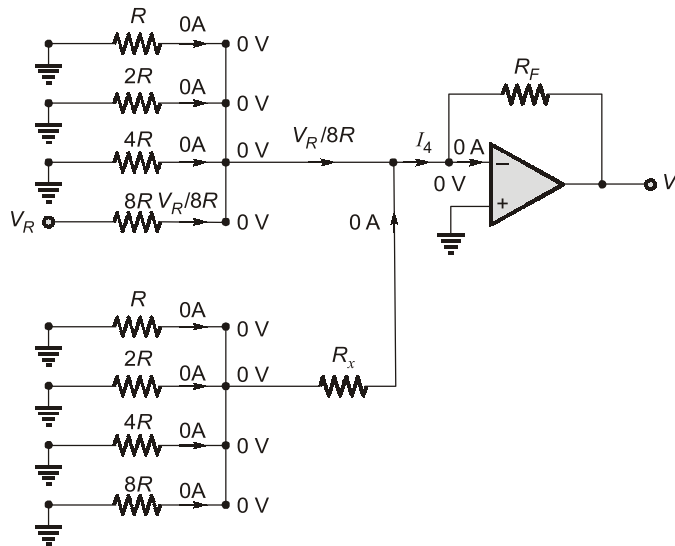- When $(b_7 \dots b_0) = (0001\ 0000)$, the given circuit can be equivalently drawn as,




So,


$$I_4 = \frac{V_R}{8R} \quad \dots(ii)$$

To calculate I_0 :

 - When $(b_7 \dots b_0) = (0000\ 0001)$, the given circuit can be equivalently drawn as,



 - The above circuit can be further reduced as,



By applying KCL at node 'A', we get,

$$\frac{V_R - V_A}{8R} = \frac{V_A}{R_P} + \frac{V_A - 0}{R_x} ; R_P = R \parallel 2R \parallel 4R = \frac{4R}{7}$$

$$V_A \left(\frac{1}{8R} + \frac{7}{4R} + \frac{1}{R_x} \right) = \frac{V_R}{8R}$$

$$V_A (R_x + 14R_x + 8R) = V_R R_x$$

$$V_A = \frac{V_R R_x}{8R + 15R_x}$$

and,

$$I_0 = \frac{V_A - 0}{R_x} = \frac{V_A}{R_x} = \frac{V_R R_x}{R_x (8R + 15R_x)} \quad \dots(iii)$$

- From equations (i), (ii) and (iii),

$$\frac{V_R}{8R} = 16 \left[\frac{V_R R_x}{R_x (8R + 15R_x)} \right]$$

$$15R_x^2 + 8RR_x = 128RR_x$$

$$15R_x = 120R$$

$$R_x = 8R$$

- So, when $R_x = 8R$, the given circuit can be used as an 8-bit (binary) digital-to-analog converter.

(ii) When the given circuit is used as a 2-decade BCD digital-to-analog converter,

$$I_4 = 10I_0 \quad \dots(iv)$$

- From equations (ii), (iii) and (iv), we get,

$$\frac{V_R}{8R} = 10 \left[\frac{V_R R_x}{R_x (8R + 15R_x)} \right]$$

$$15R_x^2 + 8RR_x = 80RR_x$$

$$15R_x = 72R$$

$$R_x = \frac{72}{15}R = 4.8R$$

- So, when $R_x = 4.8R$, the given circuit can be used as a 2-decade BCD digital-to-analog converter.

7.1.3 The Switched-Capacitor Type DAC

The switched-capacitor type DAC employs weighted capacitors instead of weighted resistors. In this method, charged capacitors form a capacitive voltage divider whose output is proportional to the sum of the binary inputs.

- Q.12** In a standard 4-bit flash type ADCs total number of resistors connected are
 (a) 4 (b) 15
 (c) 6 (d) 8
- Q.13** Consider an n-bit slowest Dual-slope type ADC having conversion time ' t_c ' equals to 2 msec is clocked with 16 kHz pulses, then this ADC converts a binary sequence of
 (a) 4-bits (b) 5-bits
 (c) 6-bits (d) 16-bits
- Q.14** The ratio of maximum conversion time of 8 bit digital ramp type ADC to that of 8 bit successive approximation type is
 (a) 256 (b) 32
 (c) 8 (d) 2
- Q.15** Consider a 6-bit digital ramp ADC having clock frequency is 1 MHz. If a DAC has full scale output is 10.2 V and a threshold voltage of comparator is $V_T = 4$ mV.
 (i) The digital binary equivalent for an input voltage of 3.5 volts will be
 (a) 001011 (b) 010110
 (c) 011011 (d) 001110
- (ii) For the above statement, the conversion time to reach this value equals to
 (a) 21.95 μ sec (b) 10.98 μ sec
 (c) 13.92 μ sec (d) 26.97 μ sec
- Q.16** An 8-bit ADC with a full-scale output voltage of 8.5 V is designed to have a $\pm \frac{1}{2}$ LSB accuracy.
 If the ADC is calibrated at 25°C and operating temperature ranges from 0°C – 50°C, then maximum net temperature coefficient of ADC should not exceed
 (a) $\pm 977 \mu\text{V}/^\circ\text{C}$ (b) $\pm 1953 \mu\text{V}/^\circ\text{C}$
 (c) $\pm 1000 \mu\text{V}/^\circ\text{C}$ (d) $\pm 1450 \mu\text{V}/^\circ\text{C}$
- Q.17** In a tracking-type A/D converter a 5 MHz clock pulse is to applied to convert a single analog input to a digital output sequence 01101110. Required average conversion time is
 (a) 51 μ sec (b) 25.5 μ sec
 (c) 102 μ sec (d) 12.8 μ sec
- Answer Key:**
 1. (d) 2. (c) 3. (d) 4. (b) 5. (d)
 6. (b) 7. (i) (a) & (ii) (c) 8. (b) 9. (d)
 10. (d) 11. (c) 12. (c) 13. (a) 14. (b)
 15 (i) (b) 15 (ii) (a) 16. (b) 17. (b)

