try to avoid calculation



Read question carefully

Leading Institute for ESE, GATE & PSUs

ESE 2025 : Mains Test Series

UPSC ENGINEERING SERVICES EXAMINATION

Electrical Engineering

Test-2: Digital Electronics + Microprocessors + Systems and Signal Processing

Name :			
Roll No:			
Test Centr	es		Student's Signature
Delhi 🗆	Bhopal	Jaipur 🗆	
Pune _	Kolkata 🗌	Hyderabad 🗆 ·	

Instructions for Candidates

- Do furnish the appropriate details in the answer sheet (viz. Name & Roll No).
- 2. There are Eight questions divided in TWO sections.
- 3. Candidate has to attempt FIVE questions in all in English only.
- 4. Question no. 1 and 5 are compulsory and out of the remaining THREE are to be attempted choosing at least ONE question from each section.
- 5. Use only black/blue pen.
- 6. The space limit for every part of the question is specified in this Question Cum Answer Booklet. Candidate should write the answer in the space provided.
- 7. Any page or portion of the page left blank in the Question Cum Answer Booklet must be clearly struck off.
- 8. There are few rough work sheets at the end of this booklet. Strike off these pages after completion of the examination.

Question No.	Marks Obtained
Section	and the second second
· · · · · · · · · · · · · · · · · · ·	
Q.1	24
Q.2	45
Q.3	
Q.4	
Section	on-B
Q.5	. 49
Q.6	41
Q.7	32
Q.8	
Total Marks	191
Obtained	

Signature of Evaluator

Cross Checked by

IMPORTANT INSTRUCTIONS

CANDIDATES SHOULD READ THE UNDERMENTIONED INSTRUCTIONS CAREFULLY. VIOLATION OF ANY OF THE INSTRUCTIONS MAY LEAD TO PENALTY.

DONT'S

- Do not write your name or registration number anywhere inside this Question-cum-Answer Booklet (QCAB).
- 2. Do not write anything other than the actual answers to the questions anywhere inside your QCAB.
- 3. Do not tear off any leaves from your QCAB, if you find any page missing do not fail to notify the supervisor/invigilator.
- 4. Do not leave behind your QCAB on your table unattended, it should be handed over to the invigilator after conclusion of the exam.

DO'S

- 1. Read the Instructions on the cover page and strictly follow them.
- 2. Write your registration number and other particulars, in the space provided on the cover of QCAB.
- 3. Write legibly and neatly.
- 4. For rough notes or calculation, the last two blank pages of this booklet should be used. The rough notes should be crossed through afterwards.
- If you wish to cancel any work, draw your pen through it or write "Cancelled" across it, otherwise it may be evaluated.
- 6. Handover your QCAB personally to the invigilator before leaving the examination hall.

sd:-

Section A : Digital Electronics + Microprocessors

.1 (a) Perform the BCD operation on the following number system:

- (i) (010001101001.0110) + (100000010111.1000)
- (ii) (011001010100.0101) (100101111001.0110)
- (iii)(011001100110.0110) (010010011001.1001)

[4+4+4 marks]

(1) (010001101001.0110)= -1129.075

4 (100 00 0010111.1000) = 23.50

⇒ (010001101001·0110) + (100000010111·1000) -1129·75 + 28.50

- 2 -1106.25.
- » (101010101010).

ii) (011001010100.001010)-(10010100100)

9 0110 01010100.0101


+0110 1000 0110 . 1010


110011011010.1101

Actual result =

1100.10100100 1100

Go through the golution

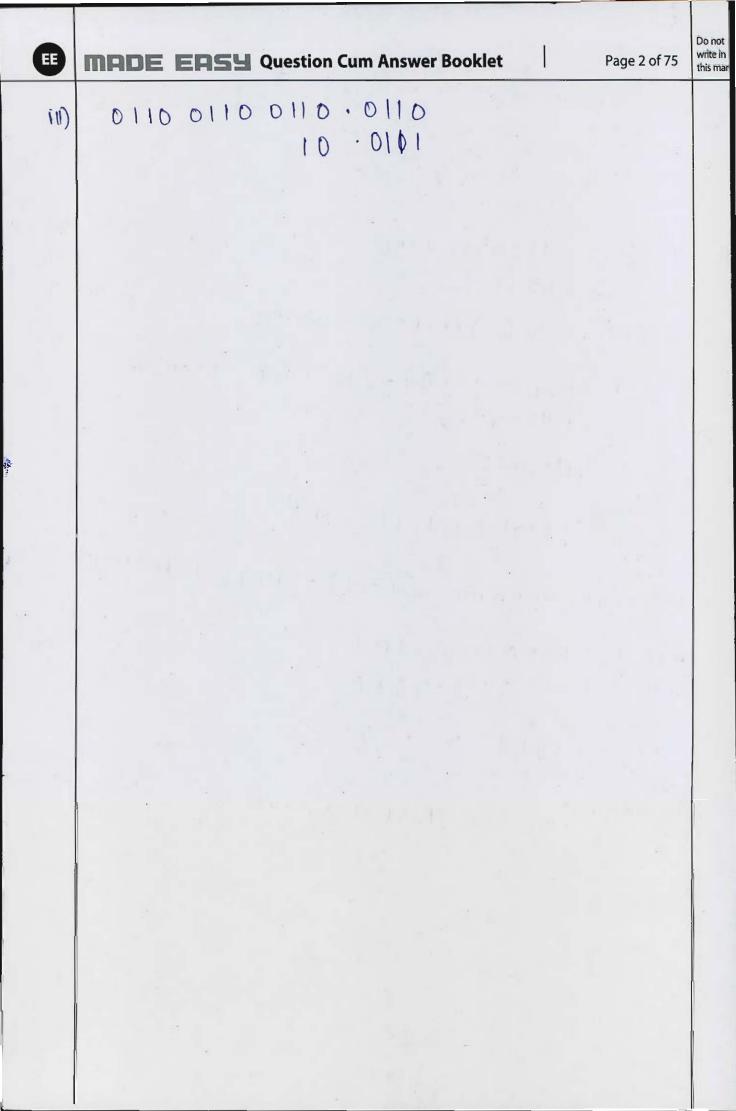

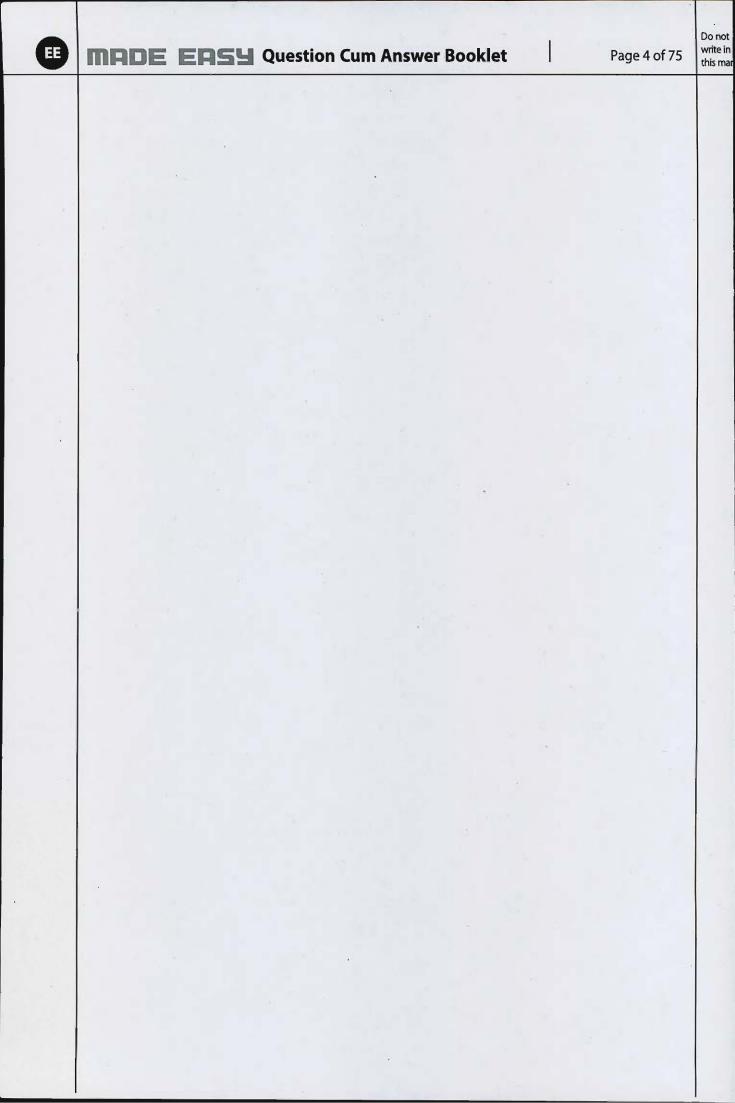

.1 (c)

Determine the minimized expression for the given below Boolean function in SOP form using K-map:

 $F(A, B, C, D) = \Pi(0, 1, 4, 5, 6, 7, 9, 13).$

Implement the minimized function using NAND gate only.

[12 marks]

sdc)


F(AB, CD = TL (0, 1, 4, 5, 6, 7, 9, 13) F(AB, CD) = Σ (2,3,8,10,11,12,14,15). CD CD CD CD

Franco) = AC + BC + AD

= AC+BC+AD


AC. BC + AD



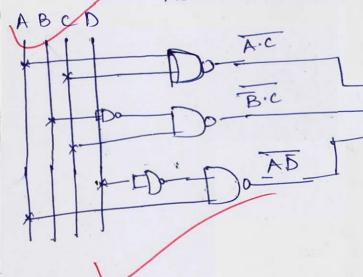




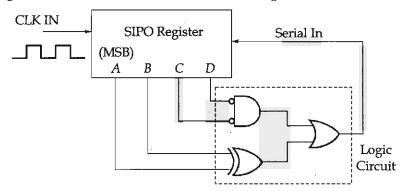1 (d) A shift register with associated combinational logic circuit is shown in figure below:



Explain its operation by drawing waveforms for the output of shift register (ABCD). Assume that initially shift register is in state ABCD = 1111.

[12 marks]

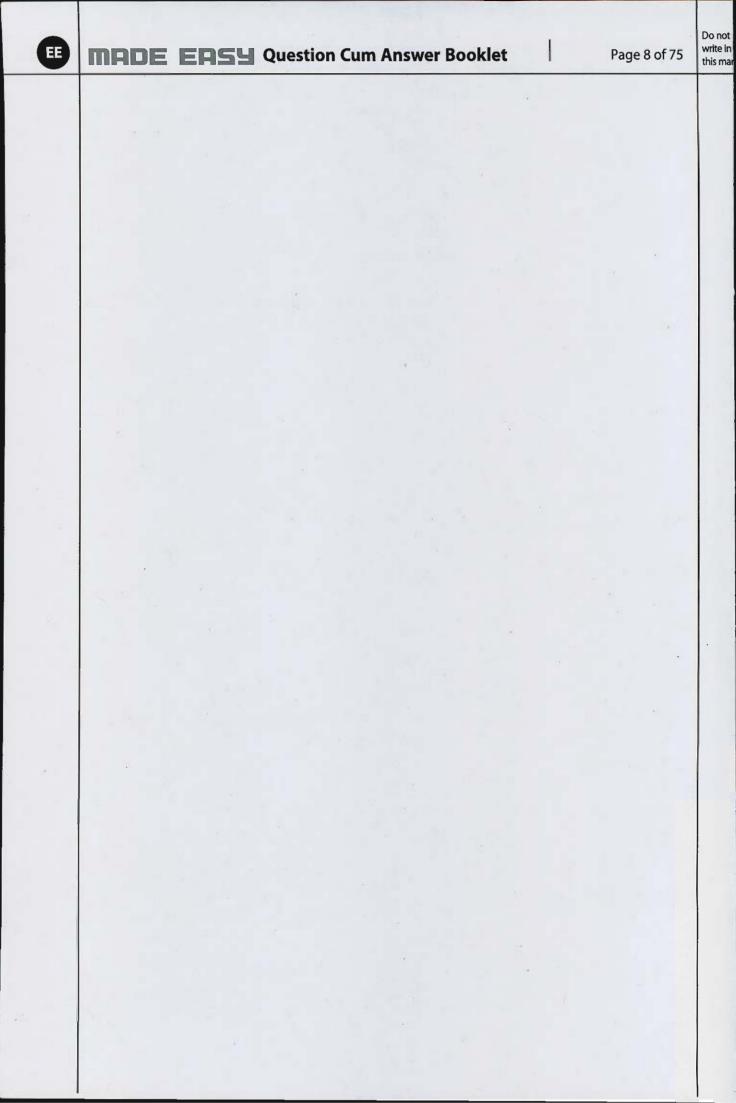

.1 (e)

For an 8085 microprocessor write an assembly language program to move a block of 10 bytes of data from one section of memory to another section of memory. Write comments for selected instructions.

01:

Consider the 10 byte data is Stored at [12 marks] and Need to be transferred location C300H D 300 H. to

initiated the HL with Address where is initiated DE poir with Address where is country for Lobyte to transfer LX1 H . C300 H MVI B 09 H data

data is copied from Memorry MOV A, M localin to accumulator

Try to avoid MX H

DETSTA D

:- Initaled the HL with Address when data LXI H C 300H

- initiazed DE pair with Address while data LXI D D300H

need to be stoned Initial Counter for 1018 yte of dalit MVIBDAH

: Content of Memory is moved to Accounter LOOP MOV A, M.

Content of Acculations stored to DE.


STAX D : Increate for next date


- Increment DE to Store plata into INXH

DEINXD new localt :- counter is decrease DCRB

JNZ LOOP

Halt HLT

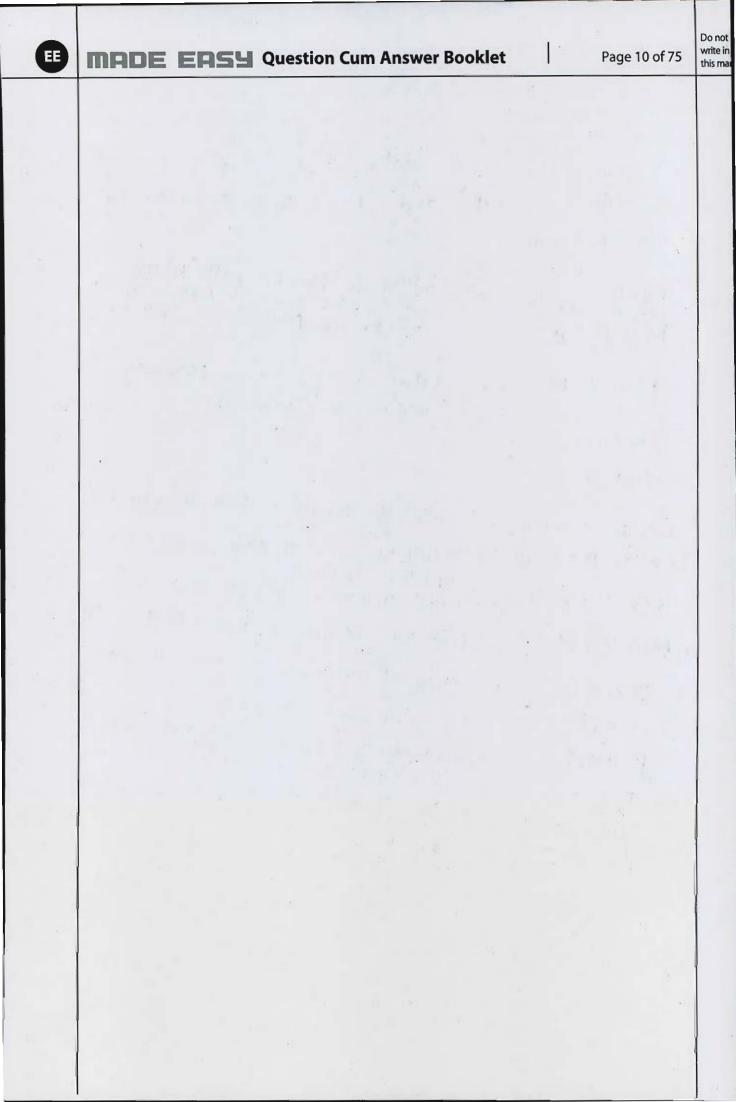

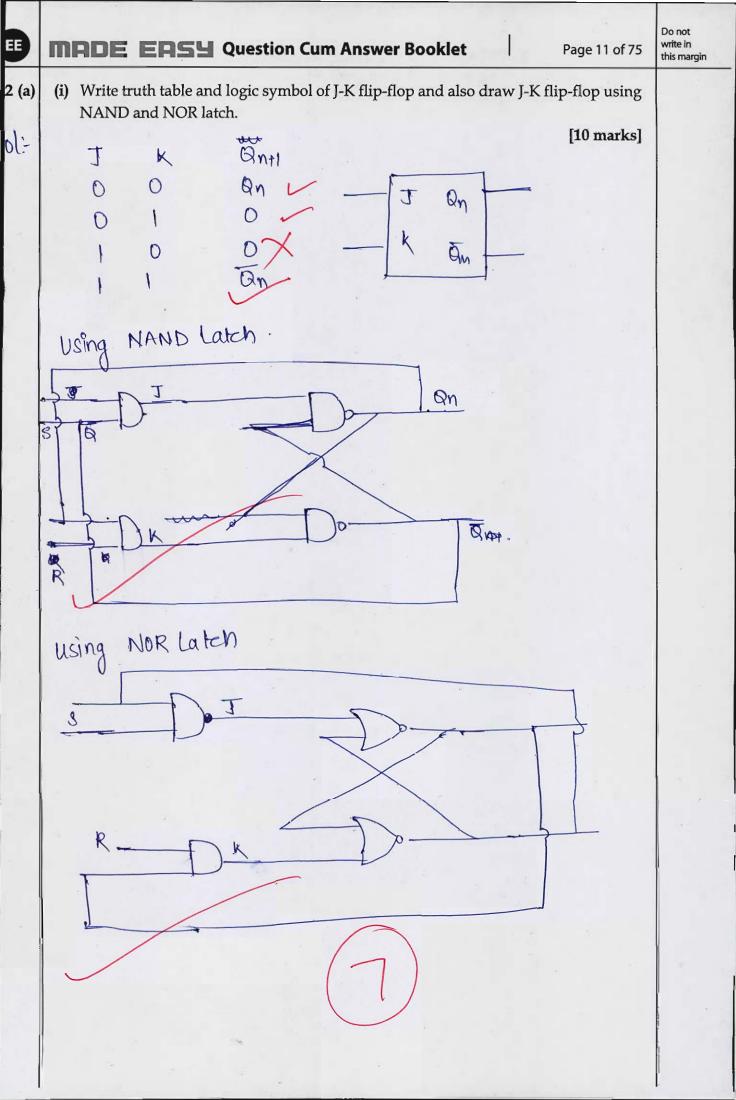




2 (a)


(ii) Convert SR flip-flop into JK flip-flop and explain race around condition in J-K flip-flop.


iol:

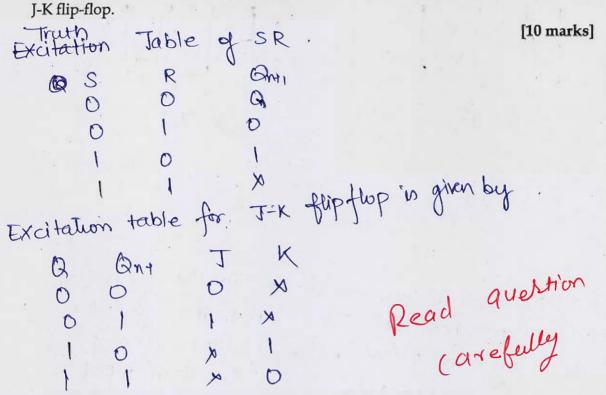


Now

S	R	Qn	anti	1	K	•
0		0	0	0	X	and the
D	0	1	1	×	0	
0	1	0	0	0	×	
0	1	1	0	×	1	:
1	0	0	+	1	×	
1	0	1	1	×	0	
1	1	0	Ø 8 1	洋	×	1 × 1
1	I	1	000	×	Ø I	1.

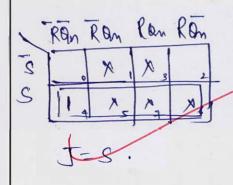

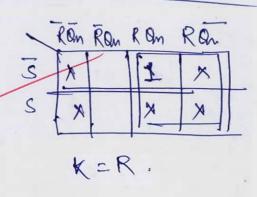

1

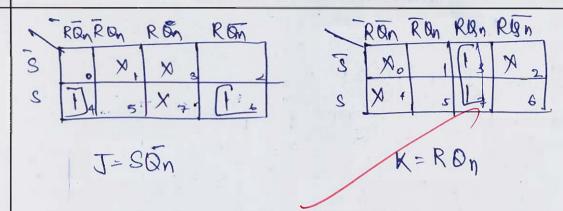



The Race around condition in JK flip flop occur in JK flip when Both the imput are high. The state loggle is present state multiple time if the width of CLK pulse is greater than input
The width of CLK pulse is greater than input
bulse. To avoid race around condition.


- 1) Edge trigging is used.
 2) Pulse width must be that the textingur-
- Master-Salve this configuration is used

2 (b) Design a 3 × 8 decoder with active low enable pin and also draw its logic circuit.

臣	A.	B	C	10	II	12	[3]	4	T 5	16.	T 7
0	0	0	0	1	0	0	0	0	0	0	0
0	0	0	1	0	153	0	0	0	0	0	0
0	0	1.	0	. 0	0	1	0	0	0	0	0
0	0	1	1	D	0	0	1	0	0	0	0
0	1	0	0	0	O	0	0	1	0	0	0,
0		0	1	0	0	0	0	Ó	1	8	0
0	1	1	0	0	0	0	0	0	0	1	0
0	1	1	1	0	0	0	0	0	0	0	1
1	0	0	0	0	0	O	0	0	0	0	_
1	0	0	1	O	0	0		1	0		0
1	0	1	0	0	0	0			0	0	0
1	0	1		0	0	0		-	0	0	0
1	+	0	0	0	0	C	, ,	5	0	0	0
1	1	0	1	0	0	C	0		0	0	0
+	1	1	0	0	0	C	0		0	0	0
1	1	1	1	0	0	C	0		0	0	0

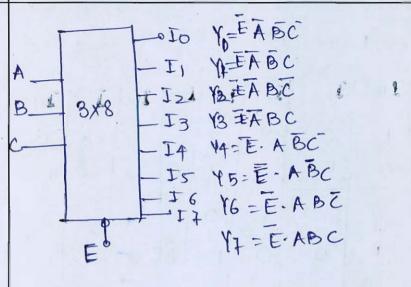

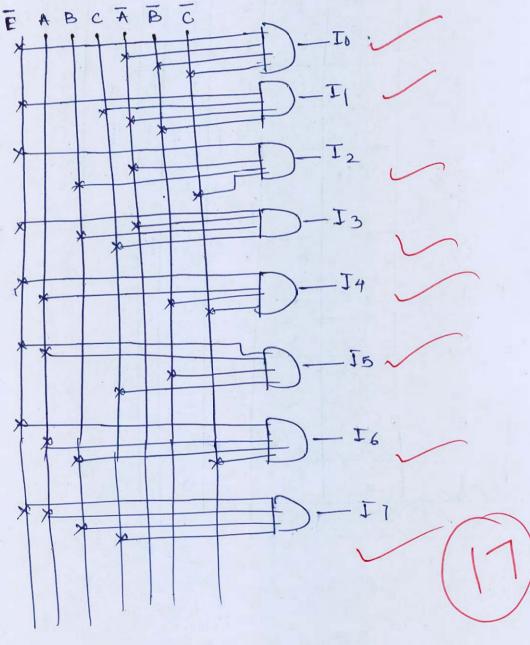

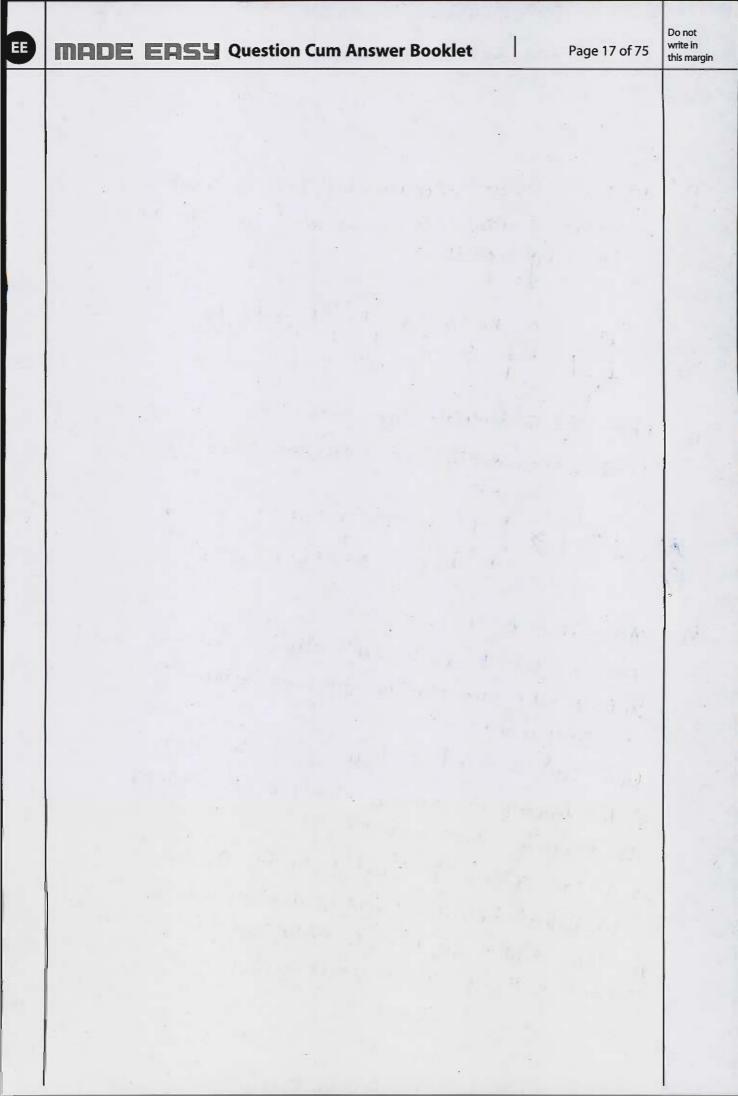

Page 18 of 75 Q.2(c)Explain the following instructions of 8085 microprocessor: (i) RLC (iii) CALL 16-bit address (ii) RAR (iv) RET (v) CMP RLC .: Rotate Accumulator Left without Carny I) -> content of acculmator is rotate to with carriy bit beings update Dg Dz P1 D7 D6 D5 D4 RAR: Rotate Accolatmator Right through Carry bil-In this Acculatmatus is solate as through Carry bit 1) DO DI DA CALL-16 bit Address This is the beauch instruction which is used iu) to call - lhe sub-rountine program return written in programme. When call is excuted following is the sequen 1) The from next address stored in Pc counter is push to stack register ii) The Call address is boaded to PC counter so as to desired location where sub-southi is written-It take 5M/c and 184 state as GT-opcode

feetch 2 Read & 2 weite cycle

W)

RET: If is return statement which is weed to lake programme to that point from wher call instruction is being called twhen RET is excuted. Instruction is being called twhen RET is excuted. He orginal Address stored in stack counter by the precounter and program return. In pushed to pre counter and program return.

V)


CMP:- It is logical instruction know as COMPARE If Compare the Accumulation Content with registre or memory content and affect the cy and ZD.

ABY B CY=D Z=0.

A < B CY=1 Z=0.


A = B CY=0 Z=1.



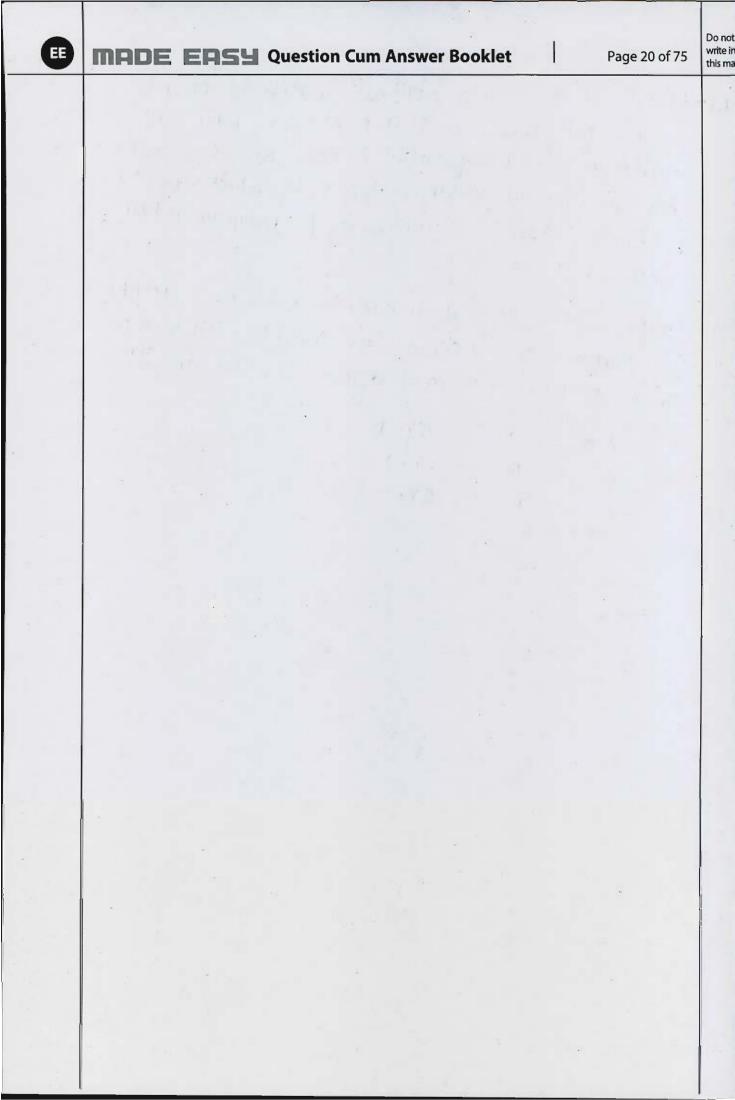

.3 (a)

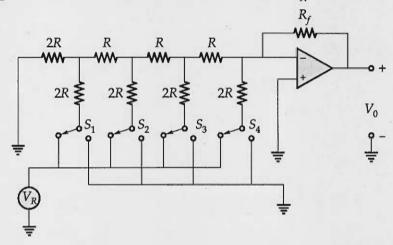
(i) Consider a 4-bit R-2R DAC shown in figure. Assume the feedback resistance R_f of the op-amp is variable, the resistance $R = 10 \text{ k}\Omega$ and $V_R = 10 \text{ V}$.





Determine the values of R_f that should be connected to achieve the following output conditions:


- 1. The value of 1 LSB at the output is 0.5 V.
- 2. An analog output of 6 V for a binary input of 1000.
- 3. The full scale output voltage of 12 V.
- 4. The actual maximum output voltage of 10 V.
- (ii) Explain the working of flash type ADC with the help of truth table.

[10 + 10 marks]

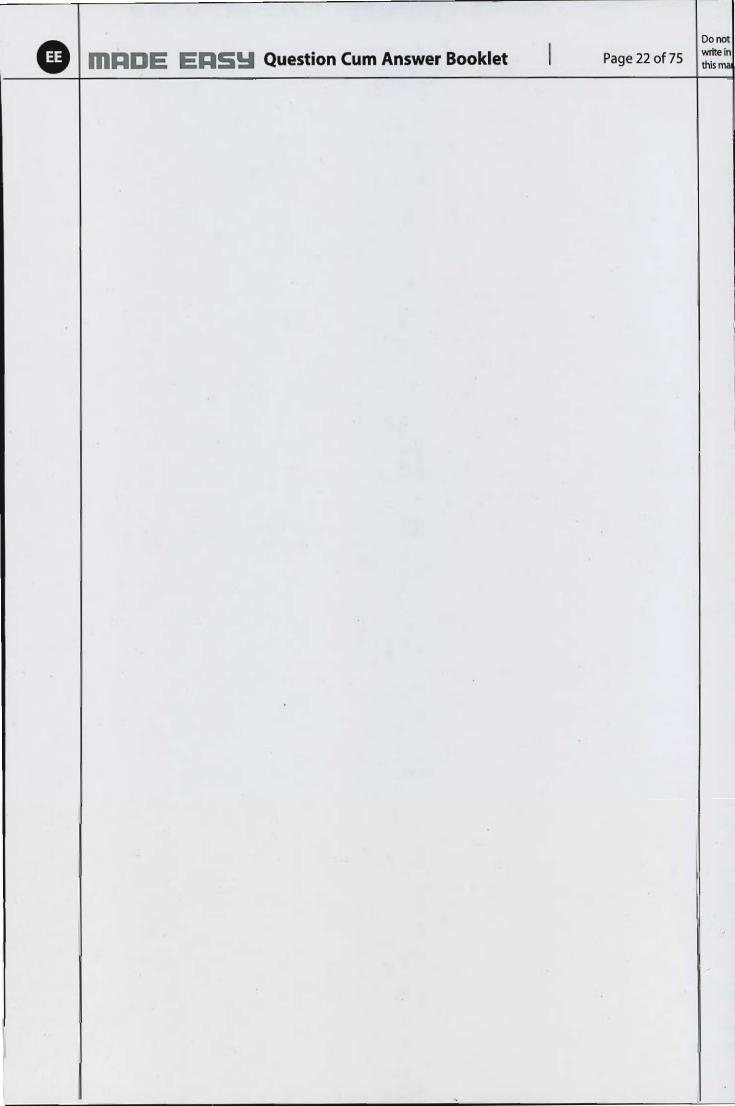


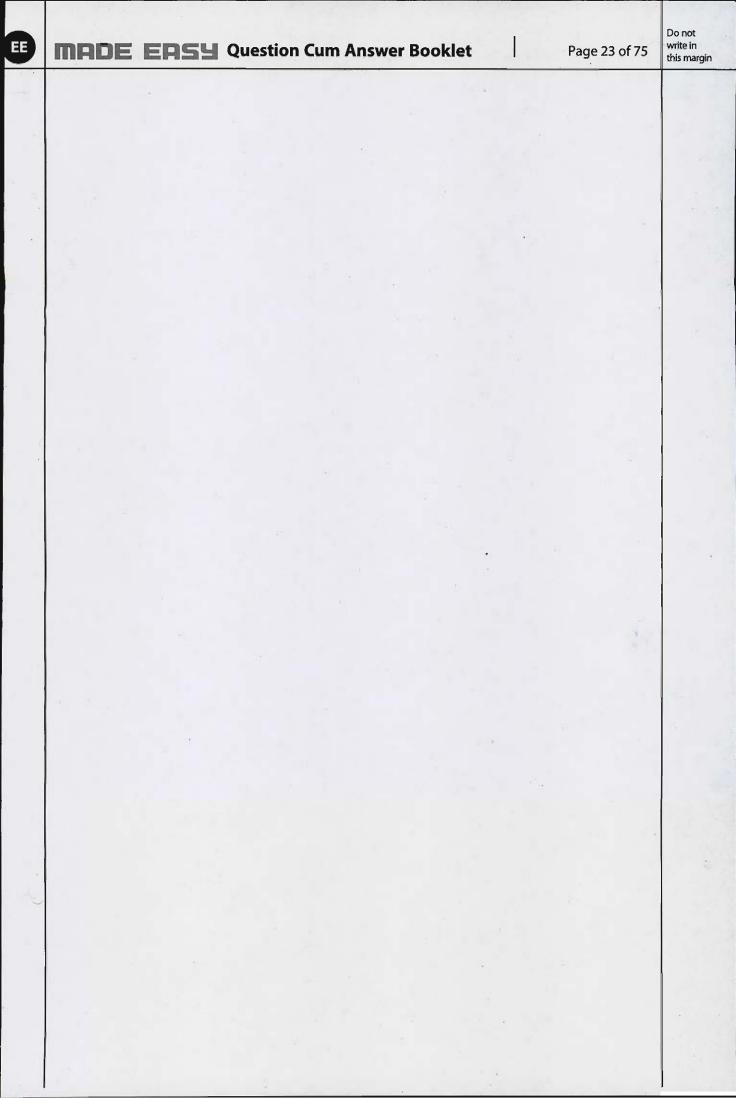

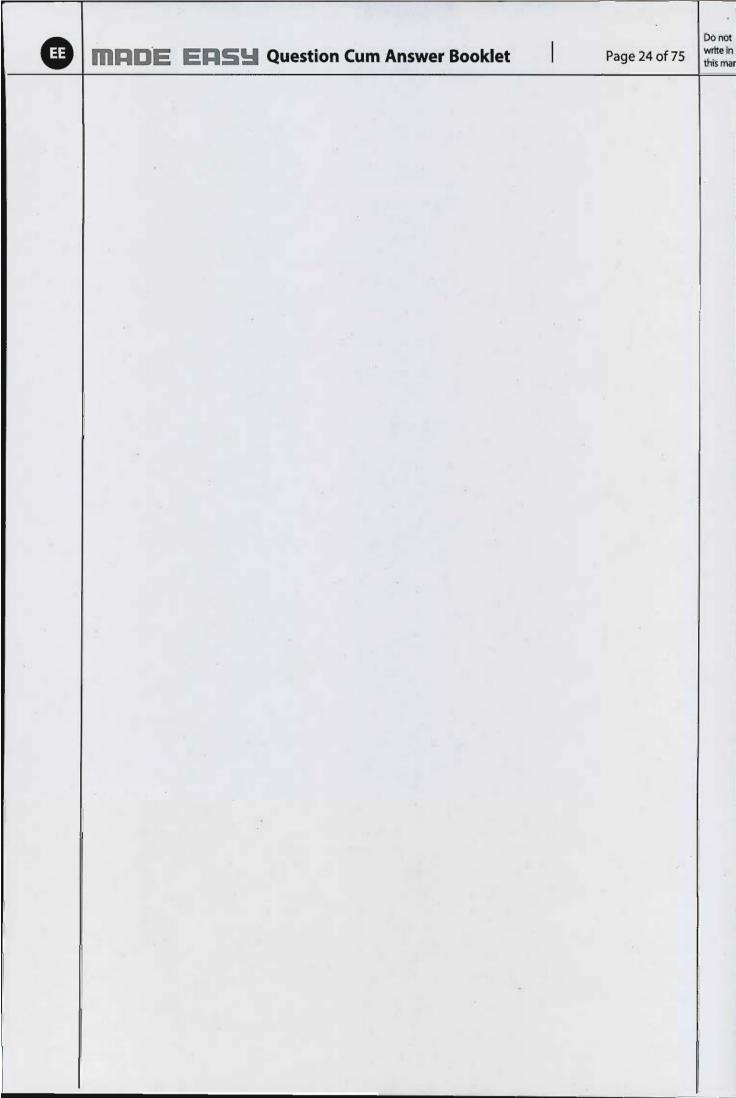

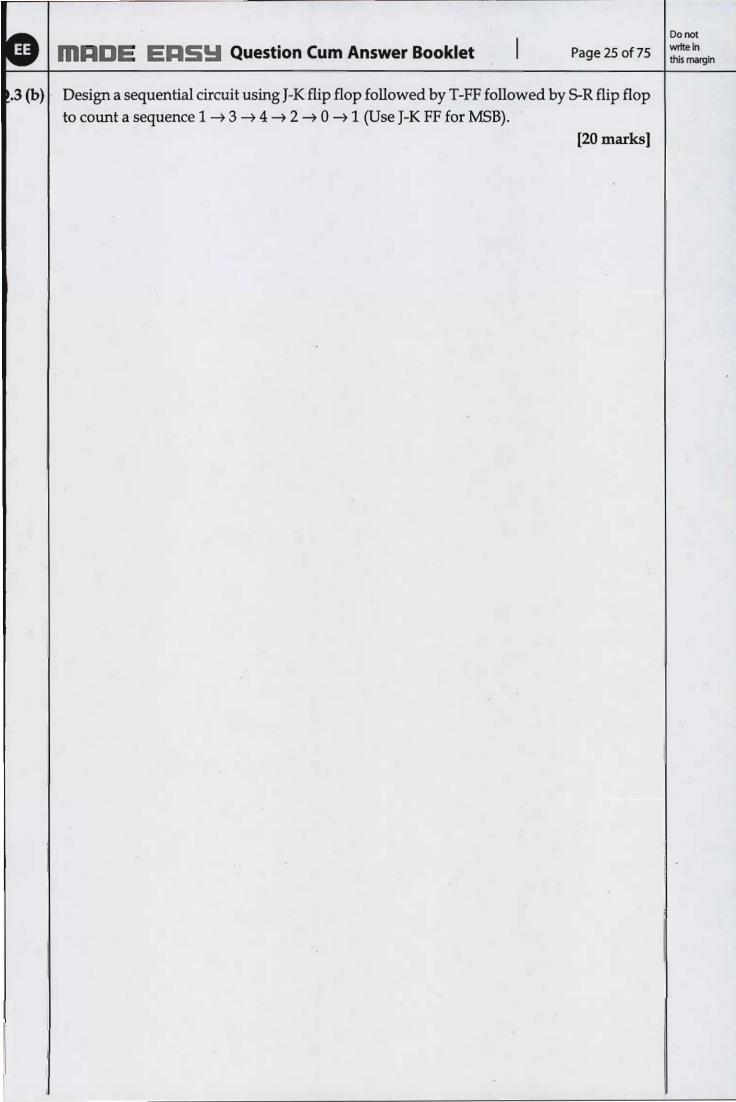




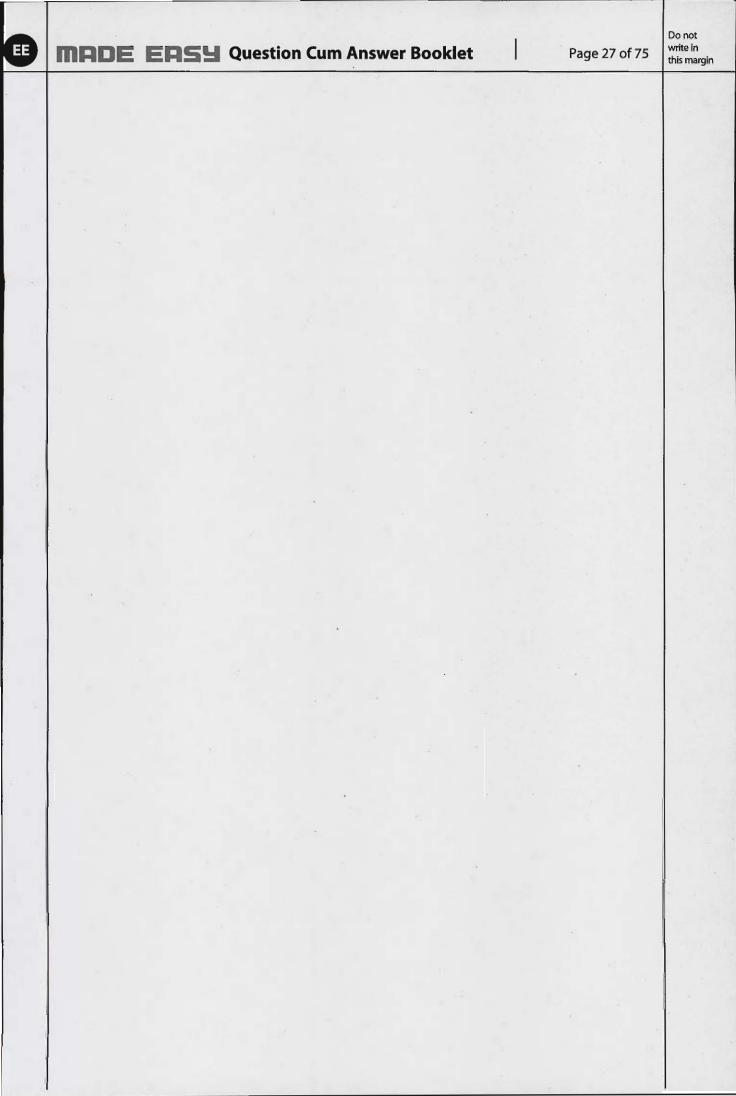

Q.3 (c)

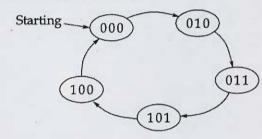
(i) The state transition diagram of a synchronous counter is given in figure. Design the counter circuit using S-R flip flops.




(ii) Draw EX-OR gate using transmission gates.

[14 + 6 marks]



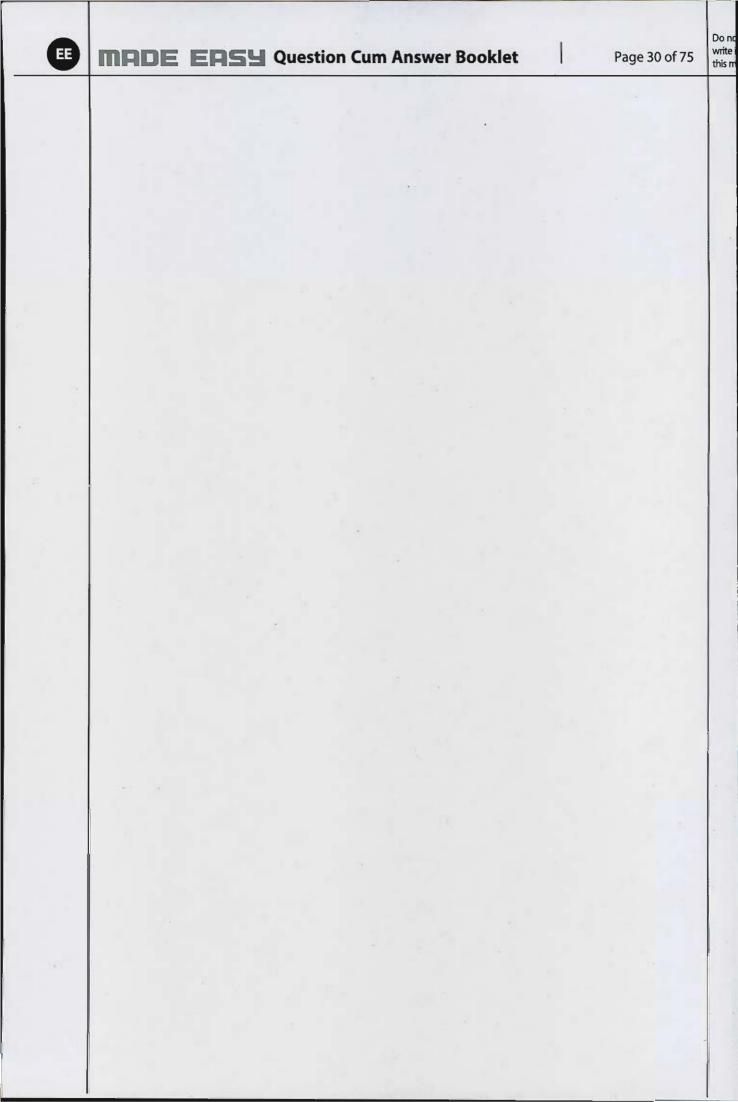

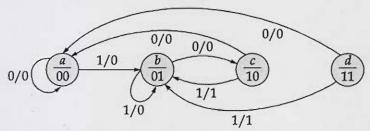4 (a) Consider the state diagram shown below:



- (i) Obtain the state reduction diagram.
- (ii) Design a clocked sequential machine using JK FFs for the given sequential circuit.


[8 + 12 marks]





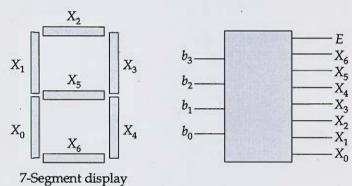Q.4 (b)

A seven segment display consists of seven light-emitting diodes (LEDs) as shown below:





where, E = 0 for valid digit with the display showing the corresponding digit.

E = 1 for invalid digit with the display showing the symbol 'E'.


Implement the above given seven segment display using a ROM.

[20 marks]

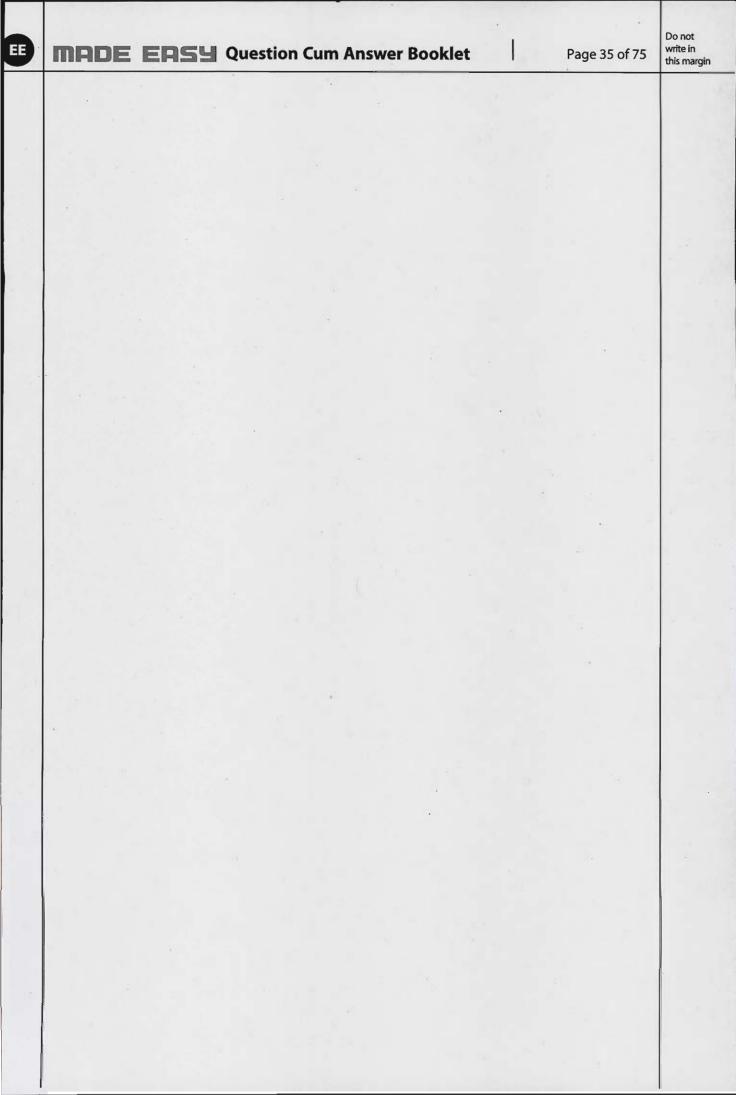

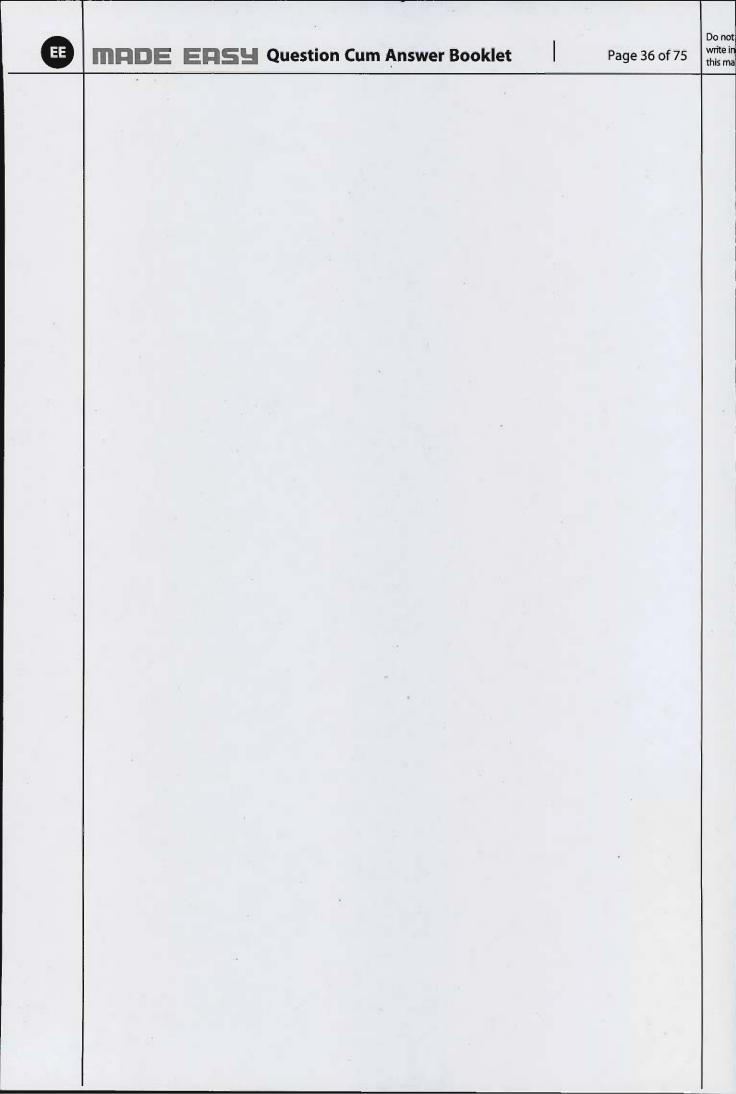



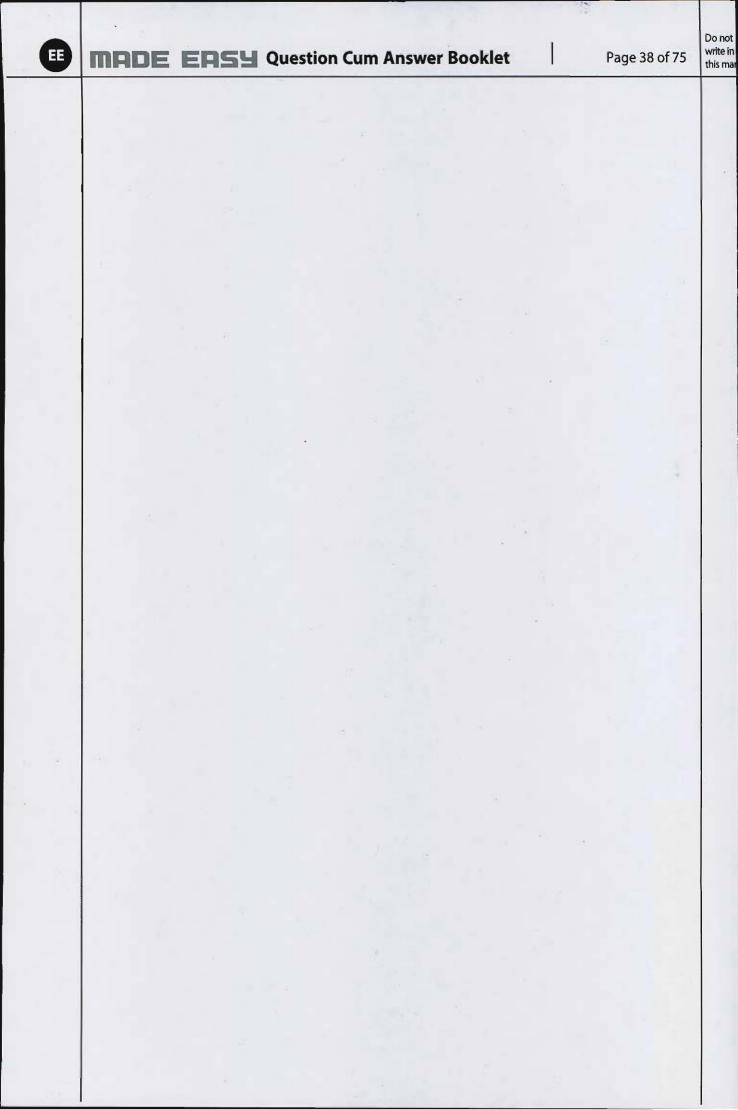

[4+4+4 marks]

Section B: Systems and Signal Processing

Q.5 (a)

A stable system with zero initial conditions is described by the difference equation y(n) = x(n) - 2x(n-1) + x(n+1).

- (i) Find the impulse response h(n) of the system.
- (ii) Plot the output y[n] for an input, x[n] = u[n-2]
- (iii) Find the value of $\sum_{n=1}^{\infty} y[n]$ for input x[n] = u[n-2].

Taking & transferm of difference equalin

Taky universe Z-transform


$$h(n) = 8(n) + 8(n+1) - 28(n-1)$$

Cii


$$y(n) = \chi(n) * h(n)$$

 $y(n) = (u(n-2)) * (8(n) + 8(n+1) - 28(n-1))$
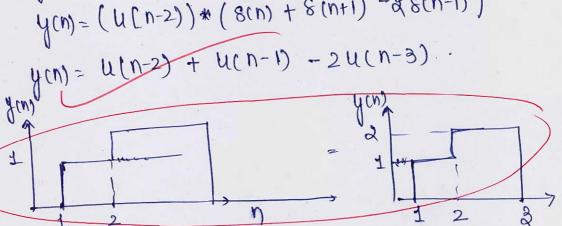
$$\frac{1111-27+4111-1)}{1111-27+4111-1}$$



(iii)

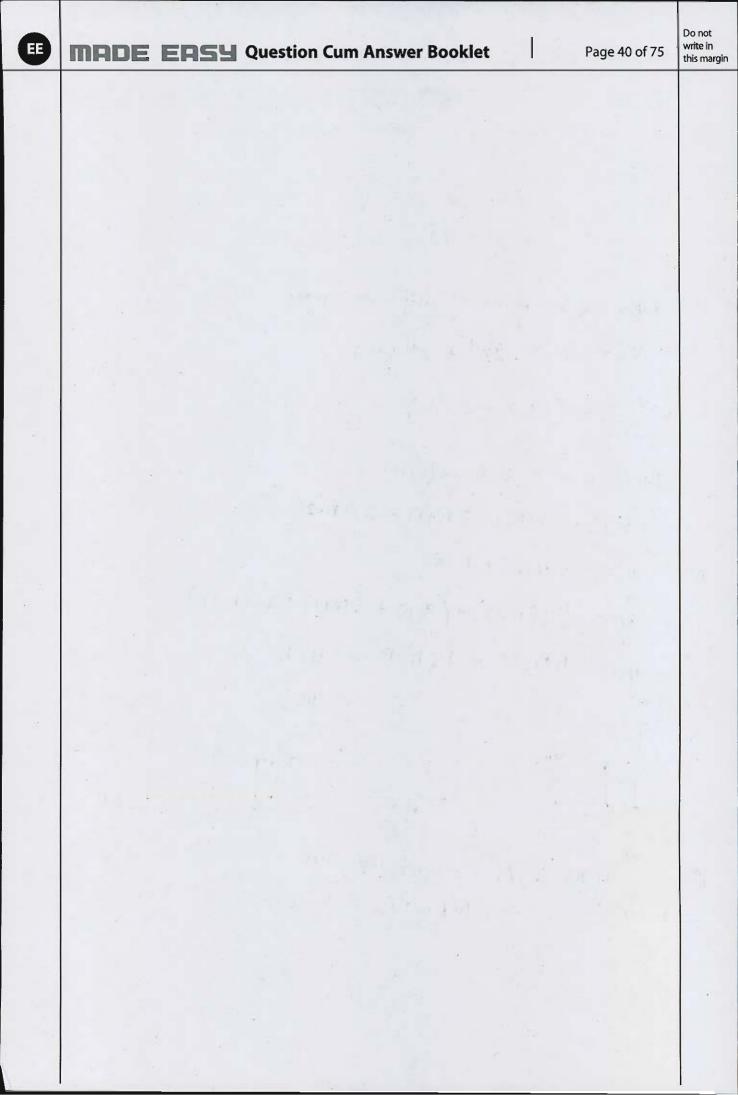

Q.5(b)

Determine the inverse z-transform of the following X(z) by the partial fraction expansion method,

$$X(z) = \frac{z+2}{2z^2 - 7z + 3}$$
if the ROCs are (a) $|z| > 3$, (b) $|z| < 1/2$ and (c) $1/2 < |z| < 3$.

[12 marks]

Sol:

$$\chi(z) = \frac{z+2}{(z-3)(z-1/2)}$$

$$\chi(z) = 2$$
 $(z-3)$ $(z-1/2)$

a) ROC 12173. R.H. Signal

Inverse z transform

$$X(\mathbf{Z}) = \frac{2z^{\dagger}}{(1-3z^{\dagger})} - \frac{z^{\dagger}}{(1+1)z^{\dagger}}$$

I averse & transform.

werse a transporting
$$= 2(3)^{n+1}u(n+1) - (\frac{1}{2})^{n+1}u(n+1)$$
.


b) For ROC |Z| < 1/2. Left from 2 signing

$$\chi(n) = -2 (3)^{n+1} u(-n) + (\frac{1}{2})^{n+1} u(-n)$$
c) For Roc $\frac{1}{2}(+z) < 3$

For ROC
$$\frac{1}{2}$$
 is RH signal & $\frac{2}{(2-3)}$ is Litt signal $\frac{2}{(1-1)2^{2}}$ is RH signal
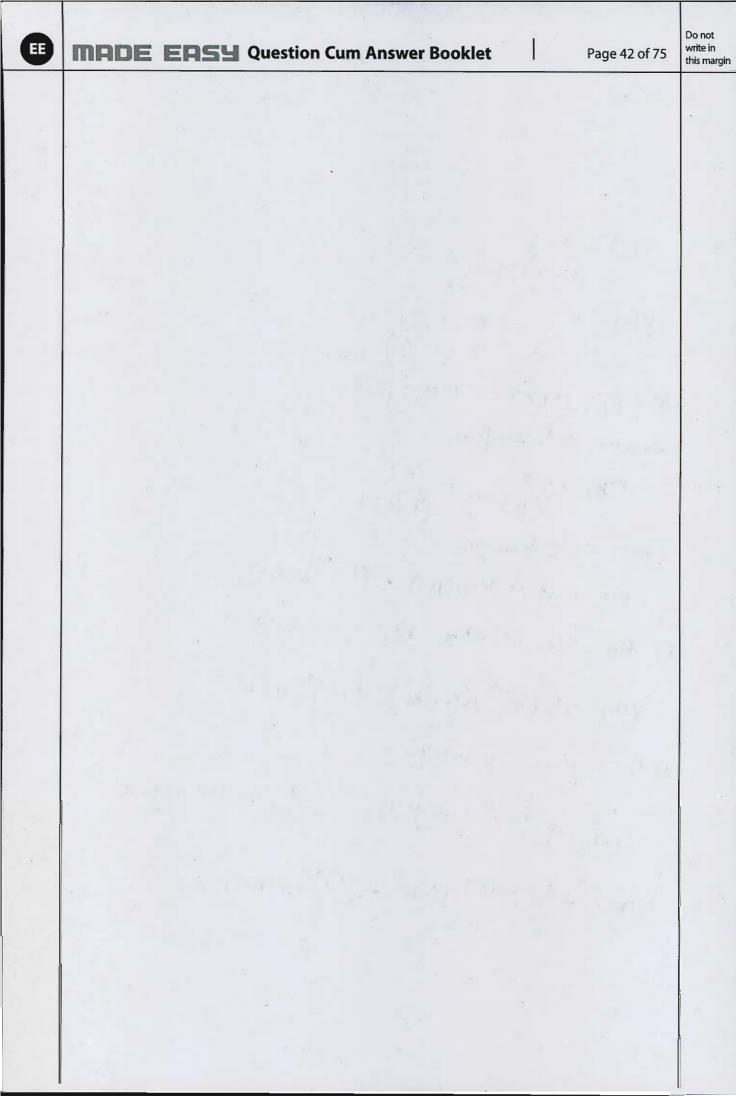
$$\chi(n) = -2 (3)^{n+1} u(-n) - (\frac{1}{2})^{n+1} u(n-1)$$





[12 marks]

Q.5 (c)

Determine the z-transform and the ROC of the signal, $x(n) = a^n u(n) - a^n u(n-1)$.

Sol :-

Z-transform of signal is given by

$$\chi(z) = \sum_{n=0}^{\infty} \chi(n) \alpha z^{-n}$$

$$\chi(z) = \sum_{n=-\infty}^{\infty} (a^n u(n) - a^n u(n-1))^n z^{-n}$$

$$\chi(z) = \sum_{n=0}^{\infty} (az^{-1})^n - \sum_{n=1}^{\infty} (az^{-1})^n$$

$$\Rightarrow \frac{1-az^{\dagger}}{1-az^{\dagger}} = 1$$

Dince it is finite signed Henre it ROC is complete & plane expect \$20 \$300.



Do not

write in

this margin

Q.5 (d)

An LTI system has a unit step response given by $s(t) = (1 - e^{-t} - te^{-t}) u(t)$. For a certain input x(t), the output is observed to be equal to $y(t) = (2 - 3e^{-t} + e^{-3t}) u(t)$. What is x(t)? [12 marks]

30l -

$$S(s) = \frac{1}{s} - \frac{1}{s+1} - \frac{1}{(s+1)^2} = \frac{(s+1)^2 - S(s+1) - s}{s(s+1)^2}$$

$$S(S) = \frac{1}{S(SH)^2}$$

Now, -lo-llies system alt) es applied result in y(t)

$$y(t) = (2-3e^{-t} + e^{-t}) + (st3) - 3s(st3) + s(st1)$$

$$y(t) = \frac{2}{s} - \frac{3}{s} + \frac{1}{s+3} = \frac{3(st1)(st3) - 3s(st3) + s(st1)}{s(st1)(st3)}$$

$$Y(S) \Rightarrow 2(S^2+4S+3) - 3S^2-9S+S^2+S$$

 $S(S+1)(S+3)$

$$Y(s) = \frac{6}{s(s+1)(s+3)}$$

$$X(S) = \frac{G(SH)}{S(S+3)}$$

Hence x(t) = (2 +1e-3t) u(t)

: | x(t) = (2+4e-3t) ut)

Coog cools

Q.5 (e)

ol e)

Consider the signal $y(t) = e^{-2t}u(t)$ is the output of a causal all-pass system for which the system function is

$$H(s) = \frac{s-1}{s+1}$$

- Find and sketch at least two possible inputs x(t) that could produce y(t).
- (ii) From the solutions obtained in part (i), what is the input x(t) if it known that a stable system exists that will have x(t) as an output and y(t) as the input? Find the impulse response h(t) for this system.

[12 marks]

NOW
$$Y(S) = H(S) \cdot X(S)$$


 $X(S) = \frac{Y(S)}{H(S)} = \frac{p(S+1)}{(S+2)(S-1)}$


FOR ROC 15171

For ROC 59-2.

For stability of system, the system Roc must-include Jos axis: include Roc go axis Hence

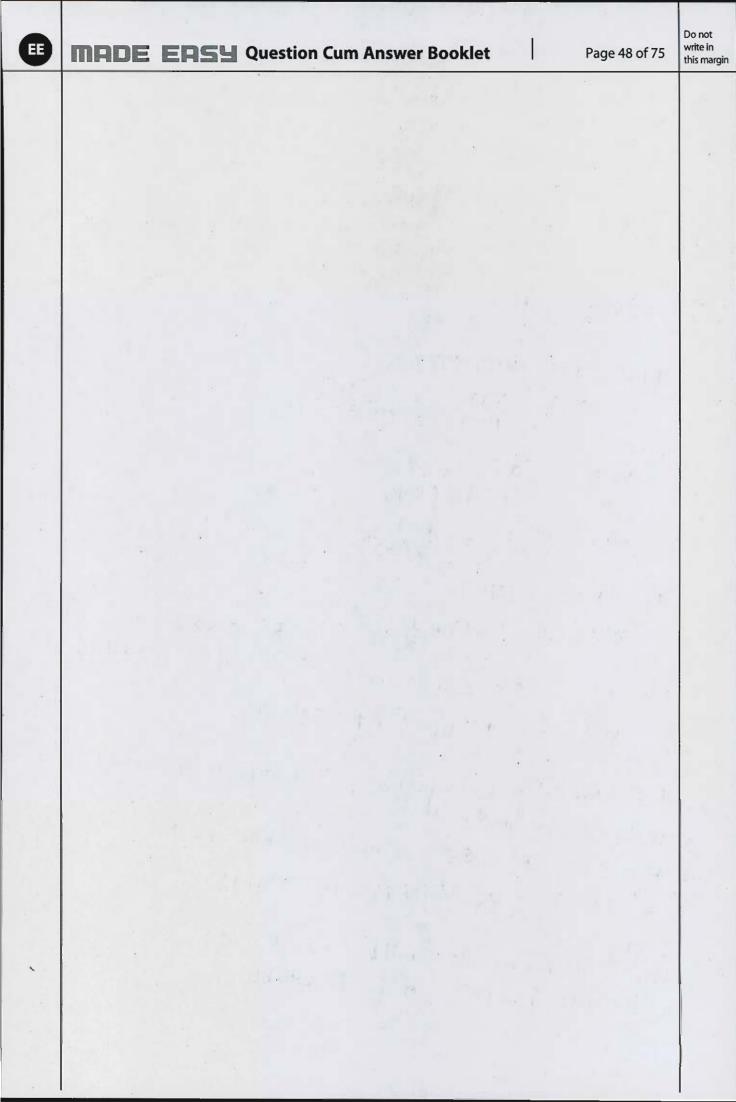Hence—the imput—will -2 < ROCKI include jou axis and is stable.



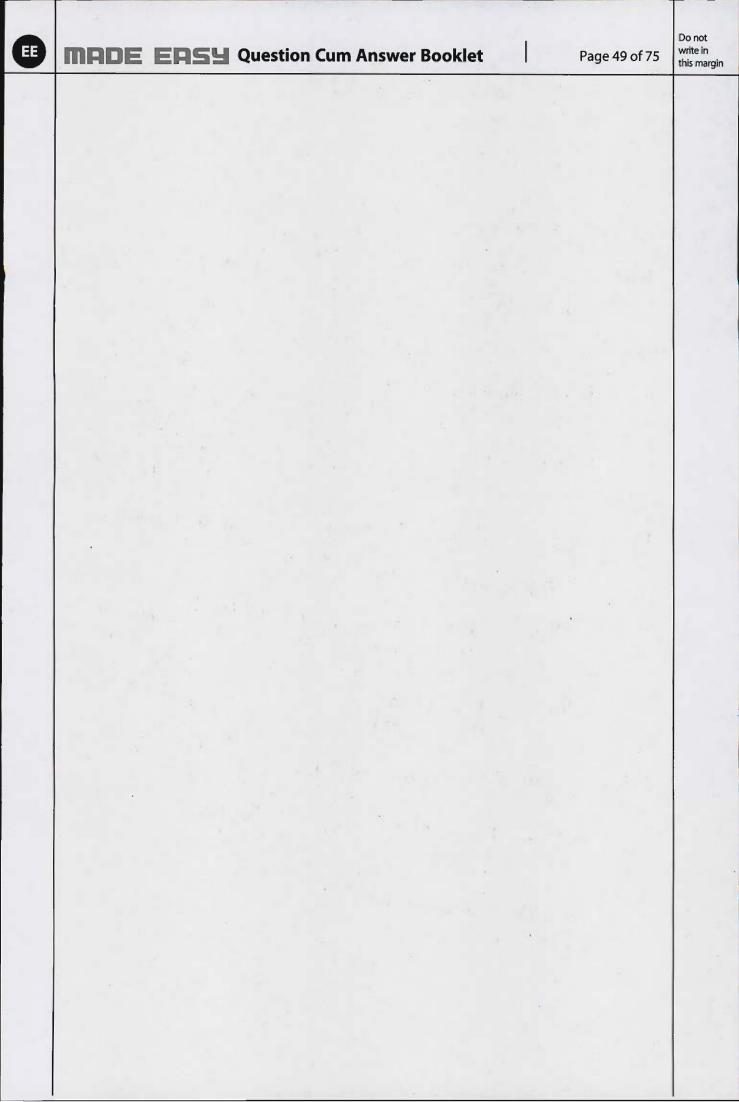

- Q.6 (a)
- (i) Compute: y(t) = x(t) * h(t) where, $x(t) = \operatorname{sinc} \alpha t$, $h(t) = \operatorname{sinc} \beta t$; $\alpha > \beta$
- (ii) Compute : y(t) = x(t) * h(t)

$$x(t) = \operatorname{rect}\left(\frac{t-6}{2}\right), h(t) = \operatorname{rect}\left(\frac{t}{2}-3\right)$$

[10 + 10 marks]

X(W)

$$F[hH] = H(w) = b tect \left(\frac{w}{2bx}\right) \xrightarrow{Ax} bx \qquad w$$

$$Y(w) = \frac{1}{b} \operatorname{rect}\left(\frac{w}{2\pi b}\right)$$
, $\frac{1}{a} \operatorname{rect}\left(\frac{w}{2\pi a}\right)$ Since $\frac{1}{2\pi a}$ $\frac{1}{2\pi a}$ $\frac{1}{2\pi a}$ $\frac{1}{2\pi a}$


$$Y(w) = \frac{1}{ab} \frac{\text{rect}(w)}{2\pi b}$$

$$y(t) = \frac{1}{a} sa(\pi bt)$$
 or $\frac{1}{a} sincpt$

Good Hoarn

$$\chi(t) = rect \left(\frac{t-6}{2} \right)$$

$$h(t) = rect \left(\frac{t-6}{2} \right)$$

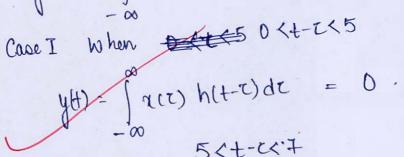



Case II

Case
$$\Pi$$
-

 $(t-z)$ 7 7 .

 $t+z$
 $y(t)$ - $\int x(z) h(t-0) = 0$

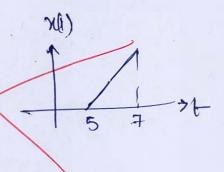

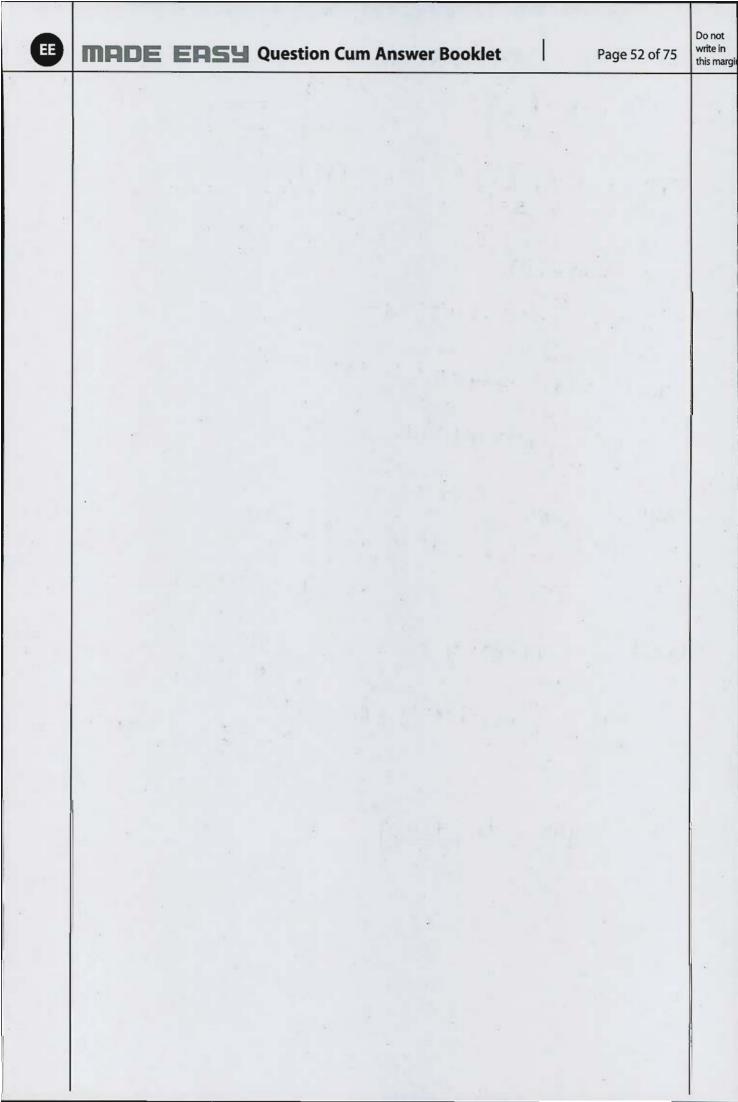

Q.6(b)

Given below are the impulse response of FIR filter. Identify the type of filter implemented using this impulse response.

(i)
$$h[n] = 5\delta[n] - 7\delta[n-1] + 7\delta[n-3] - 5\delta[n-4]$$

(ii)
$$h[n] = 5[\delta[n] - \delta[n-2]]$$

[10 + 10 marks]

1)
$$h(n) = 58(n) - 78(n-1) + 78(n-3) - 58(n-4)$$

Taking I transformer

Taking & This fitter filter is symmettical about 8(n-2) and is odden symmetric.

around Stn-2)

Hence this filter is even symmetrical. 1-71

58cm


h(m) = 58(n) - 58(n-2) 11) Since - His

taking ztransforms of hon)

This filter is symmetrical about -8(n-1). The and follow the

X(n) = - X(-n)

Hence it is odd symmettical filter

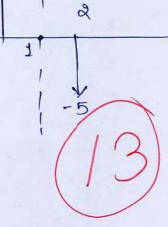



Q.6(c)

ol 1)

- (i) Using impulse invariant method, convert the given analog filter transfer function $H(s) = \frac{1}{c^2 + \sqrt{2}c + 1}$ to digital transfer function with a sampling period 1 sec.
- (ii) Find the Fourier transform of Gaussian modulated signal $x(t) = e^{-at^2} \cos \omega_c t$.

[10 + 10 marks]

The root of this equation
$$S^2 + J_2S + I = 0$$
.
 $S = -J_2 + I_2S + I = 0$.

$$H(S) = \frac{1}{(S+1/52)^2 + (\frac{1}{152})^2}$$

Now

EE

$$\sin(w_0 n) u(n) = \frac{Z \sin n w_0}{Z^2 - 2Z \cos w_0 + 1}$$

$$\sin(\frac{1}{2}n) = \frac{z \sin(\frac{1}{2}x)}{z^2 - 2z \cos(\frac{1}{2}x) + 1} = \frac{z(0.650)}{z^2 - z \cos(\frac{1}{2}x) + 1}$$

Question Cum Answer Booklet

Hence.

$$H(Z) = 0.650 \cdot (2/0.493)$$
 = $\frac{1.81Z}{4.11Z^2 - 9.08Z + 1}$.
 $(2/0.493) = \frac{1.52}{0.493} + 1$.


$$H(z) = \frac{0.82 z^{-1}}{(1 - 0.75 z^{-1} + 0.24 z^{-2})}$$

ii)
$$F(\omega) = \int_{-\infty}^{\infty} x(t) e^{-j\omega t} dt$$

$$F(\omega) = \int_{-\infty}^{\infty} e^{-at^2} \cdot \cos \omega ct \cdot e^{-j\omega t} dt$$

$$f(\omega) = \int_{2}^{\infty} (e^{-at^2} e^{+j(wc-\omega)t} + e^{-j(wc+\omega)t}). d$$

In Complete solution

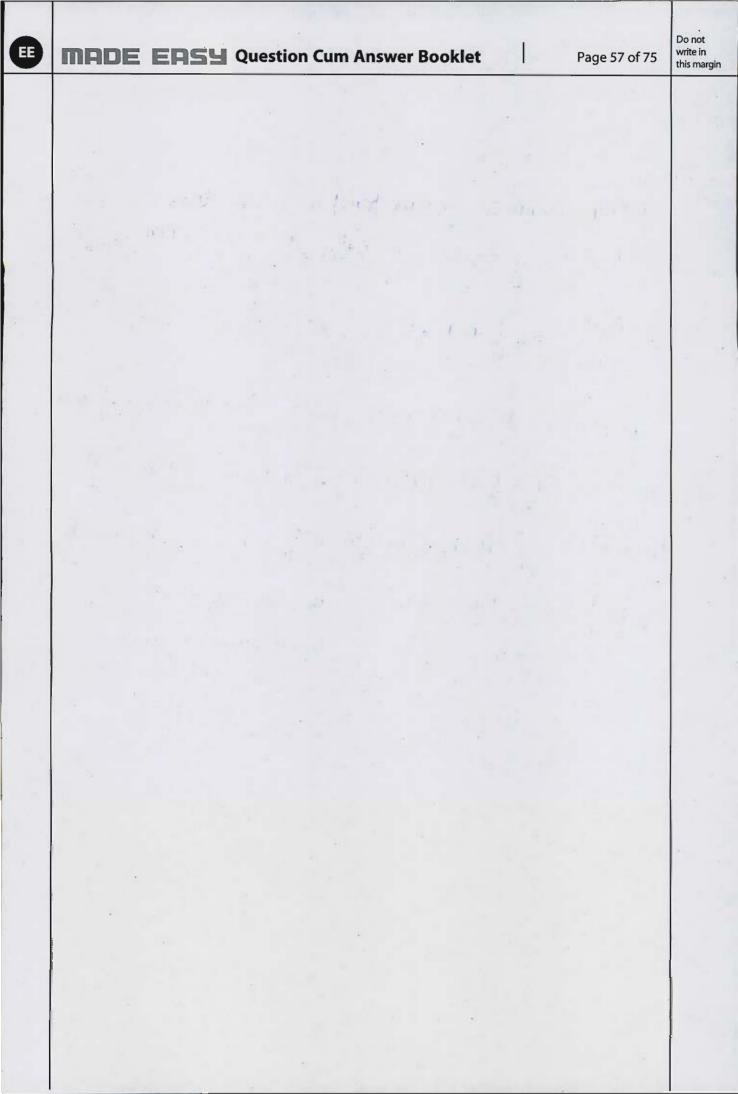

- Q.7 (a)
- (i) Find the magnitude and phase response for the system characterized by the difference equation

$$y(n) = \frac{1}{6}x(n) + \frac{1}{3}x(n-1) + \frac{1}{6}x(n-2)$$

[8 marks]

Sol:

Taking Diskarete fourier transform of function $Y(ejw) = \frac{1}{6} \times (ejw) + \frac{1}{3} \times (e^{\dagger jw}) \cdot e^{\dagger jw} + \frac{1}{6} e^{-\frac{1}{3}2w} \times (e^{jw})$ $\frac{Y(ejw)}{Y(ejw)} = \frac{1}{6} + \frac{1}{3} e^{-\frac{1}{3}2w} + \frac{1}{6} e^{-\frac{1}{3}2w} \cdot \frac{1}{6}$ $\frac{Y(ejw)}{Y(ejw)} = \frac{1}{6} + \frac{1}{3} e^{-\frac{1}{3}2w} + \frac{1}{6} e^{-\frac{1}{3}2w} \cdot \frac{1}{6}$

 $H(eiw) = 4 + 1 (\cos w - j \sin w) + \frac{1}{6} (\cos 2w - j \sin 2w)$

 $H(e^{i\omega}) = \left(\frac{1}{6} + \frac{1}{3}\cos\omega + \frac{1}{6}\cos2\omega\right) - \frac{1}{3}\left(\frac{1}{3}\sin\omega + \frac{1}{6}\cos2\omega\right)$

[H(eio)] = (1/6+1/3cosus+1/6cosus)2+(+ sincu+ + sincu)2

 $LH(e^{i\omega}) = \frac{180^{\circ} - \tan^{2} \int_{6}^{6} \frac{1}{3} \cos \omega + \frac{1}{6} \cos \omega}{\frac{1}{6} + \frac{1}{3} \cos \omega + \frac{1}{6} \cos 2\omega}$

- Q.7 (a)
- (ii) A filter is to be designed with the following desired frequency response using rectangular window:

$$H_d(e^{j\omega}) = \begin{cases} 0, & -\pi/4 \le \omega \le \pi/4 \\ e^{-j2\omega}, & \pi/4 \le |\omega| \le \pi \end{cases}$$

Determine the filter coefficients $h_d(n)$ if the window function is defined as

$$w(n) = \begin{cases} 1, & 0 \le n \le 4 \\ 0, & \text{otherwise} \end{cases}$$

Also, determine the frequency response $H(e^{i\omega})$ of the designed filter.

$$H(n) = \frac{1}{2\pi} \int_{-\pi}^{\pi} H(e^{j\omega}) \cdot e^{j\omega n} d\omega$$

$$H(n) = \frac{1}{2\pi} \int_{-\pi}^{\pi} e^{-j2\omega} e^{j\omega n} d\omega$$

$$h(n) = \frac{1}{2\pi} \int_{-\pi}^{\pi} e^{j(n-2)\omega} d\omega$$

$$h(n) = \frac{1}{2\pi} \int_{-\pi}^{\pi} e^{j(n-2)\omega} d\omega$$

$$h(n) = \frac{1}{2\pi} \int_{-\pi}^{\pi} e^{j(n-2)\omega} d\omega$$

$$h(n) = \frac{1}{2\pi} \int_{-\pi}^{\pi} e^{j(n-2)\pi} e^{j(n-2)\pi/4} \int_{-\pi}^{\pi} e^{j(n-2)\pi/4}$$

$$h(n) = \frac{1}{(n-2)\pi} \int_{-\pi}^{\pi} e^{j(n-2)\pi/4} e^{j(n-2)\pi/4} \int_{-\pi}^{\pi} e^{j(n-2)\pi/4}$$


$$h(n) = \frac{1}{(n-2)\pi} \int_{-\pi}^{\pi} e^{j(n-2)\pi/4} e^{j(n-2)\pi/4} \int_{-\pi}^{\pi} e^{j(n-2)\pi/4} \int_{-\pi}^{\pi$$

2.7(b)

Soli

Do not write in this margin

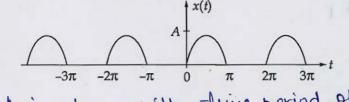Find the exponential Fourier series for the half wave rectified sine wave shown in figure.



$$\chi(t) = A \sin \alpha t \qquad \text{with -line period of } 2\pi \qquad \text{[20 marks]}$$

$$C_n = \frac{1}{T} \int_{0}^{\infty} \chi(t) \cdot e^{-\int_{0}^{\infty} n \, \omega t} \, dt \cdot \frac{1}{T_0} = 1 \cos d.$$

$$Cn = A \int_{2\pi}^{\pi} \left\{ \frac{e^{i(t-n)t} - e^{-i(t+n)t}}{2} \right\} dt \cdot As \cdot wo=1$$

$$Cn = \frac{A}{2\pi} \int_{0}^{\pi} \left\{ \frac{e^{j(n-n)t} - e^{-j(n+n)t}}{2^{j}} \right\} dt$$

$$Cn = \frac{A}{4\pi i} \left[\frac{e^{j(n-n)t}}{4^{j}(n-n)} + \frac{e^{j(n+n)t}}{j(n+n)} \right]_{0}^{\pi}$$

$$Cn = \frac{A}{4\pi i} \left[\frac{e^{i(1-n)\pi}}{i(1-n)} + \frac{e^{i(1+n)\pi}}{i(1+n)} \right]$$

$$-\left(\frac{1}{(1+n)} + \frac{1}{(1+n)}\right)$$

$$C_{n} = \frac{4\pi}{4\pi j^{n}j} \left[\frac{\cos(1-n)\pi}{(1-n)} + \frac{\cos(1+n)\pi}{(1+n)} - \left(\frac{2}{1-n^{2}}\right) \right]$$

$$C_{n} = -\frac{A}{4\pi} \left[\frac{\cos(\pi - \pi n)}{(1-n)} + \frac{\cos(\pi + \pi n)}{(1+n)} - \frac{2}{1-n^{2}} \right]$$


$$\frac{Cn = -\frac{A}{4\pi} \left[-\frac{Cos(\pi n)}{1-n} + -\frac{Cos(\pi n)}{1-n^2} \right]}{1-n^2}$$

$$C_{n} = -\frac{A}{4\pi} \left[-(-1)^{n} + \frac{1}{1+n} \right] - \frac{2}{(1-n^{2})}$$

$$c_{n} = \frac{1}{4\pi} \left[\frac{2}{(1-n^{2})} ^{2} \right] \cdot \left[\frac{1}{(1-n^{2})} \right]$$

$$Cn = \frac{A}{2\pi(+n^2)} \left\{ (1-6(-1)^n) \right\}$$

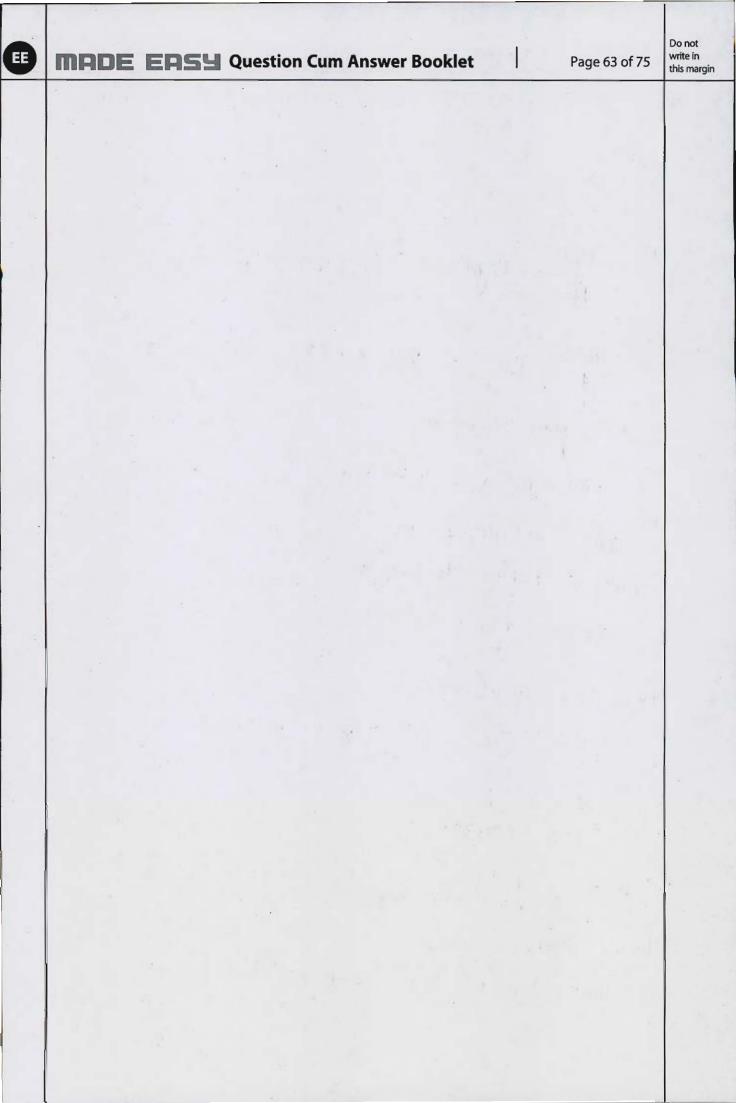Hence,
$$\infty$$
 $\chi(t) = \sum_{n=0}^{\infty} \frac{A}{\chi(1-n^2)}$ eint.



- Q.7 (c)
- (i) The output y(t) of a causal LTI system is related to the input x(t) by the equation

$$\frac{dy(t)}{dt} + 10y(t) = \int_{-\infty}^{\infty} x(\tau)z(t-\tau)d\tau - x(t)$$

where, $z(t) = e^{-t}u(t) + \delta(t)$.

Determine the impulse response of the system.

[10 marks]

Sol

$$\frac{dy(t)}{dt} + 10y(t) = \int_{-\infty}^{\infty} \chi(z) \chi(t-z) dz - \chi(t)$$

Taking Laplace transform

$$\chi(t) = e^{-t}u(t) + S(t)$$


Taky it Laplace transform.

$$Z(s) = \frac{1}{S+1} + 1 = \frac{S+2}{S+1}$$

Now using equation

$$Y(S) (S+10) = \left(\frac{S+2}{S+1}\right) \times (S) - \times (S)$$

Taking waverse laplace

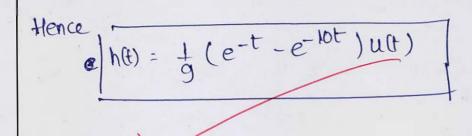



Good Approach

[10 marks]

- Q.7 (c)
- (ii) Convert the analog filter with system transfer function $H(s) = \frac{s+0.1}{(s+0.1)^2+9}$ into a digital IIR filter using bilinear transformation. The digital filter should have a resonant frequency of $\frac{\pi}{4}$.

solc) ii Given
$$w = \pi_4$$
 radisec
 $\Omega = 0$ Bradisec

$$\Omega = \frac{2}{T_c} \tan\left(\frac{\omega}{2}\right) = \frac{2}{3}$$

$$-334 = \frac{2}{Ts} + an(\frac{x}{8})$$
. $T_s = 0.092$ ALC.

$$H(s) = \frac{s + 0.1}{s^2 + 0.01 + 0.2s + 9}$$

$$H(s) = \frac{8+0.1}{s^2+0.2s+9.01}$$

$$H(s) = \frac{8+0.1}{s^2+0.2s+9.01}$$
 where $s = \frac{2}{Ts} \left[\frac{2-z}{z+1} \right]$

$$H(s) = \frac{7.24 \left[\frac{Z-1}{Z+1}\right] + 0.1}{\left(\frac{Z-1}{Z+1}\right)^{2} + 0.2 \times 7.24 \left(\frac{Z-1}{Z+1}\right)^{2} + 9.01}$$

$$H(Z) = \frac{7.24(Z+1)(Z+1)}{(7.24)^2(Z-1)^2} + 0.1(Z+1)^2$$

$$H(E) = \frac{4 \cdot 24}{(x^2 - 1)} + 0.1(x^2 + 2x + 1)$$

$$(7.24)^2(x^2 - 2x + 1) + 1.44(x^2 - 1) + 9.01(x^2 + 1x + 1)$$

$$H(z) = \frac{7.84z^2 + 0.2z - 7.14}{62.8676 z^2 - 86.815Z + 59.99}$$


$$H(z) = \frac{0.12 + 8.18 \times 10^{-3} z + -0.11 z^{-2}}{1 - 1.38 z + 0.95 z^{-2}}$$

$$H(z) = 0.12 \pm 0.0032z^{-1} - 0.11z^{-2}$$
 $1 - 1.38z^{-1} + 0.95z^{-2}$




Q.8 (a)

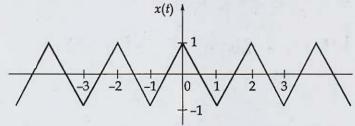(i) Write down the exponential Fourier series representation of the signal x(t).



(ii) Find the amount of power (in mW) contained in the 7^{th} harmonic of the Fourier series representation of x(t).

[10 + 10 marks]

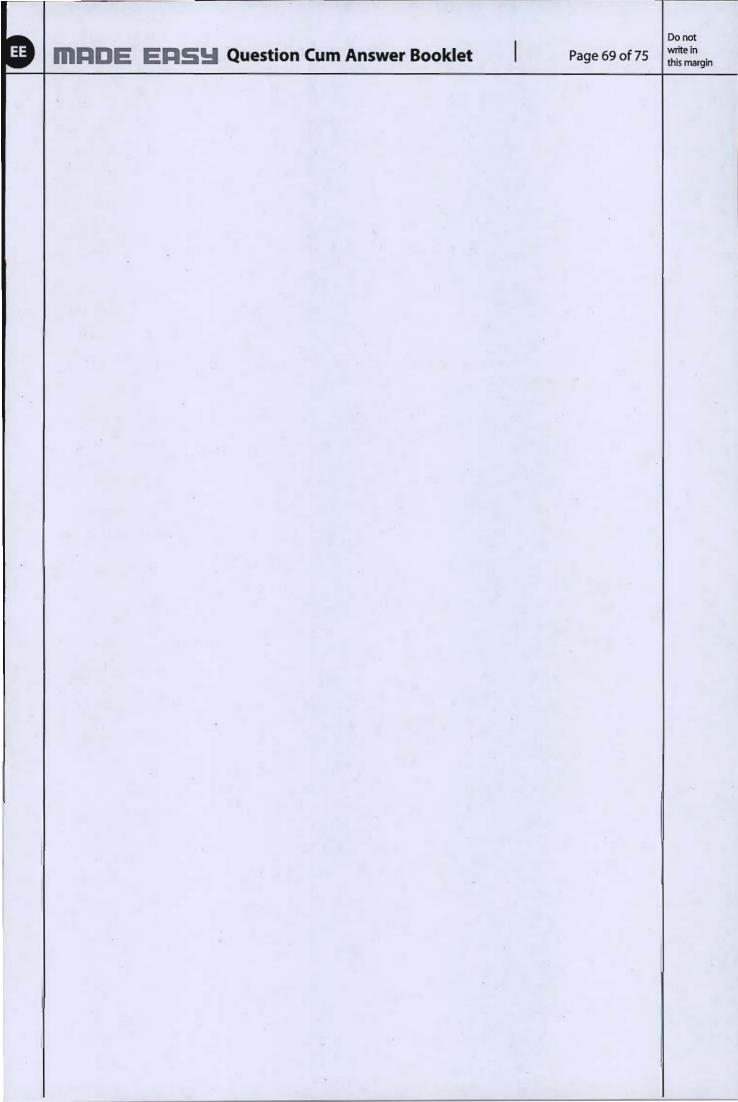



MADE EASY Question Cum Answer Booklet

Page 70 of 75

Do not write in this ma .8 (b)

Let $g(t) = x(t)\cos^2 t * \frac{\sin t}{\pi t}$, where * is convolution. Assuming that x(t) is real and $X(\omega) = 0$ for $|\omega| \ge 1$, show that there exists an LTI system 'S' such that $x(t) \longrightarrow S \longrightarrow g(t)$

[20 marks]

8 (c) Determine the values of P_x and E_x for each of the following signals:

(i)
$$x_1(t) = e^{j(2t + \pi/4)}$$

(ii)
$$x_2(n) = \left(\frac{1}{2}\right)^n u(n)$$

(iii)
$$x_3(n) = e^{j\left(\frac{\pi}{2}n + \frac{\pi}{8}\right)}$$

(iv)
$$x_4(n) = \cos\left(\frac{n\pi}{4}\right)$$

(Where P_x = Power and E_x = Energy)

[20 marks]

Do no write in this m

Do not write in this margin MADE EASY Question Cum Answer Booklet Page 75 of 75 0000