



# **ESE 2026**

## **Prelims Solutions**

**Electrical  
Engineering**

**SET-B**

**Exam held on 08-02-2026**

**MADE EASY Corporate Office:**

44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016

**Centres : Delhi, Hyderabad, Jaipur, Bhopal, Pune | [www.madeeasy.in](http://www.madeeasy.in) | Ph: 9021300500**



**ELECTRICAL ENGINEERING**  
**Paper Analysis of ESE 2026**  
**Preliminary Examination**

Sl.	Subjects	Number of Questions
1.	Electric Circuits	10
2.	Electrical Machines	17
3.	Power Systems	11
4.	Digital Electronics	4
5.	Power Electronics	12
6.	Measurement	12
7.	Analog Electronics	18
8.	Electromagnetic Theory	2
9.	Microprocessor	4
10.	Communication System	5
11.	Control Systems	12
12.	Signals & Systems	12
13.	Electrical Materials	12
14.	Computer Fundamentals	8
15.	Engineering Mathematics	11

**Click to Watch**


**UPSC ESE Prelims 2026**

**ELECTRICAL ENGINEERING Solutions**

by **MADE EASY** faculties



Ans. (d)

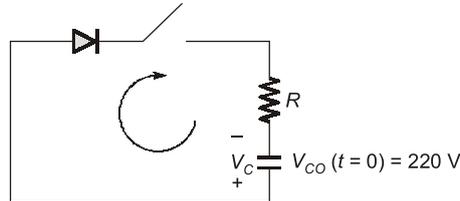

$$\frac{1}{2}CV_{Co}^2 = I^2Rt \quad (\text{energy balance})$$

$$\therefore \frac{1}{2}CV_{Co}^2 = \frac{1}{2} \times (0.1 \times 10^{-6}) (220)^2 = 2.42 \text{ mJ}$$

End of Solution

Q.5 Which of the following is not a limitation of MOSFET?

- (a) High on-state drop, as high as 10 V.
- (b) Unipolar voltage device.
- (c) Slower switching speed.
- (d) Lower off-state voltage capability.

Ans. (b)

MOSFET is unipolar device.

$\therefore$  Conduction is only due to majority carriers only which leads to fast switching frequency.


$\therefore$  This is an Advantage (Not a limitation).

End of Solution

Q.6 Two BJTs are connected in parallel to share the total current 25 A. The collector-to-emitter voltage of  $T_1$  and  $T_2$  are 1.5 V and 1.75 V respectively. What is the difference in emitter current sharing by the two transistors, when the current-sharing series resistances are  $R_{E1} = 0.25 \Omega$  and  $R_{E2} = 0.35 \Omega$ ?

- (a) 0.5 A
- (b) 5 A
- (c) 0.25 A
- (d) 2.5 A

Ans. (b)

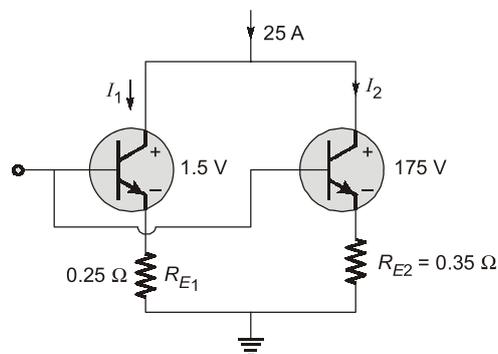





GET UPTO

**100%**

**SCHOLARSHIP**

# NATIONAL SCHOLARSHIP TEST **NST-2**



Scan to register

Test Mode : **Online**

Last date to Register :

**20 FEB**

Test Date :

**22 FEB**

For details, visit : [nst.madeeasy.in](http://nst.madeeasy.in)

## For **ESE 2027** & **GATE 2027**

### Offline Batches

Delhi	19 Feb & 5 Mar 2026
Bhopal	19 Feb & 16 Mar 2026
Jaipur	9 Mar 2026
Hyderabad	20 Feb & 19 Mar 2026
Pune	26 Feb 2026

### Live-Online Batches

20 Feb 2026 &  
11 Mar 2026

**Admissions Open**  
More Batches to be  
announced soon.



**Delhi**

Ph : 9021300500

**Hyderabad**

Ph : 9440695415

**Bhopal**

Ph : 7290068507

**Jaipur**

Ph : 7290068512

**Pune**


Ph : 7290068508

Web : [www.madeeasy.in](http://www.madeeasy.in)

Helpline : 9021300500

- Q.8** The firing frequency of relaxation oscillator is varied by changing the value of charging resistance  $R$ . What are the maximum and minimum values of  $R$ ? (Assume  $\eta = 0.65$ ,  $I_P = 0.65$  mA,  $V_P = 12$  V,  $I_V = 2.0$  mA,  $V_V = 1.5$  V,  $V_{BB} = 20$  V and  $C = 0.047$   $\mu$ F.)
- (a)  $R_{\min} = 9.25$  k $\Omega$  and  $R_{\max} = 12.3076$  k $\Omega$   
 (b)  $R_{\min} = 835$  k $\Omega$  and  $R_{\max} = 4.5$  k $\Omega$   
 (c)  $R_{\min} = 425$  k $\Omega$  and  $R_{\max} = 18.2469$  k $\Omega$   
 (d)  $R_{\min} = 11.86$  k $\Omega$  and  $R_{\max} = 19.2751$  k $\Omega$

Ans. (a)

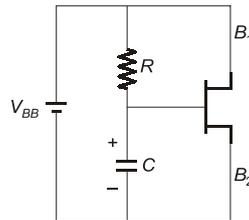

When UJT  $\rightarrow$  OFF, capacitor charges till peak point voltage.

$$\therefore V_{BB} \geq I_P R + V_P$$

$$\therefore R \leq \frac{V_{BB} - V_P}{I_P}$$

$$\therefore R_{\max} = \frac{V_{BB} - V_P}{I_P} = \frac{20 - 12}{0.65 \times 10^{-3}} = 12.3 \text{ k}\Omega$$

When UJT  $\rightarrow$  ON, capacitor discharges till valley voltage.

$$\therefore V_{BB} \leq I_V R + V_V$$

$$\therefore R \geq \frac{V_{BB} - V_V}{I_V}$$

$$\therefore R_{\min} = \frac{V_{BB} - V_V}{I_V} = \frac{20 - 1.5}{2 \times 10^{-3}} = 9.25 \text{ k}\Omega$$

End of Solution

- Q.9** The capacitance ( $C_{J2}$ ) value of reverse-biased junction  $J2$  of a thyristor is independent of off-state voltage. The limit value of the charging current to turn the thyristor is about 15 mA. If the critical value of  $dv/dt$  is 750 V/ $\mu$ s, what is the value of the junction capacitance ( $C_{J2}$ )?

- (a) 200 pF (b) 200  $\mu$ F  
 (c) 50 pF (d) 50  $\mu$ F

Ans. (c)

$$I_C = C \cdot \frac{dv}{dt}$$

$$C = \frac{I_C}{dv/dt} = \frac{15 \cdot 10^{-3}}{750 \text{ V}/\mu\text{s}} = 20 \text{ pF}$$

$$C = 50 \text{ pF (nearest)}$$

End of Solution

**Q.10** A single-phase, half-wave controlled rectifier with  $R$  load is supplied from a 230 V, 50 Hz AC source. When the average DC output voltage is 50% of maximum possible average DC output voltage, what are the firing angle of thyristor and average DC output voltage respectively?

- (a)  $45^\circ$  and 37.32 V (b)  $90^\circ$  and 36.61 V  
(c)  $90^\circ$  and 51.78 V (d)  $45^\circ$  and 26.39 V

Ans. (c)

$$V_0 = \frac{V_m}{2\pi}(1 + \cos\alpha) \text{ and } (V_0)_{\max} = \frac{V_m}{\pi}$$

Given:  $V_0 = 50\%$  of  $(V_0)_{\max}$

$$V_0 = \frac{V_m}{2\pi} = \frac{V_m}{2\pi}(1 + \cos\alpha)$$

$\therefore \alpha = 90^\circ$

$$V_0 = \frac{V_m}{2\pi} = \frac{230\sqrt{2}}{2\pi} = 51.77 \text{ V}$$

End of Solution

**Q.11** A single-phase semi-converter is supplied by 200 V, 50 Hz and it is connected with an R-L-E load, where  $R = 15 \Omega$ ,  $E = 80 \text{ V}$  and  $L$  is very large such that the load current is ripple-free. What is the average output current at  $\alpha = 90^\circ$ ?

- (a) 5.58 A (b) 3.95 A  
(c) 0.66 A (d) 0.24 A

Ans. (c)

1- $\phi$  semi converter fed RLE load

$$V_0 = \frac{V_m}{\pi}(1 + \cos\alpha) = E + IR$$

$$\frac{200\sqrt{2}}{\pi}(1 + \cos 90) = 80 + I \times 15$$

$$90.03 \text{ V} = 80 + I \times 15$$


$$I = \frac{90.03 - 80}{15} = 0.668 \text{ A}$$

End of Solution

**Q.12** A step-down chopper has a load resistance of  $20 \Omega$  and input DC voltage is 200 V. When the chopper switch is ON, the voltage across load switches to 2 V. If the chopping frequency is 1.5 kHz and duty ratio is 40%, what is the average DC output voltage?

- (a) 40 V (b) 80 V  
(c) 39.6 V (d) 174.4 V

Ans. (b)

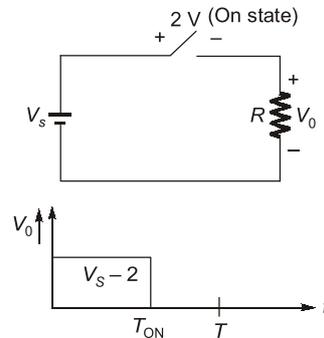

$$V_0 = (V_s - 2) \frac{T_{ON}}{T} = (200 - 2) \times 0.4 = 79.2 \text{ V}$$

$$V_0 \approx 80 \text{ V}$$

End of Solution

Q.13 What is the expression for distortion factor (DF) in inverters?

(a)  $DF = \frac{\left[ \sum_{n=2,3,4,5,\dots}^{\infty} \left( \frac{V_n}{n^2} \right)^2 \right]^{1/2}}{V_1}$

(b)  $DF = \frac{\left[ \sum_{n=2,3,4,5,\dots}^{\infty} \left( \frac{V_n}{n^2} \right) \right]^{1/2}}{V_1}$

(c)  $DF = \frac{\left[ \sum_{n=2,3,4,5,\dots}^{\infty} \left( \frac{V_n}{n} \right)^2 \right]^{1/2}}{V_1}$

(d)  $DF = \frac{\left[ \sum_{n=2,3,4,5,\dots}^{\infty} \left( \frac{V_n}{n} \right) \right]^{1/2}}{V_1}$

Ans. (c)

$$\text{Distortion factor} = \frac{\sqrt{\sum_{n=2,3,4,\dots}^{\infty} \left( \frac{V_n}{n} \right)^2}}{V_1}$$

End of Solution

Q.14 A separately excited DC motor is controlled by a single-phase full converter which is supplied from 440 V, 50 Hz AC supply. If the field circuit is fed through a single-phase half converter with  $0^\circ$  firing angle, the delay angle of armature converter is  $30^\circ$  and load current is 20 A, what is the field current? Assume that the armature resistance  $R_a = 0.5 \Omega$ , the field resistance  $R_f = 140 \Omega$ , and the current waveform is ripple-free.

(a) 2.83 A

(b) 20 A

(c) 20.19

(d) 0.79 A



**Q.17** The total iron losses in the armature of a DC machine running at 875 rpm are 1100 W. What is the approximate braking torque due to iron losses?

- (a) 8 N-m (b) 16.42 N-m  
(c) 8.85 N-m (d) 12 N-m

Ans. (d)

$$T = \frac{1100}{\frac{2\pi \times 875}{60}} = \frac{1100 \times 60}{2\pi \times 875} = 12 \text{ Nm}$$

End of Solution

**Q.18** A 0.5 hp, 6-pole induction motor is excited by a 3-phase, 60 Hz source. If the full-load speed is 1140 rpm, what is the percentage of slip?

- (a) 6% (b) 12%  
(c) 5% (d) 3%

Ans. (c)

$$P = 60$$

$$F = 60 \text{ Hz}$$

$$N_s = \frac{120 \times 60}{6} = 1200 \text{ rpm}$$

Given, Speed = 1140 rpm

$$\% \text{ speed} = \frac{N_s - N}{N_s} \times 100 = \frac{1200 - 1140}{1200} \times 100$$

$$= 5\%$$

End of Solution

**Q.19** A 50 Hz induction motor wound for pole-amplitude modulation has 20 initial poles and the modulating function has 8 poles. At what two speeds will the motor run?

- (a) 300 rpm and 214.286 rpm (b) 400 rpm and 318.524 rpm  
(c) 150 rpm and 414.495 rpm (d) 450 rpm and 115.359 rpm

Ans. (a)

$$P_1 = 20$$

$$P = P_i \pm P_m$$

$$P = 20 \pm 8$$

$$N_s = \frac{120 \times 50}{20} = 300 \text{ rpm}$$

$$P_1 = 12, \quad N_s = \frac{120 \times 50}{12} = 500 \text{ rpm}$$

$$P_2 = 28, \quad N_s = \frac{120 \times 50}{28} = 214.286 \text{ rpm}$$

End of Solution



# Detailed Solutions of ESE 2026 Preliminary Exam | Set-B

## Electrical Engineering

Exam Date  
08-02-2026

- Q.20** A 3-phase synchronous generator produces an open-circuit line voltage of 6928 V, when the DC exciting current is 50 A. The AC terminals are then short-circuited and the three line currents are found to be 800 A. What is the synchronous reactance per phase?
- (a) 138.5  $\Omega$  (b) 8.6  $\Omega$   
(c) 80  $\Omega$  (d) 5  $\Omega$

**Ans. (d)**

$$(X_s)_{ph} = \frac{6928 / \sqrt{3}}{800} = \frac{8.66}{\sqrt{3}} = 5 \Omega/\text{Phase}$$

End of Solution

- Q.21** Consider the following advantages of hydrogen cooling of alternators in steam power generation:
1. Less noise due to the lower density of hydrogen
  2. Ventilation losses (fan power absorbed) are higher by 10%
  3. The heat transfer is more than that of air.
- Which of the above advantages is/are correct?
- (a) 2 and 3 (b) 2 only  
(c) 1 only (d) 1 and 3

**Ans. (d)**

Large size generation uses hydrogen as cooling medium which has

1. Low density causes has noise.
3. Better heat transfer.

**Alternate Solution:**

Hydrogen density is  $\frac{1}{14}$ <sup>th</sup> of air. So, less windage or friction loss. So results in much quieter operation. Hydrogen thermal conductivity is very high.

End of Solution

- Q.22** Match the following lists regarding Surge Impedance loading (SIL) of AC lines:

**List-I (Conductor configuration and line voltage)**      **List-II [(SIL (MW))]**

- |                                    |               |
|------------------------------------|---------------|
| <b>P.</b> Quad Bersimis - 400 kV   | <b>1.</b> 647 |
| <b>Q.</b> Twin Moose - 400 kV      | <b>2.</b> 605 |
| <b>R.</b> Quad Zebra - 400 kV      | <b>3.</b> 691 |
| <b>S.</b> Triple Snowbird - 400 kV | <b>4.</b> 515 |

Select the correct answer using the code given below.

- |     | <b>P</b> | <b>Q</b> | <b>R</b> | <b>S</b> |
|-----|----------|----------|----------|----------|
| (a) | 3        | 4        | 1        | 2        |
| (b) | 2        | 1        | 4        | 3        |
| (c) | 1        | 4        | 2        | 3        |
| (d) | 4        | 3        | 2        | 1        |

Ans. (a)

$$SIL = \frac{V^2}{Z_s}$$

Quad bundle has less resistance compared to triple and twin.

End of Solution

**Q.23** If  $d$  is the distance between the conductors and  $e$  is Euler's number, then the maximum critical disruptive voltage occurs when the radius ( $r$ ) of the conductors is:

- (a)  $d \times e$  (b)  $d/(1 - e)$   
(c)  $d/e$  (d)  $d/(1 + e)$

Ans. (c)

In corona disruptive voltage,

$$V_c = m_o g r \delta \ln\left(\frac{d}{r}\right)$$

For maximum,  $V_c \Rightarrow \frac{d}{r} = e \Rightarrow r = \left(\frac{d}{e}\right)$

End of Solution

**Q.24** Match the following Lists regarding cable conductors:

**List-I (Property)**

**List-II (Value)**

- |  |                                 |
|--|---------------------------------|
| <b>P.</b> Specific gravity of copper             | <b>1.</b> 15 kg/mm <sup>2</sup> |
| <b>Q.</b> Ultimate tensile strength of copper    | <b>2.</b> 8.890                 |
| <b>R.</b> Specific gravity of aluminium          | <b>3.</b> 40 kg/mm <sup>2</sup> |
| <b>S.</b> Ultimate tensile strength of aluminium | <b>4.</b> 2.71                  |

Select the correct answer using the code given below.

- |     | <b>P</b> | <b>Q</b> | <b>R</b> | <b>S</b> |
|-----|----------|----------|----------|----------|
| (a) | 3        | 4        | 1        | 2        |
| (b) | 2        | 3        | 4        | 1        |
| (c) | 1        | 3        | 4        | 2        |
| (d) | 4        | 1        | 2        | 3        |

Ans. (b)

Copper is much denser and has higher mechanical strength than Aluminium.

- |  |                                 |
|--|---------------------------------|
| <b>P.</b> Specific gravity of copper             | <b>2.</b> 8.890                 |
| <b>Q.</b> Ultimate tensile strength of copper    | <b>3.</b> 40 kg/mm <sup>2</sup> |
| <b>R.</b> Specific gravity of aluminium          | <b>4.</b> 2.71                  |
| <b>S.</b> Ultimate tensile strength of aluminium | <b>1.</b> 15 kg/mm <sup>2</sup> |

End of Solution





Peak to peak input voltage =  $2V_m = 0.398 \text{ V}$

End of Solution


- Q.31** The signal space should be divided as
- periodic only, whereas the system should be either time scaling or shifting.
  - non-periodic only, whereas the system should be either time shifting.
  - either periodic or non-periodic, whereas the system should be either time scaling or shifting.
  - neither periodic nor non-periodic, whereas the system should be time scaling.

**Ans. (c)**

The signal space can either be periodic or non-periodic and the system should be capable of either time scaling or shifting.

End of Solution

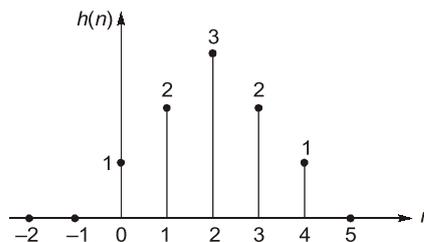- Q.32** Consider a non-recursive filter with the impulse response  $h(n]$  shown in the figure:




What is the group delay in terms of frequency?

- 1
- 2
- 3
- 4

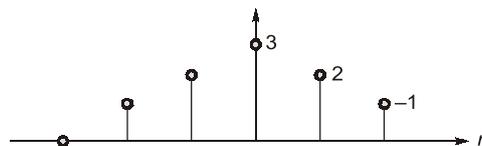**Ans. (b)**

Let

$$h_1(n) = \text{real and even} \iff H_1(e^{j\omega}) = \text{real and even}$$



So,

$$\angle H_1(e^{j\omega}) = 0^\circ$$

Now,

$$h(n) = h_1(n - 2)$$

$$H(e^{j\omega}) = H_1(e^{j\omega}) \times e^{-j2\omega}$$

So,

$$\begin{aligned} \angle H(e^{j\omega}) &\simeq \angle H_1(e^{j\omega}) + (-2\omega) \\ &= 0 - 2\omega = -2\omega \end{aligned}$$

Now, group delay of system

$$\tau_g = -\frac{d\angle H(e^{j\omega})}{d\omega} = -\frac{d}{d\omega}(-2\omega) = 2$$

End of Solution



Announcing

# Classroom Courses & Live-Online Courses for

**GATE  
2027**

**ESE  
2027**

## Salient Features :

- ✓ Classes by experienced & renowned faculties.
- ✓ Systematic subject sequence & timely completion.
- ✓ Comprehensive & updated books (Optional).
- ✓ Efficient teaching with comprehensive coverage.
- ✓ Regular performance assessment through class tests.
- ✓ Facility for doubt removal.
- ✓ Concept practice through workbook solving.
- ✓ Exam oriented learning ecosystem.
- ✓ Proper notes making & study concentration.
- ✓ Similar teaching pedagogy in offline & online classes.



**Classroom Courses  
at Delhi**

**19 Feb 2026 &  
05 Mar 2026**



**Live-Online  
Courses**

**20 Feb 2026 &  
11 Mar 2026**



Scan to enroll

**Streams:** CE, ME/PI, EE, EC/IN, CS

**Admissions Open | More batches to be announced in Apr, May & June**

**Delhi Centre :** 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

**MADE EASY Centres :** Delhi | Bhopal | Hyderabad | Jaipur | Pune [www.madeeasy.in](http://www.madeeasy.in)



**Q.35** If  $x(n) = \{\dots, 0, 0, 1, 1, 1, 1, 1, 1, 0, 0, \dots\}$  what is the value of  $y(n) = x(2n)$ ?

- (a)  $y(n) = x(2n) + x(n)$                       (b)  $y(n) = u(n) - u(n-7)$   
(c)  $y(n) = u(n) - u(n-4)$                       (d)  $y(n) = x(n) - x(n-7)$

**Ans. (c)**

$$x(n) = \{0, 1, 1, 1, 1, 1, 1, 0, 0\}$$

$$y(n) = x(2n) = \{1, 1, 1, 1\} = u(n) - u(n-4)$$

End of Solution

**Q.36** Consider a finite-duration sequence such as  $x(n) = \{1, 2, 4, 8, 16\}$ . What is the new

sequence produced, when it revolves 4 units in the circular shift operation?

- (a)  $\{4, 8, 16, 1, 2\}$                       (b)  $\{2, 4, 8, 16, 1\}$   
(c)  $\{1, 2, 4, 8, 16\}$                       (d)  $\{16, 1, 2, 4, 8\}$

**Ans. (b, d)**

$$x(n) = \{1, 2, 4, 8, 16\}$$

Circular right-shifting by '4'

$$x(n-4) \Big|_{\text{mod } 5} = \{2, 4, 8, 16, 1\}$$

Circular left-shifting by '4'

$$x(n+4) \Big|_{\text{mod } 5} = \{16, 1, 2, 4, 8\}$$

End of Solution

**Q.37** What is the linear convolution response  $y(5)$  of the given sequence?

$$x(n) = \begin{cases} \frac{2}{\sqrt{3}} \sin\left(\frac{\pi n}{3}\right), & 0 \leq n \leq 5 \\ 0, & \text{elsewhere} \end{cases} \quad \text{and } h(n) = \{1, 2, 3, 2, 1\}$$

- (a) 0                      (b) 9  
(c) 14                      (d) 28

Ans. (a)

$$x(n) = \{0, 1, 1, 0, -1, -1\}$$

↑

$$h(n) = \{1, 2, 3, 2, 1\}$$

↑

Tabular method:

$h(n) \backslash x(n)$	0	1	1	0	-1	-1
1	0	1	1	0	-1	-1
2	0	2	2	0	-2	-2
3	0	3	3	0	-3	-3
2	0	2	2	0	-2	-2
1	0	1	1	0	-1	-1

$$y(n) = \{0, 1, 3, 5, 4, 0, -4, -5, -3, -1\}$$

↑

$$y(n) = 0$$

End of Solution

**Q.38** By using the 3-point DFT of the sequence  $h(n) = a^{-n}$ ,  $0 \leq n \leq 2$ , for  $a = 1.369$ , what is the relationship between the output sequence?

- (a)  $H(0) + H(1) + H(2) = 4$                       (b)  $H(0) + H(1) = H(2)$   
 (c)  $H(1) = H(2)$                                       (d)  $H(2) = H^*(1)$

Ans. (d)

$$h(n) = \{1, a^{-1}, a^{-2}\}, \text{ where } a = 1.369, N = 3$$

↑

$\therefore h(n)$  is real signal

$\therefore H(k)$  will be conjugate symmetric signal

i.e.,  $H(k) = H^*(N-k)$

$$\downarrow K = 1, N = 3$$

$$H(1) = H^*(2)$$

or  $H(2) = H^*(1)$

End of Solution

**Q.39** If  $X(s) = L\{x(t)\}$ , what is the initial value  $x(0)$  and the final value  $x(\infty)$  respectively, for

the given signal  $X(s) = \frac{7s+6}{s(3s+5)}$ , using initial value and final value theorems?

- (a)  $\frac{6}{5}, \frac{7}{3}$     (b)  $2, \frac{7}{3}$   
 (c)  $\frac{7}{3}, 2$     (d)  $\frac{7}{3}, \frac{6}{5}$

Ans. (d)

Given,

$$X(s) = \frac{7s+6}{s(3s+5)}$$

$$x(0) = \lim_{s \rightarrow \infty} [sX(s)] = \lim_{s \rightarrow \infty} \frac{7s^2}{3s^2} = \frac{7}{3}$$

$$x(\infty) = \lim_{s \rightarrow 0} [sX(s)] = \lim_{s \rightarrow 0} \frac{s(7s+6)}{s(3s+5)}$$

$$= \lim_{s \rightarrow 0} \frac{7s+6}{3s+5} = \frac{6}{5}$$

End of Solution

**Q.40** If  $X(s) = \mathcal{L}\{x(t)\}$ , what is the inverse Laplace transform of the signal  $X(s) = \frac{2}{s(s+1)(s+2)^2}$ ?

- (a)  $x(t) = (0.5 - 2e^{-t} + te^{-2t} + 1.5e^{-2t})u(t)$   
 (b)  $x(t) = (0.5 - 2e^{-t} + te^{-2t} + 2e^{-2t})u(t)$   
 (c)  $x(t) = (0.5 - e^{-t} + te^{-2t} + 2e^{-2t})u(t)$   
 (d)  $x(t) = (1 - e^{-t} + te^{-2t})u(t)$

Ans. (a)

$$X(s) = \frac{2}{s(s+1)(s+2)^2}$$

$$= \frac{A}{s} + \frac{B}{s+1} + \frac{C}{s+2} + \frac{D}{(s+2)^2}$$

$$= \frac{1}{2} \cdot \frac{1}{2} - 2 \cdot \frac{1}{s+1} + 1.5 \cdot \left( \frac{1}{s+1} \right) + \frac{1}{(s+2)^2}$$

$$x(t) = 0.5u(t) - 2e^{-t}u(t) + 1.5e^{-2t}u(t) + te^{-2t}u(t)$$

$$= (0.5 - 2e^{-t} + 1.5e^{-2t} + te^{-2t})u(t)$$

End of Solution

**Q.41** What is the DC gain (zero frequency) for a system which has a transfer function of  $G(s) = \frac{s+2}{(s+1)(s+3)(s+4)}$ ?

- (a)  $\frac{1}{6}$  (b)  $\frac{2}{3}$   
 (c)  $\frac{1}{3}$  (d)  $\frac{1}{2}$

Ans. (a)

$$\text{DC gain} = G(s)|_{s=0} = \frac{s+2}{(s+1)(s+3)(s+4)} \Big|_{s=0}$$

$$= \frac{2}{3 \times 4} = \frac{1}{6}$$

End of Solution





**Q.47** An inverting amplifier using the 741C must have a flat response up to 40 kHz. The gain of the amplifier is 10. What maximum peak-to-peak input signal can be applied without distorting the output?

- (a) 0.398 V (b) 3.98 V  
(c) 30.98 V (d) 0.0398 V

**Ans. (a)**

Assume SR = 0.5 V/μs

$$\frac{A_{CL} V_m \omega_o}{10^6} \leq SR$$

$$V_m = \frac{SR \times 10^6}{A_{CL} \omega_o} = \frac{0.5 \times 10^6}{10 \times 2\pi \times 40 \times 10^3} = 0.199 \text{ V}$$

Peak to peak input voltage,  
=  $2V_m = 0.398 \text{ V}$

End of Solution

**Q.48** Consider the following statements regarding bistable multivibrator:

1. The bistable multivibrator is used as memory elements in shift registers, counters.
2. It is used to generate sine wave by sending regular triggering pulse to the input.
3. It can also be used as a frequency divider.

Which of the above statements is/are correct?

- (a) 1 and 3 (b) 3 only  
(c) 2 only (d) 1 and 2

**Ans. (a)**

Multivibrators are switching circuits, they produce square/rectangular waves, not sine wave.

End of Solution

**Q.49** What is the percentage of resolution of the eight-bit DAC?

- (a) 0.0244% (b) 0.392%  
(c) 0.568% (d) 0.0148%

**Ans. (b)**

$$\begin{aligned} \% \text{resolution} &= \frac{1}{2^n - 1} \times 100 \\ &= \frac{1}{2^8 - 1} \times 100 = \frac{100}{255} = 0.392\% \end{aligned}$$

End of Solution

**Q.50** What is the value of the capacitance to use in a capacitor filter connected to a full-wave rectifier operating at a standard aircraft power frequency of 400 Hz, if the ripple factor is 10% for a load of 500 Ω?

- (a) 72.2 μF (b) 87.6 μF  
(c) 25.2 μF (d) 102.4 μF

Ans. (\*)

$$r.f. = \frac{1}{4\sqrt{3} f_o R_L C}$$

$$C = \frac{1}{4\sqrt{3} f_o R_L r \cdot f} = \frac{1}{4\sqrt{3} \times 400 \times 500 \times 0.1}$$

$$C = \frac{1}{138564.06} = 7.22 \mu\text{F}$$

End of Solution

Q.51 Match the following Lists regarding R-C filter circuit:

**List-I (Component)**

**List-II (Output voltage ( $V_{out}$ ))**

P. Low-pass filter

1.  $\frac{1}{RC} \int_0^t V_{in} dt$

Q. R-C circuit as integrator

2.  $V_{in} \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$

R. High-pass filter

3.  $RC \frac{dV_{in}}{dt}$

S. R-C circuit as differentiator

4.  $V_{in} \frac{1}{\sqrt{1 + (\omega RC)^2}}$

Select the correct answer using the code given below.

	P	Q	R	S
(a)	4	3	2	1
(b)	1	3	2	4
(c)	4	1	2	3
(d)	2	1	4	3

Ans. (c)

End of Solution

Q.52 Match the following Lists:

**List-I (Name of the flag)**

**List-II (Bit position in flag register)**

P. Auxiliary carry flag

1.  $D_0$

Q. Parity flag

2.  $D_2$

R. Zero flag

3.  $D_4$

S. Carry flag

4.  $D_6$

Select the correct answer using the code given below.

	P	Q	R	S
(a)	4	3	2	1
(b)	1	3	2	4
(c)	2	3	4	1
(d)	3	2	4	1

Ans. (d)

End of Solution



# Foundation Courses for

## ESE 2027

## GATE 2027



### Tablet Course

- Pre-loaded full fledged recorded course
- Android OS based 10.5 inch Samsung tablet
- Internet access does not required
- Classes by senior faculties
- Validity: 2 Years
- Learn at your own pace
- Tablet is reusable for normal purpose after validity expires



### Recorded Course

- Recorded Course
- Full fledged holistic preparation
- Classes by senior faculties
- Lectures can be watched anytime/ anywhere
- Courses are accessible on PC & Mac desktops/laptops/android/ iOS mobile devices.
- Learn at your own pace
- Validity: 1 year
- Internet connection required

### Teaching Hours

- ✓ **GATE Exclusive** • CE, ME, EE : 800 to 900 Hrs.  
• EC, IN, CS, CH : 650-700 Hrs.
- ✓ **GATE + ESE** • CE, ME, EE, EC : 1100 to 1200 Hrs.
- ✓ **GATE + SES-GS** • CE, ME, EE : 1150 to 1250 Hrs. ✓ **GATE + ESE + SES-GS** • CE, ME, EE, EC : 1450 to 1550 Hrs.  
• EC, IN, CS, CH : 950-1050 Hrs.

**Note :** State Engineering Services Examination. • The course is offered with a validity options of 1 year and 2 years.

Low Cost EMI Facility Available

Admissions open



Scan to enroll

**Delhi Centre :** 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

**MADE EASY Centres :** Delhi | Bhopal | Hyderabad | Jaipur | Pune

[www.madeeasy.in](http://www.madeeasy.in)

**Q.53** Match the following Lists regarding interfacing the 8155 memory section:

**List-I (Address lines)**

**List-II (Function used for)**

**P.** A11 to A15

**1.** Don't Care

**Q.** A0 to A7

**2.** Chip Enable

**R.** A8 to A10

**3.** Register Select

Select the correct answer using the code given below.

**P Q R**

(a) 2 3 1

(b) 1 3 2

(c) 3 1 2

(d) 3 2 1

**Ans. (b)**

**P.** A11 to A15

**1.** Don't care

**Q.** A0 to A7

**3.** Register select

**R.** A8 to A10

**2.** Chip select

End of Solution

**Q.54** The emission current of a diode is 12.5 mA. What is the rms value of shot noise current for a 10 MHz bandwidth?

(a) 18.2  $\mu$ A

(b) 1.3  $\mu$ A

(c) 0.2  $\mu$ A

(d) 2.7  $\mu$ A

**Ans. (c)**

RMS shot noise current  $i_n = \sqrt{2qI\Delta f}$

$q$  is the electronic charge =  $1.6 \times 10^{-19}$  C

$I$  is the direct current (i.e. emission current)

$\Delta f$  is the bandwidth in Hz.

$$i_n = \sqrt{2 \times (1.6 \times 10^{-19}) \times (12.5 \times 10^{-3}) \times (10^7)}$$

$$= 2 \times 10^{-7} = 0.2 \mu\text{A}$$

End of Solution

**Q.55** A transmitter supplies 10 kW power to an aerial, when unmodulated. What is the power radiated, when modulated to 30%?

(a) 3 kW

(b) 10.45 kW

(c) 14.8 kW

(d) 4 kW

**Ans. (b)**

$$P_c = 10 \text{ kW}$$

$$\mu = 0.3$$

$$P_t = P_c \left[ 1 + \frac{\mu^2}{2} \right] = 10 \text{ K} \left[ 1 + \frac{0.09}{2} \right] = 10.45 \text{ kW}$$

End of Solution



**Q – 1:**

Flat top sampling uses sample-and-hold principle. Flat top sampling involves taking a sample and holding its instantaneous value constant for the duration of the pulse.

**R – 2**

Ideal (or Impulse) sampling is a theoretical process where message signal is multiplied by a periodic train of impulses.

End of Solution

**Q.59** The diode falls under which type of system?

- (a) Stable only (b) Unstable only  
(c) Either stable or unstable (d) Neither stable nor unstable

Ans. (a)

$$i_D = i_o \left[ e^{\frac{V_D}{nV_T}} - 1 \right] \rightarrow \text{Stable}$$

End of Solution

**Q.60** Which of the following properties of convolution system exhibits/exhibit the result of superposition principle for unit impulse response in linear time-invariant systems?

- (a) Commutativity only (b) Distributivity only  
(c) Associativity only (d) Both distributivity and associativity

Ans. (d)

End of Solution

**Q.61** Consider the following statements regarding behavior of second-order underdamped system:

1. The peak time is inversely proportional to the imaginary part of the complex pole.
2. Percent overload is a function of only the damping ratio.
3. Settling time is directly proportional to the real part of the complex pole.

Which of the above statements are correct?

- (a) 1 and 3 only (b) 1, 2 and 3  
(c) 1 and 2 only (d) 2 and 3 only

Ans. (c)

1.  $t_p = \frac{\pi}{\omega_d}$   
and complex pole =  $-\alpha \pm j\omega_d = -\xi\omega_n \pm j\omega_d$

So,  $t_p \propto \frac{1}{\text{img}(\text{complex pole})}$

2.  $\%M_p = e^{-\xi\pi/\sqrt{1-\xi^2}}$   
So,  $\%M_p = f(\xi)$

3.  $t_s = \frac{4}{\xi\omega_n}$

i.e.  $t_s \propto \frac{1}{\text{real (complex pole)}}$

So, statement-3 is incorrect.

End of Solution

**Q.62** For the closed-loop transfer function given below, what is the system condition based on the number of poles in the left-half plane, the right-half plane and the  $j\omega$ -axis.

$$T(s) = \frac{200}{s^4 + 6s^3 + 11s^2 + 6s + 200}$$

- The system is stable with four poles on the left-half of the plane.
- The system is unstable, since it has two right-half plane poles and two left-half plane poles.
- The system is marginally stable, since it has two left-half plane poles and two on  $j\omega$ -axis.
- The system is unstable, since it has one right-half plane pole and three left-half plane poles.

**Ans. (b)**

$s^4$	1	11	200
$s^3$	6	6	
$s^2$	10	200	
$s^1$	-114		
$s^0$	200		

Since there are two sign changes.

So, LHS pole = 2

and RHS pole = 2

and system is unstable.

End of Solution

**Q.63** Consider the following statements regarding stability for linear, time-invariant systems using natural response:

- A system is marginally stable, if the natural response neither decays nor grows but remains constant or oscillates.
- A system is unstable, if the natural response approaches infinity as time approaches zero.
- A system is unstable, if any bounded input yields an unbounded output.

Which of the above statements is/are **not** correct?

- 1 only
- 2 only
- 3 only
- 1, 2 and 3

**Ans. (b)**

Instability is defined by the behavior of the system as  $t \rightarrow \infty$ , not zero. A system is  $t \rightarrow 0$ , value of response is the initial condition of system and for an LTI system it is zero.

End of Solution

**Q.64** What are the values of positive constant ( $K_p$ ), velocity constant ( $K_v$ ) and acceleration constant ( $K_a$ ) for a type '0' unity feedback system which has the transfer function  $G(s)$

$$= \frac{1000(s+8)}{(s+7)(s+9)} ?$$

- (a)  $K_p = 0; K_v = 0; K_a = 127$       (b)  $K_p = 0; K_v = 0; K_a = 0$   
 (c)  $K_p = 0; K_v = 127; K_a = 127$       (d)  $K_p = 127; K_v = 0; K_a = 0$

**Ans. (d)**

$$K_p = \lim_{s \rightarrow 0} G(s)H(s) = \lim_{s \rightarrow 0} \frac{1000(s+8)}{(s+7)(s+9)}$$

$$= \frac{1000 \times 8}{7 \times 9} = 127$$

Since type 0 system,

So,  $K_v = 0, K_a = 0$

End of Solution

**Q.65** Consider the following statements regarding properties of a transfer function:

- The unit of a transfer function is related to the units of the system input and output. A unit is essential.
- The transfer function can be applied to describe only time-invariant linear systems whose parameters do not change or change only a little during operation.
- The transfer function is dependent of the input to the system, since the characteristics of the system are modified by the input signal.

Which of the above statements is/are correct?

- (a) 1, 2 and 3      (b) 1 and 3 only  
 (c) 2 and 3 only      (d) 2 only

**Ans. (d)**

A transfer function doesn't hv unit and it does not depend upon input.

End of Solution

**Q.66** Consider the following and give the order of the steps to be followed in performing the block diagram reduction to get the final transfer function for that system:

Step 1 : Combine all serial blocks

Step 2 : Close all inner loops

Step 3 : Combine all parallel blocks

Step 4 : Move summing junctions to the left or right of a block and tie points to the left or right

Select the correct sequence for the above steps.

- (a) Step 1, Step 2, Step 3, Step 4  
 (b) Step 1, Step 3, Step 2, Step 4  
 (c) Step 3, Step 2, Step 1, Step 4  
 (d) Step 2, Step 3, Step 1, Step 4



Ans. (a)

Given data :

$$I_0 = 2 \text{ A}$$

$$W_0 = 50 \text{ W}$$

$$V = 230 \text{ V}$$

$$W_0 = V I_0 \cos \phi_0$$

$$\Rightarrow \cos \phi_0 = \frac{W_0}{V I_0}$$

$$\cos \phi_0 = \frac{50}{2 \times 230} = 0.108$$

Core loss current,  $I_C = I_0 \cos \phi_0 = 2 \times 0.108$   
 $= 0.216$

End of Solution

**Q.70** A 500 kVA transformer has an efficiency of 95% at full load and also at 60% of full load; both at unity power factor. Separate out the losses of the transformer.

- (a)  $P_i = 12.42 \text{ kW}$  and  $P_c = 18.52 \text{ kW}$   
 (b)  $P_i = 2.45 \text{ kW}$  and  $P_c = 8.35 \text{ kW}$   
 (c)  $P_i = 8.43 \text{ kW}$  and  $P_c = 13.25 \text{ kW}$   
 (d)  $P_i = 9.87 \text{ kW}$  and  $P_c = 16.45 \text{ kW}$

Ans. (d)

Given:

Efficiency of full load UPF is 95%

Efficiency of 60% full load UPF is 95%

$$\frac{1 \times 500 \times 1}{1 \times 500 \times 1 + P_i + P_{cu}} = 0.95 \quad \dots(i)$$

$$\frac{0.6 \times 500 \times 1}{0.6 \times 500 \times 1 + P_i + (0.6)^2 P_{cu}} = 0.95 \quad \dots(ii)$$

By solving (i) and (ii) we get,

$$0.95 P_i + 0.95 P_{cu} = 25$$

$$0.95 P_i + 0.342 P_{cu} = 15$$

By solving the above equation,

$$P_i = 9.868 \text{ kW}$$

$$P_{cu} = 16.447 \text{ kW}$$

End of Solution

**Q.71** Consider the following statements regarding three-phase transformer connections:

1. Delta/delta is economical for small HV transformers.
2. Star/star suits large LV transformers.
3. Star/delta is the most commonly used connection for power systems.

Which of the above statements is/are correct?

- (a) 2 and 3  
(b) 3 only  
(c) 1 only  
(d) 1 and 2

Ans. (b)

- Delta is economical for LV.
- Star connection is best suitable for HV.
- Star/Delta (or) Delta/Star is commonly used connection in power system depending on step-down (or) step-up requirements.

HV side-star and LV side Delta


Delta suppress 3rd harmonics.

End of Solution

**Q.72** A 240 V/120 V, 12 kVA transformer has full-load unity power factor efficiency of 96.2%. It is connected as an auto-transformer to feed a load at 360 V. What is the auto-transformer rating?

- (a) 36 kVA  
(b) 18 kVA  
(c) 54 kVA  
(d) 34.63 kVA

Ans. (a)

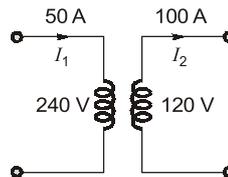


Given :

240/120 V, 12 kVA transformer reconnected as auto transformer to feed a load at 360 V.

In such case, two possibilities are available HV as common LV as common winding (Both additive polarity)


- HV as common, additive

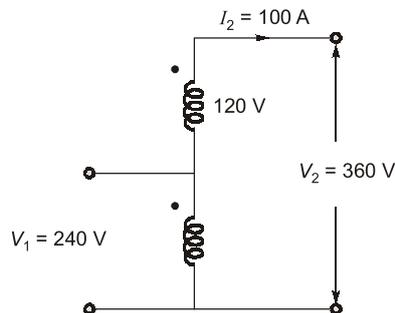

Rating :  $V_2 I_2$

$$360 \times 100 = 36 \text{ kVA}$$

2. LV common, additive

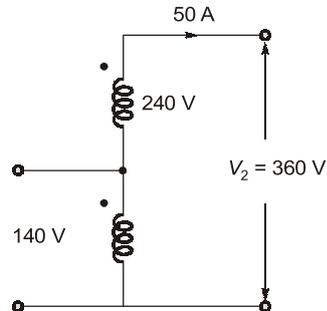

$$\text{Rating : } V_2 I_2$$

$$360 \times 50 = 18 \text{ kVA}$$

**Conclusion:**

Answer is provided for both connections. But consider the best possible rating.

End of Solution

**Q.73** The magnetic flux density on the surface of an iron face is 1.6 T, which is a typical saturation level value for ferromagnetic material. What is the force density on the iron face?

- (a)  $1.6 \times 10^6 \text{ N/m}^2$  (b)  $1.02 \times 10^6 \text{ N/m}^2$   
 (c)  $1.02 \times 10^7 \text{ N/m}^2$  (d)  $1.6 \times 10^7 \text{ N/m}^2$

**Ans. (b)**

Given:

$$B = 1.6 \text{ T}$$

Magnetic force,  $F = \frac{B^2}{2\mu_0}$

$$\Rightarrow F = \frac{(1.6)^2}{2 \times 4\pi \times 10^{-7}}$$

$$F = 1.02 \times 10^6 \text{ N/m}^2$$

End of Solution

**Q.74** For a 6-pole DC armature with 16 slots having two coil sides per slot and single-turn coils, what is the commutator pitch ( $y_c$ ) for a wave winding?

- (a) 8 segments (b) 9 segments  
 (c) 6 segments (d) 5 segments

**Ans. (c)**

$$Y_c = \frac{c \pm 1}{(P/2)} \quad (\text{Coils, } c = \text{slots} = 16)$$

$$Y_c = \frac{16 + 1}{(6/2)} = \frac{17}{3} \approx 6$$



$$\begin{aligned} \text{MTTDL} &\approx \frac{\text{MTTF}^2}{2 \times \text{MTTR}} = \frac{(100000)^2}{2 \times 10} \\ &= \frac{10^{10}}{20} \Rightarrow 5 \times 10^8 \text{ hrs} \end{aligned}$$

Convert hours into years

$$1 \text{ year} \approx 8760 \text{ hrs}$$

$$\therefore \text{MTTDL in years} = \frac{5 \times 10^8 \text{ hrs}}{8760} = 57000 \text{ years}$$

End of Solution

**Q.78** Which one of the following modifiers tells the compiler that a variable's value may be changed in ways not explicitly specified by the program?

- (a) Volatile (b) Identifier  
(c) Const (d) Typedef

**Ans. (a)**

Volatile tells the compiler that don't assume "this variable stays the same between access.

Because, the value may change due to,

- H/w registers
- Interrupts
- DMA
- another thread/process.

End of Solution

**Q.79** Consider the following statements regarding applications of a p-n junction diode:

1. It is used as a switch in DC power supplies.
2. It is used as rectifiers in voltage stabilizing circuits.
3. It is used as signal diodes in communication circuits.

Which of the above statements is/are correct?

- (a) 2 only (b) 2 and 3  
(c) 3 only (d) 1 and 3

**Ans. (d)**

Statement 1 and 3 are correct.

End of Solution

**Q.80** Consider the following statements regarding transistors:

1. They can be made to oscillate with very small power consumption.
2. They cannot sustain mechanical shocks.
3. Their application is limited up to a few megacycles only.

Which of the above statements is/are correct?

- (a) 2 only (b) 2 and 3  
(c) 3 only (d) 1 and 3

Ans. (d)

Statement 1 and 3 are correct.

End of Solution

**Q.81** A field-effect transistor operates with a drain current of 100 mA and a gate source bias of  $-1$  V. The device has dynamic forward transconductance value of  $0.25$  S. If the bias voltage decreases to  $-1.2$  V, what is the new value of the drain current?

- (a) 50 mA (b) 75 mA  
(c) 150 mA (d) 125 mA

Ans. (a)

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} = \frac{I_{D2} - I_{D1}}{V_{GS2} - V_{GS1}}$$

$$I_{D2} - I_{D1} = g_m \times \Delta V_{GS}$$

$$I_{D2} - 0.1 = -0.25 \times 0.2$$

$$I_{D2} = 0.1 - 0.05 = 0.05 \text{ A} = 50 \text{ mA}$$

End of Solution

**Q.82** Match the following Lists regarding bipolar junction transistors:

	List-I (Type of transistor)	List-II (Application)
P.	BC108 (n-p-n)	1. Switching
Q.	BF180 (n-p-n)	2. General-purpose small-signal amplifier
R.	2N3904 (n-p-n)	3. Low-frequency power
S.	2N3055 (n-p-n)	4. RF amplifier

Select the correct answer using the code given below.

	P	Q	R	S
(a)	4	2	1	3
(b)	4	3	2	1
(c)	3	4	1	2
(d)	2	4	1	3

Ans. (d)

- BC108 (n-p-n) → This is classic silicon transistor used as a general purpose small-signal amplifier due to its low noise and moderate gain.
- BF180 (n-p-n) → 'BF' prefix typically denote high-frequency transistors. This specific model is used in RF amplifier.
- 2N3904 (n-p-n) → One of the most common transistor used for switching application and low power amplification.
- 2N3055 (n-p-n) → This is high-power transistor used for low-frequency power application such as power supplies or audio amplifier.

End of Solution



# Conventional Questions Practice Programme for ESE Mains 2026




Scan to enroll

Offline

Live-Online

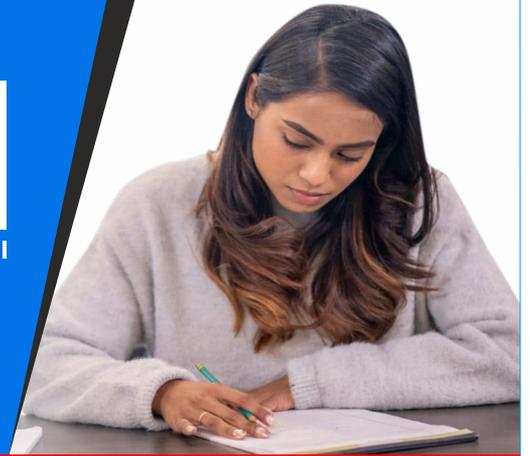- Batches Starting from 24 Feb, 2026
- Admissions Open



## ESE Mains Test Series (15 tests) Starting from 15 March, 2026

Note : Solo Mains Test Series is also available.



Scan to enroll

This conventional course is offered in offline mode at Delhi Centre.

### Key Features :

- Classes by MADE EASY senior faculties
- Beneficial to improve answer writing and presentation skills
- Updated Main exam workbooks containing diverse practice questions
- Highly useful for State Engineers Service examinations also.
- In-depth analysis and discussion on probable & potential questions
- Develops numerical questions solving techniques
- Weekly dynamic test series on every Sunday aligned with the course (optional).

Duration: 300-350 Hrs | Streams: CE, ME, EE, E&T

### Fee Structure :

#### ESE Main Course Fees

- MADE EASY students : ₹13,000 + GST
- Non-MADE EASY students : ₹15,000 + GST

#### Main Course + Test Series Fee

- MADE EASY students : ₹16,500 + GST
- Non-MADE EASY students : ₹18,500 + GST

#### Test Series Fee

For all students : ₹4,500 + GST

Delhi Centre : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

MADE EASY Centres : Delhi | Bhopal | Hyderabad | Jaipur | Pune

[www.madeeasy.in](http://www.madeeasy.in)

**Q.83** Consider the following statement regarding p-n-p transistor:

1. The base-collector junction is reverse biased to holes in the base region and electrons in the collector region.
2. The base region is very thin and is only lightly doped with electrons.
3. A large proportion of the electrons in the base region cross the base-collector junction into the collector region, creating a collector current.

Which of the above statements is/are correct?

- (a) 2 only (b) 2 and 3  
(c) 3 only (d) 1 and 3

**Ans. (a)**

Statement 1 incorrect  
Statement 2 correct  
Statement 3 incorrect

End of Solution

**Q.84** For a JFET, the typical values of amplification factor and transconductance are specified as 80 and 200  $\mu\text{S}$  respectively. What is the dynamic drain resistance of this JFET?

- (a) 25  $\text{k}\Omega$  (b) 25  $\mu\Omega$   
(c) 400  $\text{k}\Omega$  (d) 400  $\mu\Omega$

**Ans. (c)**

$$\mu = g_m r_d$$

$$r_d = \frac{\mu}{g_m} = \frac{80}{0.2 \text{ mS}} = 400 \text{ k}\Omega$$

End of Solution

**Q.85** There is no need of a driver stage, if FET is used as power amplifier instead of BJT, because

- (a) FET digital circuits need much less power compared to BJT circuits
- (b) there is no risk of thermal runaway in FET circuits
- (c) power gain of an FET is much higher than that of a BJT
- (d) FET is essentially a voltage-operated device

**Ans. (d)**

Statement 4 is correct

End of Solution

**Q.86** Match the following Lists regarding field-effect transistor amplifiers:

**List-I (Configuration)**

- P. Common source  
Q. Common drain  
R. Common gate

**List-II (Typical application)**

1. Impedance matching stages
2. General-purpose, AF and RF amplifiers
3. RF and VHF amplifiers

Select the correct answer using the code given below.

- |     | P | Q | R |
|-----|---|---|---|
| (a) | 2 | 1 | 3 |
| (b) | 1 | 3 | 2 |
| (c) | 3 | 2 | 1 |
| (d) | 2 | 3 | 1 |

Ans. (a)

End of Solution

**Q.87** Match the following Lists regarding bipolar transistor amplifiers:

**List-I (Configuration)**

- P.** Common emitter  
**Q.** Common collector  
**R.** Common base

**List-II (Typical application)**

1. RF and VHF amplifiers
2. Impedance matching, input and output stages
3. General-purpose, AF and RF amplifiers

Select the correct answer using the code given below.

- |     | P | Q | R |
|-----|---|---|---|
| (a) | 2 | 1 | 3 |
| (b) | 1 | 3 | 2 |
| (c) | 3 | 2 | 1 |
| (d) | 3 | 1 | 2 |

Ans. (c)

End of Solution

**Q.88** Consider the following statements regarding frequency response of BJT amplifiers:

1. The CE amplifier has a high gain but a relatively narrow bandwidth.
2. The CC amplifier has a lower gain but a larger bandwidth.
3. The CB amplifier has a higher gain and a larger bandwidth.

Which of the above statements is/are correct?

- |            |             |
|------------|-------------|
| (a) 2 only | (b) 2 and 3 |
| (c) 3 only | (d) 1 and 2 |

Ans. (d)

Statement 1 and 2 are correct.

End of Solution

**Q.89** In a common-collector amplifier stage, the impedance between base and emitter is magnified because of

- |                       |                             |
|-----------------------|-----------------------------|
| (a) source resistance | (b) negative feedback       |
| (c) Miller effect     | (d) high-frequency response |

Ans. (b)

Because of negative  $f_B$ .

End of Solution

- Q.90** In Colpitts oscillator circuits, the amount of feedback is controlled by the
- (a) position of the coil tap (b) ratio of inductances  
(c) ratio of capacitances (d) ratio of resistances

Ans. (c)

$$\beta = \text{Feedback ratio} = \frac{C_2}{C_1}$$

End of Solution

- Q.91** An electro-dynamometer-type wattmeter has a current coil with a resistance of  $0.1 \Omega$  and a pressure coil with resistance of  $6.5 \text{ k}\Omega$ . What is the percentage error while the meter is connected as current coil to the load side, if the load is specified as  $12 \text{ A}$  at  $250 \text{ V}$  with unity power factor?

- (a) 14.4% (b) 0.48%  
(c) 4.8% (d) 1.44%

Ans. (b)

Given,

Current coil resistance,

$$R_C = 0.1 \Omega$$

Load current,  $I = 12 \text{ A}$

Load voltage,  $V = 250 \text{ V}$

Power consumed by current coil

$$P_C = I^2 R_C = 12^2 \times 0.1 = 14.4 \text{ W}$$

True load power:

$$P = VI = 250 \times 12 = 3000 \text{ W}$$

$$\% \text{ error} = \frac{14.4}{3000} \times 100 = 0.48\%$$

End of Solution

- Q.92** What is the expression for deflecting torque in single-phase induction-type energy meter?

- (a)  $T_d \propto \frac{\phi_P \phi_S \omega}{Z} \sin \beta \cos \alpha$  (b)  $T_d \propto \frac{\phi_{1m} \phi_{2m}}{\omega Z} \sin(\alpha - \theta) \cos \beta$   
(c)  $T_d \propto \frac{\phi_{1m} \phi_{2m} \omega}{Z} \sin \alpha \cos \beta$  (d)  $T_d \propto \frac{\phi_P \phi_S}{\omega Z} \sin \alpha \cos \beta$

Ans. (a)

End of Solution

- Q.93** When secondary winding of current transformer is open circuited with primary winding still energized, the large flux greatly increases the

- (a) flux density in the core and pushes it towards saturation  
(b) power loss in the secondary winding  
(c) leakage flux manifolds  
(d) power loss in the primary winding

Ans. (a)

When the secondary of a current transformer (CT) is open and the primary is energized, the secondary current becomes zero. To maintain ampere-turn balance, the primary draws heavy magnetizing current producing very large flux that drives the core toward saturation.

End of Solution

- Q.94** The purpose of the start bit in digital voltmeter is to
- (a) hold the digital word in the display for a particular time
  - (b) provide the display of the information that comes from the A/D conversion
  - (c) give zero indication on the display during start of conversion
  - (d) give information about polarity of the measurand voltage given by the A/D converter

Ans. (c)

End of Solution

- Q.95** In general, the range of digital multimeter display is
- (a) -199 to +199
  - (b) -999 to +999
  - (c) -9999 to +9999
  - (d) -1999 to +1999

Ans. (d)

Most digital multimeters are  $3\frac{1}{2}$  digit displays, meaning the maximum count is 1999.

Range : -1999 to +1999

End of Solution

- Q.96** Which one of the following code counters is used to remove the ambiguity during the change from one state of the counter to the next during the state transition?
- (a) Gray code counter
  - (b) BCD code counter
  - (c) Excess-3 code counter
  - (d) Binary code counter

Ans. (a)

A gray code counter ensures only one bit changes at a time, removing ambiguity during state transition.

End of Solution

- Q.97** Which one of the following gates is most commonly used in the design of a bus system?
- (a) OR gate
  - (b) NOT gate
  - (c) XOR gate
  - (d) Buffer gate

Ans. (d)

A tri-state buffer is used in bus system to allow multiple devices to share a common bus without conflict.

End of Solution



**Q.101** Which one of the following is **not** an operation performed by call subroutine instruction?

- (a) The address of the next instruction available in the program counter is stored in a temporary location, so the subroutine knows where to return.
- (b) Control is transferred to the beginning of the subroutine.
- (c) The instruction return from subroutine, transfers the return address from the temporary location into the program counter.
- (d) The address of the next instruction available in the program counter is stored in an accumulator and returns whenever it is required.

**Ans. (d)**

Call instruction

1. PC → Stack memory.
2. PC → Updated with subroutine address.

**End of Solution**

**Q.102** Which of the following lines/diagrams are used when the data transfer is between an interface and an I/O device?

- (a) Strobe lines
- (b) Handshaking lines
- (c) Timing diagrams
- (d) State diagrams

**Ans. (b)**

For data transfer between an interface and an I/O device, handshaking signals are used. They provide a two-way synchronization (e.g. data ready and data acknowledged) to ensure reliable communication.

**End of Solution**

**Q.103** In which one of the following data transfer schemes, the CPU stays in a program loop until the I/O unit indicates that it is ready for data transfer while transferring data to and from peripherals?

- (a) Programmed I/O
- (b) Interrupt-initiated I/O
- (c) Direct memory access
- (d) Programmed interrupt I/O

**Ans. (b)**

When the CPU keeps running a program loop, it receives an interrupt from I/O, when I/O is ready, because of which the corresponding interrupt service routine executes. This methodology is known as interrupt initiated I/O, which avoids CPU wasting time for enquiring I/O continuously.

**End of Solution**

**Q.104** Which one of the following methods is used to detect burst errors occurring in the communication channel?

- (a) Cyclic redundancy check
- (b) Bit stuffing
- (c) Pulse code checking
- (d) Bit spoofing

Ans. (a)

CRC is standard error detection method in digital communication. It is design to detect burst errors, which are sequence of consecutive bits corrupted by noise. Bit stuffing is a technique used in data link layer protocols to prevent data from being interpreted as control bits. It is used for frame synchronization, not for error detection. Pulse code checking is not a standard term for an error detection. Pulse code modulation exits for digitizing analog signals. Bit spoofing is generally refers to a security attack where a person or program succesfully pretending as another by falsifying data.

End of Solution

**Q.105** In operating systems, which one of the following approaches is used to keep track of system activities such as the number of system calls made or the number of operations performed to a network device or disk?

- (a) Counters (b) Tracing  
(c) Scheduling (d) Pipelining

Ans. (a)

- Counters are Explicitly used to count the“ occurrences of events like system calls, disk IO operations and N/W packets.
- OS kernel maintain counters for performance “monitoring and Accounting.

End of Solution

**Q.106** What is the drift velocity of electrons knowing that in metals, the free electron concentration in about  $n_0 = 10^{28}$  electrons/m<sup>3</sup>?

(Take maximum admitted value of the density of electric current for metals as  $J = 10^7$  A/m<sup>2</sup> and electrical charge of the electron as  $q_0 = 1.602 \times 10^{-19}$  C)

- (a)  $1.6 \times 10^{-3}$  m/s (b)  $6.24 \times 10^{-22}$  m/s  
(c)  $1.6 \times 10^{-22}$  m/s (d)  $6.24 \times 10^{-3}$  m/s

Ans. (d)

$$J = nqv_d$$

$$v_d = \frac{J}{nq} = \frac{10^7}{10^{28} \times 1.602 \times 10^{-19}} = 0.624 \times 10^{-2} = 6.24 \times 10^{-3} \text{ m/s}$$

End of Solution

**Q.107** Which one of the following is generated by the supplementary (precession) movements of the conduction electrons that appear when the material is introduced in a magnetic field?

- (a) Langevin diamagnetism (b) Landau diamagnetism  
(c) Lorentz diamagnetism (d) Larmor diamagnetism

Ans. (b)

Langevin diamagnetism → due to bound electrons

Landau diamagnetism → due to free electrons i.,e conduction electrons

Larmor diamagnetism → Classical atomic orbital precession

End of Solution

- Q.108** The cermet of Au/SiO is obtained by
- the deposition on glass support and consists in conductive particles of gold spread in amorphous matrix of SiO<sub>2</sub>.
  - transforming the silicon monoxide at the deposition in a reactive component (Si) and in an insulating one SiO<sub>2</sub>.
  - the mixture of  $\alpha$ -Cr, Cr<sub>3</sub>Si and SiO<sub>2</sub> amorphous
  - the expansion of both nonconductive and conductive zones of a reactive component (Si)

**Ans. (a)**

Cermet of Au SiO consists of conductive gold particles dispersed in amorphous SiO<sub>2</sub> matrix.

End of Solution

- Q.109** Match the following Lists:

	List-I (Class of the material)	List-II (Limiting working temperature)
P.	A	1. 120° C
Q.	E	2. 180° C
R.	H	3. 90° C
S.	Y	4. 105° C

Select the correct answer using the code given below.

	P	Q	R	S
(a)	3	2	4	1
(b)	4	1	3	2
(c)	3	1	2	4
(d)	4	1	2	3


**Ans. (d)**

Class	Limiting temperature
A	105°C
E	120°C
H	180°C
Y	90°C

End of Solution

- Q.110** A transformer core is wound with a coil carrying an alternating current at a frequency of 50 Hz. The hysteresis loop has an area of 70000 units, when the axes are drawn in units of 10<sup>-4</sup> Wb-m<sup>2</sup> and 10<sup>2</sup> A-m<sup>-1</sup>. What is the hysteresis loss by assuming the magnetization to be uniform throughout the core volume of 0.02 m<sup>3</sup> ?
- 350 W
  - 700 W
  - 3500 W
  - 7000 W

Ans. (b)

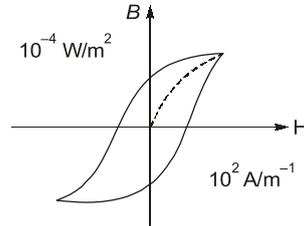

Hysteresis loop area given : 70000 units

$$f = 50 \text{ Hz}$$

$$\text{Core volume} = 0.02 \text{ m}^3$$

Area of B-H loop is Hysteresis loss per cycle per unit volume

From given Hysteresis loop area:

Hysteresis loss per cycle per unit volume is:

$$70000 \times 10^{-4} \times 10^2 = 700 \text{ J/m}^3 \text{ per cycle}$$

As frequency is given 50 Hz

$$\text{Hysteresis loss per unit volume} = 700 \times 50 = 35000 \text{ W/m}^3$$

Total volume of core is 0.02 m<sup>3</sup>

$$\therefore \text{Hysteresis loss} = 35000 \times 0.02 = 700 \text{ W}$$

End of Solution

**Q.111** L is measured value of inductance with magnetic core,  $L_0$  is measured value of inductance without magnetic core,  $\mu_0$  is magnetic permeability of free space,  $h$  is height of the material under test,  $c$  is outer diameter of the material under test,  $d$  is inner diameter of the material under test. What is the formula for relative magnetic permeability ( $\mu_r$ )?

$$(a) \mu_r = \frac{\mu_0}{2\pi} \frac{L - L_0}{h \ln\left(\frac{c}{d}\right)}$$

$$(b) \mu_r = \frac{L - L_0}{\mu_0} \frac{2\pi}{h \ln\left(\frac{c}{d}\right)}$$

$$(c) \mu_r = \frac{\mu_0}{2\pi} \frac{L - L_0}{h \ln\left(\frac{d}{c}\right)}$$

$$(d) \mu_r = \frac{L - L_0}{\mu_0} \frac{2\pi}{h \ln\left(\frac{d}{c}\right)}$$

Ans. (b)

Given data,

inner diameter =  $d$ ; outer diameter =  $c$ ; height =  $h$

Magnetic field due to a toroid,

$$H = \frac{I}{2\pi r}; \quad r = \text{mean radius}$$

$$\Rightarrow B = \mu H = \frac{\mu I}{2\pi r}; \quad \mu = \mu_0 \mu_r$$

$$\Rightarrow \phi = \bar{B} \cdot \bar{ds} = B \times h dr$$

$$\Rightarrow \phi = \frac{\mu I}{2\pi r} h dr$$



Ans. (a)

$$\begin{aligned}\sigma &= \frac{nq^2\tau_c}{m} = \frac{8.5 \times 10^{28} \times (1.6 \times 10^{-19})^2 \times 2 \times 10^{-14}}{9.1 \times 10^{-31}} \\ &= 4.78 \times 10^{28 - 38 - 14 + 31} \\ &= 4.78 \times 10^7 = 4.8 \times 10^7 \text{ ohm}^{-1} \text{ m}^{-1}\end{aligned}$$

End of Solution

Q.114 Match the following Lists:

**List-I (Material)**

- P. Silver
- Q. Copper
- R. Gold
- S. Aluminium

**List-II (Density)**

- 1.  $2.70 \times 10^3 \text{ kg-m}^{-3}$
- 2.  $8.96 \times 10^3 \text{ kg-m}^{-3}$
- 3.  $10.49 \times 10^3 \text{ kg-m}^{-3}$
- 4.  $19.32 \times 10^3 \text{ kg-m}^{-3}$

Select the correct answer using the code given below.

- |     | P | Q | R | S |
|-----|---|---|---|---|
| (a) | 3 | 2 | 1 | 4 |
| (b) | 4 | 1 | 3 | 2 |
| (c) | 3 | 2 | 4 | 1 |
| (d) | 4 | 1 | 2 | 3 |

Ans. (c)

Aluminium has lowest density among all these metals.

End of Solution

Q.115 The resistivity of pure copper at room temperature is  $1.8 \times 10^{-8} \text{ ohm-m}$ . The resistivity of Cu-4% Ni alloy at room temperature is  $7.0 \times 10^{-8} \text{ ohm-m}$ . What is the resistivity due to impurity scattering by 1% of nickel in the copper lattice?


- (a)  $2.2 \times 10^{-8} \text{ ohm-m}$
- (b)  $6.5 \times 10^{-8} \text{ ohm-m}$
- (c)  $0.2 \times 10^{-8} \text{ ohm-m}$
- (d)  $1.3 \times 10^{-8} \text{ ohm-m}$

Ans. (d)

$$\begin{aligned}\rho_{\text{Cu}} &= 1.8 \times 10^{-8} \text{ } \Omega\text{-m} \\ \rho_{\text{alloy}} &= \rho_{\text{pure}} + \rho_{\text{impurity}} \\ \rho_{\text{impurity}} &= 7 \times 10^{-8} - 1.8 \times 10^{-8} \\ &= 5.2 \times 10^{-8} \text{ } \Omega\text{-m with 4\% Ni} \\ \therefore \text{ For 4\% Ni} &\rightarrow 5.2 \times 10^{-8} \text{ } \Omega\text{-m} \\ \therefore \text{ For 1\% Ni} &\rightarrow \frac{5.2 \times 10^{-8}}{4} = 1.3 \times 10^{-8} \text{ } \Omega\text{-m}\end{aligned}$$

End of Solution

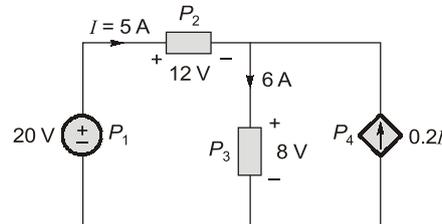**Q.116** What is the power supplied by each element in the circuit shown below?



- (a)  $P_1 = -100 \text{ W}$ ;  $P_2 = 60 \text{ W}$ ;  $P_3 = -48 \text{ W}$ ;  $P_4 = -8 \text{ W}$   
 (b)  $P_1 = 100 \text{ W}$ ;  $P_2 = -60 \text{ W}$ ;  $P_3 = -48 \text{ W}$ ;  $P_4 = 8 \text{ W}$   
 (c)  $P_1 = -100 \text{ W}$ ;  $P_2 = -60 \text{ W}$ ;  $P_3 = 48 \text{ W}$ ;  $P_4 = -8 \text{ W}$   
 (d)  $P_1 = -100 \text{ W}$ ;  $P_2 = 60 \text{ W}$ ;  $P_3 = 48 \text{ W}$ ;  $P_4 = -8 \text{ W}$

**Ans. (d)**

$$P_1 = V_1 I_1$$

$$P_1 = (20)(5) = 100 \text{ W}$$

Power delivering is 100 watts

$$P_1 = -100 \text{ W}$$

$$P_2 = 12.5 = 60 \text{ W}$$

Power absorbing is 60 W

$$P_2 = 60 \text{ W}$$

$$P_3 = 8 \times 6 = 48 \text{ W}$$

Power absorbing is 48 W

$$P_3 = 48 \text{ W}$$

$$P_4 = (0.2 I)(8)$$

$$= (0.2)(5)(8)$$


$$P_4 = 8 \text{ Watts}$$

Power delivering is 8 W

$$P_4 = -8 \text{ W}$$

**End of Solution**

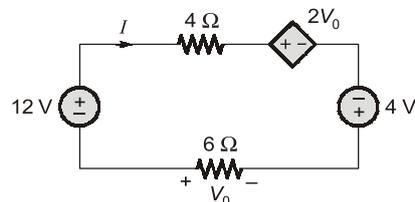**Q.117** What are  $V_0$  and  $i$  respectively in the circuit shown below?



- (a) +48 V, -8 A  
 (b) +24 V, -4 A  
 (c) -48 V, +8 A  
 (d) -24 V, +4 A

Ans. (a)

Write KVL equation,

$$12 - 4i - 2V_0 + 4 - 6i = 0$$

$$16 - 10i - 2V_0 = 0 \quad \dots(i)$$

$$V_0 = -6i$$

Substitute  $V_0$  in equation (i),

$$i = -8A$$

$$V_0 = -6i = (-6)(-8) = 48 \text{ V}$$

End of Solution

**Q.118** The electron beam in a TV picture tube carries  $10^{15}$  electrons per second. What is the voltage  $V_0$  needed to accelerate the electron beam to achieve 4 W?

(a) 10 kV

(b) 15 kV

(c) 30 kV

(d) 25 kV

Ans. (d)

$$I = \frac{Q}{t} = \frac{ne}{t} = \frac{10^{15}(1.602 \times 10^{-19})}{1}$$

$$I = 10^{-4}(1.602)$$

$$P = VI$$

$$V = \frac{P}{I} = \frac{4}{(1.602)(10^{-4})} \simeq 25 \text{ kV}$$

End of Solution

**Q.119** Consider the following statements regarding network theorems:

1. With independent sources, superposition theorem can be used only when the control functions are external to the network containing the sources, so that the controls are unchanged as the sources act one at a time.
2. A linear, active, resistive network, which contains one or more voltage or current sources, can be replaced by a single voltage source and a series resistance or by a single current source and a parallel resistance. The voltage is called the Thevenin equivalent voltage and the current is Norton current.
3. The two resistances are the same in both Thévenin's and Norton's theorems which are obtained by deactivating all the sources.

Which of the above statements is/are correct?

(a) 1 only

(b) 2 only


(c) 1 and 2

(d) 2 and 3

Ans. (d)

Statement 1 is incorrect.

Statement 2 and 3 are correct.

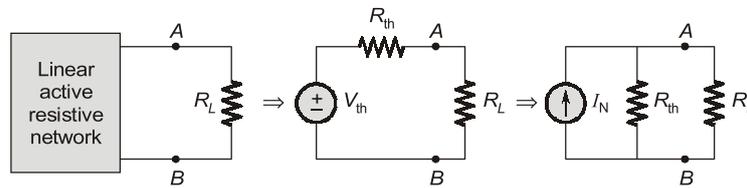

End of Solution

**Q.120** A 10-ohm resistor has a current of  $i = 2.5 \sin \omega t$  (A). What are the values of voltage and power respectively over one cycle of  $\omega = 500$  rad/s?

- (a)  $25 \sin \omega t$  (V);  $62.5 \sin^2 \omega t$  (W)      (b)  $250 \sin \omega t$  (V);  $625 \sin^2 \omega t$  (W)  
 (c)  $2.5 \sin \omega t$  (V);  $62.5 \sin^2 \omega t$  (W)      (d)  $25 \sin \omega t$  (V);  $625 \sin^2 \omega t$  (W)

Ans. (a)

$$V = iR = (2.5 \sin \omega t) (10)$$

$$v(t) = 25 \sin \omega t$$

$$P(t) = v(t) \cdot i(t)$$

$$= (25 \sin \omega t) (2.5 \sin \omega t)$$

$$P(t) = 62.5 \sin^2 \omega t$$

End of Solution

**Q.121** A box contains 10 screws, three of which are defective. If two screws are drawn at random without replacement, then what is the probability that neither of the two screws is defective?

- (a)  $49/100$       (b)  $14/30$   
 (c)  $9/10$       (d)  $2/3$

Ans. (b)

$$\frac{{}^3D}{{}^7ND} \Rightarrow \frac{{}^7C_2}{{}^{10}C_2} = \frac{7 \times 6}{10 \times 9} = \frac{14}{30}$$

End of Solution

**Q.122** If the random variable  $X$ , which is the sum of the two numbers of two fair dice turned up, is discrete, then what is the probability of sum of at least 4 and at most 8?

- (a)  $26/36$       (b)  $1/6$   
 (c)  $23/36$       (d)  $1/12$

Ans. (c)

$$4 \leq P(X = \text{sum of both dice}) \leq 8$$

$$P(4) + P(5) + P(6) + P(7) + P(8)$$

$$= \frac{3+4+5+6+5}{36} = \frac{23}{36}$$

End of Solution



# POSTAL PACKAGES

- CSE
- ESE
- GATE
- PSUs
- SSC-JE
- RRB-JE
- UPPSC-AE
- BPSC-AE
- MPSC
- Other State Engineering Exams

## Salient Features of Postal Study Package

Our Postal Book Packages cater to the needs of college-going students, working professionals, and individuals unable to join classroom courses. These books, offered by MADE EASY, are designed to be compact, comprehensive, and easily understandable. We have put our efforts to ensure error-free content, incorporating smart and shortcut techniques specifically tailored for solving numerical problems.

- **Complete syllabus coverage aligned with latest pattern/syllabus.**
- **Detailed theory and practice exercises.**
- **Latest and updated study material**
- **Step by step solutions**
- **Ample no. of practice questions with PYQs.**
- **Emphasis on technical and non technical sections both.**
- **Subject-wise theory objective and conventional practice sets.**
- **Proven track record of student success.**

For online purchase, visit :

[www.madeeasypublications.org](http://www.madeeasypublications.org) | Helpline : 8860378004

For offline purchase, visit in-person at any MADE EASY center.  
Books will be sent to your provided address.



Scan to enroll

Address : 44-A/4, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016

9021300500

[www.madeeasypublications.org](http://www.madeeasypublications.org)

**Q.123** A bag contains 7 green and 5 yellow balls. Two balls are selected at random, one at a time. What is the probability that the two balls are of different colors, if the selection is made with replacement?

- (a)  $5/12$  (b)  $37/72$   
(c)  $5/72$  (d)  $35/72$

Ans. (d)

$$\begin{array}{|c|} \hline 7G \\ \hline 5Y \\ \hline \end{array} \Rightarrow \frac{G}{12} \times \frac{Y}{12} + \frac{YG}{12 \times 12} = \frac{35 \times 2}{12 \times 12} = \frac{35}{72}$$

End of Solution

**Q.124** If the events A and B are such that  $P(A) = 0.6$ ,  $P(B) = 0.2$  and  $P(A \cup B) = 0.7$ , then  $P(B | A)$  is

- (a)  $1/4$  (b)  $1/6$   
(c)  $2/3$  (d)  $1/7$

Ans. (b)

$$P(B|A) = \frac{P(A \cap B)}{P(A)} = \frac{0.1}{0.6} = \frac{1}{6}$$

$$P(A \cup B) = P(A) + P(B) - P(A \cap B)$$

$$0.7 = 0.6 + 0.2 - P(A \cap B)$$

$$P(A \cap B) = 0.1$$

End of Solution

**Q.125** If  $X \sim \text{Binomial} \left( 16, \frac{1}{2} \right)$ , then what is the variance of the random variable?

- (a) 8 (b) 4  
(c) 2 (d) 6

Ans. (b)

$$\left. \begin{array}{l} X \sim B(n, P) \\ X \sim B(16, 1/2) \end{array} \right\} n = 16$$

$$p = \frac{1}{2}$$

$$q = 1 - \frac{1}{2} = \frac{1}{2}$$

$$\text{Variance} = npq$$

$$= 16 \times \frac{1}{2} \times \frac{1}{2} = 4$$

End of Solution

**Q.126** If  $X \sim N(15, 6.25)$ , then what is the value of  $X$ , which is 1.2 standard deviations below the mean?

- (a) 12 (b) 15  
(c) 16 (d) 14

Ans. (a)

$$\begin{aligned} X &\sim N(15, 6.25) \\ \mu &= 15, \sigma^2 = 6.25 \\ \sigma &= 2.5 \\ X &= \mu - 1.2\sigma \\ &= 15 - 1.2 \times 2.5 \\ &= 15 - 3 = 12 \end{aligned}$$

End of Solution

**Q.127** If the height  $h$  in metres of a swing above the ground at time  $t$  seconds is given by  $h = 2 - 1.5 \sin t$  for  $0 < t < 3$ , then the maximum height of the swing is

- (a) 4 m (b) 1.79 m  
(c) 2 m (d) 6 m

Ans. (c)

$$h = 2 - 1.5 \sin t \quad 0 < t < 3$$

From  $h_{\max}$ ,

minimum value of  $\sin t = 0$  in  $0 < t < 3$

$$\begin{aligned} h_{\max} &= 2 - 1.5 \times 0 \\ &= 2 \end{aligned}$$

End of Solution

**Q.128** Consider the following statements regarding rank in terms of column vectors:

- The rank  $r$  of a matrix  $A$  equals the maximum number of linearly independent column vectors of  $A$ .
- The matrix  $A$  and its transpose  $A^T$  have the same rank.
- Consider  $p$  vectors each having  $n$  components; if  $n < p$ , then these vectors are linearly independent.

Which of the above statements is/are **not** correct?

- (a) 1 and 2 (b) 1 and 3  
(c) 2 and 3 (d) 3 only

Ans. (d)

$$\begin{aligned} A &= [ \ ]_{m \times n} \\ \rho(A) &= \text{number of linearly independent column} \\ \rho(A) &= \rho(A^T) \end{aligned}$$

Statement 3 is wrong.

End of Solution



Ans. (c)

$$r(t) = at\hat{i} + bt\hat{j} + ct\hat{k} + c$$

End of Solution

**Q.132** Consider the following statements regarding properties of eigenvalues:

1. Any square matrix  $A$  and its transpose  $A^T$  have the same eigenvalues.
2. The eigenvalues of a triangular matrix are just the diagonal elements of the matrix.
3. The sum of the eigenvalues of a matrix is the product of the elements of the principal diagonal.

Which of the above statements are correct?

- |                  |                  |
|------------------|------------------|
| (a) 1 and 2 only | (b) 2 and 3 only |
| (c) 1 and 3 only | (d) 1, 2 and 3   |

Ans. (a)

Statement 1 and 2 are correct.

End of Solution

**Q.133** Let  $r$  be the rank for the coefficient matrix  $A$  of the system of homogeneous linear equations having  $m$  number of equations and  $n$  number of variables.

1. If  $r < n$ , then the equations have  $(n - r)$  linearly independent solutions.
2. If  $m < n$ , the number of solutions is finite.
3. If  $m = n$ , then such solution is non-trivial solution.

Which of the above statements is/are **not** correct?

- |             |             |
|-------------|-------------|
| (a) 1 and 2 | (b) 2 only  |
| (c) 1 only  | (d) 2 and 3 |

Ans. (d)

$$[A]_{m \times n}$$

$$AX = 0$$

1. If  $r < n \Rightarrow n - r \Rightarrow$  linearly independent solution
2.  $m < n \Rightarrow$  Number of solution in infinite
3.  $m = n \Rightarrow k$

End of Solution

**Q.134** Consider the following statements regarding atomic bonds:

1. If two ions with same ionization potential form a bond, then this bond will most probably be ionic.
2. With the increase in the difference of the ionization potentials, the bond will be more and more ionic.
3. If the atom or molecule has completely filled outer shell, then the bonding between the atoms or molecules will be a primary bond at the time of solidification.

Which of the above statements is/are correct?

- |             |             |
|-------------|-------------|
| (a) 1 and 2 | (b) 2 only  |
| (c) 3 only  | (d) 2 and 3 |

Ans. (b)

Same ionization potential → Covalent bond

Completely filled outer sheet (e.g. : Inert gases) → Vander Wall's force → Secondary bond.

End of Solution

Q.135 Match the following Lists:

List-I (Metal)

List-II (Resistivity)

- |       |  |
|-------|--|
| P. Li | 1. $4.34 \times 10^{-8} \Omega\text{-m}$ |
| Q. Na | 2. $1.56 \times 10^{-8} \Omega\text{-m}$ |
| R. Cu | 3. $8.33 \times 10^{-8} \Omega\text{-m}$ |
| S. Ag | 4. $1.47 \times 10^{-8} \Omega\text{-m}$ |

Select the correct answer using the code given below.


- |     | P | Q | R | S |
|-----|---|---|---|---|
| (a) | 3 | 2 | 4 | 1 |
| (b) | 3 | 1 | 4 | 2 |
| (c) | 3 | 1 | 2 | 4 |
| (d) | 3 | 2 | 1 | 4 |

Ans. (c)

Silver is the best conductor followed by copper among all these metals.

End of Solution

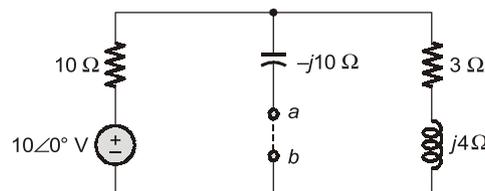Q.136 For the network given below, what are the Norton's current and Thévenin's voltage at the terminals  $a$  and  $b$ ?




$$(a) I_{ab} = \left[ \frac{10\angle 0^\circ}{10 + \frac{(-j10)(3-j4)}{3+j6}} \right] \left( \frac{3-j4}{3+j6} \right) \text{A and } V_{ab} = \frac{3-j4}{13+j4} (10\angle 0^\circ) \text{V}$$

$$(b) I_{ab} = \left[ \frac{10\angle 0^\circ}{10 + \frac{(-j10)(3+j4)}{3+j6}} \right] \left( \frac{3-j4}{3+j6} \right) \text{A and } V_{ab} = \frac{3-j4}{13+j4} (10\angle 0^\circ) \text{V}$$

$$(c) I_{ab} = \left[ \frac{10\angle 0^\circ}{10 + \frac{(-j10)(3-j4)}{3-j6}} \right] \left( \frac{3-j4}{3-j6} \right) \text{A and } V_{ab} = \frac{3+j4}{13-j14} (10\angle 0^\circ) \text{V}$$



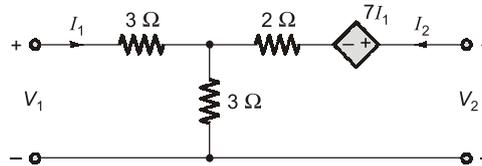**Q.138** What are the Z-parameters for the network given below?



- (a)  $Z_{11} = 6$ ;  $Z_{12} = 3$ ;  $Z_{21} = 10$ ;  $Z_{22} = 5$   
 (b)  $Z_{11} = 5$ ;  $Z_{12} = 10$ ;  $Z_{21} = 3$ ;  $Z_{22} = 6$   
 (c)  $Z_{11} = 6$ ;  $Z_{12} = 10$ ;  $Z_{21} = 10$ ;  $Z_{22} = 5$   
 (d)  $Z_{11} = 6$ ;  $Z_{12} = 3$ ;  $Z_{21} = 3$ ;  $Z_{22} = 5$

**Ans. (a)**

Write KVL equation input port loop

$$V_1 = 3I_1 + 3(I_1 + I_2)$$

$$V_1 = 6I_1 + 3I_2 \quad \dots(i)$$

Write KVL equation in output port loop.

$$V_2 = 7I_1 + 3(I_1 + I_2) + 2I_2$$


$$V_2 = 10I_1 + 5I_2 \quad \dots(ii)$$

$$[Z] = \begin{bmatrix} 6 & 3 \\ 10 & 5 \end{bmatrix}$$

$$Z_{11} = 6\Omega, Z_{12} = 3\Omega, Z_{21} = 10\Omega, Z_{22} = 5\Omega$$

End of Solution

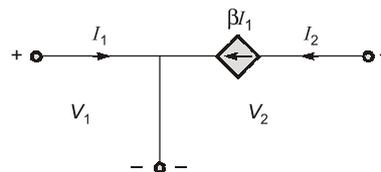**Q.139** The simplified model of a bipolar junction transistor for small signals is shown in the figure below:



What are the  $h$ -parameters?

- (a)  $h_{11} = h_{22} = h_{21} = 0$  and  $h_{12} = \beta$     (b)  $h_{22} = h_{12} = h_{21} = 0$  and  $h_{11} = \beta$   
 (c)  $h_{11} = h_{12} = h_{21} = 0$  and  $h_{22} = \beta$     (d)  $h_{11} = h_{12} = h_{21} = 0$  and  $h_{22} = \beta$

**Ans. (c)**

$$V_1 = 0 \cdot I_1 + 0 \cdot V_2$$

$$I_2 = \beta I_1 + 0 \cdot V_2$$

Comparing it with stable equations

$$h_{11} = h_{12} = h_{21} = 0$$

and  $h_{22} = \beta$

End of Solution

**Q.140** Which one of the following statements is **not** correct regarding mutual inductance and transformers?

- (a) When the assumed currents both enter or both leave a pair of coupled coils by the dotted terminals, the signs on the  $M$ -terms will be the same as the signs on the  $L$ -terms.
- (b) When one current enters by a dotted terminal while the other leaves by a dotted terminal, the signs on the  $M$ -terms will be opposite to the signs on the  $L$ -terms.
- (c) The term 'close coupling' is used to describe the case where most of the flux links the coils, either by way of a magnetic core to contain the flux or by interleaving the turns of the coils directly over one another. Coils placed side-by-side without a core are loosely coupled and have correspondingly high values of  $k$ .
- (d) If all the flux links the coil without any leakage flux, then  $k = 1$ . On the other extreme, the coil axes may be oriented such that no flux from one can induce a voltage in the other, which results in  $k = 0$ .

**Ans. (c)**

Close coupling means high flux linkage. However the statement says loosely coupled coils have high value of  $K$ . So, (c) is incorrect.

End of Solution

**Q.141** Consider the following statements regarding factors affecting the capacitance :

- 1. The area of the plates is directly proportional to the charge; the larger the plate area, the more electric charges that can be stored.
- 2. The longer the distance between the two plates, the stronger the produced electric field that will increase the ability to store charges. Therefore, the distance between the two plates is directly proportional to the capacitance.
- 3. Different insulating materials will have different impacts on the capacitance. The dielectric constant is directly proportional to the capacitance.

Which of the above statements is/are correct?

- (a) 2 and 3
- (b) 1 and 2
- (c) 1 and 3
- (d) 3 only

**Ans. (c)**

$$C = \frac{A\epsilon}{d}$$

$$C \propto \frac{1}{d}$$

So, statement-2 is incorrect.

End of Solution

# MADE EASY students top in ESE 2025

**4 Streams 4 Toppers**  
all 4 MADE EASY Students

**39 selections**  
in Top 10

**434 selections out of**  
**458 Vacancies (95% Selections)**

<b>CE</b> 9 in Top 10	<b>1</b> AIR MOHAMMAD SHAQUIB Live Online Foundation Course	<b>2</b> AIR PRAKHAR SHRI Classroom Foundation Course	<b>3</b> AIR ARJUN SHARMA Mains Online Course	<b>4</b> AIR BOLLA U NANDAN Classroom Foundation Course	<b>5</b> AIR KESHAV Test Series & IGP	<b>7</b> AIR TUSHAR AGGARWAL Classroom Foundation Course	<b>8</b> AIR AYUSH JAIN Classroom Foundation Course	<b>9</b> AIR ADITYA P SINGH Test Series & IGP	<b>10</b> AIR PUSHPENDRA RATHORE Test Series & IGP	
<b>ME</b> 10 in Top 10	<b>1</b> AIR NIMESH CHANDRA Classroom Foundation Course	<b>2</b> AIR ASHOK KUMAR Classroom Foundation Course	<b>3</b> AIR HARI SINGH Mains Online Course	<b>4</b> AIR SIDDESH RAO GS Online Course	<b>5</b> AIR GOLLANGI SATEESH Mains Online Course	<b>6</b> AIR AVINASH VERMA Mains Online Course	<b>7</b> AIR PRASHANT SINGH Mains Offline Course	<b>8</b> AIR MONU KUMAR Classroom Foundation Course	<b>9</b> AIR NIKHIL KUMAR SAHA Test Series & IGP	<b>10</b> AIR AMIT KUMAR SINGH Classroom Foundation Course
<b>EE</b> 10 in Top 10	<b>1</b> AIR RAJAN KUMAR Classroom Foundation Course	<b>2</b> AIR VISHNU SAINI Live Online Foundation Course	<b>3</b> AIR OMPRAKASH RAJPUT Classroom Foundation Course	<b>4</b> AIR TUSHAR CHAUDHARY Classroom Foundation Course	<b>5</b> AIR RAM KUMAR Test Series & IGP	<b>6</b> AIR PUNIT MEENA Classroom Foundation Course	<b>7</b> AIR JYOTI K. PANDA Classroom Foundation Course	<b>8</b> AIR D A SAI RAM REDDY Test Series & IGP	<b>9</b> AIR DHURUV KAWAT Classroom Foundation Course	<b>10</b> AIR AKSHIT PARASHARI Live Online Foundation Course
<b>E&amp;T</b> 10 in Top 10	<b>1</b> AIR UTKARSH PATHAK Live Online Foundation Course	<b>2</b> AIR RAJESH TIWARI Live Online Foundation Course	<b>3</b> AIR PRASHANT LAVANIA Classroom Foundation Course	<b>4</b> AIR PRADEEP SHUKLA Mains Online Course	<b>5</b> AIR ASHISH SINGH PATEL Classroom Foundation Course	<b>6</b> AIR TANYA TYAGI Mains Online Course	<b>7</b> AIR PALAK MISHRA Mains Online Course	<b>8</b> AIR HAYAT ALI Classroom Foundation Course	<b>9</b> AIR VIDHU SHREE Live Online Foundation Course	<b>10</b> AIR RAM PAL SINGH Classroom Foundation Course

# MADE EASY students top in GATE 2025

**5 All India Rank 1**  
(CE, ME, IN, ES & EE)

**45 Selections**  
in Top 10

**399 Selections**  
in Top 100

<b>1</b> AIR CE Abhay Singh Classroom Course	<b>1</b> AIR ME Rajneesh Bijarniya Classroom Course	<b>1</b> AIR EE Pradip Chauhan Test Series	<b>1</b> AIR IN Kailash Goyal Classroom Course	<b>1</b> AIR ES Yash Jain Classroom Course	<b>2</b> AIR CE Harshvardhan Singh Classroom Course	<b>2</b> AIR ME Gollangi Sateesh Online Course	<b>2</b> AIR EE Kailash Goyal Classroom Course	<b>2</b> AIR EC Ankush Philip John Postal Package & Test Series	
<b>2</b> AIR IN S. Bhattacharya Test Series	<b>2</b> AIR ES Jitesh Choudhary Classroom Course	<b>2</b> AIR ES Tarun Yadav Classroom Course	<b>3</b> AIR CE Pankaj Meena Classroom Course	<b>3</b> AIR ME Nimesh Chandra Classroom Course	<b>3</b> AIR PI Aditya Kr. Prasad Classroom Course	<b>3</b> AIR XE Rohan Kr. Biswal Test Series	<b>5</b> AIR CE Kartik Pokhriyal Classroom Course		
<b>5</b> AIR PI Kuldeep Singh Naruka Classroom Course	<b>5</b> AIR IN Sachin Yadav Test Series	<b>5</b> AIR EC M. M. Nafeez Test Series	<b>5</b> AIR ES Sachin Kumar Classroom Course	<b>6</b> AIR PI Kaushal Kr. Kaushik Online Course	<b>6</b> AIR CE Shivnand Chaurasia Online Course	<b>6</b> AIR CE Nimish Upadhyay Online Course	<b>6</b> AIR EE Puneet Soni Test Series	<b>6</b> AIR EE Shivam Kr. Gupta Test Series	
<b>6</b> AIR EC Pentela J. Bhavani Test Series	<b>6</b> AIR IN Utkarsh P. Patil Classroom Course	<b>7</b> AIR PI Waleed Shaikh Test Series	<b>7</b> AIR ME Abhinn Online Course	<b>7</b> AIR IN Dev J. Patel Test Series	<b>7</b> AIR ES Ankit Kumar Classroom Course	<b>8</b> AIR ME Goutam Kumar Test Series	<b>9</b> AIR CE Tarun Yadav Classroom Course	<b>9</b> AIR CS Omhari Test Series	<b>9</b> AIR EC Chilukuri S. Charan Test Series
<b>9</b> AIR XE Apar Harsh Chandra Classroom Course	<b>10</b> AIR CE Adnan Quasain Classroom Course	<b>10</b> AIR CE Rahul Singh Online Course	<b>10</b> AIR ME Ashutosh Kumar Classroom Course	<b>10</b> AIR ME Jetti Ganateja Test Series	<b>10</b> AIR ME Muhammed Sinan K Test Series	<b>10</b> AIR ME Pitchika Kr. Vasu Online Course	<b>10</b> AIR PI M Gopu Ganesh Test Series	<b>10</b> AIR EE Neelava Mukherjee Postal Package & Test Series	

Course-wise details of "top 100 rank holders of GATE 2025" and "selected candidates of ESE 2025 from MADE EASY" are available on our website.

**Delhi Centre :** 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016 • Ph: 9021300500

**MADE EASY Centres :** Delhi | Bhopal | Hyderabad | Jaipur | Pune

[www.madeeasy.in](http://www.madeeasy.in)



At  $t = 3\tau$ ,

$$V_C = E e^{-3} = 0.05 E = 5\% \text{ of } E$$

At  $t = 4\tau$ ,

$$V_C = E e^{-4} = 0.0187 E = 1.87\% \text{ of } E$$

At  $t = 5\tau$ ,

$$V_C = E e^{-5} = 0.0007 E = 0.67\% \text{ of } E$$

End of Solution

**Q.144** A single-range laboratory-type potentiometer has an 18-step dial switch where each step represents 0.1 V. The dial resistors are 10  $\Omega$  each. The slide wire of the potentiometer is circular and has 11 turns and a resistance of 1  $\Omega$  per turn. The slide wire has 100 divisions and interpolation can be done to one-fourth of a division. What is the measuring range of the potentiometer?

- (a) 1.1 V (b) 0.25 V  
(c) 1.91 V (d) 0.01 V

**Ans. (c)**

18-step dial, each step = 0.1 V

Maximum dial voltage =  $18 \times 0.1 = 1.8$  V

Slide wire resistance,

$$11 \text{ turns} = 11 \Omega$$

$$\text{Total dial resistance} = 18 \times 10 = 180 \Omega$$

$$\text{Voltage per ohm} = \frac{0.1}{10} = 0.01 \text{ V}/\Omega$$

$$\text{Resistance per division} = \frac{1\Omega}{100} = 0.01\Omega$$

Since interpolation is upto  $\frac{1}{4}$  division

$$\frac{0.01}{4} = 0.0025 \Omega$$

$$\begin{aligned} \text{Smallest voltage} &= 0.0025 \times 0.01 \\ &= 0.000025 \text{ V} \end{aligned}$$

Very small indicates high resolution

$$\begin{aligned} \text{Total range} &= \text{Dial range} + \text{Slide wire voltage} \\ &= 1.8 + 11 \times 0.01 \\ &= 1.91 \text{ V} \end{aligned}$$

End of Solution

**Q.145** Consider the following statements regarding Maxwell's bridge:

1. Maxwell's bridge is limited to measurement of low  $Q$  inductors.
2. The final balance equations of Maxwell's bridge are dependent of frequency.
3. The balance equation of Maxwell's bridge is dependent of losses associated with the inductor.

Which of the above statements is/are correct?

- (a) 2 and 3 (b) 2 only  
(c) 1 only (d) 1 and 3

Ans. (c)

- Maxwell's bridge works best for medium  $Q(1 - 10)$  coils. It is not suitable for high  $Q$  coils (Hay's bridge is used there). So effectively it is used for relatively low  $Q$  inductors.
- One major advantage of Maxwell bridge is that the balance condition does not depend on frequency.

End of Solution

Q.146 Match the following Lists:

List-I (Name of the bridge)

List-II (Inductance equation)

- |                                |   |
|--------------------------------|---|
| P. Maxwell's inductance bridge | 1. $L_1 = \frac{R_2 R_3 C_4}{1 + \omega^2 R_4^2 C_4^2}$ |
| Q. Hay's bridge                | 2. $L_1 = C \frac{R_3}{R_4} [r(R_2 + R_4) + R_2 R_4]$   |
| R. Anderson's bridge           | 3. $L_1 = L_2 \frac{R_3}{R_4}$                          |
| S. Owen's bridge               | 4. $L_1 = R_2 R_3 C_4$                                  |

Select the correct answer using the code given below.

- |     | P | Q | R | S |
|-----|---|---|---|---|
| (a) | 3 | 1 | 2 | 4 |
| (b) | 4 | 1 | 3 | 2 |
| (c) | 3 | 2 | 4 | 1 |
| (d) | 3 | 2 | 1 | 4 |

Ans. (a)

End of Solution

Q.147 The coil of a moving-coil voltmeter is 40 mm long and 30 mm wide, and has 100 turns on it. The control spring exerts a torque of  $240 \times 10^{-6}$  N-m when the deflection is 100 divisions on full scale. If the flux density of the magnetic field in the air gap is  $1 \text{ Wb/m}^2$ , what is the resistance that must be put in series with the coil to give one volt per division? (The resistance of the voltmeter coil may be neglected)

- (a)  $120 \times 10^3 \Omega$  (b)  $50 \times 10^3 \Omega$   
(c)  $5 \times 10^3 \Omega$  (d)  $12 \times 10^3 \Omega$

Ans. (b)

- Given, Length,  $l = 40 \text{ mm} = 0.04 \text{ m}$   
Width,  $b = 30 \text{ mm} = 0.03 \text{ m}$   
Turn,  $N = 100$   
Flux density,  $B = 1 \text{ Wb/m}^2$



