



ESE 2022

**Preliminary
Examination**

**Detailed
Solution of
ELECTRONICS &
TELECOMMUNICATION
ENGINEERING**

Set-A

Scroll down



Corporate Office : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016

MADE EASY Centres : Delhi | Hyderabad | Jaipur | Lucknow | Bhopal | Bhubaneswar | Pune | Patna | Kolkata

9021300500

www.madeeasy.in



Electronics & Telecom Engg. Paper Analysis of ESE 2022 Preliminary Examination

Sl.	Subjects	Number of Questions
1	Materials Science	13
2	Electronic Devices and Circuits	6
3	Analog Circuits	6
4	Network Theory	13
5	Control Systems	15
6	Electromagnetic Theory	12
7	Measurements	14
8	Communication Systems	13
9	Advance Communications	15
10	Advance Electronics	6
11	Basic Electrical Engineering	7
12	Computer Organization	11
13	Signals and Systems	4
14	Digital Circuits	10
15	Microprocessors & Microcontrollers	5

UPSC ESE Prelims Exam 2022 E&T analysis by MADE EASY faculties

https://www.youtube.com/watch?v=Vjy_xS0Giq4



- Q.1 The atomic packing factor of a simple cubic structure is
- (a) 0.42 (b) 0.62
(c) 0.52 (d) 0.72

Ans. (c)

$$\text{Atomic packing factor} = \frac{\text{Sum of atomic volume in a unit cell}}{\text{Volume of a unit cell}}$$

$$\Rightarrow \text{APF} = \frac{N \times \frac{4}{3} \pi R^3}{a^3}$$

For simple Cubic,

$$N = 1$$
$$a = 2R$$

$$\therefore \text{APF} = \frac{1 \times \frac{4}{3} \pi R^3}{(2R)^3} = 0.52$$

End of Solution

- Q.2 For some solid materials, each atom possesses a permanent dipole moment by
- (a) virtue of incomplete cancellation of electron spin and/or orbital magnetic moments
(b) rotation and alignment with external field
(c) the presence of external field
(d) rotation in opposite direction with external field

Ans. (a)

Permanent dipole moment is due to incomplete cancellation of electron spin and/or orbital magnetic moments.

End of Solution

- Q.3 Which one of the following statements is **not** correct regarding laminates?
- (a) Paper reinforced laminates can be used in thickness ranging between 0.2 mm and 50 mm.
(b) Paper reinforced laminates are used in applications involving power frequencies and voltages up to 1 kV.
(c) Glass reinforced laminates make use of phenol formaldehyde as impregnant and adhesive.
(d) Asbestos reinforced laminates have higher electrical characteristics than paper reinforced laminates.

Ans. (c)

Fiberglass is used as impregnant.

End of Solution



ESE 2022

Mains Exclusive

Batches

**Conventional Question Practice
Programme with Main Test Series**

OFFLINE BATCHES

3rd Mar, 2022

ONLINE BATCHES

Direct **LIVE** from Offline Classes

3rd Mar, 2022

Course Duration :
80 to 90 days

Teaching Hours :
300 to 350 hours

Class Duration :
5 to 6 days (6-7 hrs per day)

Key Features

- In-depth discussion on conventional questions.
- Beneficial to develop numerical question solving techniques.
- Helps to improve answer writing & presentation skills.
- Discussion on probable questions.
- Updated Mains workbook with wide range of practice questions sets.
- Test series will be conducted on every Sunday in synchronization with the subjects.

Register online at : www.madeeasy.in

Corporate Office : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016

MADE EASY Centres : Delhi | Hyderabad | Jaipur | Lucknow | Bhopal | Bhubaneswar | Pune | Patna | Kolkata

📞 9021300500

🌐 www.madeeasy.in

- Q.4 Which one of the following statements is **not** correct regarding mercury?
- Mercury is a heavy silver white metal.
 - The specific weight of mercury is approximately 31.55 gm/cm^3 .
 - Mercury is the only metal which is liquid at room temperature.
 - The boiling point of mercury is approximately 357°C .

Ans. (b)

The specific weight of mercury is approx 13.6 g/cm^3 .

End of Solution

- Q.5 What is the value of interplanar spacing for (2 3 1) plane of an FCC structure whose atomic radius is 0.125 nm ?
- $d_{231} = 0.443 \text{ nm}$
 - $d_{231} = 0.343 \text{ nm}$
 - $d_{231} = 0.094 \text{ nm}$
 - $d_{231} = 0.194 \text{ nm}$

Ans. (c)

$$(h \ k \ l) = (2 \ 3 \ 1)$$

$$R = 0.125 \text{ nm}$$

For FCC,

$$a = 2\sqrt{2} R = 2\sqrt{2} \times 0.125 \text{ nm} = 0.353 \text{ nm}$$

$$d_{231} = \frac{a}{\sqrt{h^2 + k^2 + l^2}} = \frac{0.353 \text{ nm}}{\sqrt{4 + 9 + 1}}$$

$$d_{231} = 0.094 \text{ nm}$$

End of Solution

- Q.6 When a bar is subjected to a rapidly alternating magnetic field, there is rapidly alternating magnetic field, there is rapid extension and contraction in the length of the bar. This phenomenon is known as
- hysteresis
 - saturation magnetization
 - magnetostriction
 - diamagnetism

Ans. (c)

Magnetostriction : Changes in the dimensions of magnetic materials when they are subjected to an alternating field.

End of Solution

- Q.7 The material composed of C_{60} molecule that contains sixty carbon atoms in a network of sp^2 bonding which form a spherical structure, is known as
- buckminsterfullerene
 - haeckelite
 - carbon nanocone
 - carbon nanotube

Ans. (a)

A single molecule of buckminsterfullerene contains sixty carbon atoms (C_{60}) in a network of sp^2 bonding forming a hollow spherical shape.

End of Solution

- Q.8** The electronic properties of the nanotube could be changed between metallic and semiconducting simply by varying
- (a) the tube length
 - (b) the tube diameter
 - (c) the tube perimeter
 - (d) the tube width

Ans. (b)

The properties of CNT depends upon diameter of nanotube.

End of Solution

- Q.9** A very low temperature, where resistivity of certain materials abruptly plunges from a finite value to one that is virtually zero and remains there upon further cooling, is called
- (a) knee temperature
 - (b) ambient temperature
 - (c) critical temperature
 - (d) Curie temperature

Ans. (c)

In superconducting materials resistivity becomes virtually zero below critical temperature.

End of Solution

- Q.10** Superconducting materials are used in which of the following application?

1. Magnetic Resonance Imaging (MRI).
2. Magnetic Resonance Spectroscopy (MRS).
3. High-speed switching and signal transmission for computers.
4. High-speed magnetically levitated trains.

Select the correct answer using the code given below:

- (a) 1 and 2 only
- (b) 3 and 4 only
- (c) 2, 3 and 4 only
- (d) 1, 2, 3 and 4

Ans. (d)

End of Solution

- Q.11** Consider the following statements:

1. Some materials are capable of absorbing energy and then reemitting visible light in a phenomenon called luminescence.
2. If the delay time between absorption and reemission is much less than one second, the phenomenon is termed as phosphorescence.
3. If the delay time between absorption and reemission is much greater than one second, the phenomenon is termed as fluorescence.

Which of the above statements is/are **not** correct?

- (a) 1 only
- (b) 2 only
- (c) 1 and 2
- (d) 2 and 3

Ans. (d)

Phosphorescence → Delayed emission.

Fluorescence → Immediate emission.

End of Solution

Q.12 Which of the following are **not** the production methods for carbon nanotubes?

1. Electric arc discharge method
2. Laser vaporization method
3. Czochralski method
4. Metallization method

Select the correct answer using the code given below:

- (a) 1 and 2 (b) 2 and 3 only
(c) 3 and 4 only (d) 2, 3 and 4

Ans. (c)

Czochralski method is for production of semiconductors.

End of Solution

Q.13 Which one of the following statements is correct regarding induction motor?

- (a) If the stator voltage is changed the torque will not change.
(b) The motor has no starting torque.
(c) At high slip (speed), the torque is inversely proportional to square of the slip.
(d) At low slip (speed), the torque is directly proportional to the slip.

Ans. (d)

$$T \propto V^2$$

At high slip (speed),
the torque is inversely proportional to slip.

At low slip (speed),
the torque, $T \propto$ slip

End of Solution

Q.14 What is the coil pitch to eliminate the 5th harmonic in the induced e.m.f. of a synchronous generator?

- (a) 36° (b) 180°
(c) 144° (d) 160°

Ans. (a)

$$\alpha_n = \frac{180}{n}$$

For 5th harmonics,

$$\alpha_5 = \frac{180}{5} = 36^\circ$$


End of Solution

- Q.15** Which one of the following represents a single element such as a voltage source or a resistor?
 (a) Branch (b) Node
 (c) Loop (d) Circuit

Ans. (a)

End of Solution

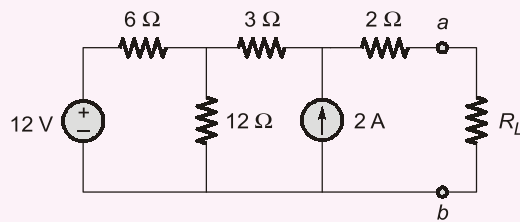- Q.16** What is the value of the maximum power transferred to the load resistor R_L in the given circuit?




- (a) 11.43 W (b) 12.43 W
 (c) 13.44 W (d) 14.44 W

Ans. (c)

Maximum power transferred to load

$$P_{\max} = \frac{V_{th}^2}{4R_{th}}$$


$R_{th} \rightarrow$

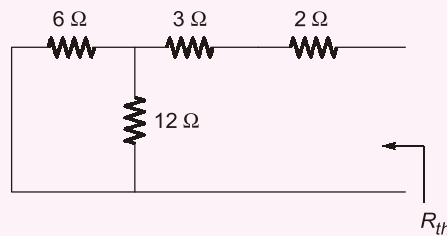

$$R_{th} = (6 \parallel 12) + 3 + 2$$


$$R_{th} = 9 \Omega$$

$V_{th} \rightarrow$

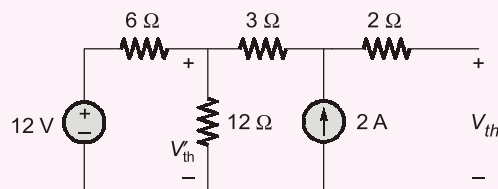

$$V_{th}' = \frac{12 \times 12}{18} = 8 \text{ V}$$

$$R_{th}' = 6 \parallel 12 = 4 \Omega$$

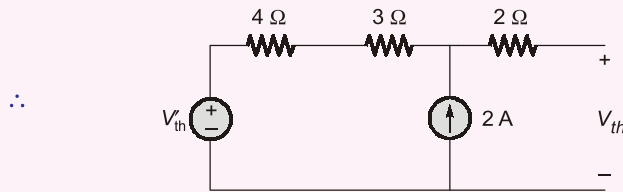


$$V_{th} = 22 \text{ volt}$$

$$P_{max} = \frac{22 \times 22}{4 \times 9} = 13.44 \text{ Watts}$$

End of Solution

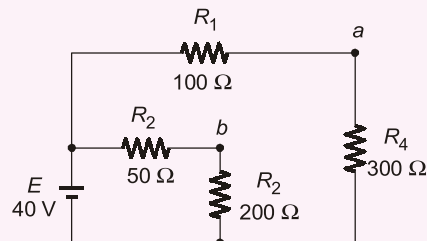Q.17 In the figure given below, the value of voltage drop across the resistor R_1 is



- (a) 100 V
(b) 10 V
(c) 1 V
(d) 0.1 V

Ans. (b)
Using voltage division rule,

$$V_{R1} = \frac{40 \times R_1}{R_1 + R_4}$$

$$= \frac{40 \times 100}{100 + 300}$$

$$V_{R1} = 10 \text{ volt}$$

End of Solution

Q.18 Which one of the following is a merit of nuclear power plant?

- (a) Large quantity of fuel storage facility is required in nuclear power plant
(b) The maintenance cost of hydro plants is very low as compared to that of steam and nuclear plants
(c) As compared to thermal plant, the space required for nuclear power plant is less
(d) The initial cost of nuclear power plant is higher as compared to that of the other types of power plants

Ans. (c)
The space required for nuclear power plant is less as compared to thermal plant.

End of Solution

Q.19 Which one of the following is **not** a part of the nuclear reactor?

- (a) Moderator (b) Biological shield
(c) Economizer (d) Reflector

Ans. (c)

End of Solution

Q.20 The efficiency of a nuclear plant is

- (a) 48% (b) 35%
(c) greater than 50% (d) less than 30%

Ans. (b)

The efficiency of a nuclear plant is 35%.

End of Solution

Q.21 The voltage induced in a coil by a changing flux will be of such a polarity that if a current could flow as a result of that induced voltage, the flux established by that current would oppose the causing or original flux change. It is known as

- (a) Faraday's law (b) Lenz's law
(c) Biot-Savart law (d) Ampere's circuital law

Ans. (b)

End of Solution

Q.22 The measure of a coil's ability to produce flux is called

- (a) electromotive force (b) magnetic lines of force
(c) magnetomotive force (d) magnetism

Ans. (c)

In a magnetic circuit, the measure of a coil's ability to produce flux is called as magnetomotive force.

End of Solution

Q.23 Which one of the following temperatures exists for the magnetic moments of a ferromagnetic material which become sufficiently diverse in orientation that the material becomes nonmagnetic?

- (a) Room temperature (b) Absolute temperature
(c) Curie temperature (d) Ambient temperature

Ans. (c)

At Curie temperature all the dipoles become randomly oriented and ferromagnetic material becomes paramagnetic.

End of Solution

- Q.24** Which one of the following statements is correct regarding Leclanche cell?
- The resulting cell voltage for Leclanche cell is 3.5 V.
 - Zinc powder acts as cathode in Leclanche cell.
 - Manganese dioxide acts as anode in Leclanche cell
 - A coal/manganese dioxide cathode, a zinc anode and ammonium chloride solution as electrolyte are used in Leclanche cell.

Ans. (d)

End of Solution

- Q.25** Which one of the following statements is **not** correct regarding carrier lifetime in semiconductors?
- Carrier lifetime ranges from nanoseconds to hundreds of microseconds.
 - On an average, a hole (an electron) will exist for τ_p sec before recombination.
 - τ_n is the time, it takes the total concentration to fall to approximately 63% of its initial value.
 - τ_p is the time, it takes the injected concentration to fall to approximately 37% of its initial value.

Ans. (c)

Let $\delta n(t)$ is the injected carrier concentration

$$\delta n(t) = \delta n(0) e^{-t/\tau_n}$$

$\delta n(0)$ is the initial injected carrier concentration,

At $t = \tau_n$

$$\delta n(t) = \delta n(0) e^{-1}$$

$$\delta n(\tau_n) = 0.37[\delta n(0)]$$

$$\delta n(\tau_n) \neq 0.63[\delta n(0)]$$

End of Solution

- Q.26** At what condition does the Fermi energy level (E_f) lie exactly between the band gap for intrinsic semiconductor?
- The effective masses of a hole and a free electron are the same
 - The effective mass of a free electron is less than the effective mass of a hole
 - The effective mass of a free electron is greater than the effective mass of a hole
 - The effective mass of a hole is always in the centre of the forbidden energy band

Ans. (a)

$$E_i = E_{\text{mid gap}} + \frac{3}{4} kT \ln \left(\frac{m_p^*}{m_n^*} \right)$$

$$m_p^* = m_n^*$$

$$\ln(1) = 0$$

$$\therefore E_i = E_{\text{mid gap}}$$

End of Solution

- Q.27** In resistance levels, the AC or the dynamic resistance of a $p-n$ junction diode is defined by
- a point on the characteristics
 - a tangent line at the Q-point in graphical determination
 - the straight line between limits of operation
 - the ratio of current through load to voltage across load

Ans. (b)


AC or dynamic resistance is calculated from $V-I$ characteristic.

$$\text{Slope} = \frac{dI}{dV}$$

$$\therefore r = \frac{1}{\text{Slope}} = \frac{dV}{dI}$$

Dynamic resistance is the reciprocal of the slope of the tangent line at the Q-point in $V-I$ characteristic.

Hence, the correct answer is (b).

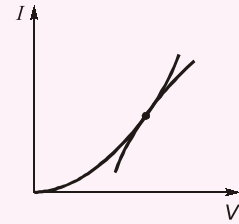

End of Solution

- Q.28** Consider the following statements regarding comparison of FET with BJT:
- BJT is less noisy than FET.
 - FET is current-controlled device, whereas BJT is voltage-controlled device.
 - FETs are more temperature stable compared to BJTs.
 - FETs are simple to fabricate and occupy less area on the single chip.

Which of the above statements are correct?

- 1 and 2
- 1 and 3
- 3 and 4
- 1 and 4

Ans. (c)

FET is less noisy than BJT.

FET is voltage-controlled device.

End of Solution

- Q.29** Which one of the following is correct regarding stability factor with standard notations?

(a) $S(I_{CO}) = \frac{\Delta I_C}{\Delta I_{CO}}$

(b) $S(I_{CO}) = \frac{\Delta I_{CO}}{\Delta I_C}$

(c) $S(V_{BE}) = \frac{\Delta I_C}{\Delta I_{CO}}$

(d) $S(V_{BE}) = \frac{\Delta I_C}{\Delta \beta}$

Ans. (a)

Stability factor, $S = \frac{\partial I_C}{\partial I_{CO}} = \frac{\Delta I_C}{\Delta I_{CO}}$

End of Solution

Q.30 Which one of the following is a transfer characteristic of NMOS with standard notations?

- (a) $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$ (b) $I_D = I_{DSS} \left(1 - \frac{V_P}{V_{GS}}\right)^2$
 (c) $I_D = k(V_{GS} - V_T)^2$ (d) $I_D = k(V_T + V_{GS})^2$

Ans. (c)

Transfer characteristics specifies the input-output relationship of a device.

End of Solution

Q.31 Which one of the following statements is correct for n -channel or p -channel MOSFET?

- (a) Drain resistance of MOSFET is very larger than JFET.
 (b) Transconductance and inter-electrode capacitances have comparable values for the two types of devices.
 (c) Input resistance and feedback resistance are very smaller than JFET.
 (d) Input resistance and feedback resistance are comparable to JFET.

Ans. (b)

Input resistance of MOSFET is greater than input resistance of JFET.

$$R_i(\text{MOSFET}) \gg R_i(\text{JFET})$$

Drain resistance of JFET is greater than drain resistance of MOSFET.

$$R_d(\text{JFET}) > R_d(\text{MOSFET})$$

$$g_m(\text{NMOS}) \simeq g_m(\text{PMOS})$$

End of Solution

Q.32 Which one of the following statements is **not** correct for typical h -parameter values for a transistor?

- (a) Input impedance is high in case of common emitter and common collector as compared to common base configuration.
 (b) Output conductance is low in case of common emitter and common collector as compared to common base configuration.
 (c) Reverse voltage gain is high in common collector as compared to common base and common emitter configuration.
 (d) Current gain is positive for common emitter and negative for common collector and common base configuration.

Ans. (b)

$$h_{oc} = h_{oe}$$

and

$$h_{ob} = \frac{h_{oe}}{1 + h_{fe}}$$

∴

$$h_{oc} = h_{oe} > h_{ob}$$

Hence, option (b) is the correct answer.

End of Solution



MADE EASY
India's Best Institute for IES, GATE & PSUs

Under the guidance of
Mr. B. Singh
CMD, MADE EASY GROUP



- Quality Teaching
- Well Planned Curriculum
- Systematic Subject Sequence
- Comprehensive Study Materials

Admission open in Foundation Courses

**GATE
2023**

**ESE 2023 +
GATE 2023**

- ✓ Classes by experienced & renowned faculties.
- ✓ Systematic subject sequence.
- ✓ Efficient teaching with comprehensive coverage.
- ✓ Concept practice through workbook solving.
- ✓ Regular performance assessment through class tests.
- ✓ Exam oriented learning ecosystem.
- ✓ Timely completion of syllabus.
- ✓ Similar teaching pedagogy in online & offline classes.
- ✓ Comprehensive & updated theory & practice books.

OFFLINE CLASSES

Special Discount to Ex. MADE EASY students in CLASSROOM COURSES :
50% OF FEE PAID
will be discounted (any course)

www.madeeasy.in

Regular Batches Commencement dates at Delhi Centre

CE & ME

- 23rd Feb, 2022 • 21st Mar, 2022
- 13th Apr, 2022 • 04th May, 2022 • 25th May, 2022

EE & EC

- 24th Feb, 2022 • 22nd Mar, 2022
- 14th Apr, 2022 • 05th May, 2022 • 26th May, 2022

CS

- 24th Feb, 2022 • 23rd Mar, 2022 • 06th May, 2022

CH

- 21st Feb, 2022 • 23rd Mar, 2022 • 11th May, 2022

Batches commencing in Mar, April & May at all centres of MADE EASY.
For more details, visit our website.

LIVE ONLINE CLASSES

Download the app now



Android



iOS

www.madeeasyprime.com

New Batches Commencement Dates

Facility to CONVERT ONLINE to OFFLINE

Morning Batches

- Medium : **Hinglish** | Time : **8:00 AM - 2:00 PM**
• CE: 8th Mar, 2022 • ME: 14th Feb & 8th Mar, 2022

Evening Batches

- Medium : **Hinglish** | Time : **6:00 PM - 10:00 PM**
• CE, ME, EE, EC : 8th Mar, 2022
• CH : 8th Mar, 2022

Evening Batches

- Medium : **English** | Time : **6:00 PM - 10:00 PM**
• CE : 17th Feb, 2022 & 8th Mar, 2022
• ME : 30th Jan, 2022 & 8th Mar, 2022
• EE, EC, IN : 8th Mar, 2022
• CS : 8th Mar, 2022

Corporate Office : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016

MADE EASY Centres : Delhi | Hyderabad | Jaipur | Lucknow | Bhopal | Bhubaneswar | Pune | Patna | Kolkata

☎ 9021300500

🌐 www.madeeasy.in

- Q.33** Which one of the following technologies consumes less power?
(a) Surface-mount technology (b) CMOS
(c) NMOS (d) PMOS

Ans. (b)
CMOS consumes less power

End of Solution

- Q.34** Which one of the following requires additional process steps in their fabrication?
(a) Thin film resistor (b) Epitaxial resistor
(c) Pinched resistor (d) Junction resistor

Ans. (a)

End of Solution

- Q.35** In monolithic integrated circuits, the concentration of acceptor atoms in the region between isolation islands will be
(a) much higher than in the p -type substrate
(b) much lesser than in the p -type substrate
(c) equal to the p -type substrate
(d) not equal to the p -type substrate

Ans. (a)

End of Solution

- Q.36** A circuit that amplifies the difference between two signals is called
(a) differential amplifier (b) operational amplifier
(c) buffer (d) level translator

Ans. (a)
A differential amplifier amplifies the difference between two signals.

End of Solution

- Q.37** The output of an LVDT is connected to a 5 V voltmeter through an amplifier whose amplification factor is 200. An output of 2 mV appears across the terminals of the LVDT when the core moves through a distance of 0.5 mm. The milli-voltmeter scale has 100 divisions and scale can read to 1/5 of a division. The sensitivity and the resolution of the instrument are respectively
(a) 400 mV/mm and 2.25×10^{-3} mm (b) 800 mV/mm and 2.25×10^{-3} mm
(c) 800 mV/mm and 1.25×10^{-3} mm (d) 400 mV/mm and 1.25×10^{-3} mm

Ans. (*)



$$S_{\text{LVDT}} = \frac{dV}{dx} = \frac{2}{0.5} = 4 \text{ mV/mm}$$

$$S_{\text{overall}} = S_{\text{LVDT}} \times A = 4 \times 200 = 800 \text{ mV/mm}$$

$$\text{Resolution} = \frac{V_{\text{min}}}{S_{\text{overall}}} = \frac{5}{100} \times \frac{1}{5} \times \frac{1}{800 \times 10^{-3}}$$

$$= 0.0125 \text{ mm} = 12.5 \times 10^{-3} \text{ mm}$$

End of Solution

- Q.38** The coil of a recording ammeter is 65 mm long and 25 mm wide. The rated current of the coil is 10 mA. The flux density in the air gap is 0.0046 Wb/m². The damping constant is 0.008 N-m/rad-s⁻¹. The moment of inertia is 0.008 kg-m². The spring constant is 0.016 N-m/rad. The Coulomb friction is 0.2 × 10⁻⁶ N-m. The number of turns on the coil to produce a deflection of 100° at rated current is approximately
- (a) 374582 (b) 471548
(c) 581548 (d) 675284

Ans. (a)

$$T_d = T_e$$

$$NBI_A = K\theta$$

$$N \times 0.046 \times 10 \times 10^{-3} \times 65 \times 25 \times 10^{-6} = 0.016 \times 100 \times \frac{\pi}{180}$$

$$N = 374582$$

End of Solution

- Q.39** Consider the following statements regarding data acquisition systems :
1. Digital data acquisition systems are used when wide frequency width is required.
 2. Analog data acquisition systems are more complex than digital systems.
 3. Digital data acquisition systems are used when the physical quantity being monitored has a narrow bandwidth.

Which of the above statements are not correct?

- (a) 1 and 2 only (b) 1 and 3 only
(c) 1, 2 and 3 (d) 2 and 3 only

Ans. (a)

End of Solution

- Q.40** Wave analyzer is also known as
- (a) selective level meter (b) precision receiver
(c) modulation analyzer (d) audio analyzer

Ans. (a)

End of Solution

- Q.41** What is the displayed rise time (approximately) when a pulse waveform with a rise time of 21 ns is applied to an oscilloscope that has an upper cutoff frequency of 50 MHz?
- (a) 18 ns (b) 22 ns
(c) 32 ns (d) 28 ns

Ans. (b)

Frequency corresponding to 21 ns rise time

$$\Rightarrow \frac{1}{21 \times 10^{-9}} = 47.62 \text{ MHz}$$

47.62 MHz < 50 MHz (upper cut-off frequency oscilloscope)

Here, upto nearly 21 nsec \approx 22 nsec can be displayed.

End of Solution

Q.42 An FM telemetry system uses a 370 Hz-430 Hz voltage-controlled oscillator to carry the fuel level of 3000 I tank, where 370 Hz represents an empty tank and 430 Hz represents full tank. What level does 408 Hz represent?

- (a) 1650.66 I (b) 2533.33 I
(c) 3301.32 I (d) 4504.18 I

Ans. (*)

Change in frequency from empty tank to full tank
= 430 – 370 = 60 Hz

At 408 Hz, change in frequency from empty tank
= 408 – 370 = 38 Hz

\therefore A frequency of 408 Hz represents a fuel level

$$= 38 \times \frac{3000}{60} = 1900 \text{ L}$$


(*) No options are matching.

End of Solution

Q.43 Four strain gauges are mounted on a simple flat tensile specimen arranged for complete temperature compensation and maximum sensitivity when connected in a four-arm bridge circuit. An $8 \times 10^5 \Omega$ calibration resistor is shunted across one of the strain gauges. If the gauge resistances are each 188Ω and the gauge factors are 1.22, then the effective strain is

- (a) 545×10^{-6} (b) 775×10^{-6}
(c) 48.1×10^{-6} (d) 32.4×10^{-6}

Ans. (c)

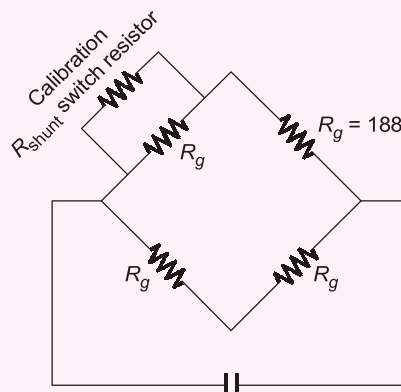

With switch open and switch close position change in resistance is calculated.

$$\begin{aligned}\Delta R &= \frac{R_g R_{\text{shunt}}}{R_g + R_{\text{shunt}}} - R_g \\ &= \frac{188 \times 8 \times 10^5}{188 + 8 \times 10^5} - 188 = -0.04417 \Omega \\ G_f &= \frac{\Delta R / R}{\epsilon_l} \\ \epsilon_l = \text{Strain} &= \frac{\Delta R}{R G_f} = \frac{0.04417}{188 \times 1.22}\end{aligned}$$

For quarter bridge effective strain

$$= \frac{192 \times 10^{-6}}{4} = 48.1 \times 10^{-6}$$

End of Solution

- Q.44** A 0-200 V voltmeter has a guaranteed accuracy of 1 percent of full-scale reading. The voltage measured by this instrument is 150 V. The percentage limiting
- (a) 25.00% (b) 12.50%
(c) 2.66% (d) 1.33%

Ans. (d)

$$\text{Error at reading} = \frac{200 \times 1}{150} = 1.33\%$$

End of Solution

- Q.45** A voltage has a true value of 1.55 V. An analog indicating instrument with a scale range of 0-2.5 V shows a voltage of 1.48 V. What is the relative error?
- (a) -2.67% (b) -1.60%
(c) -4.52% (d) -2.80%

Ans. (c)

$$\% \epsilon_r = \frac{1.48 - 1.55}{1.55} \times 100 = -4.52\%$$

End of Solution

- Q.46** The measurement precision of an instrument defines the smallest change in measured quantity that can be observed, which is called
- (a) accuracy of the instrument (b) precision of the instrument
(c) resolution of the instrument (d) significant figure of the instrument

Ans. (c)

End of Solution

Q.47 Consider the following statements :

1. The caesium beam and the hydrogen maser are the primary or absolute standards.
2. The rubidium vapour standard is based on the hyperfine transition in rubidium-78 gas, between the states $F = 2$ and $F = 1$.
3. The secondary standard of e.m.f. is the unsaturated Weston cell.

Which of the above statements are correct?

- (a) 1 and 2 only (b) 1 and 3 only
(c) 1, 2 and 3 (d) 2 and 3 only

Ans. (c)

End of Solution

Q.48 Which one of the following statements is correct regarding standards of measurements?

- (a) The primary standards are as accurate as the international standards.
- (b) The secondary standards are preserved at the 'International Bureau of Weights and Measures' and not available to the ordinary users.
- (c) The secondary standards are the absolute standards and not as accurate as the international standards.
- (d) Working standards are used by manufacturers for comparing and standardizing their products.

Ans. (a)

End of Solution

Q.49 A path is a particular subgraph consisting of an ordered sequence of branches having which of the following properties?

1. At all but two of its nodes, called internal nodes, there are incident exactly two branches of the subgraph.
2. At each of the remaining two nodes, called terminal nodes, there is incident exactly one branch of the subgraph.


Select the correct answer using the code given below.

- (a) 1 only (b) 2 only
(c) Neither 1 nor 2 (d) Both 1 and 2

Ans. (d)


End of Solution

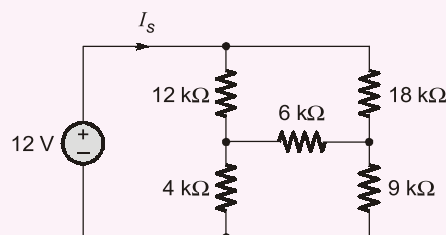Q.50 What is the value of the source current (I_s) of the given network in the figure?



- (a) 1.2 A (b) 12 A
(c) 1.2 mA (d) 12 mA

Ans. (c)

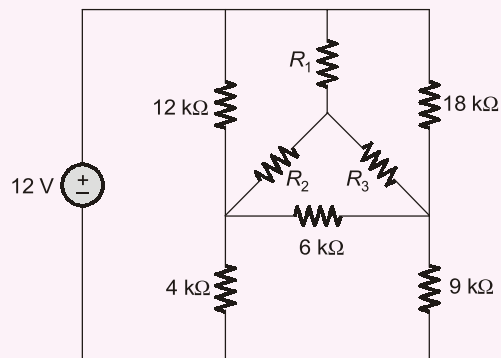


Using Delta-Star transformation

$$R_1 = \frac{12 \times 18}{12 + 18 + 6} = \frac{12 \times 18}{36} = 6 \text{ k}\Omega$$

$$R_2 = \frac{12 \times 6}{36} = 2 \text{ k}\Omega$$
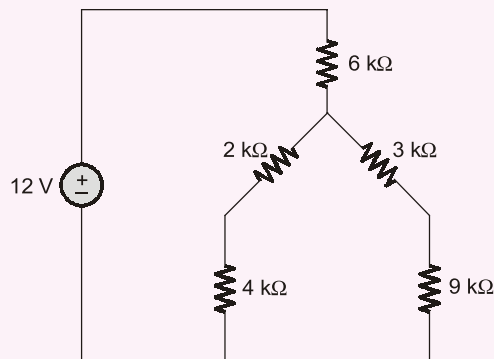
$$R_3 = \frac{18 \times 6}{36} = 3 \text{ k}\Omega$$



$$R_{eq} = 6 + 6 \parallel 12$$

$$R_{eq} = 6 + 4 = 10 \text{ k}\Omega$$

$$\therefore I_s = \frac{12}{10} = 1.2 \text{ mA}$$

End of Solution

Q.51 Which of the following properties of the circuits of a graph are correct?

1. The minimum number of branches possible in a circuit will be equal to the number of nodes or vertices.
2. There are exactly two paths between any pair of vertices in a circuit.
3. There are at least two branches in a circuit.


Select the correct answer using the code given below.

- | | |
|------------------|------------------|
| (a) 1 and 2 only | (b) 1 and 3 only |
| (c) 2 and 3 only | (d) 1, 2 and 3 |

Ans. (b)

End of Solution

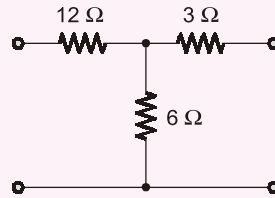Q.52 What are the open-circuit reverse voltage gain and the short-circuit forward current gain respectively for the two-port network shown in the figure?



- (a) $\frac{1}{3}$ and $-\frac{1}{3}$ (b) $-\frac{1}{3}$ and $\frac{1}{3}$
 (c) $\frac{2}{3}$ and $-\frac{2}{3}$ (d) $-\frac{2}{3}$ and $\frac{2}{3}$


Ans. (c)

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$V_1 = \frac{V_2 \times 6}{6+3} = \frac{V_2 \times 6}{9} = V_2 \times \frac{2}{3}$$


$$\frac{V_1}{V_2} = \frac{2}{3}$$

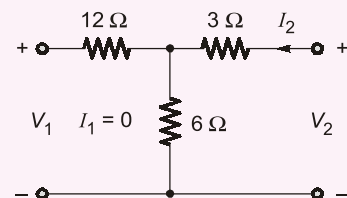

Hence, by using elimination process, the correct answer is option (c)

End of Solution

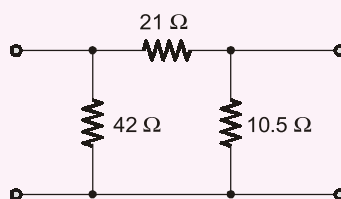Q.53 What are the open-circuit transfer admittance and the negative short-circuit current ratio respectively for the two-port network shown in the figure?




- (a) $\frac{2}{3} S$ and $\frac{3}{2}$ (b) $\frac{1}{6} S$ and $\frac{3}{2}$
 (c) $\frac{1}{6} S$ and $\frac{2}{3}$ (d) $\frac{2}{3} S$ and $\frac{2}{3}$

Ans. (b)

$$I_1 = CV_2 - DI_2$$

Open circuit transfer admittance

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

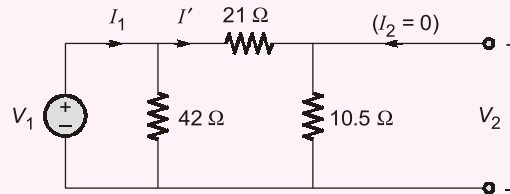

$$I' = \frac{I_1 \times 42}{42 + 21 + 10.5} \quad \dots(i)$$

$$V_2 = 10.5I' \quad \dots(ii)$$

$$I' = \frac{4}{7}I_1$$



$$V_2 = 10.5I'$$

$$V_2 = 10.5 \times \frac{4}{7}I_1$$

$$C = \frac{I_1}{V_2} = \frac{1}{6}$$

Negative short circuit current ratio i.e.,

$$D = \left. -\frac{I_1}{I_2} \right|_{V_2=0}$$

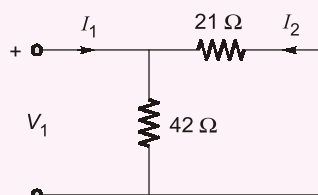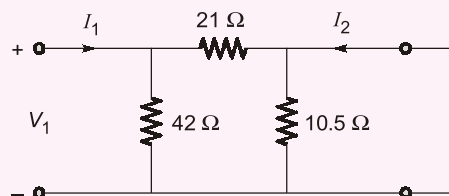

$$I_2 = -I_1 \times \frac{42}{42 + 21}$$

$$D = -\frac{I_1}{I_2} = \frac{3}{2}$$

Hence, the correct option is (b).

End of Solution

Q.54 The dynamics of an n th order single-input single-output system can be written by the vector-matrix differential equation $\dot{x} = Ax + Bu$ and output $y = Cx$. What is the size of the output coupling matrix C ?

- (a) $n \times n$ (b) $n \times 1$
(c) $1 \times n$ (d) 1×1

Ans. (c)

End of Solution


Q.55 For the state variable formulation of R-L-C network, which one of the following statements is correct?

- (a) The voltage across the inductor and the current through the capacitor are chosen as the state variables.
(b) Only the current through the inductor is chosen as the state variable.
(c) Only the voltage across the capacitor is chosen as the state variable.
(d) The current through the inductor and the voltage across the capacitor are chosen as the state variables.

Ans. (d)

End of Solution

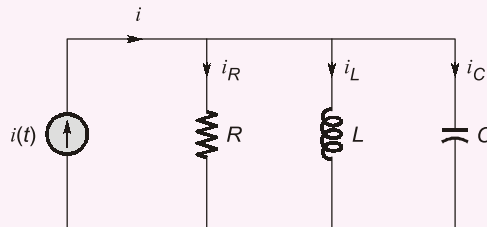Q.56 If $i(t) = I_0 \sin \omega t$, then the state variable formulation of the R-L-C circuit shown in the figure is




- (a)
$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ I_0(\omega/C)\cos\omega t \end{bmatrix}$$
- (b)
$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ \frac{1}{LC} & \frac{1}{RC} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ I_0(\omega/C)\sin\omega t \end{bmatrix}$$
- (c)
$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ \frac{1}{LC} & \frac{1}{RC} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ I_0(\omega/C)\cos\omega t \end{bmatrix}$$
- (d)
$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ I_0(\omega/C)\sin\omega t \end{bmatrix}$$

Ans. (d)


End of Solution

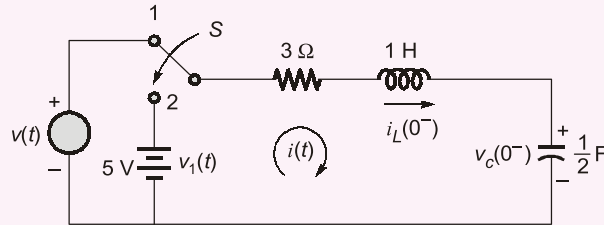Q.57 In the figure, the switch is thrown from position 1 to 2 at time $t = 0$. Just before the switch is thrown, the initial conditions are $i_L(0^-) = 2$ A, $v_C(0^-) = 2$ V. What is the current $i(t)$ after switching action?



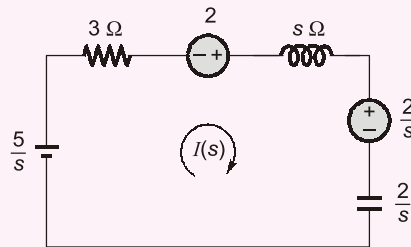- (a) $e^{-t} + e^{-3t}$ (b) $e^{-t} + e^{-2t}$
(c) $e^t + e^{3t}$ (d) $e^t + e^{2t}$

Ans. (b)
Apply Laplace transform to the circuit.



$$I(s) = \frac{\frac{5}{s} + 2 - \frac{2}{s}}{3 + s + \frac{2}{s}} = \frac{2s + 3}{s^2 + 3s + 2} = \frac{2s + 3}{(s + 1)(s + 2)}$$


$$I(s) = \frac{A}{(s + 1)} + \frac{B}{(s + 2)}$$

$$I(s) = \frac{1}{(s + 1)} + \frac{1}{(s + 2)}$$

$$i(t) = e^{-t} + e^{-2t}$$

End of Solution

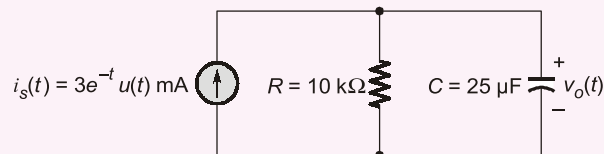
Q.58 What is the output voltage $v_o(t)$ of the circuit shown in the figure



- (a) $v_o(t) = 20[e^{-t} - e^{-2t}] u(t)$ V (b) $v_o(t) = 40[e^{-t} - e^{-2t}] u(t)$ V
(c) $v_o(t) = 40[e^{-t} - e^{-4t}] u(t)$ V (d) $v_o(t) = 20[e^{-t} - e^{-4t}] u(t)$ V

Ans. (c)

Apply Laplace transform the circuit

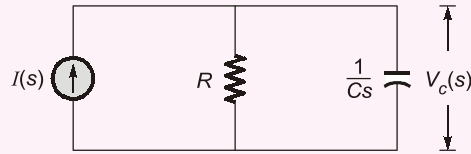

$$V_c(s) = I(s) \cdot \frac{R}{\left(R + \frac{1}{Cs}\right)} \times \frac{1}{Cs}$$

$$V_c(s) = I(s) \cdot \frac{R}{(1+RCs)} = I(s) \frac{1/C}{\left(s + \frac{1}{RC}\right)}$$

$$= \frac{3 \times 10^{-3}}{(s+1)} \times \frac{1}{25 \times 10^{-6} \left(s + \frac{1}{10 \times 10^3 \times 25 \times 10^{-6}}\right)}$$

$$V_c(s) = \frac{3 \times 40}{(s+1)(s+4)}$$


$$V_c(s) = \frac{A}{(s+1)} + \frac{B}{(s+4)}$$

$$V_c(s) = \frac{40}{(s+1)} - \frac{40}{(s+4)}$$

$$v_c(t) = 40(e^{-t} - e^{-4t}) u(t)$$

End of Solution

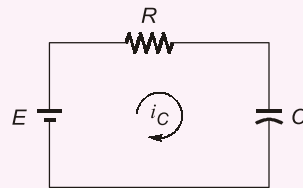Q.59 If the value of $E = 100$ V, $R = 10$ k Ω and $C = 10$ mF in the circuit shown in the figure, then the capacitor current (i_C) at $t = 150$ ms is



(a) $100e^{-1.5}$ mA

(b) $50e^{-1.5}$ mA

(c) $10e^{-1.5}$ mA

(d) $20e^{-1.5}$ mA

Ans. (c)

$$i(t) = \frac{E}{R} e^{-t/RC} = \frac{100}{10 \times 10^3} e^{-t/(10 \times 10^3 \times 10^{-3} \times 10)} = 10 \times 10^{-3} \cdot e^{-t/(100)}$$

At $t = 150$ msec

$$= 10e^{-\frac{150 \times 10^{-3}}{100}} \text{ mA}$$

$$i(t) = 10e^{-1.5 \times 10^{-3}} \text{ mA}$$

As no option is matching, if we consider $C = 10$ μ F, then option (c) is correct.

End of Solution



Announcing

SUPER TALENT BATCHES

for **ESE 2023 & GATE 2023**

Batches commencing from

27th April, 2022

CE, ME

28th April, 2022

EE, EC

- **Course duration** : 6-7 months
- **Teaching hours** : 1000-1200

Note : These batches will be conducted only at Delhi Centre.

Key Features

- Highly competitive environment.
- Meritorious students group.
- Classes by senior faculty members.
- In-depth coverage of syllabus.
- Focus on problem solving techniques.

Register online at : www.madeeasy.in


Corporate Office : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016

MADE EASY Centres : Delhi | Hyderabad | Jaipur | Lucknow | Bhopal | Bhubaneswar | Pune | Patna | Kolkata

☎ **9021300500**

🌐 www.madeeasy.in

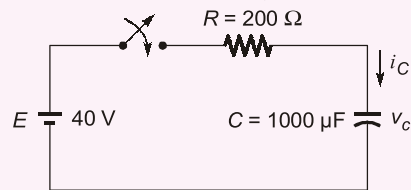Q.60 The capacitor of the figure shown below has 25 V on it with polarity shown at the time the switch is closed. The expression for v_C is



- (a) $(40 - 15e^{-5t})$ volts
 (b) $(40 - 20e^{-5t})$ volts
 (c) $(40 - 25e^{-3t})$ volts
 (d) $(40 - 40e^{-3t})$ volts

Ans. (a)

$$V_C(0^+) = 25 \text{ V}$$

In steady state, capacitor acts as open circuit for DC supply.

$$V_C(\infty) = 40 \text{ V}$$

$$\text{Time constant } (\tau) = RC = 200 \times 1000 \times 10^{-6} = 0.2$$

$$V_C(t) = V_C(\infty) + [V_C(0^+) - V_C(\infty)] e^{-t/\tau}$$

$$V_C(t) = 40 + (25 - 40)e^{-t/0.2}$$

$$V_C(t) = 40 - 15e^{-5t} \text{ Volt}$$

End of Solution

Q.61 Convert $(329.54)_{10}$ to hexadecimal.

- (a) $(149.8A3D70A)_{16}$
 (b) $(219.8A3D70A)_{16}$
 (c) $(149.8A70AD)_{16}$
 (d) $(219.8A70AD)_{16}$

Ans. (a)

16	329	
16	20	9
16	1	4
	0	1

$$(329)_{10} = (149)_{16}$$

$$0.54 \times 16 = 8.64 \Rightarrow 8$$

$$0.64 \times 16 = 10.24 \Rightarrow A$$

$$0.24 \times 16 = 3.84 \Rightarrow 3$$

$$0.84 \times 16 = 13.44 \Rightarrow D$$

$$0.44 \times 16 = 7.04 \Rightarrow 7$$

$$0.04 \times 16 = 0.64 \Rightarrow 0$$

$$0.64 \times 16 = 10.24 \Rightarrow A$$

$$(329.54)_{10} = (149.8A3D70A)_{16}$$

End of Solution


- Q.62** Represent the decimal number 396 in binary, Gray and excess-3 codes respectively.
 (a) 110001100, 101011010, 110001111 (b) 110001010, 101101011, 110010000
 (c) 101001010, 110001100, 110011111 (d) 110001100, 101001010, 110001111

Ans. (d)

2	396	
2	198	0
2	99	0
2	49	1
2	24	1
2	12	0
2	6	0
2	3	0
2	1	1
	0	1

$(396)_{10} = (110001100)_2$

Grey Code

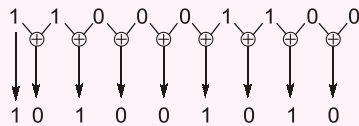

Excess-3

$$\begin{array}{r} 110001100 \\ + \quad \quad 11 \\ \hline 110001111 \end{array}$$

End of Solution

- Q.63** The most personal computers (PCs)-compatible computer systems use a 20-bit address code to identify each of over 1 million memory locations. What is the 5-digit hexadecimal address of the 500th memory location?
 (a) 001F3 (b) 001F4
 (c) 001F5 (d) 001F6

Ans. (a)

First memory location → 00000 H

500th memory location = $(500 - 1)_{10} = (499)_{10}$

16	499	
16	31	3
16	1	F
	0	1

The address of 500th memory location is 001F3 H.

End of Solution


- Q.64** Simplify the following Boolean function:

$f(A, B, C) = \bar{A}BC + A\bar{B}C + ABC\bar{C} + ABC$

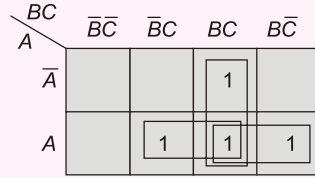- (a) $\bar{A}BC + A\bar{B}C + AB$ (b) $A\bar{B}C + AC + AB$
 (c) $AB + BC + AC$ (d) $\bar{A}BC + AC + AB$

Ans. (c)


$$f(A, B, C) = \bar{A}BC + A\bar{B}C + ABC\bar{C} + ABC$$



$$f(A, B, C) = AB + BC + AC$$


End of Solution

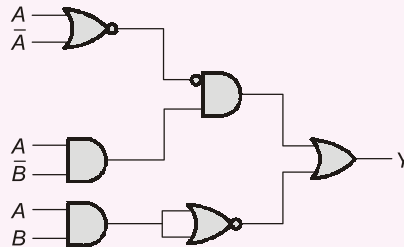Q.65 What is the output Y for the logic circuit shown in the figure?



- (a) $A\bar{B} + \bar{A}B$ (b) $A\bar{B} + \bar{A} + B$
(c) $A\bar{B} + \bar{A}\bar{B}$ (d) $\bar{A} + \bar{B}$

Ans. (d)

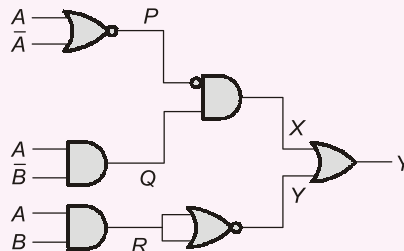

$$Y = X + Y$$

$$Y = A\bar{B} + \bar{A}\bar{B} = A\bar{B} + \bar{A} + \bar{B}$$

$$Y = \bar{A} + \bar{B}$$

End of Solution

Q.66 A, B and C_{in} are the three inputs of a full adder circuit and D_0, D_1, \dots, D_7 are the inputs of 8 : 1 multiplexer. S_2 (MSB), S_1 and S_0 (LSB) are the selection lines of the multiplexer. To implement the expression of sum of full adder circuit using this multiplexer, the connections of the input ports and selection lines are

- (a) $D_0 = D_3 = D_5 = D_6 = 0, D_1 = D_2 = D_4 = D_7 = 1, S_2 = A, S_1 = B$ and $S_0 = C_{in}$
(b) $D_0 = D_3 = D_5 = D_6 = 1, D_1 = D_2 = D_4 = D_7 = 0, S_2 = C_{in}, S_1 = B$ and $S_0 = A$
(c) $D_0 = D_2 = D_3 = D_6 = 0, D_1 = D_4 = D_5 = D_7 = 1, S_2 = A, S_1 = B$ and $S_0 = C_{in}$
(d) $D_0 = D_1 = D_5 = D_7 = 1, D_2 = D_3 = D_4 = D_6 = 0, S_2 = C_{in}, S_1 = B$ and $S_0 = A$

Q.68 The Schmitt trigger can be used as which of the following?

- 1. Square-wave generator.
- 2. Comparator
- 3. Astable multivibrator

Select the correct answer using the code given below:

- (a) 1 and 3 only
- (b) 1 and 2 only
- (c) 2 and 3 only
- (d) 1, 2 and 3

Ans. (b)

Schmitt trigger provides square wave output whatever be the input to it. Hence, it can be considered as square wave generator.


Schmitt trigger is a comparator circuit having positive feedback. Schmitt trigger is also called as regenerative comparator.

Astable multivibrator is a different circuit. It is formed by connecting one more RC network in the Schmitt trigger.

Hence, the correct answer is option (b)

End of Solution

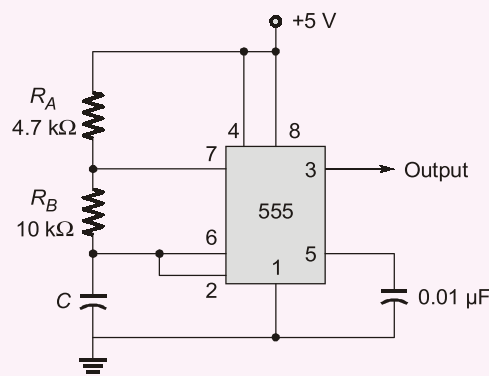Q.69 What are the approximate values of t_1 , t_2 , frequency and duty cycle of a 555 timer used as an astable multivibrator respectively? (Take $C = 680 \text{ pF}$)



- (a) 4.76 µsec, 6.997 µsec, 85 kHz and 59.5%
- (b) 6.84 nsec, 9.997 nsec, 68 kHz and 59.5%
- (c) 4.76 µsec, 6.997 µsec, 68 kHz and 68%
- (d) 6.84 nsec, 9.997 nsec, 85 kHz and 68%

Ans. (a)

Given data : $C = 680 \text{ pF}$; $R_A = 4.7 \text{ k}\Omega$; $R_B = 10 \text{ k}\Omega$

$$t_1 = t_{low} = 0.69 R_B C = 0.69 \times 10 \times 10^3 \times 680 \times 10^{-12}$$
$$t_1 = 4.76 \text{ }\mu\text{sec}$$

$$t_2 = t_{high} = 0.69 (R_A + R_B)C = 0.69 \times 14.7 \times 10^3 \times 680 \times 10^{-12}$$
$$t_2 = 4.76 + 6.997$$

$$T_o = 11.757 \text{ }\mu\text{sec}$$

Frequency, $f_o = \frac{1}{T_o} = \frac{1}{11.757 \text{ }\mu\text{sec}}$


$$f_o = 85 \text{ kHz}$$

$$\text{Duty cycle} = \frac{t_{\text{high}}}{T_o} \times 100\% = \frac{6.997}{11.757} \times 100$$

$$\text{Duty cycle} = 59.5\%$$

End of Solution

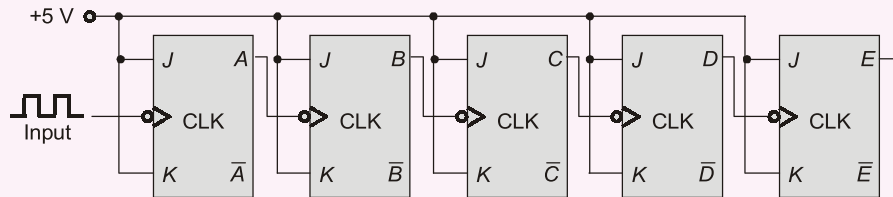Q.70 A five-bit asynchronous counter is shown in the figure. If the clock input frequency is 22.4 MHz, what is the frequency at the output E?



- (a) 700 kHz
(b) 350 kHz
(c) 150 MHz
(d) 300 MHz

Ans. (a)

Given:

$$\text{Input clock frequency} = 22.4 \text{ MHz}$$

The given counter is mod-32 up counter.

$$\text{The frequency at the output } E = \frac{22.4}{32} \times 10^6$$

$$f_{\text{out}} = 700 \text{ kHz}$$

End of Solution

Q.71 A certain J-K flip-flop has propagation delay 12 picoseconds. What is the largest MOD of a counter that can be constructed from these J-K flip-flops and operates up to 10 GHz?

- (a) 64
(b) 128
(c) 256
(d) 512

Ans. (c)

Given: The propagation delay, $t_{pd} = 12 \text{ psec}$

We know that, $f \leq \frac{1}{nt_{pdFF}}$

$$10 \times 10^9 \leq \frac{1}{n \times 12 \times 10^{-12}}$$

$$n \leq \frac{1}{10 \times 10^9 \times 12 \times 10^{-12}}$$

$$n \leq \frac{1000}{120}$$

$$n \leq 8.33$$

\therefore No. of flip flops required is 8, therefore the largest MOD of a counter with 8 flip flops is 256

End of Solution

Q.72 Simplify the following Boolean expression using the De Morgan's theorem :

$$f(A, B, C, D, E, F) = \overline{(A + B)\overline{CD} + (E + \overline{F})}$$

- (a) $(\overline{A} + \overline{B} + \overline{C})(\overline{D} + \overline{E} + \overline{F})$ (b) $\overline{AB + CD + EF}$
 (c) $(\overline{A}\overline{B} + C + D)\overline{E}F$ (d) $\overline{ABC + DEF}$

Ans. (c)

$$\begin{aligned} f(A, B, C, D, E, F) &= \overline{(A + B)\overline{CD} + (E + \overline{F})} \\ &= \overline{(A + B)\overline{CD}} \cdot \overline{(E + \overline{F})} \\ &= (\overline{A + B} + \overline{\overline{CD}})\overline{E + \overline{F}} \\ &= (\overline{A}\overline{B} + C + D)\overline{E}F \end{aligned}$$

End of Solution

Q.73 The internet protocol (IP) (RFC 791) is the heart of the TCP/IP protocol suite. IP corresponds to the network layer in the OSI reference model and provides.

- (a) a connectionless service to the application layer which requires a virtual circuit
 (b) high reliability in packet delivery
 (c) a connectionless best effort delivery service to the transport layer
 (d) reliability functions within a higher layer protocol

Ans. (c)

IP corresponds to the network layer in the OSI reference model provides a connectionless best effort delivery service to the transport layer.

End of Solution

Q.74 The orbital satellites are

- (a) symmetrical (b) asymmetrical
 (c) synchronous (d) non synchronous

Ans. (d)

Most of the orbital satellites are non-synchronous.

End of Solution

Q.75 The requirement for reliability, long life, stability, high efficiency and suitability for space environment are met by the use of

- (a) IF amplifier (b) RF amplifier
 (c) travelling wave tube amplifier (d) ultrasonic amplifier

Ans. (c)

In space communication, we deal with microwave frequencies which uses travelling wave tube amplifier.

End of Solution

- Q.76** The highest frequency that is returned to the earth at a given distance is called
 (a) maximum available frequency (b) maximum communication frequency
 (c) maximum bandwidth frequency (d) maximum usable frequency

Ans. (d)

End of Solution

- Q.77** The mean sun does move at a uniform speed but otherwise requires the same time as the real sun to complete one orbit of the earth, this time being
 (a) the tropical year (b) the leap year
 (c) the Julian calendar year (d) the Gregorian calendar year

Ans. (a)

End of Solution

- Q.78** Which one of the following statements is not correct regarding SONET networks?
 (a) A point-to-point network is normally made of an STS multiplexer.
 (b) A linear synchronous optical network can be point-to-point or multipoint.
 (c) The signal flow can be unidirectional or bidirectional.
 (d) A multipoint network uses STS multiplexers to allow the communications between several terminals.

Ans. (d)

A multipoint network uses Add and Drop Multipliers (ADM) to allow the communications between several terminals.

End of Solution

- Q.79** A digital optical fiber communication system operating at a wavelength of $1 \mu\text{m}$ requires a maximum bit error rate of 10^{-9} . What is the theoretical quantum limit at the receiver in terms of the quantum efficiency of the detector and the energy of an incident photon?

- (a) $\frac{20.7hf}{\eta}$ (b) $\frac{10.7hf}{\eta}$
 (c) $\frac{20.7\eta}{hf}$ (d) $\frac{10.7\eta}{hf}$

Ans. (a)

Probability of error,

$$P_e = \exp(-Z_m) = 10^{-9}$$

$$Z_m = 20.7$$

$$Z_m = \frac{\eta P_o \tau}{hf}$$

$$E_{\min} = P_o \tau = \frac{Z_m \times hf}{\eta}$$

$$P_o \tau = E_{\min} = \frac{20.7hf}{\eta}$$

End of Solution

- Q.80** With frequency reuse, several cells with no space in a given coverage area use the same set of frequencies. Two cells using the same set of frequencies are called
- (a) hexagonal shape cells (b) adjacent channel cells
(c) cluster neighbour cells (d) co-channel cells

Ans. (d)
Two cells using same set of frequencies are called co-channel cell.

End of Solution

- Q.81** The component in the satellite that takes an uplink signal and converts into a downlink signal is called
- (a) uplink device (b) transponder
(c) downlink device (d) transmitter

Ans. (b)

End of Solution

- Q.82** An advantage of passive satellites is that they do not require sophisticated electronic equipment on board, although they are not necessary void of power. Some passive satellites require which one of the following for tracking and ranging purposes?
- (a) Radio beacon transmitter (b) Defense launched courier
(c) Radio beacon receiver (d) Satellite beacon launcher

Ans. (a)
Radio beacon transmitter is used for tracking and ranging purpose.

End of Solution

- Q.83** Some of the diffracted light continues down the fiber and some of it escapes through the cladding. The light rays that escape represent a loss in light power which is called
- (a) Rayleigh scattering loss (b) chromic distortion loss
(c) chromatic distortion loss (d) predominant fiber loss

Ans. (a)

End of Solution

- Q.84** Numerical aperture is closely related to acceptance angle and is the figure of merit commonly used to measure
- (a) the sine of the maximum angle (b) the magnitude of the acceptance angle
(c) the maximum angle of light ray (d) the intensity of light ray entering the cable

Ans. (b)

End of Solution



MADE EASY

India's Best Institute for IES, GATE & PSUs



NST

NATIONAL SCHOLARSHIP TEST

For **ESE 2023** & **GATE 2023**
LIVE-ONLINE & OFFLINE COURSES

NST-1

22nd Feb, 2022
For **LIVE-ONLINE** Courses

UP TO **50%** SCHOLARSHIP
in Total Fee

Exam Mode : **ONLINE**

Time Duration : 45 Min | Total Question : 50
Total Marks : 100 | Negative Marking : 0.66 Marks

Note: 50% weightage will be given to marks obtained in B.Tech.
Merit list will be prepared on the basis of NST score & B. Tech marks.

Last Date to Apply 20th Feb'22

NST-2

27th Feb, 2022
For **CLASSROOM** Courses

UP TO **100%** SCHOLARSHIP
in Tuition Fee

Exam Mode : **OFFLINE**

Time Duration : 60 Min | Total Question : 50
Total Marks : 100 | Negative Marking : 0.66 Marks

Test Centres: Agra, Prayagraj, Bhilai, Chandigarh, Chennai, Mumbai,
Visakhapatnam, Indore, Bengaluru, Nagpur, Jabalpur, Dehradun, Delhi, Bhopal,
Bhubaneswar, Hyderabad, Jaipur, Kolkata, Lucknow, Patna & Pune

Last Date to Apply 21st Feb'22

Register at : www.madeeasy.in

Scholarship applicable on batches commencing after **1st March, 2022**

Corporate Office : 44-A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi-110016

MADE EASY Centres : Delhi | Hyderabad | Jaipur | Lucknow | Bhopal | Bhubaneswar | Pune | Patna | Kolkata

☎ **9021300500**

🌐 **www.madeeasy.in**

Alternate:

Number of RAM chips required

$$\Rightarrow \frac{\text{Memory needed to design}}{\text{RAM chip size}}$$

$$= \frac{8 \text{ kB}}{1024 \times 1\text{-bit}} = \frac{8 \text{ K} \times 8 \text{ bits}}{1024 \text{ bits}}$$

$$= \frac{2^3 \times 2^{10} \times 2^3}{2^{10}} = 2^6 = 64$$

End of Solution

Q.88 Which one of the following statements is correct for the given system?

$$y(n) = x^2(n) + \frac{1}{x^2(n-1)}$$

- (a) The given system is linear, non-causal and shift-variant.
- (b) The given system is non-linear, causal and shift-invariant.
- (c) The given system is non-linear, causal and shift-variant.
- (d) The given system is linear, non-causal and shift-invariant.

Ans. (b)

$$y(n) = x^2(n) + \frac{1}{x^2(n-1)}$$

As output $y(n)$ depends on the square of the input, therefore system is non-linear.

Delay in input, $y(n) = x^2(n-n_0) + \frac{1}{x^2(n-n_0-1)}$

Delay in output, $y(n-n_0) = x^2(n-n_0) + \frac{1}{x^2(n-n_0-1)}$

$$y(n) = y(n-n_0)$$

\therefore System is time invariant.

At $n = 0$,

$$\underbrace{y(0)}_{\text{Present output}} = \underbrace{x^2(0)}_{\text{Present input}} + \frac{1}{\underbrace{x^2(-1)}_{\text{Past input}}}$$

Present output depends on present and past values of input.

\therefore System is causal.

End of Solution

Q.89 If the impulse response $h(n)$ and the output $y(n)$ of a system are given as

$$h(n) = \{2, 1, 0, -1, 3\} \text{ and } y(n) = \{2, -5, 1, 1, 6, -11, 6\}$$

then the input $x(n)$ of the system is

- (a) $\{1, -3, 2\}$
- (b) $\{2, -3, 1\}$
- (c) $\{1, 3, 2, 1\}$
- (d) $\{2, -3, 1, 1\}$

Ans. (a)

$$y(n) = x(n) * h(n)$$

Taking Z-transform, $Y(z) = X(z) \cdot H(z)$

$$X(z) = \frac{Y(z)}{H(z)}$$

$$h(n) = \{2, 1, 0, -1, 3\}$$

Taking z-transform of $h(n)$

$$H(z) = 2 + z^{-1} + (-1)z^{-3} + 3z^{-4}$$

$$y(n) = \{2, -5, 1, 1, 6, -11, 6\}$$

$$Y(z) = 2 - 5z^{-1} + z^{-2} + z^{-3} + 6z^{-4} - 11z^{-5} + 6z^{-6}$$

$$X(z) = \frac{2 - 5z^{-1} + z^{-2} + z^{-3} + 6z^{-4} - 11z^{-5} + 6z^{-6}}{2 + z^{-1} - z^{-3} + 3z^{-4}}$$

$$X(z) = 1 - 3z^{-1} + 2z^{-2}$$

Applying inverse z-transform,

$$x(n) = \{1, -3, 2\}$$

End of Solution

Q.90 The approximate transition width of main lobe in Blackman window is

- (a) $4\pi/N$ (b) $8\pi/N$
(c) $12\pi/N$ (d) $16\pi/N$

Ans. (c)

End of Solution

Q.91 Consider the following statements regarding filters :

1. Causer filter has equiripple passband and stopband.
2. For a given filter order, passband and stopband deviations, Causer filters have more transition bandwidth as compared to Chebyshev filters.
3. Linear phase characteristics cannot be achieved in IIR filters.

Which of the above statements are correct?

- (a) 1 and 2 only (b) 1 and 3 only
(c) 2 and 3 only (d) 1, 2 and 3

Ans. (b)

Causer filters have less transition bandwidth as compared to Chebyshev filters.

End of Solution

Q.92 Consider the following statements regarding 8051 microcontroller:

1. The size of RAM in 8051 is 128 bytes.
2. RAM locations 00-1FH are assigned to the register banks and stack.
3. RAM locations 20-2FH are available as a place to save byte-sized data.

Which of the above statements are correct?

- (a) 1 and 2 only (b) 1 and 3 only
(c) 2 and 3 only (d) 1, 2 and 3

Ans. (d)

End of Solution

Q.97 If V is a scalar, then the given equation (in spherical coordinate system)

$$\frac{1}{r^2} \frac{\partial}{\partial r} \left(r^2 \frac{\partial V}{\partial r} \right) + \frac{1}{r^2 \sin \theta} \frac{\partial}{\partial \theta} \left(\sin \theta \frac{\partial V}{\partial \theta} \right) + \frac{1}{r^2 \sin^2 \theta} \frac{\partial^2 V}{\partial \phi^2} = -\frac{\rho}{\epsilon}$$

is referred to as

- (a) Laplace's equation
(b) Poisson's equation
(c) gradient of V
(d) divergence of V

Ans. (b)

Poisson's equation: $\nabla^2 V = \frac{-\rho_V}{\epsilon}$; $\rho_V =$ Volume charge density

In spherical co-ordinate system;

$$\nabla^2 V = \frac{1}{r^2} \frac{\partial}{\partial r} \left(r^2 \frac{\partial V}{\partial r} \right) + \frac{1}{r^2 \sin \theta} \frac{\partial}{\partial \theta} \left(\sin \theta \frac{\partial V}{\partial \theta} \right) + \frac{1}{r^2 \sin^2 \theta} \frac{\partial^2 V}{\partial \phi^2} = \frac{-\rho_V}{\epsilon}$$

End of Solution

Q.98 The intrinsic impedance of free space is

- (a) 107 Ω
(b) 214 Ω
(c) 377 Ω
(d) 754 Ω

Ans. (c)

The intrinsic impedance of free space is given as

$$\begin{aligned} \eta &= \sqrt{\frac{\mu}{\epsilon}} \\ &= \sqrt{\frac{\mu_0}{\epsilon_0}} = 120\pi \text{ (or) } 377 \Omega \end{aligned}$$

End of Solution

Q.99 Which one of the following is an angle at which there is no reflected wave when the incident wave is parallel (or vertically) polarized?

- (a) Critical angle
(b) Reference angle
(c) Relative angle
(d) Brewster angle

Ans. (d)

Brewster angle is that angle at which if incident wave falls, then there will be no reflection.

End of Solution

Q.100 The condition for the low-loss transmission line is

- (a) $R \gg \omega C$ and $G \gg \omega L$
(b) $R \ll \omega C$ and $G \ll \omega C$
(c) $\frac{R}{G} = \frac{L}{C}$
(d) $RG \gg LC$

Ans. (b)

For a low-loss transmission line;

$$R \ll \omega L$$

$$G \ll \omega C$$

End of Solution

Q.101 Consider the following statements regarding impedance matching :

1. When the line is terminated in an impedance other than its characteristic impedance, reflection will occur and there will be standing waves of voltage and current along the line which may be very large if there is considerable mismatch.
 2. The single-stub device has the advantage that it will match any load.
 3. The double stub has the disadvantage that the line length needs to be adjustable.
- Which of the above statements are correct?

(a) 2 and 3 only

(b) 1 and 2 only

(c) 1 and 3 only

(d) 1, 2 and 3

Ans. (d)

- There exists reflections at load end, if load is not matched to the characteristic impedance of transmission line.
- Single stub can be used to match any complex load to the characteristic impedance of transmission line.
- Once the stub locations are fixed, a certain range of load admittance cannot be matched.

End of Solution

Q.102 The wave impedance in z direction for TE wave is

$$(a) Z_z(TE) = \frac{\eta}{\sqrt{\left(1 + \frac{\omega_c^2}{\omega^2}\right)}}$$

$$(b) Z_z(TE) = \frac{2\eta}{\sqrt{\left(1 - \frac{\omega_c^2}{\omega^2}\right)}}$$

$$(c) Z_z(TE) = \frac{\eta}{\sqrt{\left(1 - \frac{\omega_c^2}{\omega^2}\right)}}$$

$$(d) Z_z(TE) = \frac{2\eta}{\sqrt{\left(1 + \frac{\omega_c^2}{2\omega^2}\right)}}$$

Ans. (c)

For a TE wave; wave impedance is given as

$$\eta_{TE} = \frac{\eta_{TEM}}{\sqrt{1 - \left(\frac{f_c}{f}\right)^2}}$$

$$\Rightarrow \eta_{TE} = \frac{\eta_{TEM}}{\sqrt{1 - \left(\frac{\omega_C}{\omega}\right)^2}}$$

End of Solution

- Q.103** Which one of the following is the ratio of power lost per unit length to the twice of power transmitted?
- (a) Attenuation factor (b) Power efficiency
(c) Quality factor (d) Transmission efficiency

Ans. (a)

The ratio of the power loss per unit length to twice the power transmitted through the guide is called as the attenuation constant of the guide walls.
Mathematically;

$$\alpha_g = \frac{P_L}{2P_{tr}};$$

P_L = Power loss per unit length; P_{tr} = Power transmitted

End of Solution

- Q.104** A section of X-band waveguide with dimensions $a = 2.286$ cm and $b = 1.016$ cm has perfectly conducting walls and is filled with a lossy dielectric ($\sigma_d = 367.5 \frac{\mu S}{m}$, $\epsilon_r = 2.1$, $\mu_r = 1$). The cutoff frequency of TE_{10} for the dominant mode of propagation at a frequency of 9 GHz is
- (a) 2.27 GHz (b) 4.53 GHz
(c) 6.80 GHz (d) 9.07 GHz

Ans. (b)

Given data; $a = 2.286$ cm; $b = 1.016$ cm; $\sigma_d = 367.5 \mu S/m$; $\epsilon_r = 2.1$; $\mu_r = 1$
 $f = 9$ GHz; $f_c = ?$
For TE_{10}

$$f_c = \frac{v}{2a}; \quad v = \frac{c}{\sqrt{\epsilon_r}}$$

$$\Rightarrow f_c = \frac{c}{2\sqrt{\epsilon_r} a} = \frac{3 \times 10^{10}}{2 \times \sqrt{2.1} \times 2.286} = 4.53 \times 10^9 \text{ Hz}$$

$$\therefore f_{c|TE_{10}} = 4.53 \text{ GHz}$$

End of Solution

- Q.105** The antenna or array designed to yield directive gain appreciably greater than that obtainable from uniform distribution has become known as
- (a) superheterodyne array (b) supergain array
(c) super antenna (d) universal antenna

Ans. (b)

End of Solution

Q.106 In antennas, if S_A is the input signal generated by the source (by the receiving antenna) at temperature T_A , T_E is the effective noise temperature of the receiver network (referred to the input terminal), B is bandwidth and k is Boltzmann's constant, then the output signal-to-noise ratio is

- (a) $\frac{S}{N} = \frac{S_A}{(T_A + T_E)kB}$ (b) $\frac{S}{N} = \frac{S_A T_A}{kBT_E}$
 (c) $\frac{S}{N} = \frac{S_A(1+T_A)}{kB(1+T_E)}$ (d) $\frac{S}{N} = \frac{S_A T_A}{kB(1+T_E)}$

Ans. (a)

End of Solution

Q.107 The average value of the electrostatic field over the volume V of a sphere due to a point charge q somewhere within the sphere, where r_0 is the position of the charge, is

- (a) $E_{av} = -\frac{qr_0}{3\epsilon_0 V}$ (b) $E_{av} = -\frac{qr_0}{4\pi\epsilon_0 V}$
 (c) $E_{av} = \frac{qr_0}{3\epsilon_0 V}$ (d) $E_{av} = \frac{qr_0}{4\pi\epsilon_0 V}$

Ans. (c)

End of Solution

Q.108 In the relation between the field and the potential, if $r < a$, then the potential at a point r inside a uniformly charged sphere of radius a , is

- (a) $\frac{a^3\rho}{3\epsilon_0 r}$ (b) $\frac{\rho}{6\epsilon_0}(3a^2 - r^2)$
 (c) $\frac{4\pi a^3}{3r}$ (d) $\frac{2\pi}{3}(3a^2 - r^2)$

Ans. (b)

$$V = -\int_{r=\infty}^r \vec{E} \cdot d\vec{l}$$

Let ρ be the volume charge density;
 Then using Gauss's law for ($r < a$)


$$\oint \vec{D} \cdot d\vec{S} = Q_{enc} = \int \rho dV$$

$$\Rightarrow \epsilon_0 E \cdot 4\pi r^2 = \rho \cdot \frac{4}{3}\pi r^3$$

$$\Rightarrow E = \frac{\rho r}{3\epsilon_0}$$

$$\Rightarrow E = \frac{\rho r}{3\epsilon_0} \hat{a}_r$$

For $r > a$;

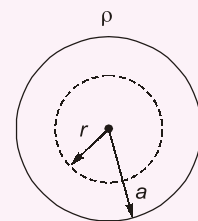

$$\Rightarrow \epsilon_0 E \cdot 4\pi r^2 = \rho \cdot \frac{4}{3} \pi a^3$$

$$\Rightarrow E = \frac{\rho a^3}{3\epsilon_0 r^2}$$

$$\Rightarrow \vec{E} = \frac{\rho a^3}{3\epsilon_0 r^2} \hat{a}_r$$

$$\text{Now, } V = - \int_{r=\infty}^r \vec{E} \cdot d\vec{l}$$

$$\Rightarrow V = - \left[\int_{r=\infty}^a \frac{\rho a^3}{3\epsilon_0 r^2} dr + \int_a^r \frac{\rho r}{3\epsilon_0} dr \right]$$

$$\Rightarrow V = - \left[\frac{\rho a^3}{3\epsilon_0} \left(-\frac{1}{r} \right)_{\infty}^a + \frac{\rho}{3\epsilon_0} \left(\frac{r^2}{2} \right)_a^r \right]$$

$$\Rightarrow V = - \left[-\frac{\rho a^3}{3\epsilon_0} \left[\frac{1}{a} - \frac{1}{\infty} \right] + \frac{\rho}{6\epsilon_0} [r^2 - a^2] \right]$$

$$\Rightarrow V = - \left[-\frac{\rho a^2}{3\epsilon_0} + \frac{\rho}{6\epsilon_0} [r^2 - a^2] \right]$$

$$\Rightarrow V = \frac{\rho a^2}{3\epsilon_0} - \frac{\rho}{6\epsilon_0} [r^2 - a^2]$$

$$\Rightarrow V = \frac{\rho}{6\epsilon_0} [3a^2 - r^2]$$

End of Solution

Q.109 Which one of the following techniques is used to speed up the multiplication of two signed binary numbers in 2's complement notation?

- (a) K-Map algorithm (b) Booth's algorithm
(c) Pascal's algorithm (d) De Morgan's algorithm

Ans. (b)

End of Solution

Q.110 Which one of the following functions is not correct for an operating system?

- (a) Allocating storage and memory
(b) Handling basic input and output operations
(c) Providing protected sharing of the computer among multiple applications
(d) Quick execution of instructions

Ans. (d)

Quick execution of instruction is NOT the functionality of operating system.

End of Solution

Q.111 Which of the following basic steps are needed in order to perform a memory read operation?

1. The address of the location from which the word is to be read is loaded into the memory address register (MAR).
2. A signal, called read (issued by the CPU indicating that the word whose address is in the MAR) is to be read into the MDR.
3. Corresponding to the memory delay in reading the specified word, the required word will be loaded by the memory into the MDR ready for use by the CPU.

Select the correct answer using the code given below.

- (a) 1 and 2 only (b) 2 and 3 only
(c) 1 and 3 only (d) 1, 2 and 3

Ans. (d)

The steps needed in order to perform a memory read operation is exactly as per the given statements in question.

1, 2, 3.

End of Solution

Q.112 Which one of the following addressing modes is used to compute the address of the operand by adding a constant value to the content of a register?

- (a) Immediate addressing (b) Indexed addressing
(c) Absolute addressing (d) Direct addressing

Ans. (b)

Indexed addressing mode is used to compute the address of operand by adding a constant value of the content of a register.

End of Solution

Q.113 Which of the following statements is/are correct for memory-mapped I/O?

1. The advantage of memory-mapped I/O is the ability to execute a number of memory-dedicated instructions on the registers in the I/O devices in addition to the elimination of the need for dedicated I/O instructions.
2. The disadvantage of memory-mapped I/O is the need to dedicate part of the memory address space for I/O devices.

Select the correct answer using the code given below.

- (a) 1 only (b) 2 only
(c) Neither 1 nor 2 (d) Both 1 and 2

Ans. (d)

The total memory space is shared between memory and I/O devices, so the actual memory space for instruction and data gets reduced. For memory-mapped I/O separate I/O instructions are not required.

End of Solution

Q.114 Which one of the following addressing modes is similar to the register indirect addressing mode in the sense that the effective address of the operand is the content of a register, which is included in the instruction?

- (a) Relative mode (b) Autoincrement mode
(c) Autodecrement mode (d) Immediate addressing mode

Ans. (a)

Relative addressing mode, ex: PC relative control transfer instructions.

End of Solution

Q.115 A floating-point (FP) number is said to be normalized, if the leftmost bit of the mantissa is

- (a) 1 (b) 0
(c) -1 (d) 2

Ans. (a)

A floating-point (FP) number is said to be normalized if the leftmost bit of the mantissa is 1.

End of Solution

Q.116 In order to keep track of the instruction locations, which one of the following contains the value of memory location assigned to the instruction or operand being processed?

- (a) LD (b) STA
(c) END (d) ILC

Ans. (d)

a, *b* and *c* are direct instructions.
ILC → Instruction location counter.

End of Solution

Q.117 Addition of two n -bit numbers A and B can be carried out using n consecutive full adders in an arrangement, which is known as

- (a) carry-ripple counter
(b) carry-ripple through adder
(c) carry-ripple through binary
(d) carry-ripple through subtractor

Ans. (b)

For the addition of two n -bit numbers A and B using n consecutive arrangement is known as carry-ripple through adder.

End of Solution

Q.118 Which of the following instructions are long and allow maximum parallelism since each bit controls a single control line?

- (a) Horizontal microinstructions (b) Vertical microinstructions
(c) Diagonal microinstructions (d) Jumbled microinstructions

Ans. (a)

In microprogrammed control unit, two types are possible:

1. Horizontal micro-instructions where every control signal has 1-bit, so more length of instruction decoded form of signals.
2. Vertical micro-instruction → encoded form of signals, so less instruction length low parallelism.

End of Solution

Q.119 Which one of the following tables is generated in pass one and has an entry for every symbol in the program to perform its function?

- | | |
|------------------------------|----------------------------------|
| (a) Symbol table | (b) Opcode table |
| (c) Pseudo-instruction table | (d) Addressing instruction table |

Ans. (a)

As assembler converts assembly language program to machine code which takes place in two steps.

1. First pass : generates symbol table.
2. Second pass: generates machine code.

End of Solution

Q.120 Which one of the following is the entity that can combine object modules that may have resulted from assembling multiple assembly modules separately?

- | | |
|--------------|-----------------|
| (a) Compiler | (b) Interpreter |
| (c) Linker | (d) Loader |

Ans. (c)

Combining all modules is done by linker.

End of Solution

Q.121 A unity feedback system has

$$G(s) = \frac{K(2s + 1)}{s(4s + 1)(s + 1)^2}$$

What is the value of K if the steady-state value of error is to be less than 0.1 when an input $r(t) = 1 + 5t$ is applied?

- | | |
|-------------------|------------------|
| (a) $K = 5$ | (b) $6 < K < 10$ |
| (c) $11 < K < 40$ | (d) $K > 50$ |

Ans. (d)

$$G(s) = \frac{K(2s + 1)}{s(4s + 1)(s + 1)^2}$$

As the system is Type-1, therefore steady state error is zero for step input,

For, $r(t) = 1 + 5t$

$$e_{ss} = \frac{5}{K_V}$$

$$\frac{5}{K_V} < 0.1$$

$$K_V > 50$$


$$K_V = \lim_{s \rightarrow 0} sG(s)$$

$$K_V = K$$

$$K > 50$$

End of Solution

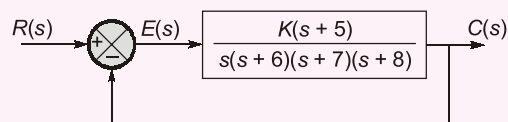Q.122 For the given control system, what is the value of K so that there is 10% error in the steady state?



(a) 172

(b) 272

(c) 572

(d) 672

Ans. (d)

$$e_{ss} = \frac{1}{K_V} = 0.1$$

$$G(s) = \frac{K(s+5)}{s(s+6)(s+7)(s+8)}$$

$$K_V = \lim_{s \rightarrow 0} sG(s)$$

$$K_V = \frac{5K}{6 \times 7 \times 8} = \frac{5K}{336}$$

$$\frac{1}{K_V} = 0.1$$

$$\frac{336}{5K} = 0.1$$

$$K = \frac{3360}{5} = 672$$

End of Solution

Q.123 In an underdamped second-order system the time required for the waveform to go from 0.1 of the final value to 0.9 of the final value is called

(a) rise time

(b) peak time

(c) settling time

(d) final time

Ans. (a)

End of Solution

Q.124 The open-loop transfer function of a unity feedback system is given by

$$G(s) = \frac{K}{s(\tau s + 1)}$$

By what factor should the amplifier gain K be multiplied so that the damping ratio is increased from 0.25 to 0.75?

- (a) 0.1111 (b) 1.1111
(c) 0.3333 (d) 3.3333

Ans. (a)

Damping ratio (ξ) is dependent on gain K as

$$\xi \propto \frac{1}{\sqrt{K}}$$

$$\frac{\xi_1}{\xi_2} = \sqrt{\frac{K_2}{K_1}}$$

$$\frac{0.25}{0.75} = \sqrt{\frac{K_2}{K_1}}$$

$$\frac{K_2}{K_1} = \left(\frac{1}{3}\right)^2$$

$$K_2 = (0.1111)K_1$$

End of Solution

Q.125 Consider the following statements regarding feedback compensation of control system:

1. A faster response can be achieved by the use of parallel compensation.
2. The environmental conditions in which the feedback control system is to be utilized affect the stability of the controlled quantity.
3. The degree of accuracy and the stability of a control system can be improved by the use of a cascade compensator.

Which of the above statements are correct?


- (a) 1 and 2 only (b) 1 and 3 only
(c) 2 and 3 only (d) 1, 2 and 3

Ans. (d)

End of Solution

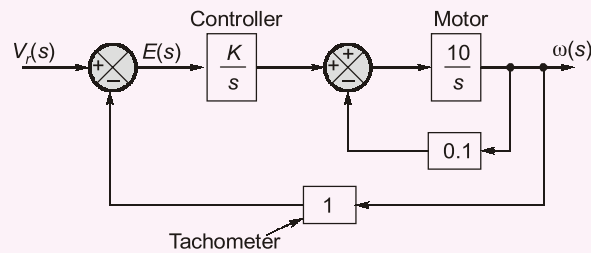Q.126 Consider the speed control system shown in the figure wherein the inner loop corresponds to motor back e.m.f, the controller is an integrator with gain K observes that the load is inertia only. What is the value of K for which steady-state error to unit ramp input

$\left(V_r(s) = \frac{1}{s^2} \right)$ is less than 0.01 rad/sec?



- (a) 5
(b) 7
(c) 10
(d) 14

Ans. (d)

Open loop transfer function, $GH(s) = \frac{10K}{s(s+1)}$

$$e_{ss} = \frac{1}{K_V}$$

$$K_V = \lim_{s \rightarrow 0} sG(s)$$

$$K_V = 10K$$

$$e_{ss} = \frac{1}{K_V} = \frac{1}{10K} < 0.01$$

$$K > 10$$

End of Solution

Q.127 The subsystem that generates the input to the plant or process is known as

- (a) controller
(b) controlled variable
(c) controllability
(d) compensator

Ans. (a)

End of Solution

Q.128 Consider the following statements regarding compensator :

1. The lead compensator reduces the noise signal level relative to the control signal.
2. Introduction of cascade lead compensator increases the gain crossover frequency and, consequently, the speed of the response of resulting system.
3. The lead compensation increases the system bandwidth.

Which of the above statements are correct?

- (a) 1 and 2 only
(b) 1 and 3 only
(c) 2 and 3 only
(d) 1, 2 and 3

Ans. (c)

End of Solution

- Q.129** Which of the following is/are used, when the cascade compensator does not employ pure integration?
- (a) Lead compensator only (b) Lag compensator only
(c) Neither lead nor lag compensator (d) Both lead and lag compensator

Ans. (b)

End of Solution

- Q.130** Consider the following statements regarding signals:
1. Deterministic signal is a signal about which there is no uncertainty with respect to its value at any time.
 2. Each signal within the ensemble has a certain probability of occurrence and the ensemble of signals is referred to as a random process.
 3. EEG signal is an example of random signal.

Which of the above statements are correct?

- (a) 1 and 2 only (b) 1 and 3 only
(c) 2 and 3 only (d) 1, 2 and 3

Ans. (d)

End of Solution

- Q.131** Which one of the following techniques can be used to analyze and design the effect of loop gain upon the system's transient response and stability?
- (a) Open-loop transfer function technique.
(b) Closed-loop transfer function technique.
(c) Root locus technique
(d) Compensation technique

Ans. (c)

In root locus technique open loop gain K is varied and based upon that system characteristics are studied.

End of Solution

- Q.132** Consider the following statements regarding time response specifications :
1. Delay time is the time required for the response to reach 10% to 90% or 5% to 95% or 0% to 100% of its final value.
 2. Peak time is the time required for the response to reach the first peak overshoot.
 3. Settling time is the time required for the response to reach and maintain beyond a specified tolerance band, i.e., either 3% or 5% of the initial value.

Which of the above statements are **not** correct?

- (a) 1 and 2 only (b) 1 and 3 only
(c) 2 and 3 only (d) 1, 2 and 3

Ans. (b)

Delay time is the time required for the response to reach 50% of its final value.
Settling time is the time required for the response to reach upto 3% or 5% of the final value.

End of Solution

- Q.133** Which one of the following fibers has the distinct advantage of low intermodal dispersion?
 (a) Multimode step-index fiber (b) Single-mode step-index fiber
 (c) Graded-index multimode fiber (d) Spatially incoherent multimode fiber

Ans. (b)

Single-mode step-index fiber has low inter-modal dispersion.

End of Solution

- Q.134** Which one of the following statements is **not** correct?
 (a) The noise performance of a full AM receiver is always inferior to that of a DSB-SC receiver.
 (b) The figure of merit of a DSB-SC receiver using coherent detection is always unity.
 (c) The figure of merit of an SSB receiver using coherent detection is always unity.
 (d) The figure of merit of an AM receiver using envelope detection is always greater than unity.

Ans. (d)

$$(FOM)_{AM} = \frac{\mu^2}{2 + \mu^2} ; \mu = 1$$

$$(FOM)_{AM} = \frac{1}{3}$$

$$(FOM)_{DSB-SC} = 1$$

$$(FOM)_{SSC-SC} = 1$$

End of Solution

- Q.135** The RF carrier range and IF bandwidth corresponding to AM radio receiver are respectively
 (a) 0.535 MHz-1.605 MHz and 100 kHz
 (b) 53.5 MHz-160.5 MHz and 10 kHz
 (c) 0.535 MHz-1.605 MHz and 10 kHz
 (d) 53.5 MHz-160.5 MHz and 100 kHz

Ans. (c)

AM radio-FCC

$$\begin{aligned} & 535 \text{ kHz} - 1605 \text{ kHz} \\ \text{Signal bandwidth} &= 10 \text{ kHz} \end{aligned}$$

End of Solution

- Q.136** For the same average transmitted or modulated signal power and the same average noise power in the message bandwidth, a coherent SSB receiver will have exactly the same output signal-to-noise ratio as
 (a) a coherent DSB-SC receiver (b) an AM receiver
 (c) a VSB receiver (d) an SSB receiver

Ans. (a, d)

End of Solution

- Q.137** Over a certain binary communication channel, the symbol 0 is transmitted with probability 0.4 and 1 is transmitted with probability 0.6. It is given that $p(\epsilon/0) = 10^{-6}$ and $p(\epsilon/1) = 10^{-4}$, where $p(\epsilon/x_i)$ is the probability of detecting the error given that x_i is transmitted. What is the error probability of the channel?
- (a) 0.604×10^{-3} (b) 0.604×10^{-5}
(c) 0.604×10^{-6} (d) 0.604×10^{-4}

Ans. (d)

Given: $P(0) = 0.4$; $P(1) = 0.6$; $P(\epsilon/0) = 10^{-6}$; $P(\epsilon/1) = 10^{-4}$

$$P(e) = P(0) P(\epsilon/0) + P(1) P(\epsilon/1)$$

$$= 0.4 \times 10^{-6} + 0.6 \times 10^{-4}$$

Probability of error, $P(e) = 0.604 \times 10^{-4}$

End of Solution

- Q.138** Which one of the following noises arises in electronic devices such as diodes and transistors because of the discrete nature of current flow?
- (a) Shot noise (b) Thermal noise
(c) Gaussian noise (d) Random noise

Ans. (a)

End of Solution

- Q.139** Which one of the following represents the output signal-to-noise ratio of a uniform quantizer? (where P denotes average power of the message signal $m(t)$ and R denotes number of bits per sample)

(a) $\left(\frac{3P}{m_{\max}^2}\right) 2^{2R}$

(b) $\left(\frac{2P}{m_{\max}^3}\right) 2^{3R}$

(c) $\left(\frac{3P}{m_{\max}^2}\right) 2^R$

(d) $\left(\frac{3P}{m_{\max}^2}\right)$

Ans. (a)

$$\text{SNR} = \frac{\text{Signal power}}{\text{Noise power}} = \frac{P}{(\Delta^2/12)}$$

$$= \frac{P \times 12}{\Delta^2} = \frac{P \times 12}{\left(\frac{2m_{\max}}{L}\right)^2} = \frac{P \times 12}{4 \times m_{\max}^2} \times L^2$$

and $L = 2^R$

where, $R \rightarrow$ Number of bits per sample

$$\therefore \text{SNR} = \frac{P \times 12}{4 \times m_{\max}^2} \times 2^{2R}$$

$$\text{SNR} = \left(\frac{3P}{m_{\text{max}}^2} \right) 2^{2R}$$

Hence, option (a) is correct answer.


End of Solution

- Q.140** Removing the redundant information before encoding is the basic idea behind
- (a) quantization
 - (b) delta modulation
 - (c) pulse-code modulation
 - (d) differential pulse-code modulation

Ans. (d)

End of Solution

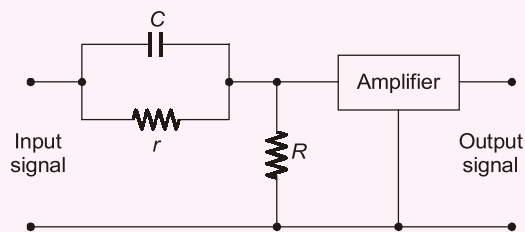- Q.141** Identify the given circuit shown in the figure.



- (a) Band-pass filter
- (b) De-emphasis filter
- (c) Pre-emphasis filter
- (d) Band-reject filter

Ans. (c)

End of Solution

- Q.142** In which one of the following techniques, RF binary signals are transmitted as given?

$$0: \sqrt{2}p'(t)\cos[\omega_c - (\Delta\omega/2)t]$$

$$1: \sqrt{2}p'(t)\cos[\omega_c + (\Delta\omega/2)t]$$

- (a) ASK
- (b) FSK
- (c) PSK
- (d) MPSK

Ans. (b)

Here, frequency is changing for binary bits 0 and 1. Hence, it is FSK technique. Hence, option (b) is correct.

End of Solution

- Q.143** Which one of the following statements is **not** correct regarding the features of CDMA?
- (a) Multipath fading may be substantially increased because the signal is spread over a large spectrum.
 - (b) Channel data rates are very high in CDMA systems.
 - (c) The near-far problem occurs at a CDMA receiver if an undesired user has a high detected power as compared to the desired user.
 - (d) Many users of a CDMA system share the same frequency.

Ans. (a)

End of Solution

Q.144 How many 6 MHz wide TV channels can be multiplexed on 800 MHz coaxial cable?

- (a) 96 (b) 266
(c) 133 (d) 48

Ans. (c)

$$\text{Number of stations} = \frac{\text{Channel BW}}{\text{Signal BW}} = \frac{800 \text{ MHz}}{6 \text{ MHz}} = 133$$

End of Solution

Directions : Each of the next six (6) items consists of two statements, one labelled as the 'Statement (I)' and the other labelled as 'Statement (II)'. You are to examine these two statements carefully and select the answers to these items using the codes given below :

Codes :

- (a) Both Statement (I) and Statement (II) is the correct explanation of Statement (I).
(b) Both Statement (I) and Statement (II) are individually true, but Statement (II) is not the correct explanation of Statement (I).
(c) Statement (I) is true, but Statement (II) is false.
(d) Statement (I) is false, but Statement (II) is true.

Q.145 **Statement (I)** : The magnetization curve is the relationship between air gap flux and the field winding m.m.f. or field winding current.

Statement (II) : No-load magnetization curve is the graph between armature-generated e.m.f. and field current with constant armature speed.

Ans. (b)

End of Solution

Q.146 **Statement (I)** : Some of the common and familiar polymers are polyethylene (PE), nylon, polyvinyl chloride (PVC), polycarbonate (PC), polystyrene (PS) and silicone rubber.

Statement (II) : Polymers include the familiar plastic and rubber materials.

Ans. (b)

End of Solution

Q.147 **Statement (I)** : Voltage (or potential difference) is the energy required to move a unit charge through an element.

Statement (II) : Power is the time rate of expending or absorbing energy.

Ans. (b)

Both statements are correct but statement-II is not the correct explanation of statement-I.

1. $V = \frac{W}{Q}$.

2. $P = \frac{dW}{dt}$.

End of Solution

Q.148 Statement (I) : A transfer function is a function which relates the current or voltage at one port to the current or voltage at another port.

Statement (II) : If the function has one or more poles in the right-half plane, then the function is non-minimum phase.

Ans. (b)

End of Solution

Q.149 Statement (I) : Antenna is a transformation device converting electromagnetic photons into circuit currents.

Statement (II) : An antenna converts photons to currents or vice versa.

Ans. (c)

End of Solution

Q.150 Statement (I) : Shannon has shown that it is possible to achieve error-free communication by adding sufficient redundancy.

Statement (II) : The addition of an extra check digit increases redundancy.

Ans. (a)

End of Solution

